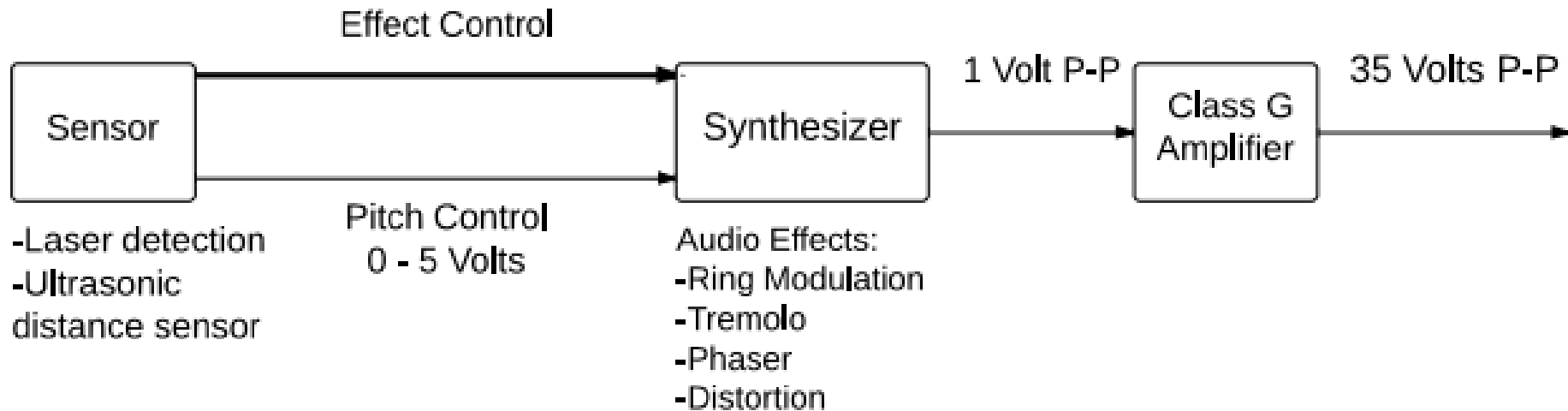


# Laser Harp




JORDAN ADDISON  
MATTHEW OKABUE  
CHAD UYEHARA


# Block Diagram



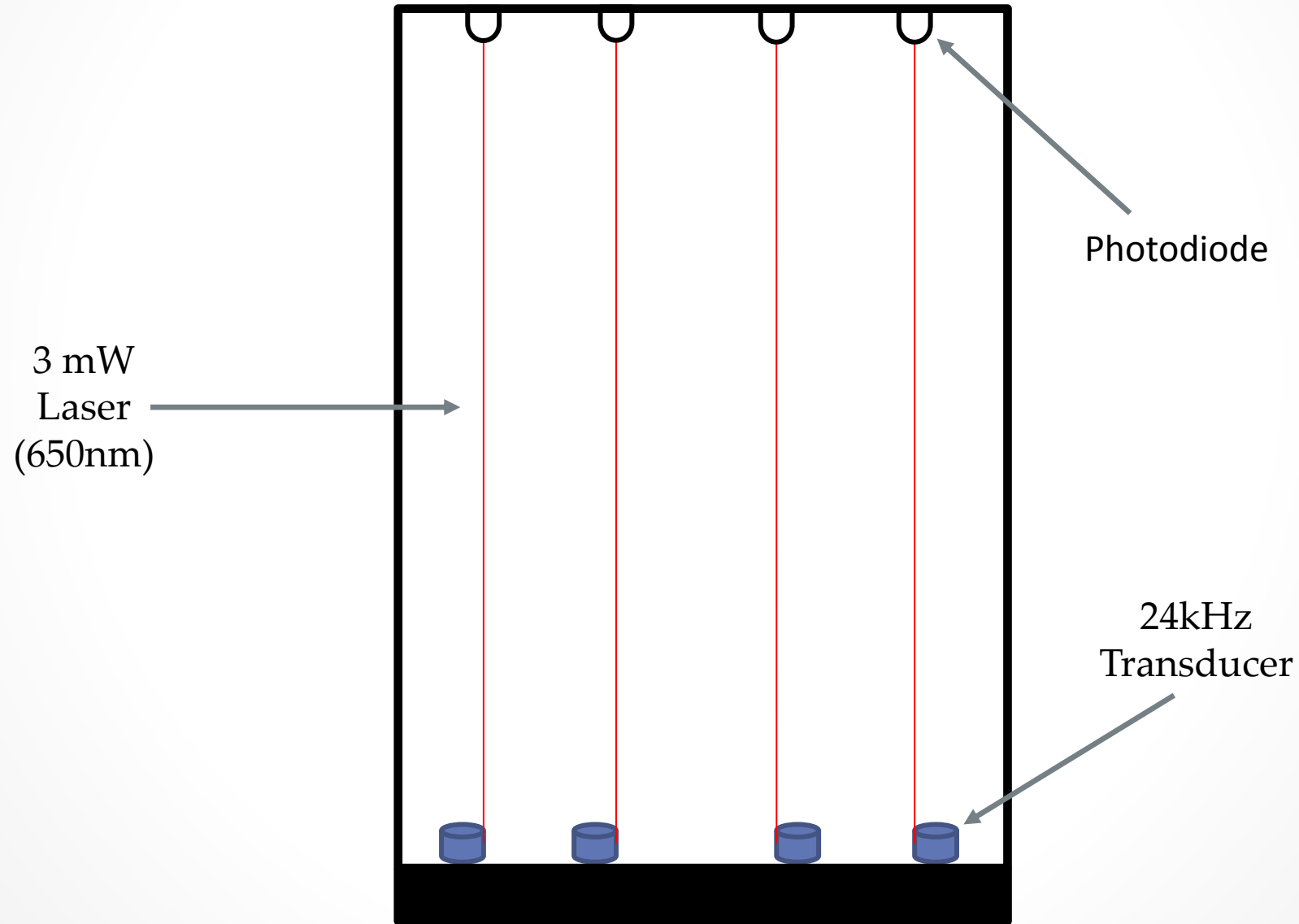
# Laser Harp Diagram (Artistic Rendition)



# Laser Detection Schematic

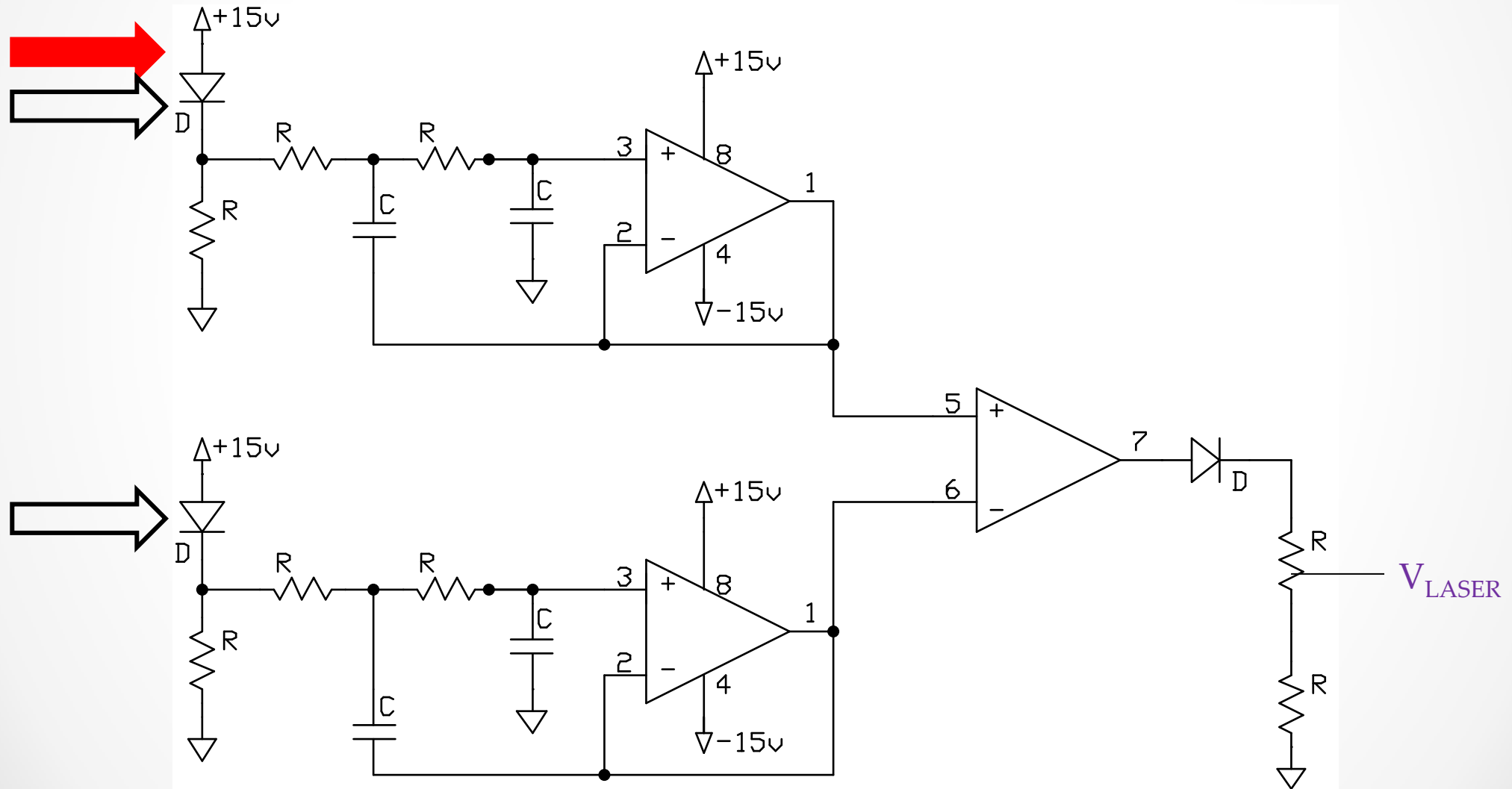

# Range Finder Block Diagram

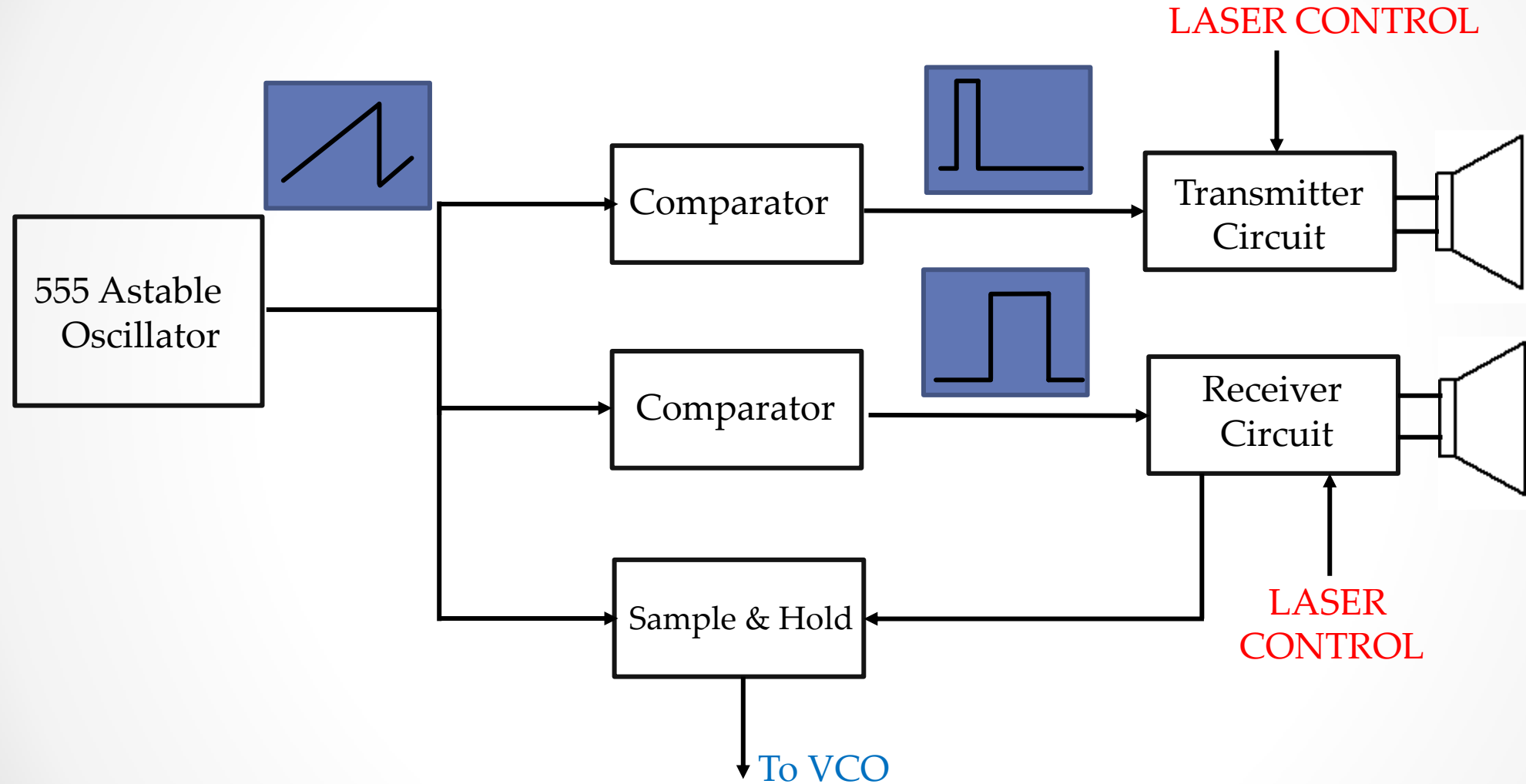


# Transmitter/Receiver Waveforms




Courtesy [kerrywong.com](http://kerrywong.com)


# Transmitter Schematic

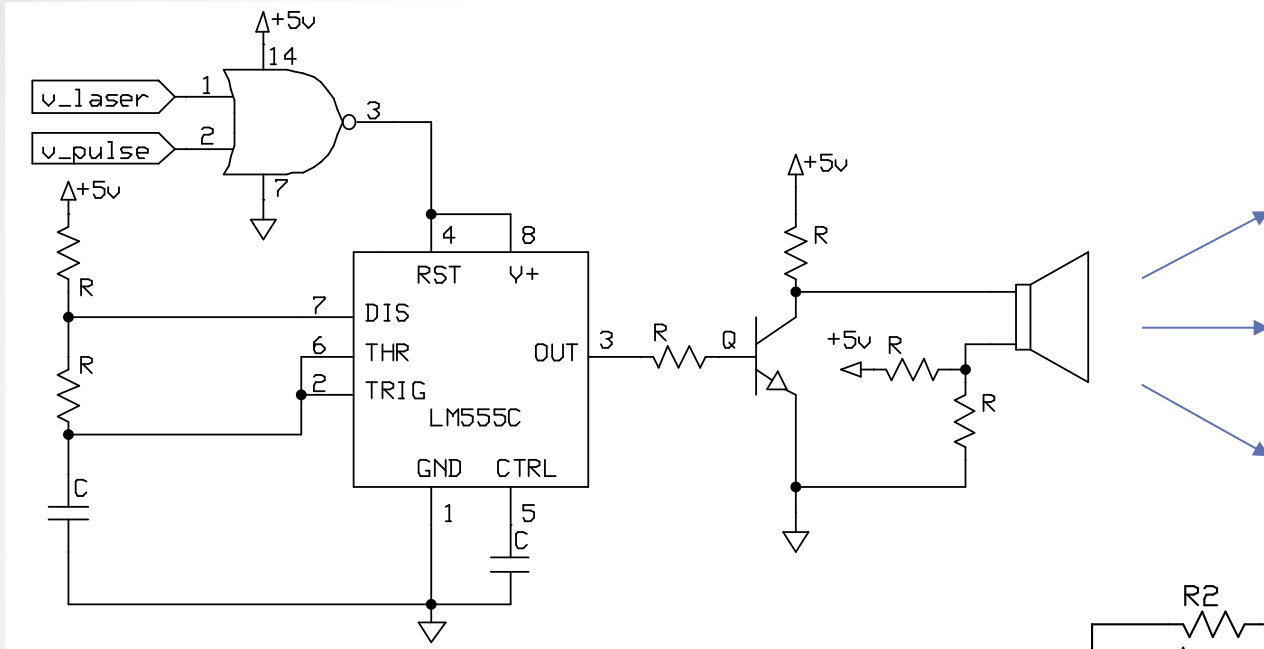


# Receiver Circuit

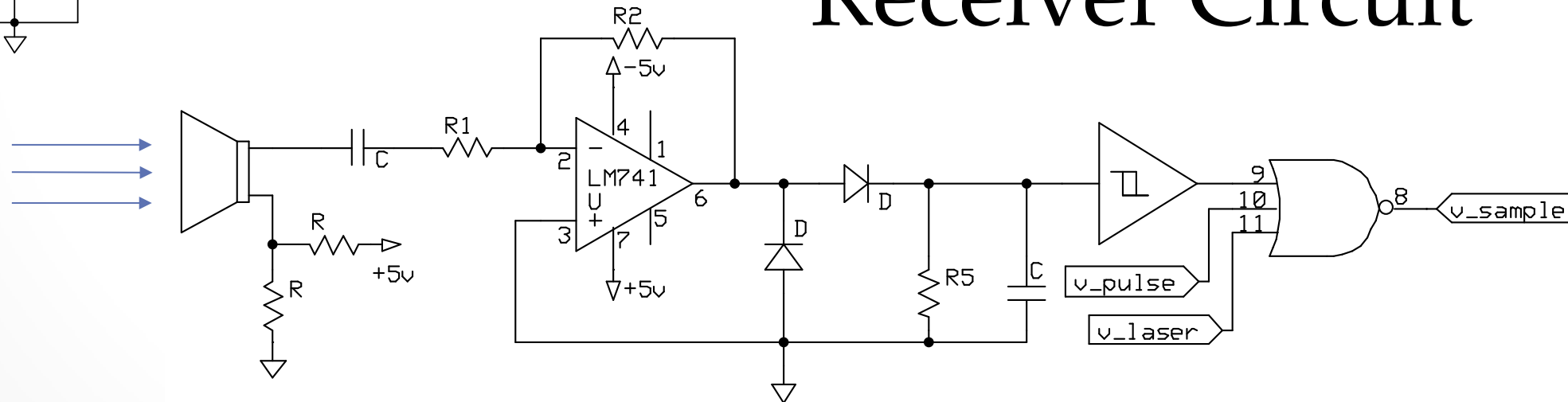


# Synthesizer

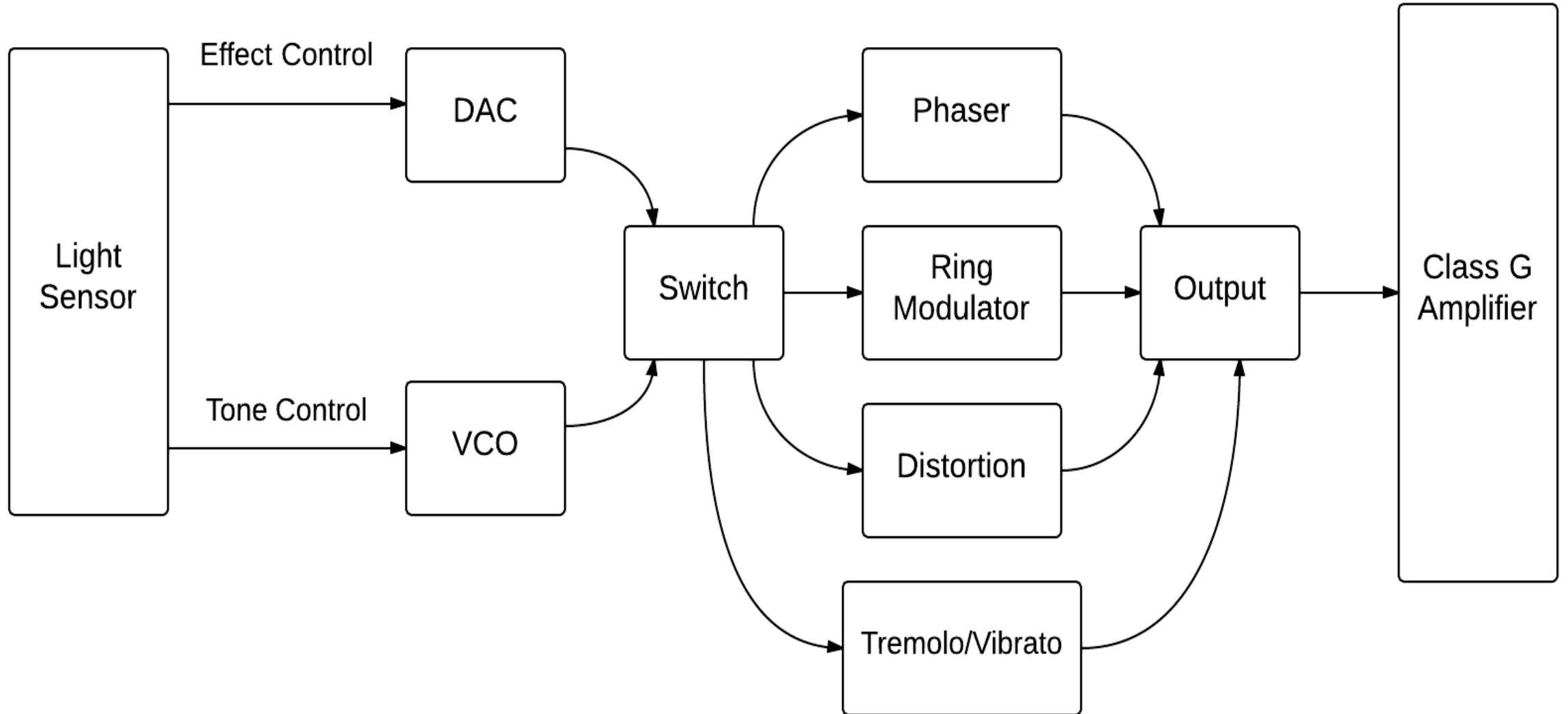


# Voltage Controlled Oscillator (VCO)

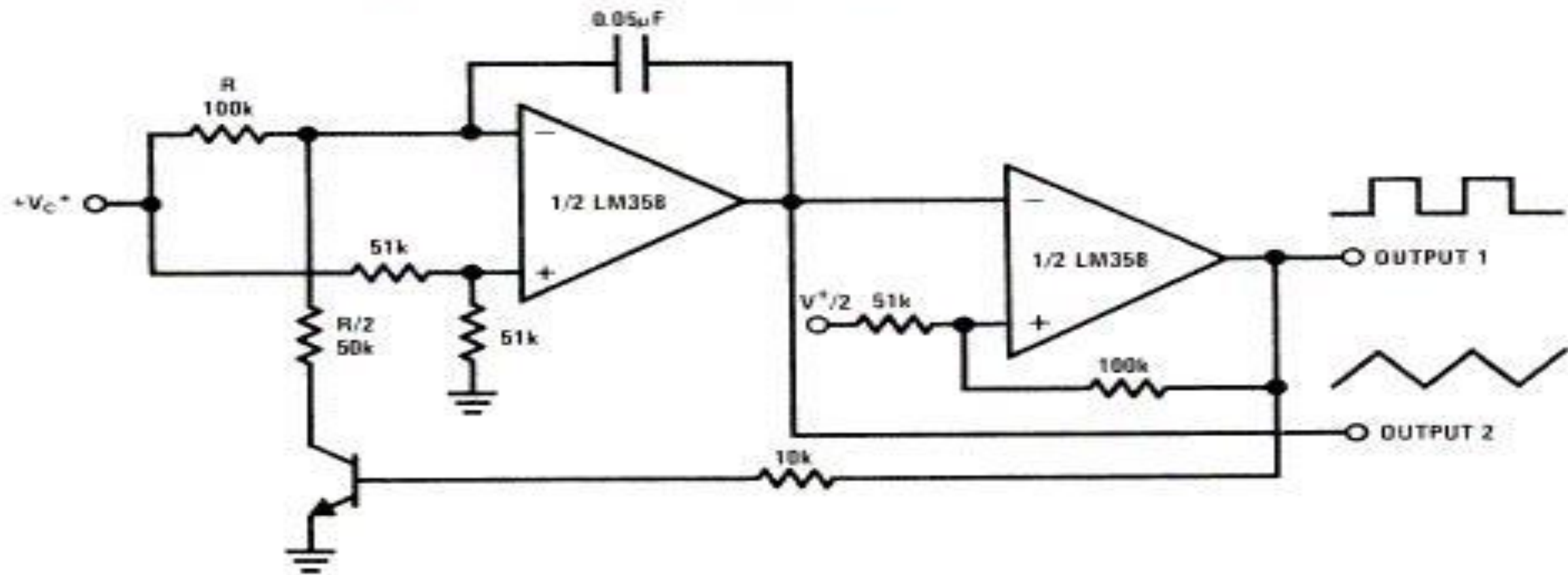

# Phaser

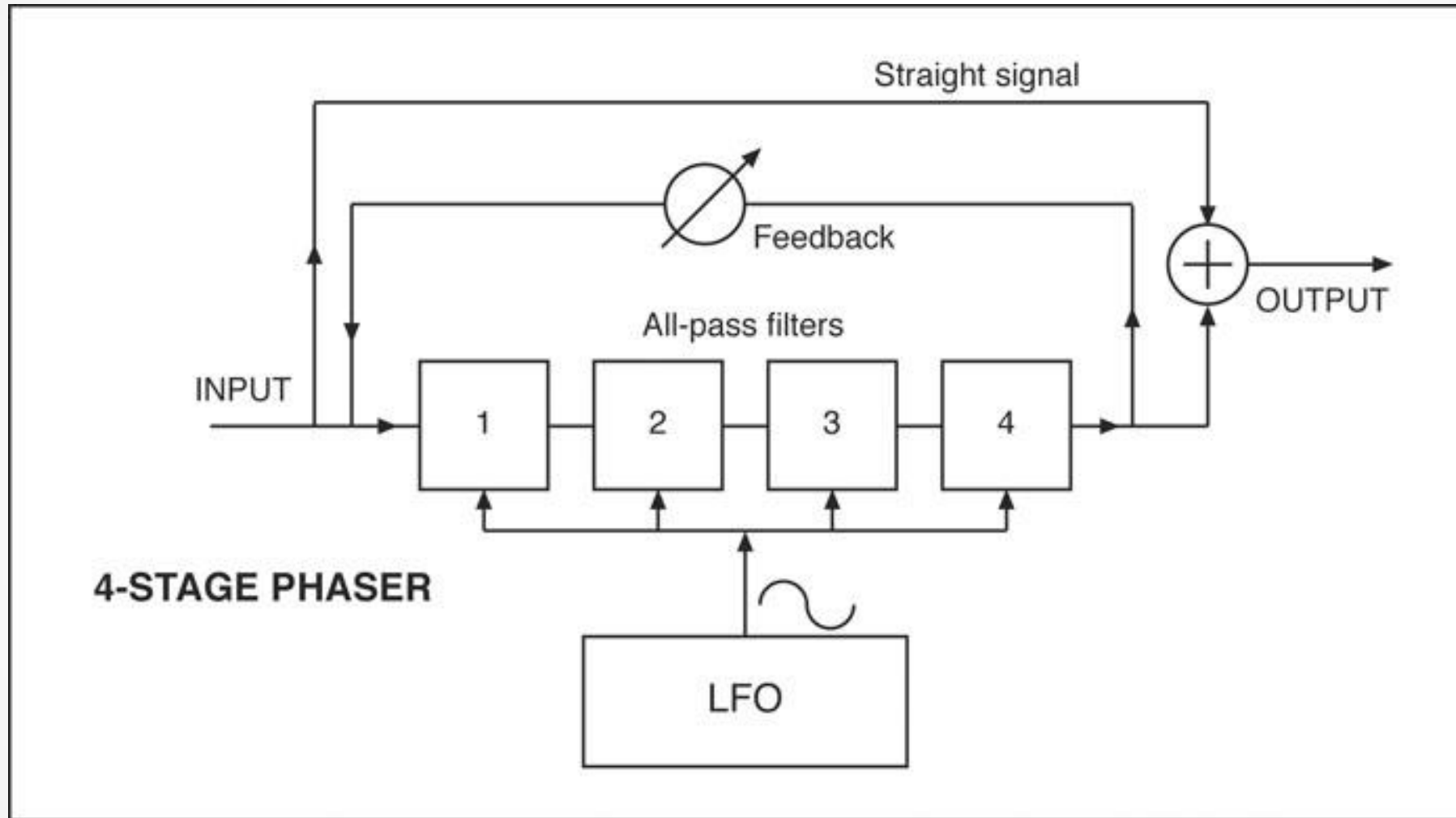


# Ring Modulator

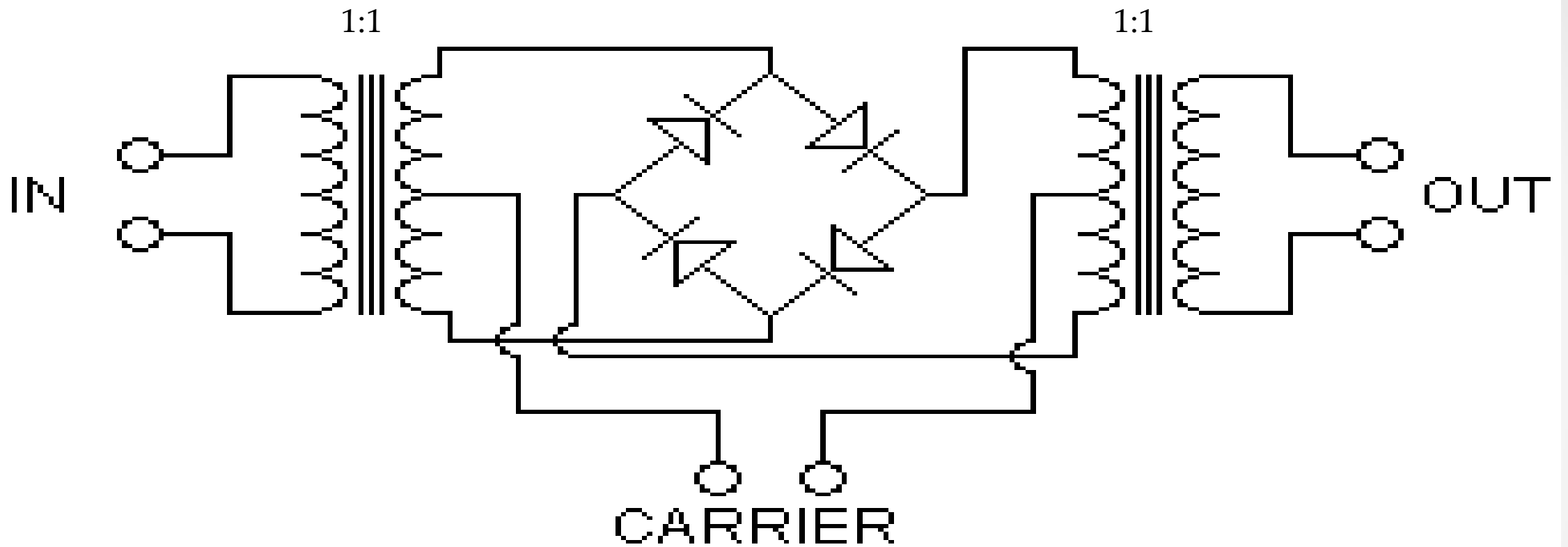


# Vibrato/Tremolo


Low Frequency Oscillator

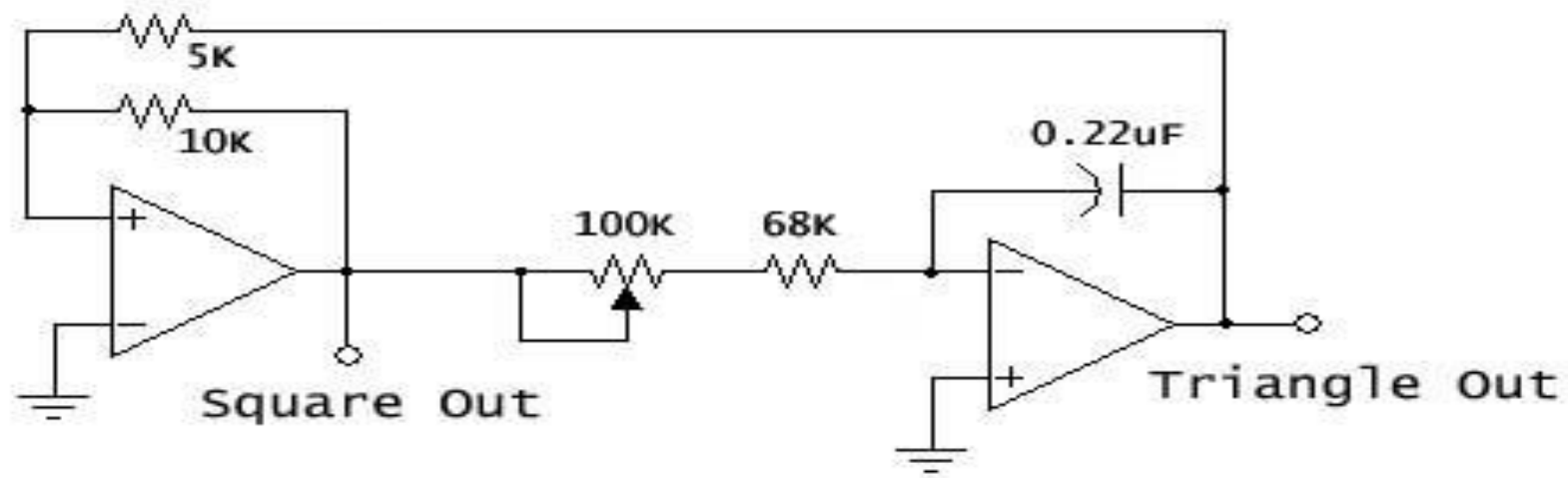

# Distortion

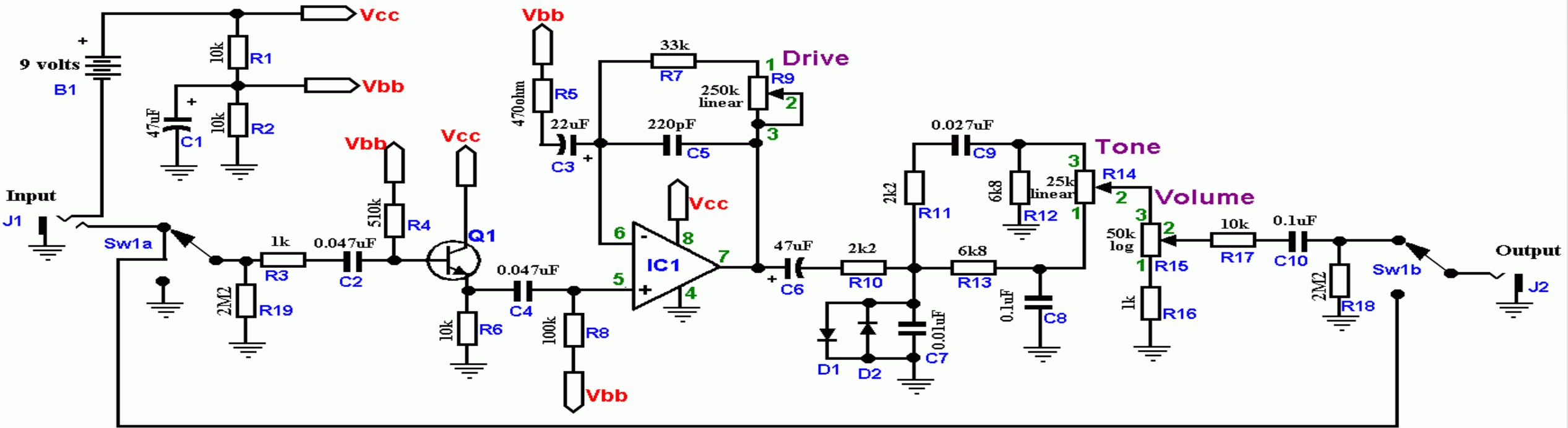


# Class G Amplifier

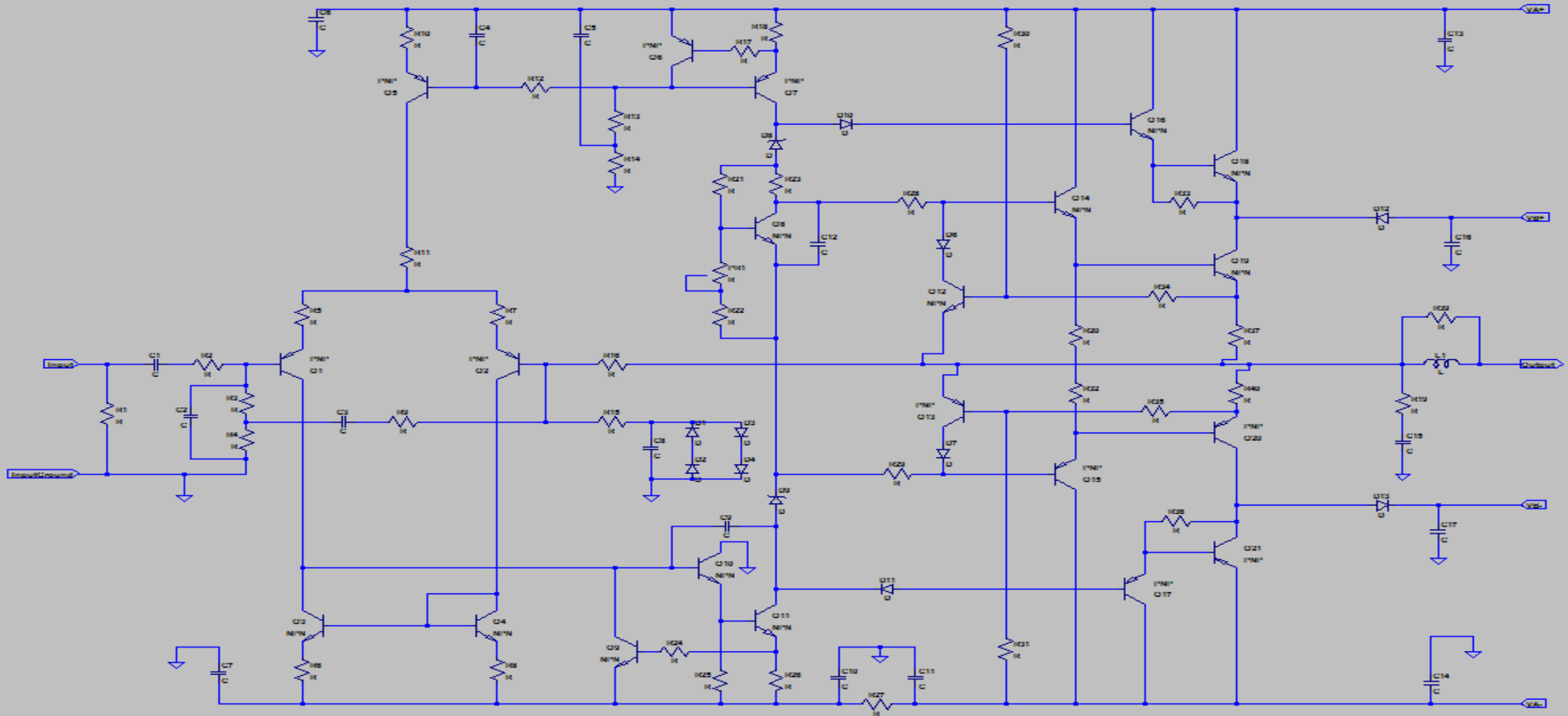


(Design from "Audio Power Amplifier Design Handbook" By Douglas Self)

# Input Stage

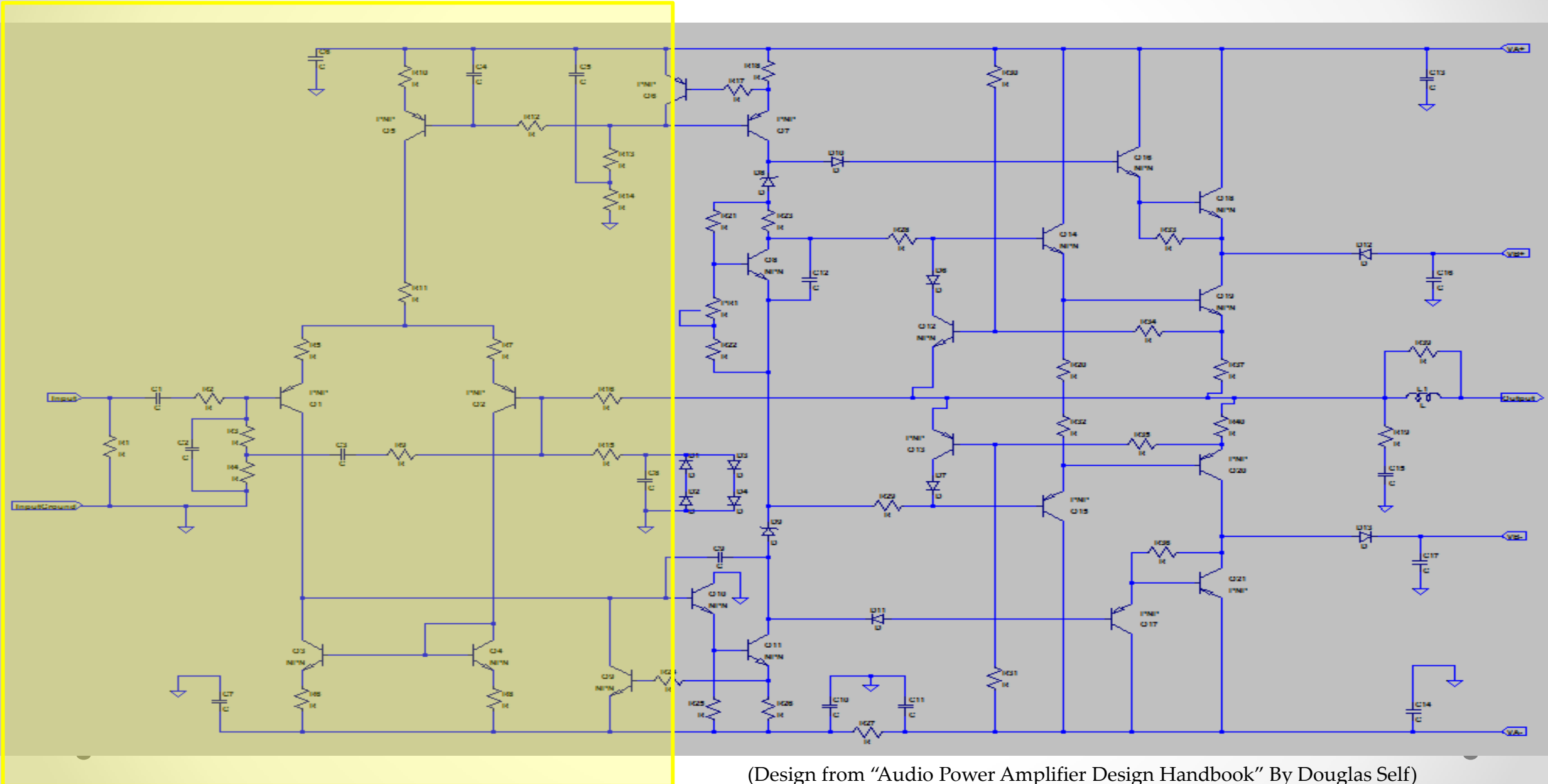


(Design from "Audio Power Amplifier Design Handbook" By Douglas Self)

# Voltage Amplification Stage

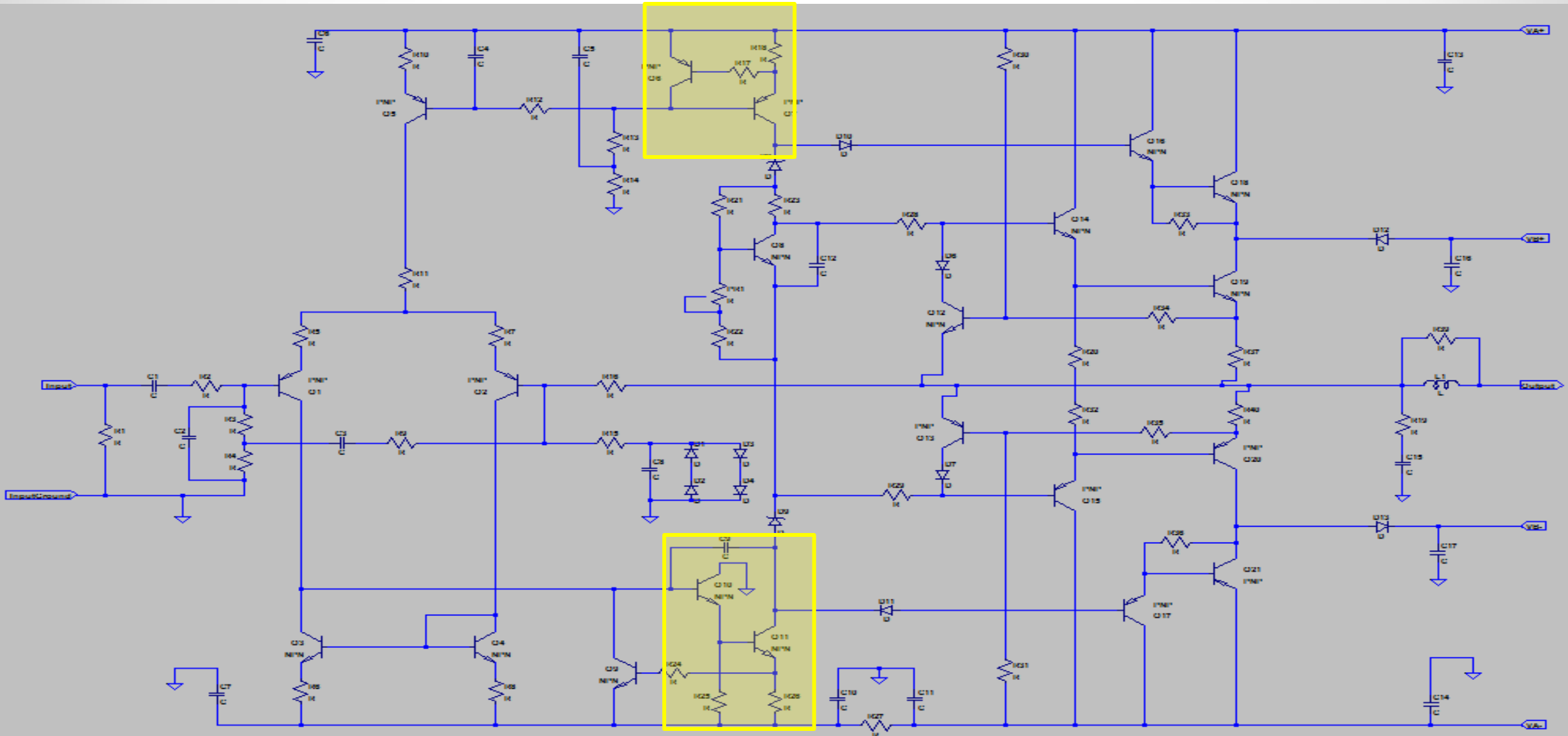


(Design from "Audio Power Amplifier Design Handbook" By Douglas Self)

# Bias Servo

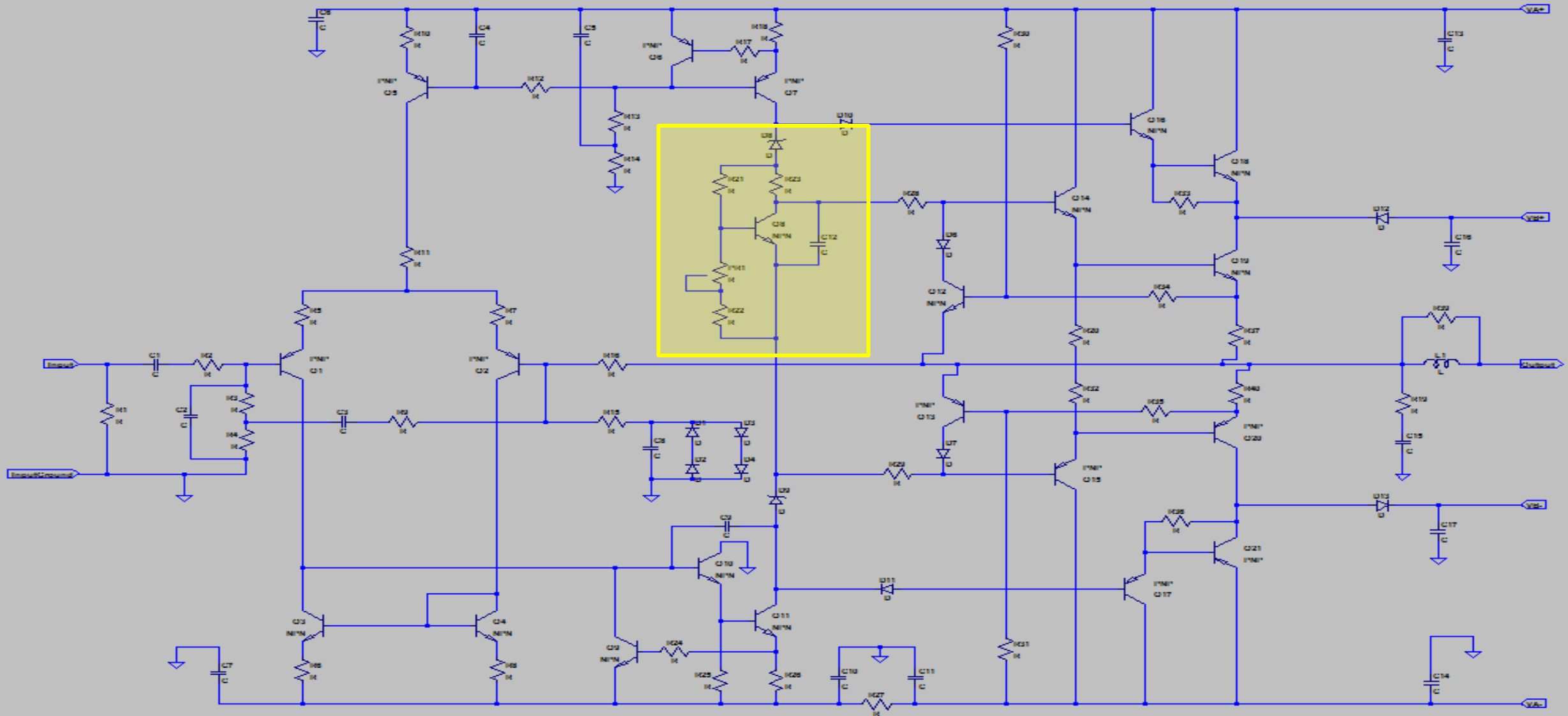


(Design from "Audio Power Amplifier Design Handbook" By Douglas Self)

# Output Stage

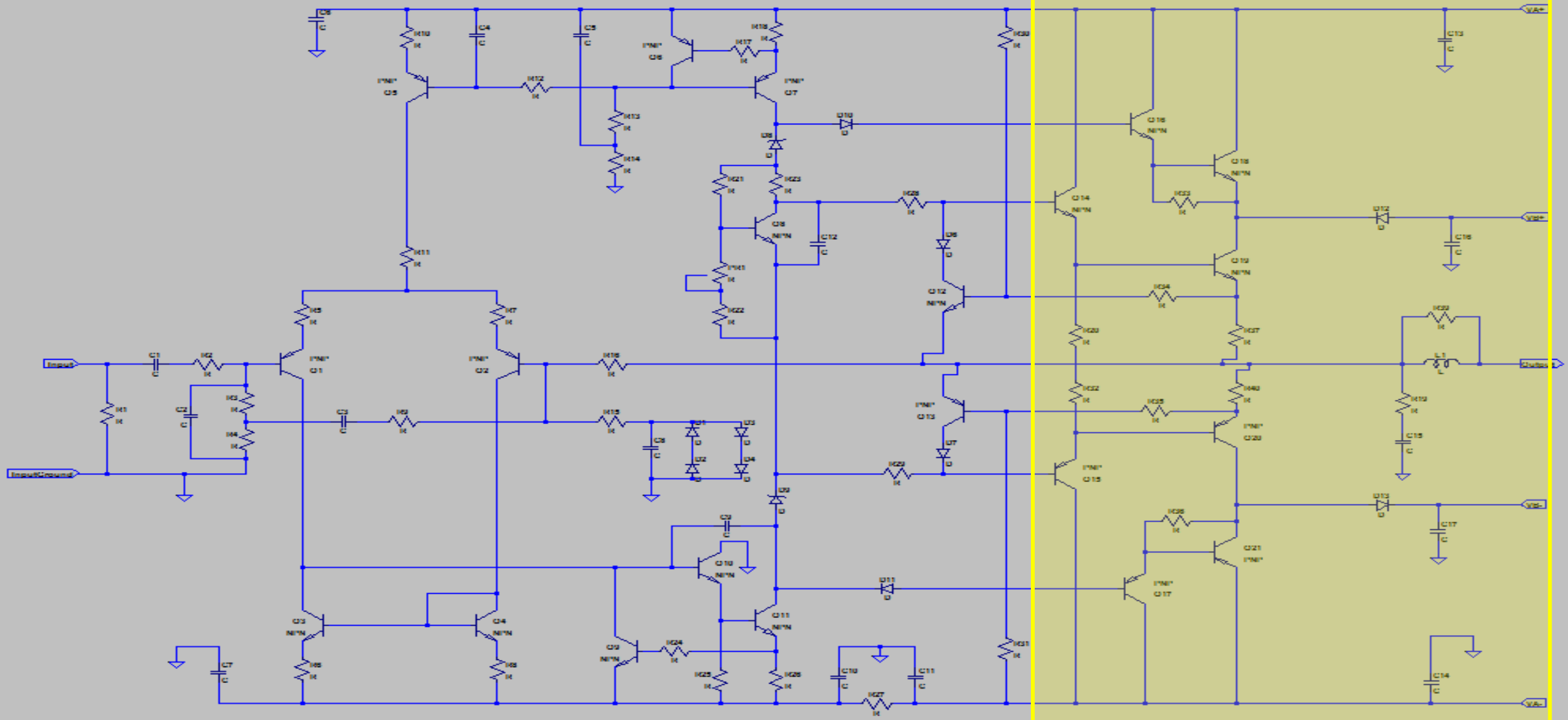


(Design from "Audio Power Amplifier Design Handbook" By Douglas Self)

# Overload Protection

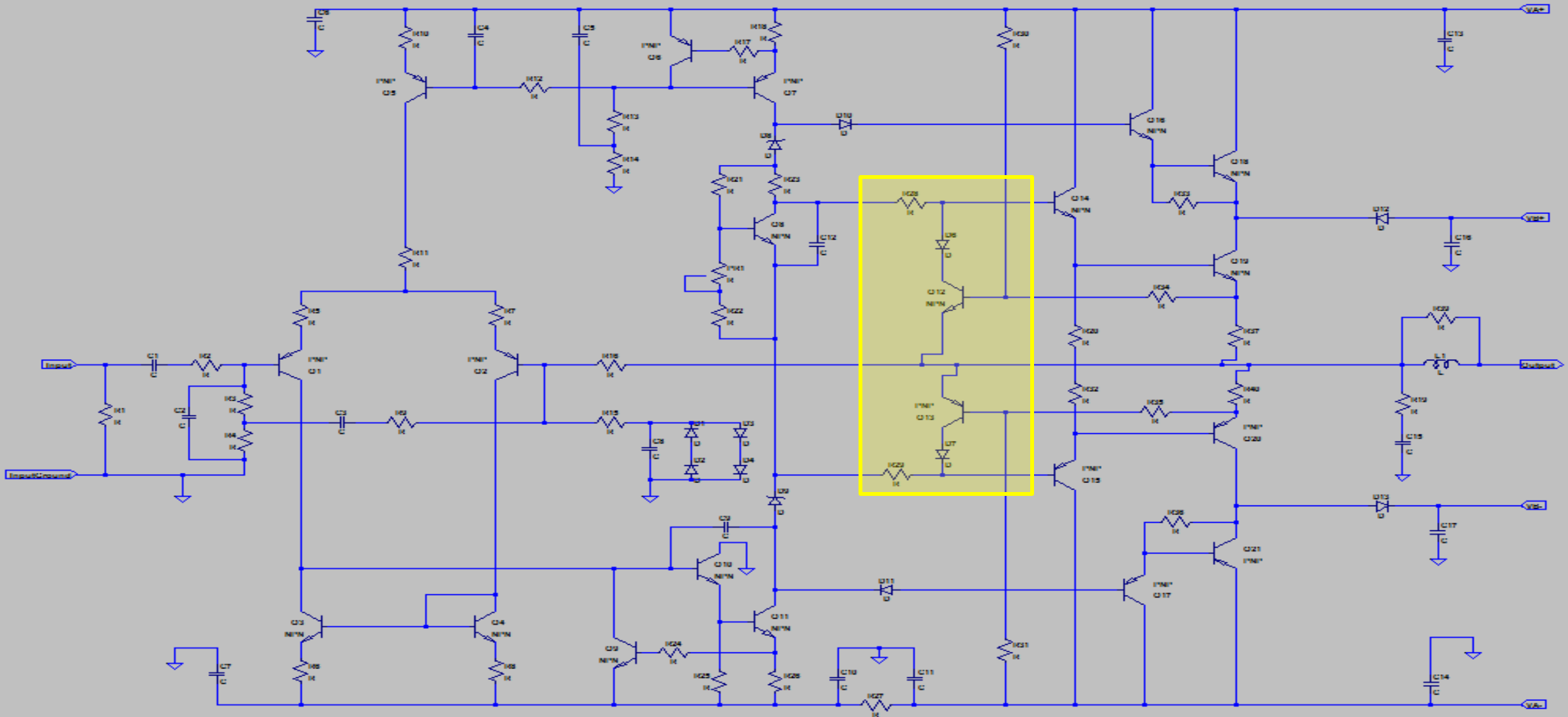


(Design from "Audio Power Amplifier Design Handbook" By Douglas Self)

# Protection Diodes

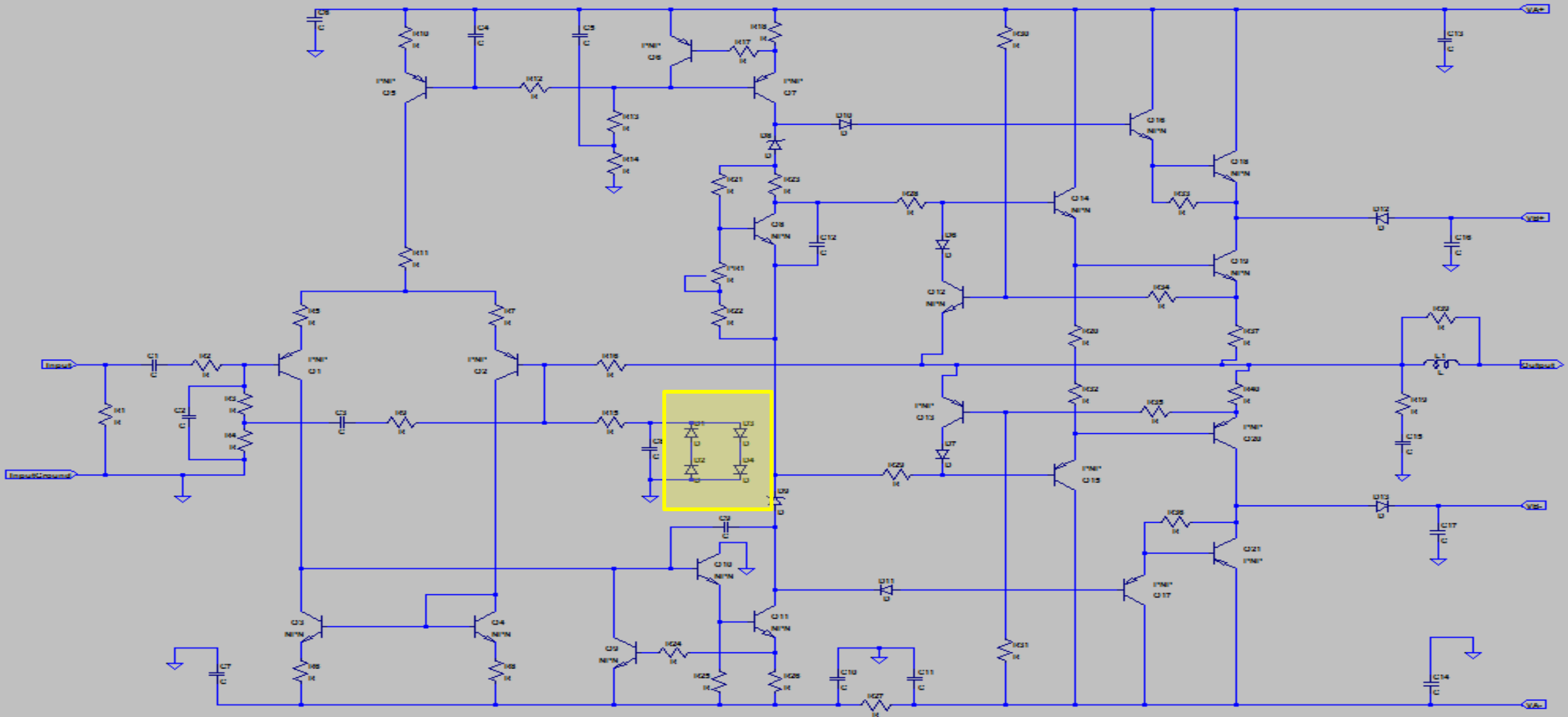

(Design from "Audio Power Amplifier Design Handbook" By Douglas Self)

# Ripple Prevention

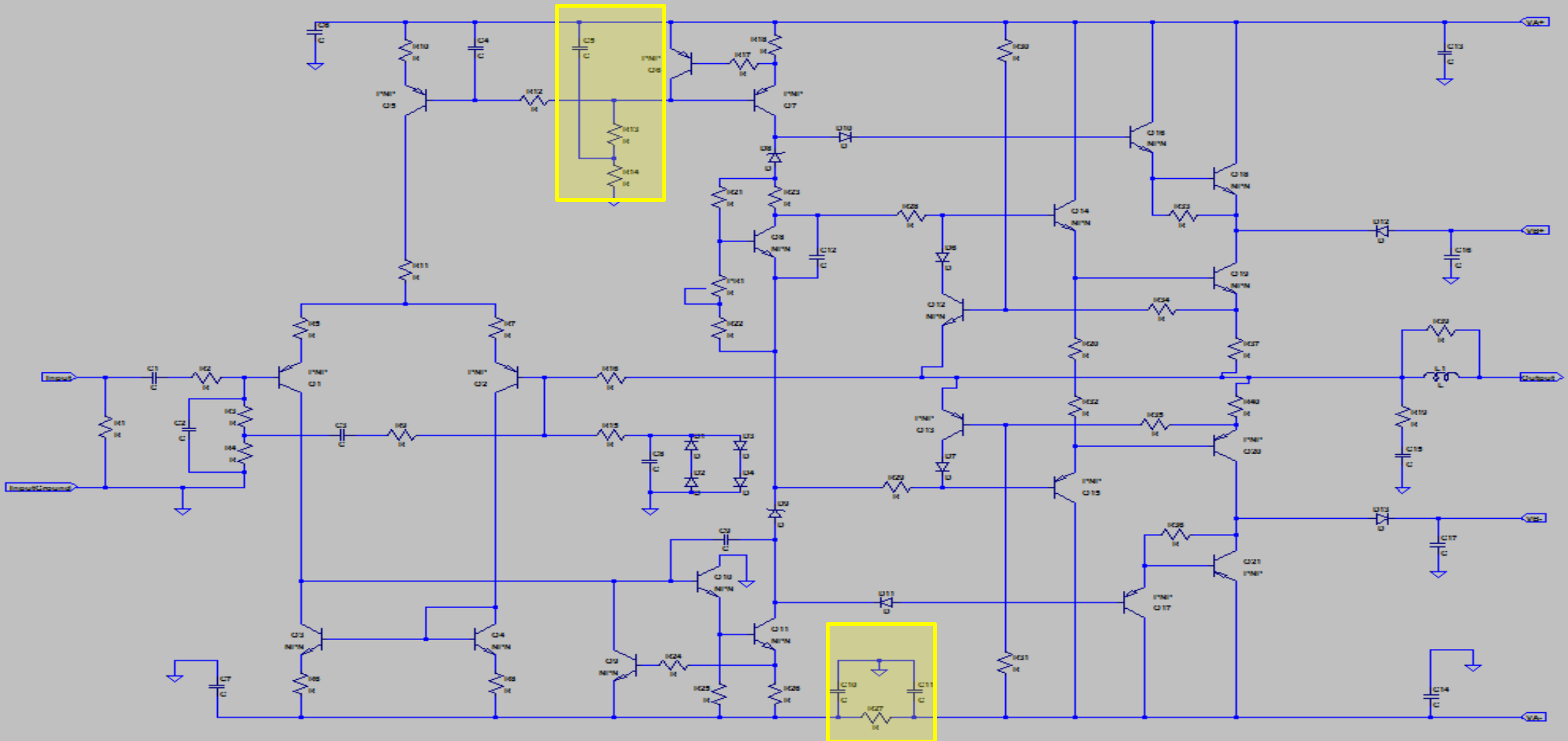

(Design from "Audio Power Amplifier Design Handbook" By Douglas Self)

# Timeline

- Week of 4/13: Schematics and Final Design
- Week of 4/20: Breadboarding and Testing Individual Modules
  - PCB Layout and Ordering
- Week of 4/27: Integration of Modules and Testing
- Week of 5/4: Presentation of Final Product

# Questions?