

Low Noise Portable Electroencephalogram (EEG)

Nick Arango

Why an EEG

- Neat Applications
 - sleep analysis
 - medical diagnosis
 - computer human interface
- Hard to measure
 - 1-100 μ V signals from .1 to 40 Hz
 - very high source impedance

Medical EEG



Medical EEG



Commercial EEG




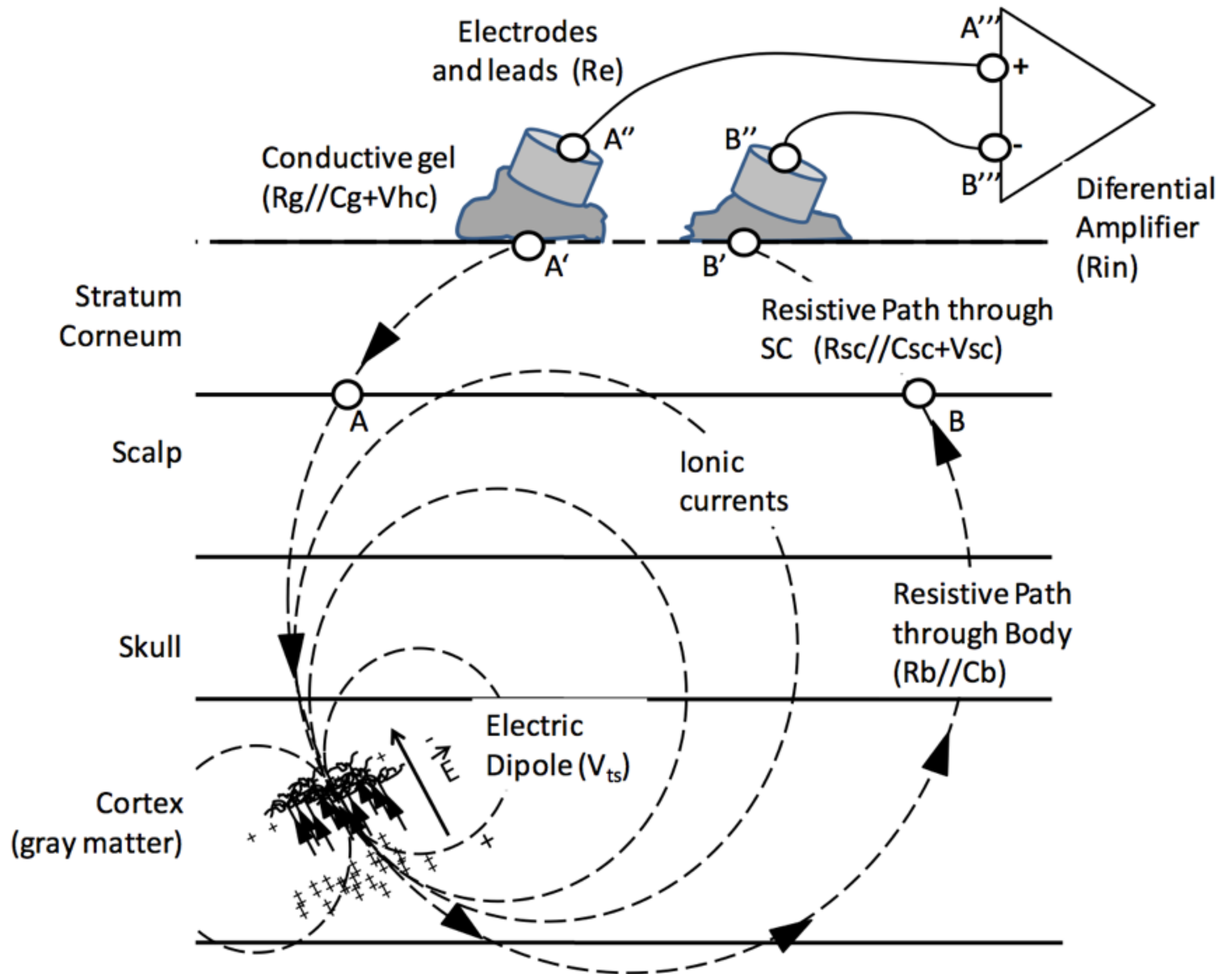


Figure from Dry EEG Electrodes M. A. Lopez-Gordo, D. Sanchez-Morillo, and F. Pelayo Valle


Design Goals

- Battery operated
- Reusable, dry electrodes
- 40dB signal to noise ratio
- Drive a computer

System Overview

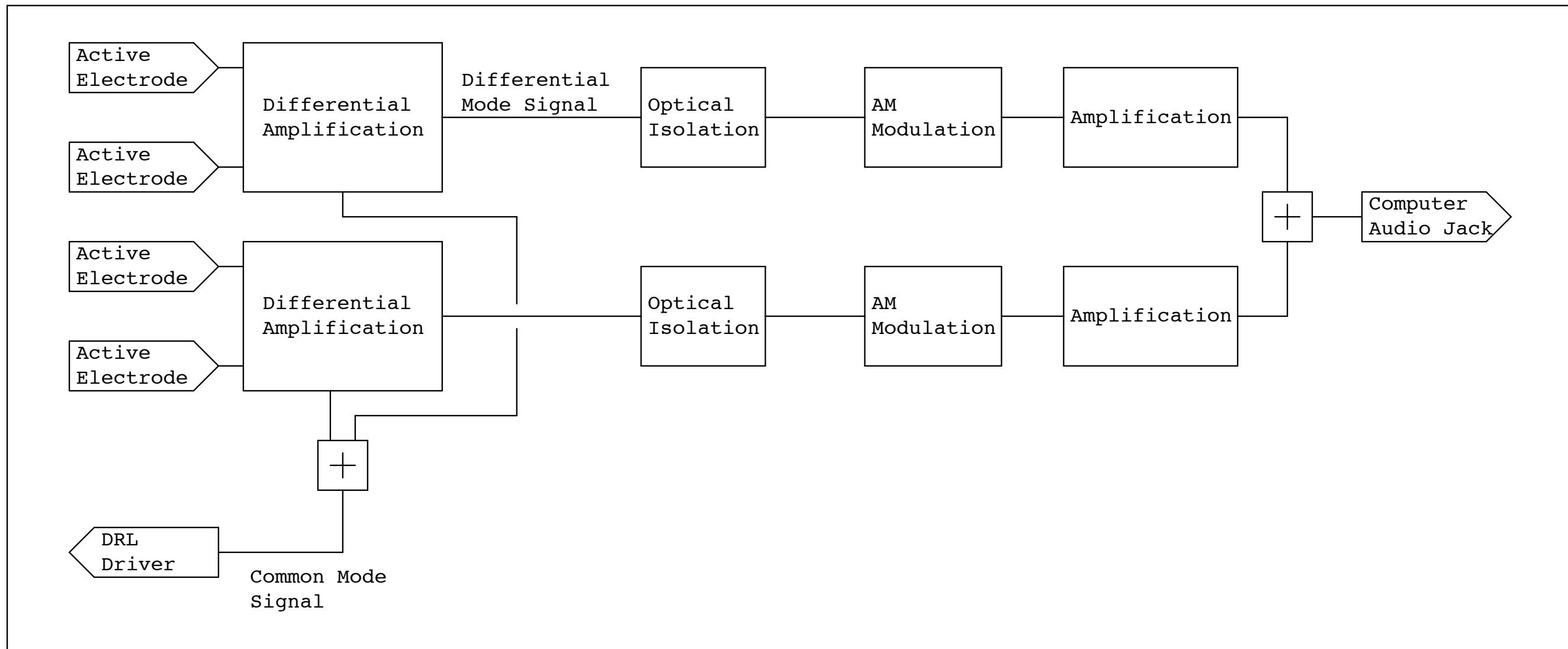


Front End Design

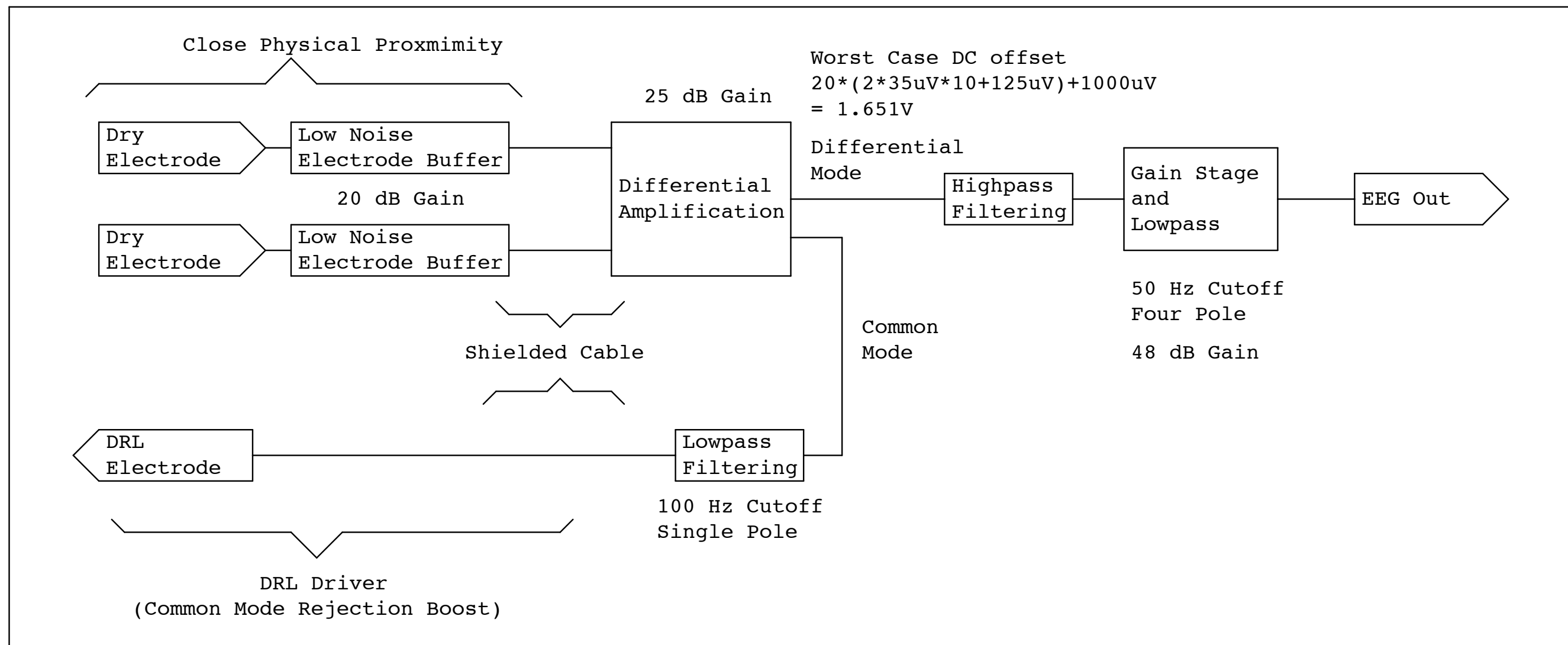


Noise Considerations

- Amplifiers must be carefully selected to minimize low frequency noise
- $1/f$ noise dominates the .1 - 40 Hz range (EEG signal range)
- both voltage and current noise must be considered

opamp noise model

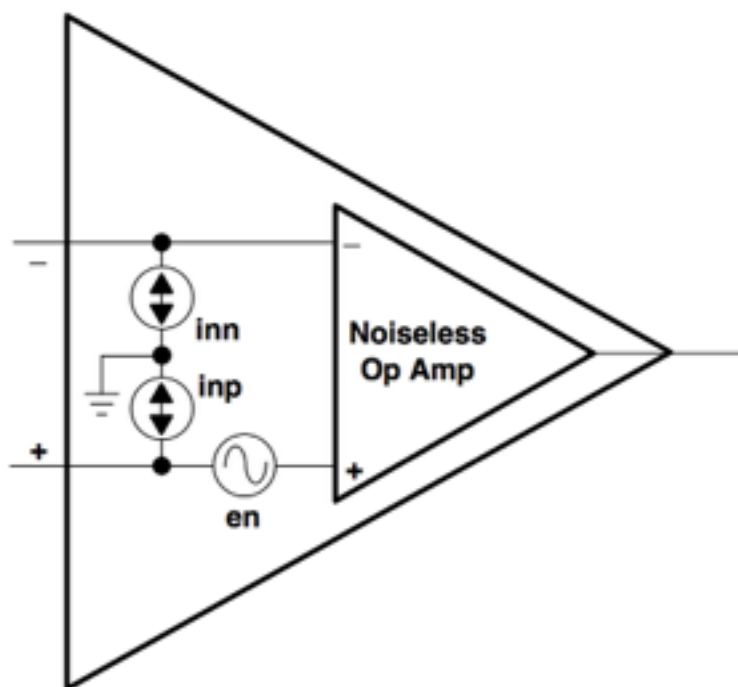



opamp voltage noise characteristics

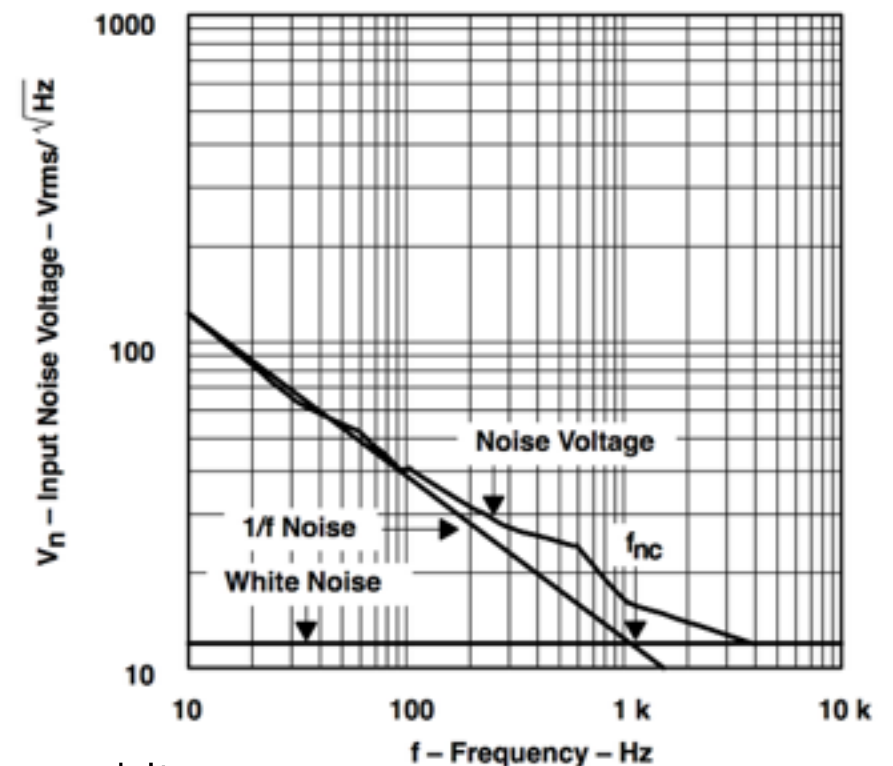

figures from TI's *Op Amps for Everyone* whitepaper

SPICE Noise Simulation

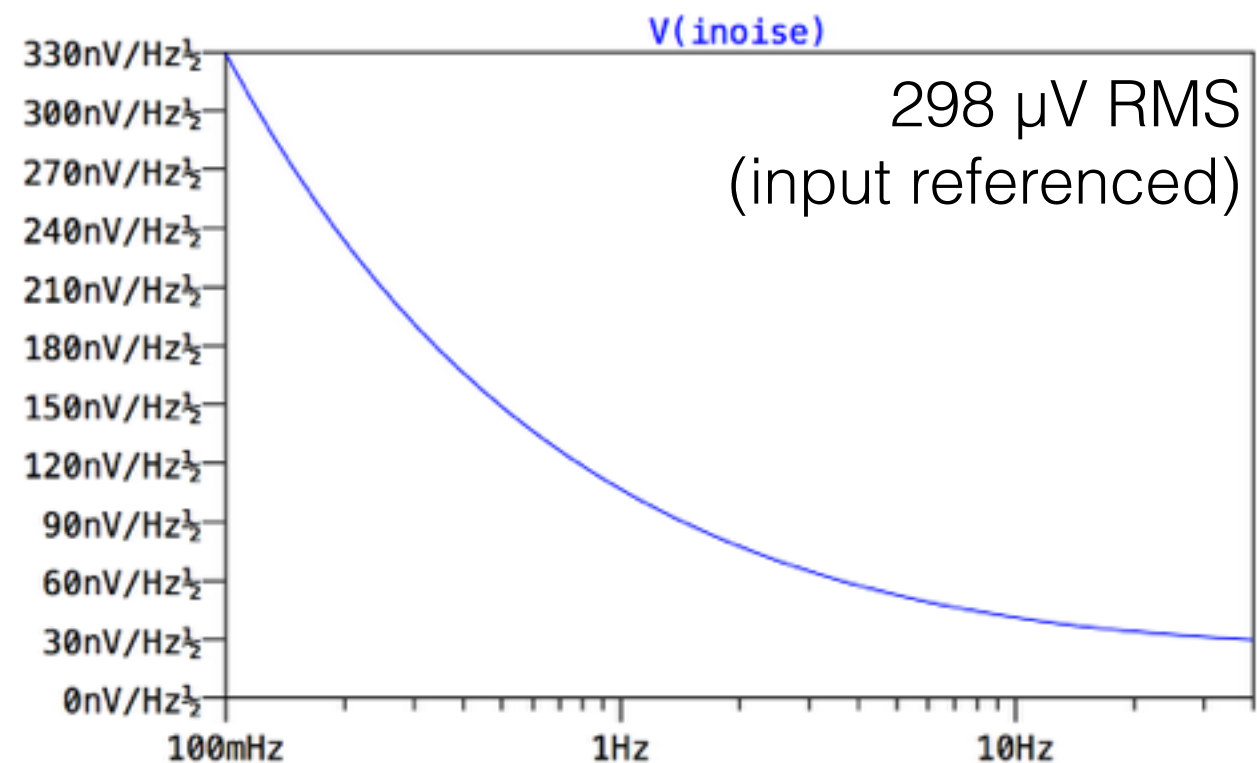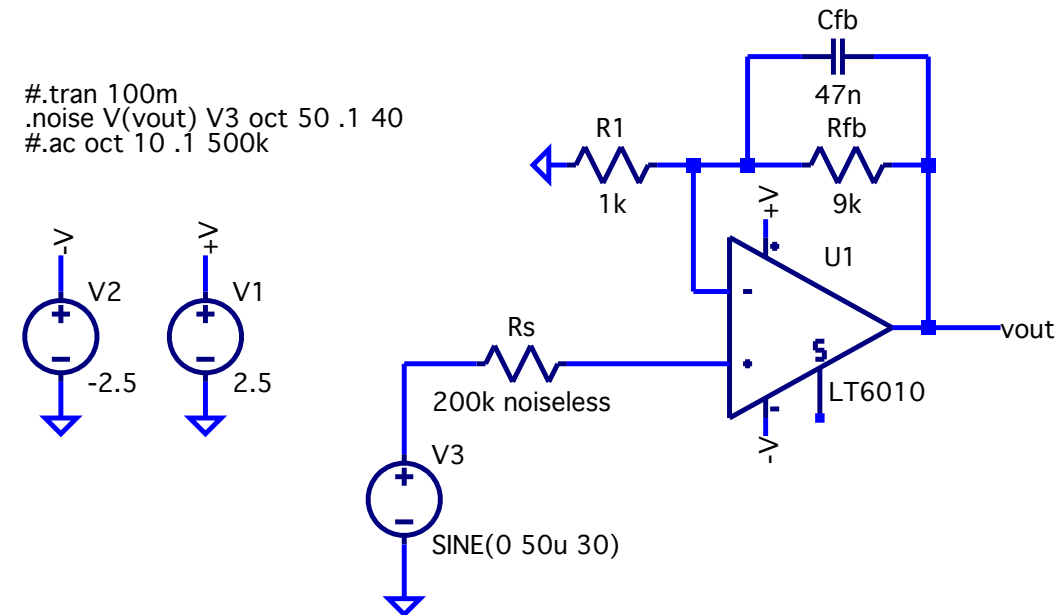- frontend noise is the most critical in the system
- must be less than 1 μ V RMS input referenced to hit 40dB SNR target
- low input offset current and voltage needed
- LT6010 selected




Differential Amplifier


- Signal on the order of 100-1000 μ V
- 60dB SNR with jellybean instrumentation amp
- Common mode feedback boosts CMMRR

AD620											
Parameter	Conditions	AD620A			AD620B			AD620S ¹			Unit
		Min	Typ	Max	Min	Typ	Max	Min	Typ	Max	
Common-Mode Rejection											
Ratio DC to 60 Hz with 1 k Ω Source Imbalance	$V_{CM} = 0$ V to ± 10 V										
G = 1		73	90		80	90		73	90		dB
G = 10		93	110		100	110		93	110		dB
G = 100		110	130		120	130		110	130		dB
G = 1000		110	130		120	130		110	130		dB
OUTPUT											
Output Swing	$R_L = 10$ k Ω $V_S = \pm 2.3$ V to ± 5 V	$-V_S + 1.1$		$+V_S - 1.2$	$-V_S + 1.1$		$+V_S - 1.2$	$-V_S + 1.1$		$+V_S - 1.2$	V
Overtemperature	$V_S = \pm 5$ V to ± 18 V	$-V_S + 1.4$		$+V_S - 1.3$	$-V_S + 1.4$		$+V_S - 1.3$	$-V_S + 1.6$		$+V_S - 1.3$	V
		$-V_S + 1.2$		$+V_S - 1.4$	$-V_S + 1.2$		$+V_S - 1.4$	$-V_S + 1.2$		$+V_S - 1.4$	V
Overtemperature Short Circuit Current		$-V_S + 1.6$		$+V_S - 1.5$	$-V_S + 1.6$		$+V_S - 1.5$	$-V_S + 2.3$		$+V_S - 1.5$	V
			± 18			± 18			± 18		mA
DYNAMIC RESPONSE											
Small Signal -3 dB Bandwidth											
G = 1			1000			1000			1000		kHz
G = 10			800			800			800		kHz
G = 100			120			120			120		kHz
G = 1000			12			12			12		kHz
Slew Rate		0.75	1.2		0.75	1.2		0.75	1.2		V/ μ s
Settling Time to 0.01%	10 V Step										
G = 1-100			15			15			15		μ s
G = 1000			150			150			150		μ s
NOISE											
Voltage Noise, 1 kHz	Total RTT Noise = $\sqrt{(e_n^2) + (e_{os}/G)^2}$										
Input, Voltage Noise, e_n			9	13		9	13		9	13	nV/ $\sqrt{\text{Hz}}$
Output, Voltage Noise, e_{os}			72	100		72	100		72	100	nV/ $\sqrt{\text{Hz}}$
RTI, 0.1 Hz to 10 Hz											
G = 1			3.0			3.0	6.0		3.0	6.0	μ V p-p
G = 10			0.55			0.55	0.8		0.55	0.8	μ V p-p
G = 100-1000			0.28			0.28	0.4		0.28	0.4	μ V p-p
Current Noise	$f = 1$ kHz		100			100			100		fA/ $\sqrt{\text{Hz}}$
0.1 Hz to 10 Hz			10			10			10		pA p-p


Linear Isolator Design

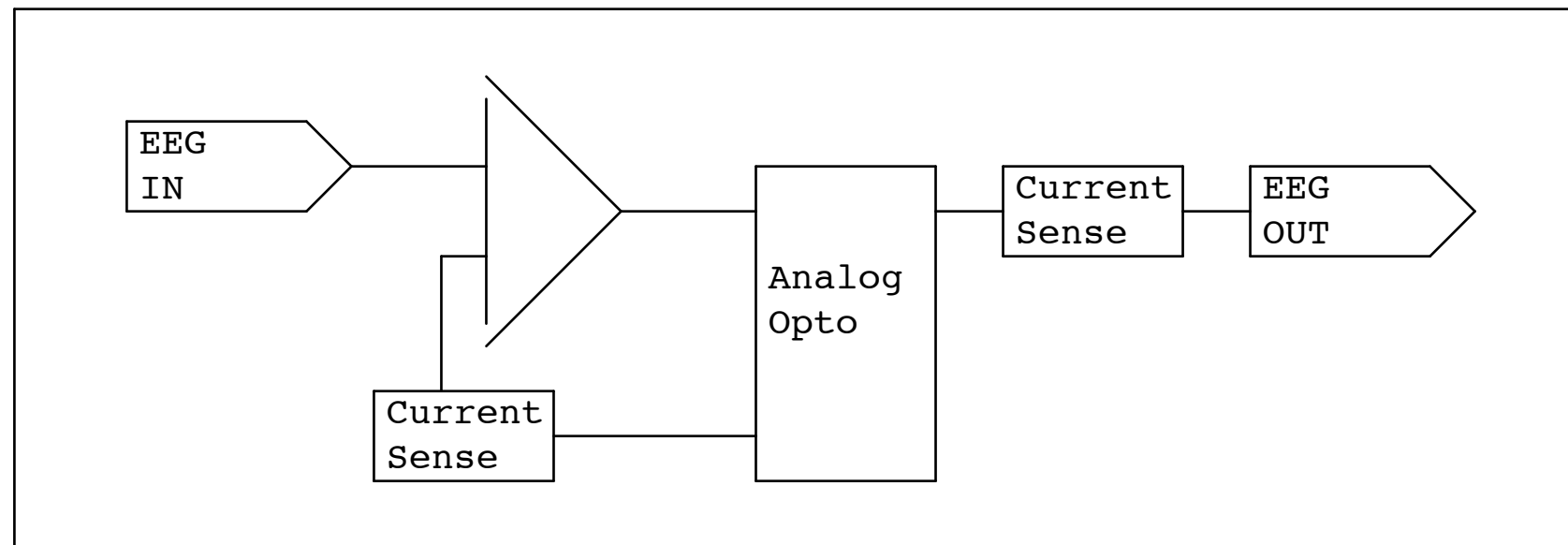

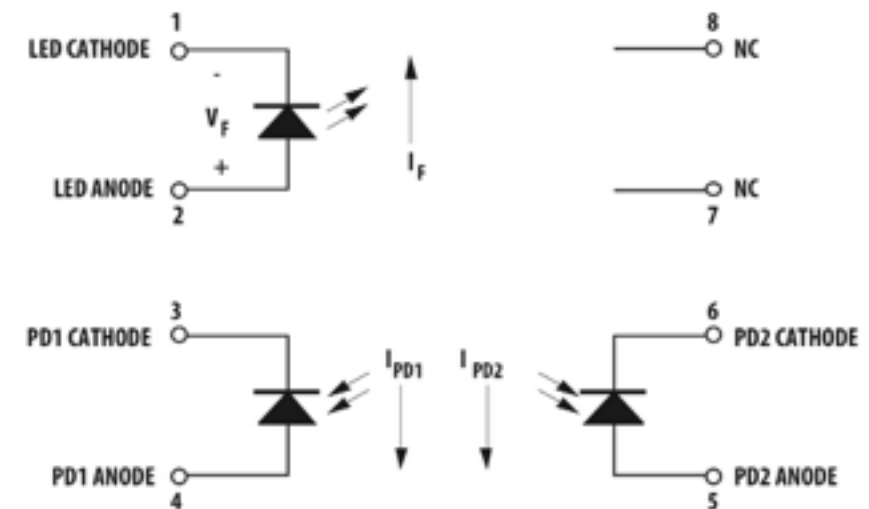- Optoisolator with photodiodes on both sides of isolation barrier
- Very low bandwidth



AM Modulation

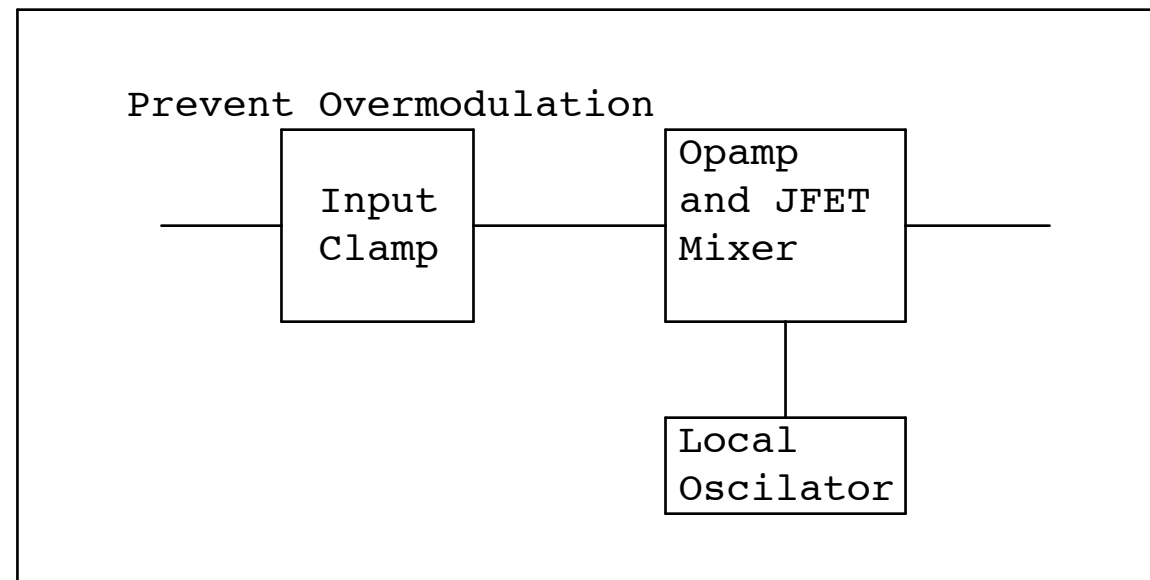

- Simple very low bandwidth AM modulation
- Reverse biased JFET as voltage controlled resistor to modulate amplifier gain.
- Linearity crucial. Why hit 40dB SNR if the EEG signal is ruined

Project Timeline

