


# LightsaberFX

—


Elizabeth Lee and Jing Wang
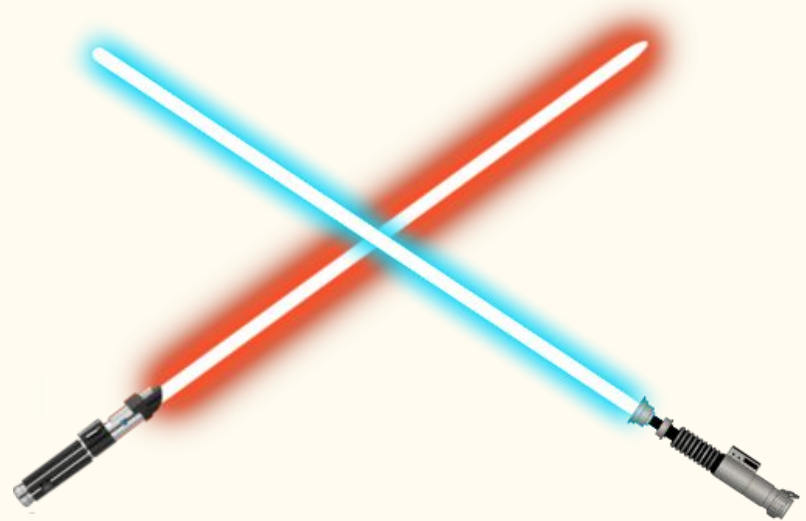
# LightsaberFX

- Circuitry completely mounted on lightsaber
- Sound effects produced with movement
- Frequency and volume varies
- “Impact” noise when hit
- Run on 9V battery




# Overview

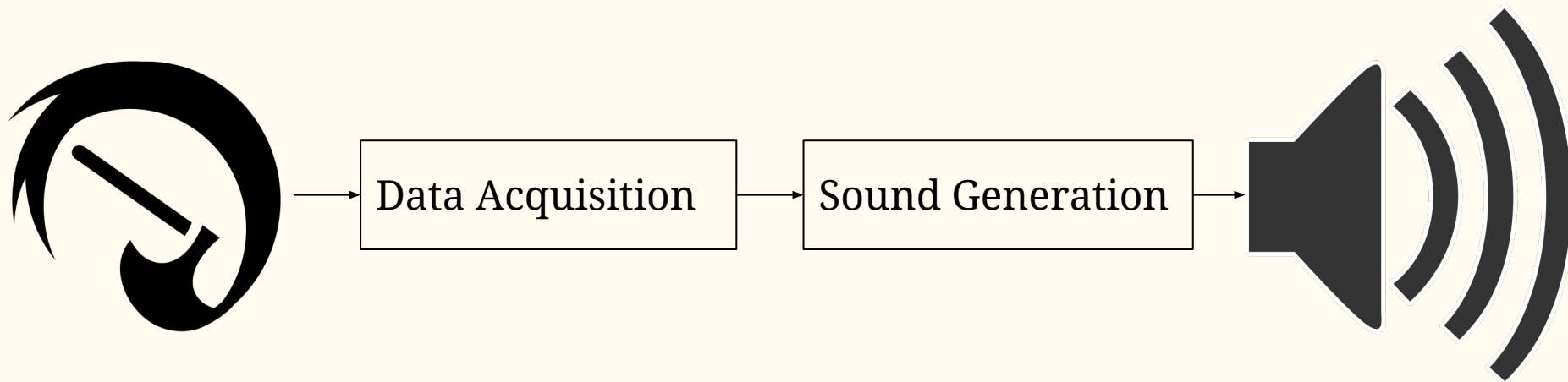

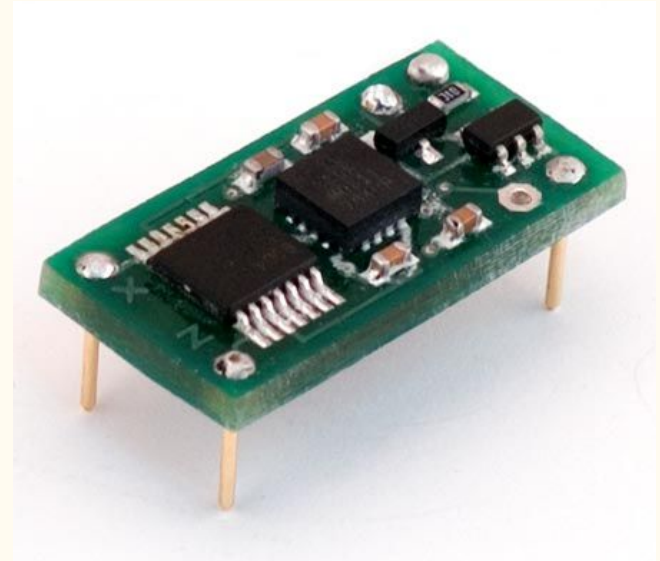
# Accelerometer


- DE-ACCM3D tri-axis accelerometer
- Voltage readings for acceleration in x, y, and z axes, including acceleration due to gravity
- 3.3V regulator
- Sensitivity: 300mV/g at 3.0V input to 360mV/g at 3.6V input
- 0.9mA current draw




# Movement Data Acquisition

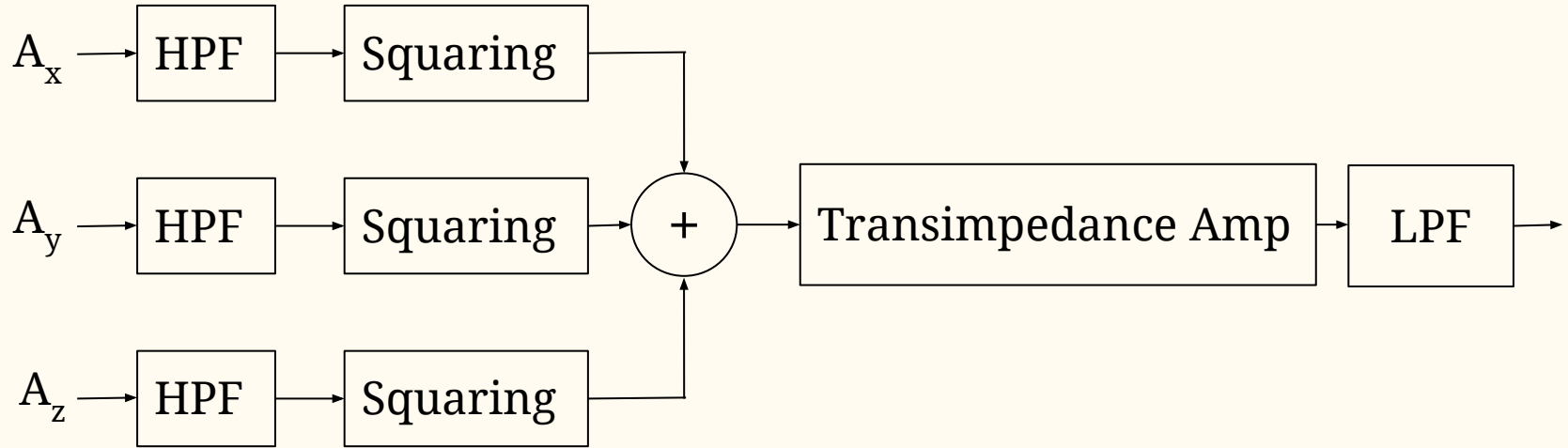

# Movement Data Acquisition Up Close

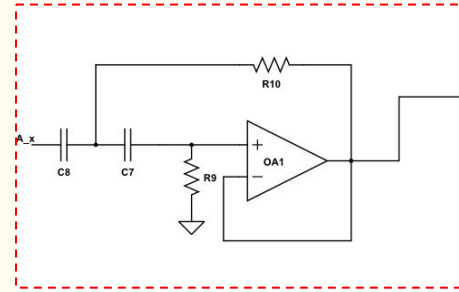


Sallen-Key HPF

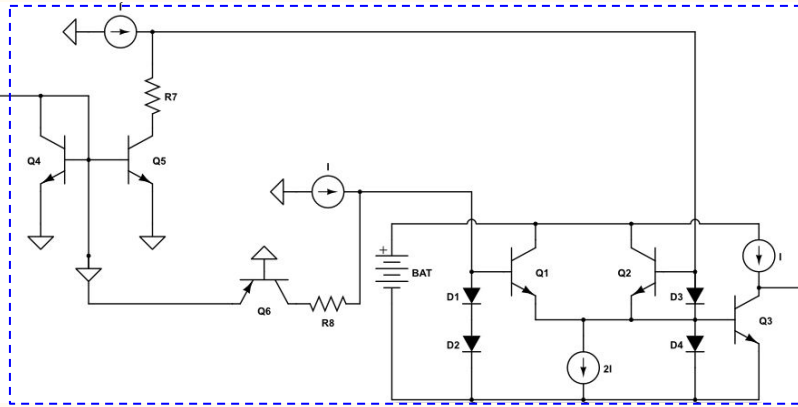


Translinear Squarer

Transimpedance  
Amplifier

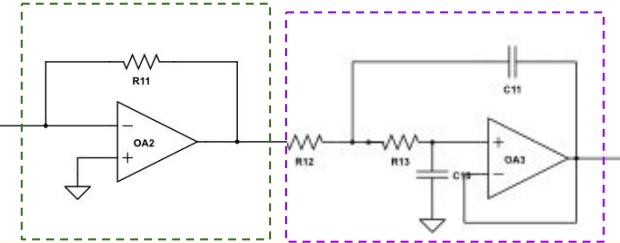


Sallen-Key LPF

# Squaring circuit

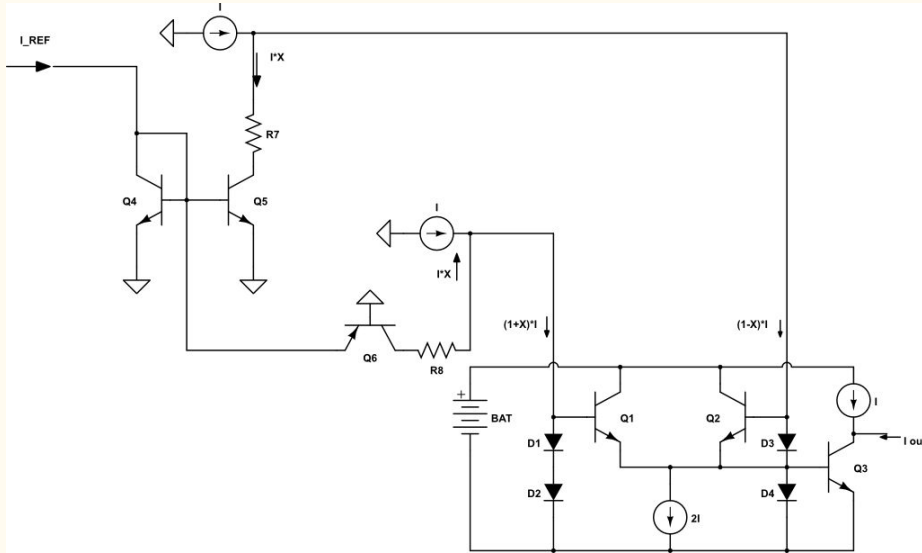

- Calculate total magnitude of acceleration
- Translinear circuit: current-dependent
- Currents generated by current mirrors
- Disclaimer: This probably won't work.


# Sound generation

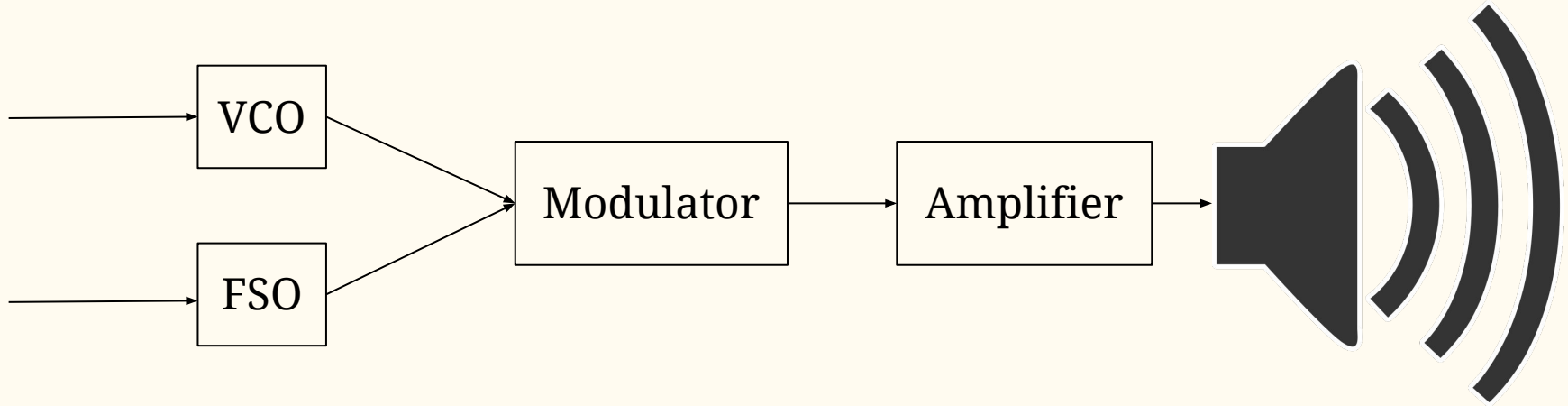



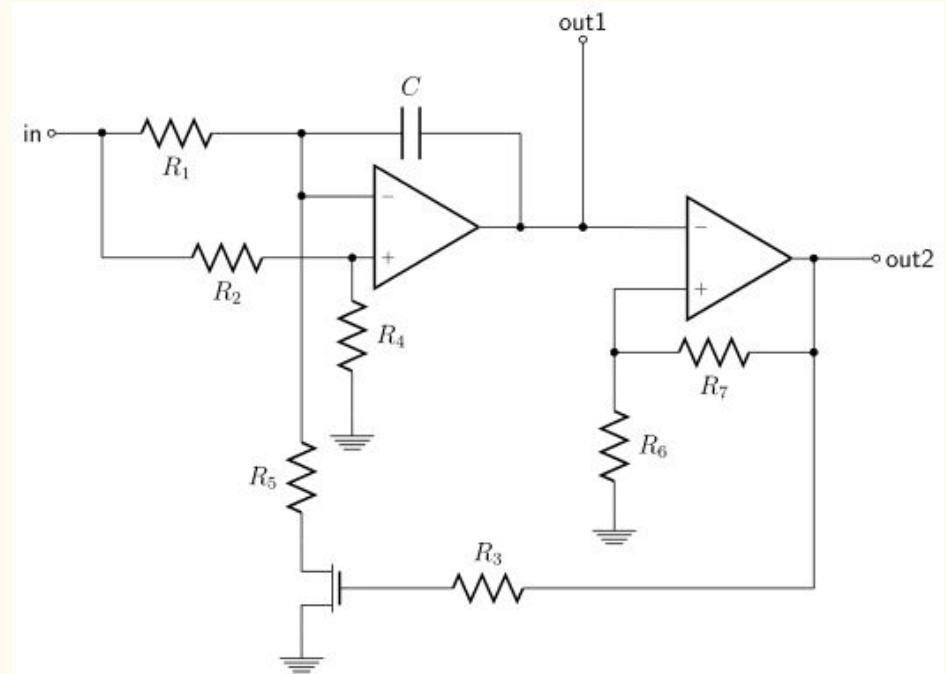
# Voltage Controlled Oscillator

- Frequency controlled by voltage input
- Serves as frequency modulation for audio output
- Carrier signal for AM modulation



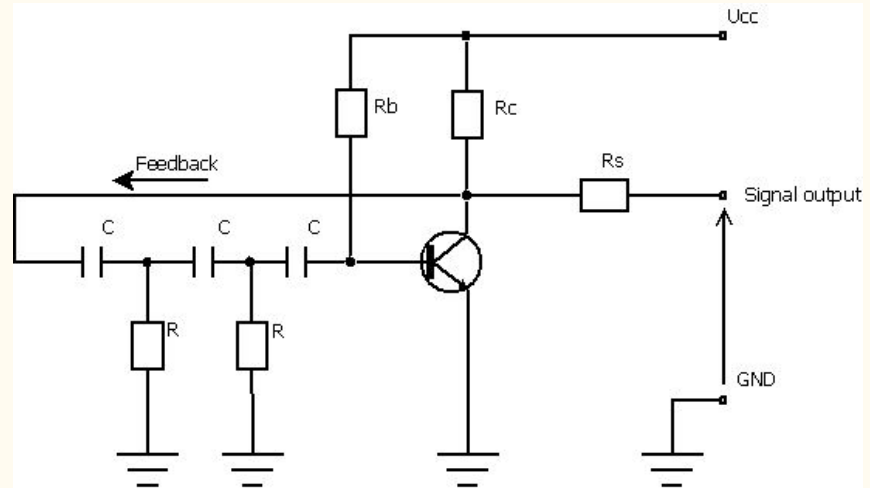
# Phase Shift Oscillator

- Phase shift oscillator for audio signal
- Power supply controlled by voltage input to control volume based on intensity of movement
- Audible range 20Hz - 20KHz


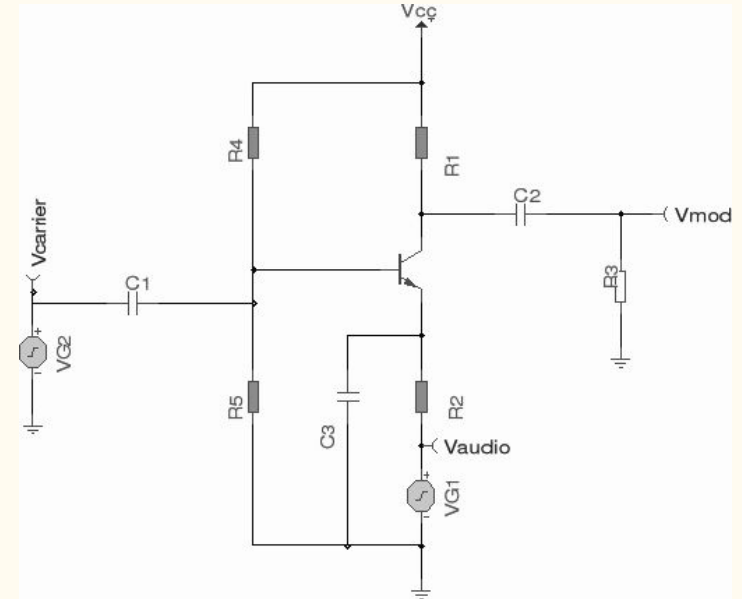
# Amplitude Modulation

- Amplitudes of signals multiplied in AM circuit
- Transistor gate controlled by carrier signal with emitter offset by audio signal
- Produces modulated signal



# Goals

- 3-axis swishing sound effects
- Powered by 9V battery

# Toe-Touch Goals


- Sound effects from impact acceleration
  - Comparator with high acceleration voltage
- System shuts off when not in use
  - Timer circuit

# SPLITS

- Replace 9V battery with 2 1.5V AA batteries
  - Boost converter to step up voltage
- Mechanism that turns on lightsaber when movement threshold is reached
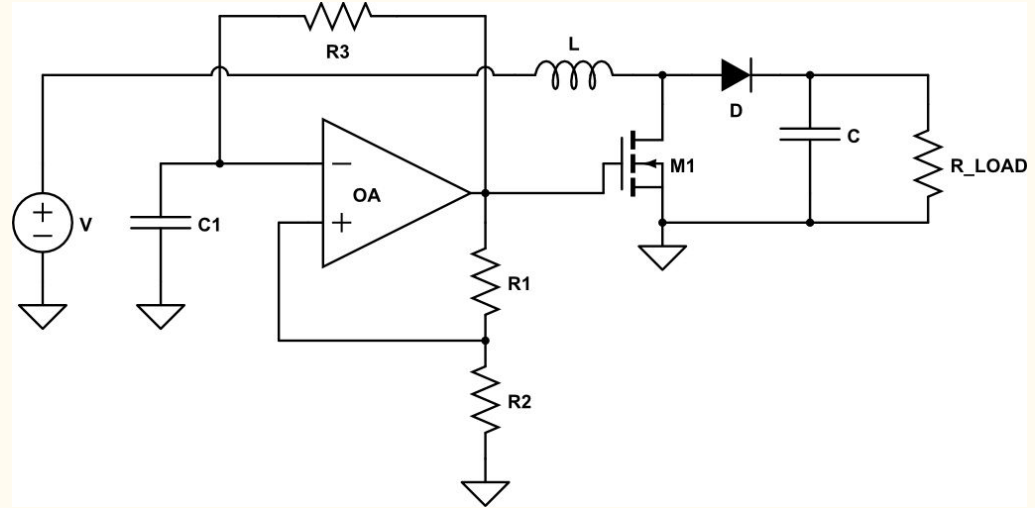
# Boost Converter

- Ramp up voltage for voltage controlled oscillator
- Voltage gain of  $1/(1-D)$ , where  $D$  is the duty cycle



# Timeline

4/23	Demonstrate sound effects for one axis
4/30	Incorporate all three axes and add hitting noise
5/4	Implement system timer circuit and try replacing 9V battery with 1.5V AA batteries  If ahead of schedule, add movement-triggered on switch
5/7	Final testing and debugging
5/9	Project demo



Questions?