

Speaker in a Box


Battery Powered with Tactile Input

Natalie Mionis, Lorenzo Vigano, Madeleine Waller


Functional Requirements

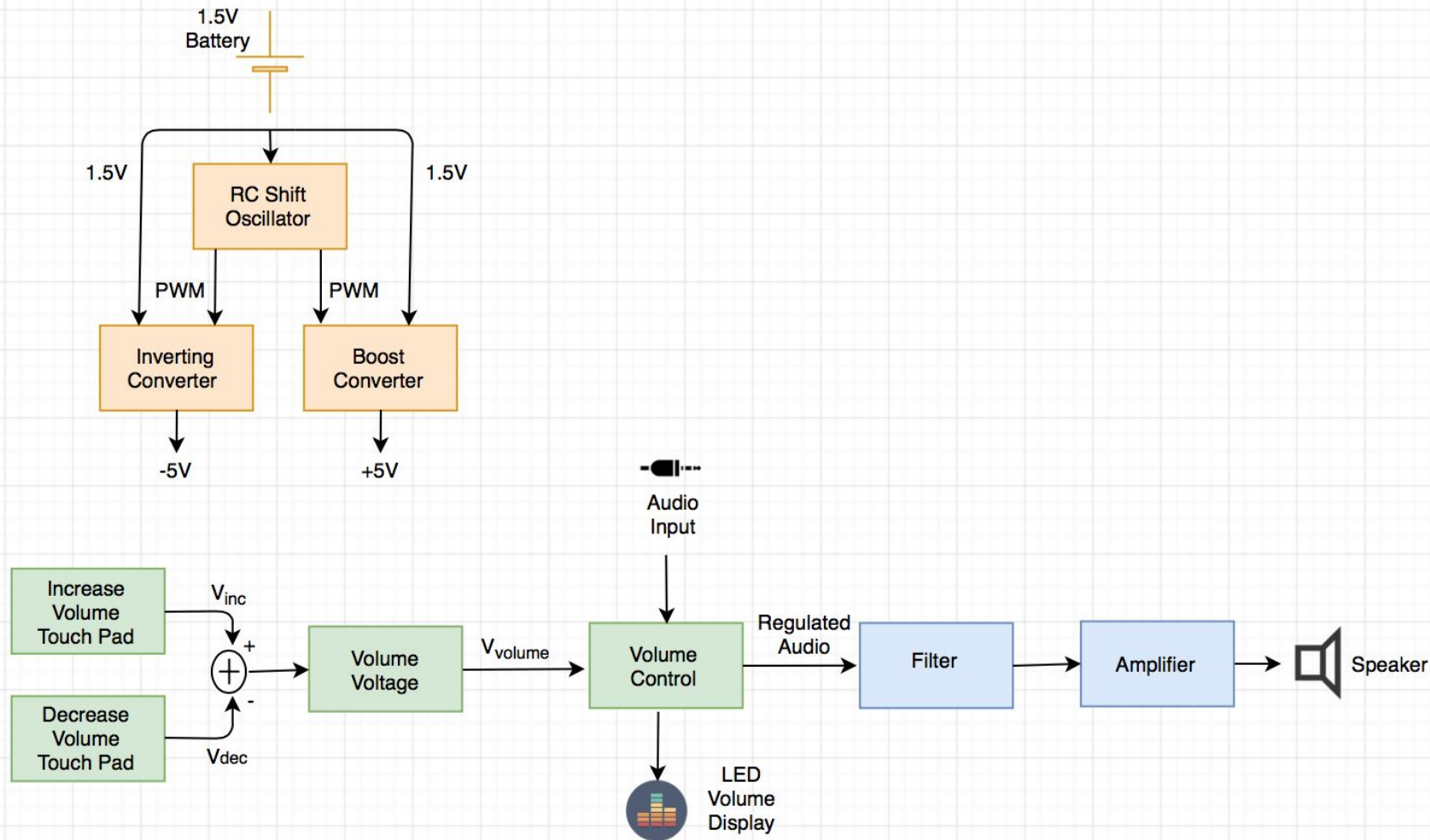- Small, portable speaker
- Powered from 1.5V battery
- Controlled via touch
- LED display







Power Module

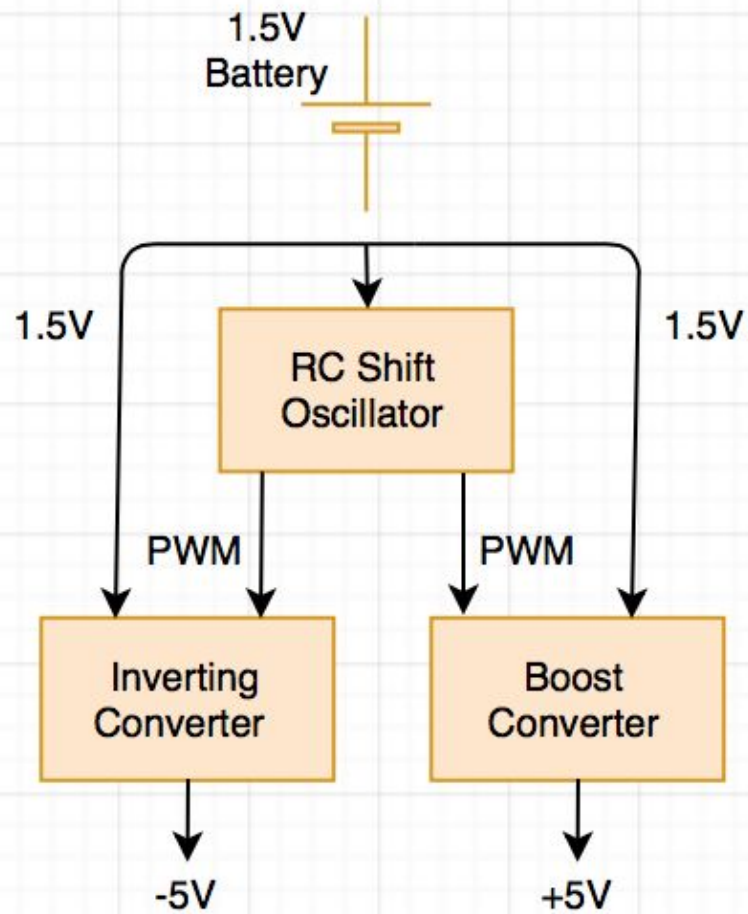


Colpitts Oscillator

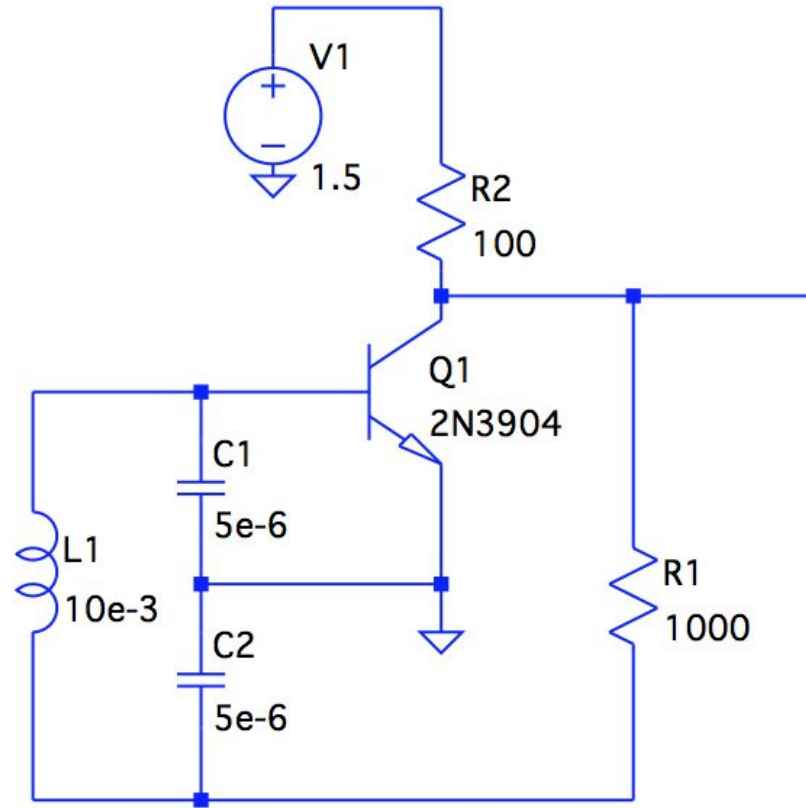

Boost Converter

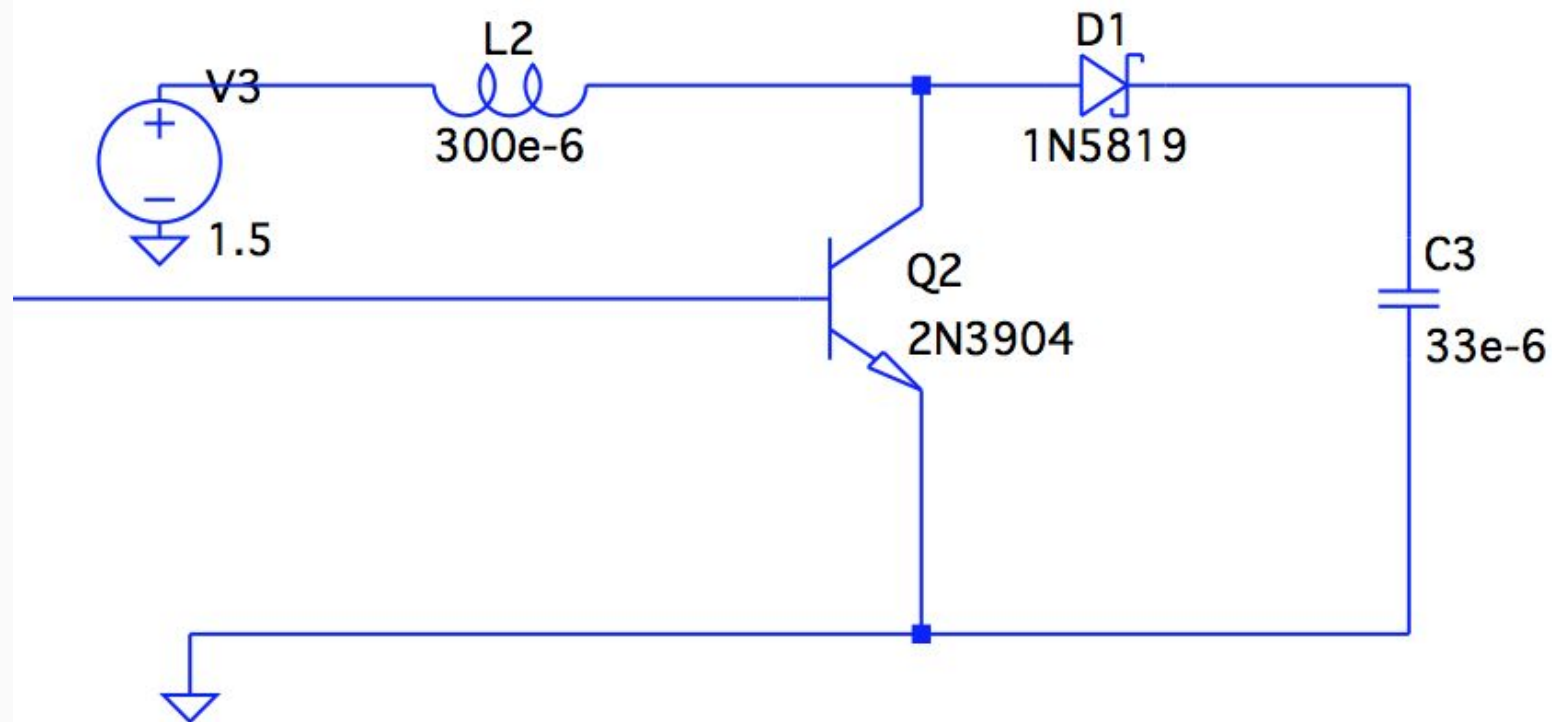

Inverting Converter

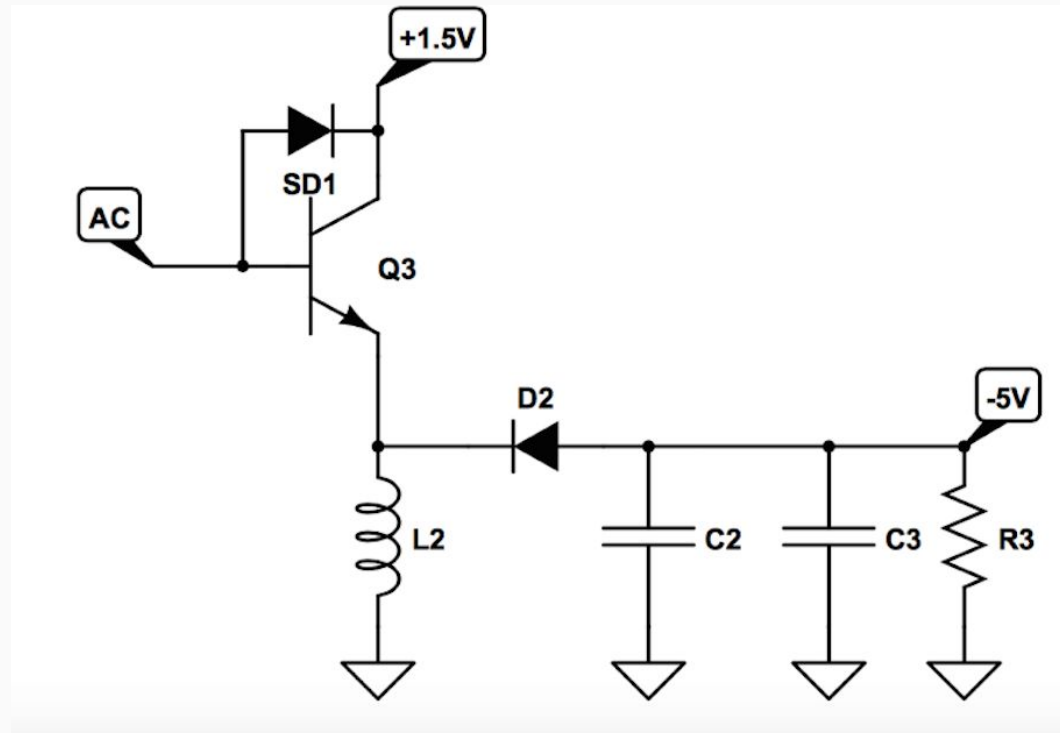

Goals and Challenges


Goal 1: Achieve $\pm 5V$ from a 1.5V battery

Goal 2: Improve efficiency for longer battery life



Challenges:

- 1.5V supply limits MOSFET use and IC use
- Must be conscious of current draw


Tactile Volume Control

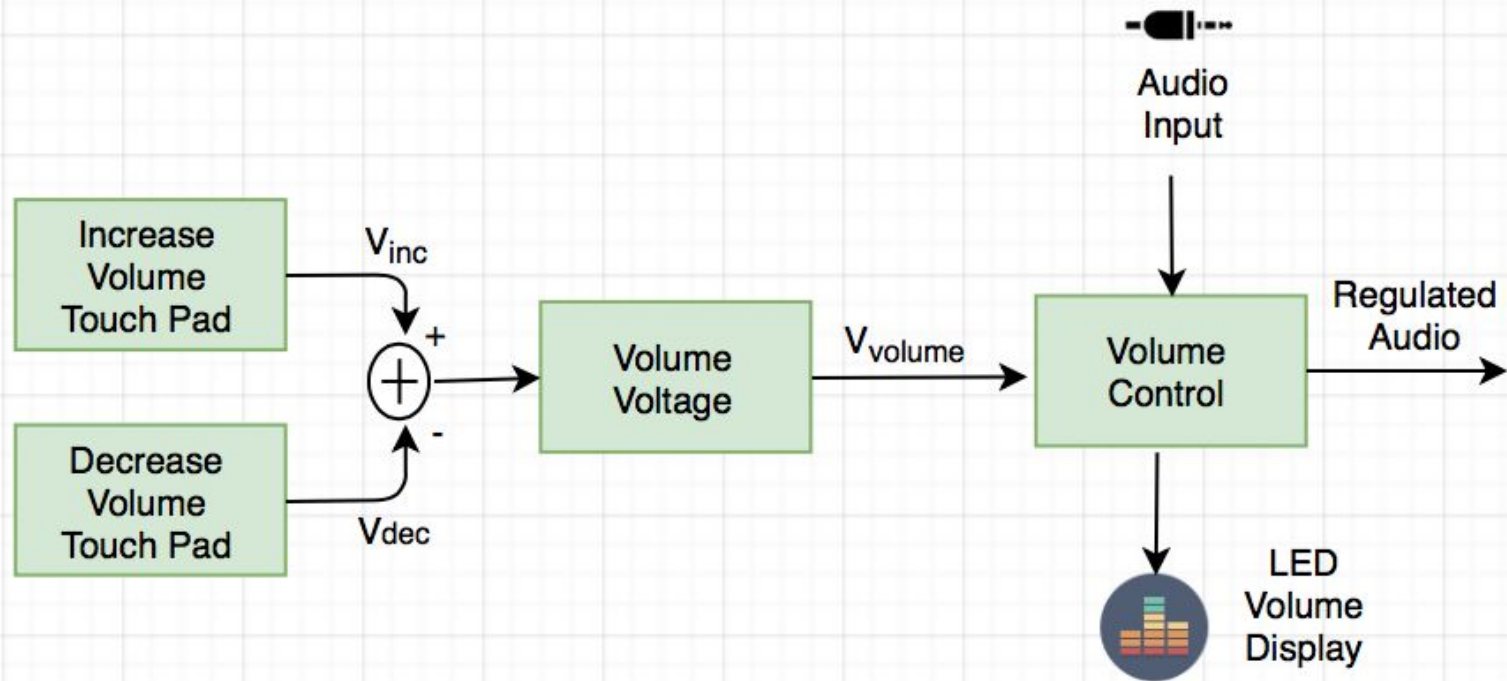


Volume Control Voltage

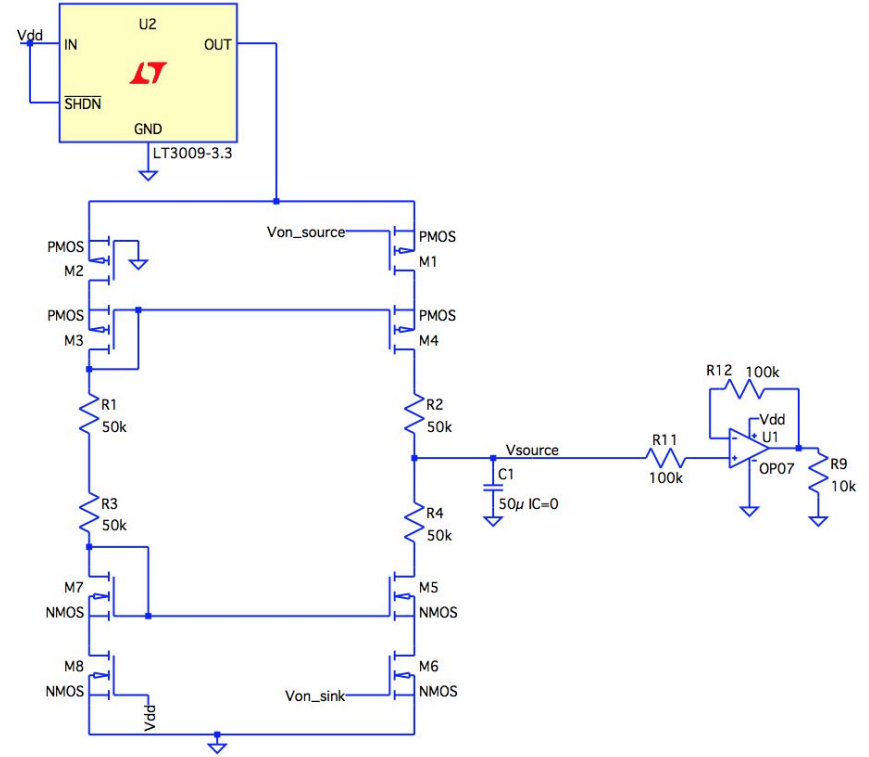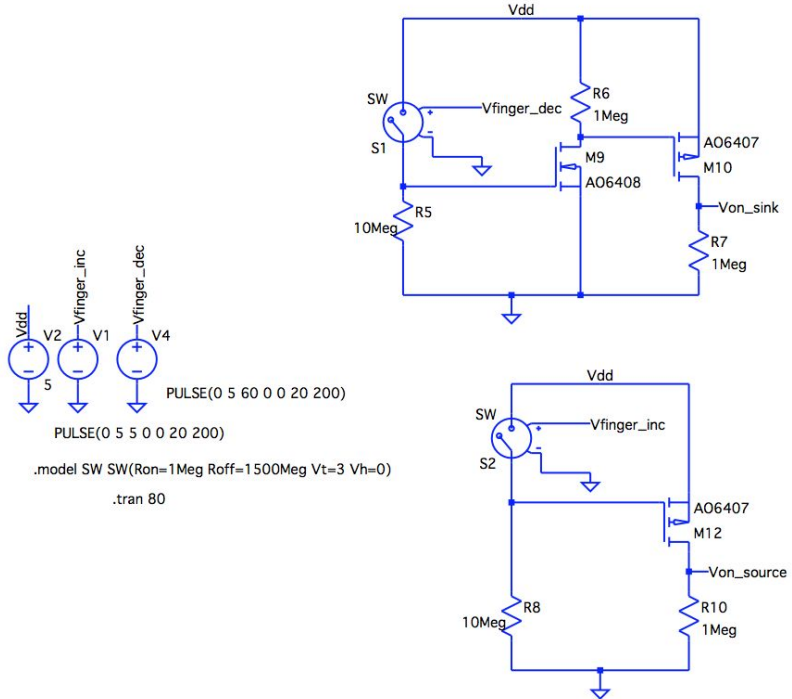

Volume LED Display

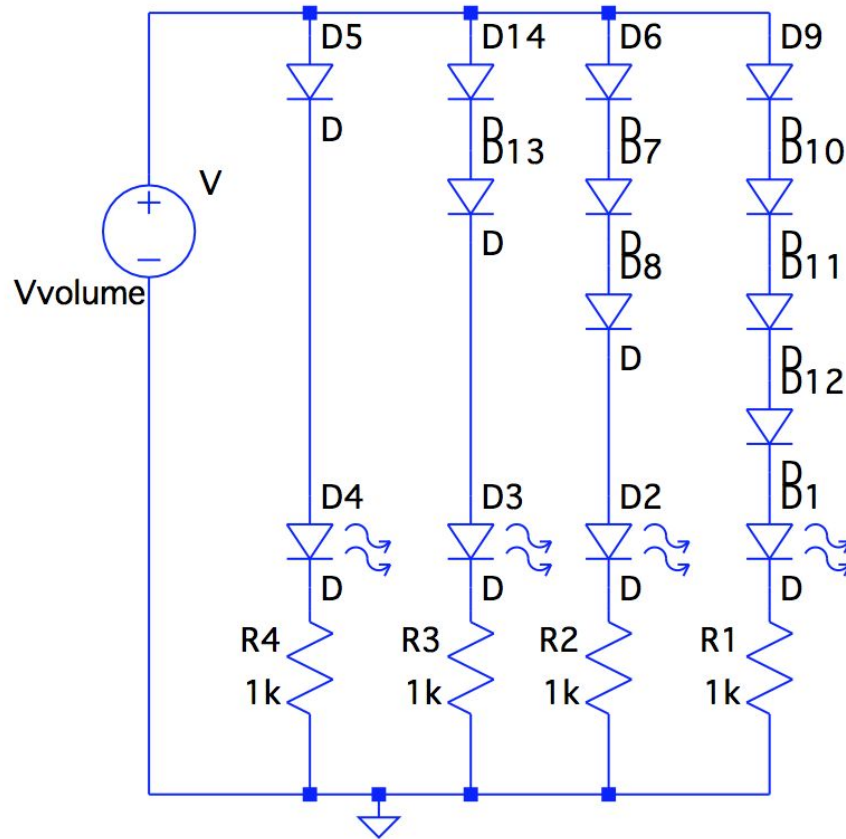

Voltage Regulated Audio Signal

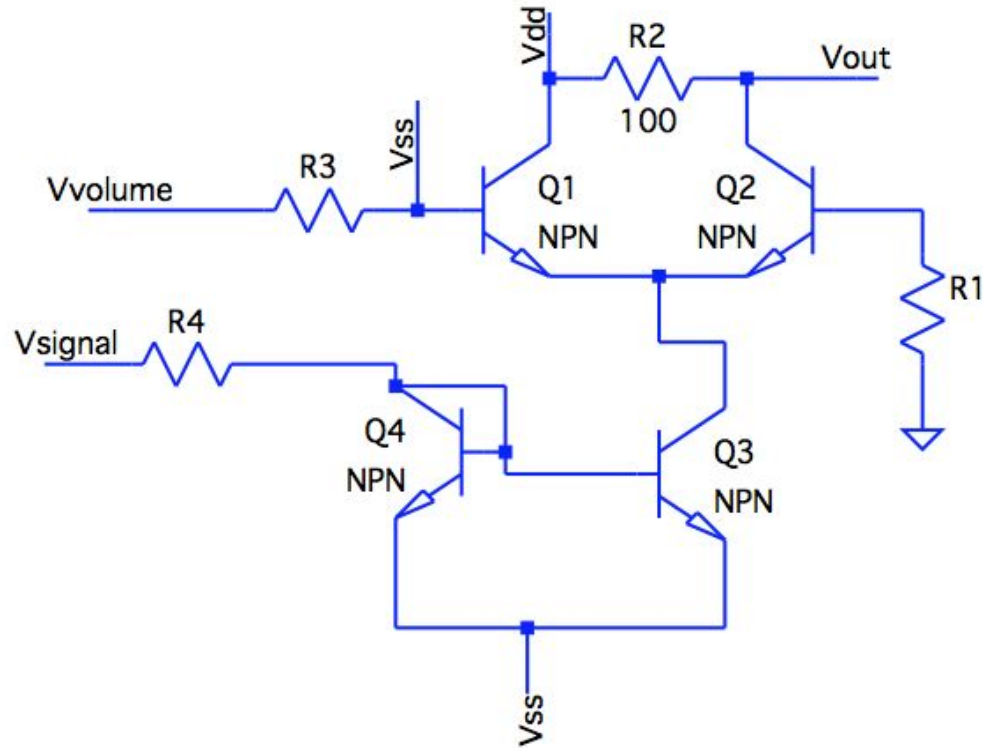



Tactile Volume Control Goals and Challenges

Goal 1: increase/decrease volume by touch


Goal 2: LED volume display bank

Stretch goal: add a linear soft pot to allow user to select volume directly

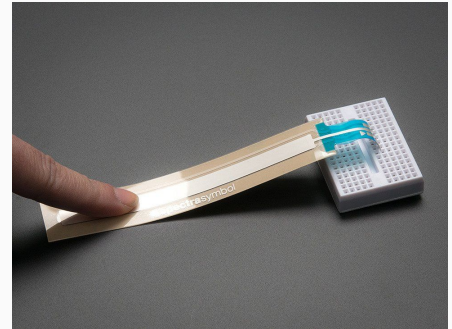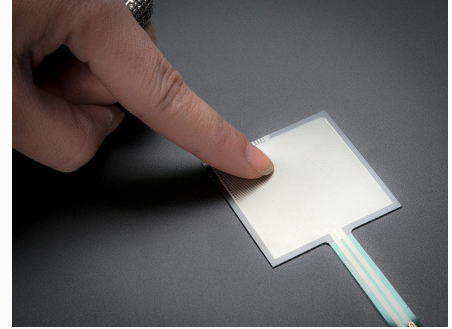
Primary challenge: maintain stable memory of current volume that responds quickly to user input




Audio, Filter, and Lights Module

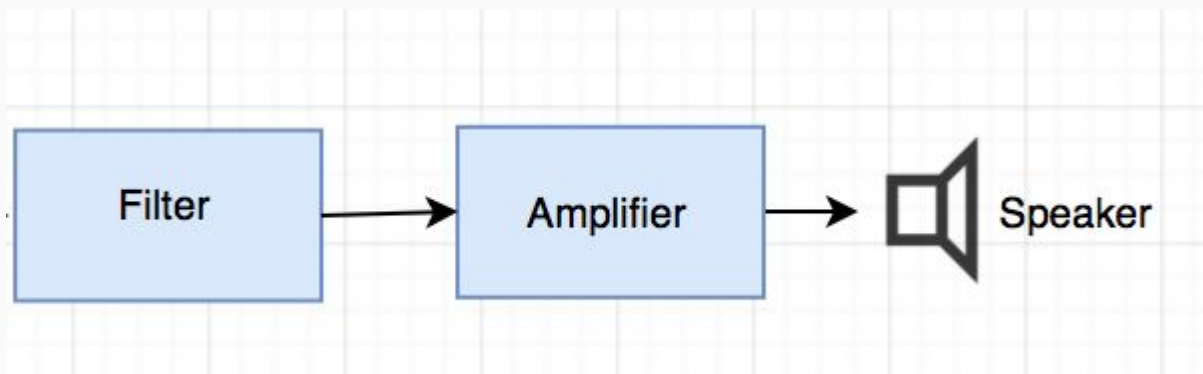


Passband Filter

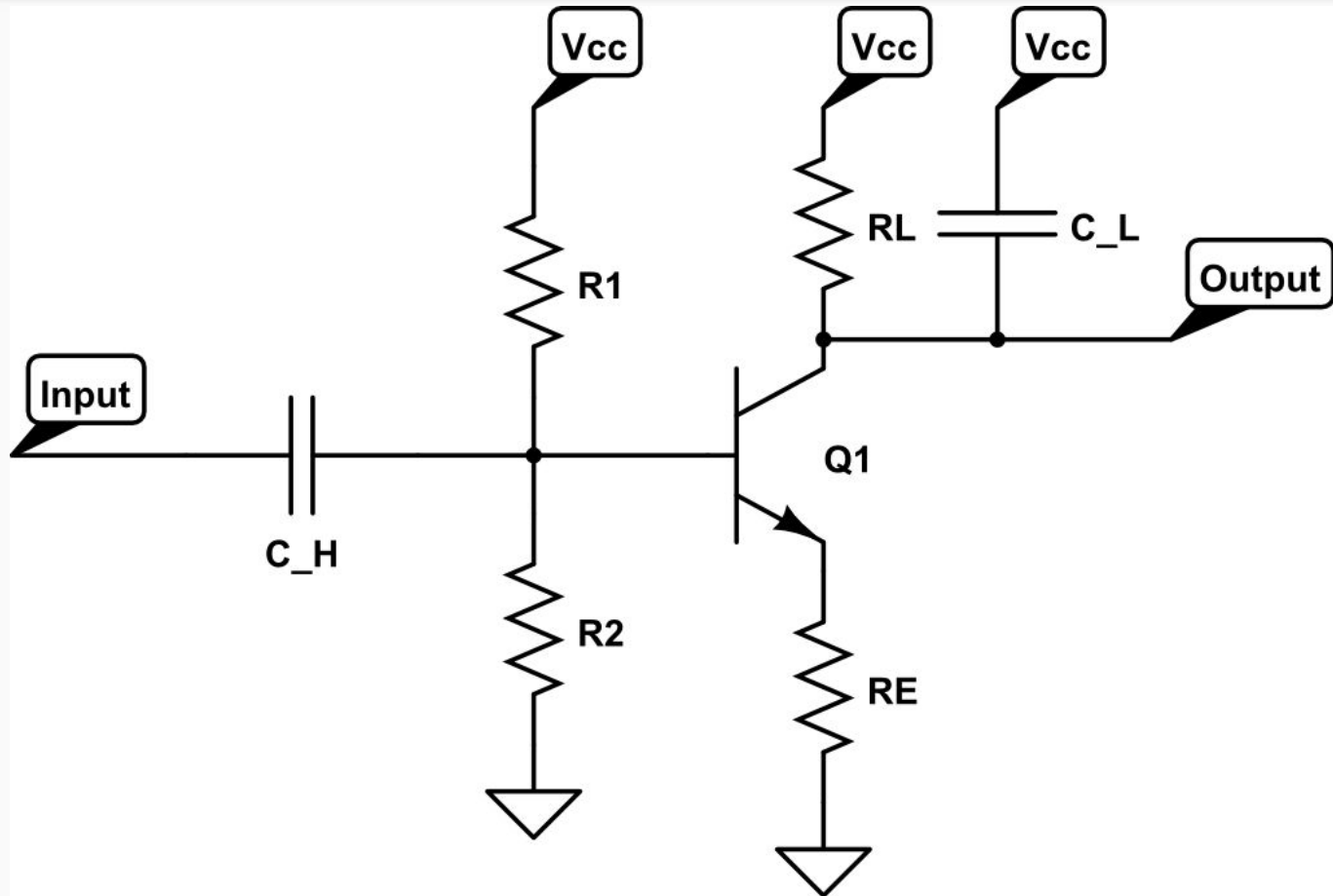

Fun with Filters

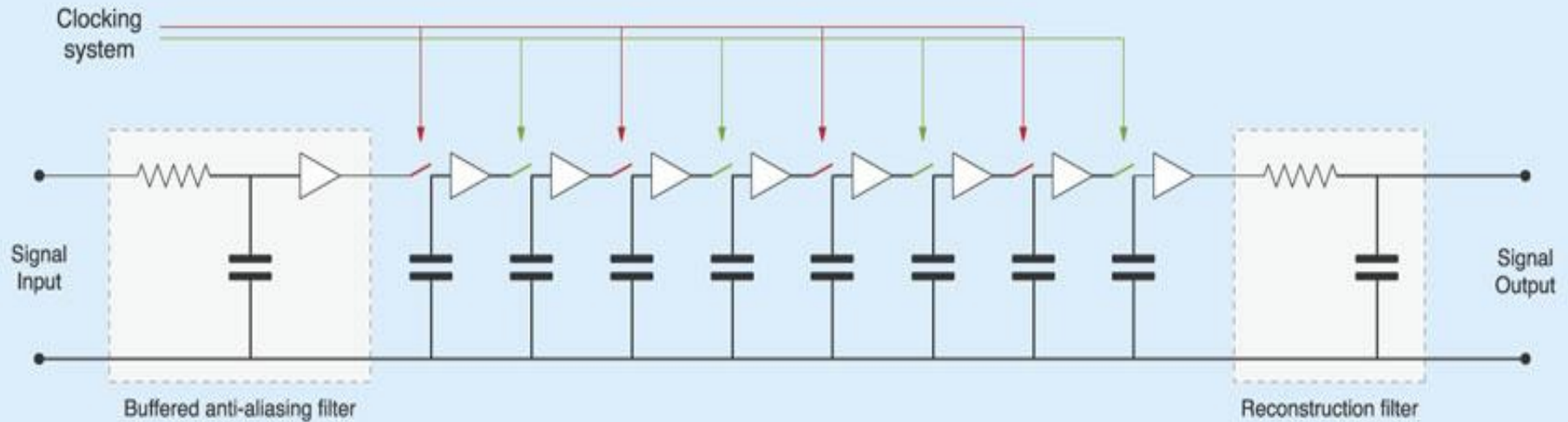

Audio Amplifier

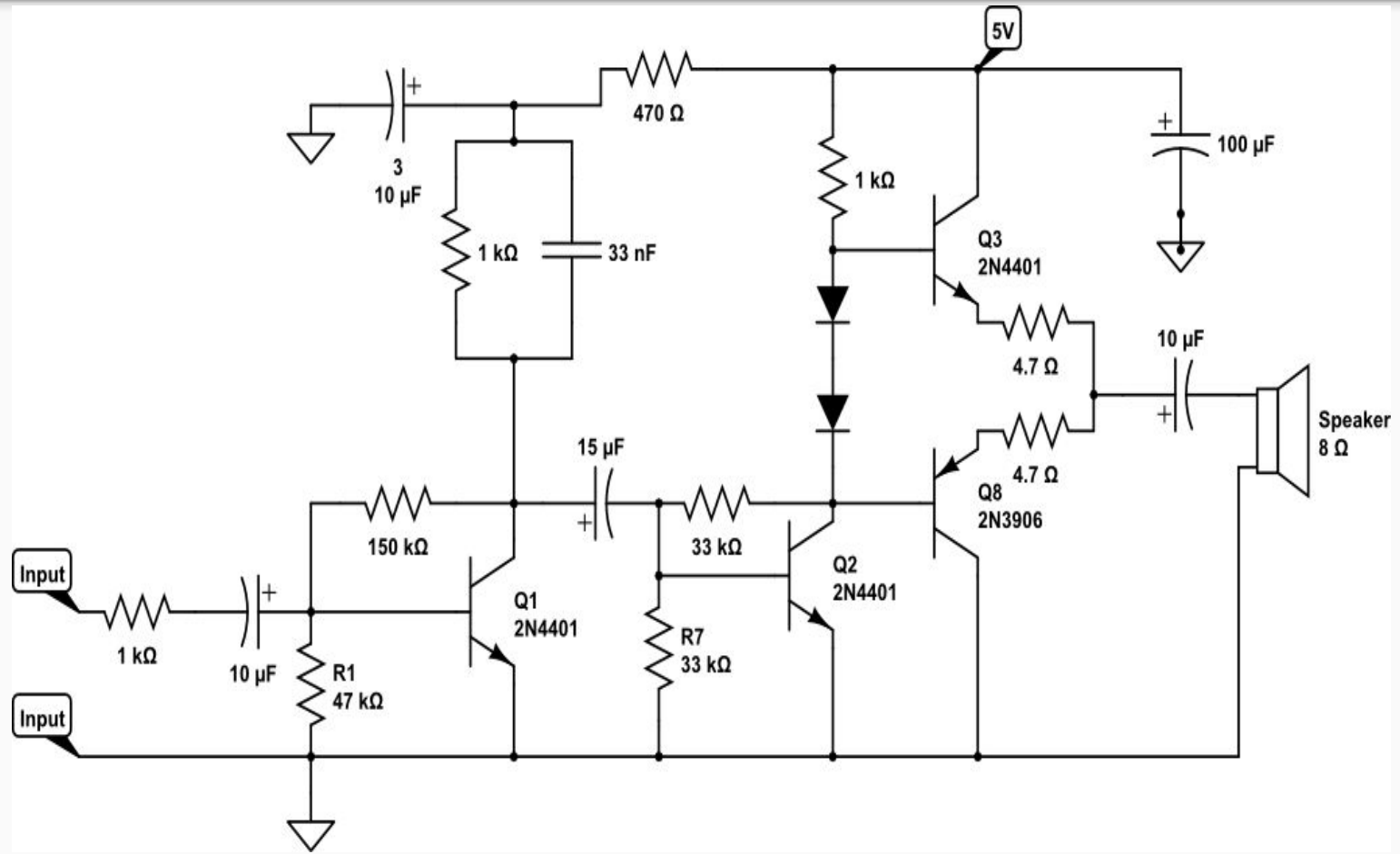

Audio and Lights Goals and Challenges

Goal 1: Achieve acceptable sound quality with limited distortion.


Goal 2: Improve efficiency for longer battery life.

Goal 3: LED display to show current volume of song.

Challenges:

- Power limitations
- Echo

COOL PARTS OF PROJECT

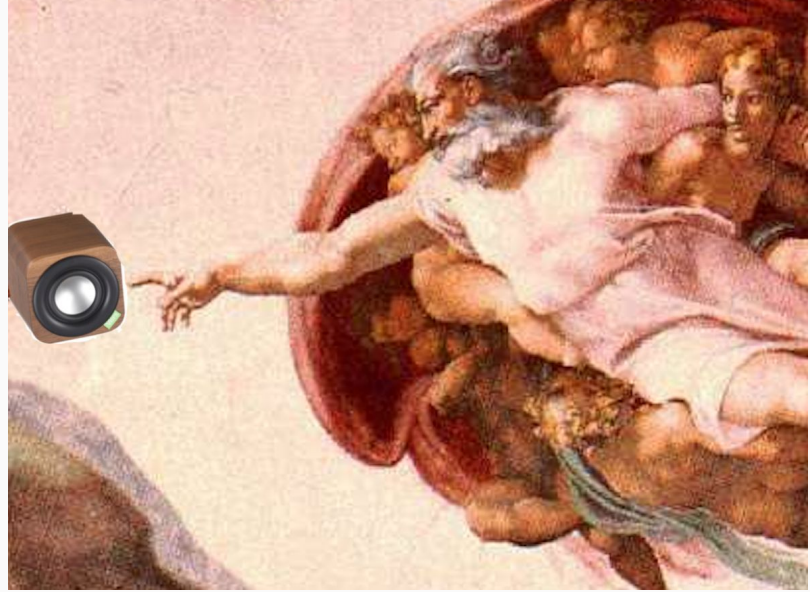

Special Materials

- Winding own inductors
- Speaker
- Machining the box
- Force sensing resistors (x2)
- Linear soft potentiometer
- Large ceramic capacitors

Timeline

	Week of 4/9	Week of 4/16	Week of 4/23	Week of 4/30	Week of 5/7	Group Effort
Research Techniques						Natalie
Order Special Parts						Madeleine
Spice Modeling: Power Supply						Lorenzo
Spice Modeling: Volume Control						
Spice Modeling: Amplifier & LED display						
Build Volume Control Circuit						
Build LED Volume Display						
Build Power Module						
Build Volume Control						
Build Amplifier and Filter						
Integrate						
Stretch Goals						
Final Debugging						
Final Report						

Questions?