



# Welcome to 6.111!

- Introductions, course mechanics
- Course overview
- Digital signaling
- Combinational logic

## Handouts

- lecture slides,
- LPset #1,
- info form,
- kit signout

Lecture material: Prof Anantha Chandrakasan and Dr. Chris Terman.

# 6.111 Introductory Digital Systems Lab

- Learn digital systems through lectures, labs and a final project using FPGAs and Verilog.
- Gain experience with hands on course with real hardware - nothing in the cloud.
- 6.111 satisfies
  - Course 6: DLAB2, II, EECS, AUS2
  - Course 16: Laboratory requirement, Professional Area subject

# Introductions



Gim Hom  
*Lectures*



Joe Steinmeyer  
*Lectures*




Driss Hafdi  
TA




Diana Wofk  
TA



Melinda Szabo

 

Mike Wang

 


Aaron Wubshet


*LA's*
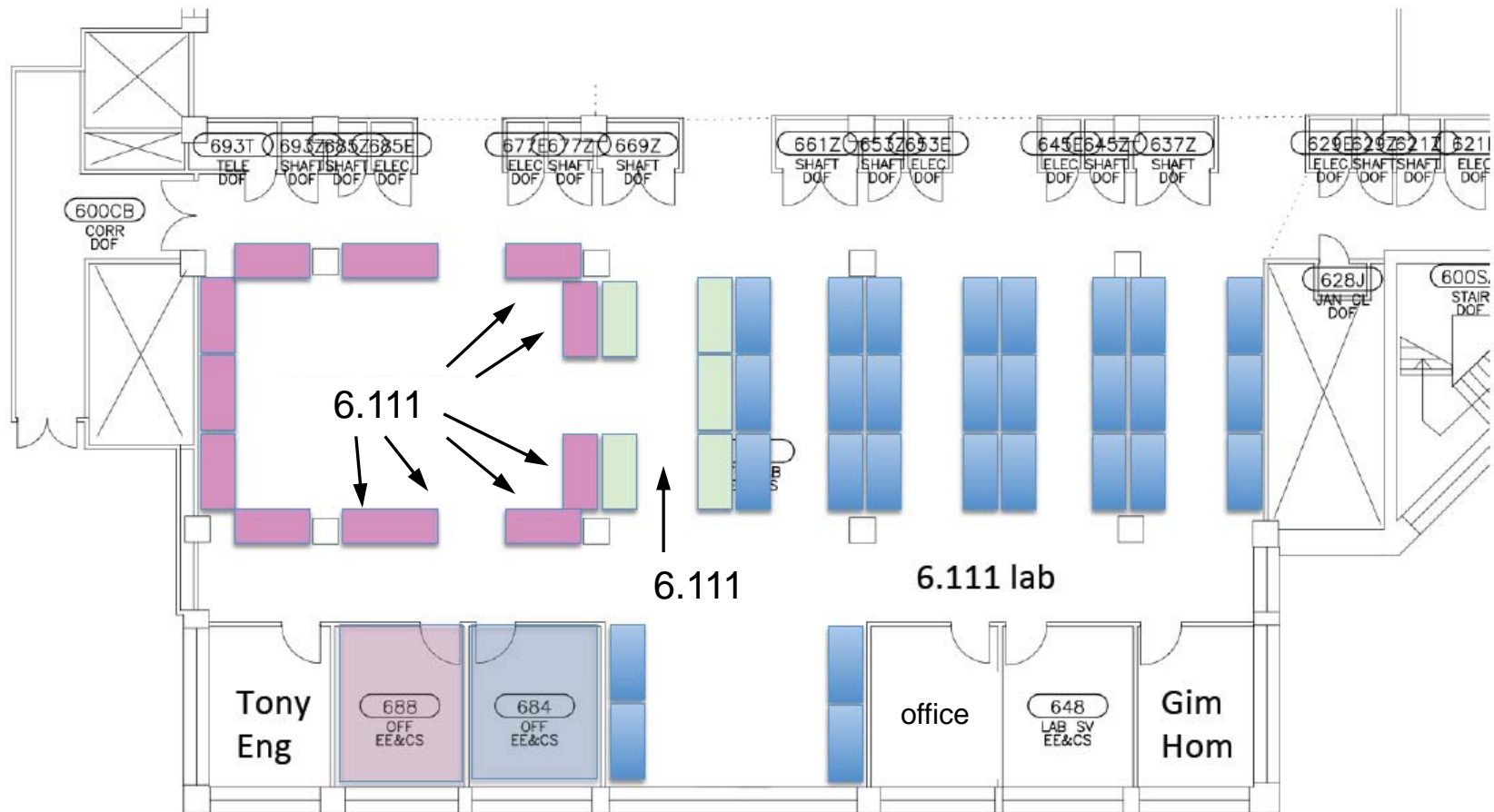
# 38-600

41 Stations

Lab hours:  
S 1-11:45p  
M-R 9-11:45p  
F 9-5p



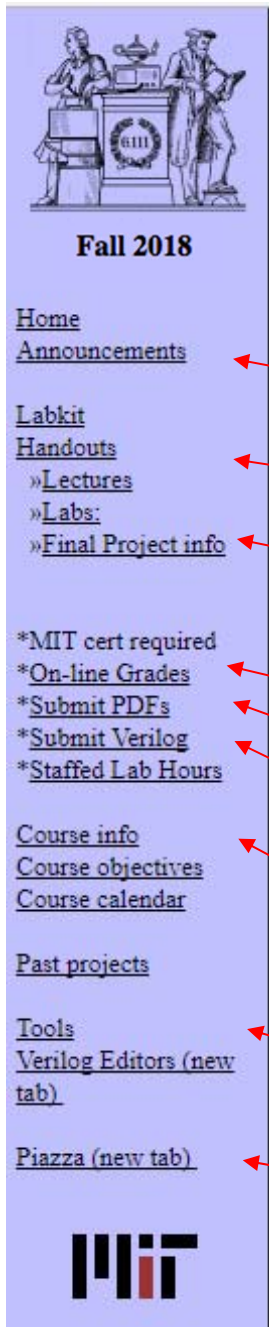


# 6.111 Introductory Digital Systems Laboratory

Course Website: [web.mit.edu/6.111](http://web.mit.edu/6.111)

Lab: 38-600

# Assignments

 

A large number of students do "A" level work and are, indeed, rewarded with a grade of "A". The corollary to this is that, since average performance levels are so high, punting any part of the subject can lead to a disappointing grade.

## **Project Presentation & Report (13%)**

- Design proposal (2%)
- Design presentation (6%)
- Final Report (5%)

# Labs: learning the ropes


- Lab 1 (2%)
  - Experiment with gates, design & implement some logic
  - Learn about lab equipment in the Digital Lab (38-600): oscilloscopes and logic analyzers
- Lab 2 (5%)
  - Introduction to Verilog, ModelSim & the labkit
  - Serial communications
- Lab 3 (8%)
  - Video circuits: a simple Pong game
    - Use Verilog to program an FPGA
    - Display images
- Lab 4 (11%)
  - Design and implement a Finite State Machine (FSM) - Car Alarm
- Lab 5 (8%)
  - Design a complicated system with multiple FSMs (Major/Minor FSM)
    - Voice recorder using AC97 codec and SRAMs or
    - Digital bubble level using IMU
- You must have a non-zero score for each of the labs and all the labs must be checked off as a prerequisite for passing the course. A missing lab will result in a failing grade.



# Final Project


- Done in groups of two or three; one person project by exception
- Open-ended
- You and the staff negotiate a project proposal
  - Must emphasize digital concepts, but inclusion of analog interfaces (e.g., data converters, sensors or motors) common and often desirable
  - Proposal Conference, several Design Reviews
  - Have fun!
- Design presentation to staff
- Staff will provide help with project definition and scope, design, debugging, and testing
- It is extremely difficult for a student to receive an A without completing the final project. Sorry, but we don't give incompletes.

# Virtual Pool - La PC Na

 


Fall 2018  
Matt Basile  
Zareen Choudhury

# FPGA Beethoven

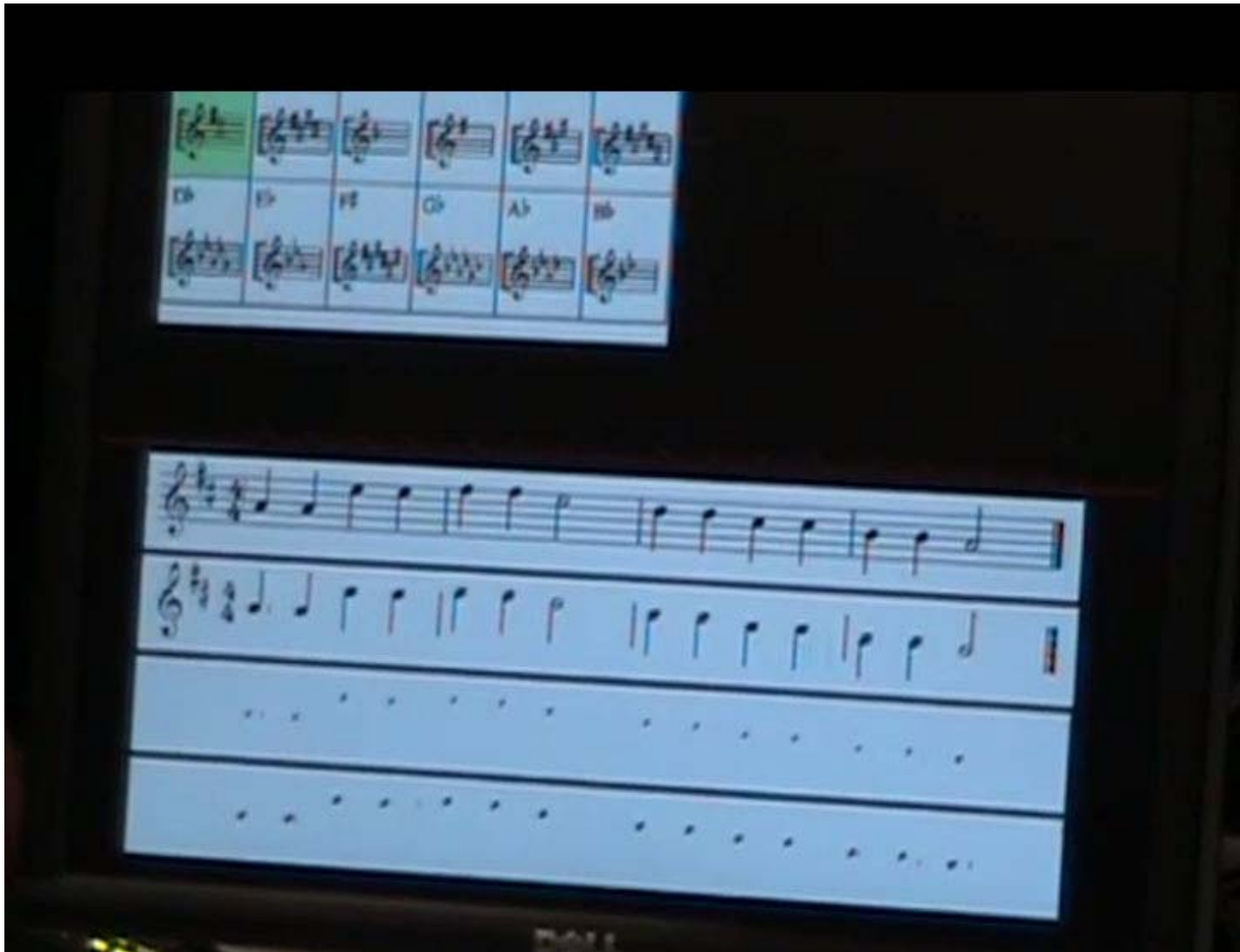

Fall 2016: Henry Love, Mark Yang

# Virtual Softball

 

Fall 2017 Katherine Shade, Melinda Szabo

# FPGA Passport



Fall 2016 Lorenzo Vigano, Diana Wofk



# Gesture Controlled Drone




Fall 2014 Lee Gross, Ben Schrenk

# Collaboration


- Labs and Ipset must be done independently but students may seek help from other students and of course staff.
- Work submitted for review must be your own

# 6.111 Topics

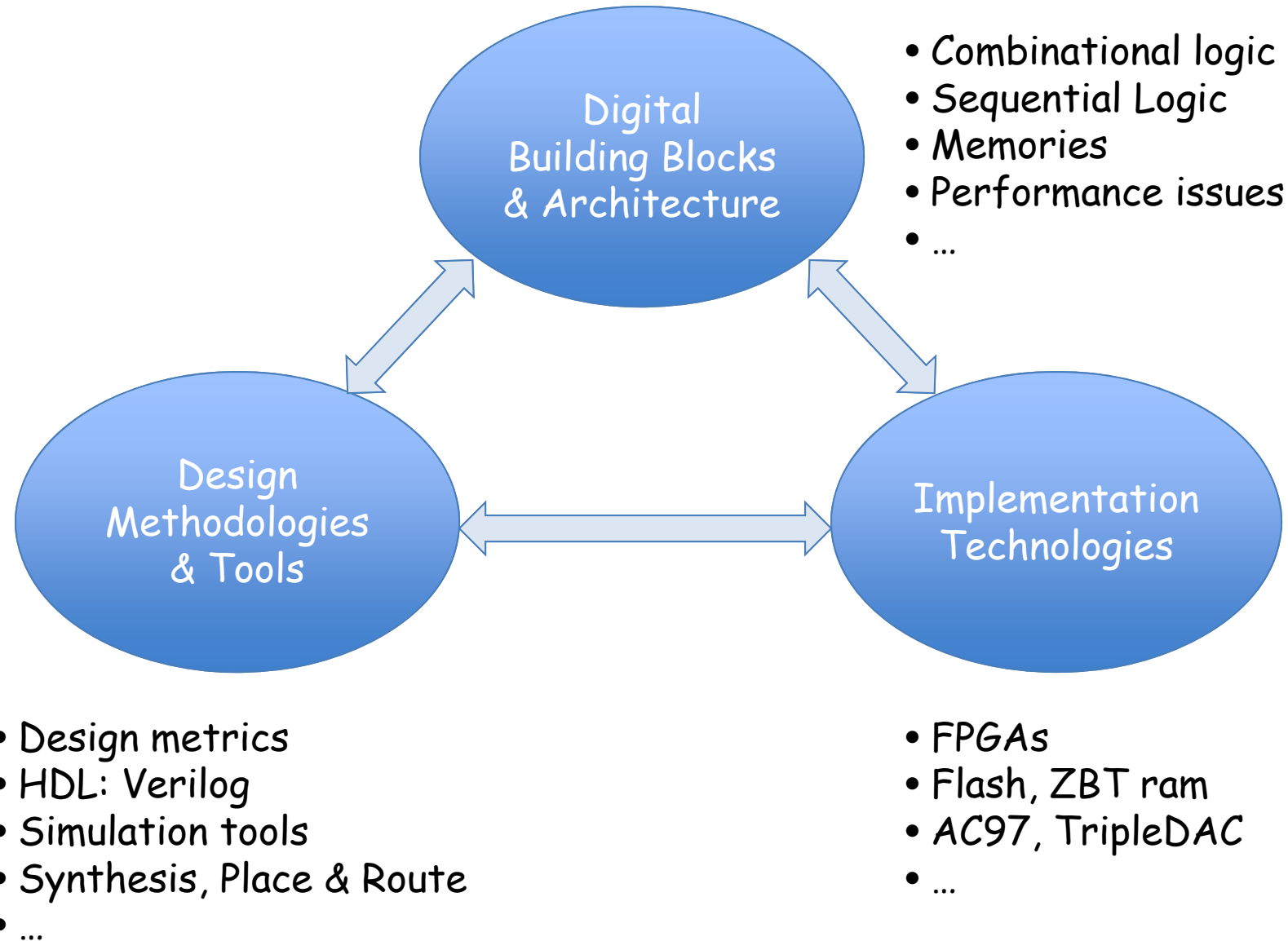




# Boolean Algebra

 


GEORGE BOOLE


AND

 

OR


 


NOT

 


- 1854: George Boole shows that **logic** is math, not just philosophy!
- Boolean algebra: the mathematics of **binary** values

# Key Link Between Logic and Circuits

  

+

 

(The Vacuum Tube)


Lee de Forest, 1906

Digital  
Electronics

- Despite existence of **relays** and introduction of **vacuum tube** in 1906, digital electronics did not emerge for thirty years!
- Claude Shannon notices similarities between Boolean algebra and electronic telephone switches
- Shannon's 1937 MIT Master's Thesis introduces the world to **binary digital electronics**

# Evolution of Digital Electronics

## Vacuum Tubes

 


ENIAC, 1946



UNIVAC, 1951

1900 adds/sec

## Transistors

 

First Transistor  
Bell Labs, 1948



IBM System/360, 1964

500,000 adds/sec

## VLSI Circuits



4004, 1971




Intel Cascade Lake  
2018 - 22 Cores  
>>7 Billion 14nm




# Digital Systems Thru the Ages


Vacuum tube  
computer  
Circa 1950

 

IBM 1401 Computer  
Circa 1962

 

DEC PDP 11  
Circa 1980

 

## 6.111 Thru the Ages




Lab kit 1990  
“digital death”




Labkit 2005

Nexys 4 - 2016

 

# 6.111 Evolution

Fall 1969

 

Fall 2018

## 6.111 Introductory Digital Systems Laboratory

U (🌱) 🧪

Prereq: 6.002 or 16.004


Units: 3-7-2

Lecture: TR2.30-4 (32-141) Lab: TBA

Introduces digital systems with lectures and labs on logic, flip flops, FPGAs, counters, timing, synchronization, and finite-state machines. Includes overview of accelerometers, gyros, time of light and other modern sensors. Prepares students for the design and implementation of a final project of their choice: games, music, digital filters, wireless communications, video, or graphics. Extensive use of Verilog for describing and implementing digital logic designs.



# The trouble with analog signaling

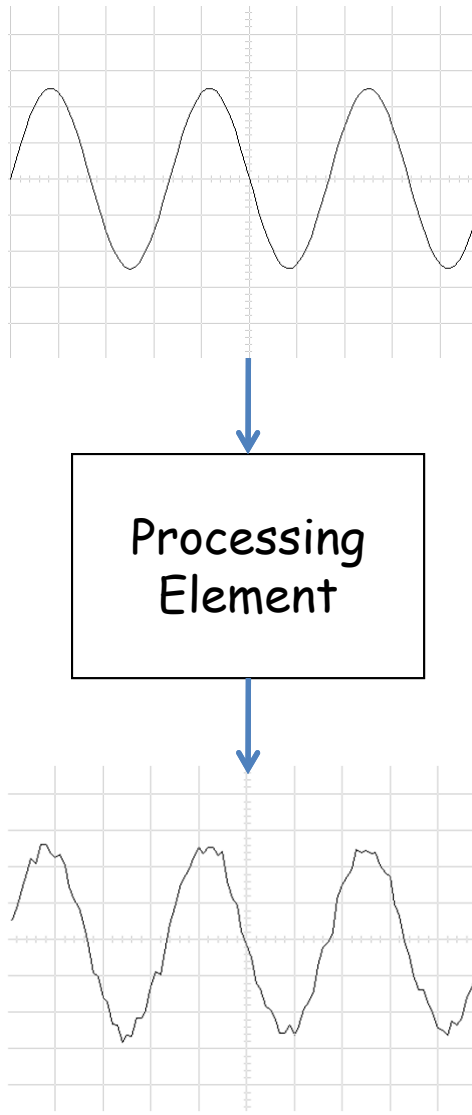


The real world is full of continuous-time continuous-value (aka “analog”) signals created by physical processes: sound vibrations, light fields, voltages and currents, phase and amplitudes, ...

But if we build processing elements to manipulate these signals we must use non-ideal components in real-world environments, so some amount of error (aka “**noise**”) is introduced. The error comes from component tolerances, electrical phenomenon (e.g., IR and  $LdI/dt$  effects), transmission losses, thermal noise, etc. Facts of life that can't be avoided...

And the more analog processing we do, the worse it gets: **signaling errors accumulate in analog systems** since we can't tell from looking at signal which wiggles were there to begin with and which got added during processing.

# Music at MIT circa 1970s

 


Need an architecture that is  
noise tolerant, inexpensive,  
reproducible.



# Solution: go digital!

Continuous values  
Continuous time

 

*So we can detect small  
changes and restore  
original values*


Discrete values  
Discrete time

*So we don't look  
while it's changing*


 
# The Digital Abstraction

Noise and inaccuracy are inevitable; we can't reliably engineer perfect components - we must **design our system to tolerate some amount of error** if it is to process information reliably.



Keep in mind that the world is not digital, we would simply like to engineer it to behave that way. Furthermore, we must use **real physical phenomena** to implement digital designs!

# Digital Encoding

To ensure we can distinguish signal from noise, we'll encode information using a fixed set of discrete values. Options are:

voltages	phase
currents	frequency

For 6.111, we'll use voltages to encode information. Current, phase and frequency encoding have uses in other applications.

Why voltage?


- easily generated, well understood
- historically used, lots of circuits
- with CMOS, almost zero power in steady state

No free lunch:

- noise sensitivity, non-ideal wires (RC time constant),

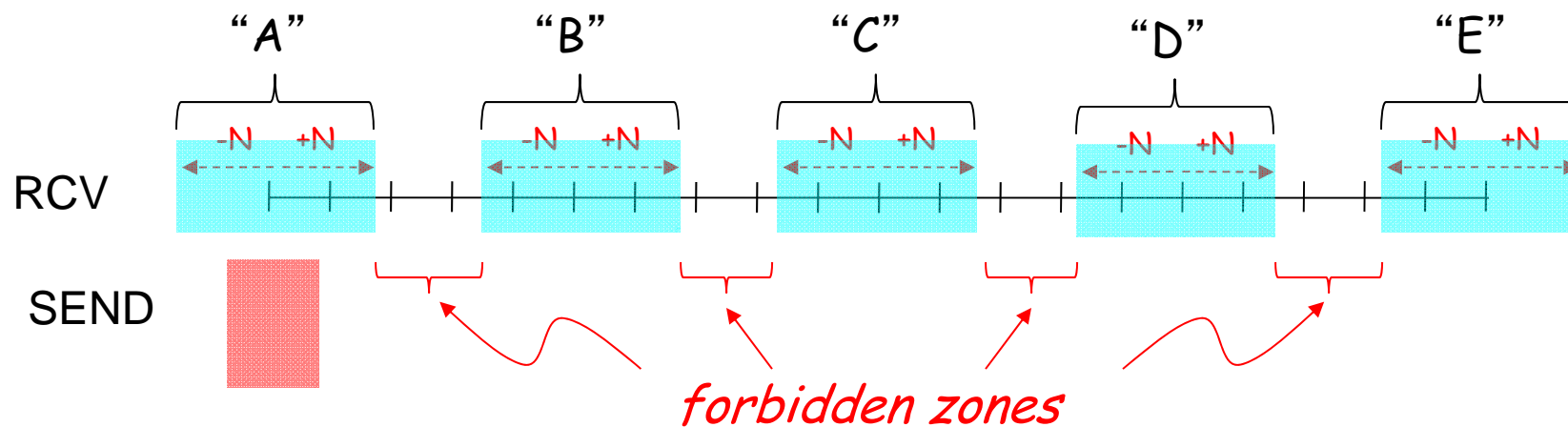
# Digital Signaling: receiving

Since the channel/wire is imperfect and we will use non-ideal components in the receiver, we require the receiver to accept a (larger) range of analog values for each symbol.



To avoid hard-to-make decisions at the boundaries between symbol representations, insert a “forbidden zone” between symbols so that some ranges of received values are not required to be mapped to a specific symbol.

# Digital processing elements

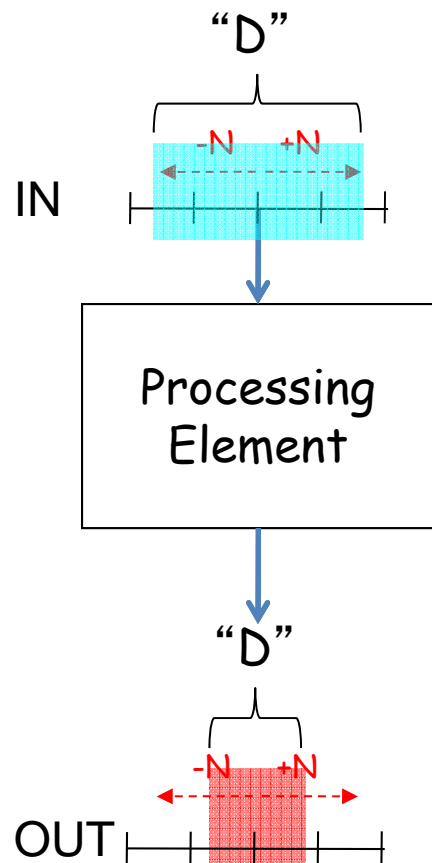


Digital processing elements *restore* noisy input values to legal output values - **signaling errors don't accumulate in digital systems**. So the number of processing elements isn't limited by noise problems!

The “trick” is that we've defined our signaling convention so that we can tell from looking at a signal which wiggles were there to begin with and which got added during processing.
 
# Using voltages to encode binary values

We'll keep things simple by designing our processing elements to use voltages to encode binary values (0 or 1). To ensure robust operation we'd like to make the noise margins as large as possible.



# Digital Signaling Specification

Digital input:  $V_{IN} < V_{IL}$  or  $V_{IN} > V_{IH}$

Digital output:  $V_{OUT} < V_{OL}$  or  $V_{OUT} > V_{OH}$

Noise margins:  $V_{IL} - V_{OL}$  and  $V_{OH} - V_{IH}$

Where  $V_{OL}$ ,  $V_{IL}$ ,  $V_{IH}$  and  $V_{OH}$  are part of the specification for a particular family of digital components.

Now that we have a way of encoding information as a signal, we can define what it means to be *digital device*.

# Sample DC (signaling) Specification

I/O Standard	$V_{IL}$		$V_{IH}$		$V_{OL}$	$V_{OH}$	$I_{OL}$	$I_{OH}$
	V, Min	V, Max	V, Min	V, Max	V, Max	V, Min	mA	mA
LVTTL	-0.3	0.8	2.0	3.45	0.4	2.4	Note(3)	Note(3)
LVC MOS33, LVDCI33	-0.3	0.8	2.0	3.45	0.4	$V_{CCO} - 0.4$	Note(3)	Note(3)
LVC MOS25, LVDCI25	-0.3	0.7	1.7	$V_{CCO} + 0.3$	0.4	$V_{CCO} - 0.4$	Note(3)	Note(3)
LVC MOS18, LVDCI18	-0.3	35% $V_{CCO}$	65% $V_{CCO}$	$V_{CCO} + 0.3$	0.45	$V_{CCO} - 0.45$	Note(4)	Note(4)
LVC MOS15, LVDCI15	-0.3	35% $V_{CCO}$	65% $V_{CCO}$	$V_{CCO} + 0.3$	25% $V_{CCO}$	75% $V_{CCO}$	Note(4)	Note(4)
LVC MOS12	-0.3	35% $V_{CCO}$	65% $V_{CCO}$	$V_{CCO} + 0.3$	25% $V_{CCO}$	75% $V_{CCO}$	Note(6)	Note(6)
PCI33_3 <sup>(5)</sup>	-0.2	30% $V_{CCO}$	50% $V_{CCO}$	$V_{CCO}$	10% $V_{CCO}$	90% $V_{CCO}$	Note(5)	Note(5)
PCI66_3 <sup>(5)</sup>	-0.2	30% $V_{CCO}$	50% $V_{CCO}$	$V_{CCO}$	10% $V_{CCO}$	90% $V_{CCO}$	Note(5)	Note(5)
PCI-X <sup>(5)</sup>	-0.2	35% $V_{CCO}$	50% $V_{CCO}$	$V_{CCO}$	10% $V_{CCO}$	90% $V_{CCO}$	Note(5)	Note(5)

Source: Xilinx Virtex 5 Datasheet



# Arduino Processor DC Specification

## 32.2. Common DC Characteristics

Table 32-2. Common DC characteristics  $T_A = -40^\circ\text{C}$  to  $105^\circ\text{C}$ ,  $V_{CC} = 1.8\text{V}$  to  $5.5\text{V}$  (unless otherwise noted)


Symbol	Parameter	Condition	Min.	Typ.	Max.	Units
$V_{IL}$	Input Low Voltage, except XTAL1 and $\overline{\text{RESET}}$ pin	$V_{CC} = 1.8\text{V} - 2.4\text{V}$	-0.5		$0.2V_{CC}^{(1)}$	V
		$V_{CC} = 2.4\text{V} - 5.5\text{V}$	-0.5		$0.3V_{CC}^{(1)}$	
$V_{IH}$	Input High Voltage, except XTAL1 and $\overline{\text{RESET}}$ pins	$V_{CC} = 1.8\text{V} - 2.4\text{V}$	$0.7V_{CC}^{(2)}$		$V_{CC} + 0.5$	V
		$V_{CC} = 2.4\text{V} - 5.5\text{V}$	$0.6V_{CC}^{(2)}$		$V_{CC} + 0.5$	
$V_{OL}$	Output Low Voltage <sup>(4)</sup> except $\overline{\text{RESET}}$ pin	$I_{OL} = 20\text{mA}$ , $V_{CC} = 5\text{V}$	$T_A = 85^\circ\text{C}$		0.9	V
			$T_A = 105^\circ\text{C}^{(5)}$		1.0	V
		$I_{OL} = 10\text{mA}$ , $V_{CC} = 3\text{V}$	$T_A = 85^\circ\text{C}$		0.6	V
			$T_A = 105^\circ\text{C}^{(5)}$		0.7	V
$V_{OH}$	Output High Voltage <sup>(3)</sup> except Reset pin	$I_{OH} = -20\text{mA}$ , $V_{CC} = 5\text{V}$	$T_A = 85^\circ\text{C}$	4.2		V
			$T_A = 105^\circ\text{C}^{(5)}$	4.1		V
		$I_{OH} = -10\text{mA}$ , $V_{CC} = 3\text{V}$	$T_A = 85^\circ\text{C}$	2.3		V
			$T_A = 105^\circ\text{C}^{(5)}$	2.1		V

Source: ATmega328P Datasheet
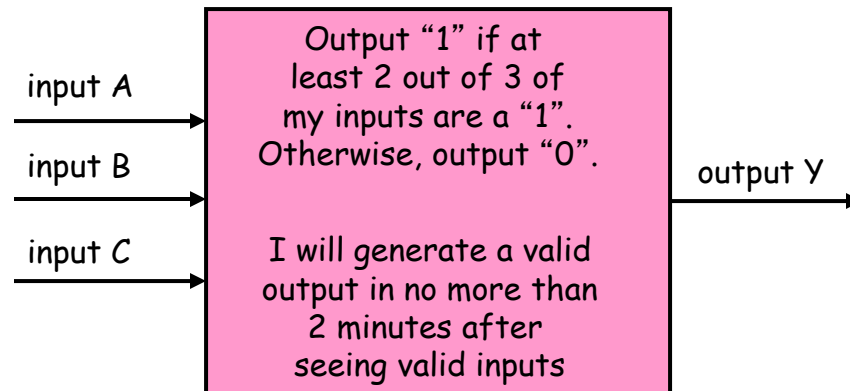
# A Digital Processing Element

A *combinational device* is a processing element that has

- Static discipline {
- one or more digital *inputs*
  - one or more digital *outputs*
  - a *functional specification* that details the value of each output for every possible combination of valid input values
  - a *timing specification* consisting (at minimum) of an upper bound  $t_{pd}$  on the required time for the device to compute the specified output values from an arbitrary set of stable, valid input values
- One of two discrete values




# Why have processing blocks?

- The goal of modular design:
 
## ABSTRACTION


- What does that mean anyway:
  - Rules simple enough for a 6-3 to follow...
  - Understanding BEHAVIOR without knowing IMPLEMENTATION
  - Predictable composition of functions
  - Tinker-toy assembly
  - Guaranteed behavior under REAL WORLD circumstances



# A Combinational Digital System

- A set of interconnected elements is a *combinational device* if
  - each circuit element is a combinational device
  - every input is connected to exactly one output or a constant (e.g., some vast supply of 0's and 1's)
  - the circuit contains no directed cycles
- Why is this true?
  - Given an acyclic circuit meeting the above constraints, we can derive functional and timing specs for the input/output behavior from the specs of its components!
  - We'll see lots of examples soon. But first, we need to build some combinational devices to work with...

# Example Device: An Inverter

 

0  $\rightarrow$  1

1  $\rightarrow$  0



**Voltage Transfer Characteristic:**  
Plot of  $V_{OUT}$  vs.  $V_{IN}$  where each measurement is taken after any transients have died out.

*Note: VTC does not tell you anything about how fast a device is—it measures static behavior not dynamic behavior*

Static Discipline requires that we avoid the shaded regions (aka “forbidden zones”), which correspond to *valid* inputs but *invalid* outputs. Net result: combinational devices must have **GAIN**  $> 1$  and be **NONLINEAR**.





$$\frac{\partial V_{OUT}}{\partial V_{IN}}$$

# Combinational Device Wish List

  


- ✓ Design our system to tolerate some amount of error
  - ⇒ Add positive noise margins
  - ⇒ VTC: gain > 1 & nonlinearity
- ✓ Lots of gain ⇒ big noise margin
- ✓ Cheap, small
- ✓ Changing voltages will require us to dissipate power, but if no voltages are changing, we'd like zero power dissipation
- ✓ Want to build devices with useful functionality (what sort of operations do we want to perform?)

# Wishes Granted: CMOS

    

# MOSFETS: Gain & Non-linearity

 



MOSFETs (metal-oxide-semiconductor field-effect transistors) are four-terminal voltage-controlled switches. Current flows between the diffusion terminals if the voltage on the gate terminal is large enough to create a conducting "channel", otherwise the mosfet is off and the diffusion terminals are not connected.



 
# Digital Integrated Circuits

IBM photomicrograph ( $\text{SiO}_2$  has been removed!)




 

# Moore's Forever?

 

# Functional Specifications

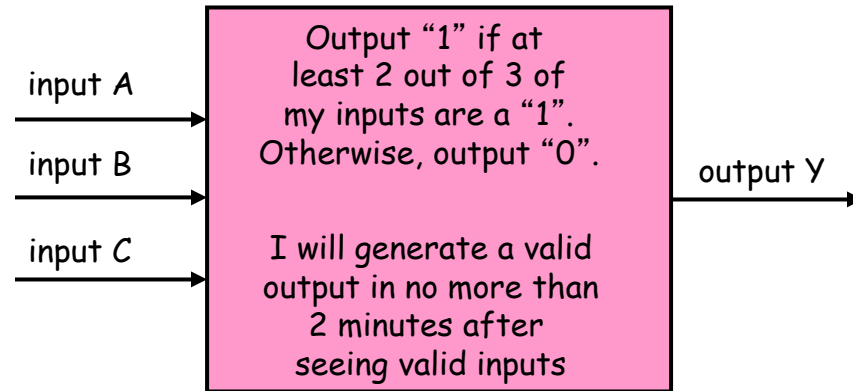


A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

*3 binary inputs  
so  $2^3 = 8$  rows in our truth table*

An concise, unambiguous technique for giving the functional specification of a combinational device is to use a *truth table* to specify the output value for each possible combination of input values (N binary inputs  $\rightarrow 2^N$  possible combinations of input values).
 
# Timing Specifications

**Propagation delay ( $t_{PD}$ ):** An upper bound on the delay from valid inputs to valid outputs (aka “ $t_{PD,MAX}$ ”)




Design goal:  
*minimize*  
propagation  
delay
 
# Contamination Delay

*an optional, additional timing spec*

Contamination delay( $t_{CD}$ ): A lower bound on the delay from invalid inputs to invalid outputs (aka “ $t_{PD,MIN}$ ”)





Do we really need  $t_{CD}$ ?

Usually not... it'll be important when we design circuits with registers (coming soon!)

If  $t_{CD}$  is not specified, safe to assume it's 0.

# The Combinational Contract

  


Note:

1. *No Promises* during **XXXXXX**
2. Default (conservative) spec:  $t_{CD} = 0$
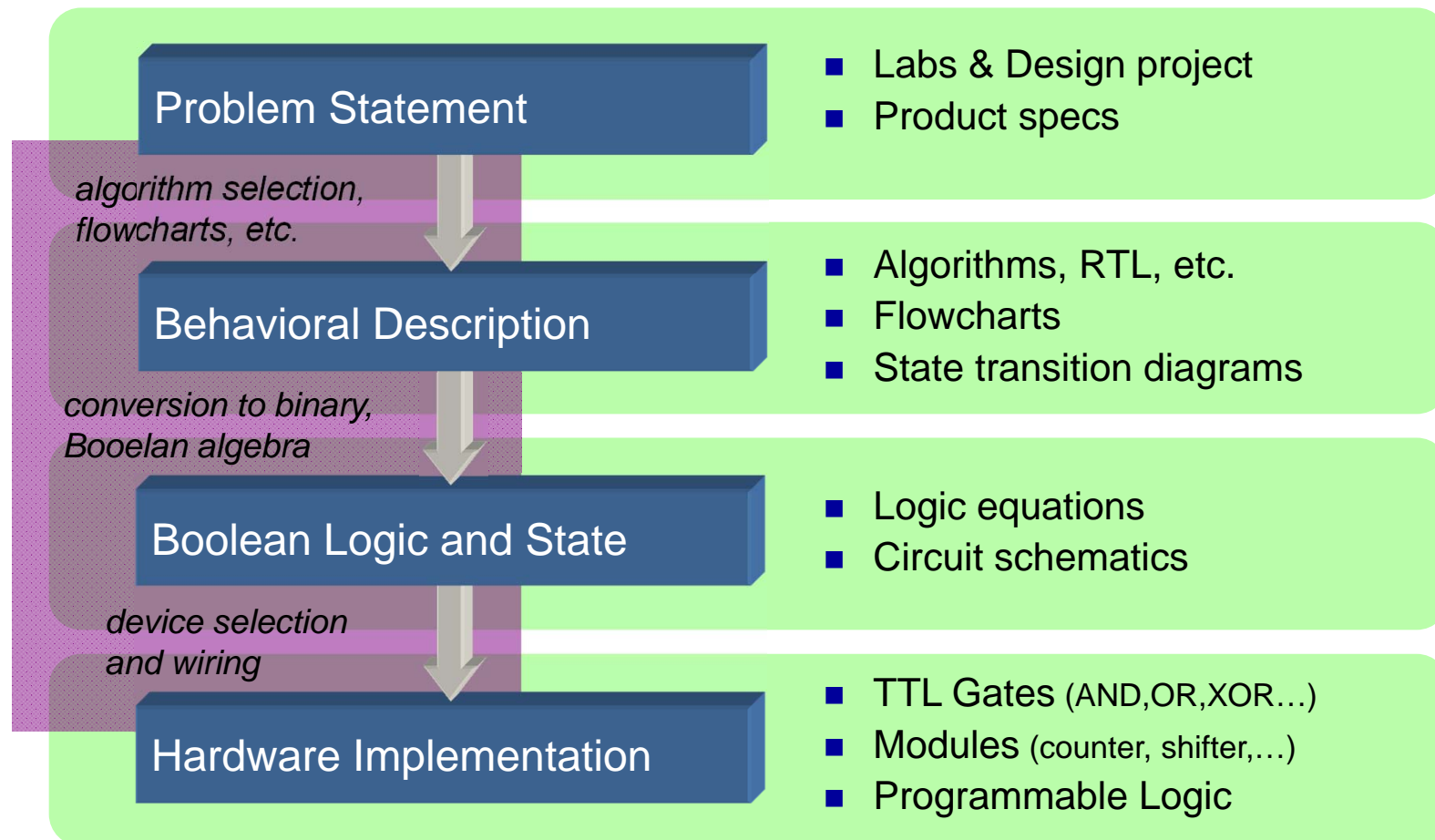
# Building Digital Systems


- Goal of 6.111: Building binary digital solutions to computational problems




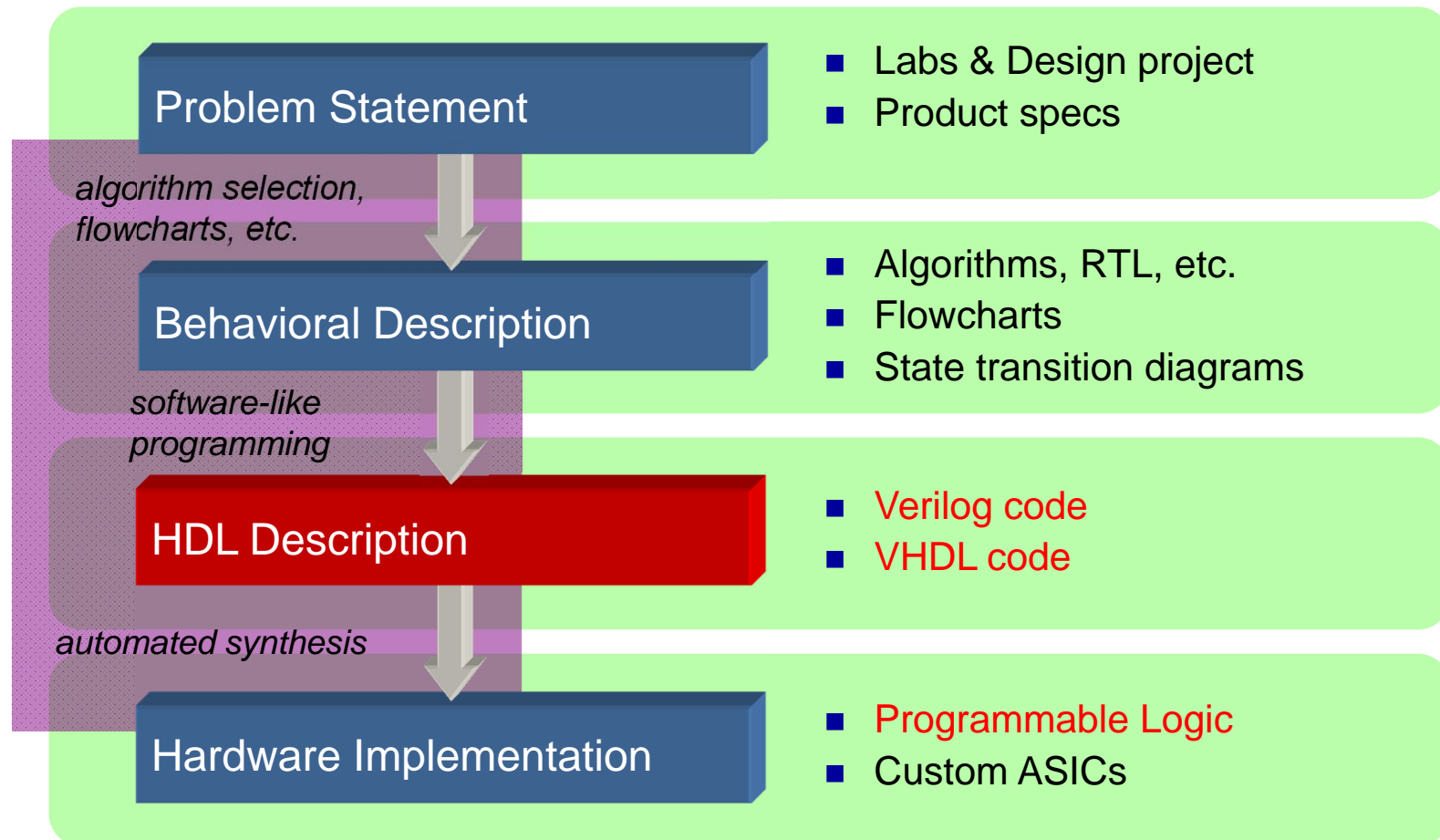
# Building Digital Systems with HDLs

- Logic synthesis using a Hardware Description Language (HDL) automates the most tedious and error-prone aspects of design



# Verilog and VHDL

## VHDL

- Commissioned in 1981 by Department of Defense; now an IEEE standard
- Initially created for ASIC synthesis
- Strongly typed; potential for verbose code
- Strong support for package management and large designs

## Verilog

- Created by Gateway Design Automation in 1985; now an IEEE standard
- Initially an interpreted language for gate-level simulation
- Less explicit typing (e.g., compiler will pad arguments of different widths)
- No special extensions for large designs


Hardware structures can be modeled effectively in either VHDL and Verilog. Verilog is similar to c and a bit easier to learn.

# Verilog HDL

- Misconceptions
  - The coding style or clarity does not matter as long as it works
  - Two different Verilog encodings that simulate the same way will synthesize to the same set of gates
  - Synthesis just can't be as good as a design done by humans
    - Shades of assembly language versus a higher level language
- What can be Synthesized
  - Combinational Functions
    - Multiplexors, Encoders, Decoders, Comparators, Parity Generators, Adders, Subtractors, ALUs, Multipliers
    - Random logic
  - Control Logic
    - FSMs
- What can't be Synthesized
  - Precise timing blocks (e.g., delay a signal by 2ns)
  - Large memory blocks (can be done, but very inefficient)
- Understand what constructs are used in simulation vs. hardware mapping
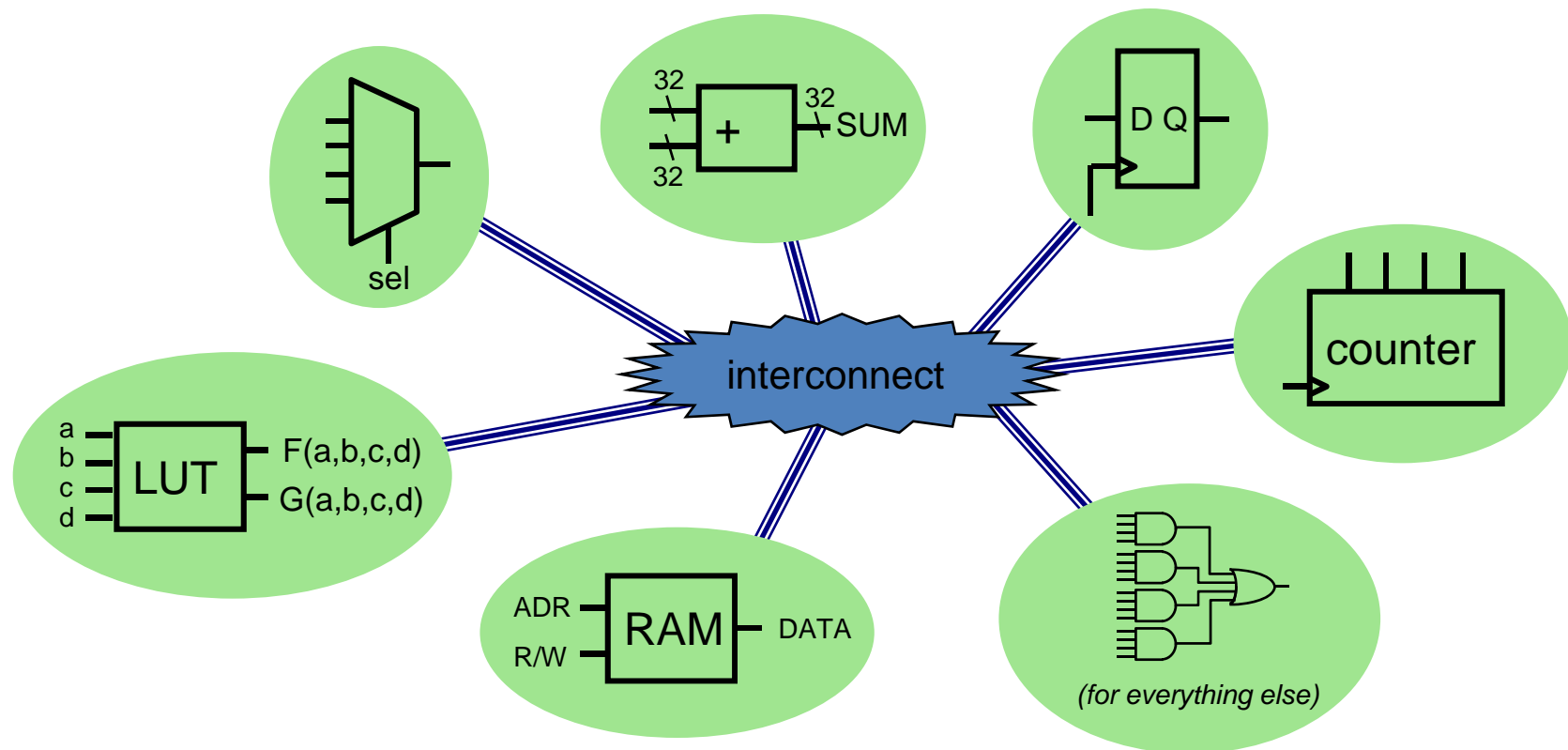
# The FPGA: A Conceptual View

- An FPGA is like an electronic breadboard that is wired together by an automated **synthesis tool**
- Built-in components are called **macros**




# Synthesis and Mapping for FPGAs

- Infer macros: choose the FPGA macros that efficiently implement various parts of the HDL code

```
...  
always @ (posedge clk)  
begin  
    count <= count + 1;  
end  
...
```


*HDL Code*

 *"This section of code looks like a counter. My FPGA has some of those..."*



*Inferred Macro*

 - Place-and-route: with area and/or speed in mind, choose the needed macros by location and route the interconnect



*"This design only uses 10% of the FPGA. Let's use the macros in one corner to minimize the distance between blocks."*

# Summary

- Use voltages to encode information
- “Digital” encoding
  - valid voltage levels for representing “0” and “1”
  - forbidden zone avoids mistaking “0” for “1” and vice versa
- Noise
  - Want to tolerate real-world conditions: NOISE.
  - Key: tougher standards for output than for input
  - devices must have gain and have a non-linear VTC
- Combinational devices
  - Each logic family has Tinkertoy-set simplicity, modularity
  - predictable composition: “parts work → whole thing works”
  - static discipline
    - digital inputs, outputs; restore marginal input voltages
    - complete functional spec, e.g., a truth table
    - valid inputs lead to valid outputs in bounded time ( $< t_{PD}$ )

# Tektronix Logic Analyzer -Demo

- 4 Sets of 16 channels plus clock = 68 channels
- Align probes with flying leads correctly
- Screen capture
- redundant keyboard/cursor/mouse controls
- cursor1/2 locator
- fastest sampling rate is 2ghz, magna view is 8ghz
- sampling can be clocked externally or internally (select judiciously)
- triggering modes - simple events, complex multiple events
- waveforms - customize via right mouse click: expand channels, change radix, rename, delete, add ...
- Future labs will have LA directly connected via analyzer ports.



# Hand in Background Information