

Sequential Logic

Reminders:

- LPSet #4 Due Thursday (short)
- Lab #2 due Friday

Stuff for Today

- Digital state: the D-Register
- Timing constraints for D-Registers
- Specifying registers in Verilog
- Blocking and nonblocking assignments
- Examples



Companies at Career Fair!!

Seriously Apple Anecdote

Lpset 2: Q1

- Parts are only guaranteed to meet *min/max specs – not typical*
- Lpset 2a: “As a design engineer using good engineering practice, what would you specify as the maximum data transfer rate to be published in a “labkit datasheet”? Ans: 150kps

6.8 Switching Characteristics: Driver

over operating free-air temperature range (unless otherwise noted)⁽¹⁾. See [Figure 8](#).

PARAMETER	TEST CONDITIONS	MIN	TYP ⁽²⁾	MAX	UNIT
Maximum data rate	$C_L = 1000 \text{ pF}$, $R_L = 3 \text{ k}\Omega$, One DOUT switching, see Figure 3	150	250		kbps
$t_{sk(p)}$ Pulse skew ⁽³⁾	$C_L = 150 \text{ pF}$ to 2500 pF , $R_L = 3 \text{ k}\Omega$ to $7 \text{ k}\Omega$, see Figure 4		300		ns

- Typical values acceptable for prototyping, testing
- Lpset 2b: 250kps

Lpset 2 Q1: Datasheet Specs

- Understand voltage margins between families

- Vcc max3222: 3.3 or 5v; CH340g: 3.3 or 5v

- Input/out voltages

max3222



6.6 Electrical Characteristics: Driver

over operating free-air temperature range (unless otherwise noted)⁽¹⁾. See Figure 8.

	PARAMETER	TEST CONDITIONS	MIN	TYP ⁽²⁾	MAX	UNIT
V _{OH}	High-level output voltage	DOUT at R _L = 3 kΩ to GND, DIN = GND	5	5.4		V
V _{OL}	Low-level output voltage	DOUT at R _L = 3 kΩ to GND, DIN = V _{CC}	-5	-5.4		V

3.2. DC characteristics CH340g

Symbol	Name		Minimum	Typical	Maximum	Unit
V _{CC}	Supply rail voltage	5V operation	4.5	5	5.5	V
		3.3V operation	3.3	3.3	3.8	
I _{CC}	Operating current			12	30	mA
I _{SLP}	Sleeping current	5V operation		150	200	μA
		3.3V operation		50	80	
V _{IL}	Low input voltage		-0.5		0.7	V
V _{IH}	High input voltage		2.0		V _{CC} +0.5	V
V _{OL}	Low output voltage				0.5	V
V _{OH}	High output voltage		V _{CC} -0.5			V

Module Instantiation

Use Explicit Port Declarations

```
module mux32two
    (input [31:0] i0,i1,
     input sel,
     output [31:0] out);

    assign out = sel ? i1 : i0;
endmodule
```

```
mux32two    adder_mux(.i0(b), .i1(32'd1),
                    .sel(f[0]), .out(addmux_out));
```

```
mux32two    adder_mux(b, 32'd1, f[0], addmux_out);
```

Order of the ports matters in this second example!

Top-Level ALU Declaration

- Given submodules:

```
module mux32two(i0,i1,sel,out);
module mux32three(i0,i1,i2,sel,out);
module add32(i0,i1,sum);
module sub32(i0,i1,diff);
module mul16(i0,i1,prod);
```

- Declaration of the ALU Module:

```
module alu
  (input [31:0] a, b,
   input [2:0] f,
   output [31:0] r);
```

```
  wire [31:0] submux_out;
  wire [31:0] add_out, sub_out, mul_out;
```


```
  mux32two      sub_mux (b, 32'd1, f[0], submux_out);
  add32         our_adder(a, addmux_out, add_out);
  sub32         our_subtractor(a, submux_out, sub_out);
  mul16         our_multiplier(a[15:0], b[15:0], mul_out);
  mux32three    output_mux(add_out, sub_out, mul_out, f[2:1], r);
```

```
endmodule
```

module
names

(unique)
instance
names

corresponding
wires/regs in
module alu

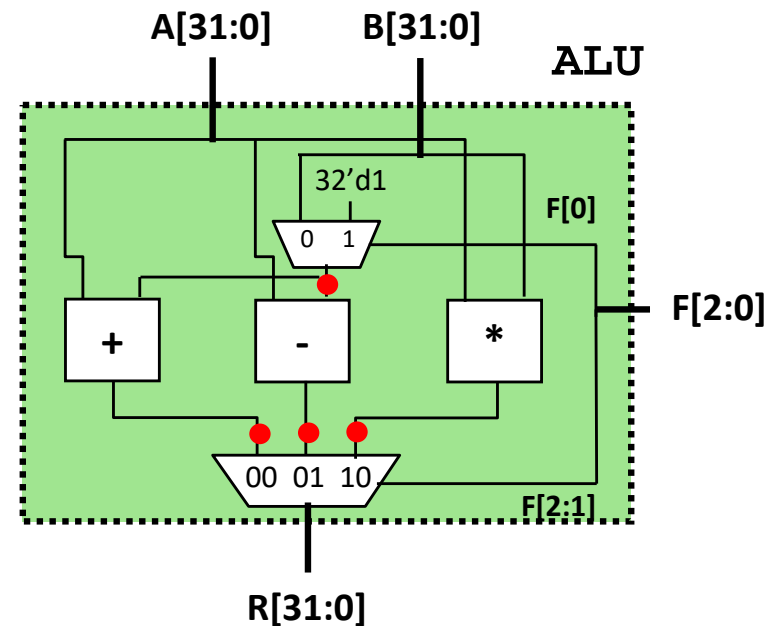

intermediate output nodes

Verilog Thoughts: Parameters

- Verilog – Hardware description language – not software program.
- Can use parameters sort of like localized constants and those can be used to specify things like widths of ports, etc...
- A convention: lowercase for variables, UPPERCASE for parameters

```
module blob
    #(parameter WIDTH = 64, // default width: 64 pixels
        HEIGHT = 64, // default height: 64 pixels
        COLOR = 3'b111) // default color: white
    (input [10:0] x,hcount, input [9:0] y,vcount, output reg [2:0] pixel);
    //stuff
endmodule
```

- Wires:

```
wire a,b,z;           // three 1-bit wires
wire [31:0] memdata;   // a 32-bit bus
wire [7:0] b1,b2,b3,b4; // four 8-bit buses
wire [WIDTH-1:0] input; // parameterized bus
```

Example Usage:

```
module tb;
  reg [7:0] D;
  reg clk;
  wire [7:0] Q;
  my_blob #(.WIDTH(8)) blobby(.D(D),.Q(Q),.clk(clk));
  initial begin
    $display("%b", Q);
    #10
    D <= 8'b10101010;
    clk <= 1'b1;
    #10
    $display("%b", Q);
  end
endmodule
```

```
module my_blob(clk,D,Q);
  parameter WIDTH=2;
  input [WIDTH-1:0] D;
  input clk;
  output [WIDTH:0] Q;
  assign Q=D;
endmodule
```

OUTPUT

```
XXXXXXXXX
10101010
```


Verilog Thoughts:

- Parameter Examples:

```
parameter MSB = 7; // defines msb as a constant value 7

parameter E = 25, F = 9; // defines two constant numbers

parameter BYTE_SIZE = 8,
        BYTE_MASK = BYTE_SIZE - 1;


parameter [31:0] DEC_CONST = 1'b1; // value converted to 32 bits

parameter NEWCONST = 3'h4; // implied range of [2:0]

parameter NEWCONS = 4; // implied range of at least [31:0]
```

Something We Cannot Build (Yet)

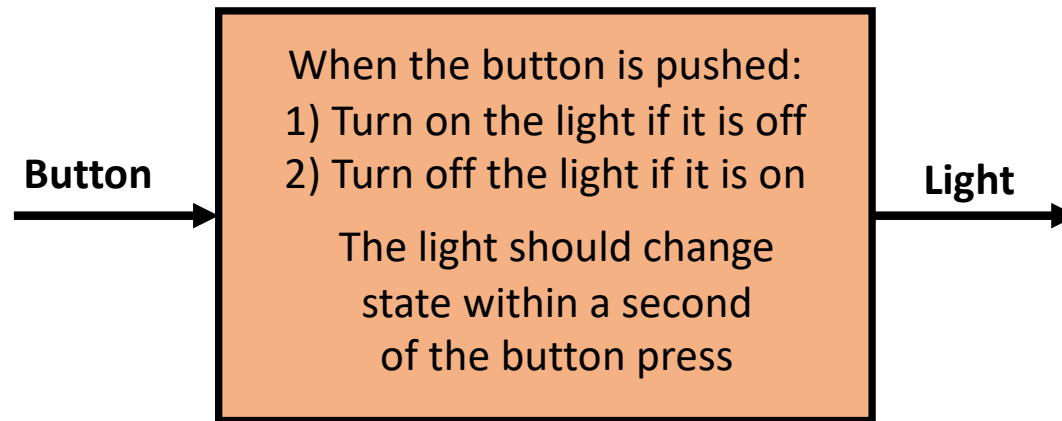
What if you were given the following design specification:



What makes this circuit so different from those we've discussed before?

1. **"State"** – i.e. the circuit has memory (become "state-ful")
2. The output was changed by a input "event" (pushing a button) rather than an input "value"

Digital State

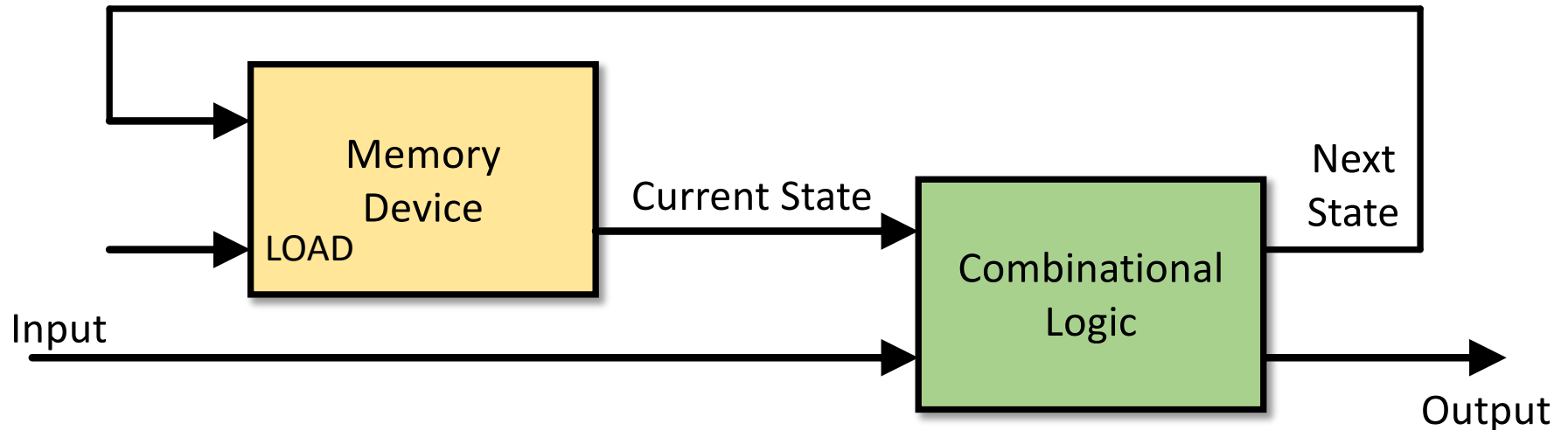

Plan: Build a Sequential Circuit with stored digital STATE –

- Memory stores CURRENT state, produced at output
- Combinational Logic computes:
 - NEXT state (from input, current state)
 - OUTPUT bit (from input, current state)
- State changes on LOAD control input

*When Output depends on input and current state, circuit is called a **Mealy** machine. If Output depends only on the current state, circuit is called a **Moore** machine.*

A New Building Block: the D Register

- The edge-triggered D register:
on the rising edge of CLK, the value of D is saved in the register and then appears shortly afterward on Q.



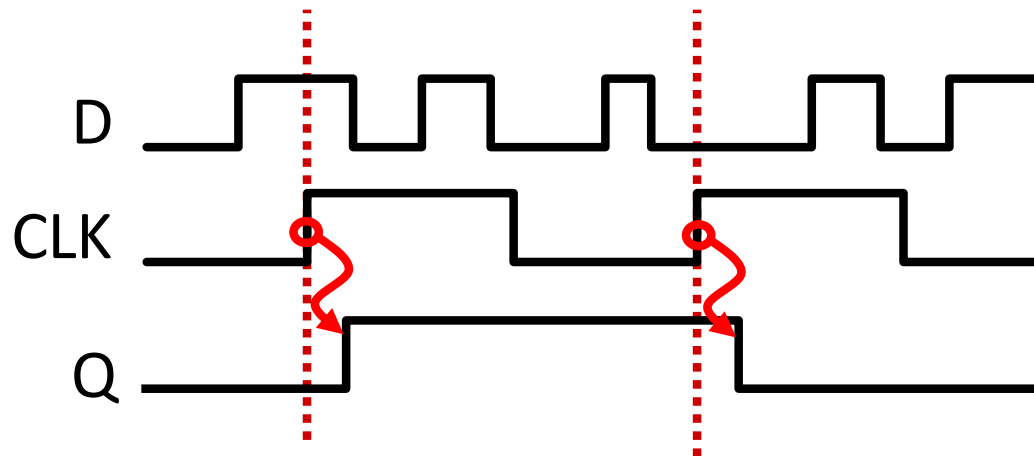
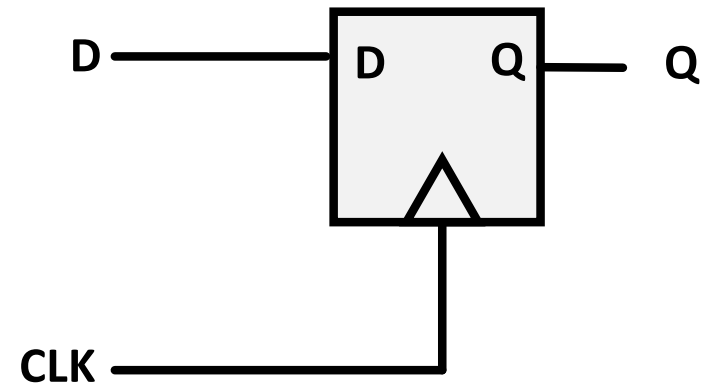


Table of truth:

clk	D	Q	\overline{Q}
0	0	Q	\overline{Q}
0	1	Q	\overline{Q}
1	0	0	1
1	1	1	0

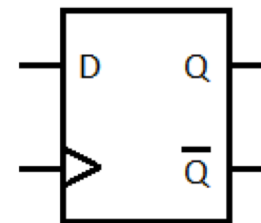

D-Register Timing 1

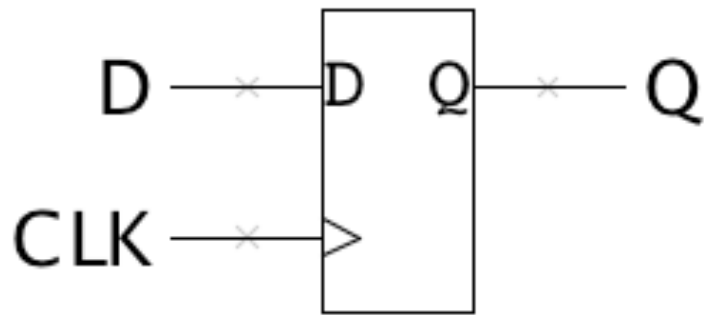

IMPORTANT:

t_{PD} : maximum propagation delay, CLK \rightarrow Q


t_{CD} : minimum contamination delay, CLK \rightarrow Q

t_{SETUP} : setup time




How long D must be stable before the rising edge of CLK

t_{HOLD} : hold time

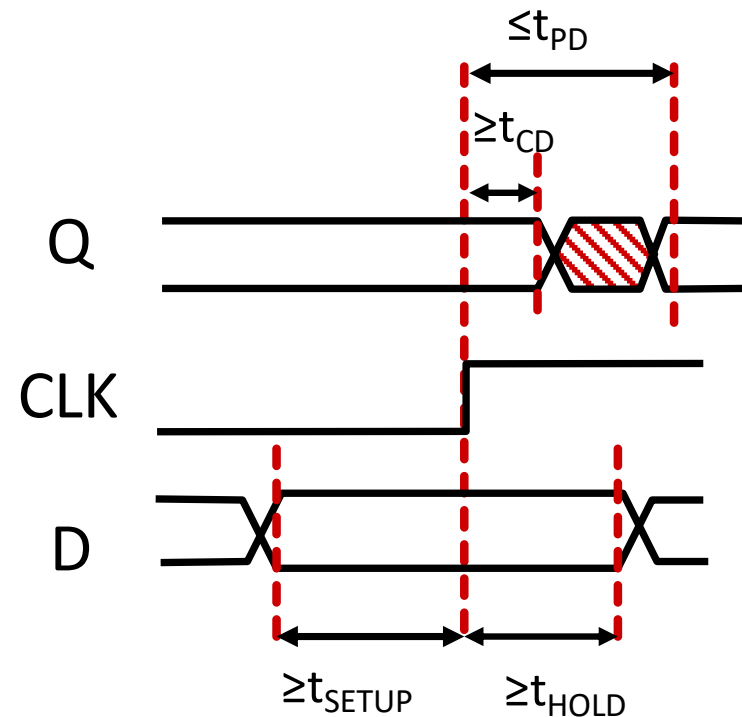How long D must be stable after the rising edge of CLK



D-Register Internals (74LS74)

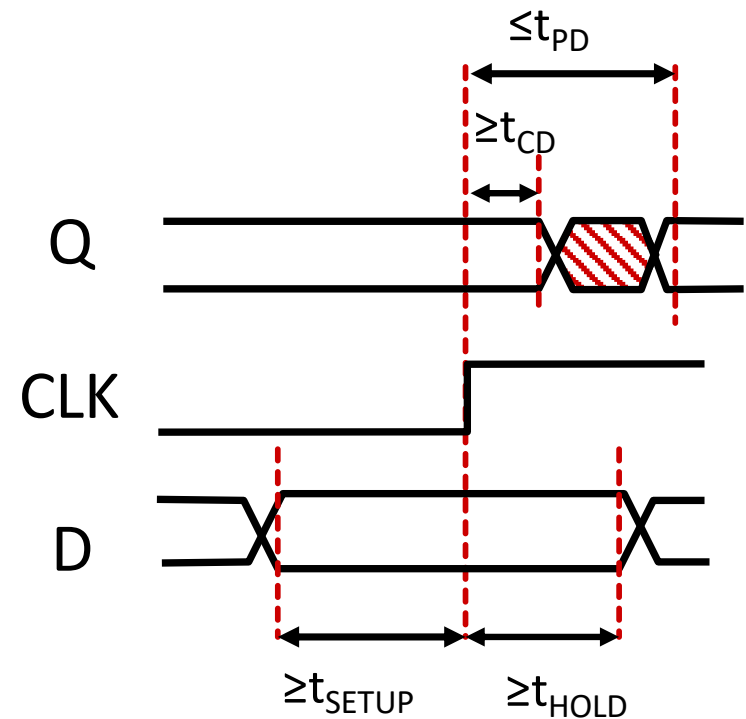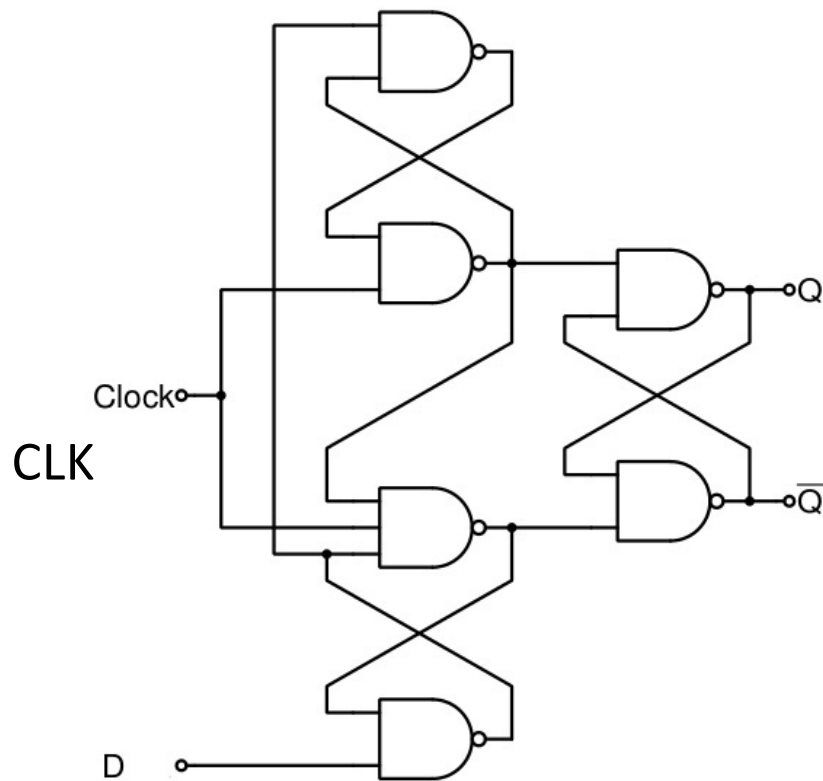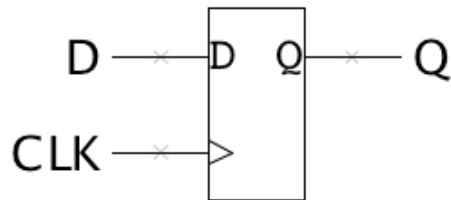



$$t_{SETUP} = 20\text{ns}$$

$$t_{PD-HL} = 40\text{ns}$$

$$t_{HOLD} = 5\text{ns}$$

$$t_{PD-LH} = 25\text{ns}$$

D-Register Timing 2

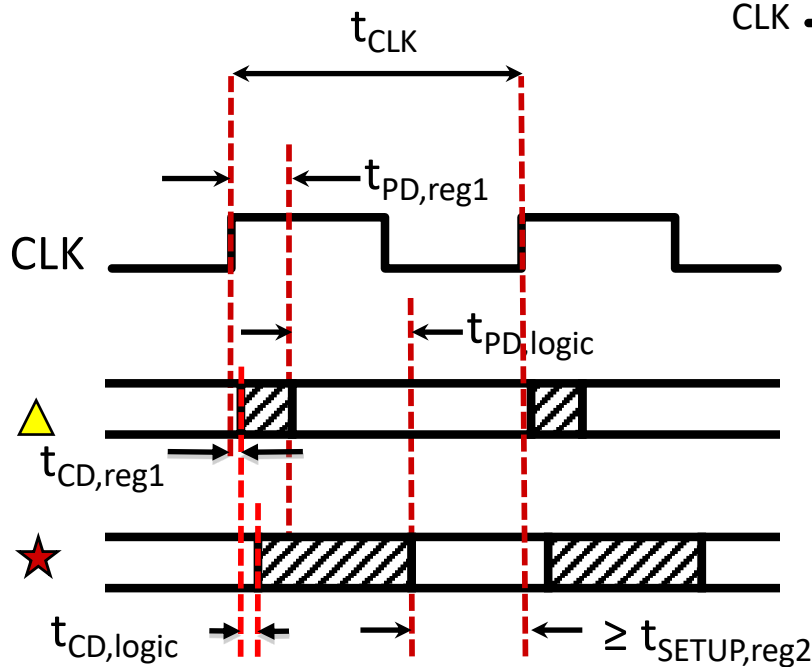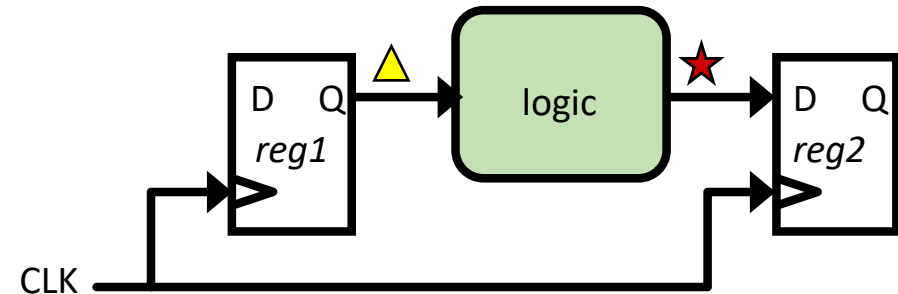

$$t_{PD,reg1} + t_{PD,logic} + t_{SETUP,reg2} \leq t_{CLK}$$


The good news: you can choose t_{CLK} so that this constraint is satisfied!


$$t_{CD,reg1} + t_{CD,logic} \geq t_{HOLD,reg2}$$

The bad news: you have to change your design if this constraint isn't met.

Single-Clock Synchronous Circuits

- Let's use registers in a highly constrained way to build digital systems


Register = 

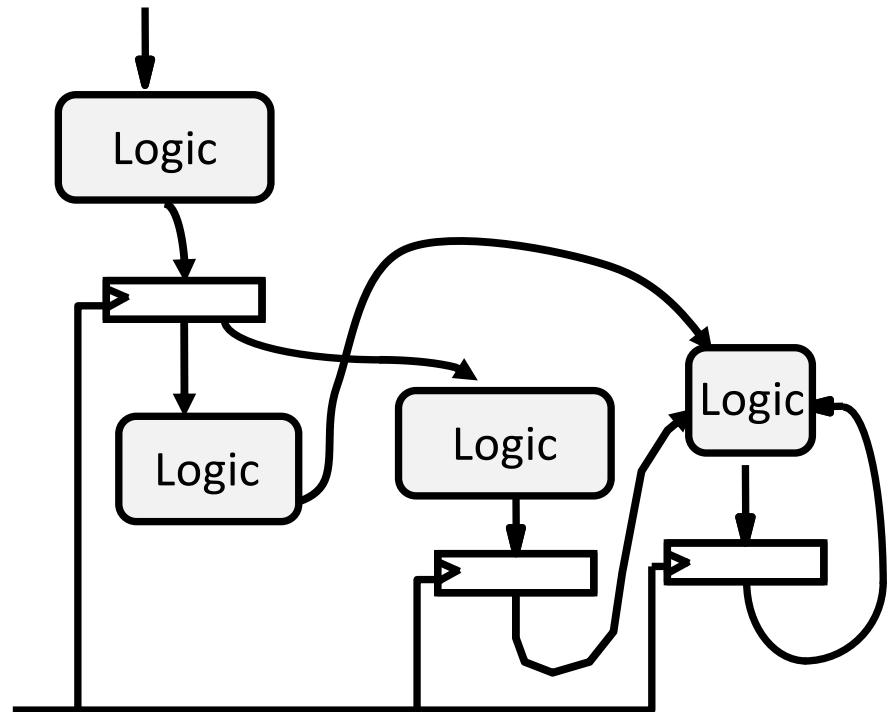


Single-Clock Synchronous Discipline:

- No combinational Cycles
- Single Clock signal shared among all clocked devices (one clock domain)
- Only care about the value of combinational circuits just before rising edge of clock
- Clock period greater than every combinational delay
- Change saved state after noise-inducing logic changes have stopped!


Clocks are Not Perfect: Clock Skew

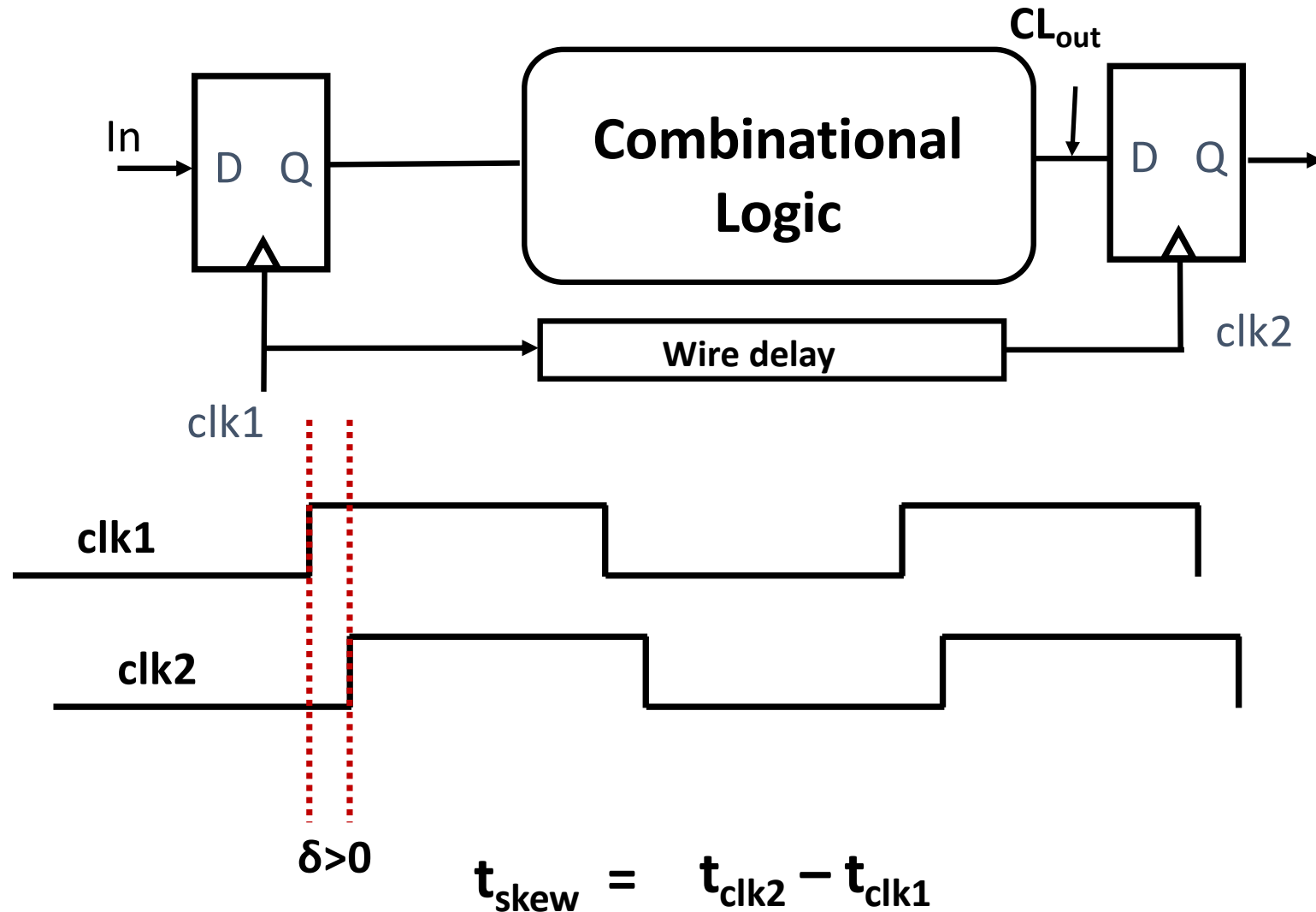

Positive and Negative Skew

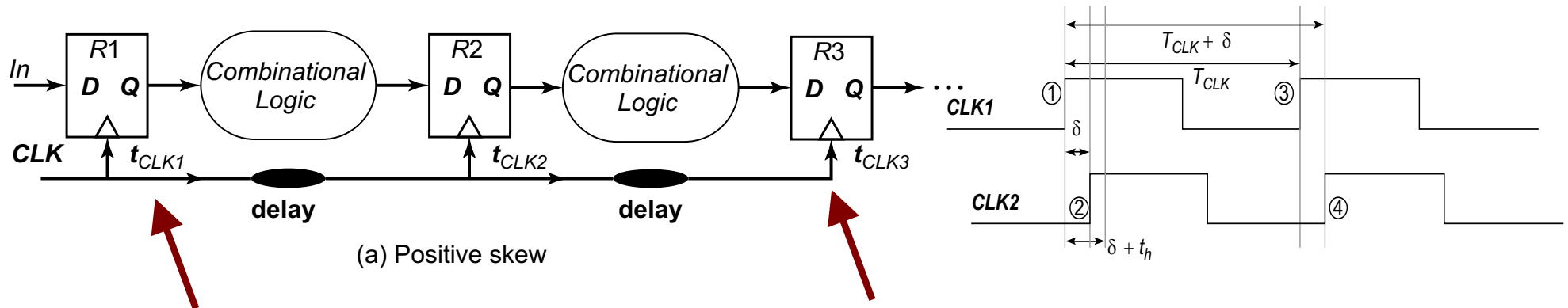

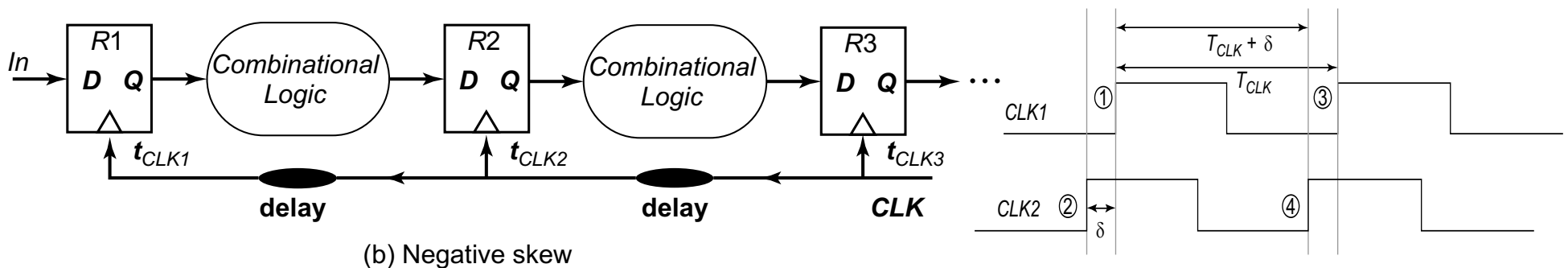
Launching edge arrives before the receiving edge (positive skew)



Receiving edge arrives before the launching edge (negative skew)

➤ Adapted from J. Rabaey, A. Chandrakasan, B. Nikolic,
 “Digital Integrated Circuits: A Design Perspective” Copyright 2003 Prentice Hall/Pearson.

D-Register Timing With Skew

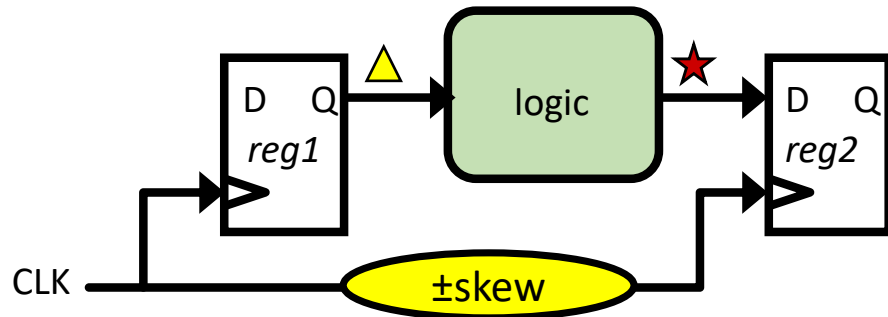

In the real world the clock signal arrives at different registers at different times. The difference in arrival times (pos or neg) is called the *clock skew* t_{skew} .

$$t_{skew} = t_{Rn,clk2} - t_{Rn,clk1}$$

We can update our two timing constraints to reflect the worst-case skew

Setup time: $t_{Rn,clk} = t_{Rn+1,clk}$

$$t_{Rn,clk1} + t_{PD,reg1} + t_{PD,logic} + t_{SETUP,reg2} \leq t_{Rn+1,clk2}$$

$$t_{PD,reg1} + t_{PD,logic} + t_{SETUP,reg2} \leq t_{CLK} + t_{skew}$$


Hold time:

$$t_{Rn,clk1} + t_{CD,reg1} + t_{CD,logic} \geq t_{Rn,clk2} + t_{HOLD,reg2}$$

$$t_{CD,reg1} + t_{CD,logic} \geq t_{HOLD,reg2} + t_{skew}$$

Thus clock skew increases the minimum cycle time of our design and makes it harder to meet register hold times.


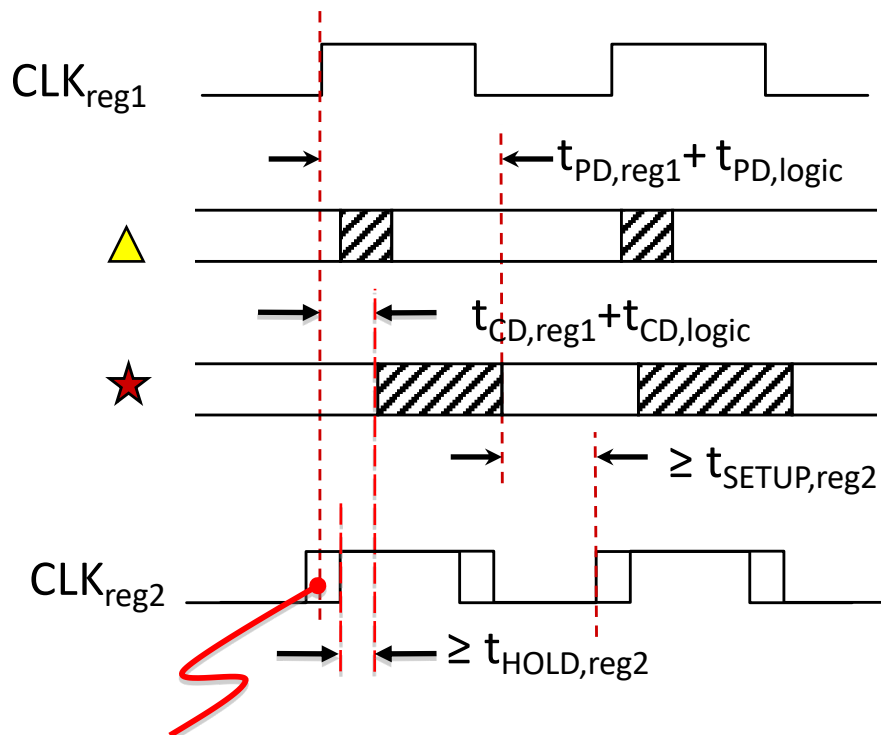
Which skew is tougher to deal with (pos or neg)?




CLK_{reg2} rising edge might fall anywhere in this region.

Delay Estimation: Simple RC Networks


Simple CMOS Circuit

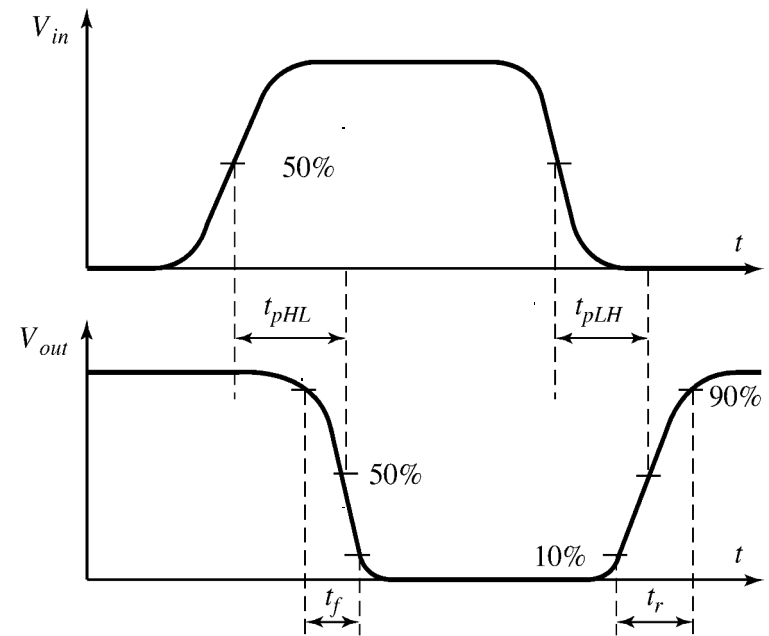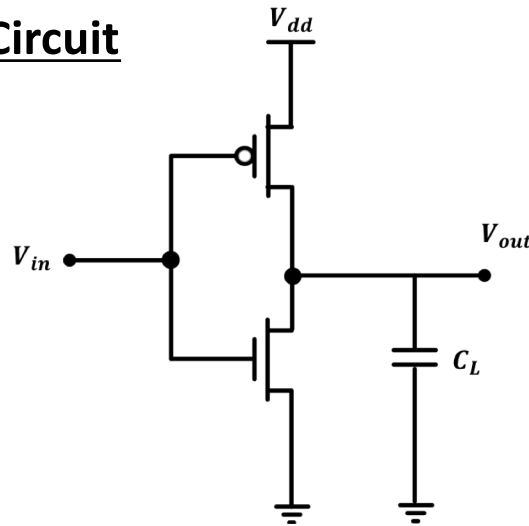


Low-to-High

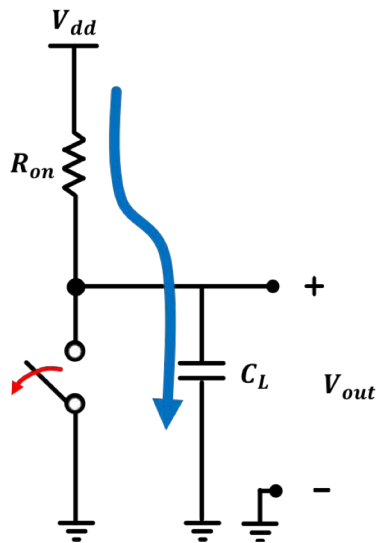

High-to-Low

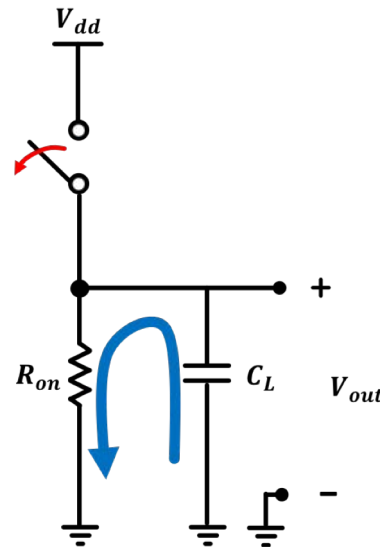


review

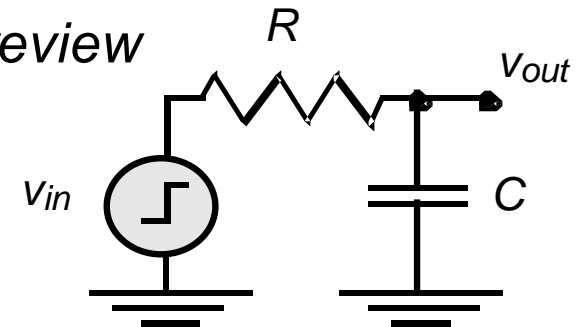

$$v_{out}(t) = (1 - e^{-t/\tau}) V$$

$$t_p = \ln(2) \tau = 0.69 RC$$

RC Equation

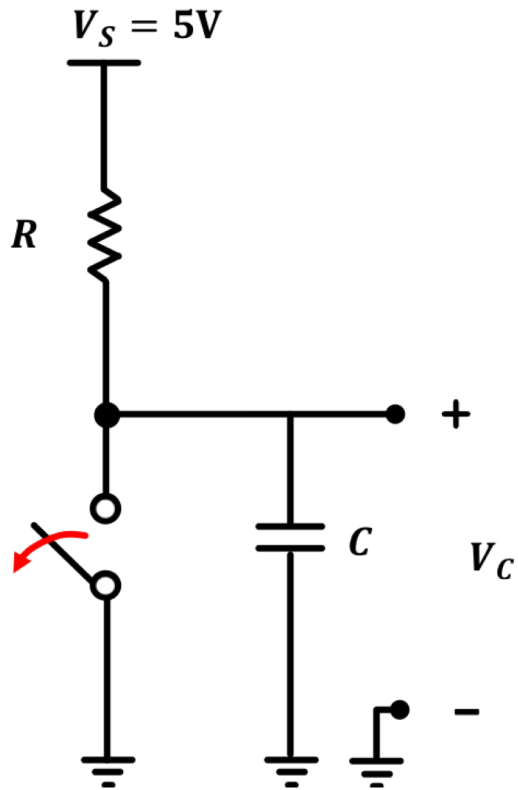

$$V_c = 5 \left(1 - e^{-\frac{t}{RC}} \right)$$

$$V_s = 5 \text{ V}$$

Switch is closed $t < 0$

Switch opens $t > 0$


$$V_s = V_R + V_C$$

$$V_s = i_R R + V_C \quad i_R = C \frac{dV_c}{dt}$$

$$V_s = RC \frac{dV_c}{dt} + V_c$$

$$V_c = V_s \left(1 - e^{-\frac{t}{RC}} \right)$$

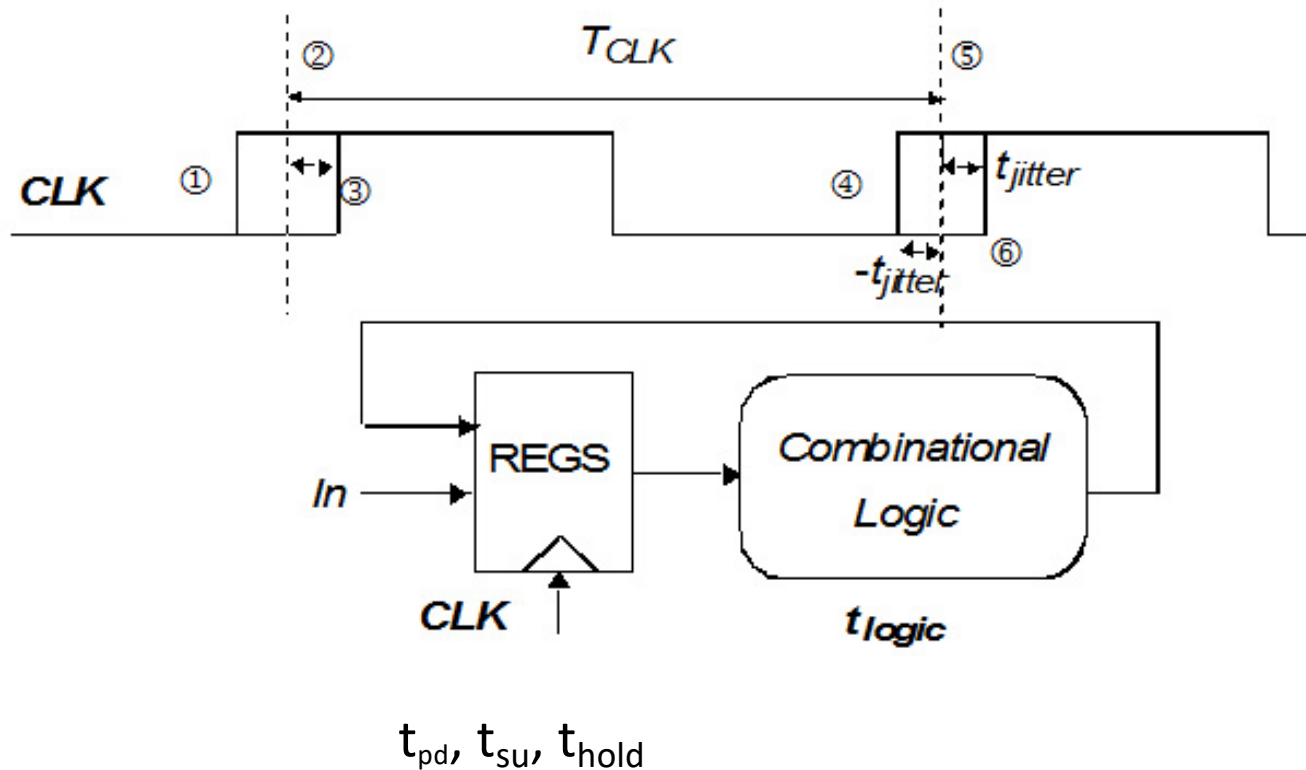
Clocks Are Not Perfectly Periodic: Jitter



$$t_{clk} - 2t_{jitter} > t_{pd} + t_{su} + t_{logic}$$

Typical crystal oscillator
100mhz (10ns)
Jitter: 1ps

Sequential Circuit Timing

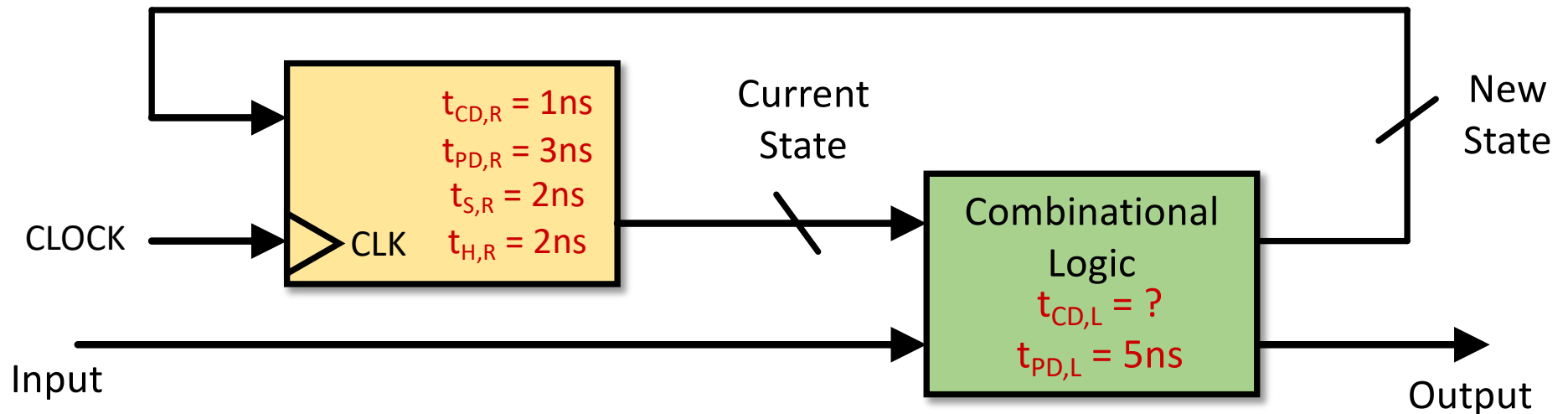

Questions:


- Constraints on t_{CD} for the logic? $> 1\text{ ns}$
- Minimum clock period? $> 10\text{ ns } (t_{PD,R} + t_{PD,L} + t_{SETUP,R})$
- Setup, Hold times for Inputs?
 - $t_{SETUP,Input} = t_{PD,L} + t_{SETUP,R}$
 - $t_{HOLD,Input} = t_{HOLD,R} - t_{CD,L}$

This is a simple *Finite State Machine* ... more on next time!

The Sequential **a**lways Block


Combinatorial
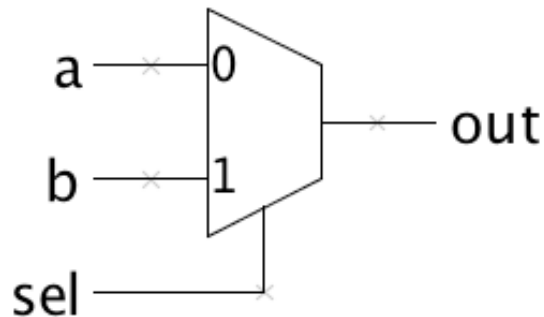
```
module comb(input a, b, sel,
             output reg out);
    always @(*) begin
        if (sel) out = b;
        else out = a;
    end
endmodule
```



Sequential
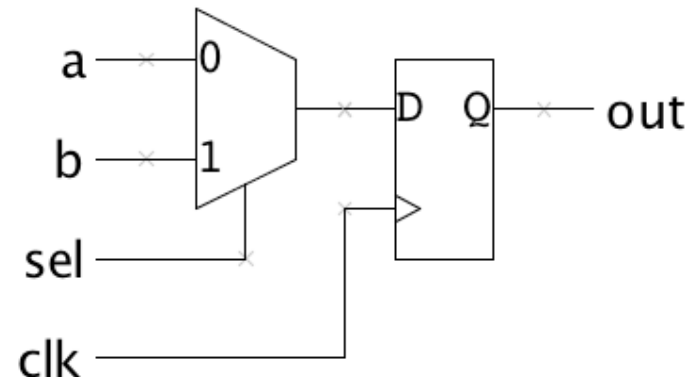
```
module seq(input a, b, sel, clk,
            output reg out);
    always @(posedge clk) begin
        if (sel) out <= b;
        else out <= a;
    end
endmodule
```



* Means WILDCARD...means any event



The Sensitivity List is Important!!

- The use of **posedge** and **negedge** makes an **always** block sequential (edge-triggered)
- Unlike a combinational **always** block, the sensitivity list *does* determine behavior for synthesis!

D-Register with **synchronous** clear

```
module dff_sync_clear(  
    input d, clearb, clock,  
    output reg q  
);  
    always @(posedge clock)  
    begin  
        if (!clearb) q <= 1'b0;  
        else q <= d;  
    end  
endmodule
```

always block entered only at each positive clock edge

D-Register with **asynchronous** clear

```
module dff_sync_clear(  
    input d, clearb, clock,  
    output reg q  
);  
    always @(negedge clearb or posedge clock)  
    begin  
        if (!clearb) q <= 1'b0;  
        else q <= d;  
    end  
endmodule
```

always block entered immediately when (active-low) *clearb* is asserted

Note: The following is incorrect syntax: **always** @(clear or negedge clock)

If one signal in the sensitivity list uses **posedge**/**negedge**, then all signals must.

- Assign any signal or variable from only one **always** block. Be wary of race conditions: **always** blocks with same trigger execute concurrently...

Blocking vs. Non-Blocking Assignments

- Verilog supports two types of assignments within `always` blocks, with subtly different behaviors.
- Blocking assignment (=)**: evaluation and assignment are immediate

```
always @(*) begin
    x = a | b;      // 1. evaluate a|b, assign result to x
    y = a ^ b ^ c;  // 2. evaluate a^b^c, assign result to y
    z = b & ~c;     // 3. evaluate b&(~c), assign result to z
end
```

- Nonblocking assignment (<=)**: all assignments deferred to end of simulation time step after all right-hand sides have been evaluated (*even those in other active `always` blocks*)

```
always @(*) begin
    x <= a | b;      // 1. evaluate a|b, but defer assignment to x
    y <= a ^ b ^ c;  // 2. evaluate a^b^c, but defer assignment to y
    z <= b & ~c;     // 3. evaluate b&(~c), but defer assignment to z
    // 4. end of time step: assign new values to x, y and z
end
```

Sometimes, as above, both produce the same result. **Sometimes, not!**

Real Life vs. Simulation!


(2001 Verilog Standard)

Ceaseless progression of time (continuous)

Discrete time steps of simulation



Each Time Step Order of Simulation

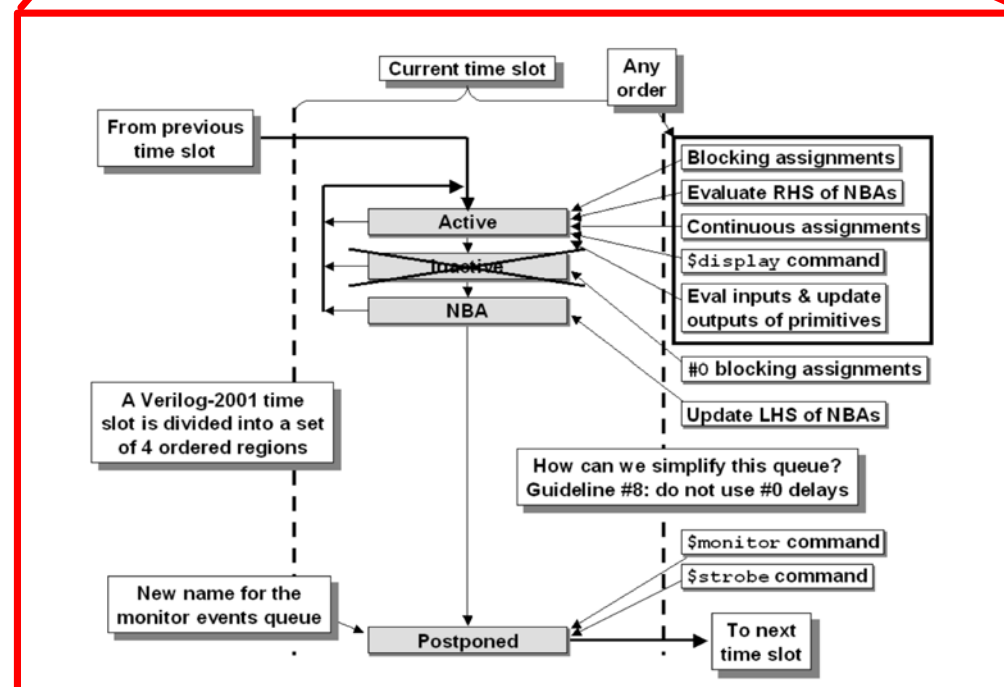

2005 SystemVerilog
Fixes some of
these issues!!

Race Conditions

- Race Conditions here, refer to simulation/software race conditions

```
module fbosc1 (y1, y2, clk, rst);
  output y1, y2;
  input  clk, rst;
  reg    y1, y2;

  always @(posedge clk or posedge rst)
    if (rst) y1 = 0; // reset
    else     y1 = y2;

  always @(posedge clk or posedge rst)
    if (rst) y2 = 1; // preset
    else     y2 = y1;
endmodule
```

```
module fbosc2 (y1, y2, clk, rst);
  output y1, y2;
  input  clk, rst;
  reg    y1, y2;

  always @(posedge clk or posedge rst)
    if (rst) y1 <= 0; // reset
    else     y1 <= y2;

  always @(posedge clk or posedge rst)
    if (rst) y2 <= 1; // preset
    else     y2 <= y1;
endmodule
```

- IEEE Standard Verilog only guarantees that these two blocks run in the same time step not that they run in a certain order
- Left one (blocking assignments) will produce different results on y2 and y1 depending on which block is chosen to be evaluated first. Non-blocking is immune to this.


From Cummings Paper (really good to read):

http://www.sunburst-design.com/papers/CummingsSNUG2000SJ_NBA.pdf

Blocking vs. Nonblocking Assignment

- Guaranteed question on job interviews with Verilog questions.
- *Blocking assignment (=)*: evaluation and assignment are immediate; subsequent statements affected.
- *Nonblocking assignment (<=)*: all assignments deferred to end of simulation time step after all right-hand sides have been evaluated (*even those in other active always blocks*)
- Sometimes, as previous page, both produce the same result. **Sometimes, not!**

Assignment Styles for Sequential Logic

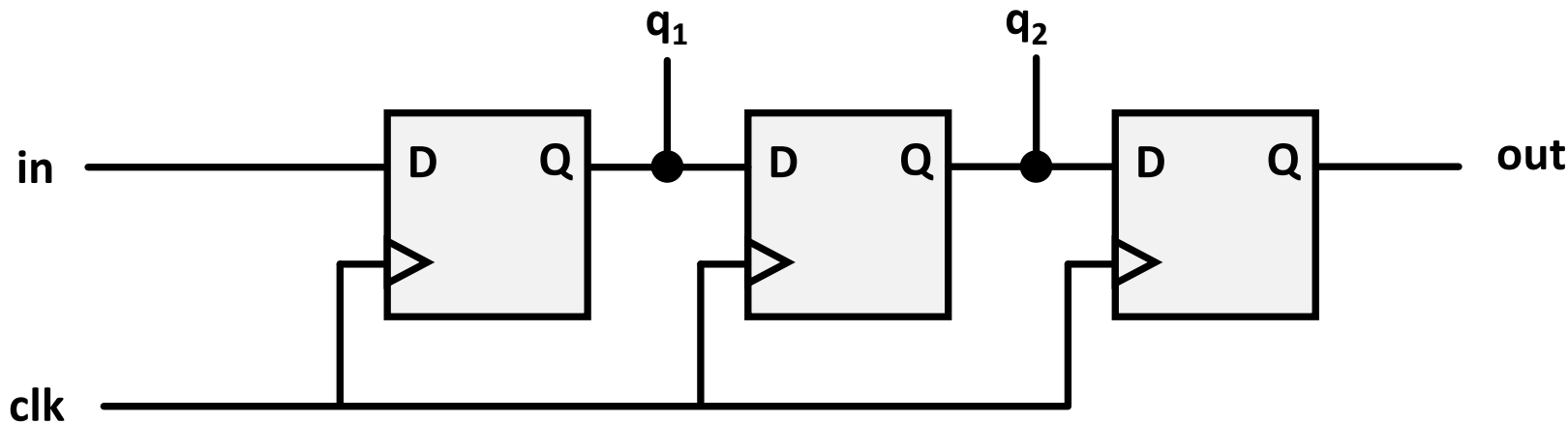

Will nonblocking and blocking assignments both produce the desired result? (“old” means value before clock edge, “new” means the value after most recent assignment)


```
module nonblocking(  
    input in, clk,  
    output reg out  
);  
    reg q1, q2;  
    always @(posedge clk) begin  
        q1 <= in;  
        q2 <= q1;    // uses old q1  
        out <= q2;    // uses old q2  
    end  
endmodule
```

```
module blocking(  
    input in, clk,  
    output reg out  
);  
    reg q1, q2;  
    always @(posedge clk) begin  
        q1 = in;  
        q2 = q1;    // uses new q1  
        out = q2;    // uses new q2  
    end  
endmodule
```

Use Nonblocking for Sequential Logic


```
always @(posedge clk) begin
    q1 <= in;
    q2 <= q1;    // uses old q1
    out <= q2;   // uses old q2
end
```

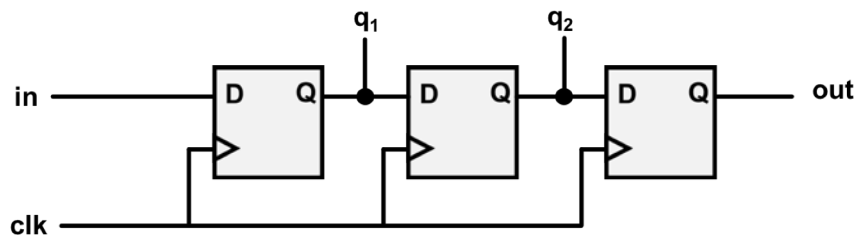“At each rising clock edge, **q1**, **q2**, and **out** simultaneously receive the old values of **in**, **q1**, and **q2**.”



```
always @(posedge clk) begin
    q1 = in;
    q2 = q1;    // uses new q1
    out = q2;   // uses new q2
end
```

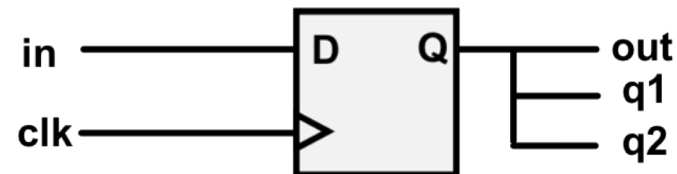“At each rising clock edge, **q1** = **in**.
After that, **q2** = **q1**.
After that, **out** = **q2**.
Therefore **out** = **in**.”



- Blocking assignments **do not** reflect the intrinsic behavior of multi-stage sequential logic
- Guideline: use **nonblocking** assignments for sequential *always* blocks

always block

- Sequential always block: `always @(posedge clock)`
- Combinatorial always block: `always @ *`
- Results of operators (LHS) inside always block (sequential and combinatorial) must be declared as “reg”
- Equivalent Verilog

```
reg z
always @ *
    z = x && y
```

← *same as* →
example of
combinatorial
always block

```
assign z = x && y
// z not a “reg”
```

- case statements must be used within an always block; **include default case!!!**

Verilog Case Statement:

```
module mux_without_default (a,b,c,d,sel,y);  
    input a, b, c, d;  
    input [1:0] sel;  
    output y; 5 6 reg y;  
  
    always @ (a or b or c or d or sel)  
        case (sel)  
            0 : y = a;  
            1 : y = b;  
            2 : y = c;  
            3 : y = d;  
            default: y=0;  
        endcase  
  
endmodule
```

Sequential always block style:

```
// There are two styles for creating this sample divider below. The
// first uses sequential always block for state assignment and
// a combinational always block for next-state. The second might result in
// fewer errors
//
// An alternate approach is to use a single always block. An example
// of a divide by 5 counter will illustrate the differences
```

```
////////////////////////////////////////
// Sequential always block with a
// combinational always block

reg [3:0] count1, next_count1;

always @(posedge clk)
    count1 <= next_count1;

always @* begin
    if (reset) next_count1 = 0;
    else next_count1 =
        (count1 == 4) ? 0 : count1 + 1;
end

assign enable1 = (count1 == 4);
////////////////////////////////////////
```

```
////////////////////////////////////////
// Single always block
//

reg [3:0] count2;

always @(posedge clk) begin
    if (reset) count2 <= 0;
    else count2 <= (count2 == 4) ? 0 : count2 + 1;
end

assign enable2 = (count2 == 4);

////////////////////////////////////////
```

Coding Guidelines

- The following helpful guidelines are from the Cummings paper. If followed, they ensure your simulation results will match what the synthesized hardware will do:

http://www.sunburst-design.com/papers/CummingsSNUG2000SJ_NBA.pdf

1. When modeling sequential logic, use nonblocking assignments.
2. When modeling latches, use nonblocking assignments.
3. When modeling combinational logic with an always block, use blocking assignments.
4. When modeling both sequential and “combinational” logic within the same always block, use nonblocking assignments.
5. Do not mix blocking and nonblocking assignments in the same always block.
6. Do not make assignments to the same variable from more than one always block.
7. Use `$strobe` to display values that have been assigned using nonblocking assignments.
8. Do not make assignments using #0 delays.

- **#1 thing we will be checking in your Verilog submissions!**

Guidelines: Sequential and “combinatorial” logic in the same always block

```
module nbex1
  (output reg q,
   input clk, rst_n,
   input a, b);

  reg y;
  always @(a or b)
    y = a ^ b;

  always @(posedge clk or
          negedge rst_n)
    if (!rst_n) q <= 1'b0;
    else q <= y;

endmodule
```

*Combinatorial
logic*



```
module nbex2
  (output q,
   input clk, rst_n,
   input a, b);

  reg q;
  always @(posedge clk or
          negedge rst_n)
    if (!rst_n) q <= 1'b0;
    else q <= a ^ b;

endmodule
```

Combinatorial logic



= vs. <= inside always

```
module main;  
  reg a,b,clk;
```

```
  initial begin  
    clk = 0; a = 0; b = 1;  
    #10 clk = 1;  
    #10 $display("a=%d b=%d\n",a,b);  
    $finish;  
  end  
endmodule
```

A

```
always @(posedge clk) begin  
  a = b;    // blocking assignment  
  b = a;    // execute sequentially  
end
```

B

```
always @(posedge clk) begin  
  a <= b;   // non-blocking assignment  
  b <= a;   // eval all RHSs first  
end
```

C

```
always @(posedge clk) a = b;  
always @(posedge clk) b = a;
```

D


```
always @(posedge clk) a <= b;  
always @(posedge clk) b <= a;
```

E


```
always @(posedge clk) begin  
  a <= b;  
  b = a;    // urk! Be consistent!  
end
```

Rule: always change state using <= (e.g., inside always @(posedge clk)...)

Implementation of On/Off Button

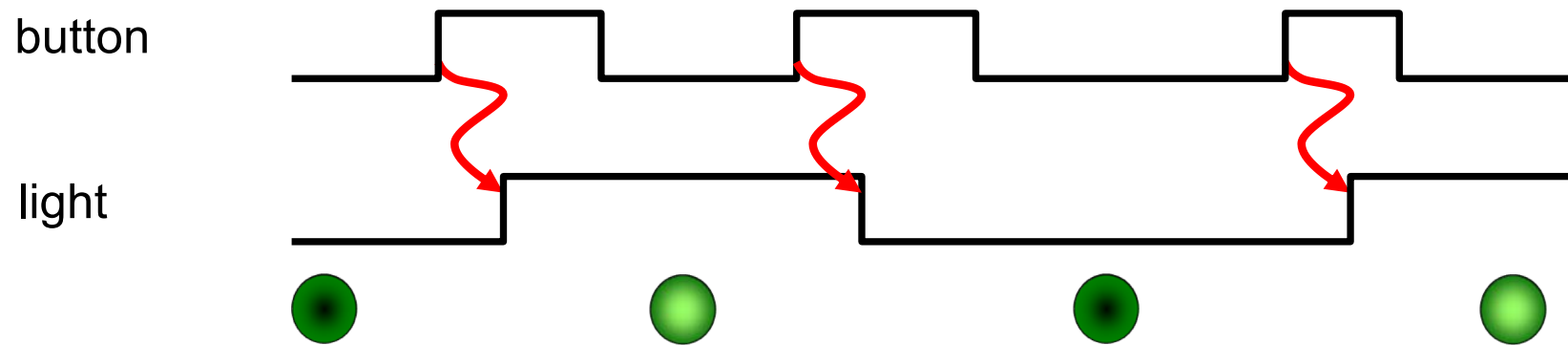
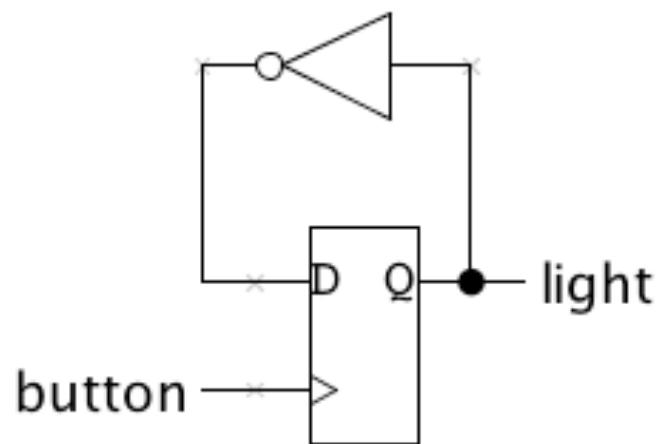
```
module onoff(input button, output reg light);  
    always @(posedge button) light <= ~light;  
endmodule
```



Synchronous On/Off Button

- When designing a system that accepts many inputs it would be hard to have input changes serve as the system clock (which input would we use?). So we'll use a single clock of some fixed frequency and have the inputs control what state changes happen on rising clock edges.
- For most of our lab designs we'll use a 27MHz system clock (37ns clock period).

```
module onoff_sync(input clk, button,  
                  output reg light);  
    always @ (posedge clk) begin  
        if (button) light <= ~light;  
    end  
endmodule
```

Resetting to a Known State!

- Usually one can't rely on registers powering-on to a particular initial state*. So most designs have a RESET signal that when asserted initializes all the state to known, mutually consistent initial values.

```
module onoff_sync(input clk, reset, button,  
                  output reg light);  
  always @ (posedge clk) begin  
    if (reset) light <= 0;  
    else if (button) light <= ~light;  
  end  
endmodule
```

* Actually, our FPGAs will reset all registers to 0 when the device is programmed. But it's nice to be able to press a reset button to return to a known state rather than starting from scratch by reprogramming the device.


Clocks are Fast, We are Slow

- The circuit on the last slide toggles the light on every rising clock edge for which button is 1. But clocks are fast (27MHz!) and our fingers are slow, so how do we press the button for just one clock edge? Answer: we can't, but we can add some state that remembers what button was last clock cycle and then detect the clock cycles when button changes from 0 to 1.


```
module onoff_sync(input clk, reset, button,output reg light);

    reg old_button; // state of button last clk
    always @ (posedge clk) begin
        if (reset)
            begin light <= 0; old_button <= 0; end
        else if (old_button==0 && button==1)
            // button changed from 0 to 1
            light <= ~light;
            old_button <= button;
        end
    endmodule
```

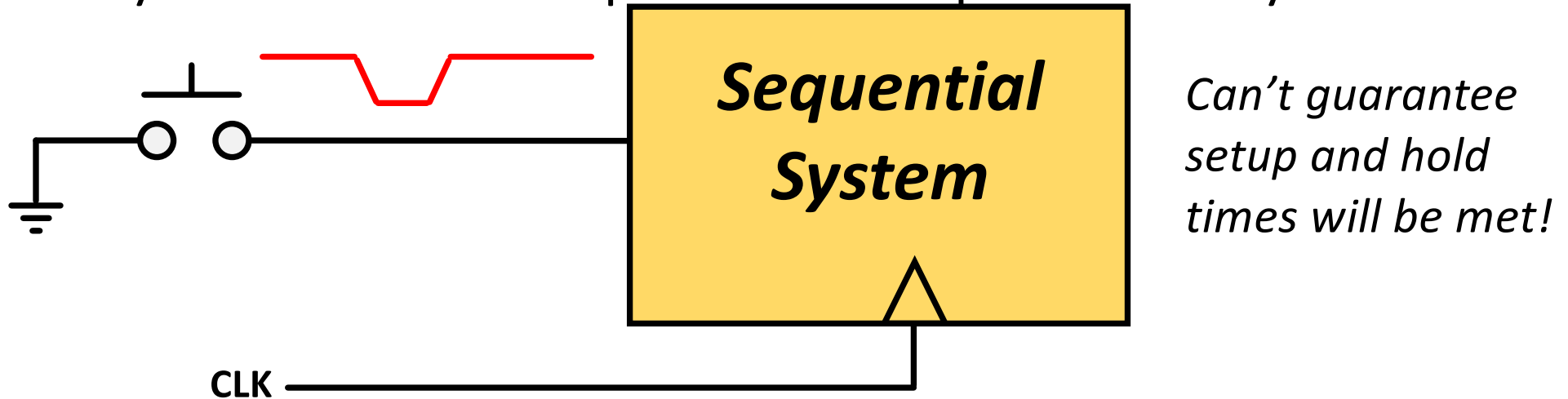Asynchronous Inputs in Sequential Systems




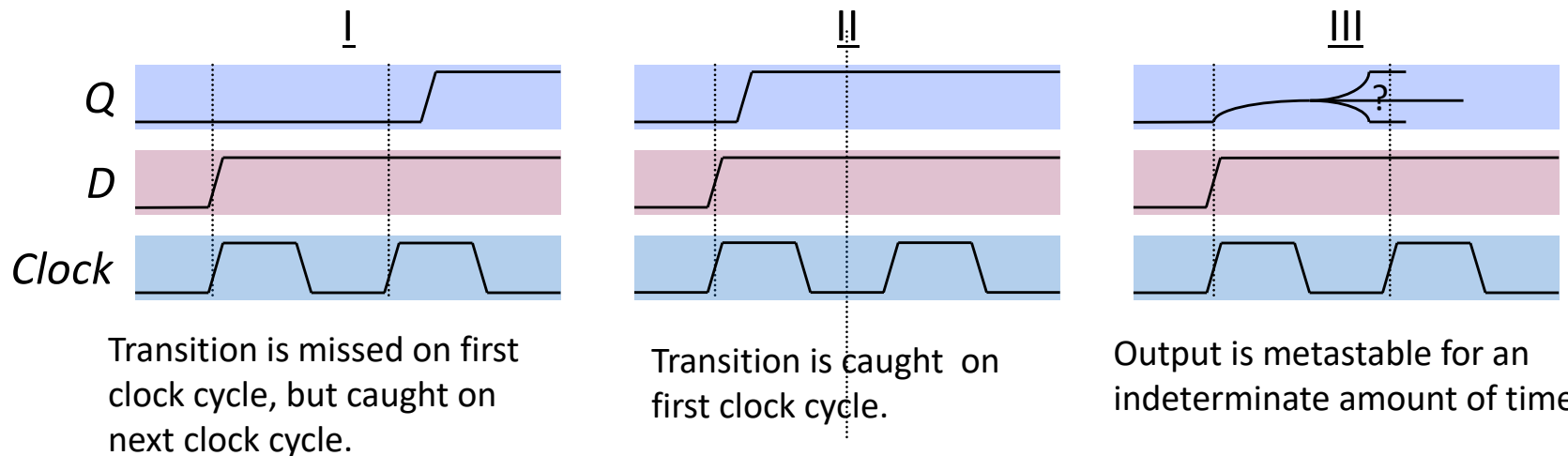
When an asynchronous signal causes a setup/hold violation...



Q: Which cases are problematic?


Asynchronous Inputs in Sequential Systems

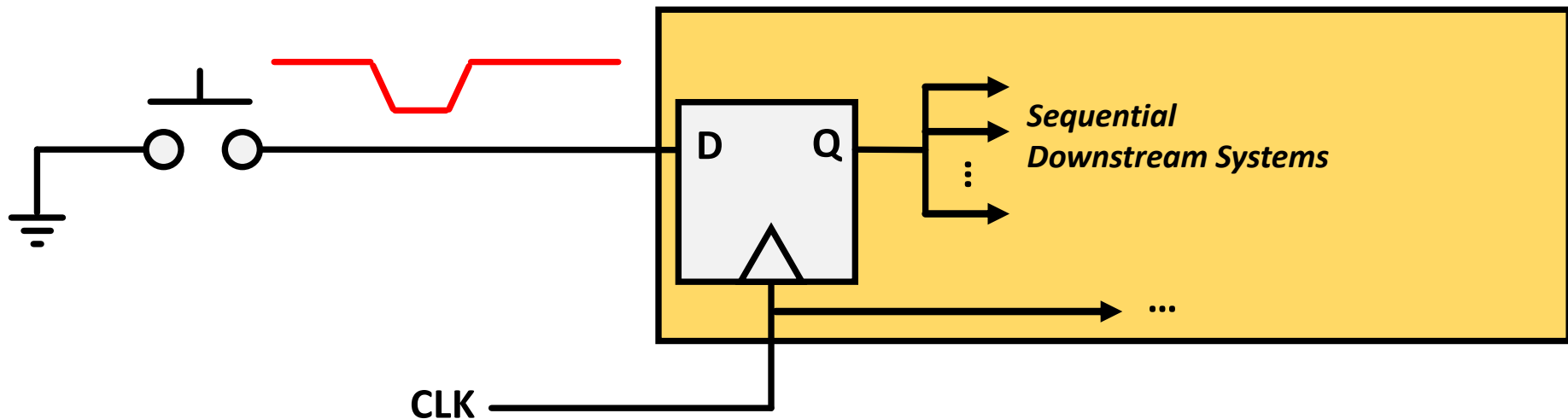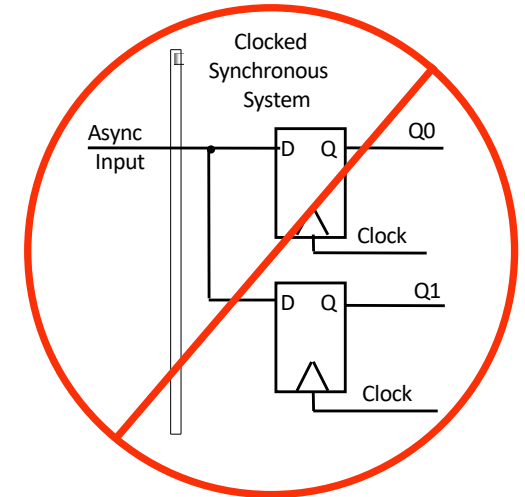- **All of them can be,** if more than one happens simultaneously within the same circuit.
- Guidelines: Ensure that external signals feed **exactly one** flip-flop



Handling Metastability

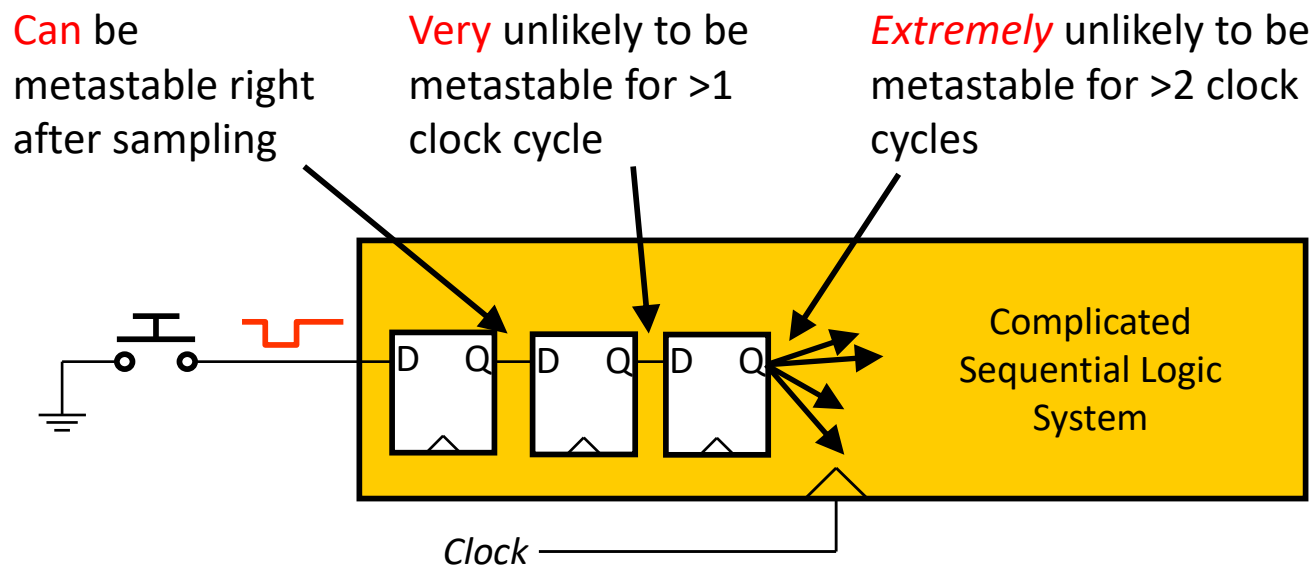- Preventing metastability turns out to be an impossible problem
- High gain of digital devices makes it likely that metastable conditions will resolve themselves quickly
- Solution to metastability: allow time for signals to stabilize




How many registers are necessary?

- Depends on many design parameters (clock speed, device speeds, ...)
- In 6.111, a pair of synchronization registers is sufficient

One Last Little Problem

- Mechanical buttons exhibit contact “bounce” when they change position, leading to multiple output transitions before finally stabilizing in the new position:

We need a debouncing circuit!

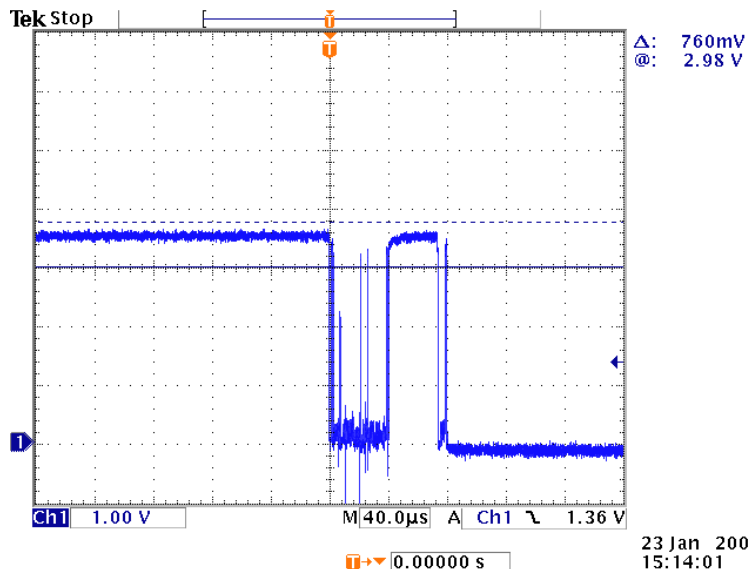

```
// Switch Debounce Module
// use your system clock for the clock input
// to produce a synchronous, debounced output
// DELAY = .01 sec with a 27Mhz clock
module debounce #(parameter DELAY=270000-1)
    (input reset, clock, bouncy,
     output reg steady);

    reg [18:0] count;
    reg old;


    always @(posedge clock)

endmodule
```

One Last Little Problem

- Mechanical buttons exhibit contact “bounce” when they change position, leading to multiple output transitions before finally stabilizing in the new position:

We need a debouncing circuit!

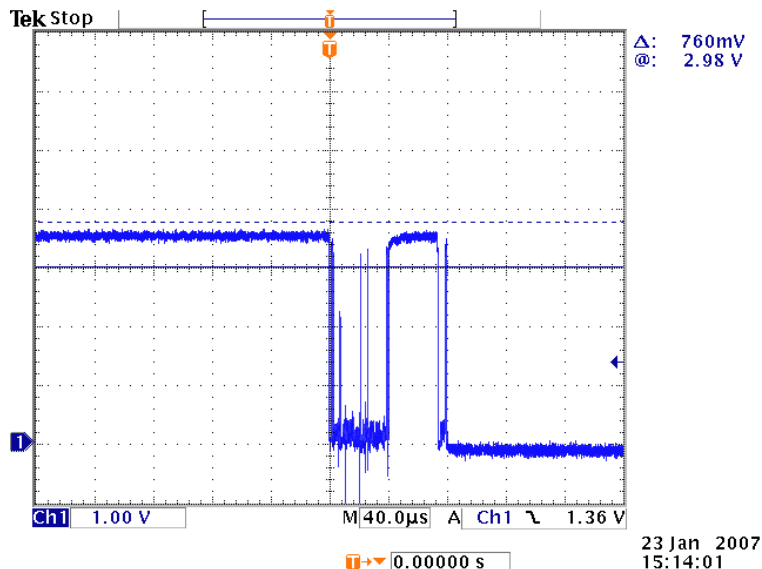

```
// Switch Debounce Module
// use your system clock for the clock input
// to produce a synchronous, debounced output
// DELAY = .01 sec with a 27Mhz clock
module debounce #(parameter DELAY=270000-1)
    (input reset, clock, bouncey,
     output reg steady);

    reg [18:0] count;
    reg old;

    always @(posedge clock)
        if (reset) // return to known state
            begin
                count <= 0;
                old <= bouncey;
                steady <= bouncey;
            end
        else if (bouncey != old) // input changed
            begin
                old <= bouncey;
                count <= 0;
            end
        else if (count == DELAY) // stable!
            steady <= old;
        else // waiting...
            count <= count+1;

endmodule
```


On/Off Final Answer

```
module onoff_sync(input clk, reset, button_in,
                  output reg light);
    // synchronizer
    reg button, btemp;
    always @(posedge clk)
        {button, btemp} <= {btemp, button_in};

    // debounce push button
    wire bpressed;
    debounce db1(.clock(clk), .reset(reset),
                .boucey(button), .steady(bpressed));

    reg old_bpressed; // state last clk cycle
    always @ (posedge clk) begin
        if (reset)
            begin light <= 0; old_bpressed <= 0; end
        else if (old_bpressed==0 && bpressed==1)
            // button changed from 0 to 1
            light <= ~light;
            old_bpressed <= bpressed;
        end
    endmodule
```

Example: Simple Counter

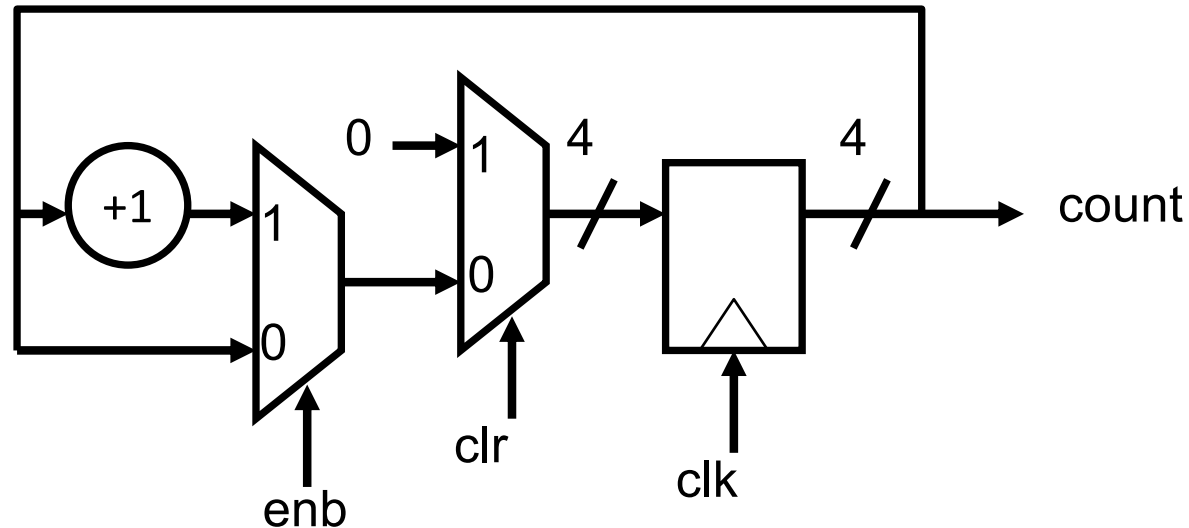

*Isn't this a lot like
Exercise 1 in Lab 2?*

```
// 4-bit counter with enable and synchronous clear
module counter(input clk,enb,clr,
               output reg [3:0] count);
    always @(posedge clk) begin
        count <= clr ? 4'b0 : (enb ? count+1 : count);
    end
endmodule
```