

Lecture 6

- Design methodology for sequential logic
 - identify distinct states
 - create state transition diagram
 - choose state encoding
 - write combinational Verilog for next-state logic
 - write combinational Verilog for output signals
- Lots of examples


9/26/2018

6.111 Fall 2018

1

Design Example: Level-to-Pulse

 - A **level-to-pulse converter** produces a single-cycle pulse each time its input goes high.
- It's a synchronous rising-edge detector.
- Sample uses:
 - Buttons and switches pressed by humans for arbitrary periods of time
 - Single-cycle enable signals for counters




9/26/2018

6.111 Fall 2018

2

Finite State Machines

 - Finite State Machines (FSMs) are a useful abstraction for **sequential circuits** with centralized “**states**” of operation
- At each clock edge, combinational logic computes **outputs** and **next state** as a function of **inputs** and **present state**



9/26/2018


6.111 Fall 2018

3


Two Types of FSMs

Moore and **Mealy** FSMs : different output generation

• Moore FSM:

 

• Mealy FSM:

 


9/26/2018

6.111 Fall 2018

4

Design Example: Level-to-Pulse

 - A **level-to-pulse converter** produces a single-cycle pulse each time its input goes high.
- It's a synchronous rising-edge detector.
- Sample uses:
 - Buttons and switches pressed by humans for arbitrary periods of time
 - Single-cycle enable signals for counters



9/26/2018

6.111 Fall 2018

5

Reminder on the Synchronizer

- Stringing several (often two or three is sufficient) registers in series is enough to isolate an asynchronous input from sensitive downstream logic and registers


9/26/2018

6.111 Fall 2018

6

Handling Metastability

 - Preventing metastability turns out to be an impossible problem
- High gain of digital devices makes it likely that metastable conditions will resolve themselves quickly
- Solution to metastability: allow time for signals to stabilize



How many registers are necessary?

- Depends on many design parameters (clock speed, device speeds, ...)
- In 6.111, a pair of synchronization registers is sufficient

9/26/2018

6.111 Lecture 4

7

Handling Metastability


 


Figure 8. Two-flip-flop synchronization circuit.

 

- FF2 (D-reg2) might go a clock cycle late, but it will almost never* go metastable

*almost never generally means actually almost never (once in ten years or something)

"Metastability and Synchronizers: A Tutorial"
Ran Ginosar, Technion Israel Institute of Technology


9/26/2018

6.111 Lecture 4


8

Step 1: State Transition Diagram

- Block diagram of desired system:

 

 - State transition diagram is a useful FSM representation and design aid:




9/26/2018

6.111 Fall 2018

9

Valid State Transition Diagrams

 

- Arcs leaving a state are **mutually exclusive**, i.e., for any combination input values there's at most one applicable arc
- Arcs leaving a state are **collectively exhaustive**, i.e., for any combination of input values there's at least one applicable arc
- So for each state: for any combination of input values there's exactly one applicable arc
- Often a starting state is specified
- Each state specifies values for all outputs (Moore)

9/26/2018

6.111 Fall 2018

10

Choosing State Representation

- Choice #1: **binary encoding**

For N states, use $\text{ceil}(\log_2 N)$ bits to encode the state with each state represented by a unique combination of the bits. Tradeoffs: most efficient use of state registers, but requires more complicated combinational logic to detect when in a particular state.

- Choice #2: **"one-hot" encoding**

For N states, use N bits to encode the state where the bit corresponding to the current state is 1, all the others 0. Tradeoffs: more state registers, but often much less combinational logic since state decoding is trivial.


9/26/2018

6.111 Fall 2018

11


Step 2: Logic Derivation

 Transition diagram is readily converted to a state transition table (just a truth table)



Current State		In	Next State		Out
S_1	S_0	L	S_1^+	S_0^+	P
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	1
1	1	0	0	0	0
1	1	1	1	1	0

 - Combinational logic may be derived using Karnaugh maps




9/26/2018


6.111 Fall 2018

12

Moore Level-to-Pulse Converter

 

 Moore FSM circuit implementation of level-to-pulse converter:




9/26/2018


6.111 Fall 2018

13

Design of a Mealy Level-to-Pulse

 

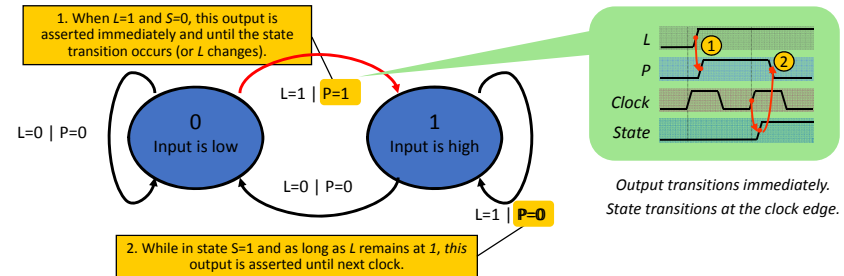- Since outputs are determined by state *and* inputs, Mealy FSMs may need fewer states than Moore FSM implementations




9/26/2018

6.111 Fall 2018


14

Mealy Level-to-Pulse Converter

 

Pres. State	In	Next State	Out
S	L	S+	P
0	0	0	0
0	1	1	1
1	1	1	0
1	0	0	0

 Mealy FSM circuit implementation of level-to-pulse converter:



- FSM's state simply remembers the previous value of L
- Circuit benefits from the Mealy FSM's implicit single-cycle assertion of outputs during state transitions

9/26/2018


6.111 Fall 2018

15


Moore/Mealy Trade-Offs

- How are they different?
 - Moore: **outputs = f(state)** only
 - Mealy **outputs = f(state and input)**
 - Mealy outputs generally occur one cycle earlier than a Moore:

Moore: delayed assertion of P

 

Mealy: immediate assertion of P

 

- Compared to a Moore FSM, a Mealy FSM might...
 - Be more difficult to conceptualize and design
 - Have fewer states


9/26/2018

6.111 Fall 2018

16

Moore/Mealy Trade-Offs

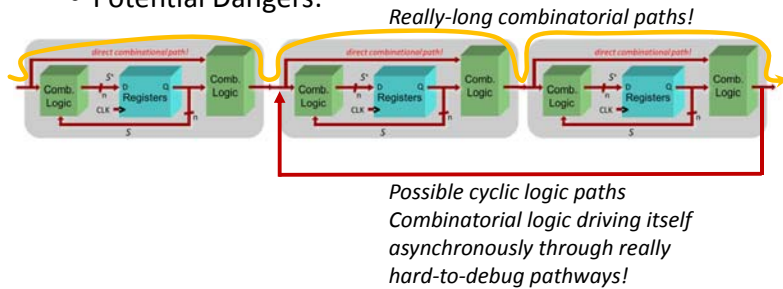- Moore:
 - Usually more states
 - Each state has a particular output
- Mealy:
 - Fewer states, outputs are specified on edges of diagram
 - Potential Dangers:



9/26/2018

6.111 Fall 2018

17

FSM Example

GOAL:

Build an electronic combination lock with a reset button, two number buttons (0 and 1), and an unlock output. The combination should be **01011**.



STEPS:


1. Design lock FSM (block diagram, state transitions)
2. Write Verilog module(s) for FSM

9/26/2018

6.111 Fall 2018

18

Step 1A: Block Diagram

 


9/26/2018

6.111 Fall 2018

19

Step 1B: State transition diagram

 

9/26/2018

6.111 Fall 2018

20

Step 2: Write Verilog

```
module lock(input clk,reset_in,b0_in,b1_in,
            output out);
```

```
// synchronize push buttons, convert to pulses
```

```
// implement state transition diagram
reg [2:0] state,next_state;
always @(*) begin
    // combinational logic!
    next_state = ???;
end
always @(posedge clk) state <= next_state;
```

```
// generate output
assign out = ???;
```

```
// debugging?
endmodule
```

9/26/2018


6.111 Fall 2018

21

Step 2A: Synchronize buttons

```
// button
// push button synchronizer and level-to-pulse converter
// OUT goes high for one cycle of CLK whenever IN makes a
// low-to-high transition.
```
 
```
module button(
    input clk,in,
    output out
);
    reg r1,r2,r3;
    always @(posedge clk)
    begin
        r1 <= in;    // first reg in synchronizer
        r2 <= r1;    // second reg in synchronizer, output is in sync!
        r3 <= r2;    // remembers previous state of button
    end
```



```
// rising edge = old value is 0, new value is 1
assign out = ~r3 & r2;
endmodule
```

9/26/2018


6.111 Fall 2018

22

Step 2B: state transition diagram

```
parameter S_RESET = 0; // state assignments
parameter S_0 = 1;
parameter S_01 = 2;
parameter S_010 = 3;
parameter S_0101 = 4;
parameter S_01011 = 5;
```

```
reg [2:0] state, next_state;
always @(*) begin
    // implement state transition diagram
    if (reset) next_state = S_RESET;
    else case (state)
        S_RESET: next_state = b0 ? S_0 : b1 ? S_RESET : state;
        S_0:      next_state = b0 ? S_0 : b1 ? S_01 : state;
        S_01:     next_state = b0 ? S_010 : b1 ? S_RESET : state;
        S_010:    next_state = b0 ? S_0 : b1 ? S_0101 : state;
        S_0101:   next_state = b0 ? S_010 : b1 ? S_01011 : state;
        S_01011:  next_state = b0 ? S_0 : b1 ? S_RESET : state;
        default:  next_state = S_RESET; // handle unused states
    endcase
end
```

 

```
always @(posedge clk) state <= next_state;
```

9/26/2018

6.111 Fall 2018

23

Step 2C: generate output

```
// it's a Moore machine! Output only depends on current state
```

```
assign out = (state == S_01011);
```

Inevitable Step 2D: debugging?

```
// hmmm. What would be useful to know? Current state?
// hex_display on labkit shows 16 four bit values
```


```
assign hex_display = {6'b0, 1'b0, state[2:0]};
```

9/26/2018

6.111 Fall 2018

24

Real FSM Security System

 

9/26/2018

6.111 Fall 2018

25

Step 2: final Verilog implementation

```
module lock(input clk,reset_in,b0_in,b1_in,
           output out, output [3:0] hex_display);

    wire reset, b0, b1; // synchronize push buttons, convert to pulses
    button b_reset(clk,reset_in,reset);
    button b_0(clk,b0_in,b0);
    button b_1(clk,b1_in,b1);

    parameter S_RESET = 0; parameter S_0 = 1; // state assignments
    parameter S_01 = 2; parameter S_010 = 3;
    parameter S_0101 = 4; parameter S_01011 = 5;

    reg [2:0] state,next_state;
    always @(*) begin // implement state transition diagram
        if (reset) next_state = S_RESET;
        else case (state)
            S_RESET: next_state = b0 ? S_0 : b1 ? S_RESET : state;
            S_0: next_state = b0 ? S_0 : b1 ? S_01 : state;
            S_01: next_state = b0 ? S_010 : b1 ? S_RESET : state;
            S_010: next_state = b0 ? S_0 : b1 ? S_0101 : state;
            S_0101: next_state = b0 ? S_010 : b1 ? S_01011 : state;
            S_01011: next_state = b0 ? S_0 : b1 ? S_RESET : state;
            default: next_state = S_RESET; // handle unused states
        endcase
    end
    always @ (posedge clk) state <= next_state;

    assign out = (state == S_01011); // assign output: Moore machine
    assign hex_display = {1'b0,state}; // debugging
endmodule
```

9/26/


26

Does it Work?

```
wire to_led;
wire [3:0] to_state_display;
lock my_lock(clk(clock_27mhz), reset_in(button_enter),
            .b0_in(button0), .b1_in(button1),
            .out(to_led), .hex_display(to_state_display));

//assign led = ~switch;
assign led = {~to_state_display,3'b0, ~to_led};
```

*Should have
debounced inputs :/*


 


9/26/2018

6.111 Fall 2018

27

Does it Work?

  

Double-click on Primary Module

*Select
"View RTL Schematic"*


9/26/2018

6.111 Fall 2018

28

Does it Work?

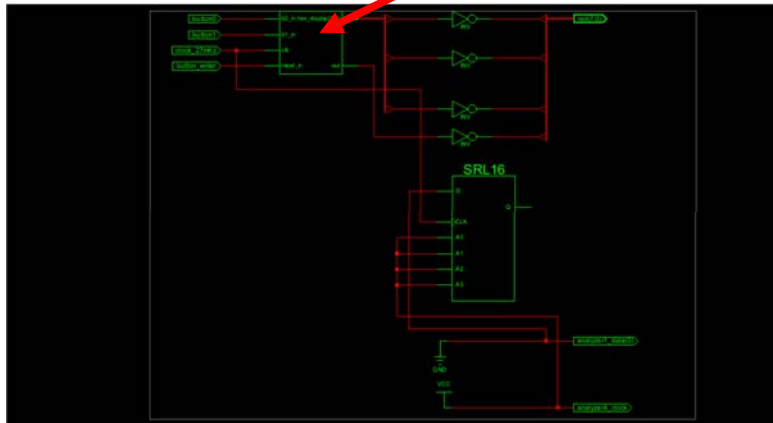Double-click on Actual Stuff I wrote Module




9/26/2018

6.111 Fall 2018

29

Does it Work?

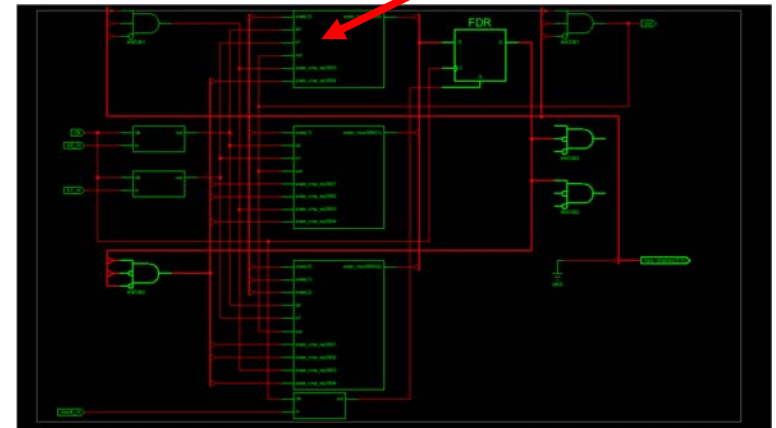Double-click on Actual Stuff I wrote Module




9/26/2018

6.111 Fall 2018

30

Does it Work?

At the lowest level of my design

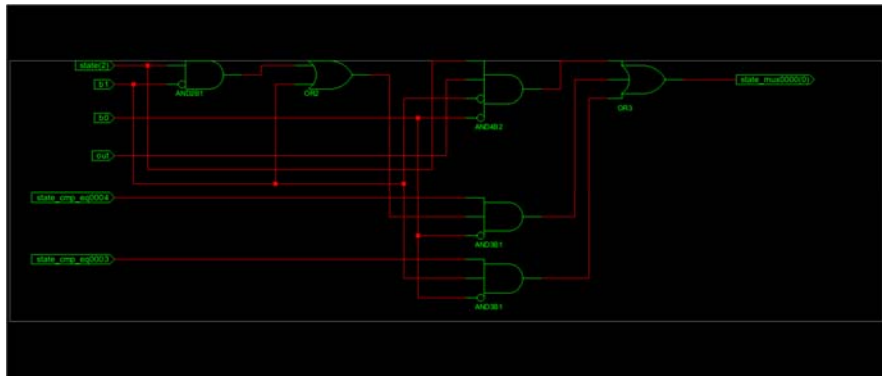


9/26/2018

6.111 Fall 2018

31

Does it Work?

One of the button synchronizers

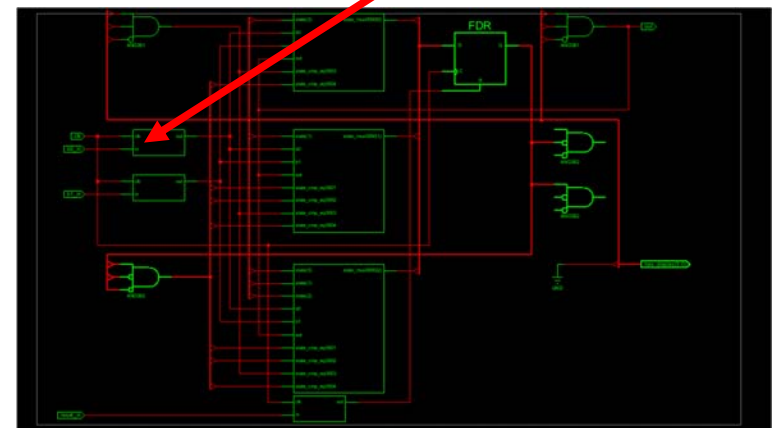

9/26/2018

6.111 Fall 2018


32

Does it Work?

```
// button
// push button synchronizer and level-to-pulse converter
// OUT goes high for one cycle of CLK whenever IN makes a
// low-to-high transition.
// One of the button synchronizers!!!

module button(
    input clk,in,
    output out
);
    reg r1,r2,r3;
    always @(posedge clk)
    begin
        r1 <= in; // first reg in synchronizer
        r2 <= r1; // second reg in synchronizer, output is in sync!
        r3 <= r2; // remembers previous state of button
    end

     // rising edge = old value is 0, new value is 1
    assign out = ~r3 & r2;
endmodule
```



9/26/2018

6.111 Fall 2018

33

Example: Intersection Traffic Lights

- Design a controller for the traffic lights at the intersection of two streets – two sets of traffic lights, one for each of the streets.
- Step 1: Draw starting state transition diagram. Just handle the usual green-yellow-red cycle for both streets. How many states? Well, how many different combinations of the two sets of lights are needed?
- Step 2: add support for a walk button and walk lights to your state transition diagram.
- Step 3: add support for a traffic sensor for each of the streets – when the sensor detects traffic the green cycle for that street is extended.

Example to be worked collaboratively on the board...

Encode all information in states!!!!

9/26/2018

6.111 Fall 2018

34

The 6.111 Vending Machine

- Lab assistants demand a new soda machine for the 6.111 lab. You design the FSM controller.
- All selections are \$0.30.
- The machine makes change. (Dimes and nickels only.)
- Inputs: limit 1 per clock
 - Q - quarter inserted
 - D - dime inserted
 - N - nickel inserted
- Outputs: limit 1 per clock
 - DC - dispense can
 - DD - dispense dime
 - DN - dispense nickel



9/26/2018

6.111 Fall 2018

35

What States are in the System?

- A starting (idle) state:

idle

- A state for each possible amount of money captured:

got5c got10c got15c ...

- What's the maximum amount of money captured before purchase?
25 cents (just shy of a purchase) + one quarter (largest coin)

... got35c got40c got45c got50c

- States to dispense change (one per coin dispensed):

got45c → Dispense Dime → Dispense Nickel


9/26/2018

6.111 Fall 2018

36

A Moore Vender

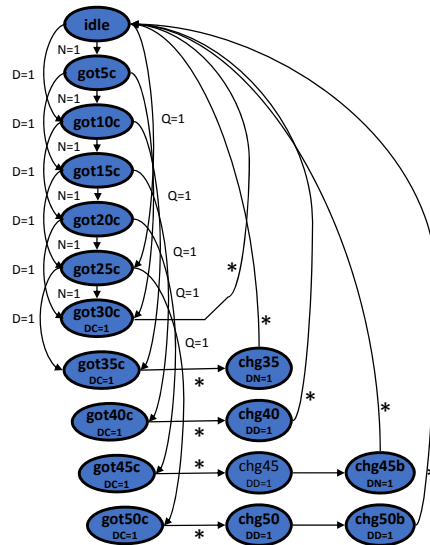Here's a first cut at the state transition diagram.




9/26/2018

6.111 Fall 2018

37

State Reduction

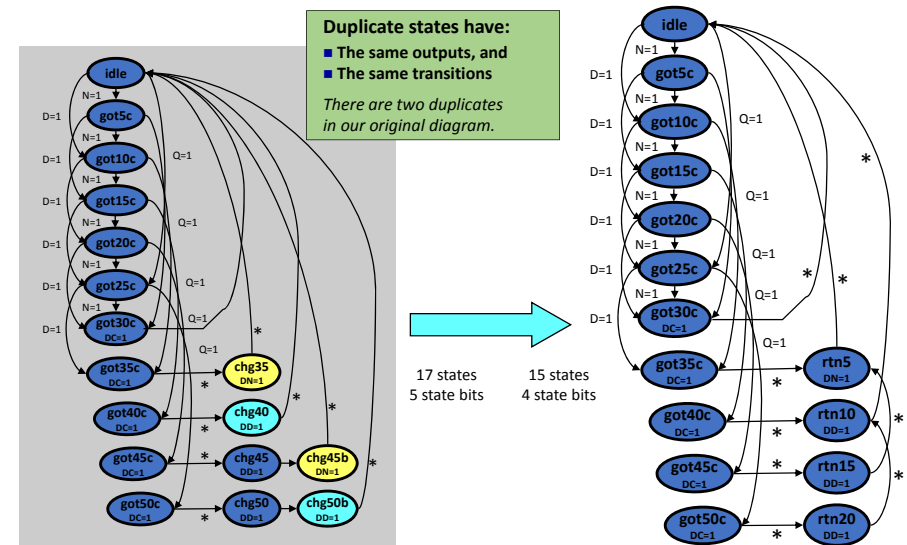


9/26/2018

6.111 Fall 2018

38

Verilog for the Moore Vender

 

FSMs are easy in Verilog.
Simply write one of each:

- State register (sequential always block) So triggered on posedge clock
- Next-state combinational logic (comb. always block with case)
- Output combinational logic block (comb. always block or assign statements)

```
module mooreVender (
    input N, D, Q, clk, reset,
    output DC, DN, DD,
    output reg [3:0] state);

    reg [3:0] next;
```

States defined with **parameter** keyword

```
parameter IDLE = 0;
parameter GOT_5c = 1;
parameter GOT_10c = 2;
parameter GOT_15c = 3;
parameter GOT_20c = 4;
parameter GOT_25c = 5;
parameter GOT_30c = 6;
parameter GOT_35c = 7;
parameter GOT_40c = 8;
parameter GOT_45c = 9;
parameter GOT_50c = 10;
parameter RETURN_20c = 11;
parameter RETURN_15c = 12;
parameter RETURN_10c = 13;
parameter RETURN_5c = 14;
```

State register defined with **sequential always** block

```
always @ (posedge clk or negedge reset)
    if (!reset) state <= IDLE;
    else state <= next;
```

9/26/2018

6.111 Fall 2018

39

Verilog for the Moore Vender

Next-state logic within a **combinational always** block

```
always @ (state or N or D or Q) begin

    case (state)
        IDLE: if (Q) next = GOT_25c;
              else if (D) next = GOT_10c;
              else if (N) next = GOT_5c;
              else next = IDLE;

        GOT_5c: if (Q) next = GOT_30c;
              else if (D) next = GOT_15c;
              else if (N) next = GOT_10c;
              else next = GOT_5c;

        GOT_10c: if (Q) next = GOT_35c;
              else if (D) next = GOT_20c;
              else if (N) next = GOT_15c;
              else next = GOT_10c;

        GOT_15c: if (Q) next = GOT_40c;
              else if (D) next = GOT_25c;
              else if (N) next = GOT_20c;
              else next = GOT_15c;

        GOT_20c: if (Q) next = GOT_45c;
              else if (D) next = GOT_30c;
              else if (N) next = GOT_25c;
              else next = GOT_20c;
```

```
GOT_25c: if (Q) next = GOT_50c;
         else if (D) next = GOT_35c;
         else if (N) next = GOT_30c;
         else next = GOT_25c;
```

```
GOT_30c: next = IDLE;
GOT_35c: next = RETURN_5c;
GOT_40c: next = RETURN_10c;
GOT_45c: next = RETURN_15c;
GOT_50c: next = RETURN_20c;

RETURN_20c: next = RETURN_10c;
RETURN_15c: next = RETURN_5c;
RETURN_10c: next = IDLE;
RETURN_5c: next = IDLE;

default: next = IDLE;
endcase
end
```

Combinational output assignment


```
assign DC = (state == GOT_30c || state == GOT_35c ||
             state == GOT_40c || state == GOT_45c ||
             state == GOT_50c);
assign DN = (state == RETURN_20c || state == RETURN_15c ||
             state == RETURN_10c);
endmodule
```

9/26/2018

6.111 Fall 2018

40

Simulation of Moore Vender

 


9/26/2018

6.111 Fall 2018

41

FSM Output Glitching

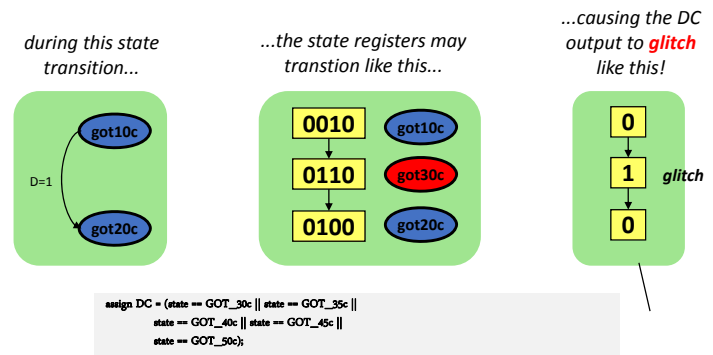- FSM state bits may not transition at precisely the same time
- Combinational logic for outputs may contain hazards
- Result: your FSM outputs may glitch!



If the soda dispenser is glitch-sensitive, your customers can get a 20-cent soda!


9/26/2018

6.111 Fall 2018

42

One way to fix Glitches:

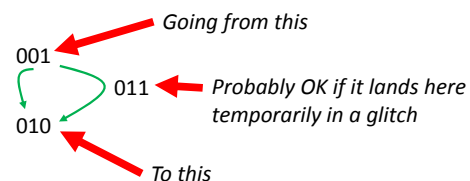- Don't have to have state 3 (3'b011) go into state 4 (3'b100). Use different state naming/use different numbers!!! *A rose by any other name would smell as sweet*
- Perhaps a Gray code (??):
 - Count up like: 000, 001, 011, 010, 110, 111, 101, 100, ...
 - Have the really important/glitch-sensitive states only require transistions of one bit
- One-hot encoding:




9/26/2018

 6.111 Fall 2018

43

Another Solution:
Registered FSM Outputs are Glitch-Free



- Move output generation into the sequential always block
- Calculate outputs based on next state
- Delays outputs by one clock cycle. Problematic in some application.

```

reg DC, DN, DD;

// Sequential always block for state assignment
always @ (posedge clk or negedge reset) begin
    if (!reset)    state <= IDLE;
    else if (clk)  state <= next;

    DC <= (next == GOT_30c || next == GOT_35c ||
           next == GOT_40c || next == GOT_45c ||
           next == GOT_50c);
    DN <= (next == RETURN_5c);
    DD <= (next == RETURN_20c || next == RETURN_15c ||
           next == RETURN_10c);
end

```

Note this is inside an edged always with non-blocking assigns!
This will synthesize to registered outputs!

9/26/2018

6.111 Fall 2018

44


Where should CLK come from?

- Option 1: external crystal
 - Stable, known frequency, typically 50% duty cycle
- Option 2: internal signals
 - Option 2A: output of combinational logic



- No! If inputs to logic change, output may make several transitions before settling to final value → several rising edges, not just one! Hard to design away output glitches...

 - Option 2B: output of a register
 - Okay, but timing of CLK2 won't line up with CLK1



9/26/2018