

Lecture 7

LPset6 is due Wednesday October 3 (not Tuesday)

Lab 3 is Due next Tuesday October 2



10/1/2018

6.111 Fall 2018

1

Pong in History:

- <http://www.pong-story.com/gi.htm>



AY-3-8500 "Ball-and-Paddle" chip

<https://commons.wikimedia.org/wiki/File:AY-3-8500.jpg>


10/1/2018

6.111 Fall 2018

2

Toward FSM Modularity

- Consider the following abstract FSM:

 

- Suppose that each set of states $a_x \dots d_x$ is a "sub-FSM" that produces exactly the same outputs.
- Can we simplify the FSM by removing equivalent states?
No! The outputs may be the same, but the next-state transitions are not.
- This situation closely resembles a **procedure call** or **function call** in software...how can we apply this concept to FSMs?


Acknowledgements: Rex Min

10/1/2018

6.111 Fall 2018

3

The Major/Minor FSM Abstraction

 


- Subtasks are encapsulated in **minor FSMs** with common reset and clock
- Simple communication abstraction:
 - START: tells the minor FSM to begin operation (the call)
 - BUSY: tells the major FSM whether the minor is done (the return)
- The major/minor abstraction is great for...
 - Modular designs (*always* a good thing)
 - Tasks that occur often but in different contexts
 - Tasks that require a variable/unknown period of time
 - Event-driven systems

10/1/2018

6.111 Fall 2018

4


Inside the Major FSM

 

1. Wait until the minor FSM is ready

2. Trigger the minor FSM (and make sure it's started)

3. Wait until the minor FSM is done

 

Variations:



- Usually don't need both Step 1 and Step 3
- One cycle "done" signal instead of multi-cycle "busy"

10/1/2018

6.111 Fall 2018

5

Inside the Minor FSM

  


10/1/2018

6.111 Fall 2018

6


Optimizing the Minor FSM

 Good idea: de-assert BUSY one cycle early



Bad idea #1:

T_4 may not immediately return to T_1

 


10/1/2018

6.111 Fall 2018



7

Bad idea #2:

BUSY never asserts!

 

A Four-FSM Example

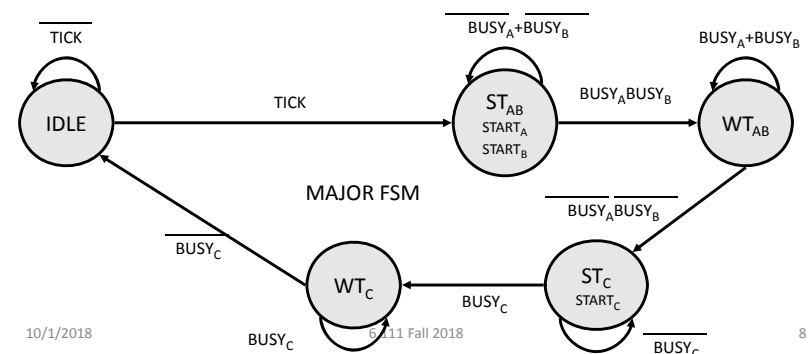 


10/1/2018

6.111 Fall 2018

8

Four-FSM Sample Waveform

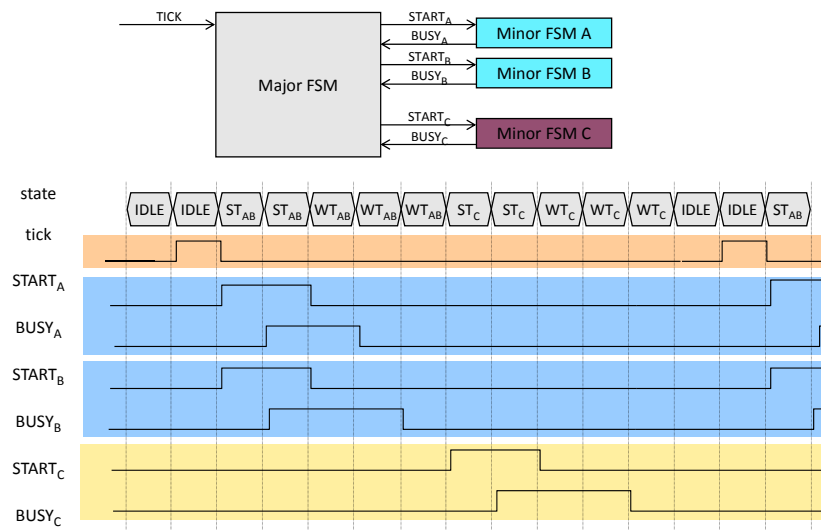


10/1/2018


6.111 Fall 2018

9

Clocking and Synchronous Communication

 

Ideal world:

 


M1 and M2 clock edges aligned in time

10/1/2018

6.111 Fall 2018

10


Clock Skew

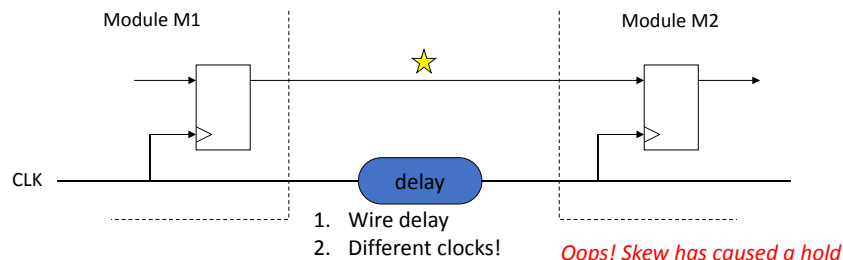

1. Wire delay
2. Different clocks!

Oops! Skew has caused a hold time problem!

Real world has clock skew:

 


M2 clock delayed with respect to M1 clock

10/1/2018

6.111 Fall 2018

11

Low-skew Clocking in FPGAs

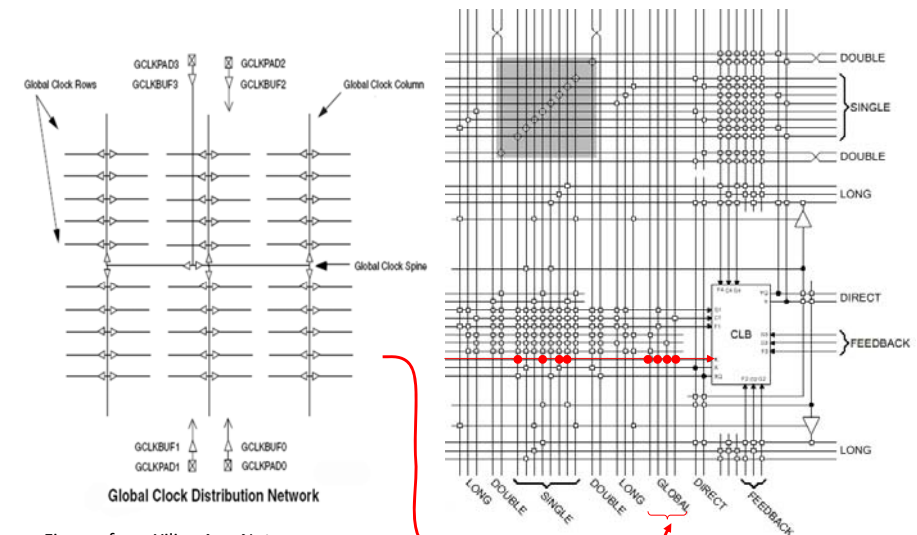

Figures from Xilinx App Notes

10/1/2018


6.111 Fall 2018

12

Goal: use as few clock domains as possible

Suppose we wanted clocks at $f/2$, $f/4$, $f/8$, etc.:
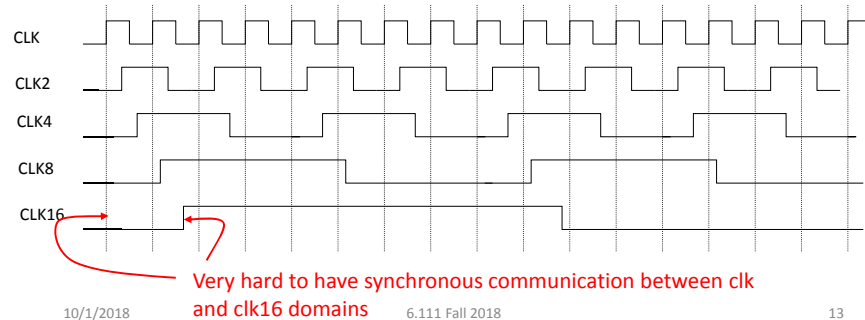
```
reg clk2,clk4,clk8,clk16;
always @(posedge clk) clk2 <= ~clk2;
always @(posedge clk2) clk4 <= ~clk4;
always @(posedge clk4) clk8 <= ~clk8;
always @(posedge clk8) clk16 <= ~clk16;
```



10/1/2018 6.111 Fall 2018

13


Solution: 1 clock, many enables

Use one (high speed) clock, but create enable signals to select a subset of the edges to use for a particular piece of sequential logic

```
reg [3:0] count;
always @(posedge clk) count <= count + 1; // counts 0..15
```

```
wire enb2 = (count[0] == 1'b1);
wire enb4 = (count[1:0] == 2'b11);
wire enb8 = (count[2:0] == 3'b111);
wire enb16 = (count[3:0] == 4'b1111);
```
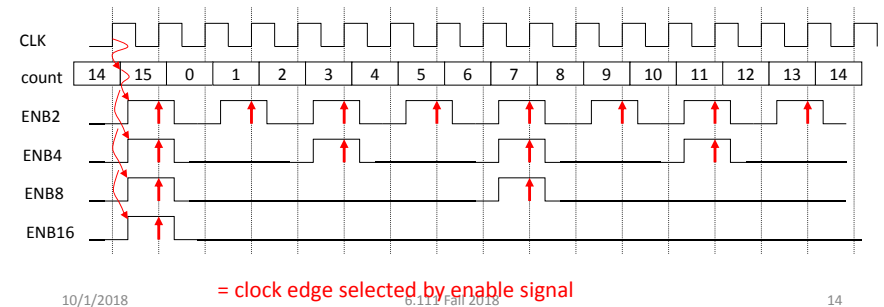
```
always @(posedge clk)
if (enb2) begin
// get here every 2nd cycle
end
```



10/1/2018 6.111 Fall 2018

14

Using External Clocks


IOB stands for Input/Output Block

Sometimes you need to communicate synchronously with circuitry outside of the FPGA (memories, I/O, ...)

Problem: different delays along internal paths for DATA and CLK change timing relationship

Solutions:

 - 1) Bound internal delay from pin to internal reg; add that delay to setup time (t_{SU}) specification
- 2) Make internal clock edge aligned with external clock edge (but what about delay of pad and clock driver)




10/1/2018

6.111 Fall 2018

15

 1) Bound Internal Data Delay

Solution: use registers built into the IOB pin interface:




10/1/2018

6.111 Fall 2018

16

2) Align external and internal clocks

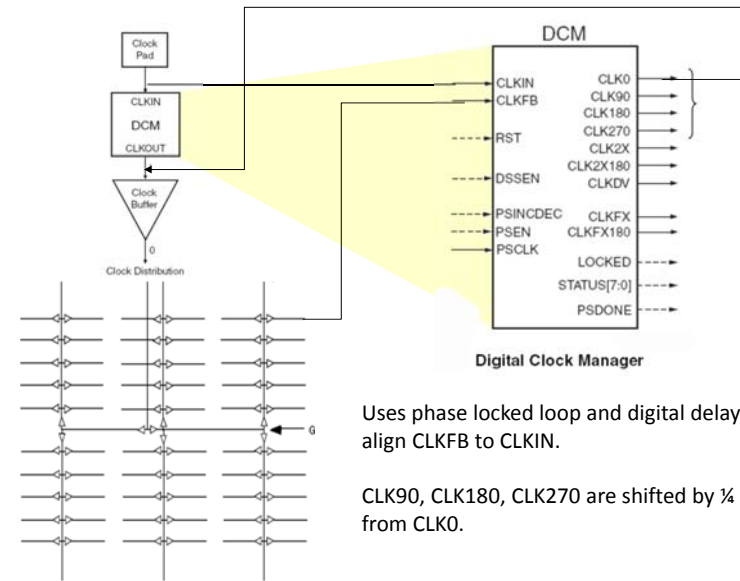


10/1/2018

6.111 Fall 2018

17

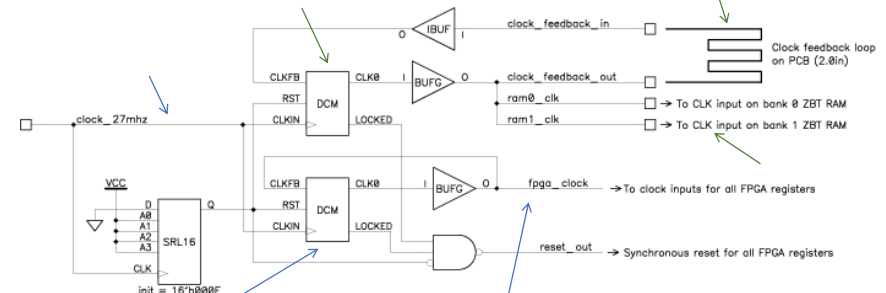Example: Labkit ZBT interface

The upper DCM is used to generate the de-skewed clock for the external ZBT memories. The feedback loop for this DCM includes a 2.0 inch long trace on the labkit PCB and matches in distance all of the PCB traces from the FPGA to the ZBT memories. The propagation delay from the output of the upper DCM back to its CLKFB input should be almost exactly the same as the propagation delay from the DCM output to the ZBT memories.



The lower DCM is used to ensure that the fpga_clock signal, which clocks all of the FPGA flip-flops, is in phase with the reference clock (clock_27mhz).


10/1/2018

6.111 Fall 2018

18

Generating Other Clock Frequencies (again)

 The labkit has a 27MHz crystal (37ns period). Use DCM to generate other frequencies e.g., 65MHz to generate 1024x768 VGA video.



The DCM (ISE only) can also synthesize certain multiples of the CLKIN frequency (eg, multiples of 27MHz):

$$f_{CLKFX} = \left(\frac{M}{D} \right) f_{CLKIN}$$

Where M = 2--32 and D = 2--32 with a output frequency of range of 24MHz to 210MHz.

Vivado uses a Clock Wizard to simplify clock generation.

10/1/2018

6.111 Fall 2018

19

Verilog to generate 65MHz clock

```
// use FPGA's digital clock manager to produce a
// 65MHz clock (actually 64.8MHz)
wire clock_65mhz_unbuf, clock_65mhz;
DCM vc1k1(.CLKIN(clock_27mhz), .CLKFX(clock_65mhz_unbuf));
// synthesis attribute CLKFX_DIVIDE of vc1k1 is 10
// synthesis attribute CLKFX_MULTIPLY of vc1k1 is 24
// synthesis attribute CLK_FEEDBACK of vc1k1 is NONE
// synthesis attribute CLKIN_PERIOD of vc1k1 is 37
BUFG vc1k2(.O(clock_65mhz), .I(clock_65mhz_unbuf));
```

$$f_{CLKFX} = \left(\frac{24}{10} \right) (27MHz) = 64.8MHz$$

10/1/2018

6.111 Fall 2018


20

Where do we get frequencies?



16MHz Crystal

 - Most frequencies come from Crystal Oscillators made of quartz
- Equivalent to very High-Q LRC tank circuits
- https://en.wikipedia.org/wiki/Crystal_oscillator_frequencies
- Incorporate into circuit like that below and boom, you've got a square wave of some specified frequency dependent largely on the crystal



<http://www.z80.info/uexosc.htm>

https://en.wikipedia.org/wiki/Crystal_oscillator

10/1/2018

21

High Frequencies

- Very hard to get a crystal oscillator to operate above ~200 MHz (7th harmonic of resonance of crystal itself, which usually is limited to about 30 MHz due to fabrication limitations)
- Where does the 2.33 GHz clock of my iPhone come from then?
- Frequency Multipliers!

10/1/2018

22


Voltage Controlled Oscillator

- It is very easy to make voltage-controlled oscillators that run up to 1GHz or more.

- Why don't we just:



 - Pick the voltage V_i that is needed to get the frequency we want f_o ? That's gotta be specified right?
- Same reason we don't see op amps in open loop out in the wild...they are too unstable...gotta place them in negative feedback



A simple VCO (not type found in FPGA)


10/1/2018

<http://www.electronicshub.org/voltage-controlled-oscillators-vco/>

23

Phase Locked Loop

 - Place the unstable, but capable VCO in a feedback loop.
- This type of circuit is a phase-locked loop variant




10/1/2018

24

Phase Locked Loop

 
- Circuit that can track an input phase of a system and reproduce it at the output



10/1/2018

25

Phase, Frequency Detector


 


10/1/2018

26

Phase Detector

- Can be a simple XOR gate

  

- If near the desired frequency already this can work...if it is too far out, it won't and can be very unreliable since phase and frequency are related but not quite the same thing, it will lock onto harmonics, etc...


- For frequency we instead use a PFD:
 - Phase/Frequency Detector:

10/1/2018

27

Phase-Frequency Detection

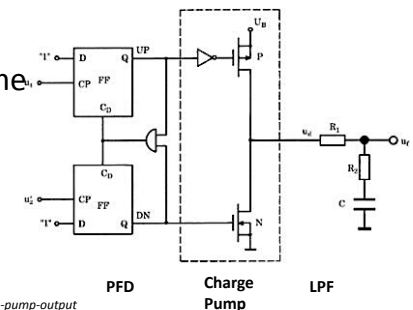- Detects both change and which clock signal is consistently leading the other one
- Using MOSFETs you charge/discharge a capacitor accordingly which also with some resistors low-pass filter's the signal
- The output voltage is then roughly proportional to the frequency error!




<http://www.globalspec.com/reference/72819/203279/2-7-phase-detectors-with-charge-pump-output>

10/1/2018

28

Phase Frequency Detection

 


10/1/2018

6.111 Fall 2018

29

PFD, Charge Pump, LP Filter

 


- So this circuit can make $f_o = f_{ref}$ That doesn't help us!
- How can we make a higher frequency?

10/1/2018

30

 Use Resistors in Voltage Divider in Feedback Path!



- A voltage divider in feedback path gives us voltage gain!

$$K = \frac{1}{1 - p + G} \quad p \approx 0.9999 \text{ means} \quad K = \frac{1}{G}$$

$$G = \frac{R_1}{R_1 + R_2}$$

The gain A_v of this circuit is therefore:

$$A_v = \frac{R_1 + R_2}{R_1}$$


The gain of a "non-inverting amplifier"

$$V_- = V_o \frac{R_1}{R_1 + R_2}$$

10/1/2018

31

Use a Clock Divider in Feedback Path!

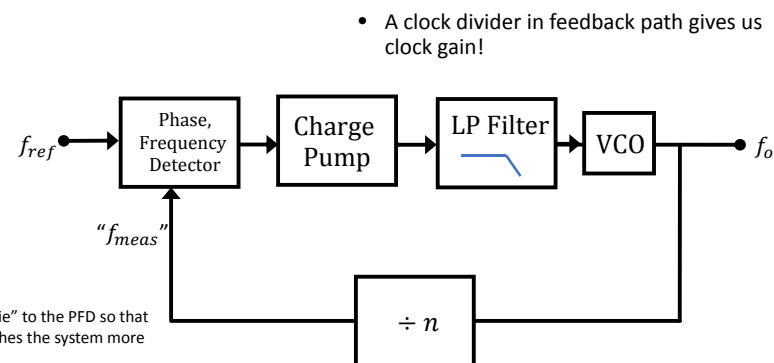


- A clock divider in feedback path gives us clock gain!

We "lie" to the PFD so that it pushes the system more

10/1/2018

32

Use a Clock Divider in Feedback Path!

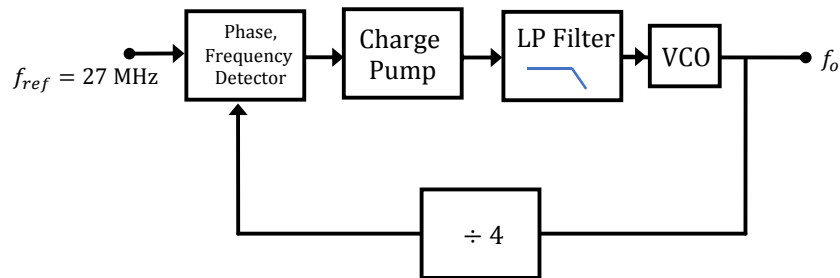

```

reg clk2,clk4,clk8,clk16;
always @(posedge clk) clk2 <= ~clk2;
always @(posedge clk2) clk4 <= ~clk4;
always @(posedge clk4) clk8 <= ~clk8;
always @(posedge clk8) clk16 <= ~clk16;
  
```

10/1/2018

33

RESETEing to a known state

Just after configuration, all the registers/memories are in a known state (eg, default value for regs is 0). But you may need to include a RESET signal to set the initial state to what you want. *Note the Verilog initial block only works in simulation and has no effect when synthesizing hardware.*

Solution: have your logic take a RESET signal which can be asserted on start up and by an external push button:

```

// power-on reset generation
wire power_on_reset; // remain high for first 16 clocks
SRL16 reset_sr (.D(1'b0), .CLK(clock_27mhz), .Q(power_on_reset),
               .A0(1'b1), .A1(1'b1), .A2(1'b1),
               .A3(1'b1));
defparam reset_sr.INIT = 16'hFFFF;

// ENTER button is user reset
wire reset,user_reset;
debounce db1(.reset(power_on_reset),.clock(clock_27mhz),
             .noisy(~button_enter),.clean(user_reset));
assign reset = user_reset | power_on_reset;
  
```

10/1/2018

6.111 Fall 2018

34

Debugging: making the state visible

To figure out what your circuit is doing it can be very useful to include logic that makes various pieces of state visible to the outside world. Some suggestions:

- **turn the leds on and off** to signal events, entry into particular pieces of code, etc.
 - **use the 16-character fluorescent display** to show more complex state information
 - **drive useful data onto the ANALYZER pins** and use the adapters to hook them up to the logic analyzer. Include your master clock signal and the configure the logic analyzer to sample the data on the non-active edge of the clock (to avoid setup and hold problems introduced by I/O pad delays). The logic analyzer can capture thousands of cycles of data and display the results in useful ways (including interpreting multi-bit data as samples of an analog waveform).
- magnivue can get down to 125 ps sample period! Great for finding glitches

10/1/2018

6.111 Fall 2018

35

Encoding numbers

It is straightforward to encode positive integers as a sequence of bits. Each bit is assigned a weight. Ordered from right to left, these weights are increasing powers of 2. The value of an n-bit number encoded in this fashion is given by the following formula:

$$v = \sum_{i=0}^{n-1} 2^i b_i$$

$$\begin{array}{cccccccc} 2^{11} & 2^{10} & 2^9 & 2^8 & 2^7 & 2^6 & 2^5 & 2^4 & 2^3 & 2^2 & 2^1 & 2^0 \\ \hline 0 & 1 & 1 & 1 & 1 & 1 & 0 & 1 & 0 & 0 & 0 & 0 \end{array} = 2000_{10}$$

7 d 0

Oftentimes we will find it convenient to cluster groups of bits together for a more compact notation. Two popular groupings are clusters of 3 bits and 4 bits.

03720
Octal - base 8

0x7d0
Hexadecimal - base 16

000 - 0	0000 - 0	1000 - 8
001 - 1	0001 - 1	1001 - 9
010 - 2	0010 - 2	1010 - a
011 - 3	0011 - 3	1011 - b
100 - 4	0100 - 4	1100 - c
101 - 5	0101 - 5	1101 - d
110 - 6	0110 - 6	1110 - e
111 - 7	0111 - 7	1111 - f

10/1/2018

6.111 Fall 2018

36

Binary Representation of Numbers

How to represent negative numbers?

- Three common schemes:
 - sign-magnitude, ones complement, twos complement
- **Sign-magnitude:** MSB = 0 for positive, 1 for negative
 - Range: $-(2^{N-1} - 1)$ to $+(2^{N-1} - 1)$
 - Two representations for zero: 0000... & 1000...
 - Simple multiplication but complicated addition/subtraction
- **Ones complement:** if N is positive then its negative is \bar{N}
 - Example: 0111 = 7, 1000 = -7
 - Range: $-(2^{N-1} - 1)$ to $+(2^{N-1} - 1)$
 - Two representations for zero: 0000... & 1111...
 - Subtraction is addition followed by end-around carry (subtraction is different from addition unit)

10/1/2018

6.111 Fall 2018

37

Representing negative integers

To keep our arithmetic circuits simple, we'd like to find a representation for negative numbers so that we can use a single operation (binary addition) when we wish to find the sum of two integers, independent of whether they are positive or negative.

We certainly want $A + (-A) = 0$. Consider the following 8-bit binary addition where we only keep 8 bits of the result:

$$\begin{array}{r} 11111111 \\ + 00000001 \\ \hline 00000000 \end{array}$$

which implies that the 8-bit representation of -1 is 11111111. More generally

Negation:
Complement and add 1

$$\begin{aligned} -A &= 0 - A \\ &= (-1 + 1) - A \\ &= (-1 - A) + 1 \\ &= \sim A + 1 \end{aligned}$$

~ means bit-wise complement


1	1	1	1	1	1	1	1
A_7	A_6	A_5	A_4	A_3	A_2	A_1	A_0

10/1/2018

6.111 Fall 2018

38

Signed integers: 2's complement

 

8-bit 2's complement example:

$$11010110 = -2^7 + 2^6 + 2^4 + 2^2 + 2^1 = -128 + 64 + 16 + 4 + 2 = -42$$

If we use a two's complement representation for signed integers, the same binary addition mod 2^n procedure will work for adding positive and negative numbers (don't need separate subtraction rules). The same procedure will also handle unsigned numbers!

By moving the implicit location of "decimal" point, we can represent fractions too:

$$1101.0110 = -2^3 + 2^2 + 2^0 + 2^{-2} + 2^{-3} = -8 + 4 + 1 + 0.25 + 0.125 = -2.625$$

10/1/2018

6.111 Fall 2018

39

Sign extension

Consider the 8-bit 2's complement representation of:

$$\begin{aligned} 42 &= 00101010 & -5 &= \sim 00000101 + 1 \\ & & &= 11111010 + 1 \\ & & &= 11111011 \end{aligned}$$

What is their 16-bit 2's complement representation?

$$42 = 0000000000101010$$

$$-5 = 1111111111111011$$

Extend the MSB (aka the "sign bit") into the higher-order bit positions

10/1/2018

6.111 Fall 2018

40

Using Signed Arithmetic in Verilog

BE CAUTIOUS

```
reg signed [63:0] data;  
wire signed [7:0] vector;  
input signed [31:0] a;  
function signed [128:0] alu;
```

```
16'hC501 //an unsigned 16-bit hex value  
16'shC501 //a signed 16-bit hex value
```

16'ghC501

Use care with signed arithmetic!

```
wire signed [7:0] total;  
wire [3:0] counter; // max value 15, counting widgets off the mfg line  
wire signed [5:0] available;
```

```
assign total = available + counter; // does this give the correct answer?  
//NO! counter = 4'b1111 is treated as -1. Need to "append" a leading zero
```

```
assign total = available + {1'b0, counter}; // or use $unsigned()  
assign total = available + $unsigned(counter);
```

10/1/2018

6.111 Fall 2018

41

Using Signed Arithmetic in Verilog

“<<<” and “>>>” tokens result in arithmetic (signed) left and right shifts: multiple by 2 and divide by 2.

Right shifts will maintain the sign by filling in with sign bit values during shift

wire signed [3:0] value = 4'b1000; // -8

value >> 2 // results in 0010 or 2

value >>> 2 // results in 1110 or -2

10/1/2018

6.111 Fall 2018

42

Using Signed Arithmetic in Verilog

ALL OF THE FOLLOWING ARE TREATED AS UNSIGNED IN VERILOG!!!

- Any operation on two operands, unless **both operands are signed**
- Based numbers (e.g. 12'd10), unless the explicit “s” modifier is used)
- Bit-select results `a[5]`
- Part-select results `a[4:2]`
- Concatenations

```
reg [15:0] a; // Unsigned  
reg signed [15:0] b;  
wire signed [16:0] signed_a;  
wire signed [31:0] a_mult_b;
```

```
assign signed_a = a;//Convert to signed  
assign a_mult_b = signed_a * b
```

Example of multiplying signed by unsigned

<http://billauer.co.il/blog/2012/10/signed-arithmetics-verilog/>

10/1/2018

6.111 Fall 2018

43

For example:

```
module jdoodle;  
  reg signed [3:0] x;  
  reg [3:0] y;  
  reg signed [8:0] z;  
  initial begin  
    x = -2;  
    y=3;  
    z = x*y;  
    $display(x, y, z);  
    $finish;  
  end  
endmodule
```

Result:

-2 3 42

```
module jdoodle;  
  reg signed [3:0] x;  
  reg signed [3:0] y;  
  reg signed [8:0] z;  
  initial begin  
    x = -2;  
    y=3;  
    z = x*y;  
    $display(x, y, z);  
    $finish;  
  end  
endmodule
```

Result:


-2 3 -6

10/1/2018

6.111 Fall 2018

44

Memory Controller

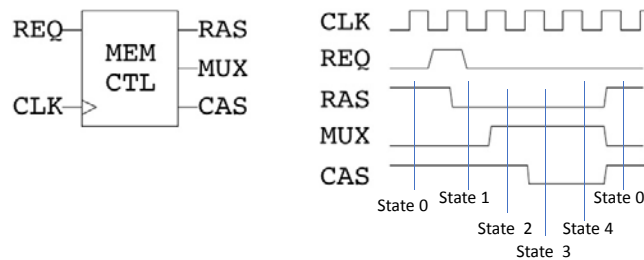

10/1/2018

6.111 Fall 2018

45

1GB RAM




10/1/2018

6.111 Fall 2018

46

FSM

 

```
always @(posedge clock)
    state <= next_state;
```

```
always @ *
begin // logic to determine next_state
    case (state)
        state_1: next_state = . . .
        state_2: next_state = . . .
        . . .
        default: next_state = STATE_0;
    endcase
end
```

10/1/2018

6.111 Fall 2018

47

Potentially Glitchy Solution

```
module (
    input req, clk,
    output ras, mux, cas
);

reg [3:0] state, next_state;


parameter [3:0] STATE_0 = 0; // 0000
parameter [3:0] STATE_1 = 1; // 0001
parameter [3:0] STATE_2 = 2; // 0010
parameter [3:0] STATE_3 = 3; // 0011
parameter [3:0] STATE_4 = 4; // 0100

always @(posedge clk) state <= next_state;

always @ * begin
    case (state)
        STATE_0: next_state = req ? STATE_1 : STATE_0;
        STATE_1: next_state = STATE_2;
        STATE_2: next_state = STATE_3;
        STATE_3: next_state = STATE_4;
        STATE_4: next_state = STATE_0;
        default: next_state = state_0;
    endcase
end

assign ras = !((state==STATE_1)|| (state==STATE_2)|| (state==STATE_3)|| (state==STATE_4));
assign mux = (state==STATE_2)|| (state==STATE_3)|| (state==STATE_4);
assign cas = !((state==STATE_3)|| (state==STATE_4));

endmodule
```

 


10/1/2018

6.111 Fall 2018

48

FSM Output Glitching

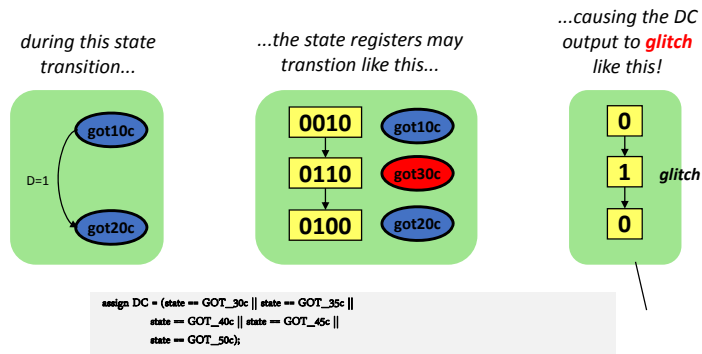- FSM state bits may not transition at precisely the same time
- Combinational logic for outputs may contain hazards
- Result: your FSM outputs may glitch!




If the soda dispenser is glitch-sensitive, your customers can get a 20-cent soda!

10/1/2018

6.111 Fall 2018

49

Registered FSM Outputs are Glitch-Free

 

- Move output generation into the sequential always block
- Calculate outputs based on next state
- Delays outputs by one clock cycle. Problematic in some application.

```
reg DC,DN,DD;

// Sequential always block for state assignment
always @(posedge clk or negedge reset) begin
    if (!reset) state <= IDLE;
    else if (clk) state <= next;

    DC <= (next == GOT_30c || next == GOT_35c ||
next == GOT_40c || next == GOT_45c ||
next == GOT_50c);
    DN <= (next == RETURN_5c);
    DD <= (next == RETURN_20c || next == RETURN_15c ||
next == RETURN_10c);
end
```

10/1/2018

6.111 Fall 2018

50

Glitchy Solution

```
module (
    input req, clk,
    output reg ras, mux, cas
);

reg [3:0] state, next_state;

parameter [3:0] STATE_0 = 0; // 0000
parameter [3:0] STATE_1 = 1; // 0001
parameter [3:0] STATE_2 = 2; // 0010
parameter [3:0] STATE_3 = 3; // 0011
parameter [3:0] STATE_4 = 4; // 0100

always @(posedge clk) state <= next_state;

always @ * begin
    case (state)
        STATE_0: next_state = req ? STATE_1 : STATE_0;
        STATE_1: next_state = STATE_2;
        STATE_2: next_state = STATE_3;
        STATE_3: next_state = STATE_4;
        STATE_4: next_state = STATE_0;
        default: next_state = state_0;
    endcase
end

assign ras = !((state==STATE_1)||((state==STATE_2)||((state==STATE_3)||((state==STATE_4)))));
assign mux = ((state==STATE_2)||((state==STATE_3)||((state==STATE_4)||((state==STATE_0)))));
assign cas = !((state==STATE_3)||((state==STATE_4)||((state==STATE_0)||((state==STATE_1)))));

endmodule
```

10/1/2018

6.111 Fall 2018

51

Another Glitch Free Solution

```
module (
    input req, clk,
    output reg ras, mux, cas
);

reg [3:0] state, next_state;

parameter [3:0] STATE_0 = 4'b1010;
parameter [3:0] STATE_1 = 4'b0010;
parameter [3:0] STATE_2 = 4'b0110;
parameter [3:0] STATE_3 = 4'b0100;
parameter [3:0] STATE_4 = 4'b0101;

always @(posedge clk) state <= next_state;

always @ * begin
    case (state)
        STATE_0: next_state = req ? STATE_1 : STATE_0;
        STATE_1: next_state = STATE_2;
        STATE_2: next_state = STATE_3;
        STATE_3: next_state = STATE_4;
        STATE_4: next_state = STATE_0;
        default: next_state = STATE_0;
    endcase
end

assign {ras, mux, cas} = {state[3],state[2],state[1]};

endmodule
```

Hint: You will need four bits for your state variable.

10/1/2018

6.111 Fall 2018

52

Alternative Verilog

```
module (
    input req, clk,
    output reg ras, mux, cas
);
```


```
reg [3:0] state, next_state;
```

```
parameter [3:0] STATE_0 = 4'b01010;
parameter [3:0] STATE_1 = 4'b0010;
parameter [3:0] STATE_2 = 4'b0110;
parameter [3:0] STATE_3 = 4'b0100;
parameter [3:0] STATE_4 = 4'b0101;
```

```
always @(posedge clk) state <= next_state;
```

```
always @* begin
    case (state)
        STATE_0: next_state = req ? STATE_1 : STATE_0;
        STATE_1: next_state = STATE_2;
        STATE_2: next_state = STATE_3;
        STATE_3: next_state = STATE_4;
        STATE_4: next_state = STATE_0;
        default: next_state = STATE_0;
    endcase
end
assign {ras, mux, cas} = {state[3], state[2], state[1]};
```

```
endmodule
```

 

```
// next_state not needed
always @(posedge clk) begin
    case (state)
        STATE_0: state <= req ? STATE_1 : STATE_0;
        STATE_1: state <= STATE_2;
        STATE_2: state <= STATE_3;
        STATE_3: state <= STATE_4;
        STATE_4: state <= STATE_0;
        default: state <= STATE_0;
    endcase
end
```


10/1/2018

6.111 Fall 2018

53

Could a Glitchy solution actually not glitch?

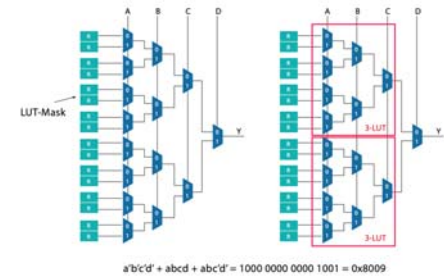ISE develops its combinational solutions using Lookup Tables (has 10,000s of them)



LUTs are basically multiplexers with SRAM to hold 0's and 1's at inputs

```
assign ras = ~(state==STATE_1)[(state==STATE_2)][(state==STATE_3)][(state==STATE_4)];
assign mux = (state==STATE_2)[(state==STATE_3)][(state==STATE_4)];
assign cas = ~(state==STATE_3)[(state==STATE_4)];
```

Configurations

Look-Up Table

Virtex-II function generators are implemented as 4-input look-up tables (LUTs). Four independent inputs are provided to each of the two function generators in a slice (F and G). These function generators are each capable of implementing any arbitrarily defined boolean function of four inputs. The propagation delay is therefore independent of the function implemented. Signals from the function generators can exit the slice (X or Y output), can input the XOR dedicated gate (see arithmetic logic), or input the carry logic multiplexer (see fast look-ahead carry logic), or feed the D input of the storage element, or go to the MUXFS (not shown in Figure 10).

10/1/2018

6.111 Fall 2018

54

Verilog Grading

Logistics

- Verilog submission with 2 days after lab checkoff. Lab must be checkoff first.
- Resubmission for regrade permitted for Lab 2 and Lab 3 only (email grader for regrading)

Grading


- Proper use of blocking and non-blocking assignments
- Readable Code with comments and consistent indenting
- Use of default in case statement
- Use of parameter statements for symbolic name and constants (state==5 vs state==DATA_READY)
- Parameterized modules when appropriate
- Readable logical flow, properly formatted (see "Verilog Editors")
- No long nested if statements.
- 20% off for each occurrence.

10/1/2018

6.111 Fall 2018

55

Nexys 4 - DDR

 

\$179 9/2017

6.111 Fall 2017


Lecture 7

56

Low Cost FPGA Boards



 - Basys3
 - Artix-7 FPGA
 - 12 bit VGA
 - Switches/LEDs
 - \$89 (9/2017)
 - Vivado Webpack



- PYNQ-Z1
 - 650MHz dual core Cortex A9
 - Artix-7
 - 512MB DDR3
 - \$65 (9/2017)
 - Vivado Webpack

10/1/2018

6.111 Fall 2018

57