



Analog Building Blocks

- Sampling theorem
- Undersampling, antialiasing
- FIR digital filters
- Quantization noise, oversampling
- OpAmps, DACs, ADCs


Handouts

- lecture slides,
- Lpset 8

Fri: Lab 4 Checkoff
Tue: form project teams

Cyclic redundancy check - CRC
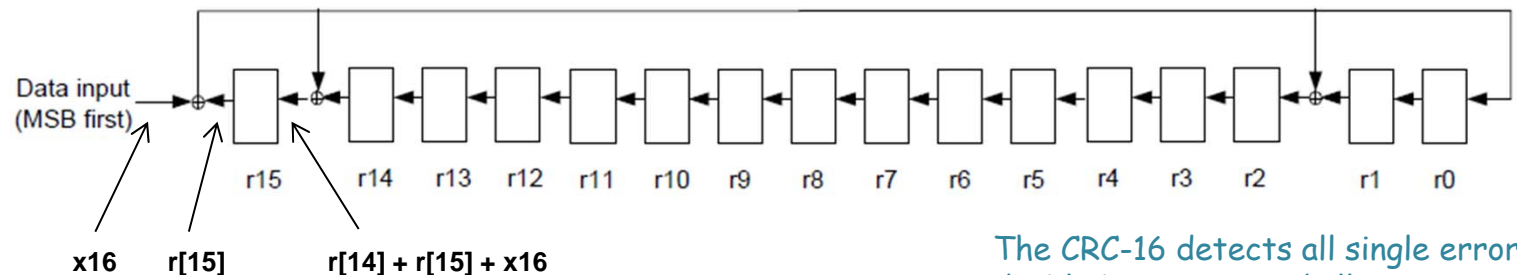
$$\text{CRC16 } (x^{16} + x^{15} + x^2 + 1)$$



The CRC-16 detects all single errors, all double bit errors and all errors with burst less than 16 bits in length.

- Each “r” is a register, all clocked with a common clock. Common clock not shown
- As shown, for register r_{15} , the output is $r[15]$ and the input is the sum of $r[14]$, $r[15]$ and data input x_{16} , etc
- The small round circles with the plus sign are adders implemented with XOR gates.
- Initialize r to 16'hFFFF at start

CRC Solution

CRC16: $x^{16} + x^{15} + x^2 + 1$

```

module lpset6(
    input clock,
    input start,
    input data,
    output done,
    output reg [15:0] r
);
    parameter IDLE=0;
    parameter CRC_CALC=1;

    wire x16 = data;
    reg state=0;
    reg [5:0] counter=0; //my counter




    always @ (posedge clock) begin
        case (state)
            IDLE: begin
                state <= (start) ? CRC_CALC : IDLE;
                r <= 16'hFFFF; //start reset FSM
                counter <= 47;
            end

            CRC_CALC: begin
                r[15] <= r[14] + r[15] + x16;
                r[14:3] <= r[13:2];
                r[2] <= r[1] + r[15] + x16;
                r[1] <= r[0];
                r[0] <= r[15] + x16;
                counter <= counter - 1;
                state <= (counter == 1) ? IDLE : CRC_CALC;
            end

        endcase
    end


    assign done = (counter == 0);
endmodule

```

 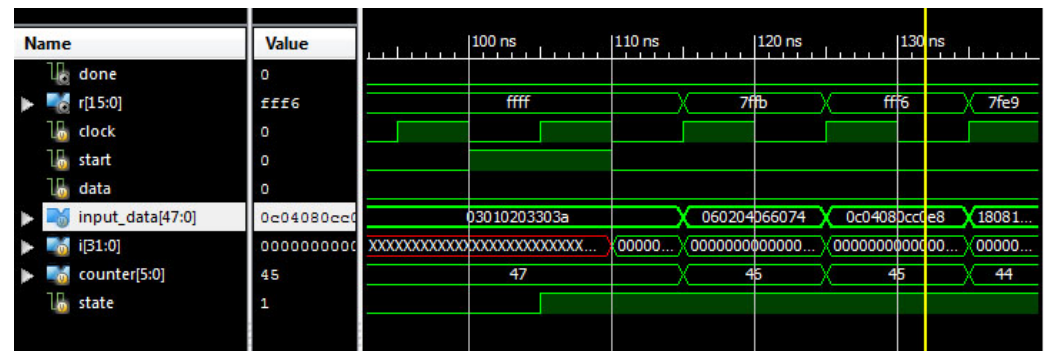 


Digital Representations of Analog Waveforms

Continuous time
Continuous values

 

Discrete time
Discrete values

 


Discrete Time


Let's use an **impulse train** to sample a continuous-time function at a regular interval T :

$\delta(x)$ is a narrow impulse at $x=0$,
where $\int_{-\infty}^{\infty} f(t)\delta(t-a)dt = f(a)$
 
$$p(t) = \sum_{n=-\infty}^{\infty} \delta(t - nT)$$




Time Domain

 


Reconstruction

 Is it possible to reconstruct the original waveform using only the discrete time samples?





Frequency Domain

 Looks like modulation by ω_s and its harmonics



  So, if $\omega_m < \omega_s - \omega_m$, we can recover the original waveform with a low-pass filter!



Sampling Theorem

Let $x(t)$ be a band-limited signal, ie, $X(j\omega)=0$ for $|\omega| > \omega_M$. Then $x(t)$ is uniquely determined by its samples $x(nT)$, $n = 0, \pm 1, \pm 2, \dots$, if

$$\omega_s > 2\omega_M$$

where

$$\omega_s = \frac{2\pi}{T}$$





$2\omega_M$ is called the "Nyquist rate" and $\omega_s/2$ the "Nyquist frequency"

Given these samples, we can reconstruct $x(t)$ by generating a periodic impulse train in which successive impulses have amplitudes that are successive sample values, then passing the train through an ideal LPF with gain T and a cutoff frequency greater than ω_M and less than $\omega_s - \omega_M$.


Undersampling → Aliasing

If $\omega_s \leq 2\omega_M$ there's an overlap of frequencies between one image and its neighbors and we discover that those overlaps introduce additional frequency content in the sampled signal, a phenomenon called **aliasing**.

$$\omega_M = 5, \omega_s = 6$$

  


 There are now tones at 1 (= 6 - 5) and 4 (= 6 - 2) in addition to the original tones at 2 and 5.



Antialias Filters

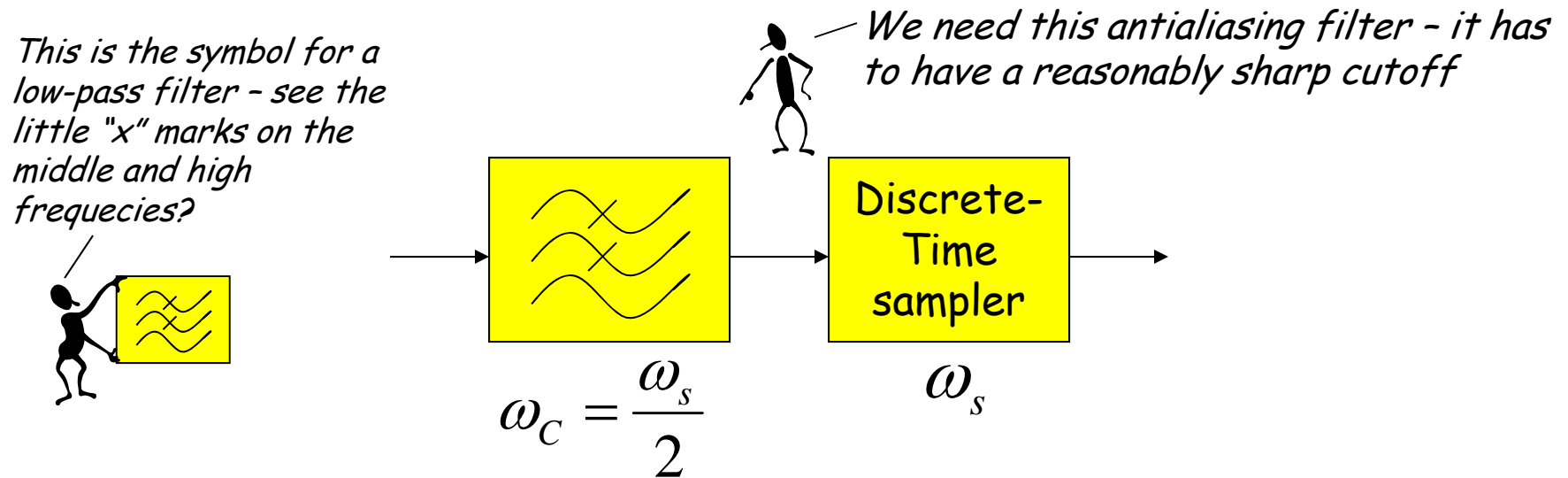If we wish to create samples at some fixed frequency ω_s , then to avoid aliasing we need to use a low-pass filter on the original waveform to remove any frequency content $\geq \omega_s/2$.



The frequency response of human ears essentially drops to zero above 20kHz. So the "Red Book" standard for CD Audio chose a 44.1kHz sampling rate, yielding a Nyquist frequency of 22.05kHz. The 2kHz of elbow room is needed because practical antialiasing filters have finite slope...


$$f_s = (3 \text{ samples/line})(490 \text{ lines/frame})(30 \text{ frames/s}) = 44.1 \text{ kHz}$$

More info: <http://www.cs.columbia.edu/~hgs/audio/44.1.html>

Digital Filters

Equation for an N-tap finite impulse response (FIR) filter:

$$y[n] = \sum_{k=0}^N b_k x[n-k]$$

 


What components are part of the t_{PD} of this circuit?
How does t_{PD} grow as N gets larger?

Filter coefficients

- Use Matlab command: $b = \text{fir1}(N, \omega_c/(\omega_s/2))$
 - N is the number of taps (we'll get $N+1$ coefficients). Larger N gives sharper roll-off in filter response; usually want N to be as large as reasonably possible.
 - ω_c is the cutoff frequency (3kHz in Lab 5)
 - ω_s is the sample frequency (48kHz in Lab 5)
 - The second argument to the `fir1` command is the cutoff frequency as a fraction of the Nyquist frequency (i.e., half the sample rate).
 - By default you get a lowpass filter, but can also ask for a highpass, bandpass, bandstop.
- The b coefficients are real numbers between 0 and 1. But since we don't want to do floating point arithmetic, we usually scale them by some power of two and then round to integers.
 - Since coefficients are scaled by 2^S , we'll have to re-scale the answer by dividing by 2^S . But this is easy - just get rid of the bottom S bits!


Retiming the FIR circuit

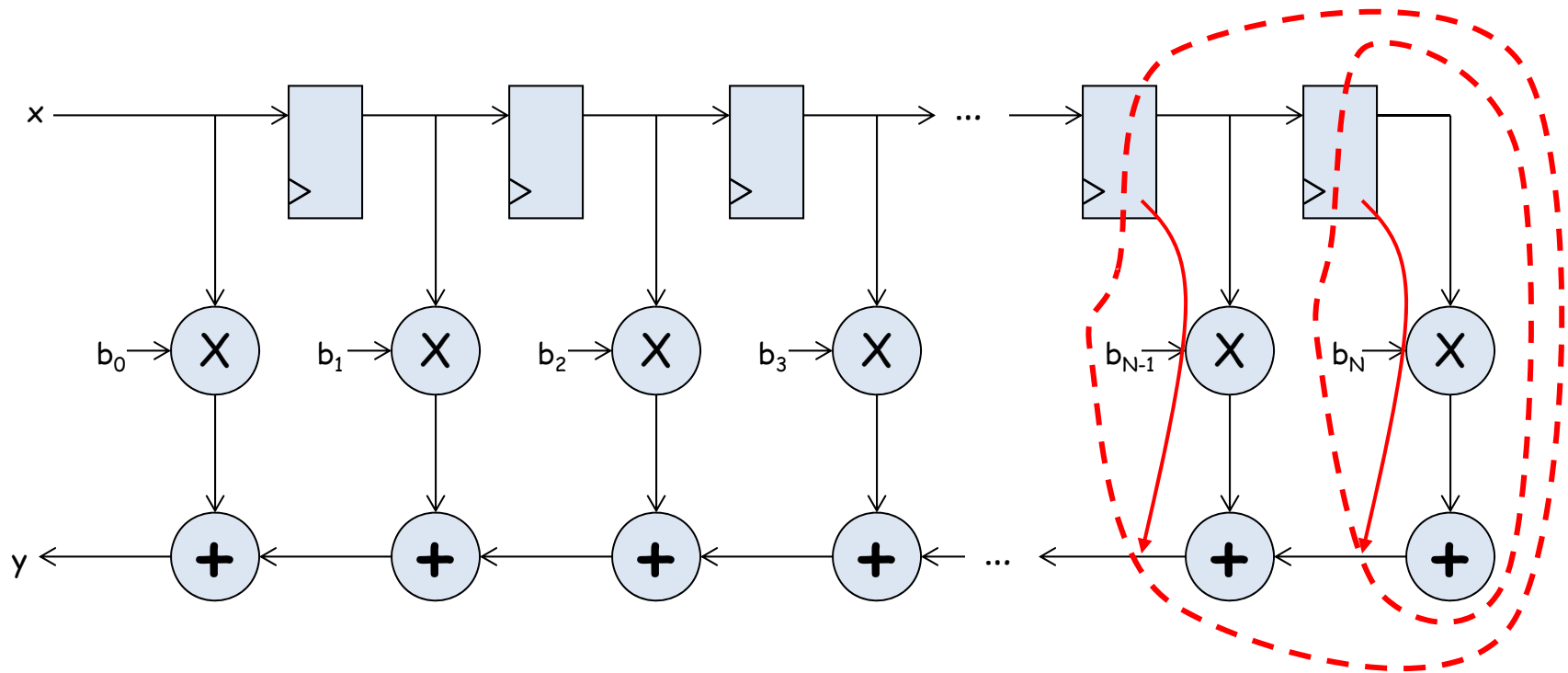Apply the cut-set retiming transformation repeatedly...




Retimed FIR filter circuit

"Transposed Form" of a FIR filter

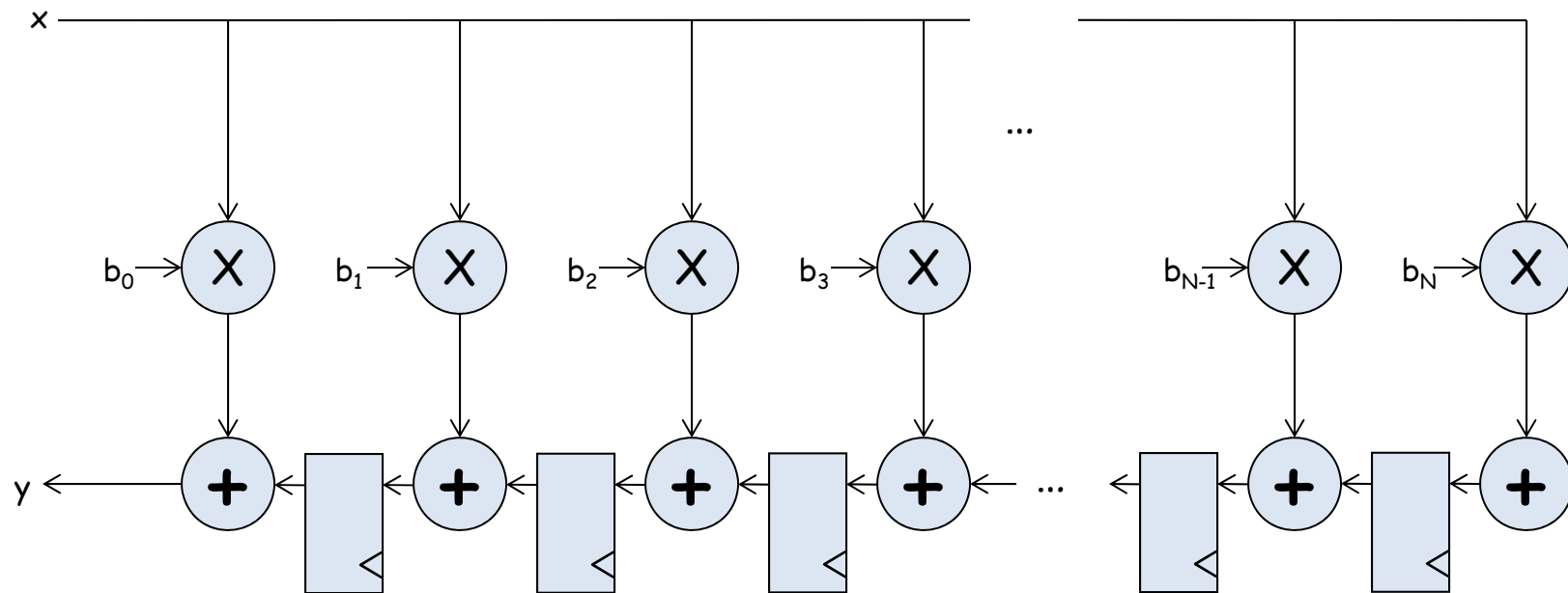

What components are part of the t_{PD} of this circuit?
How does t_{PD} grow as N gets larger?

N-tap FIR: less hardware, N+1 cycles...

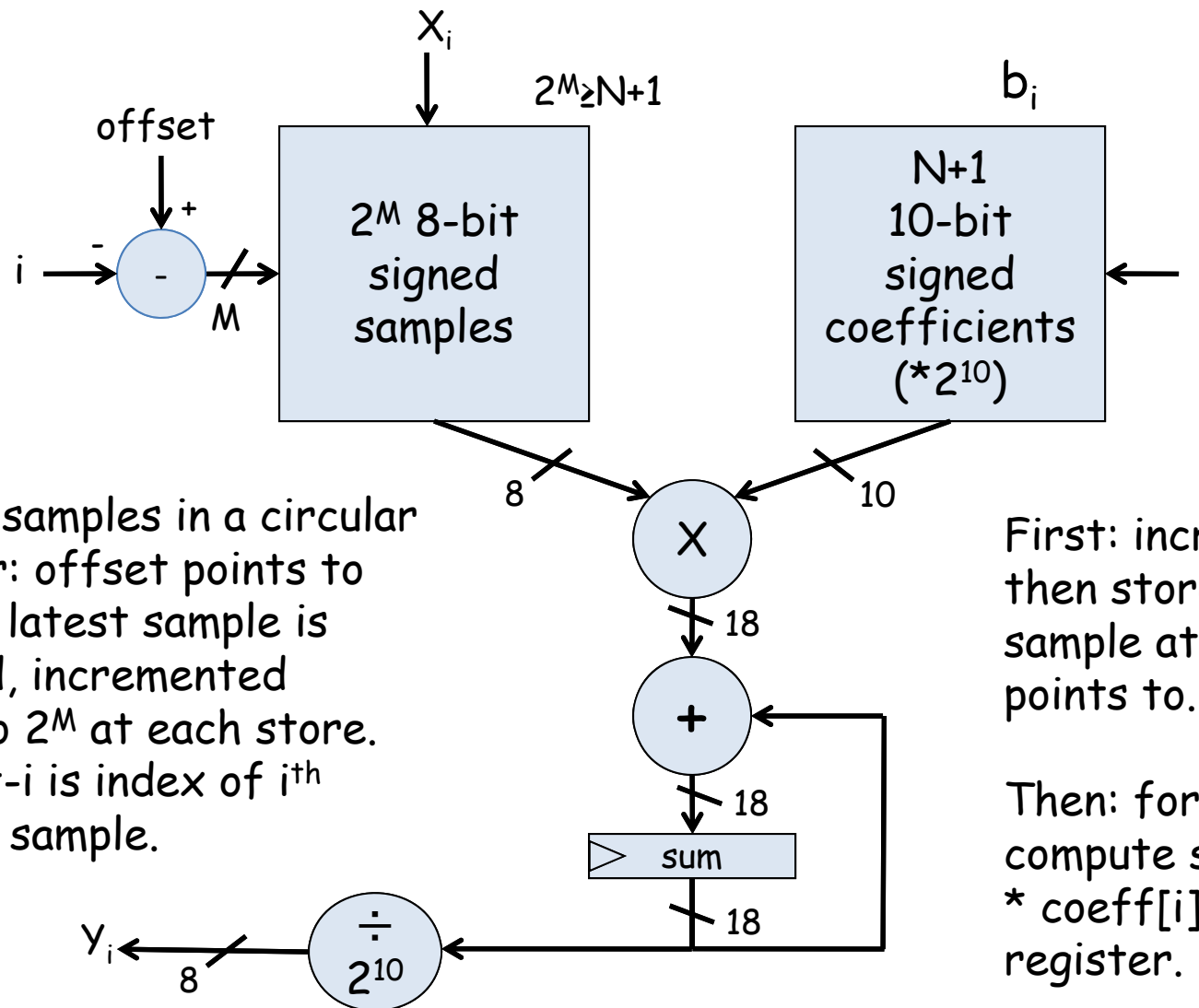

Store samples in a circular buffer: offset points to where latest sample is stored, incremented modulo 2^M at each store. offset- i is index of i^{th} oldest sample.


First: increment offset, then store incoming sample at location it points to. Clear sum.

Then: for i from 0 to N , compute sample[offset- i] * coeff[i] and add to register.

Finally: result in sum


Lab 5A overview

 Assignment: build a voice recorder that records and plays back 8-bit PCM data @ 6KHz



About 11 seconds of speech @ 6KHz

BRAM Operation


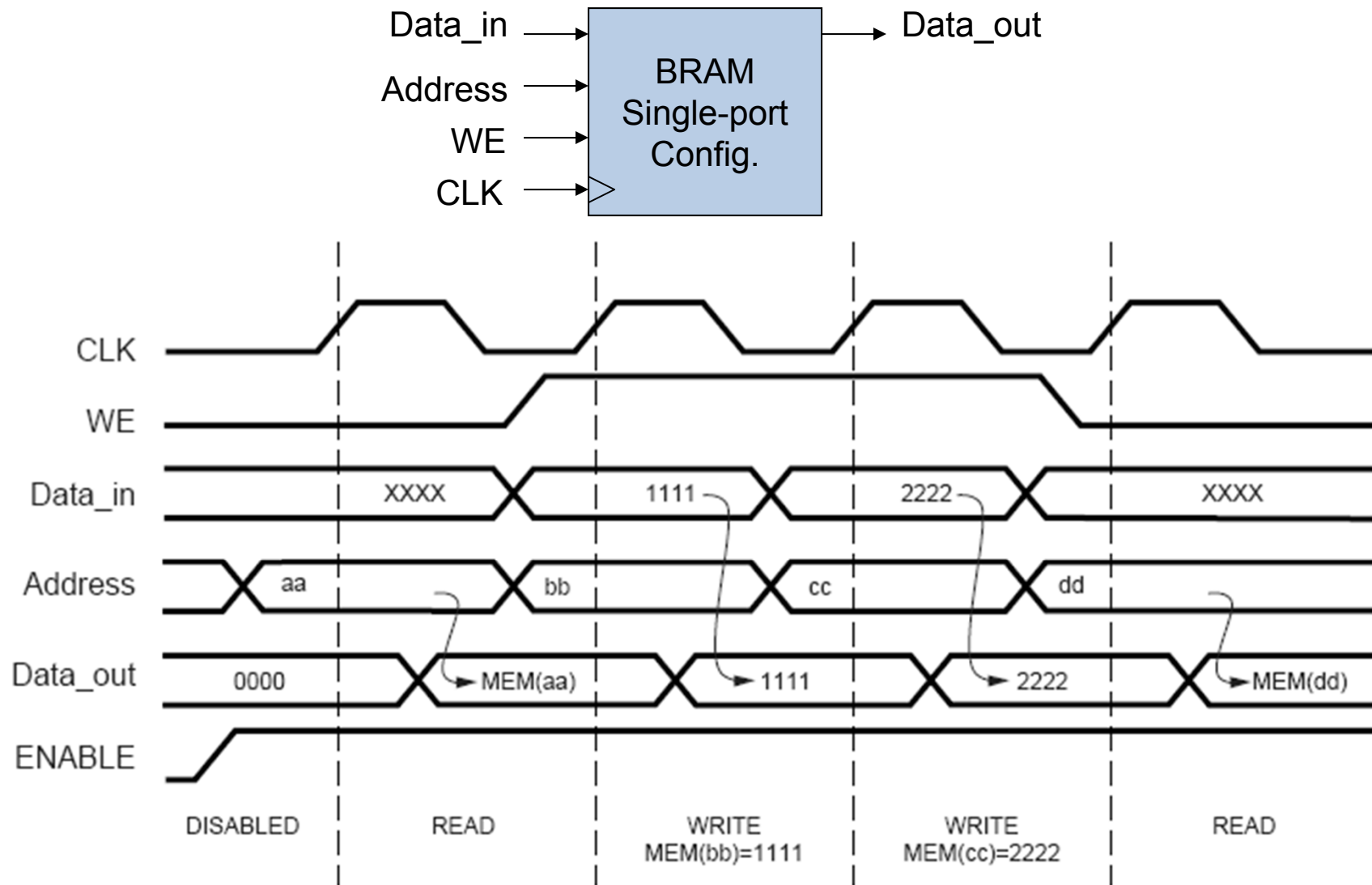


Source: Xilinx App Note 463

AC97: PCM data

PCM = pulse code modulation

  Sample waveform at 48kHz,
encode results as an N-bit signed
number. For our AC97 chip, N =
18.




FPGA sends output frame to AC97 while AC97 sends input frame to FPGA




ready selects a particular *clock_27mhz* clock edge when
you should store input data from the AC97
(*from_ac97_data*) and provide new output to the AC97
(*to_ac97_data*).

Lab 5a* w/ FIR filter

 - Since we're down-sampling by a factor of 8, to avoid aliasing (makes the recording sound "scratchy") we need to pass the incoming samples through a low-pass antialiasing filter to remove audio signal above 3kHz (Nyquist frequency of a 6kHz sample rate).




 
- We need a low-pass reconstruction filter (the same filter as for antialiasing!) when playing back the 6kHz samples. Actually we'll run it at 48kHz and achieve a 6kHz playback rate by feeding it a sample, 7 zeros, the next sample, 7 more zeros, etc.



*Choose Lab5a or Lab5b

... X_i , 0, 0, 0, 0, 0, 0, 0, X_{i+1} , 0, 0, 0, 0, 0, 0, 0, X_{i+2} , ...

FIR Filter

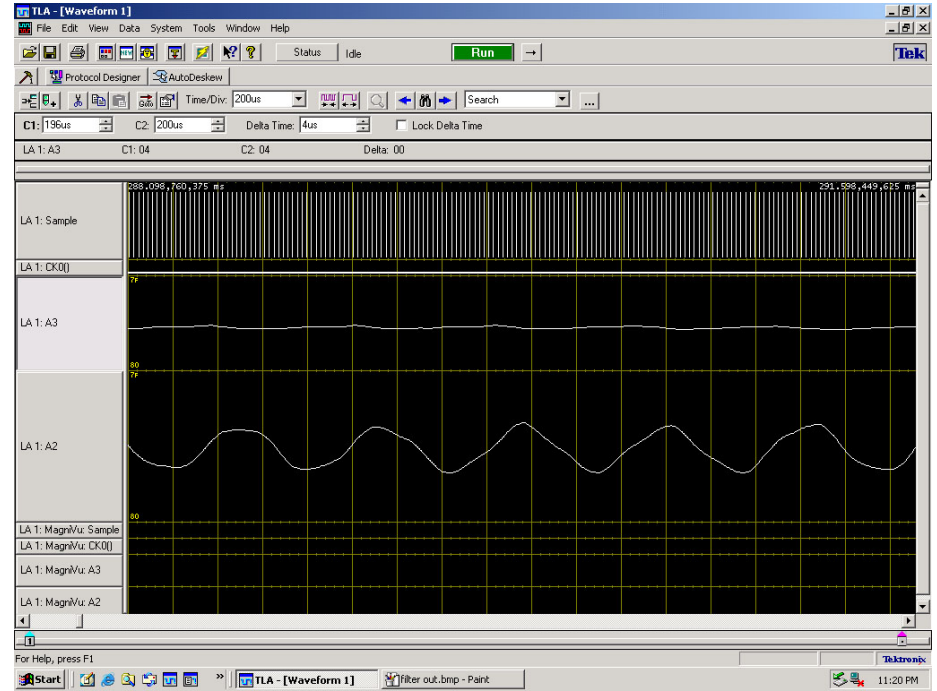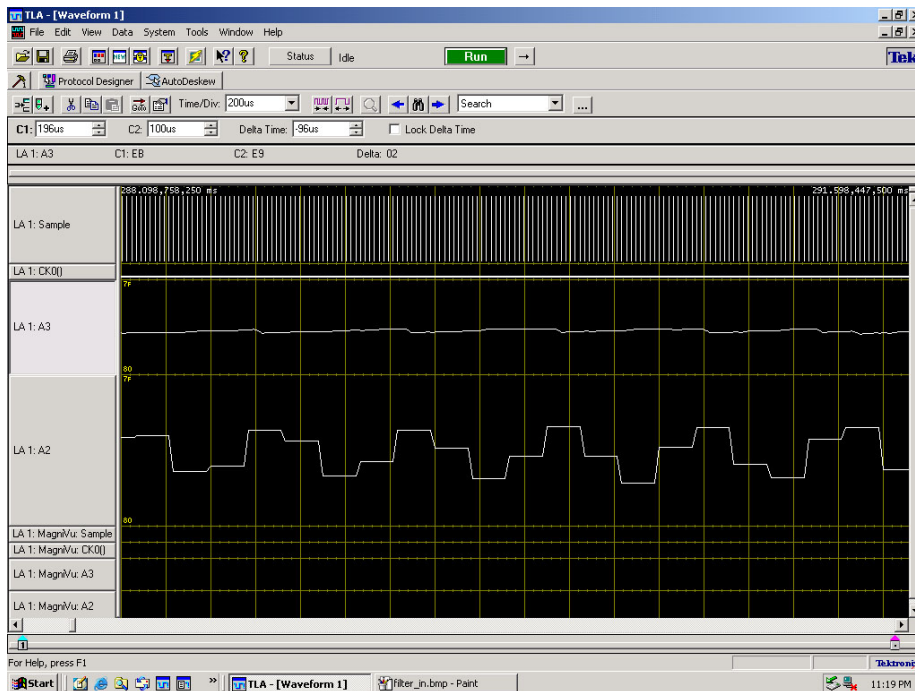

Discrete Values

If we use N bits to encode the magnitude of one of the discrete-time samples, we can capture 2^N possible values.

So we'll divide up the range of possible sample values into 2^N intervals and choose the index of the enclosing interval as the encoding for the sample value.


	V_{MAX}			

			7	15
				14
sample voltage		3		13
			6	12
	1			11
			5	10
		2		9
			4	8
				7
			3	6
		1		5
			2	4
	0			3
			1	2
		0		1
			0	0
	V_{MIN}			


quantized value	1	3	6	13
	1-bit	2-bit	3-bit	4-bit

Quantization Error

 Note that when we quantize the scaled sample values we may be off by up to $\pm \frac{1}{2}$ step from the true sampled values.





Quantization Noise

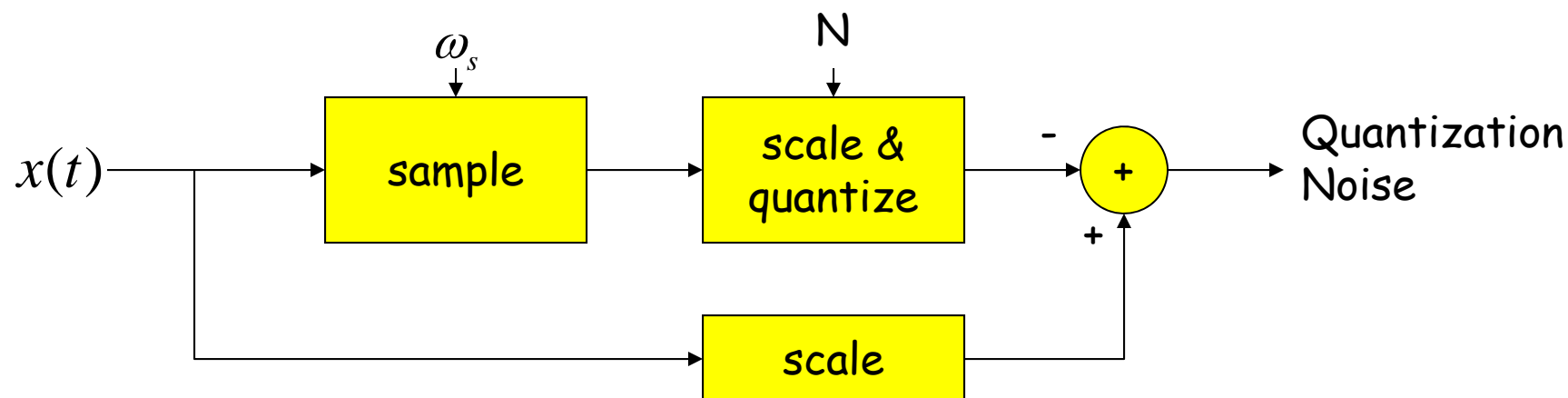

Time Domain

Freq. Domain

  

Decibel (dB) – 3dB point

$$dB = 20 \log \left(\frac{V_o}{V_i} \right)$$

$$dB = 10 \log \left(\frac{P_o}{P_i} \right)$$

$$\log_{10}(2) = .301$$

3 dB point = ?

half power point

$$100 \text{ dB} = 100,000 = 10^5$$

$$80 \text{ dB} = 10,000 = 10^4$$


$$60 \text{ dB} = 1,000 = 10^3$$

$$40 \text{ dB} = 100 = 10^2$$

Common Decibel Units

dB UNIT	reference	application
dBV	1 Volt rms	routine voltage measurements [comparisons!]
dBm	1 mW into 50Ω [0.224V] or 600Ω [0.775V]	radio-frequency [50Ω] or audio [600Ω] power measurements [in England, the dBu is used to mean 0.775V reference without regard to impedance or power]
dB mV	1 millivolt rms	signal levels in cable systems
dBW	1 Watt	audio power amplifier output [usually into 8, 4, or 2Ω impedances]
dBf	1 femtowatt [10^{-15} watt]	communications and stereo receiver sensitivity [usually 50Ω, 75Ω unbalanced, or 300Ω balanced antenna input impedances]
dB (SPL)	0.0002μbar, = 20μPa [=Pascals] [1 bar = 10^6 dynes/cm ² ~1AT]	Sound Pressure Level measurements: the reference is the “threshold of hearing”.

Sound Levels*

 


noise induced hearing loss (NIHL)

mosquito at 3 yards


* www.osha.gov

SNR: Signal-to-Noise Ratio

$$SNR = 10\log_{10}\left(\frac{P_{SIGNAL}}{P_{NOISE}}\right) = 10\log_{10}\left(\frac{A_{SIGNAL}^2}{A_{NOISE}^2}\right) = 20\log_{10}\left(\frac{A_{SIGNAL}}{A_{NOISE}}\right)$$

 RMS amplitude

 SNR is measured in decibels (dB). Note that it's a logarithmic scale: if SNR increases by 3dB the ratio has increased by a factor 2. When applied to audible sounds: the ratio of normal speech levels to the faintest audible sound is 60-70 dB.




$$SNR = 20\log_{10}\left(\frac{A_{signal}}{A_{noise}}\right) \approx 20\log_{10}(2^N)$$

$$\approx N \cdot 6.02dB$$


Oversampling

To avoid aliasing we know that ω_s must be at least $2\omega_M$. Is there any advantage to oversampling, i.e., $\omega_s = K \cdot 2\omega_M$?

 
Suppose we look at the frequency spectrum of quantized samples of a sine wave: (sample freq. = ω_s)



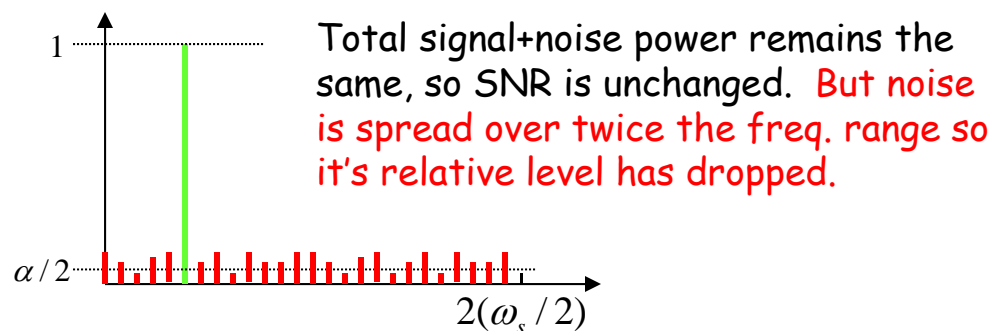Let's double the sample frequency to $2\omega_s$.



 Now let's use a low pass filter to eliminate half the noise! Note that we're not affecting the signal at all...




Oversampling+LPF reduces noise by 3dB/octave


Lab 5c Overview

Assignment: Design a digital bubble level using data from an inertial measurement unit (IMU) and display the results on a monitor.

 - MPU-9250 IMU
 - 3 axis accelerometer
 - 3 axis gyro
 - 3 axis magnetometer
- Data sent via i2c to Teensy
- Data transmitted by Teensy via serial protocol at 100hz




Lab 5c Data Format

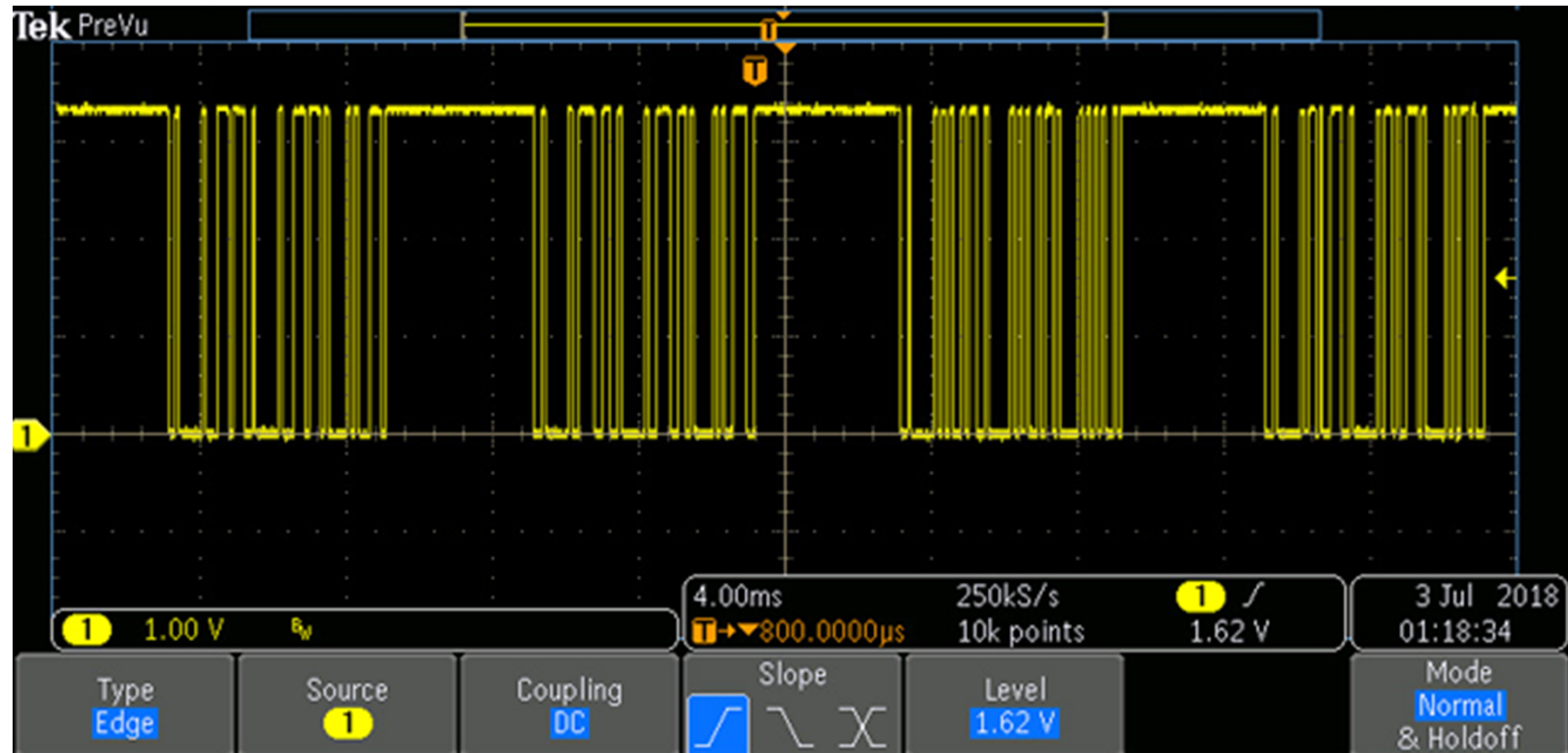



- 3 axis transmitted, only x,y axis data used
- 16 bit 2's complement format
- 9600 baud, lsb first

Lab 5c Interconnect

 

Color coded wires
provided for Nexys4

  Move blue jumper two pins right
and attach 2 wires for +5V




IMU Inertial Measurement Unit

- MEMS Accelerometer - MicroElectroMechanical Systems
- MEMS components generally 1-100 microns
- Silicon based - MEMS device fabricated on same silicon as circuits
- Circuits and digital processing key to MEMS


Movement sensing

- Accelerometers
 - Acceleration - movement from one point to another
 - Tilt sensing - measures inclination/angle with respect to gravity
- Gyroscopes
 - Rotation sensing - measures angular rate.

Capacitance

 
 
$$C = \frac{K\epsilon_0 A}{d} \quad i = C \frac{dv}{dt}$$



MEMS Capacitors*


 


Image by MIT OpenCourseWare.


*6.777J OCW

2 Axis Accelerometer

 


ADXL202 Sensor Structure

 Courtesy of Analog Devices, Inc. Used with permission.



 Courtesy of Analog Devices, Inc. Used with permission.





Courtesy of Analog Devices, Inc. Used with permission.

Giant "MEMS" Capacitor


Mems

- Passenger sensor
- Tire pressure sensor
- Airbag deployment
- Phone rotation

Our Analog Building Block: OpAmp

  


Linear Mode

 


If $-V_{CC} < v_{out} < V_{CC}$

Negative Saturation

 

$v_{id} < -e$


Positive Saturation

 

$v_{id} > e$

Very small input range for "open loop" configuration

The Power of (Negative) Feedback

 


$$\frac{V_{in} + V_{id}}{R_1} + \frac{V_{out} + V_{id}}{R_2} = 0 \quad V_{id} = \frac{V_{out}}{a} \quad \frac{V_{in}}{R_1} = -\frac{V_{out}}{a} \left[\frac{1}{R_1} + \frac{a}{R_2} + \frac{1}{R_2} \right]$$

$$\frac{V_{out}}{V_{in}} = -\frac{R_2 a}{(1+a)R_1 + R_2} \approx -\frac{R_2}{R_1} \text{ (if } a \gg 1)$$

- Overall (closed loop) gain does not depend on open loop gain
- Trade gain for robustness
- Easier analysis approach: "virtual short circuit approach"
 - $v_+ = v_- = 0$ if OpAmp is linear


Basic OpAmp Circuits

Voltage Follower (buffer)

 


$$v_{out} \approx v_{in}$$

Non-inverting

 


$$v_{out} \approx \frac{R_1 + R_2}{R_1} v_{in}$$

Differential Input

 

$$v_{out} \approx \frac{R_2}{R_1} (v_{in2} - v_{in1})$$

Integrator

 

$$v_{out} \approx -\frac{1}{RC} \int_{-\infty}^t v_{in} dt$$



OpAmp as a Comparator

Analog Comparator:

Is $V_+ > V_-$? The Output is a DIGITAL signal

Analog Comparator: Analog to TTL

LM 311 Needs Pull-Up

  

LM311 uses a single supply voltage

Digital to Analog


- Common metrics:
 - Conversion rate - DC to ~500 MHz (video)
 - # bits - up to ~24
 - Voltage reference source (internal / external; stability)
 - Output drive (unipolar / bipolar / current) & settling time
 - Interface - parallel / serial
 - Power dissipation
- Common applications:
 - Real world control (motors, lights)
 - Video signal generation
 - Audio / RF "direct digital synthesis"
 - Telecommunications (light modulation)
 - Scientific & Medical (ultrasound, ...)

DAC: digital to analog converter

How can we convert a N-bit binary number to a voltage?

$V_i = 0$ volts if $B_i = 0$
 $V_i = V$ volts if $B_i = 1$

 OPAMP will vary V_{OUT} to maintain this node at 0V, i.e., the sum of the currents flowing into this node will be zero.




OKAY, this'll work, but the voltages produced by the drivers and various R 's must be carefully matched in order to get equal steps.



$$\frac{V_{OUT}}{R_F} + \frac{B_3 V}{R} + \frac{B_2 V}{2R} + \frac{B_1 V}{4R} + \frac{B_0 V}{8R} = 0$$

$$V_{OUT} = -\frac{R_F}{R} V \left(B_3 + \frac{B_2}{2} + \frac{B_1}{4} + \frac{B_0}{8} \right)$$

R-2R Ladder DAC Architecture

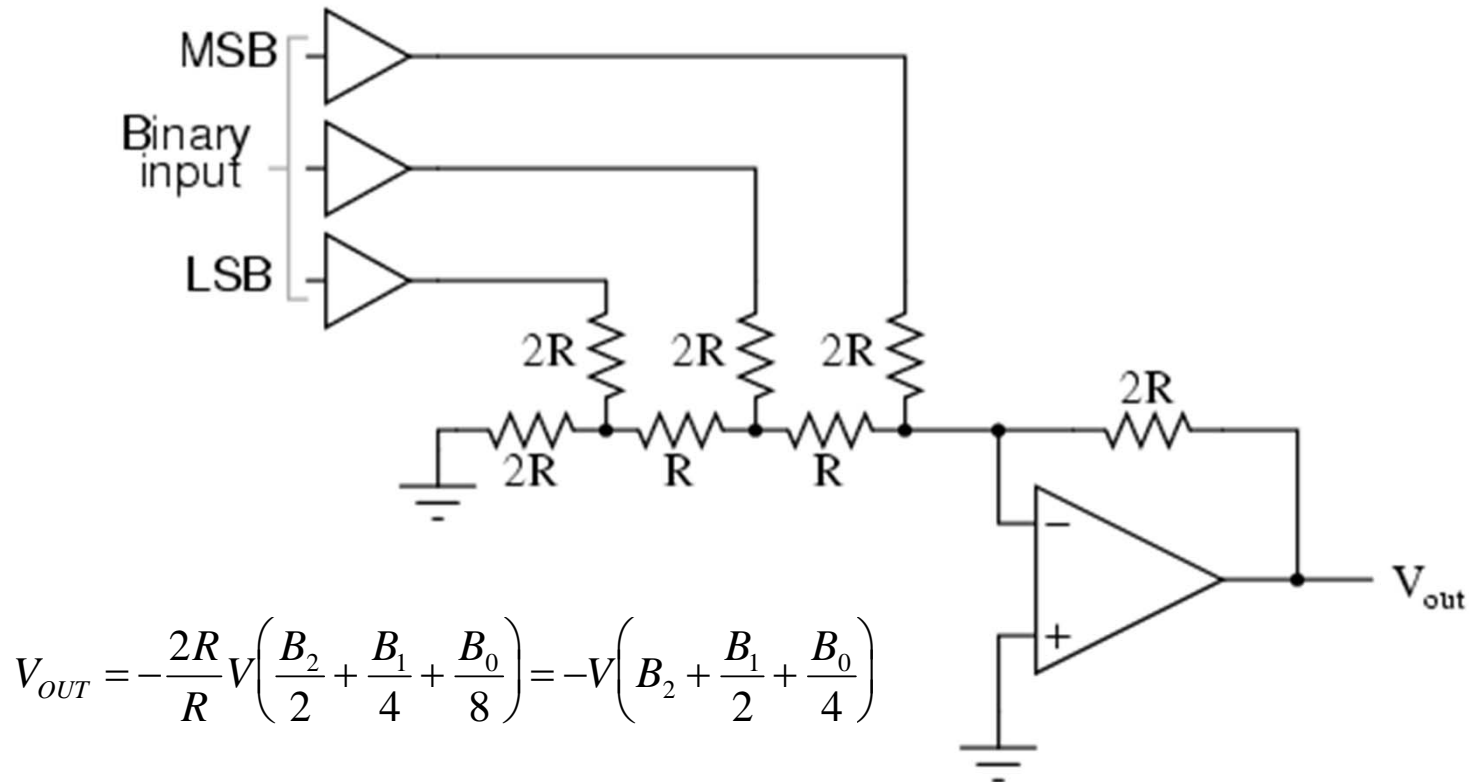

R-2R Ladder achieves large current division ratios with only two resistor values

Quantization*

A Graphical Example

How many bits are needed to represent 256 shades of gray (from white to black)?

Bits	Range		Bits	Range
1	2		5	32
2	4		6	64
3	8		7	128
4	16		8	256

* Acknowledgement: Quantization slides and photos by Prof Denny Freeman 6.003

Quantization: Images

Converting an image from a continuous representation to a discrete representation involves the same sort of issues.

This image has 280×280 pixels, with brightness quantized to 8 bits.



Quantizing Images



8 bit image



7 bit image

Quantizing Images



8 bit image



6 bit image

Quantizing Images



8 bit image



5 bit image

Quantizing Images



8 bit image



4 bit image

Quantizing Images



8 bit image



3 bit image

Quantizing Images



8 bit image



2 bit image

Quantizing Images




8 bit image




1 bit image

Quantization: $y = Q(x)$

 


Quantization with dither: $y = Q(x + n)$

$n = \pm \frac{1}{2}$ quantum

 

 Quantization with Robert's technique: $y = Q(x + n) - n$



3 Bits Quantization


8 bits




3 bits



dither

 

Robert's

 


2 Bits Quantization + Noise


8 bits




2 bits

 

dither

 

Robert's

 

1 Bit Quantization + Noise


8 bits




1 bit



dither

 

Robert's

 

Quantizing Colors



24 bit – 16M colors



8 bit – 256 colors




4 bit – 16 colors

Conclusions

- For a given application, select the resolution that meets the design target and cost target.
- For bits means higher cost, higher power consumption
- Digital processing may help.


Non-idealities in Data Conversion

 Offset - a constant voltage offset that appears at the output when the digital input is 0




Binary code

 Gain error - deviation of slope from ideal value of 1




Binary code

 Integral Nonlinearity - maximum deviation from the ideal analog output voltage




Binary code

 Differential nonlinearity - the largest increment in analog output for a 1-bit change




Binary code

Labkit: ADV7125 Triple Out Video DAC

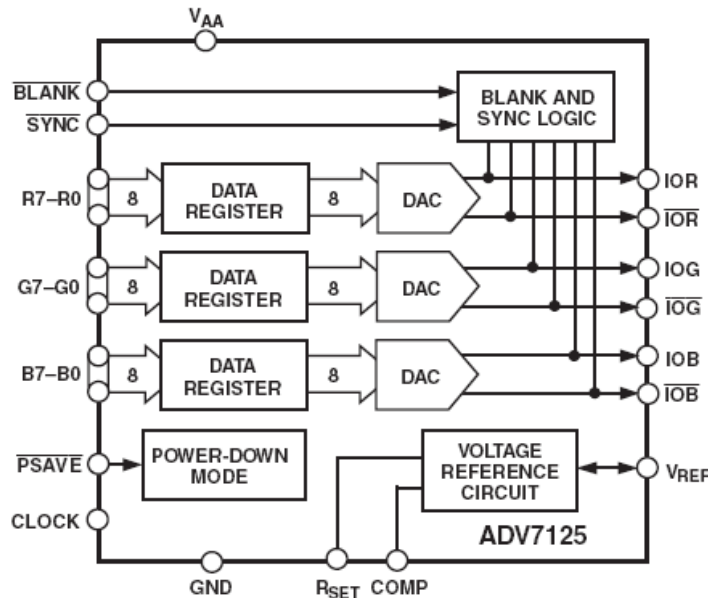


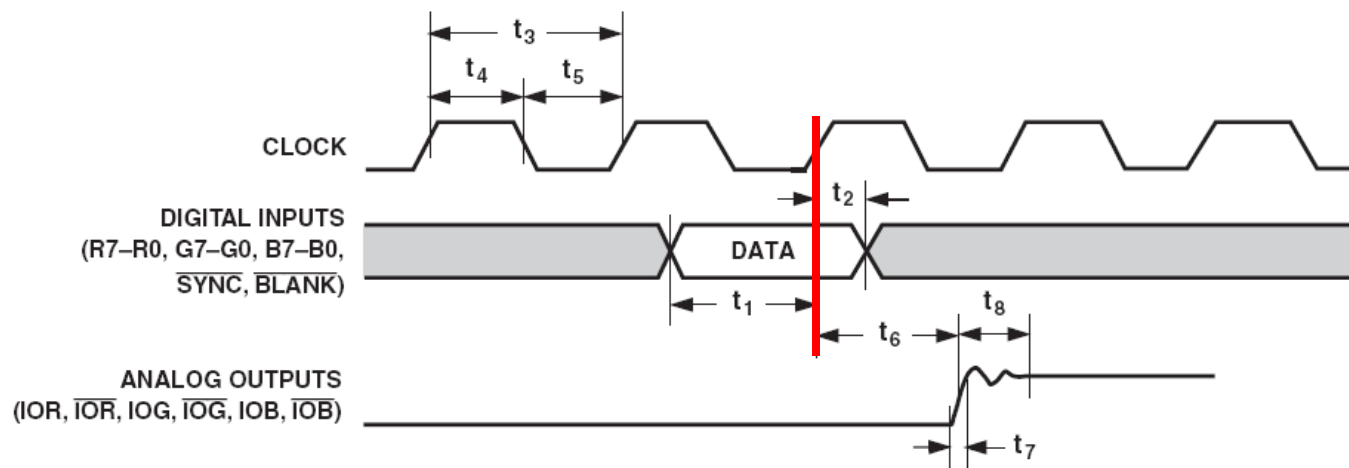
- Three 8-bit DACs
- Single Supply Op.: 3.3 to 5V
- Internal bandgap voltage ref
- Output: 2-26 mA
- 330 MSPS (million samples per second)
- Simple edge-triggered register-based interface



Glitching and Thermometer D/A


- **Glitching** is caused when switching times in a D/A are not synchronized
- **Example:** Output changes from 011 to 100 - MSB switch is delayed
- **Filtering** reduces glitch but increases the D/A settling time
- One solution is a **thermometer code** D/A - requires $2^N - 1$ switches but no ratioed currents

Binary		Thermometer		
0	0	0	0	0
0	1	0	0	1
1	0	0	1	1
1	1	1	1	1

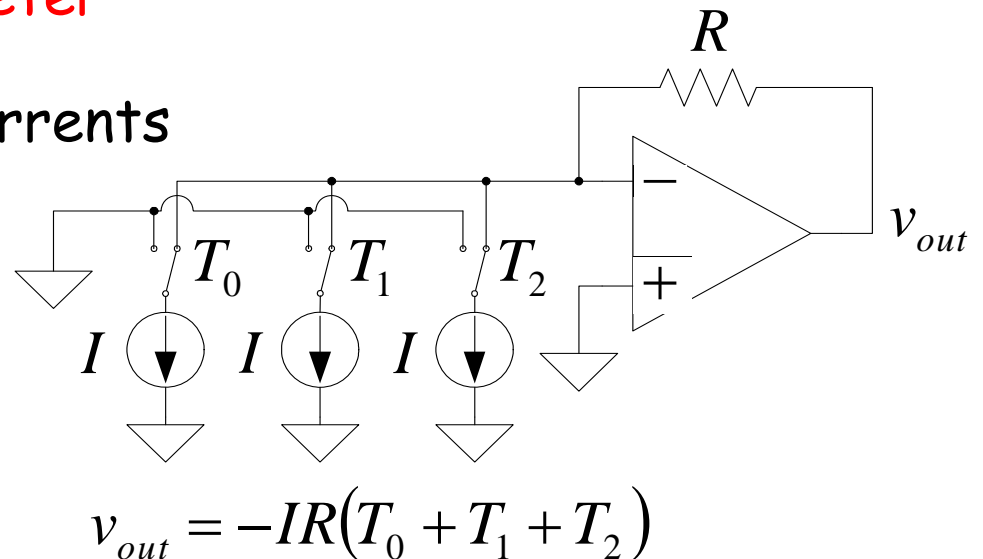 


Successive-Approximation A/D

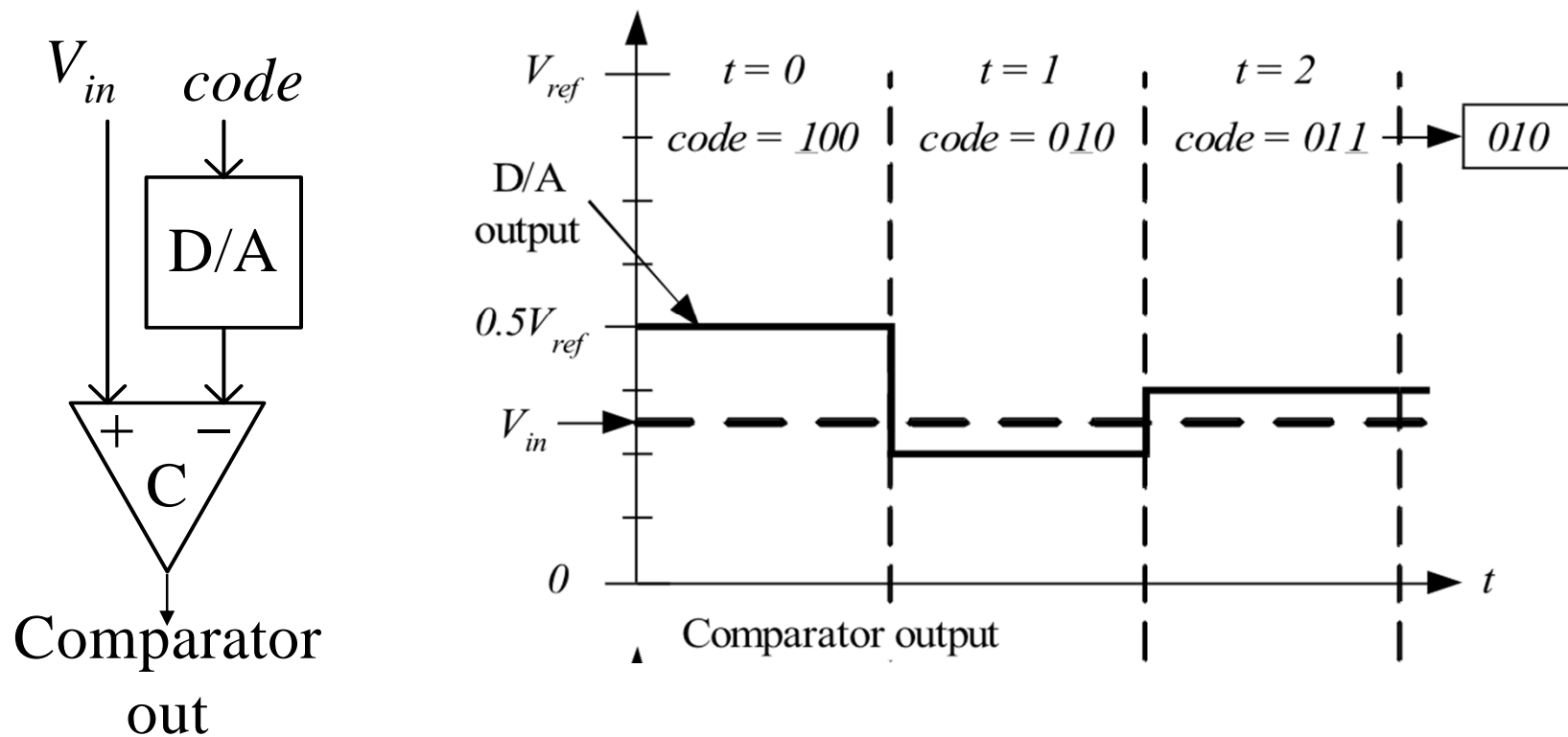- D/A converters are typically compact and easier to design. Why not A/D convert using a D/A converter and a comparator?
- DAC generates analog voltage which is compared to the input voltage
- If DAC voltage > input voltage then set that bit; otherwise, reset that bit
- This type of ADC takes a fixed amount of time proportional to the bit length




Example: 3-bit A/D conversion, $2 \text{ LSB} < V_{in} < 3 \text{ LSB}$

Successive-Approximation A/D

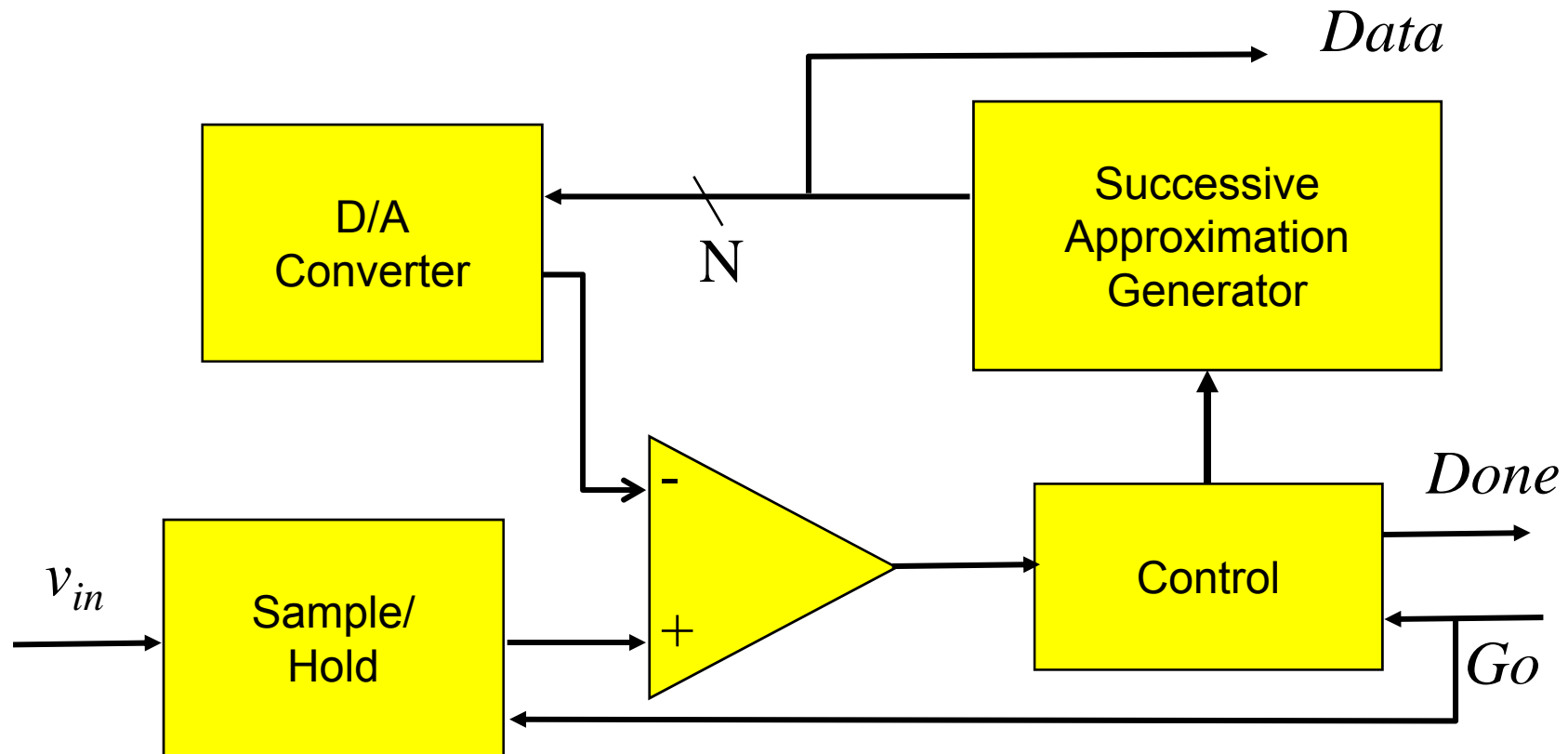



Serial conversion takes a time equal to $N(t_{D/A} + t_{comp})$

Flash A/D Converter

 

- Brute-force A/D conversion
- Simultaneously compare the analog value with every possible reference value
- Fastest method of A/D conversion
- Size scales exponentially with precision
(requires 2^N comparators)

Sigma Delta ADC

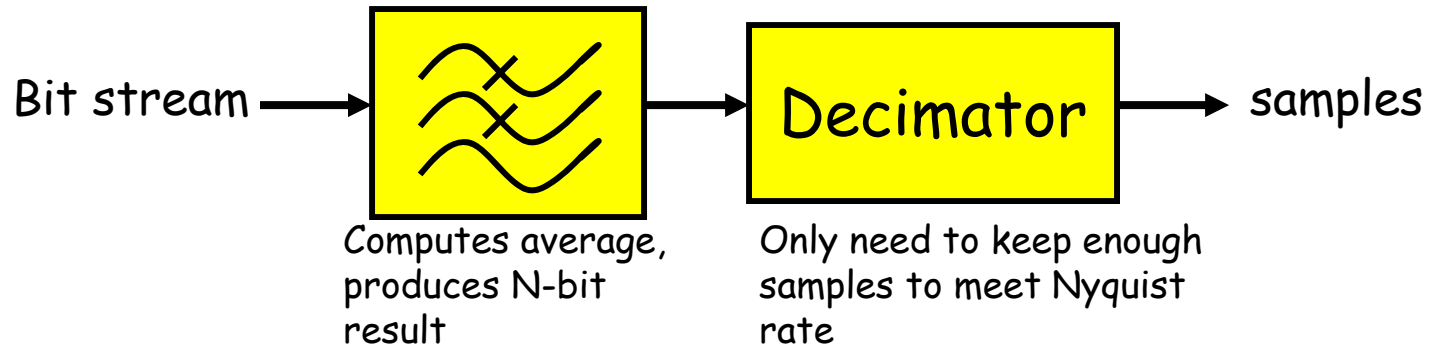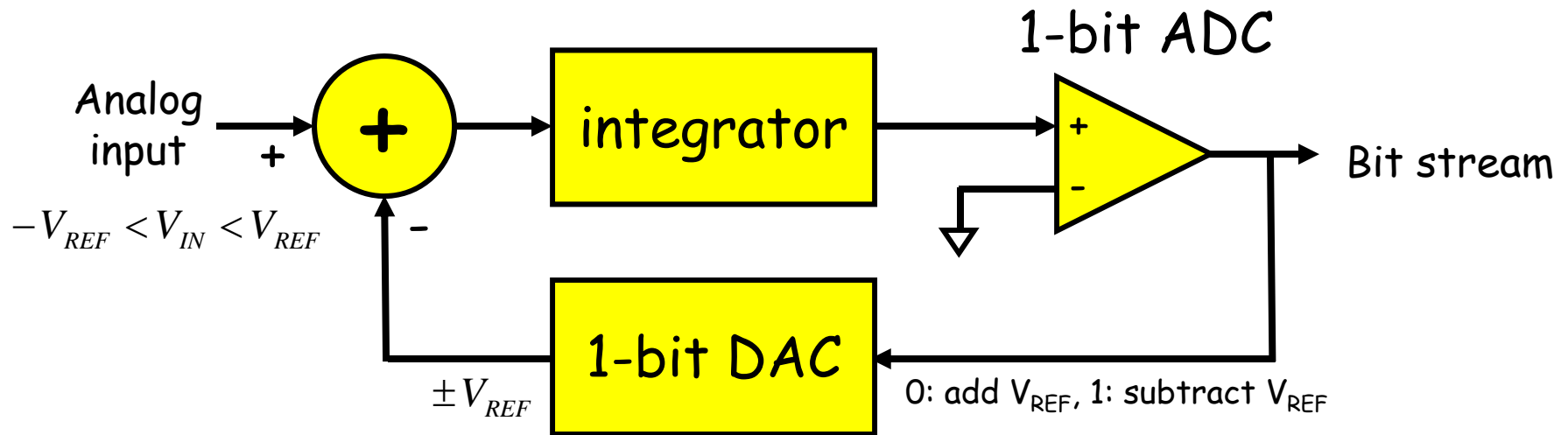


Average of bit stream ($1=V_{REF}$, $0=-V_{REF}$) gives voltage

With $V_{REF}=1V$: $V_{IN}=0.5$: 1110..., $V_{IN}=-0.25$: 00100101..., $V_{IN}=0.6$: 11110

<http://designtools.analog.com/dt/sdtutorial/sdtutorial.html#instructions>

So, what's the big deal?

 
- Can be run at high sampling rates, oversampling by, say, 8 or 9 octaves for audio applications; low power implementations
- Feedback path through the integrator changes how the noise is spread across the sampling spectrum.




- Pushing noise power to higher frequencies means more noise is eliminated by LPF: N^{th} order $\Sigma\Delta$ SNR = $(3+N*6)\text{dB/octave}$

Sigma Delta ADC


- A simple ADC:

 

- Poor Man's ADC:

 

AD Supply Voltages Consideration

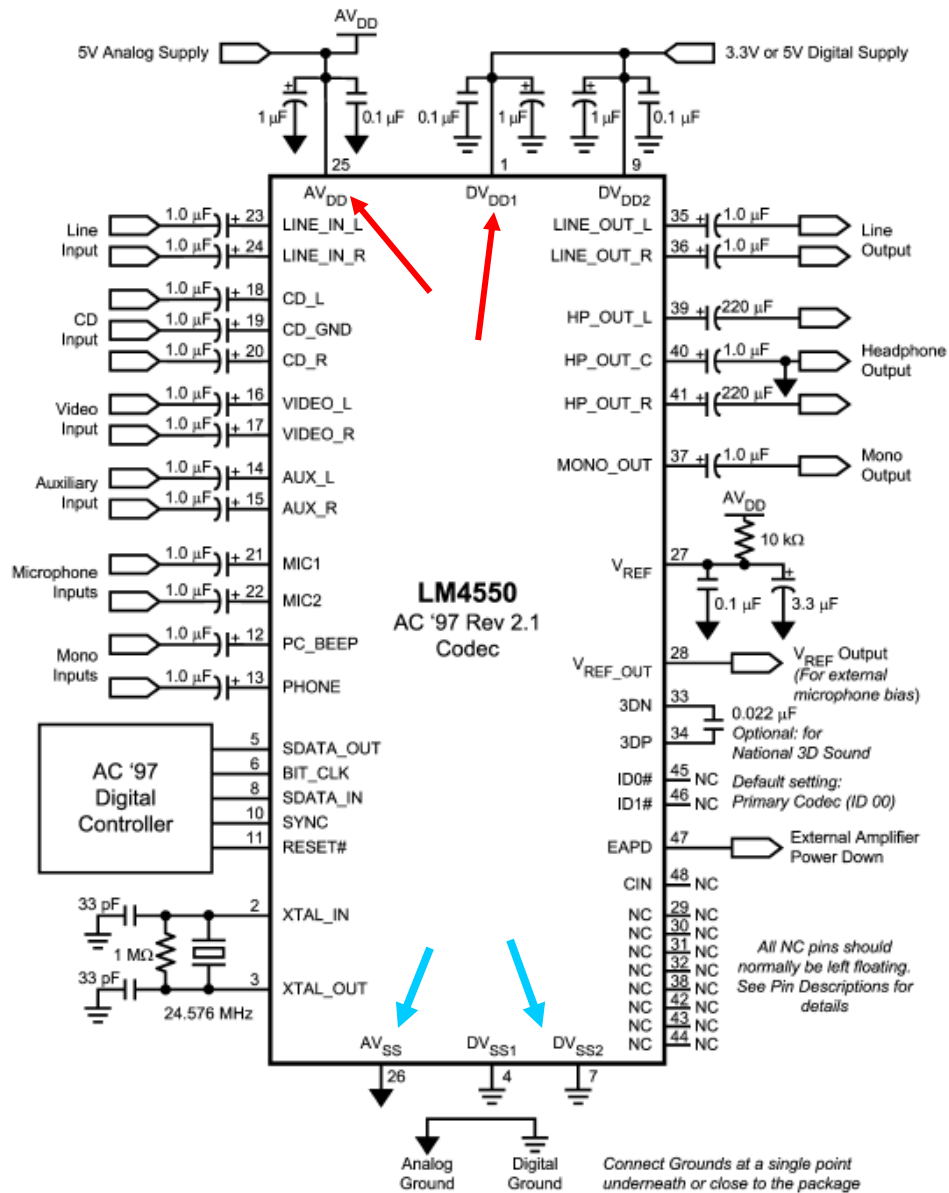


Noise caused by current spikes in fast switching digital circuits:

$$i_c = c \frac{dv}{dt}$$


- **AV_{DD}** Positive Analog Supply Voltage
- **AV_{SS}** Analog Ground
- **DV_{DD}** Positive Digital Supply Voltage
- **DV_{SS}** Digital Ground

Digital/Analog Grounds

 


Labkit Hardware

- Xilinx FPGA
- Logic analyzer pods
 - 4 banks/pods of 16 data lines
 - (analyzerN_clock) and a 16-bit data bus (analyzerN_data[15:0])
N=1,2,3,4
- VGA video output
- RS-232 Serial IO
- PS/2 keyboard and mouse input
- AC97 audio input/output
 - Intel standard for PC audio systems
 - codec's ADCs and DACs operate at a 48kHz sample rate, with 18 bits of precision
- 128Mbits Flash memory, (2) 512k x 36 ZBT SRAM

 

Labkit Hardware

 

- Bidirectional user
 - general purpose I/O, such as connecting to devices on the breadboards
 - bidirectional (inout) signals user1[31:0] through user4[31:0]
- TV Video
 - S video input/output
 - Audio input/output
 - Composite video input/output

Upload Lab 4 Verilog

- Submit by Tuesday
- Grading
 - Proper use of blocking and non-blocking assignments
 - **Readable Code (reformatted)** with comments and consistent indenting [use emacs or vim]
 - Use of default in case statement
 - Use of parameter statements for symbolic name and constants (state==5 vs state==DATA_READY)
 - Parameterized modules when appropriate
 - Readable logical flow, properly formatted (see "Verilog Editors")
 - No long nested if statements.
 - Score 1 to 3 (3 perfect); 1/2 point off for each occurrence.