

6.111 Introductory Digital Systems Laboratory
Fall 2018


Lecture PSet #3 of 8

Due: Tue, 14:30 09/18/2018

Note: Submit PDF online

 Problem 1. [This problem is based on the implementation of a digital communications research project at MIT. When facing a tough problem, coming up with a solution is easier when the problem is broken down to simpler smaller blocks. The solution to this part together with parts 2 and 3 in Lpset 7 and 8 forms the complete solution.]

For many communications systems, a forward error correcting (FEC) code such as a convolution code, is used during transmission. This will allow the receiver to correct erroneous bits when errors occur randomly in a coded sequence. [More on FEC in future lpsets.] However, the bursty nature of noise will often wipe out large number of adjacent data bits - defeating the convolution code. A simple solution is to interleave the data bits of a four byte packet so that adjacent data bits are spaced out in the transmitted sequence. Instead of sending all 8 bits of the byte 0, the low order bit pair of bytes 3, 2, 1, and 0 (starting at the LSB end) are transmitted followed by the next set of bit pairs until all bits are transmitted. This is implemented in many satellite communication systems¹.



(see other side)

¹ from <http://www.ti.com/lit/an/swra113a/swra113a.pdf>

(A) Implement a Verilog module that will interleave 4 bytes as described above.

```
module interveaver(  
    input [7:0] byte0, // data = 8'h00  
    input [7:0] byte1, // data = 8'h0E  
    input [7:0] byte2, // data = 8'h8C  
    input [7:0] byte3, // data = 8'h0C  
    output [7:0] out0,  
    output [7:0] out1,  
    output [7:0] out2,  
    output [7:0] out3  
);  
  
    assign out0 =  
    assign out1 =  
    assign out2 =  
    assign out3 =  
  
endmodule
```

There are multiple implementations. To receive credit your interleaver must encode this input [00 0E 8C 03] to the following output [C8 3C 00 20]. This will ensure compatibility with the deinterleaver. [This Verilog was used in a research project.]

(B) Write the Verilog for a deinterleaver. Any interesting observation?

Problem 2 [For full credit, Verilog must be syntactically correct.]

For each of the parts below write one or more statements of Verilog that implement the desired functionality. Your Verilog just has to produce the same values for its outputs – it doesn't have to replicate the schematic logic gate-for-gate (in fact, you should not use those "structural" constructs). Be sure to include the appropriate declarations for any wires or regs used in your code.

(A) A circuit that divides an 8-bit input operand by 16 and produces a 4-bit value.
[Division with numbers other than powers of two requirement special circuits.]

(B) A circuit to compute the 17-bit sum of two 16-bit operands.

(C) Implement a 2-bit priority encoder (a circuit which examines its four inputs (I0, I1, I2, I3) and outputs a 2-bit binary number indicating the highest-priority input which has a value of "1", where I3 has the highest priority and I0 the lowest) with "dataflow" (assign) constructs.

(D) Implement a 2-bit priority encoder with "sequential" (always) construct and "case" statement.

Problem 3. [For full credit, Verilog must be syntactically correct.]

Using the Verilog parameterized module mechanism it's possible to write modules whose operations depends on parameters specified when the module is instantiated.

- (A) Write a parameterized parity check module which takes as input a bus whose size is set by a parameter. The module has a single output which is 0 if the number of 1's in the input vector is even and 1 otherwise. [This is referred to as even parity.]
- (B) How would one instantiate an instance of your module to compute parity check on the 16-bit data bus DATA[15:0]?