




## Pipelining & Verilog

- Division
- Latency & Throughput
- Pipelining to increase throughput
- Retiming
- Verilog Math Functions
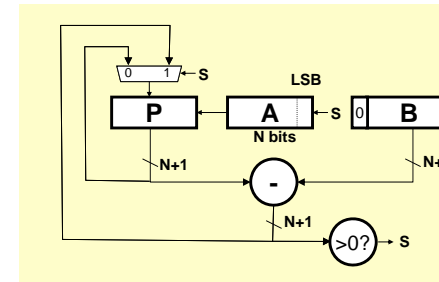
## Sequential Divider

Assume the Dividend (A) and the divisor (B) have N bits. If we only want to invest in a single N-bit adder, we can build a sequential circuit that processes a single subtraction at a time and then cycle the circuit N times. This circuit works on unsigned operands; for signed operands one can remember the signs, make operands positive, then correct sign of result.



```

Init: P ← 0, load A and B
Repeat N times {
  shift P/A left one bit
  temp = P - B
  if (temp > 0)
    {P ← temp, A_LSB ← 1}
  else A_LSB ← 0
}
Done: Q in A, R in P
  
```

## Verilog divider.v

```

// The divider module divides one number by another. It
// produces a signal named "ready" when the quotient output
// is ready, and takes a signal named "start" to indicate
// the the input dividend and divider is ready.
// sign == 0 for unsigned, 1 for twos complement

// It uses a simple restoring divide algorithm.
// http://en.wikipedia.org/wiki/Division_(digital)#Restoring_division

module divider #(parameter WIDTH = 8)
(input clk, sign, start,
input [WIDTH-1:0] dividend,
input [WIDTH-1:0] divider,
output reg [WIDTH-1:0] quotient,
output [WIDTH-1:0] remainder;
output ready);

reg [WIDTH-1:0] quotient_temp;
reg [WIDTH*2-1:0] dividend_copy, divider_copy, diff;
reg negative_output;

wire [WIDTH-1:0] remainder = (negative_output) ?
  dividend_copy[WIDTH-1:0] : ~dividend_copy[WIDTH-1:0] + 1'b1;

reg [5:0] bit;
reg del_ready = 1;
wire ready = (bit) & ~del_ready;

wire [WIDTH-2:0] zeros = 0;
initial bit = 0;
initial negative_output = 0;


always @(posedge clk) begin
  del_ready <= !bit;
  if (start) begin

    bit = WIDTH;
    quotient = 0;
    quotient_temp = 0;
    dividend_copy = (sign || !dividend[WIDTH-1]) ?
      {1'b0,zeros,dividend} :
      {1'b0,zeros,~dividend + 1'b1};
    divider_copy = (sign || !divider[WIDTH-1]) ?
      {1'b0,divider,zeros} :
      {1'b0,~divider + 1'b1,zeros};

    negative_output = sign &&
      ((divider[WIDTH-1] && !dividend[WIDTH-1])
      || (divider[WIDTH-1] && dividend[WIDTH-1]));
  end
  else if (bit > 0) begin
    diff = dividend_copy - divider_copy;
    quotient_temp = quotient_temp << 1;
    if (!diff[WIDTH*2-1]) begin
      dividend_copy = diff;
      quotient_temp[0] = 1'd1;
    end
    quotient = (negative_output) ?
      quotient_temp :
      ~quotient_temp + 1'b1;
    divider_copy = divider_copy >> 1;
    bit = bit - 1'b1;
  end
end
endmodule
  
```


L. Williams MIT '13

## Math Functions in Coregen

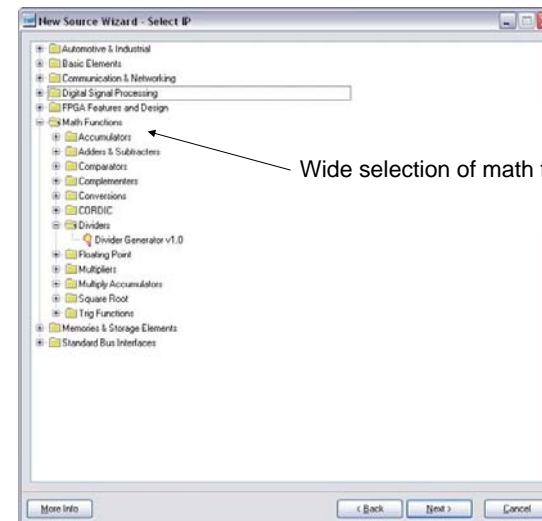


Wide selection of math functions available

# Coregen Divider

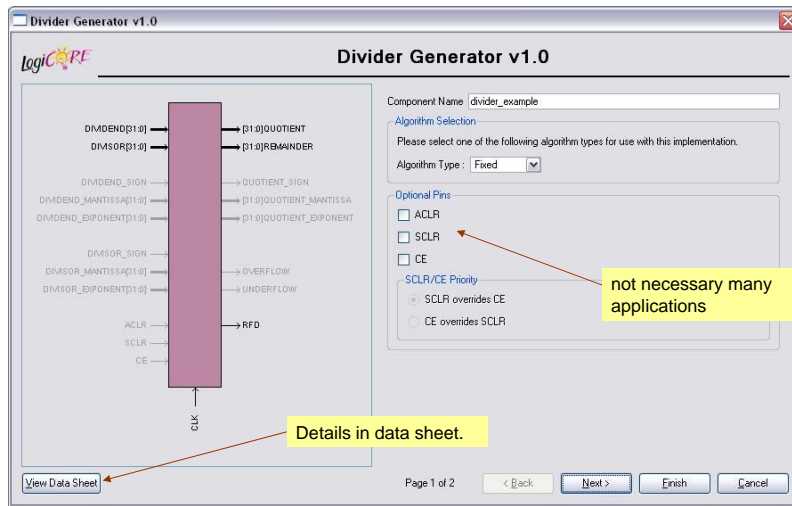

# Coregen Divider

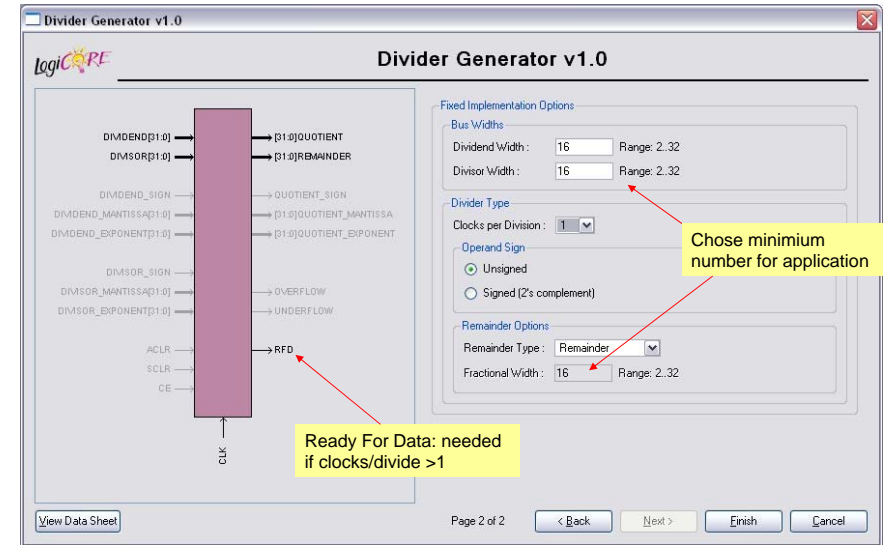

## Performance Metrics for Circuits

Circuit **Latency** (L): time between arrival of new input and generation of corresponding output.

For combinational circuits this is just  $t_{PD}$ .

Circuit **Throughput** (T): Rate at which new outputs appear.

For combinational circuits this is just  $1/t_{PD}$  or  $1/L$ .

## Coregen Divider Latency

 


Figure 2: Latency Example (Clocks per Division = 4)


Table 4: Latency of Fixed-point Solution Based on Divider Parameters

| Signed | Fractional | Ckls/Div | Latency |
|--------|------------|----------|---------|
| False  | False      | 1        | M+2     |
| False  | False      | >1       | M+3     |
| False  | True       | 1        | M+F+2   |
| False  | True       | >1       | M+F+3   |
| True   | False      | 1        | M+4     |
| True   | False      | >1       | M+5     |
| True   | True       | 1        | M+F+4   |
| True   | True       | >1       | M+F+5   |

Note: M=dividend width, F=fractional remainder width.

The divclk\_sel parameter allows a range of choices of throughput versus area. With divclk\_sel = 1, the core is fully pipelined, so it will have maximal throughput of one division per clock cycle, but will occupy the most area. The divclk\_sel selections of 2, 4 and 8 reduce the throughput by those respective factors for smaller core sizes.

# Performance of Combinational Circuits

 


For combinational logic:

$$L = t_{PD}$$

$$T = 1/t_{PD}$$

 We can't get the answer faster, but are we making effective use of our hardware at all times?




F & G are "idle", just holding their outputs stable while H performs its computation

 
# Retiming: A very useful transform

Retiming is the action of moving registers around in the system

- Registers have to be moved from ALL inputs to ALL outputs or vice versa



 **Cutset retiming:** A cutset intersects the edges, such that this would result in two disjoint partitions of the edges being cut. To retime, delays are moved from the ingoing to the outgoing edges or vice versa.




**Benefits of retiming:**

- Modify critical path delay
- Reduce total number of registers


 
# Retiming Combinational Circuits aka "Pipelining"



$$L = 45$$

$$T = 1/45$$


Assuming ideal registers:  
i.e.,  $t_{PD} = 0$ ,  $t_{SETUP} = 0$

$$t_{CLK} = 25$$

$$L = 2 * t_{CLK} = 50$$

$$T = 1/t_{CLK} = 1/25$$

# Pipeline diagrams

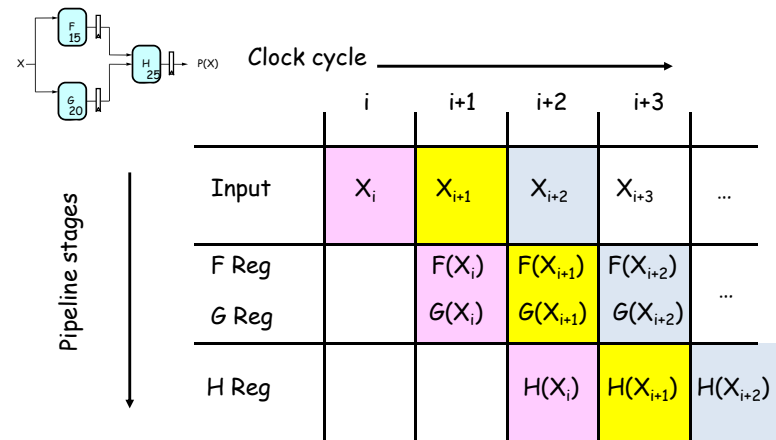

The results associated with a particular set of input data moves *diagonally* through the diagram, progressing through one pipeline stage each clock cycle.

# Pipeline Conventions

**DEFINITION:**

a *K-Stage Pipeline* ("K-pipeline") is an acyclic circuit having exactly K registers on *every* path from an input to an output.

a *COMBINATIONAL CIRCUIT* is thus an 0-stage pipeline.

**CONVENTION:**

Every pipeline stage, hence every K-Stage pipeline, has a register on its *OUTPUT* (not on its input).

**ALWAYS:**


The *CLOCK* common to all registers must have a period sufficient to cover propagation over combinational paths PLUS (input) register  $t_{PD}$  PLUS (output) register  $t_{SETUP}$ .

The *LATENCY* of a K-pipeline is K times the period of the clock common to all registers.

The *THROUGHPUT* of a K-pipeline is the frequency of the clock.

# Ill-formed pipelines

Consider a BAD job of pipelining:

 

For what value of K is the following circuit a K-Pipeline? \_\_\_\_\_ none

**Problem:**

*Successive inputs get mixed* e.g.,  $B(A(X_{i+1}), Y_i)$ . This happened because some paths from inputs to outputs have 2 registers, and some have only 1!

This **CAN'T HAPPEN** on a well-formed K pipeline!

# A pipelining methodology

**Step 1:**

Add a register on each output.


**Step 2:**

Add another register on each output. Draw a cut-set contour that includes all the new registers and some part of the circuit. Retime by moving regs from all outputs to all inputs of cut-set.


Repeat until satisfied with T.

 **STRATEGY:**

Focus your attention on placing pipelining registers around the slowest circuit elements (**BOTTLENECKS**).



# Pipeline Example

 


**OBSERVATIONS:**

- 1-pipeline improves neither L or T.
- T improved by breaking long combinational paths, allowing faster clock.
- Too many stages cost L, don't improve T.
- Back-to-back registers are often required to keep pipeline well-formed.

|         | LATENCY | THROUGHPUT |
|---------|---------|------------|
| 0-pipe: | 4       | 1/4        |
| 1-pipe: | 4       | 1/4        |
| 2-pipe: | 4       | 1/2        |
| 3-pipe: | 6       | 1/2        |

# Pipeline Example - Verilog

 


```

No pipeline
assign y = G(x); // logic for y
assign pixel = C(y) // logic for pixel
    
```

- Lab 3 Pong**
- G = game logic 8ns tpd
  - C = draw round puck, use multiply with 9ns tpd
  - System clock 65mhz = 15ns period - opps

```

 reg [N:0] x,y;
reg [23:0] pixel
always @ * begin
    y=G(x);
    pixel = C(y);
end
    
```




```

Pipeline
always @(posedge clock) begin
    ...
    y2 <= G(x); // pipeline y
    pixel <= C(y2) // pipeline pixel
end
    
```

Latency = 2 clock cycles!  
Implications?

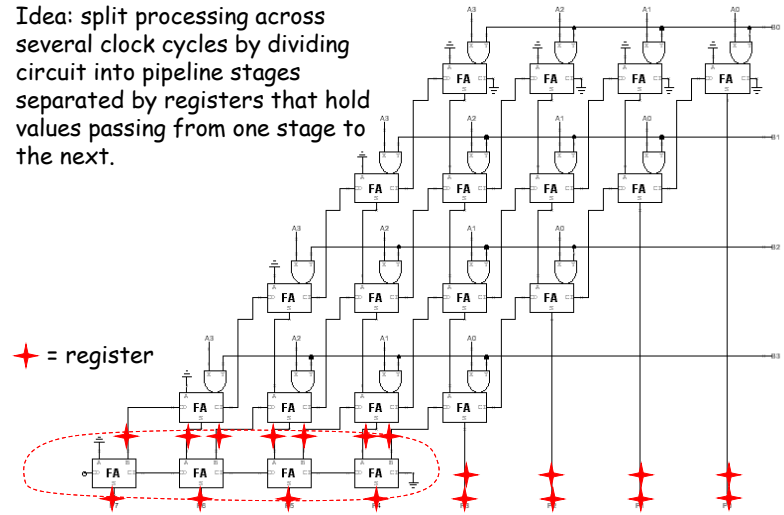
# Increasing Throughput: Pipelining

Idea: split processing across several clock cycles by dividing circuit into pipeline stages separated by registers that hold values passing from one stage to the next.



Throughput =  $1/4t_{PD,FA}$  instead of  $1/8t_{PD,FA}$

# How about $t_{PD} = 1/2t_{PD,FA}$ ?

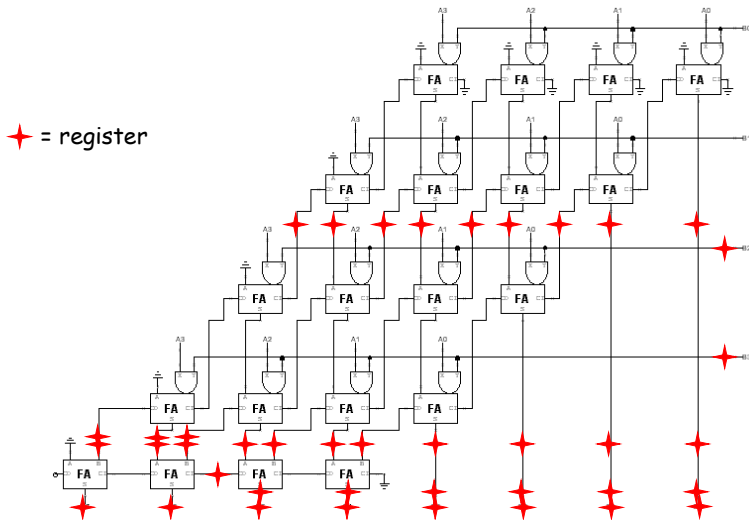

\* = register

# Timing Reports

Synthesis report



| Signal                  | Delay     | Path |
|-------------------------|-----------|------|
| 65mhz                   | 27mhz*2.4 |      |
| Multiple                | 7.251ns   |      |
| Total Propagation delay | 34.8ns    |      |

# History of Computational Fabrics

- Discrete devices: relays, transistors (1940s-50s)
- Discrete logic gates (1950s-60s)
- Integrated circuits (1960s-70s)
  - e.g. TTL packages: Data Book for 100's of different parts
- Gate Arrays (IBM 1970s)
  - Transistors are pre-placed on the chip & Place and Route software puts the chip together automatically – only program the interconnect (mask programming)
- Software Based Schemes (1970's- present)
  - Run instructions on a general purpose core
- Programmable Logic (1980's to present)
  - A chip that be reprogrammed after it has been fabricated
  - Examples: **PALs**, EPROM, EEPROM, PLDs, **FPGAs**
  - Excellent support for mapping from Verilog
- ASIC Design (1980's to present)
  - Turn Verilog directly into layout using a library of standard cells
  - Effective for high-volume and efficient use of silicon area

  
# Reconfigurable Logic

- Logic blocks**
  - To implement combinational and sequential logic
- Interconnect**
  - Wires to connect inputs and outputs to logic blocks
- I/O blocks**
  - Special logic blocks at periphery of device for external connections
- Key questions:**
  - How to make logic blocks programmable? (after chip has been fabbed!)
  - What should the logic granularity be?
  - How to make the wires programmable? (after chip has been fabbed!)
  - Specialized wiring structures for local vs. long distance routes?
  - How many wires per logic block?



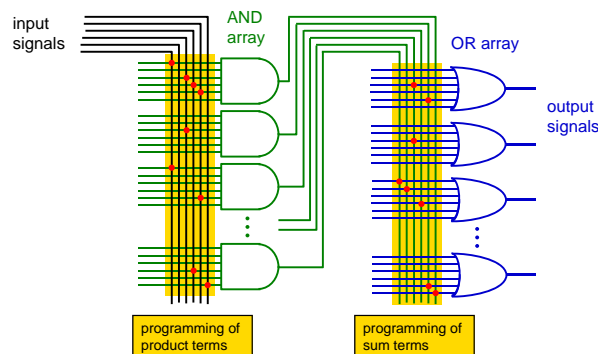
# Programmable Array Logic (PAL)

- Based on the fact that any combinational logic can be realized as a sum-of-products
- PALs feature an array of AND-OR gates with programmable interconnect



 
# RAM Based Field Programmable Logic - Xilinx


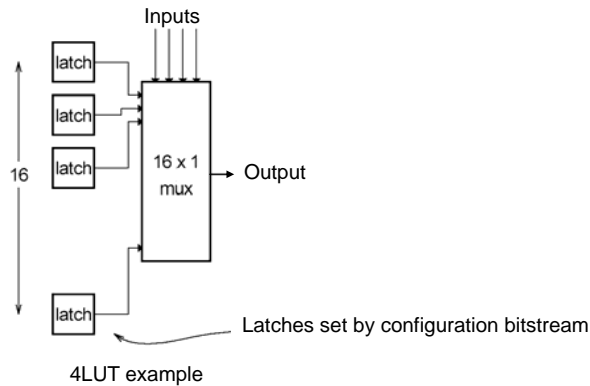
# LUT Mapping

- N-LUT direct implementation of a truth table: any function of n-inputs.
- N-LUT requires  $2^N$  storage elements (latches)
- N-inputs select one latch location (like a memory)



# Configuring the CLB as a RAM

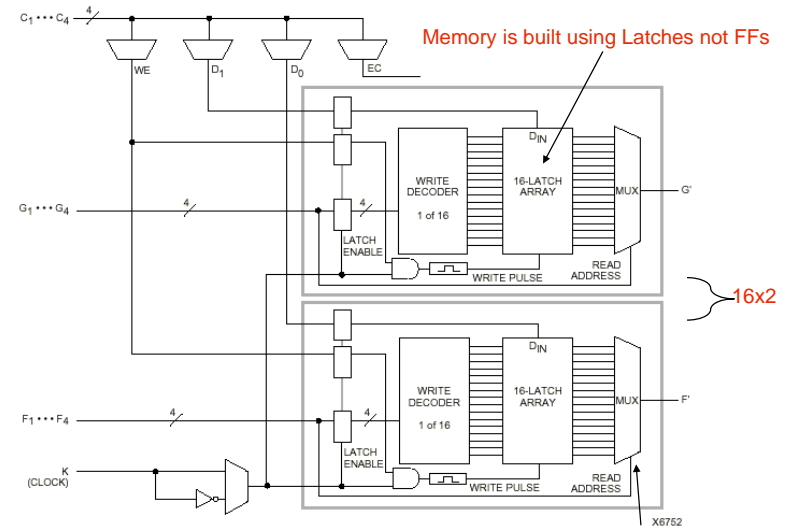


Figure 4: 16x2 (or 16x1) Edge-Triggered Single-Port RAM

Read is same a LUT Function!

# Xilinx 4000 Interconnect



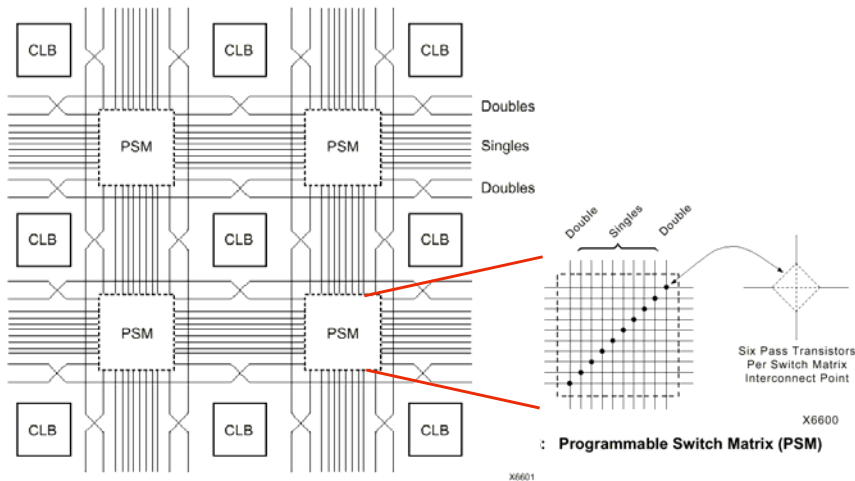


Figure 28: Single- and Double-Length Lines, with Programmable Switch Matrices (PSMs)

# Xilinx 4000 Interconnect Details

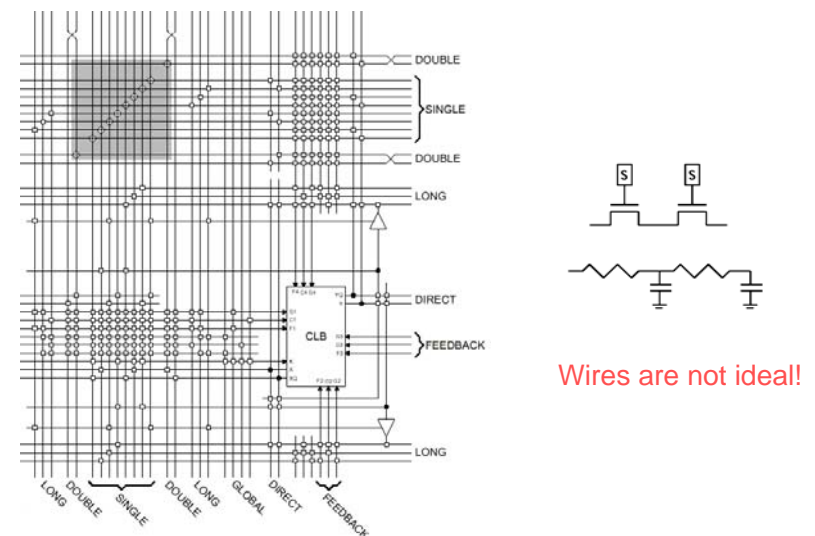


# Add Bells & Whistles

 


Courtesy of David B. Parlour, ISSCC 2004 Tutorial, "The Reality and Promise of Reconfigurable Computing in Digital Signal Processing"

# The Virtex II CLB (Half Slice Shown)

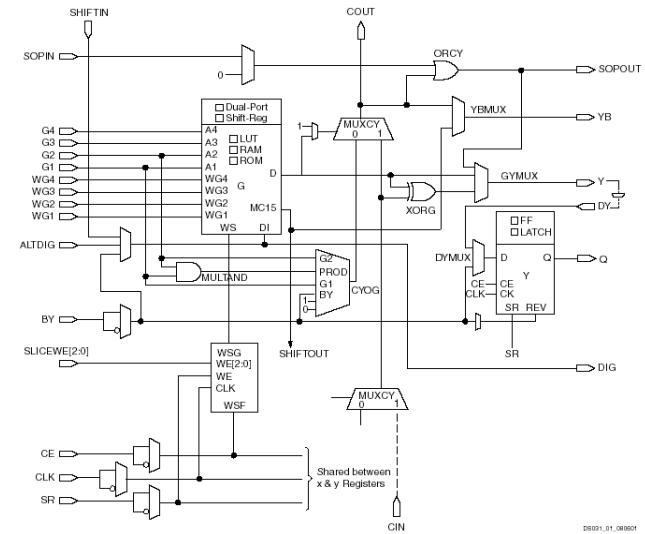

# Adder Implementation

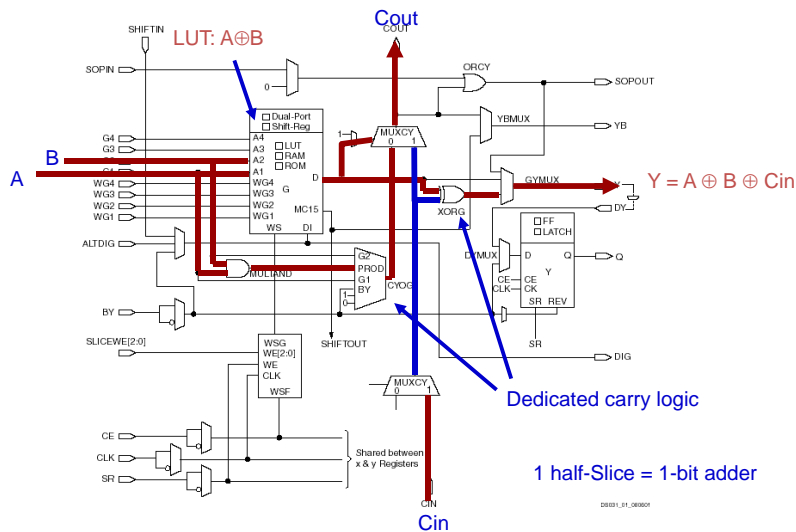

# FPGA's



DSP with 25x18 multiplier  
Gigabit ethernet support

| Part Number                           | LX150T | LX190T | LX240T | LX360T | LX500T | LX760  | FX315T | FX475T |
|---------------------------------------|--------|--------|--------|--------|--------|--------|--------|--------|
| Logic Cells                           | 74.0K  | 128K   | 200K   | 241K   | 364K   | 550K   | 750K   | 476K   |
| CLB Flip-Flops                        | 93.1K  | 160K   | 250K   | 301K   | 455K   | 687K   | 948K   | 595K   |
| Maximum Distributed RAM (Kbits)       | 1,045  | 1,740  | 3,040  | 3,850  | 4,130  | 6,200  | 8,380  | 5,000  |
| Block RAM/PIPC w/ ECIG (32Kbits each) | 106    | 284    | 344    | 416    | 416    | 632    | 720    | 1,064  |
| Total Block RAM (Kbits)               | 5,516  | 9,524  | 12,994 | 14,976 | 14,976 | 22,752 | 25,920 | 35,344 |
| Mixed-Matrix Clock Managers (MMCM)    | 6      | 10     | 10     | 12     | 12     | 18     | 18     | 18     |
| DSP48E1 Slices                        | 280    | 480    | 640    | 765    | 576    | 804    | 804    | 1,244  |
| PCI Express® Interface Blocks         | 1      | 2      | 2      | 2      | 2      | 0      | 2      | 2      |
| 10/100/1000 Ethernet MAC Blocks       | 4      | 4      | 4      | 4      | 4      | 0      | 4      | 4      |
| GTX Low Power Transceivers            | 12     | 20     | 20     | 24     | 24     | 36     | 0      | 24     |

|              | CLB     | Dist RAM   | Block RAM   | Multipliers   |
|--------------|---------|------------|-------------|---------------|
| Virtex 2     | 8,448   | 1,056 kbit | 2,592 kbit  | 144 (18x18)   |
| Virtex 6     | 667,000 | 6,200 kbit | 22,752 kbit | 1,344 (25x18) |
| Spartan 3E   | 240     | 15 kbit    | 72 kbit     | 4 (18x18)     |
| Artix-7 A100 | 7,925   | 1,188 kbit | 4,860 kbit  | 240 (25x18)   |



## Design Flow - Mapping

- Technology Mapping: Schematic/HDL to Physical Logic units
- Compile functions into basic LUT-based groups (function of target architecture)




```


always @(posedge clock or negedge reset)
begin
  if (! reset)
    q <= 0;
  else
    q <= (a&b&c) || (b&d);
end
    
```
 
## Design Flow - Placement & Route

- **Placement** - assign logic location on a particular device



 - **Routing** - iterative process to connect CLB inputs/outputs and IOBs. Optimizes critical path delay - can take hours or days for large, dense designs



Iterate placement if timing not met

Satisfy timing? → Generate Bitstream to config device

Challenge! Cannot use full chip for reasonable speeds (wires are not ideal).


Typically no more than 50% utilization.

## Example: Verilog to FPGA

```

module adder64 (
  input [63:0] a, b;
  output [63:0] sum);
  assign sum = a + b;
endmodule
    
```

- Synthesis
- Tech Map
- Place&Route

 


Virtex II - XC2V2000

64-bit Adder Example




## How are FPGAs Used?

### Logic Emulation

 

- Prototyping
  - Ensemble of gate arrays used to emulate a circuit to be manufactured
  - Get more/better/faster debugging done than with simulation
- Reconfigurable hardware
  - One hardware block used to implement more than one function
- Special-purpose computation engines
  - Hardware dedicated to solving one problem (or class of problems)
  - Accelerators attached to general-purpose computers (e.g., in a cell phone!)

 

FPGA-based Emulator (courtesy of IKOS)

## Summary

- FPGA provide a flexible platform for implementing digital computing
- A rich set of macros and I/Os supported (multipliers, block RAMS, ROMS, high-speed I/O)
- A wide range of applications from prototyping (to validate a design before ASIC mapping) to high-performance spatial computing
- Interconnects are a major bottleneck (physical design and locality are important considerations)

## Test Bench

```
module sample_tf;
  // Inputs
  reg bit_in;
  reg [3:0] bus_in;

  // Outputs
  wire out_bit;
  wire [7:0] out_bus;

  // Instantiate the Unit Under Test (UUT)
  sample uut (
    .bit_in(bit_in),
    .bus_in(bus_in),
    .out_bit(out_bit),
    .out_bus(out_bus)
  );

  initial begin
    // Initialize Inputs
    bit_in = 0;
    bus_in = 0;

    // Wait 100 ns for global reset to finish
    #100;

    // Add stimulus here

  end
endmodule
```

```
module sample(
  {input bit_in,
   input [3:0] bus_in,
  {output out_bit,
   output [7:0] out_bus
  };
  . . . Verilog . . .
endmodule
```

