



# **L10: Major/Minor FSMs, Lab 3, and RAM/ROM Instantiation**




**Acknowledgements: Rex Min**



# Toward FSM Modularity




- Consider the following abstract FSM:

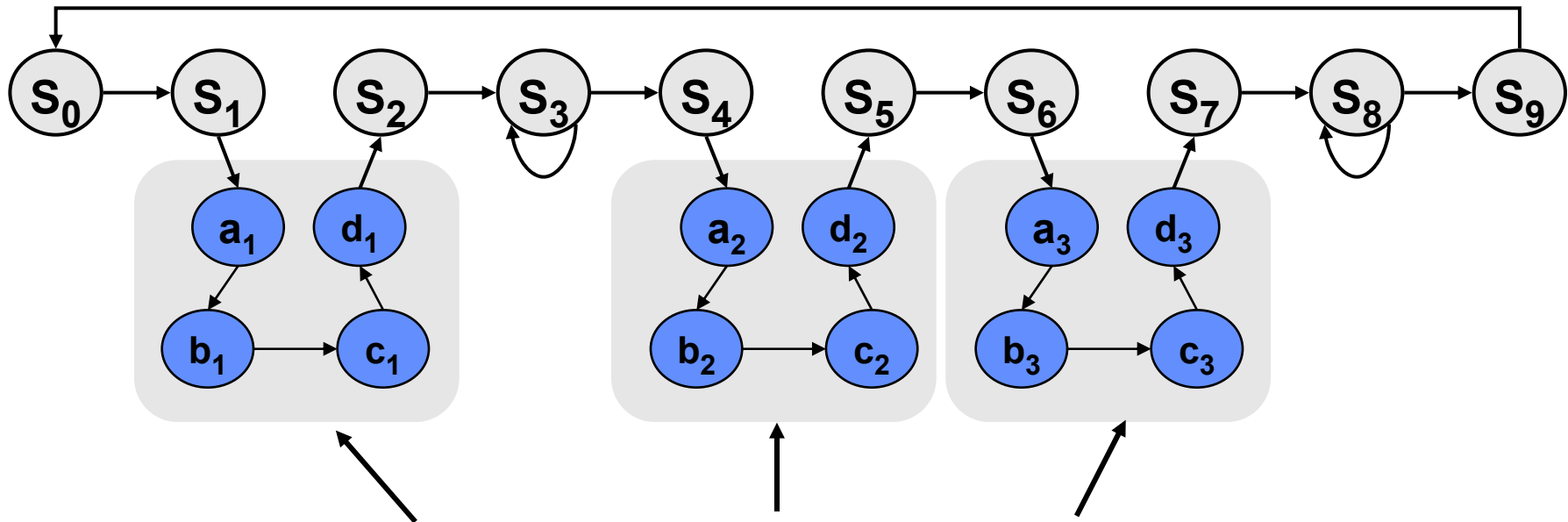

- Suppose that each set of states  $a_x \dots d_x$  is a “sub-FSM” that produces exactly the same outputs.
- Can we simplify the FSM by removing equivalent states?  
*No! The outputs may be the same, but the next-state transitions are not.*
- This situation closely resembles a **procedure call** or **function call** in software...how can we apply this concept to FSMs?




# The Major/Minor FSM Abstraction

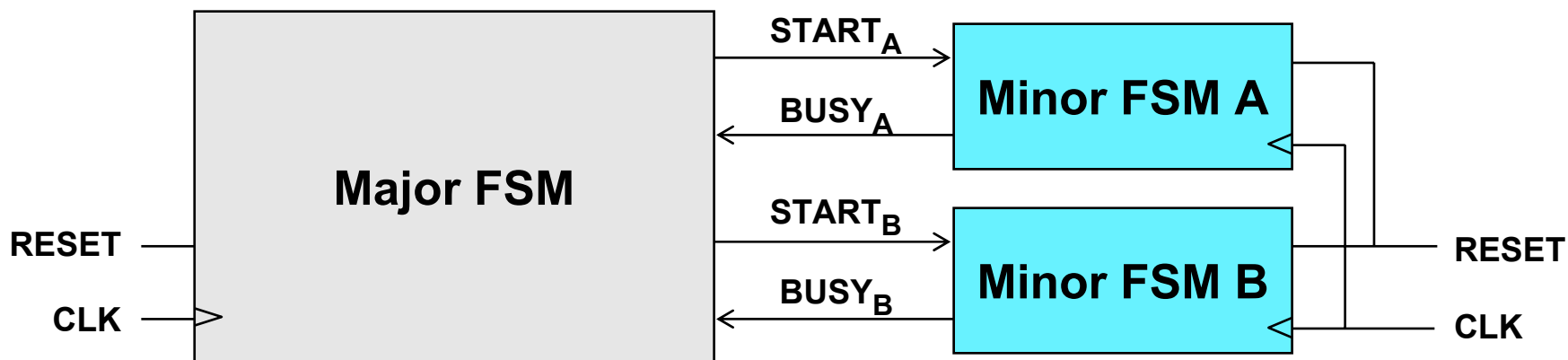

- Subtasks are encapsulated in **minor FSMs** with common reset and clock
- Simple communication abstraction:
  - **START**: tells the minor FSM to begin operation (the call)
  - **BUSY**: tells the major FSM whether the minor is done (the return)
- The major/minor abstraction is great for...
  - Modular designs (*always* a good thing)
  - Tasks that occur often but in different contexts
  - Tasks that require a variable/unknown period of time
  - Event-driven systems




# Inside the Major FSM

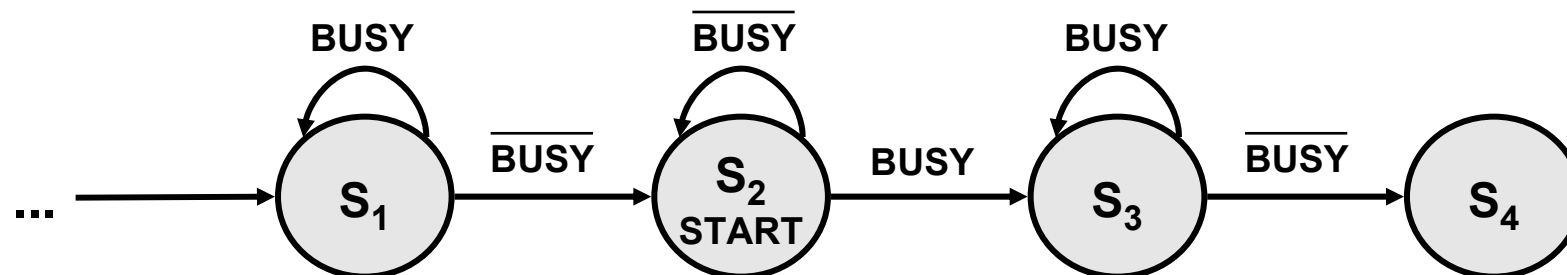

1. Wait until the minor FSM is ready

2. Trigger the minor FSM (and make sure it's started)

3. Wait until the minor FSM is done

 




# Inside the Minor FSM




1. Wait for a trigger from the major FSM

 


3. Signal to the major FSM that work is done

2. Do some useful work

 




# Optimizing the Minor FSM

 


 Good idea: de-assert BUSY one cycle early



 
## Bad idea #1:

T<sub>4</sub> may not immediately return to T<sub>1</sub>




## Bad idea #2:

BUSY never asserts!

 




# A Four-FSM Example

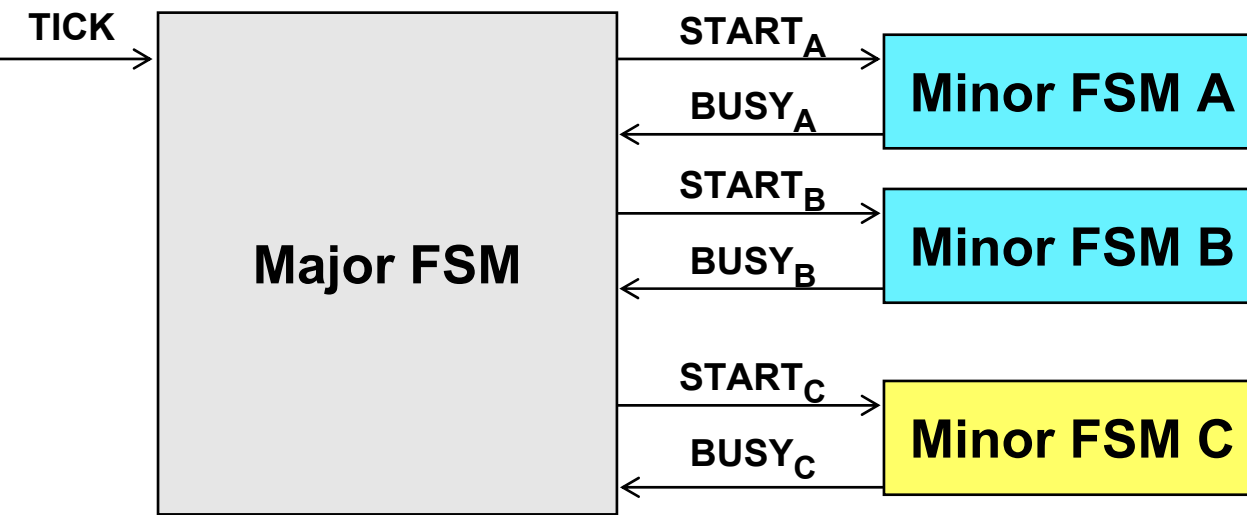


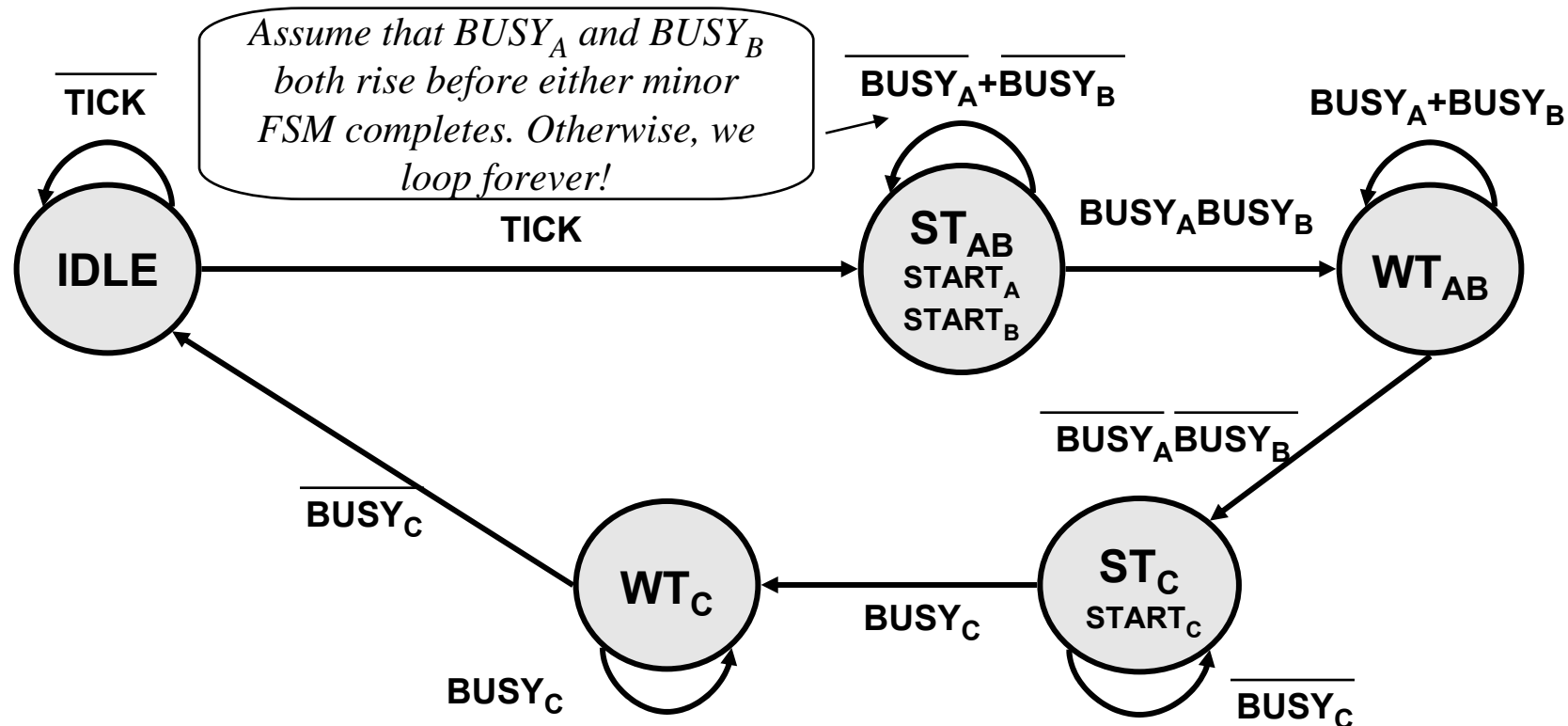
## Operating Scenario:

- Major FSM is triggered by TICK
- Minors A and B are started simultaneously
- Minor C is started once both A and B complete
- TICKs arriving before the completion of C are ignored







# Four-FSM Sample Waveform

 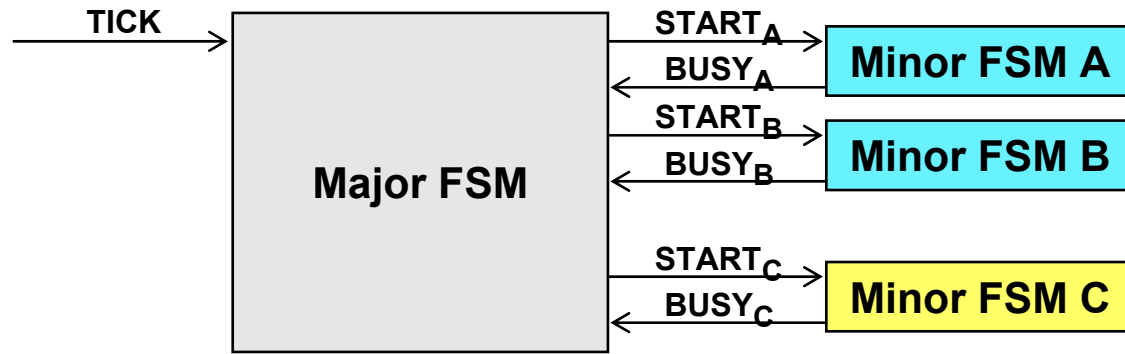





# Lab3 Block Diagram

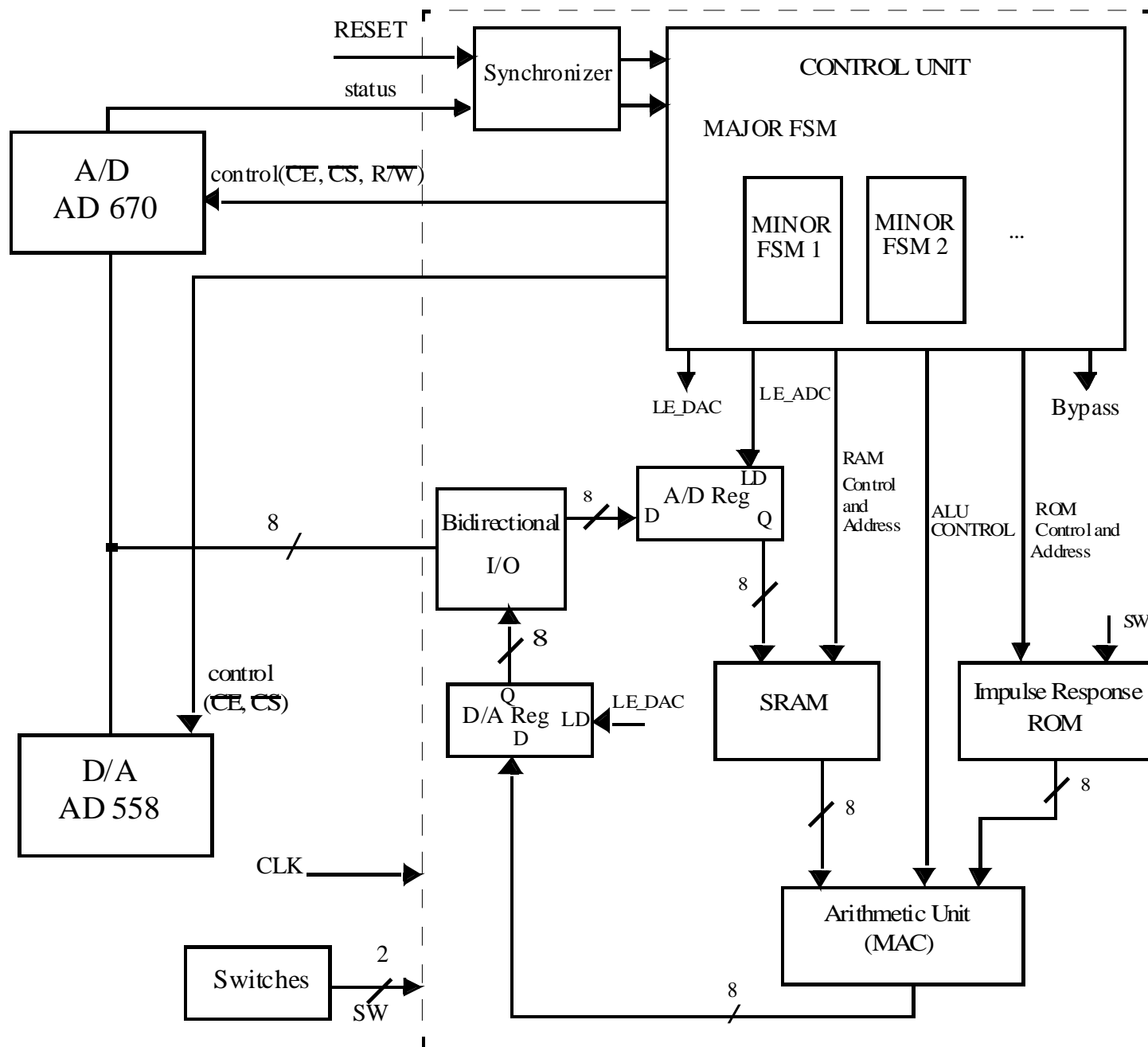 


- Must choose a shared bus for the A/D and DA
- A/D output in twos complement and ROM in sign/magnitude
- Use on-chip SRAM and ROM
- Sample rate is fixed at 20kHz
- Must use a memory based approach to FIR, not tapped delay line (i.e., registers)
- Must use Major/Minor FSM structure


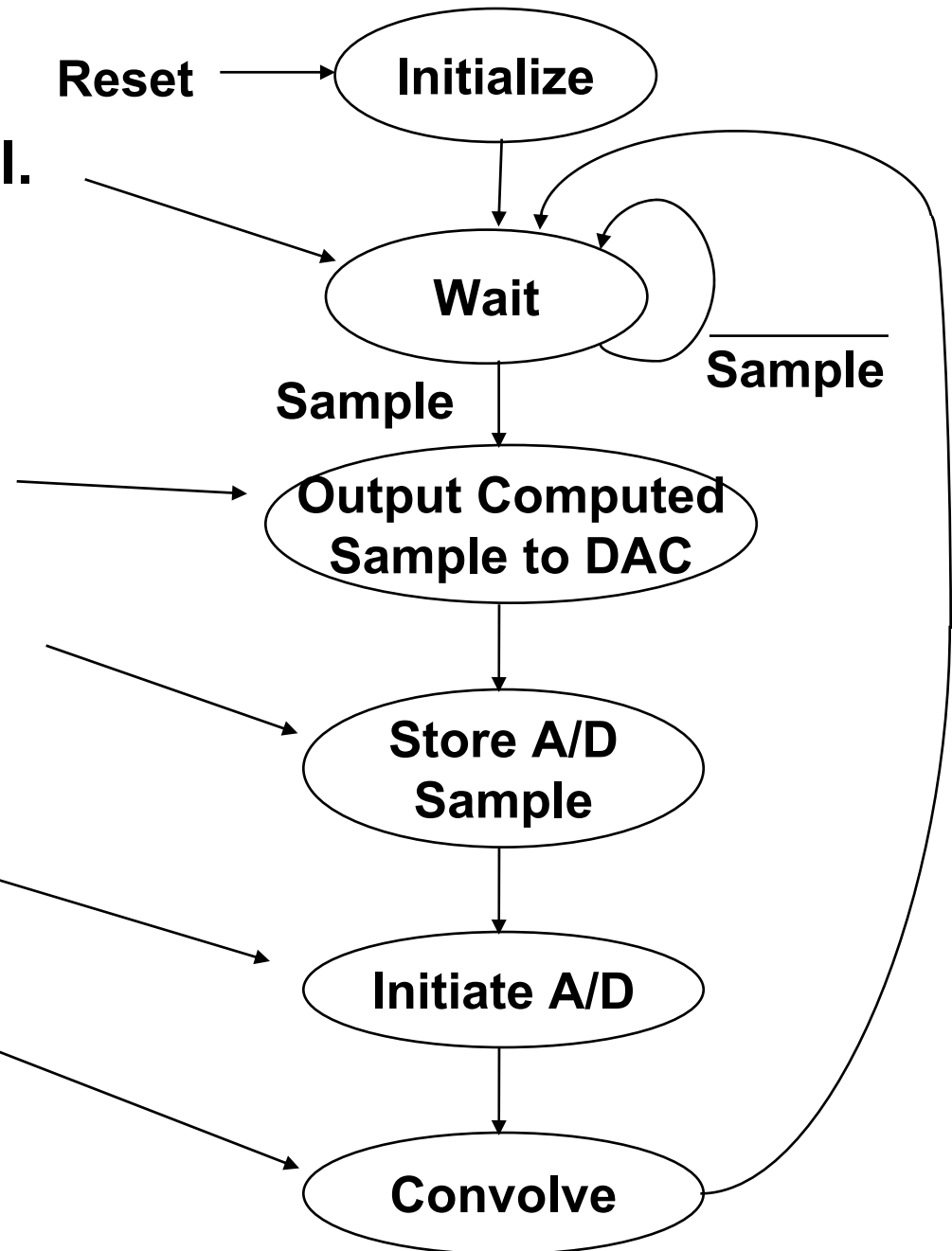
# Control Flow for Lab3



- Wait for a fixed time interval.
- Output what was computed on the last sample.
- Store the previous A/D sample into memory.
- Start the next A/D conversion.
- Do the FIR filter algorithm which is a convolution.
- Go back for more...





# Use LPM to Create ROM/RAM



- **Click on File → MegaWizard Plug-In Manager**
  - This starts up a series of windows so that you can specify parameters of the LPM module. You can choose
    - ROM
    - RAM
      - dp - Dual Ported
      - dq - Separate Inputs and Outputs
      - io - TriState Inputs and Outputs (like the 6264)
  - You choose the number of address bits and the word size.
  - You should specify a file to set the values of the ROM.
  - You can choose registered or unregistered inputs, outputs, and addresses.



# ROM Contents



- Prepare a .dat file.
  - You can type this in, write a computer program, get it from another application (speech or graphics, etc.)
  - This has numbers separated by white space.
    - The default base is HEX but you can use binary or decimal if you include the following statement (before the numbers).  
# BASE = BINARY;
  - Insert, # SET\_ADDRESS = 0; (specifies that data should start at address 0)
- Run dat2ntl on Athena to format your .dat file into Intel HEX
  - for details, after 'setup 6.111' type 'man dat2ntl'
  - dat2ntl <filename>.dat <filename>.ntl

rom8x8.dat:

# SET\_ADDRESS = 0;

7

6

5


4

3

2

1

0

 


rom8x8.ntl:

:080000000706050403020100DC

:00000001FF

tool on athena

 

See <http://web.mit.edu/6.111/www/s2004/software.html> for .mif format (memory initialization format)



# rom8x8.v (generated automatically)



```
//=====
// File Name: rom8x8.v
// Megafunction Name(s):
//                               lpm_rom
//=====
```

Example: 8 deep by 8 bits wide


```
module rom8x8 (
    address,
    q);
input    [2:0] address;
output   [7:0] q;

wire [7:0] sub_wire0;
wire [7:0] q = sub_wire0[7:0];


lpm_rom    lpm_rom_component (
    .address (address),
    .q (sub_wire0));

defparam
    lpm_rom_component.lpm_width = 8,
    lpm_rom_component.lpm_widthad = 3,
    lpm_rom_component.lpm_address_control = "UNREGISTERED",
    lpm_rom_component.lpm_outdata = "UNREGISTERED",
    lpm_rom_component.lpm_file = "rom8x8.ntl";

endmodule
```

 

← Path to location of Rom data

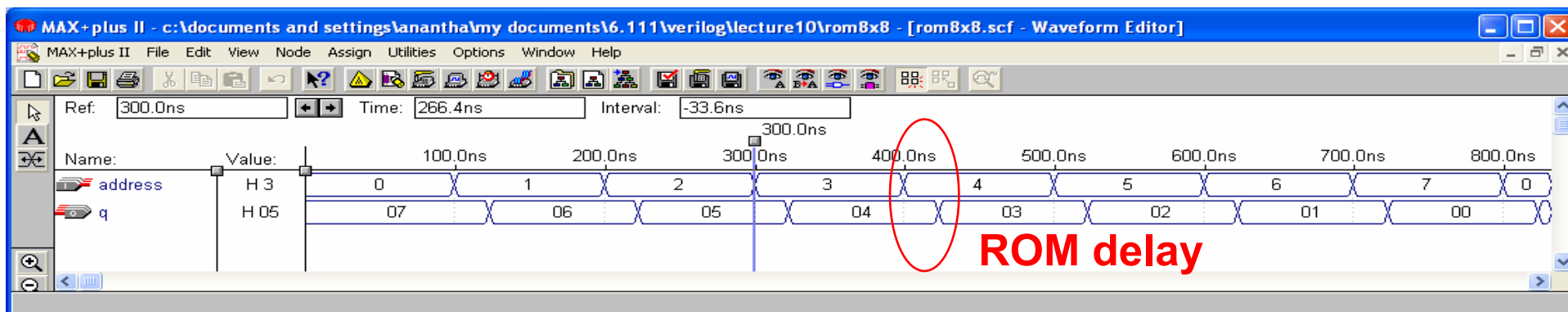



# ram4x2.v



```
// megafunction wizard: %LPM_RAM_DQ%
```

```
module ram4x2 (
```

```
    address,
```

```
    we,
```

```
    data,
```

```
    q);
```

```
    input      [1:0] address;
```

```
    input      we;
```

```
    input      [1:0] data;
```

```
    output     [1:0] q;
```

```
    wire [1:0] sub_wire0;
```

```
    wire [1:0] q = sub_wire0[1:0];
```

```
    lpm_ram_dq lpm_ram_dq_component (
```

```
        .address (address),
```

```
        .data (data),
```

```
        .we (we),
```

```
        .q (sub_wire0));
```

```
    defparam
```

```
        lpm_ram_dq_component.lpm_width = 2,
```

```
        lpm_ram_dq_component.lpm_widthad = 2,
```


```
        lpm_ram_dq_component.lpm_indata = "UNREGISTERED",
```

```
        lpm_ram_dq_component.lpm_address_control = "UNREGISTERED",
```

```
        lpm_ram_dq_component.lpm_outdata = "UNREGISTERED",
```


```
        lpm_ram_dq_component.lpm_hint = "USE_EAB=ON";
```

```
endmodule
```

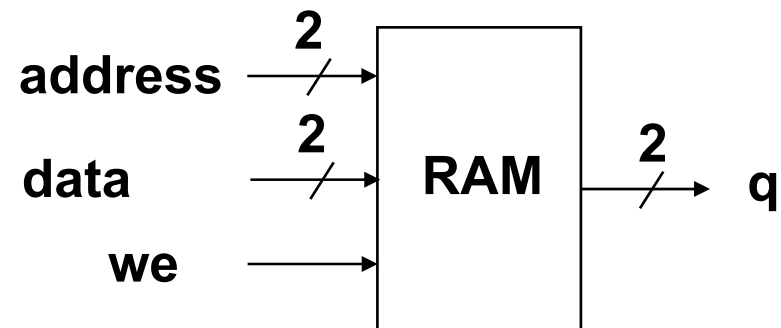



# Asynchronous RAM Simulation

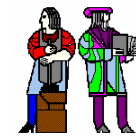


```


module ram4x2 (
    address,
    we,
    data,
    q);

    input    [1:0] address;
    input    we;
    input    [1:0] data;
    output   [1:0] q;

```


 


endmodule

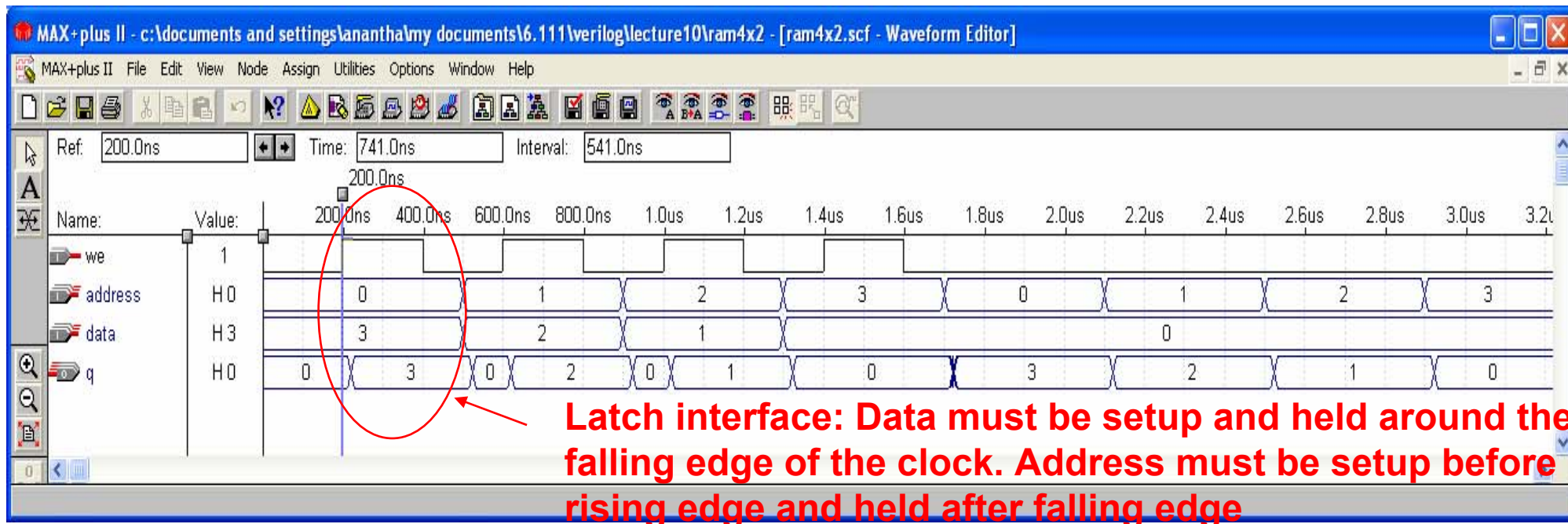


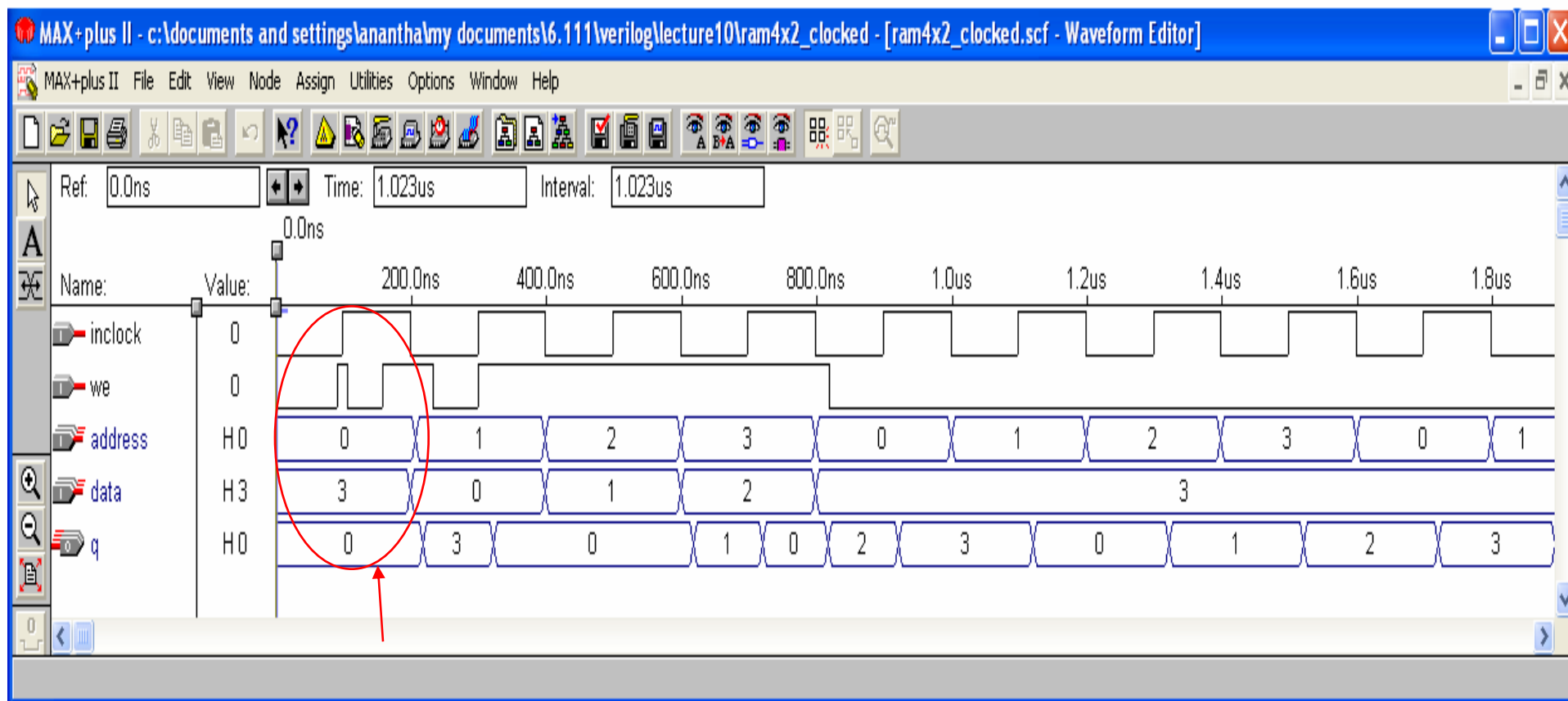 
# SRAM with Registered Address and Data (Synchronous)



## Register interface:

Address, data and we should be setup and held on the rising edge of clock

If we=1 on the rising edge, a write operation takes place

If we=0 on the rising edge, a read operation takes place