 




L15: Custom and ASIC VLSI Integration




Acknowledgement:

J. Rabaey, A. Chandrakasan, B. Nikolic, “Digital Integrated Circuits: A Design Perspective”
Prentice Hall, 2003.



Curt Schurgers



Moore's Law

 

In 1965, Gordon Moore was preparing a speech and made a memorable observation. When he started to graph data about the growth in memory chip performance, he realized there was a striking trend. Each new chip contained roughly twice as much capacity as its predecessor, and each chip was released within 18-24 months of the previous chip. If this trend continued, he reasoned, computing power would rise exponentially over relatively brief periods of time.

  


Courtesy of S. Borkar (Intel)



Layout 101





3-D Cross-Section

 

N-channel MOSFET

P-channel MOSFET

Circuit Representation

  


Layout


- Follow simple design rules (contract between process and circuit designers)




Custom Design/Layout

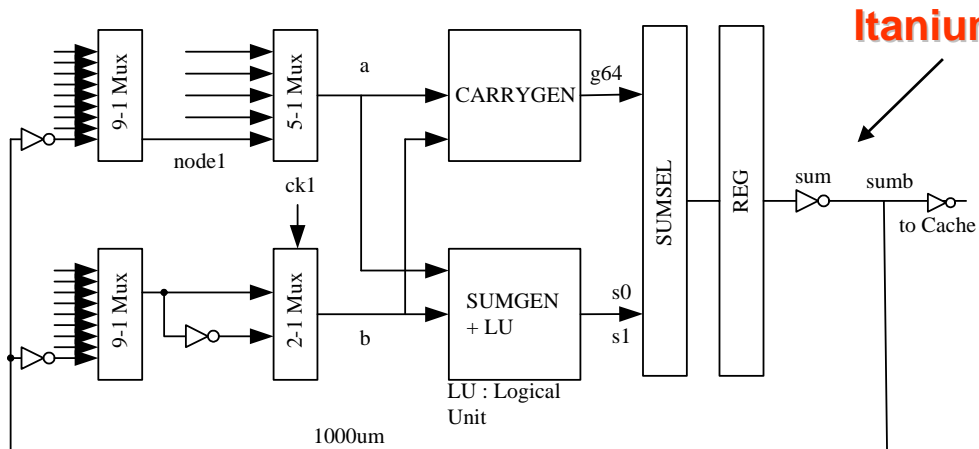

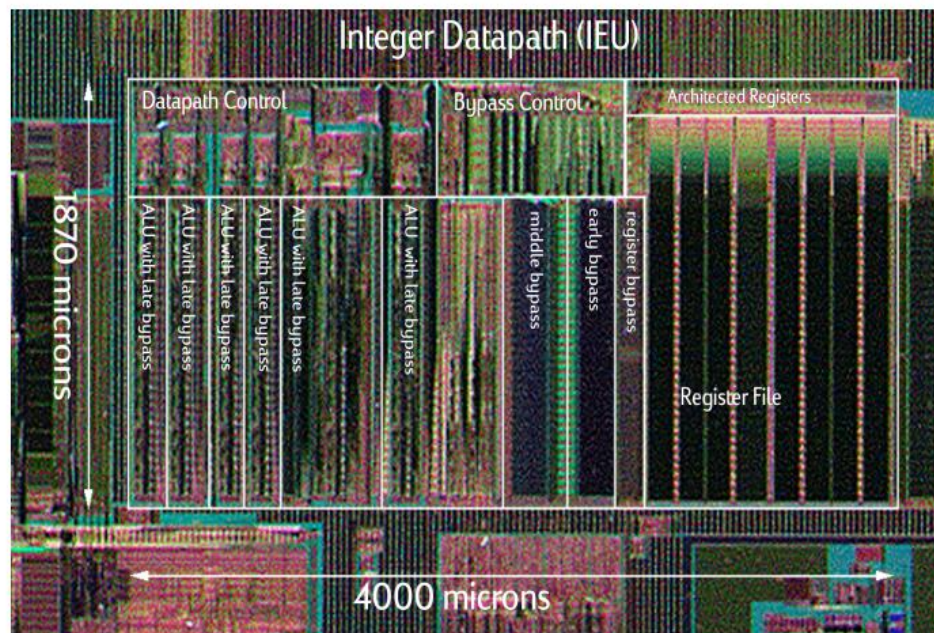Itanium has 6 integer execution units like this



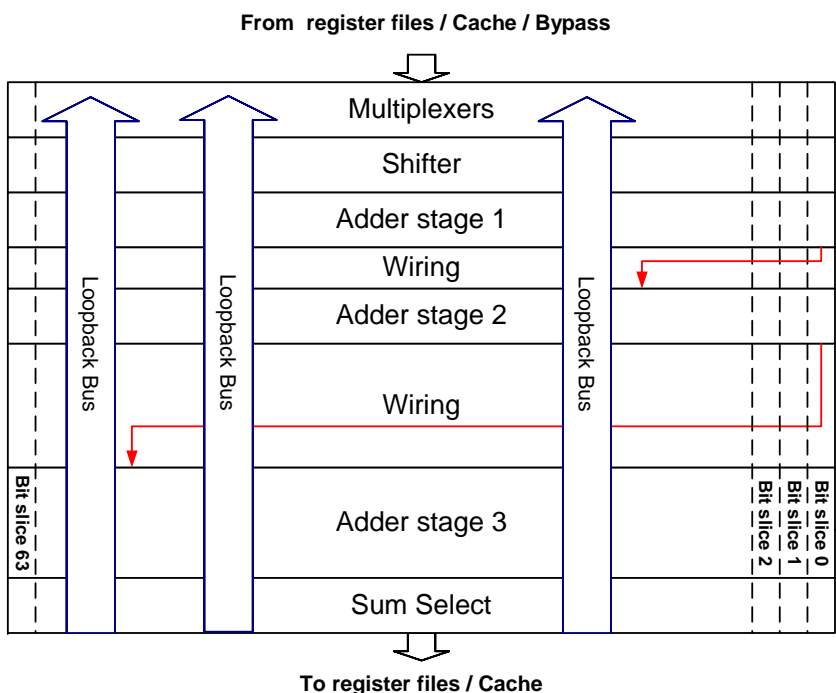Die photograph of the Itanium integer datapath




Bit-slice Design Methodology

- Hand crafting the layout to achieve maximum clock rates (> 1Ghz)
- Exploits regularity in datapath structure to optimize interconnects




The ASIC Approach

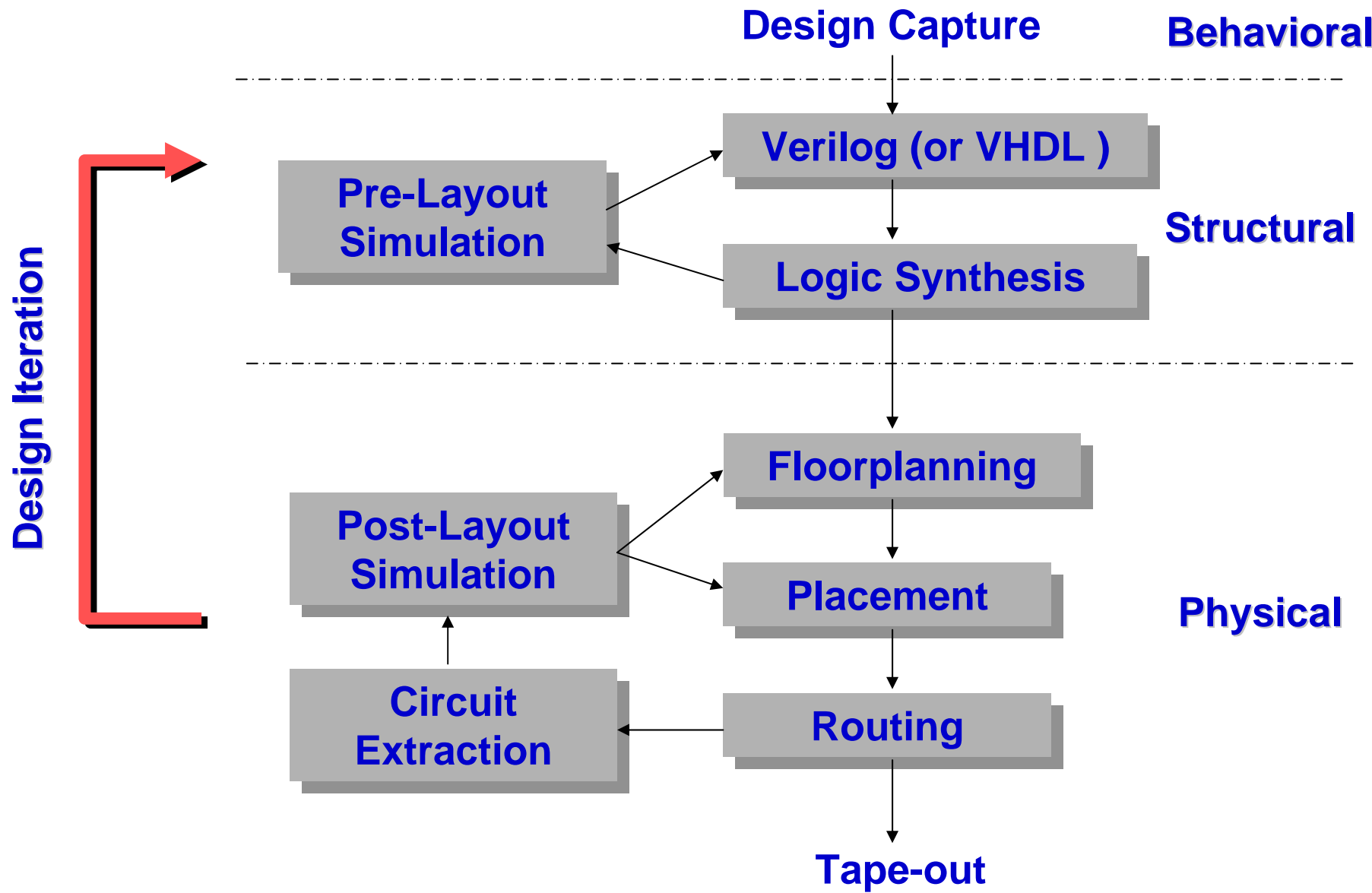

Most Common Design Approach for Designs up to 500Mhz Clock Rates



Standard Cell Example

 

Power Supply Line (V_{DD}) **Delay in (ns)!!**

Path	1.2V - 125°C	1.6V - 40°C
$In1-t_{pLH}$	$0.073+7.98C+0.317T$	$0.020+2.73C+0.253T$
$In1-t_{pHL}$	$0.069+8.43C+0.364T$	$0.018+2.14C+0.292T$
$In2-t_{pLH}$	$0.101+7.97C+0.318T$	$0.026+2.38C+0.255T$
$In2-t_{pHL}$	$0.097+8.42C+0.325T$	$0.023+2.14C+0.269T$
$In3-t_{pLH}$	$0.120+8.00C+0.318T$	$0.031+2.37C+0.258T$
$In3-t_{pHL}$	$0.110+8.41C+0.280T$	$0.027+2.15C+0.223T$

3-input NAND cell
 (from ST Microelectronics):
 C = Load capacitance
 T = input rise/fall time


Ground Supply Line (GND)

- Each library cell (FF, NAND, NOR, INV, etc.) and the variations on size (strength of the gate) is fully characterized across temperature, loading, etc.


Standard Cell Layout Methodology



2-level metal technology

 

Current Day Technology

 

Cell-structure hidden under interconnect layers

- With limited interconnect layers, dedicated routing channels between rows of standard cells are needed
- Width of the cell allowed to vary to accommodate complexity
- Interconnect plays a significant role in speed of a digital circuit



Verilog to ASIC Layout (the push button approach)




```

module adder64 (a, b, sum);
input [63:0] a, b;
output [63:0] sum;



assign sum = a + b;
endmodule

```

After Synthesis

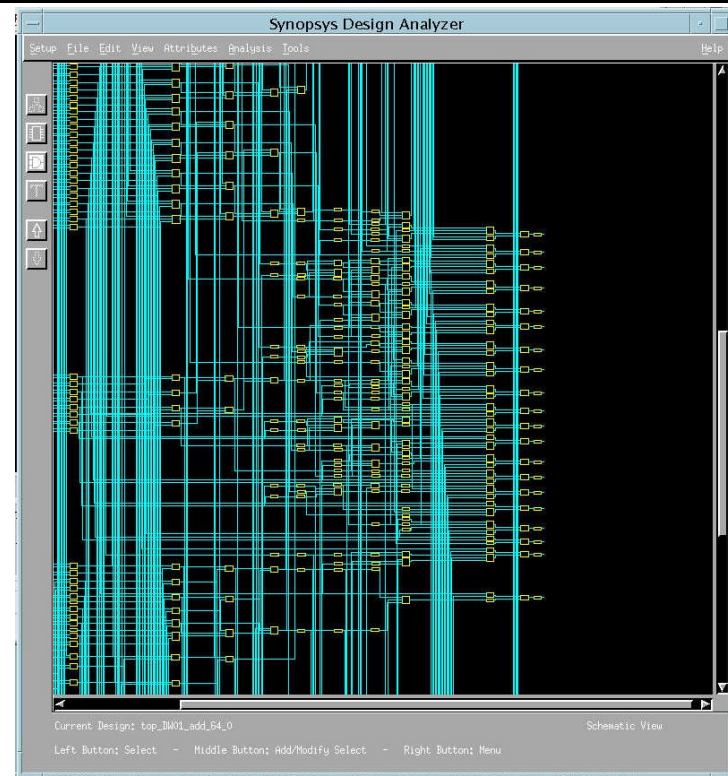



After Routing

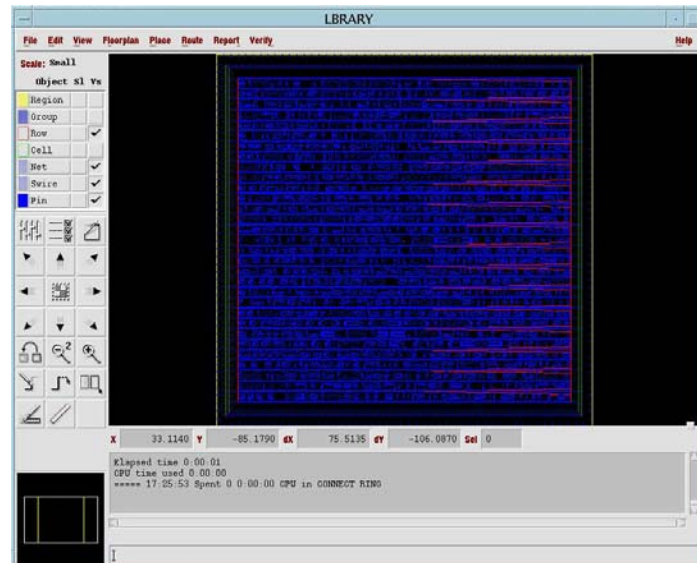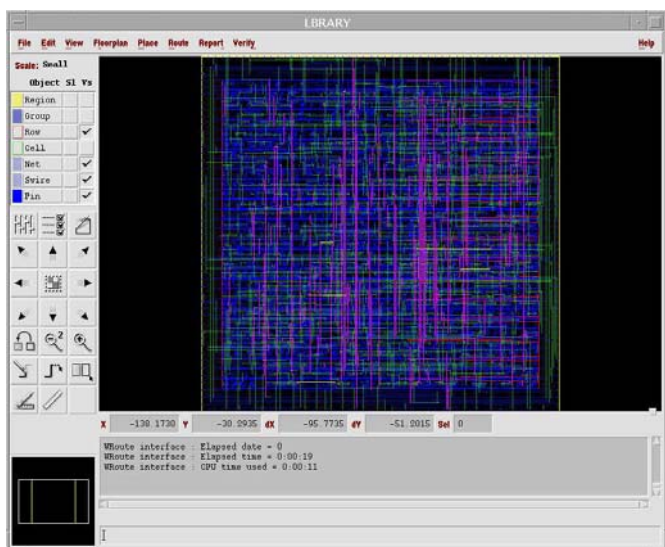

After Placement





The "Design Closure" Problem

 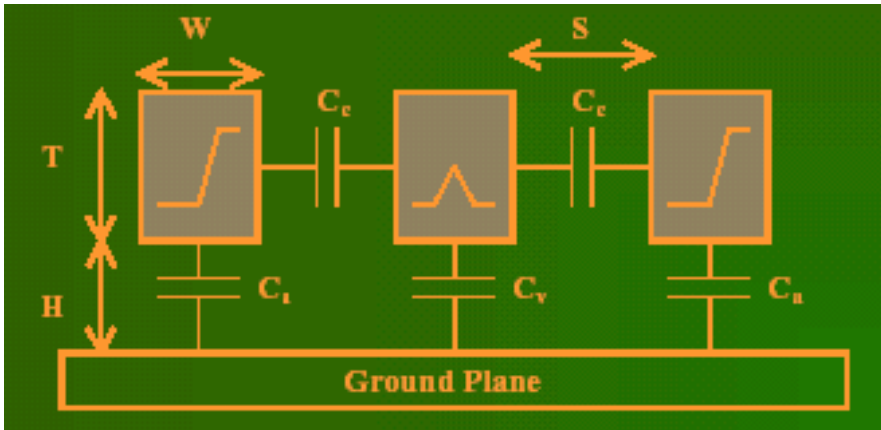

$$\lambda = \frac{C_I}{C_L} = 5$$

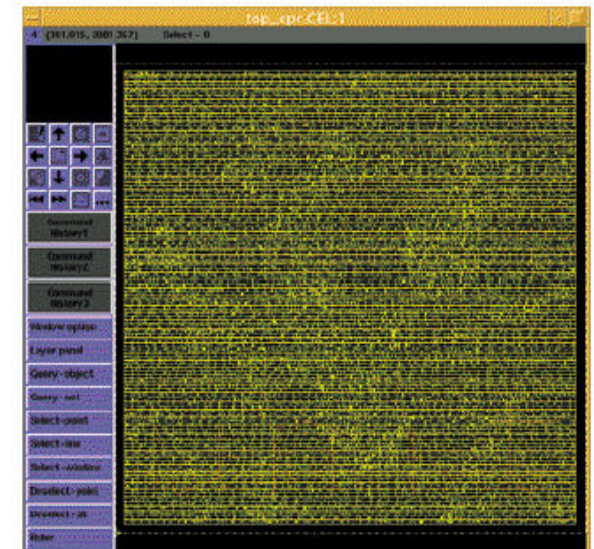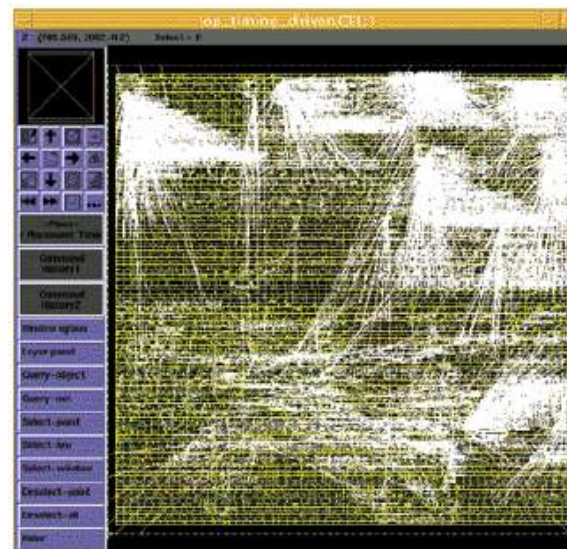Wire-to-wire capacitance causes inter-wire delay dependencies




Iterative Removal of Timing Violations (white lines)



Macro Modules



 256×32 (or 8192 bit) SRAM Generated by hard-macro module generator





- Generate highly regular structures (entire memories, multipliers, etc.) with **a few lines of code**
- Verilog models for memories **automatically** generated based on size



Clock Distribution



Clock skew, courtesy Alpha

  


For 1Ghz clock, skew budget is 100ps.



Variations along different paths arise from:

- Device: V_T , W/L , etc.
- Environment: V_{DD} , $^{\circ}C$
- Interconnect: dielectric thickness variation

IBM Clock Routing

 



The Power Supply Wires are Not Ideal!

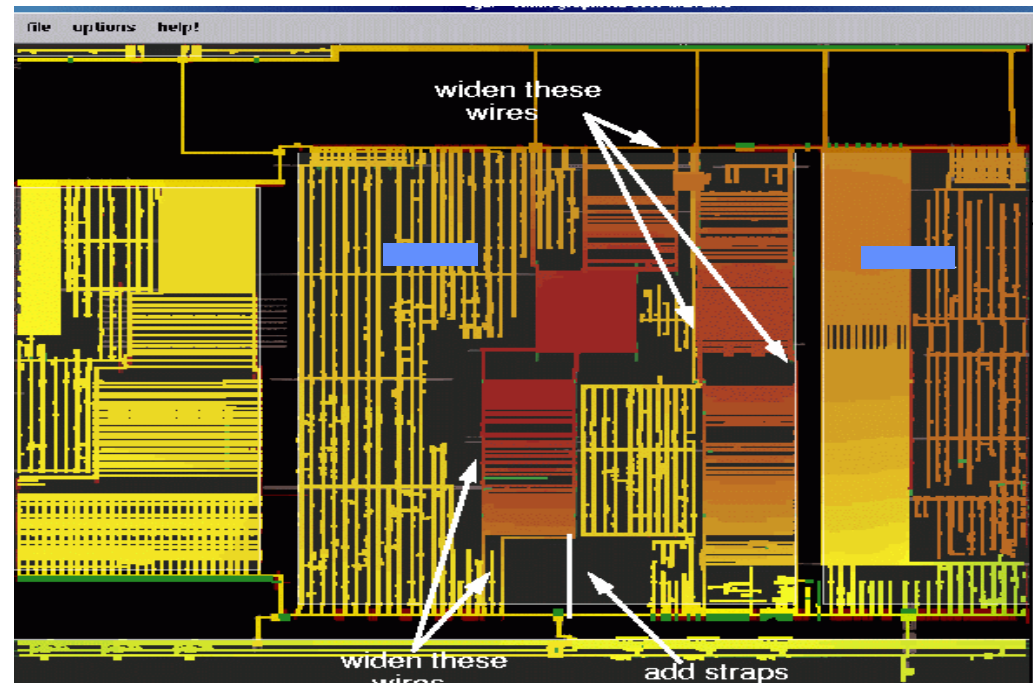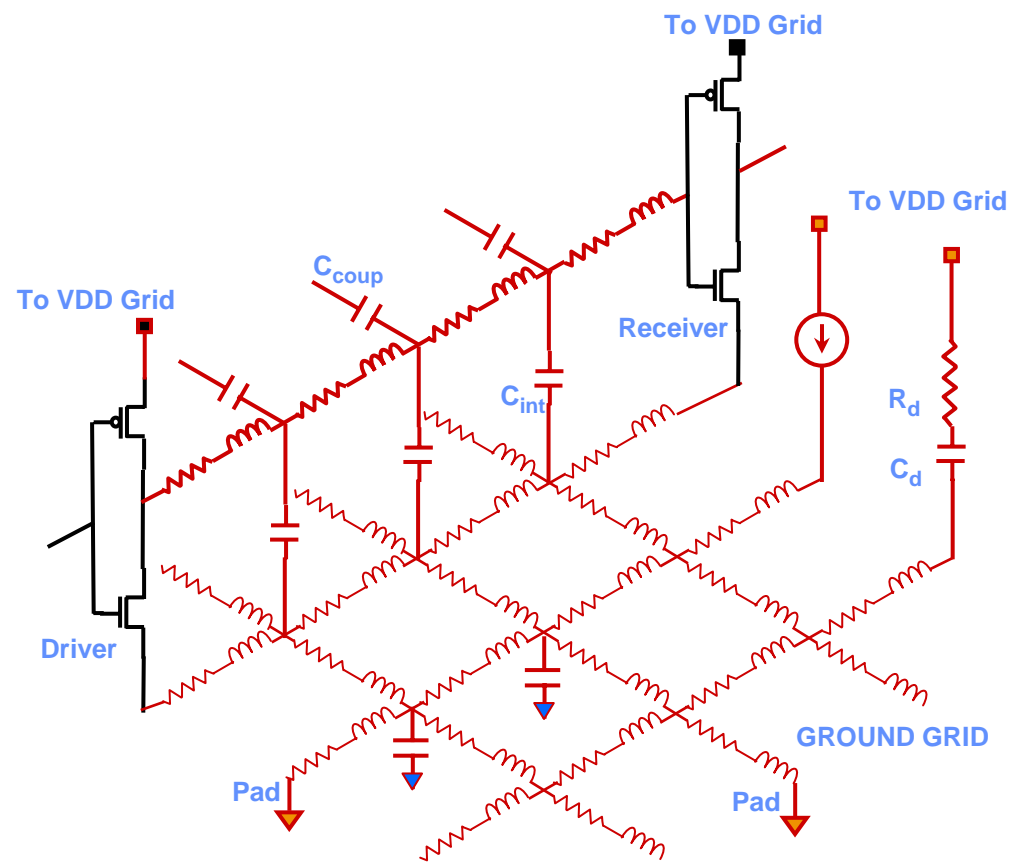

The IR-drop problem causes internal power supply voltage to be less than the external source

Courtesy David Blaauw

 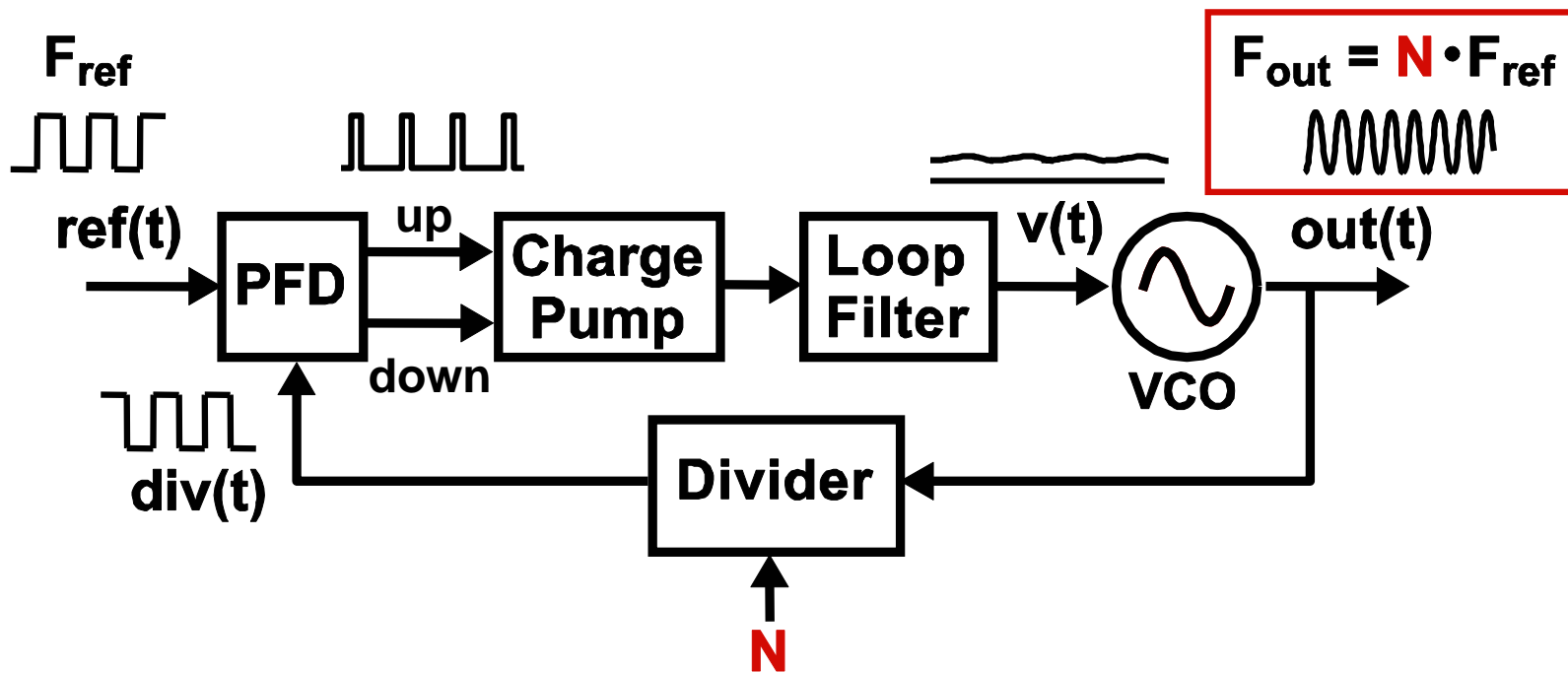Analog Circuits: Clock Frequency Multiplication (Phase Locked Loop)



Intel 486, 50Mhz

- VCO → produces high frequency square wave
- Divider → divides down VCO frequency
- PFD → compares phase of ref and div
- Loop filter → extracts phase error information

Used widely in digital systems for clock synthesis
(a standard IP block in most ASIC flows)

Courtesy M. Perrott




Behavioral Transformations



- There are a large number of implementations of the same functionality
- These implementations present a different point in the area-time-power design space
- Behavioral transformations allow exploring the design space a high-level

Optimization metrics:

 1. **Area** of the design
2. **Throughput** or sample time T_S
3. **Latency**: clock cycles between the input and associated output change
4. **Power** consumption
5. **Energy** of executing a task
6. ...





Fixed-Coefficient Multiplication



Conventional Multiplication

$$Z = X \cdot Y$$


				X_3	X_2	X_1	X_0		
				Y_3	Y_2	Y_1	Y_0		
				$X_3 \cdot Y_0$	$X_2 \cdot Y_0$	$X_1 \cdot Y_0$	$X_0 \cdot Y_0$		
				$X_3 \cdot Y_1$	$X_2 \cdot Y_1$	$X_1 \cdot Y_1$	$X_0 \cdot Y_1$		
				$X_3 \cdot Y_2$	$X_2 \cdot Y_2$	$X_1 \cdot Y_2$	$X_0 \cdot Y_2$		
				$X_3 \cdot Y_3$	$X_2 \cdot Y_3$	$X_1 \cdot Y_3$	$X_0 \cdot Y_3$		
	Z_7	Z_6	Z_5	Z_4	Z_3	Z_2	Z_1	Z_0	

Constant multiplication (become hardwired shifts and adds)

$$Z = X \cdot (1001)_2$$

				X_3	X_2	X_1	X_0		
				1	0	0	1		
				X_3	X_2	X_1	X_0		
				X_3	X_2	X_1	X_0		
	Z_7	Z_6	Z_5	Z_4	Z_3	Z_2	Z_1	Z_0	

$$Y = (1001)_2 = 2^3 + 2^0$$

 




Transform: Canonical Signed Digits (CSD)





Canonical signed digit representation is used to increase the number of zeros. It uses digits $\{-1, 0, 1\}$ instead of only $\{0, 1\}$.

 Iterative encoding: replace string of consecutive 1's



Worst case CSD has 50% non zero bits

01101111
 ||
 10010001

  


Shift translates to re-wiring



Algebraic Transformations




Commutativity

 


$$A + B = B + A$$

Distributivity

 


$$(A + B) C = AB + BC$$

Associativity

 


$$(A + B) + C = A + (B + C)$$

Common sub-expressions

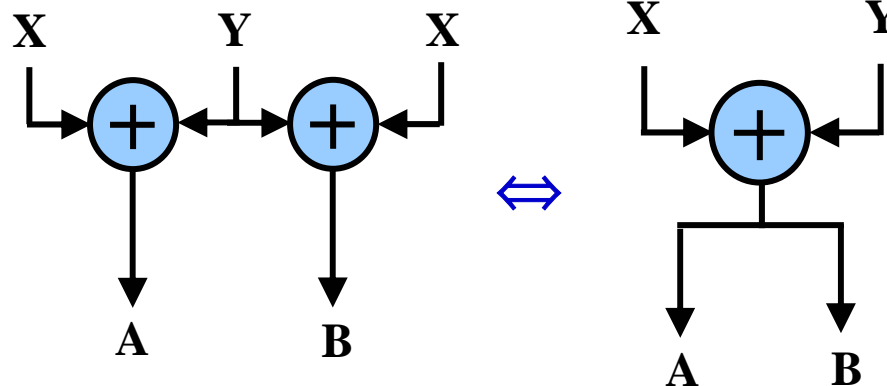




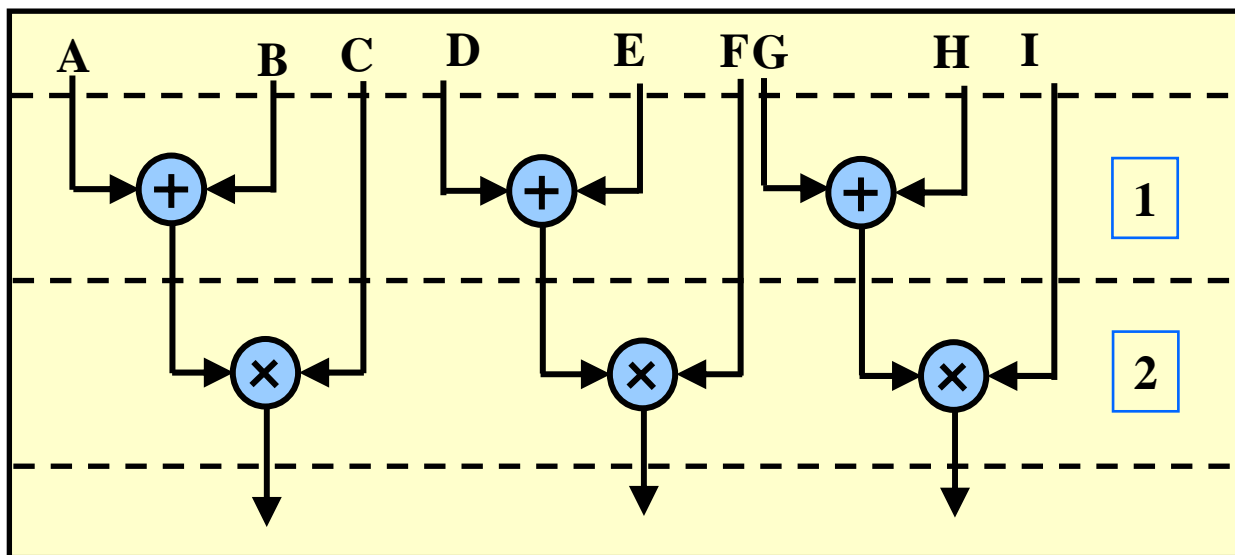
Transforms for Efficient Resource Utilization



 
Time multiplexing: mapped to 3 multipliers and 3 adders



distributivity

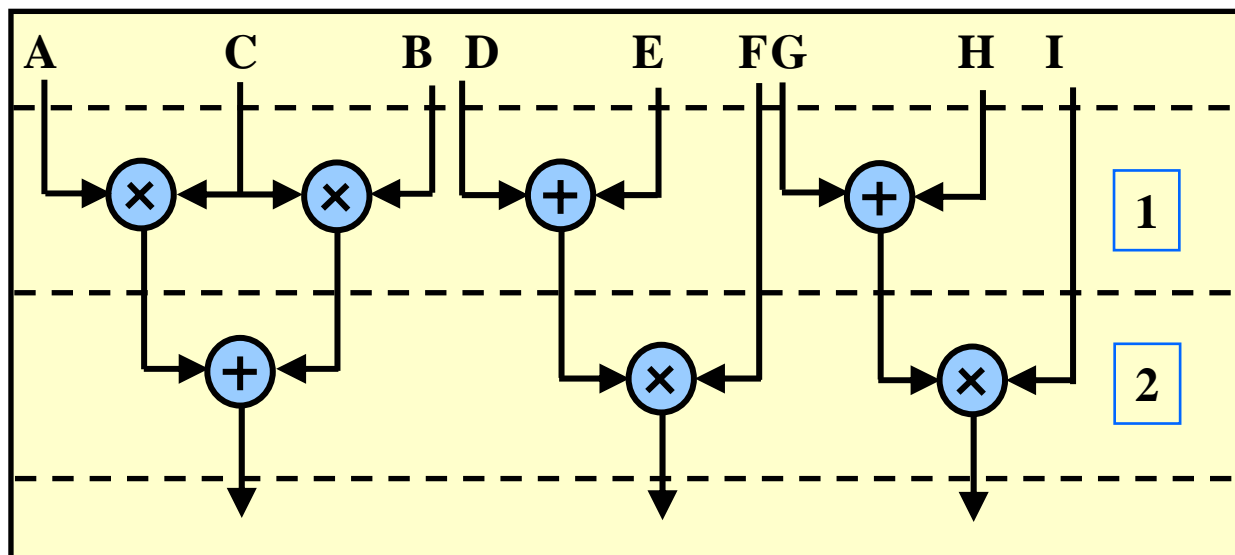

 Reduce number of operators to 2 multipliers and 2 adders






A Very Useful Transform: Retiming




Retiming is the action of moving delay around in the systems

 - Delays have to be moved from ALL inputs to ALL outputs or vice versa




 Cutset retiming: A cutset intersects the edges, such that this would result in two disjoint partitions of these edges being cut. To retime, delays are moved from the ingoing to the outgoing edges or vice versa.





Benefits of retiming:

 - Modify critical path delay
- Reduce total number of registers






Retiming Example: FIR Filter

 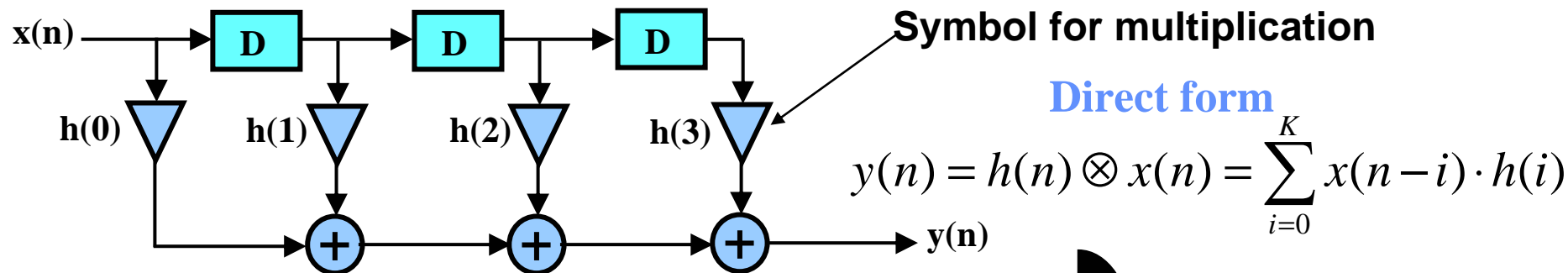

associativity of the addition

$T_{clk} = 22 \text{ ns}$

retime

 


Transposed form $T_{clk} = 14 \text{ ns}$

Note: here we use a first cut analysis that assumes the delay of a chain of operators is the sum of their individual delays. This is not accurate.




 Pipelining, Just Another Transformation (**Pipelining = Adding Delays + Retiming**)



Contrary to retiming,
pipelining adds extra registers
to the system


*add input
registers*

 

How to pipeline:

1. Add extra registers at *all* inputs
2. Retime


retime

 

The Power of Transforms: Lookahead




$$y(n) = x(n) + A y(n-1)$$

 


Try pipelining this structure

How about pipelining this structure!

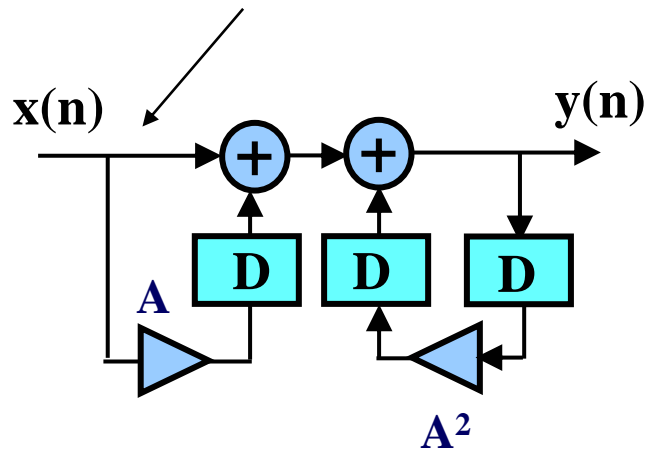


loop unrolling

 


$$y(n) = x(n) + A[x(n-1) + A y(n-2)]$$

distributivity

 

associativity

 


precomputed


retiming



Scan Testing

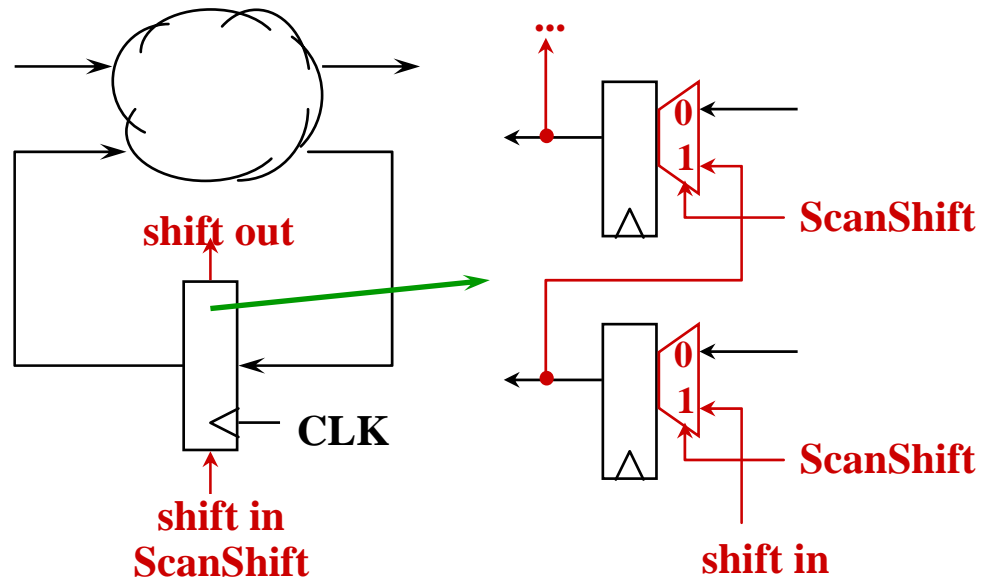


- Idea:** have a mode in which all registers are chained into one giant shift register which can be loaded/read-out bit serially. Test remaining (combinational) logic by
- (1) in “test” mode, shift in new values for all register bits thus setting up the inputs to the combinational logic
 - (2) clock the circuit once in “normal” mode, latching the outputs of the combinational logic back into the registers
 - (3) in “test” mode, shift out the values of all register bits and compare against expected results.

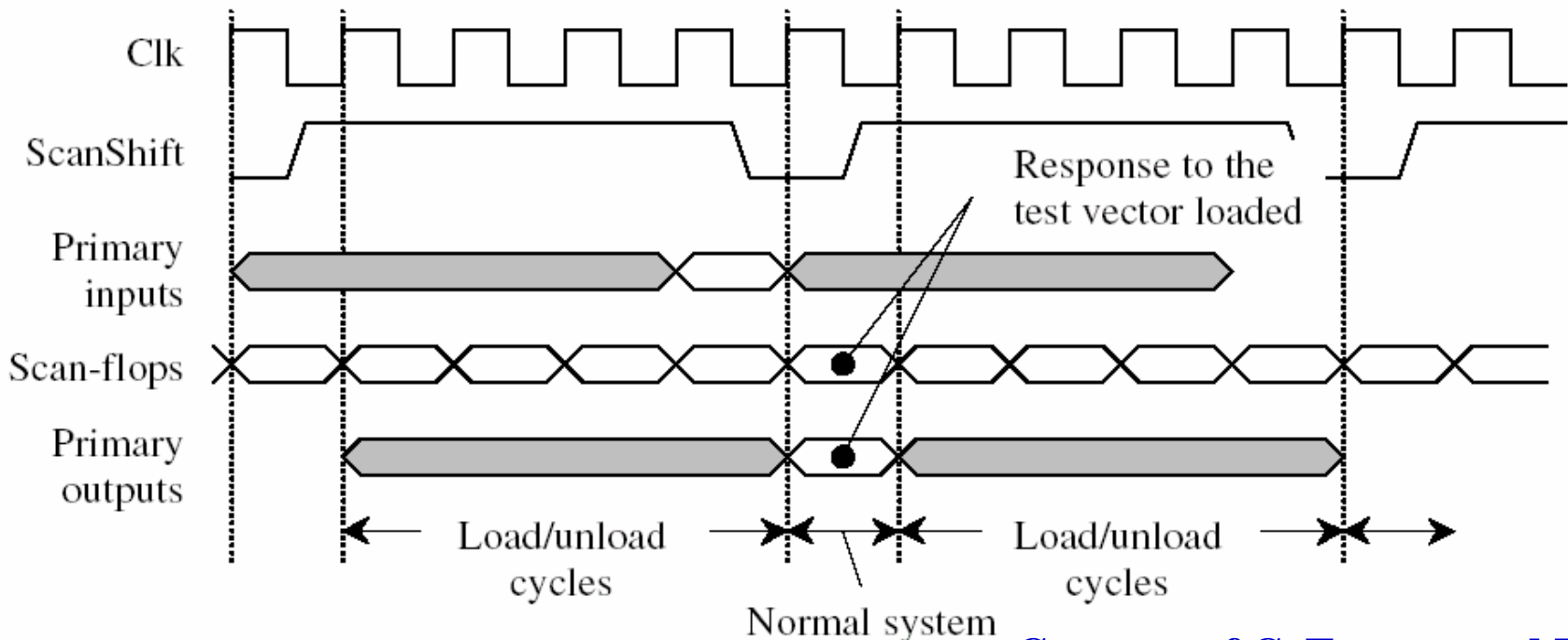

Courtesy of C. Terman and IEEE Press



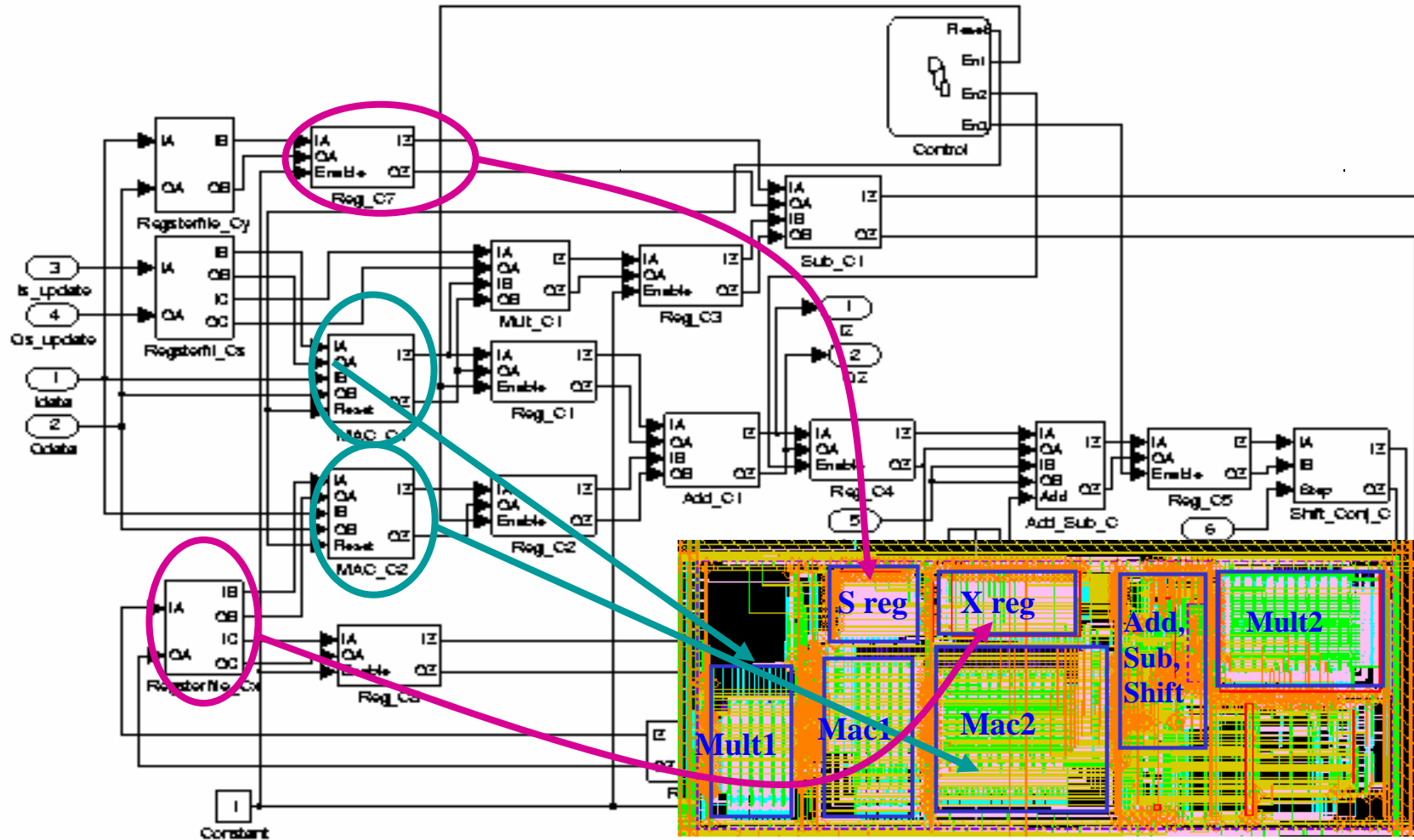Trends: "Chip in a Day" (Matlab/Simulink to Silicon...)



Map algorithms directly to silicon - bypass writing Verilog!

Courtesy of R. Brodersen





Trends: Watermarking of Digital Designs



Fingerprinting is a technique to deter people from illegally redistributing legally obtained IP by enabling the author of the IP to uniquely identify the original buyer of the resold copy.

  The essence of the **watermarking** approach is to encode the author's signature. The selection, encoding, and embedding of the signature must result in minimal performance and storage overhead.



same functionality, same area, same performance
watermark of 4768 bits embedded
(courtesy of G. Qu, M. Potkonjak)