
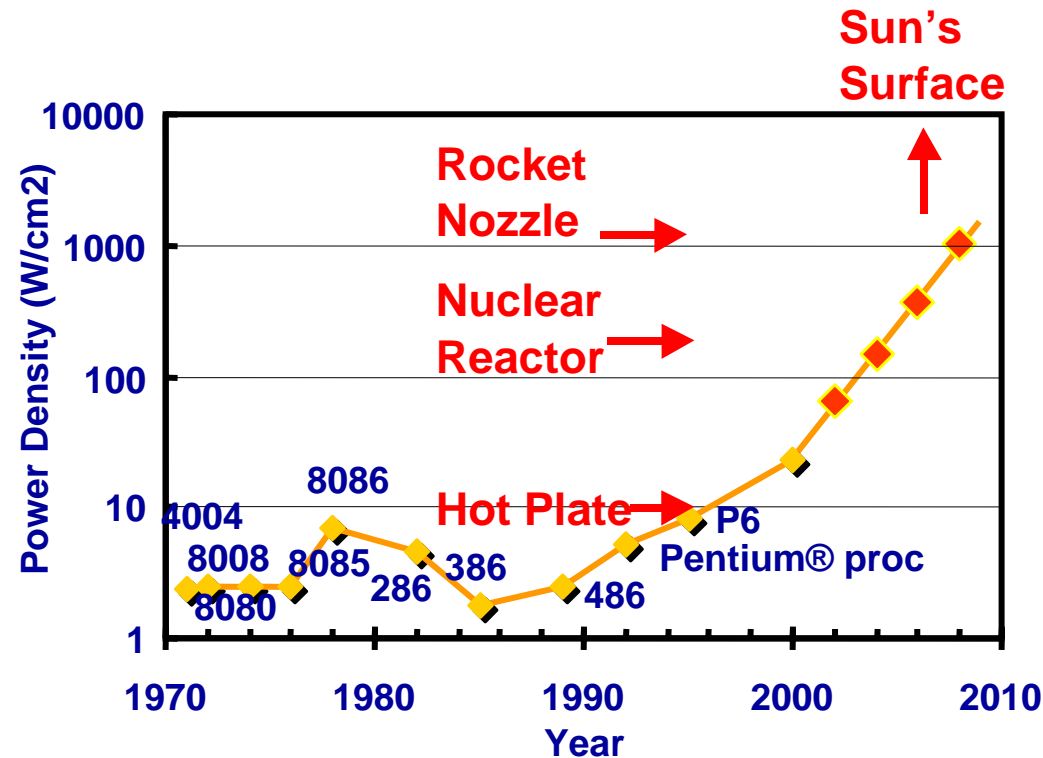


 


L16: Power Dissipation in Digital Systems

Problem #1: Power Dissipation/Heat





Courtesy Intel (S. Borkar)

How do you cool these chips??

 

Problem #2: Energy Consumption

  

(from Jon Eager, Gates Inc. , S. Watanabe, Sony Inc.)

No Moore's law for batteries...


**Today: Understand where power goes
and ways to manage it**




Dynamic Energy Dissipation



Charging

 


Discharging

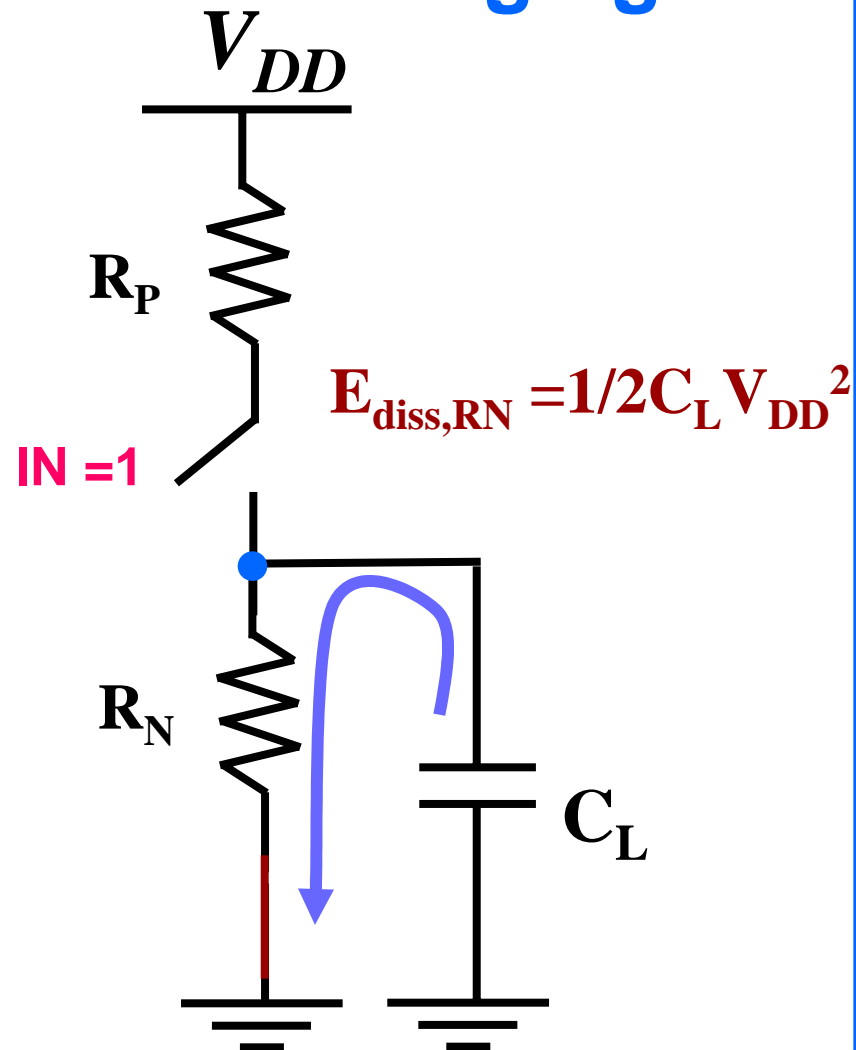


$$P = C_L V_{DD}^2 f_{clk}$$



 Transition Activity Factor $\alpha_{0 \rightarrow 1}$



Current Input	Next Input	Output Transition
00	00	1 \rightarrow 1
00	01	1 \rightarrow 1
00	10	1 \rightarrow 1
00	11	1 \rightarrow 0
01	00	1 \rightarrow 1
01	01	1 \rightarrow 1
01	10	1 \rightarrow 1
01	11	1 \rightarrow 0
10	00	1 \rightarrow 1
10	01	1 \rightarrow 1
10	10	1 \rightarrow 1
10	11	1 \rightarrow 0
11	00	0 \rightarrow 1
11	01	0 \rightarrow 1
11	10	0 \rightarrow 1
11	11	0 \rightarrow 0

 

Assume inputs (A,B) arrive at f and are uniformly distributed

What is the average power dissipation?

$$\alpha_{0 \rightarrow 1} = 3/16$$


$$P = \alpha_{0 \rightarrow 1} C_L V_{DD}^2 f$$



Junction (Silicon) Temperature




Simple Scenario

 

$$T_j - T_a = R_{\theta JA} P_D$$


 
$R_{\theta JA}$ is the thermal resistance between silicon and Ambient



$$T_j = T_a + R_{\theta JA} P_D$$

Make this as low as possible

Realistic Scenario

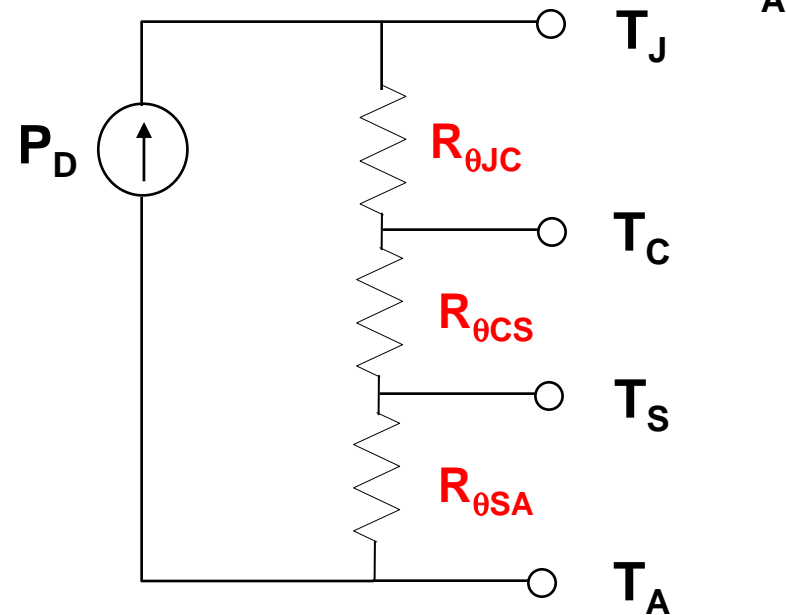 


$$R_{\theta CA} = R_{\theta CS} + R_{\theta SA}$$

is minimized by facilitating heat transfer (bolt case to extended metal surface – heat sink)



Large Thermal Gradients

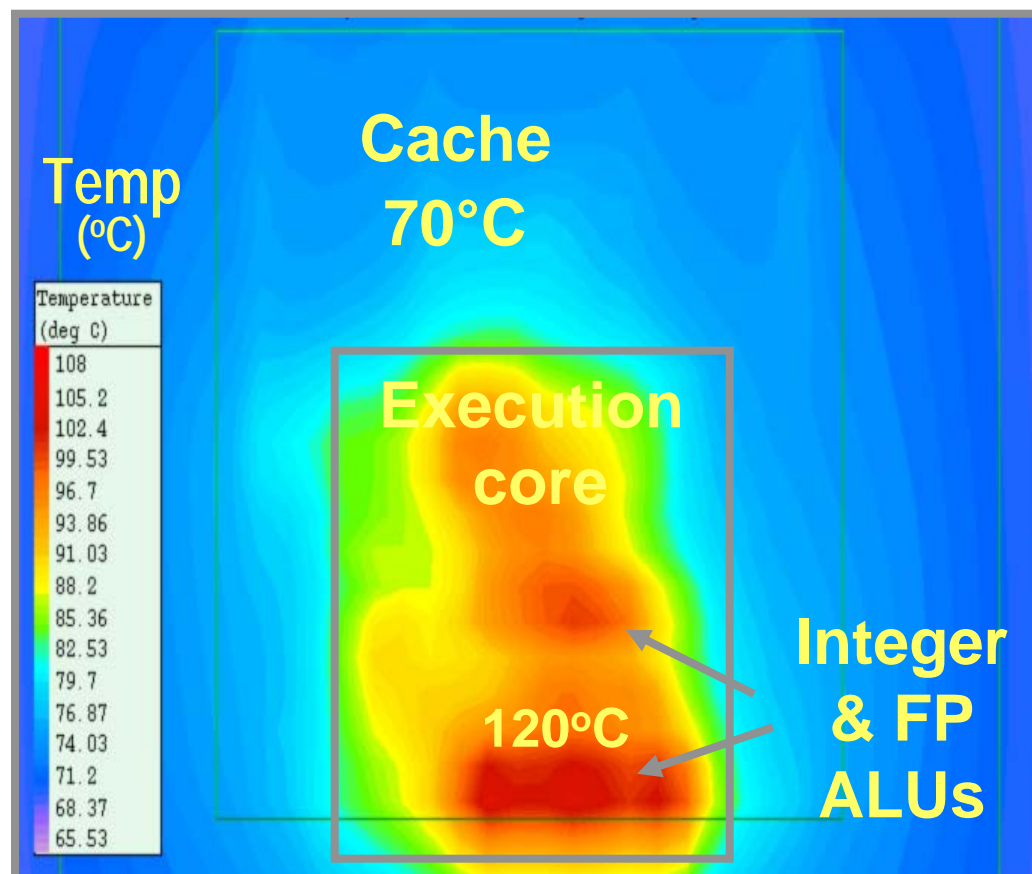



Courtesy of Intel (Ram Krishnamurthy)



Intel Pentium 4 Thermal Guidelines



  - Pentium 4 @ 3.06 GHz dissipates 81.8W!
- Maximum $T_C = 69\text{ }^\circ\text{C}$
- $R_{CA} < 0.23\text{ }^\circ\text{C/W}$ for 50 C ambient
- Typical chips dissipate 0.5-1W (cheap packages without forced air cooling)



Processor and Core Frequency	Thermal Design Power ^{1,2} (W)
Processors with VID=1.500V	
2 GHz	52.4
2.20 GHz	55.1
2.26 GHz	56.0
2.40 GHz	57.8
2.50 GHz	59.3
2.53 GHz	59.3
Processors with VID=1.525V	
2 GHz	54.3
2.20 GHz	57.1
2.26 GHz	58.0
2.40 GHz	59.8
2.50 GHz	61.0
2.53 GHz	61.5
2.60 GHz	62.6
2.66 GHz	66.1
2.80 GHz	68.4
Processors with multiple VIDs	
2 GHz	54.3
2.20 GHz	57.1
2.26 GHz	58.0
2.40 GHz	59.8
2.50 GHz	61.0
2.53 GHz	61.5
2.60 GHz	62.6
2.66 GHz	66.1
2.80 GHz	68.4
3.06 GHz	81.8



Power Reduction Strategies





$$P = \alpha_{0 \rightarrow 1} C_L V_{DD}^2 f$$

- Reduce Transition Activity or Switching Events
- Reduce Capacitance (e.g., keep wires short)
- Reduce Power Supply Voltage
- Frequency is typically fixed by the application, though this can be adjusted to control power

Optimize at all levels of design hierarchy




Clock Gating is a Good Idea!

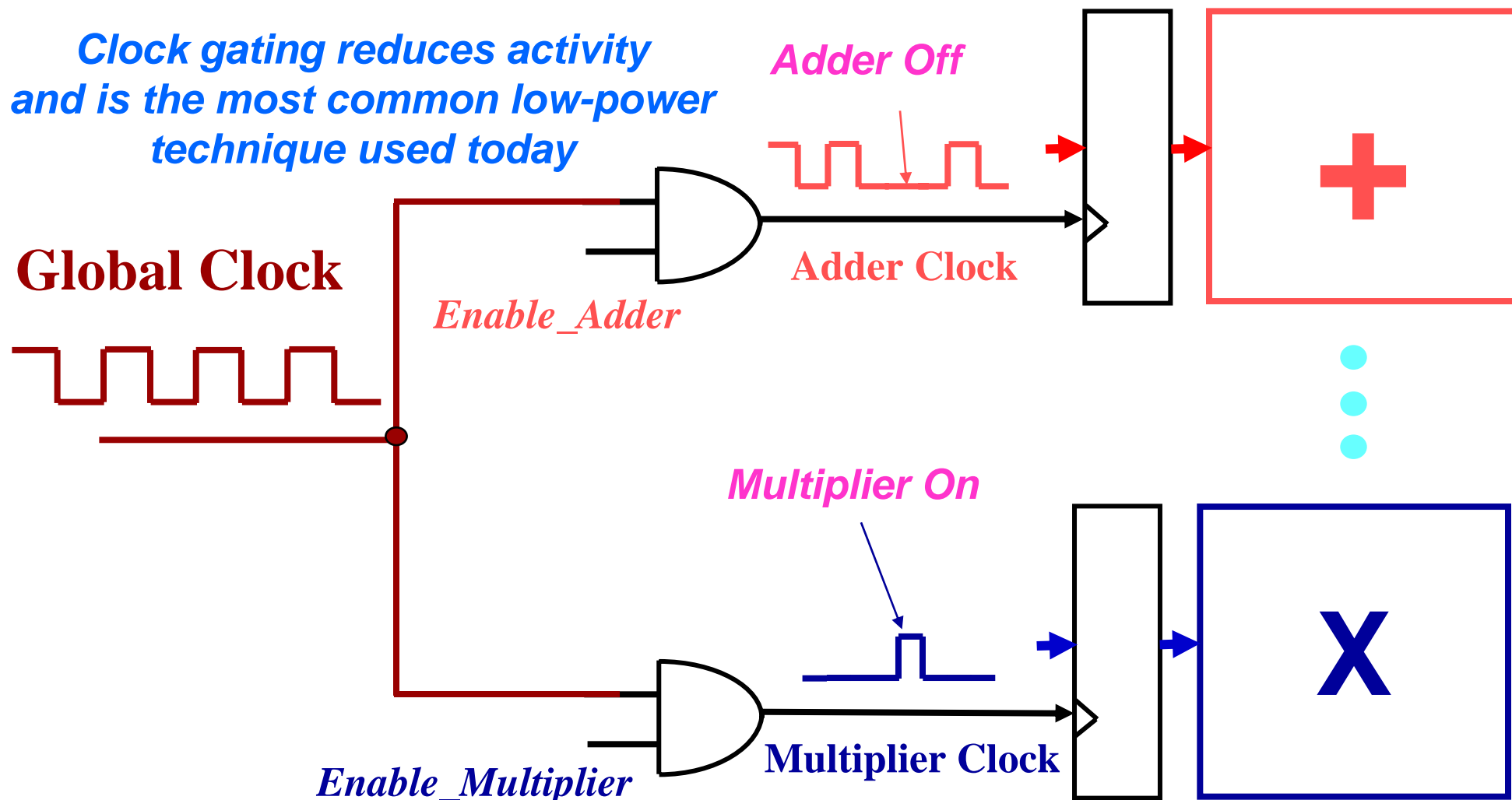 

Clock Gating Reduces Energy, does it reduce Power?





Use of Thermal Feedback

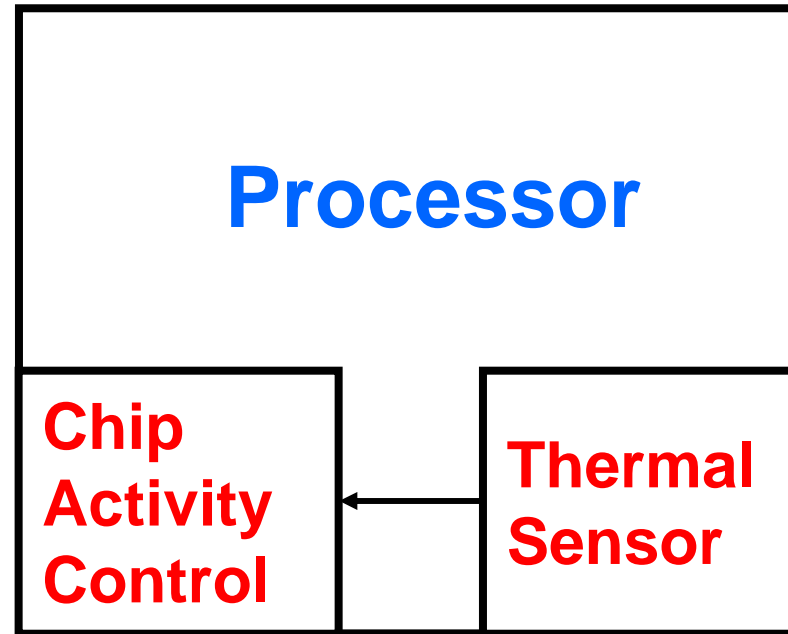

- Note that there is a difference between average and peak power
- On-chip thermal sensor (diode based), measures the silicon temperature
- If the silicon junction gets too hot, then the activity is reduced (e.g., reduce clock rate)





Power Supply Parasitics

 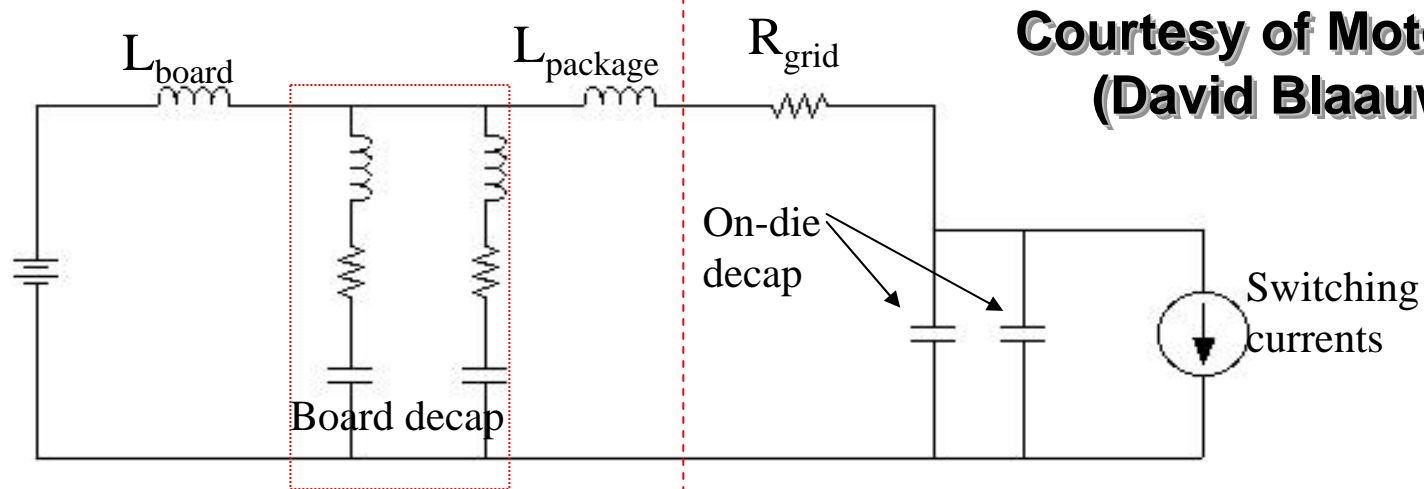

**200Mhz
Design**



Power Supply Resonance!

  





Number Representation: Two's Complement vs. Sign Magnitude



Two's complement

 


Sign-Magnitude

 

Consider a 16 bit bus where inputs toggles between +1 and -1 (i.e., a small noise input)
Which representation is more energy efficient?

Bus Coding to Reduce Activity

 


[Stan94]






Time Sharing



Parallel busses for I,Q

 


Time-shared bus for I,Q

   

Time Sharing Increases Switching Activity



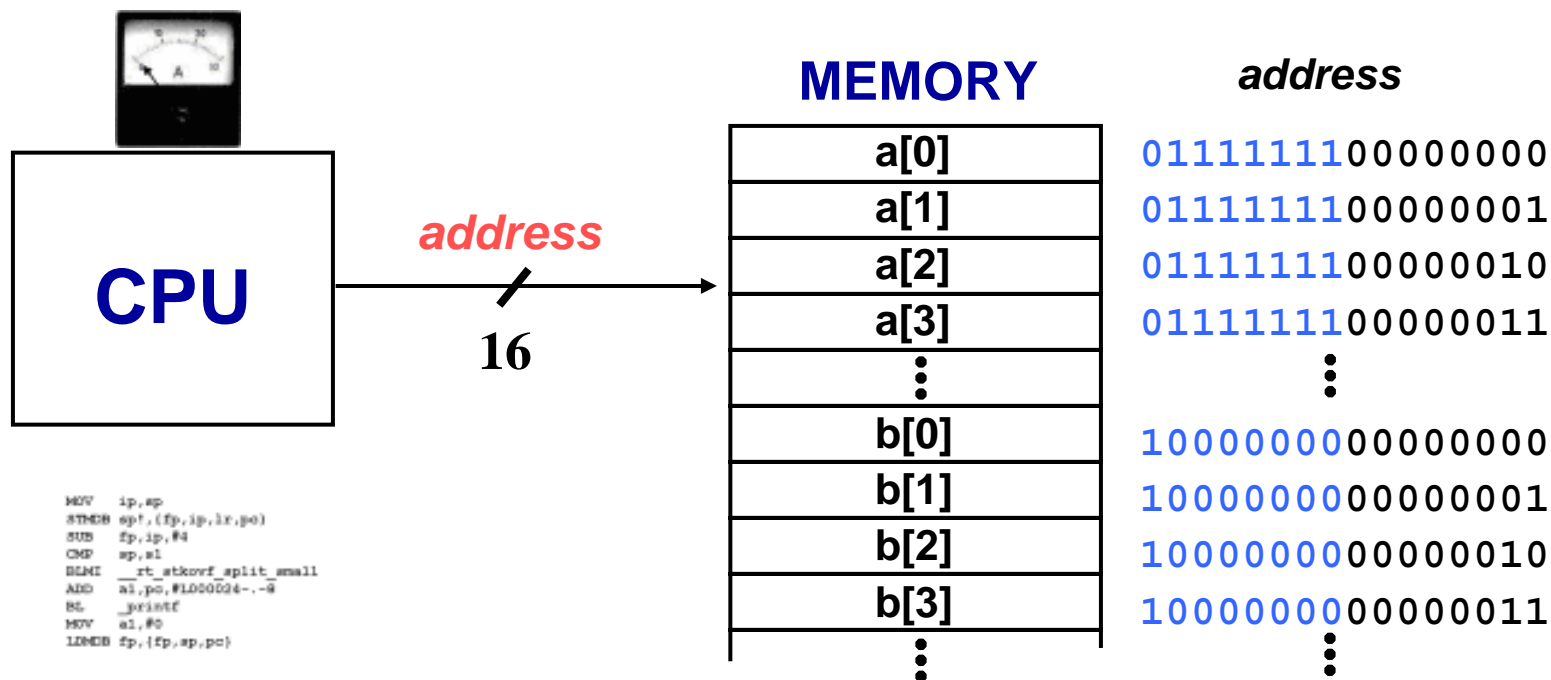Not just a 6-1 Issue: “Cool” Software ???



float a [256], b[256];
float pi= 3.14;

```

for (i = 0; i < 255; i++) {
  a[i] = sin(pi * i /256);
  b[i] = cos(pi * i /256);
}

```

512(8)+2+4+8+16+32+64+128+256
= **4607 bit transitions**

float a [256], b[256];
float pi= 3.14;

```


for (i = 0; i < 255; i++) {a[i] = sin(pi * i /256);}
for (i = 0; i < 255; i++) {b[i] = cos(pi * i /256);}

```

2(8)+2(2+4+8+16+32+64+128+256)
= **1030 transitions**



Pre-Computation

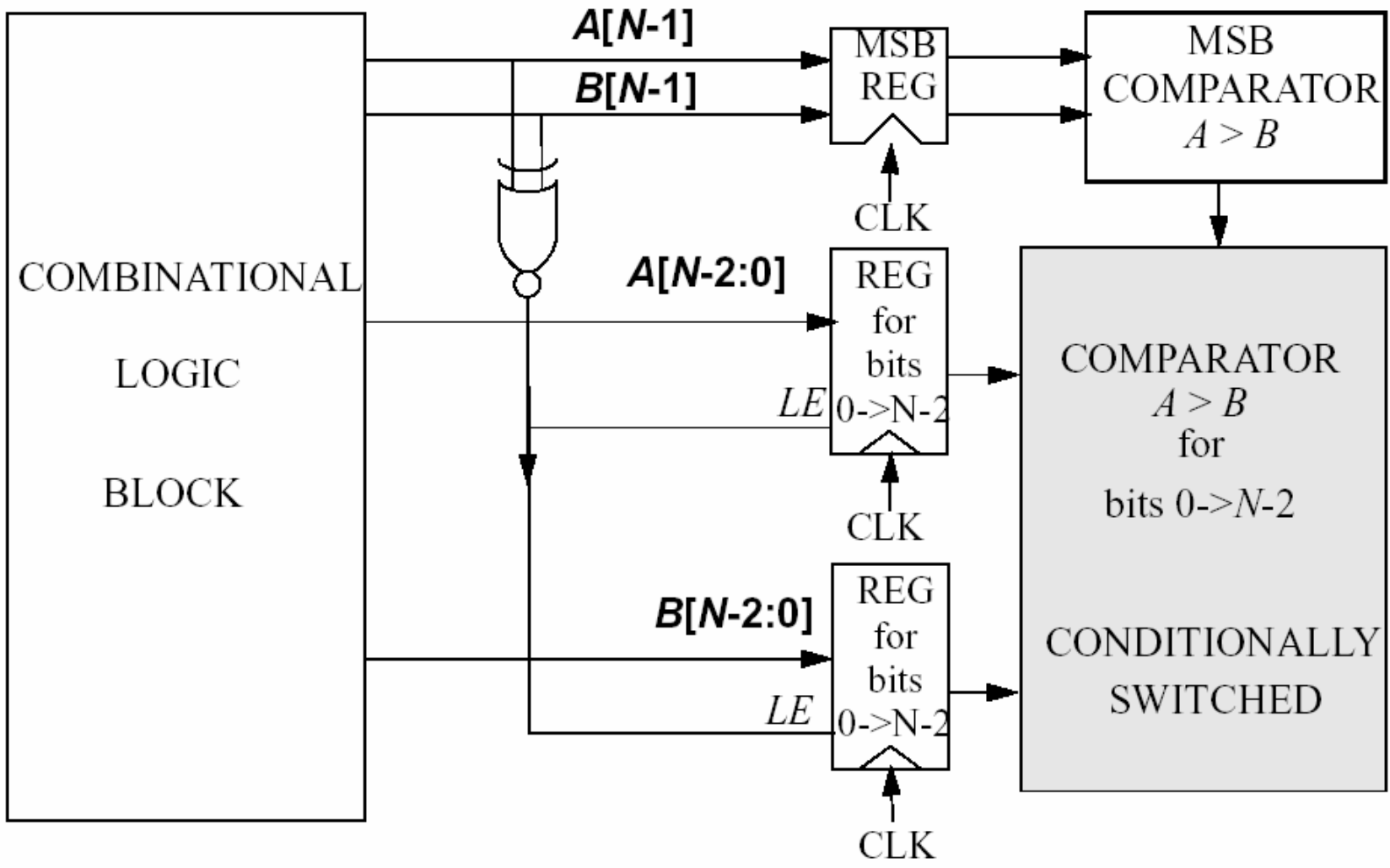


from [Alidina94]
(1994 International Workshop on Low-power Design)



Glitching Transitions




Chain Topology

 

$$(((A+B) + C)+D)$$

Tree Topology


 


$$(A+B) + (C+D)$$

- Balancing paths reduces glitching transitions
- For 4 inputs, 50% less transitions using a tree approach
- Structures such as multipliers have lot of glitching transitions
- Keeping logic depths short (e.g., pipelining) reduces glitching



Reduce Supply Voltage : But is it Free?

  

$$Delay = \frac{C_L \cdot \Delta V}{i_D} = \frac{C_L \cdot \frac{V_{DD}}{2}}{\frac{k}{2} (V_{DD} - V_T)^2} \propto \frac{V_{DD}}{(V_{DD} - V_T)^2} \approx \frac{1}{V_{DD}}$$

V_{DD} from 2V to 1V, **energy** ↓ by **x4**, **delay** ↑ **x2**




Voltage Scaling Using Parallelism



$f = 1\text{GHz}$
 $V_{DD} = 2\text{V}$


IN

 

OUT


$$P_{\text{serial}} = C_{\text{mult}} 2^2 f$$

 $f = 500\text{MHz}$ IN
 $V_{DD} = 1\text{V}$



IN

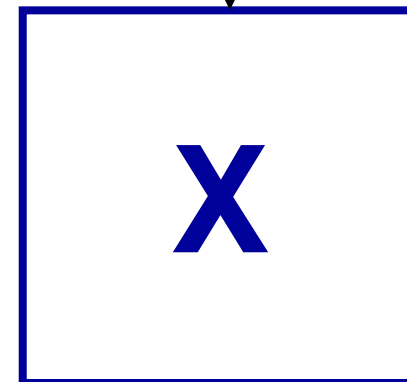$f = 500\text{MHz}$
 $V_{DD} = 1\text{V}$



SELECT

OUT

$$P_{\text{parallel}} = (2C_{\text{mult}} 1^2 f / 2) = P_{\text{serial}} / 4$$


Trade Area for Low Power




Algorithmic Workload





Compare Current Image...

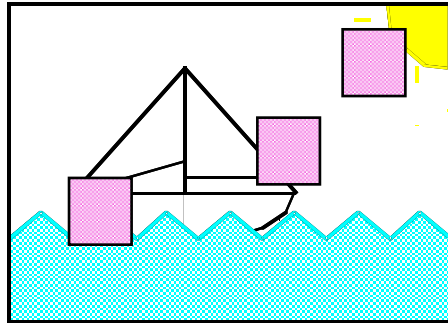

Receiver just updates

 

...to Previous Image

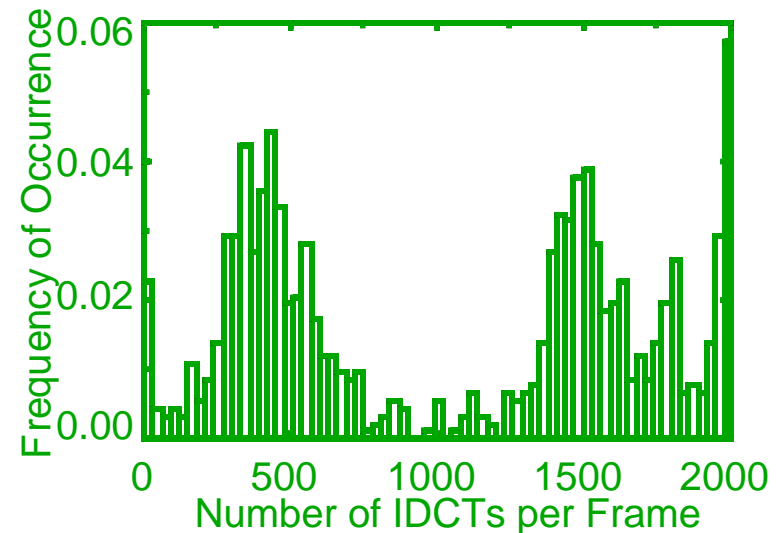 

***Exploit Time Varying Algorithmic Workload
To Vary the Power Supply Voltage***



Dynamic Voltage Scaling



Fixed Power Supply




$$E_{\text{FIXED}} = \frac{1}{2} C V_{\text{DD}}^2$$

Variable Power Supply



$$E_{\text{VARIABLE}} = \frac{1}{2} C (V_{\text{DD}}/2)^2 = E_{\text{FIXED}} / 4$$

 



[Gutnik97]



DVS on a Processor



 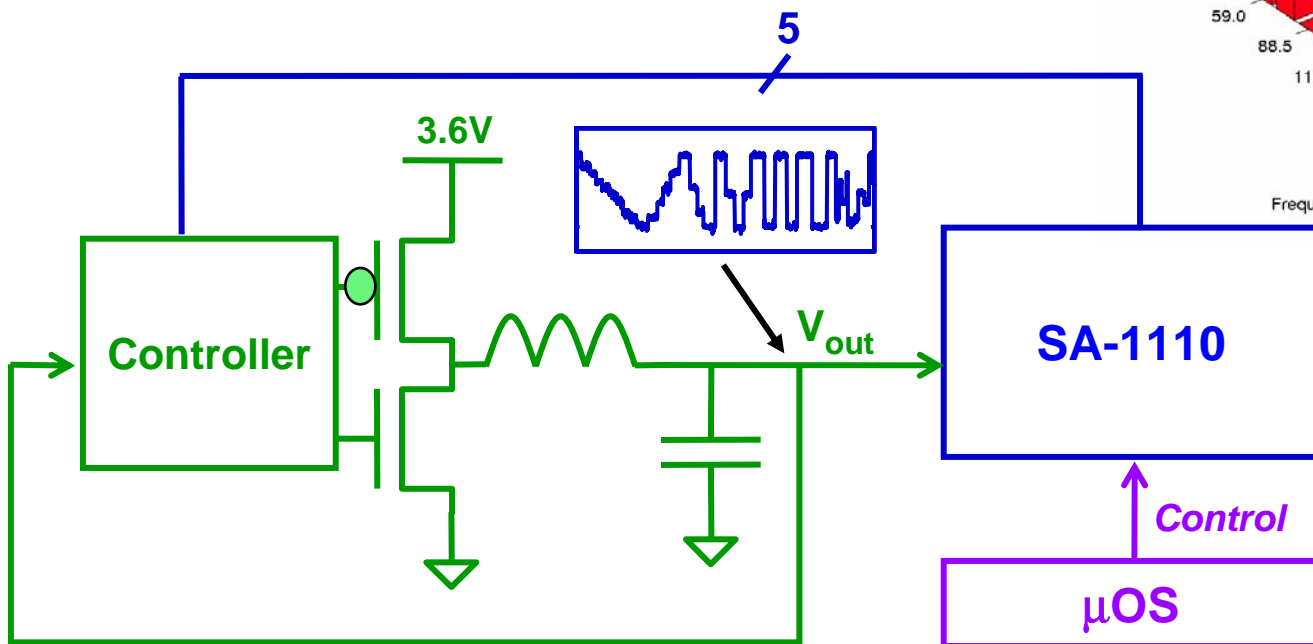Digitally adjustable DC-DC converter powers SA-1110 core



μOS selects appropriate clock frequency based on workload and latency constraints




Software Voltage Demo



- User adjusts number of filter taps
- Frequency/Voltage adjusted appropriately (via eCOS based μ OS)

Frequency /
Voltage

Workload
(filter taps)

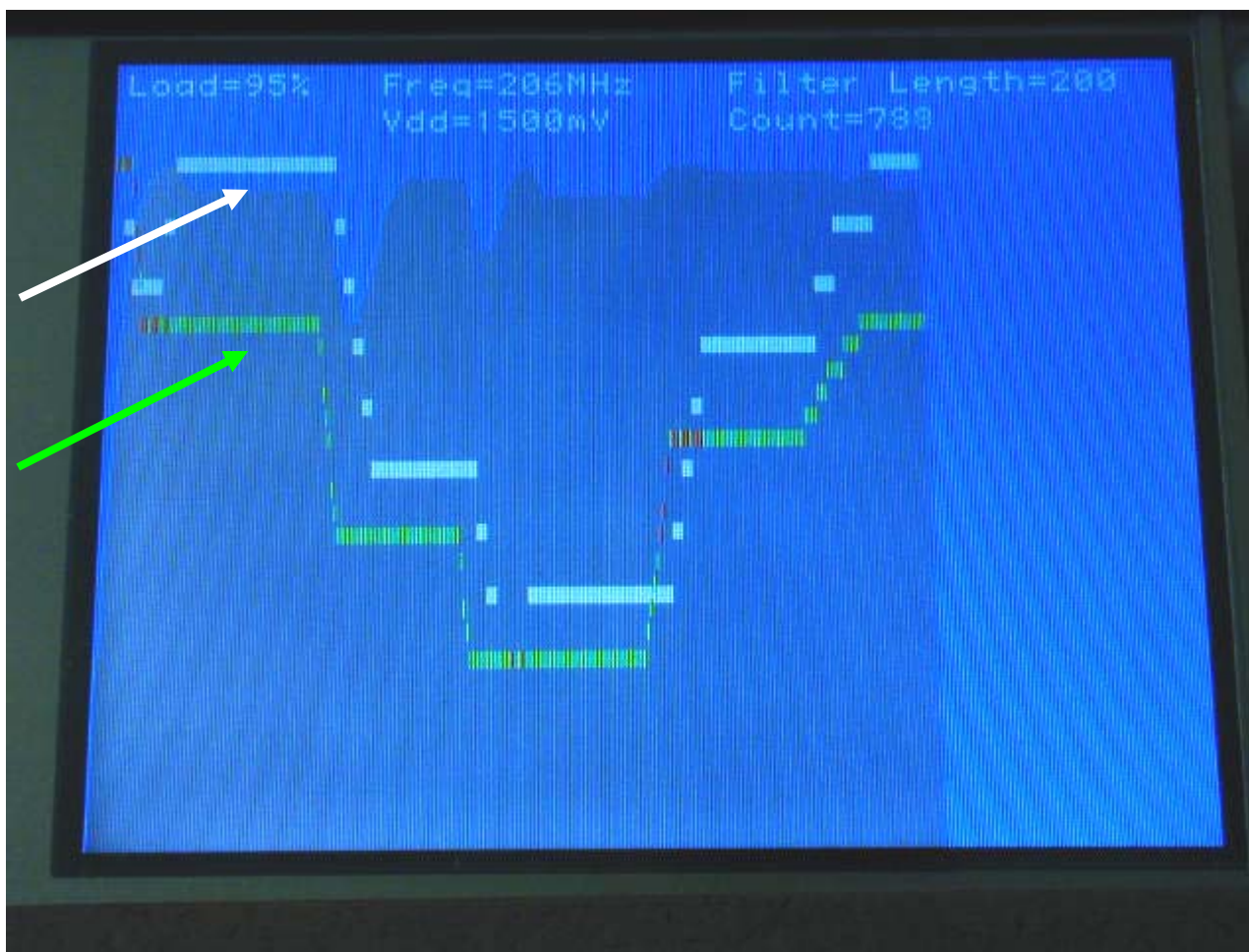




Energy Scavenging



MEMS Generator

 

Jose Mur Miranda/
Jeff Lang

Vibration-to-Electric
Conversion

~ 10 μ W

Power Harvesting Shoes



Joe Paradiso
(Media Lab)

After 3-6 steps, it provides 3 mA
for 0.5 sec

~10mW