




L2: Combinational Logic Design (Construction and Boolean Algebra)



(Most) Lecture material derived from R. Katz, “*Contemporary Logic Design*”, Addison Wesley Publishing Company, Reading, MA, 1993.





The Inverter

 

Truth Table

IN	OUT
0	1
1	0

  






$$NM_L = V_{IL} - V_{OL}$$

$$NM_H = V_{OH} - V_{IH}$$

- Large noise margins protect against various noise sources






TTL Logic Style (1970's-early 80's)

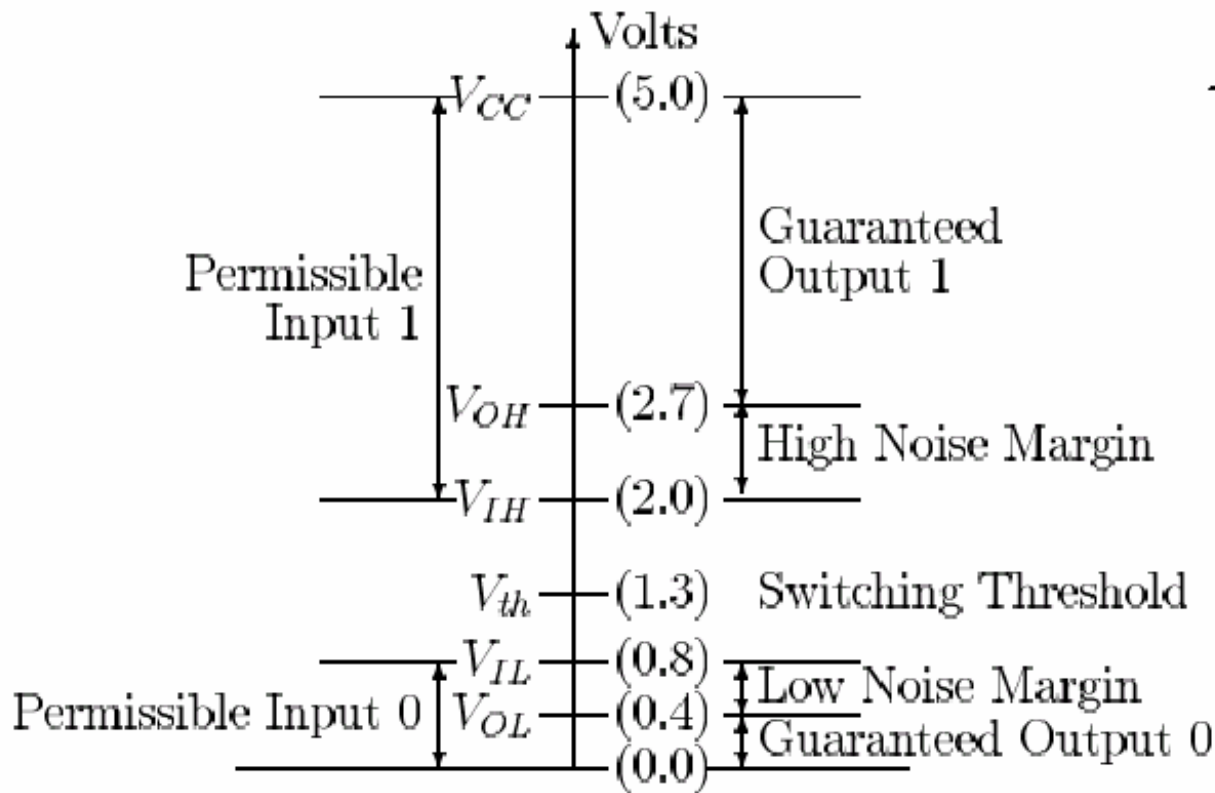    

74LS04
(courtesy TI)




MOS Technology: The NMOS Switch

   


Switch Model

OFF

 



ON

 

NMOS ON when Switch Input is High




PMOS: The Complementary Switch

  


Switch Model

OFF

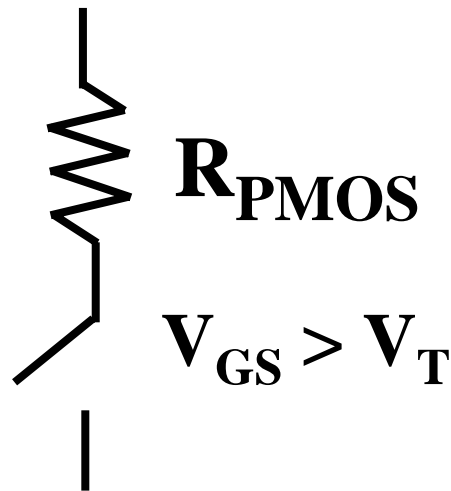

ON

 



PMOS ON when Switch Input is Low



The CMOS Inverter



Switch Model

 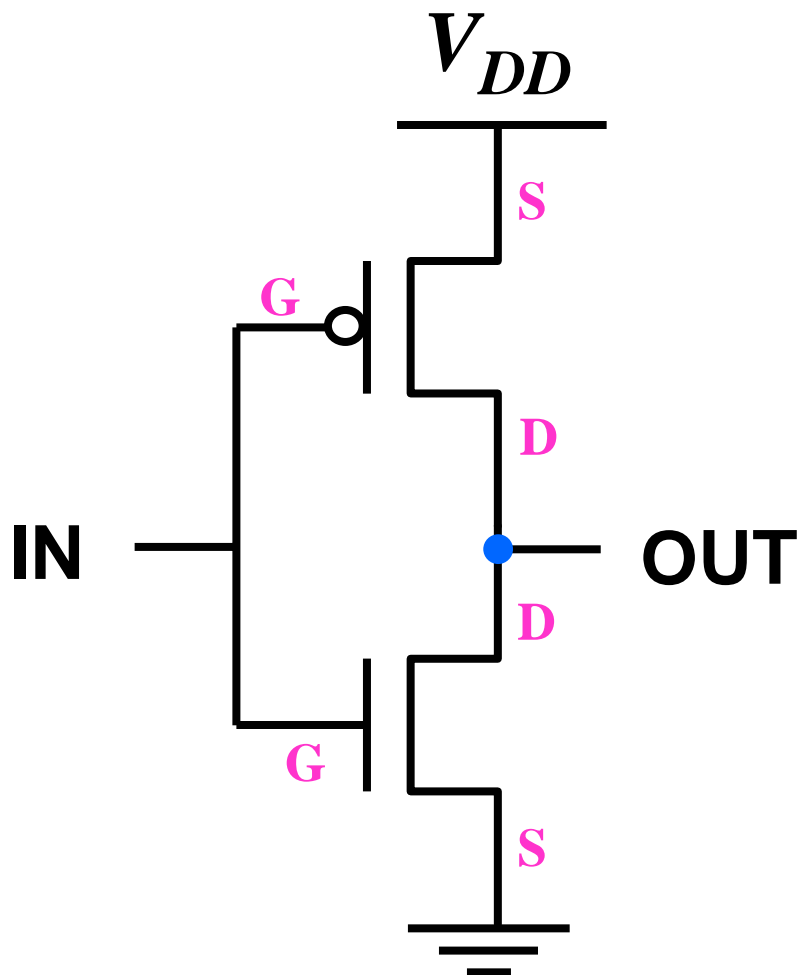


Rail-to-rail Swing in CMOS



Possible Function of Two Inputs



 There are 16 possible functions of 2 input variables:



X	Y	16 possible functions (F_0 – F_{15})																
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	1

Labels for the 16 functions (from left to right):
 0, X AND Y, X, Y, X XOR Y, X OR Y, X NOR Y, NOT (X OR Y), X = Y, NOT Y, NOT X, X NAND Y, NOT (X AND Y), 1

In general, there are $2^{(2^n)}$ functions of n inputs



Common Logic Gates




Gate

Symbol

Truth-Table

Expression


NAND

 

X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

$$Z = \overline{X \cdot Y}$$


AND

 

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

$$Z = X \cdot Y$$


NOR

 

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0

$$Z = \overline{X + Y}$$

OR

 

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1


$$Z = X + Y$$



Exclusive (N)OR Gate




XOR
 $(X \oplus Y)$

 

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0

$Z = X \bar{Y} + \bar{X} Y$
X or Y but not both
("inequality", "difference")

XNOR
 $\overline{(X \oplus Y)}$

 



X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	1

$Z = \bar{X} \bar{Y} + X Y$
X and Y the same
("equality")

Widely used in arithmetic structures such as adders and multipliers




Generic CMOS Recipe

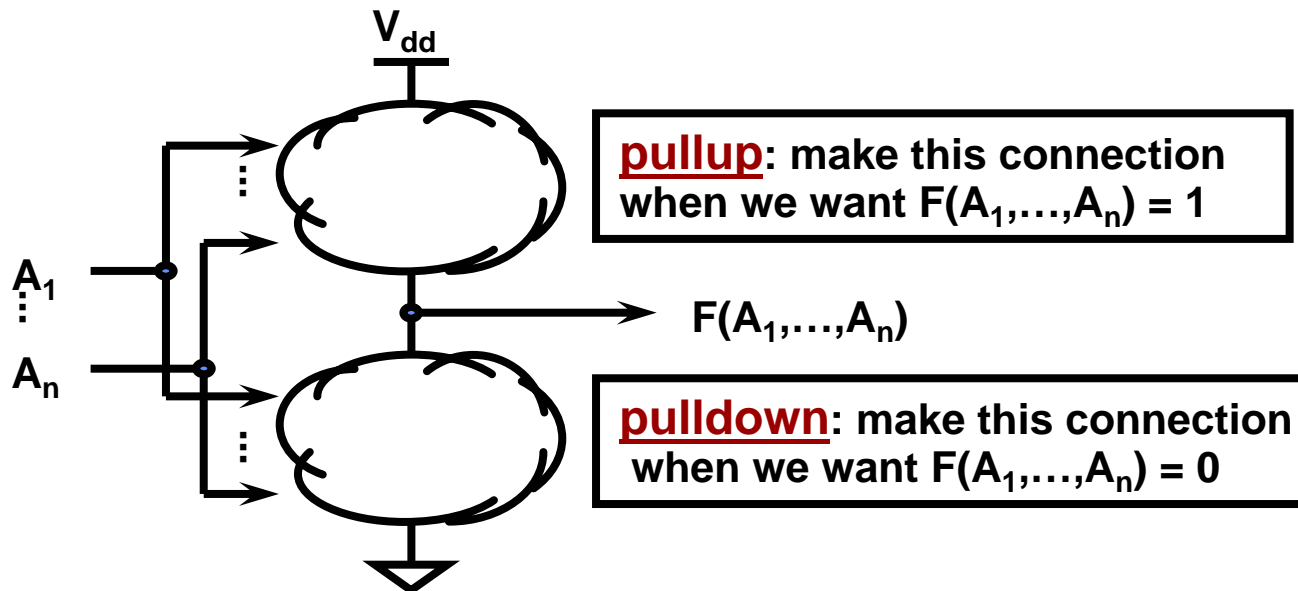 

Note: **CMOS gates result in inverting functions!**

(easier to build NAND vs. AND)

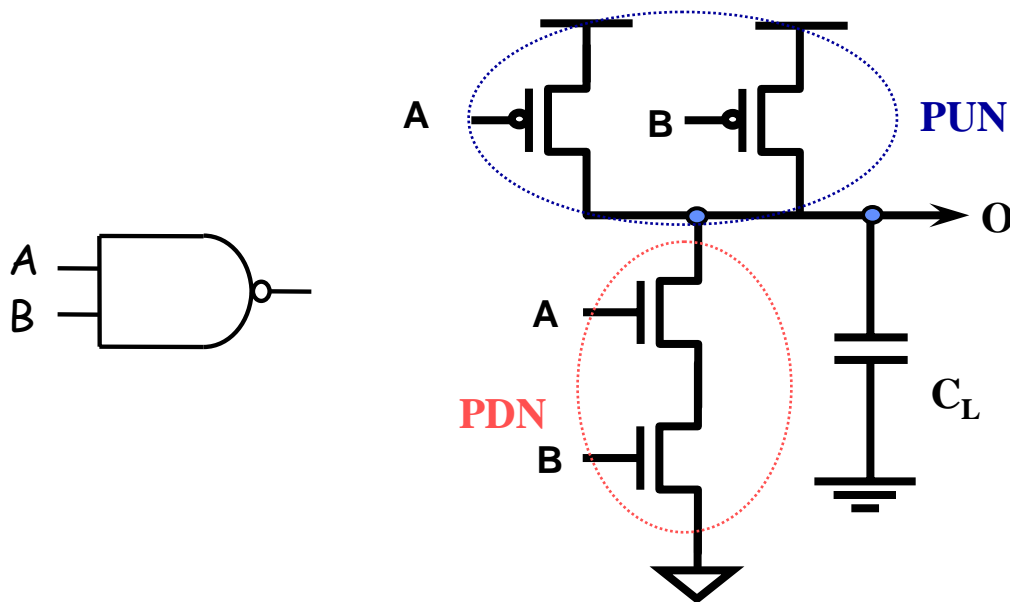

A	B	PDN	PUN	O
0	0	Off	On	1
0	1	Off	On	1
1	0	Off	On	1
1	1	On	Off	0

How do you build a 2-input NOR Gate?



Theorems of Boolean Algebra (I)



■ Elementary

1. $X + 0 = X$

2. $X + 1 = 1$

3. $X + X = X$

4. $\overline{\overline{X}} = X$

5. $X + \overline{X} = 1$

1D. $X \cdot 1 = X$

2D. $X \cdot 0 = 0$

3D. $X \cdot X = X$

5D. $X \cdot \overline{X} = 0$

■ Commutativity:

6. $X + Y = Y + X$

6D. $X \cdot Y = Y \cdot X$

■ Associativity:

7. $(X + Y) + Z = X + (Y + Z)$

7D. $(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$

■ Distributivity:

8. $X \cdot (Y + Z) = (X \cdot Y) + (X \cdot Z)$

8D. $X + (Y \cdot Z) = (X + Y) \cdot (X + Z)$

■ Uniting:

9. $X \cdot Y + X \cdot \overline{Y} = X$

9D. $(X + Y) \cdot (X + \overline{Y}) = X$

■ Absorption:

10. $X + X \cdot Y = X$

10D. $X \cdot (X + Y) = X$

11. $(X + \overline{Y}) \cdot Y = X \cdot Y$

11D. $(X \cdot \overline{Y}) + Y = X + Y$



Theorems of Boolean Algebra (II)



■ Factoring:

$$12. (X \cdot Y) + (X \cdot Z) = X \cdot (Y + Z)$$

$$12D. (X + Y) \cdot (X + Z) = X + (Y \cdot Z)$$

■ Consensus:

$$13. (X \cdot Y) + (Y \cdot Z) + (\bar{X} \cdot Z) = X \cdot Y + \bar{X} \cdot Z$$

$$13D. (X + Y) \cdot (Y + Z) \cdot (\bar{X} + Z) = (X + Y) \cdot (\bar{X} + Z)$$

■ De Morgan's:

$$14. \overline{(X + Y + \dots)} = \bar{X} \cdot \bar{Y} \cdot \dots$$

$$14D. \overline{(X \cdot Y \cdot \dots)} = \bar{X} + \bar{Y} + \dots$$

■ Generalized De Morgan's:

$$15. \overline{f(X_1, X_2, \dots, X_n, 0, 1, +, \cdot)} = f(\bar{X}_1, \bar{X}_2, \dots, \bar{X}_n, 1, 0, \cdot, +)$$

■ Duality

□ Dual of a Boolean expression is derived by replacing \cdot by $+$, $+$ by \cdot , 0 by 1, and 1 by 0, and leaving variables unchanged

$$\square f(X_1, X_2, \dots, X_n, 0, 1, +, \cdot) \Leftrightarrow f(X_1, X_2, \dots, X_n, 1, 0, \cdot, +)$$




Simple Example: One Bit Adder



■ 1-bit binary adder

 - inputs: A, B, Carry-in
- outputs: Sum, Carry-out



A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Sum-of-Products Canonical Form

$$S = \bar{A} \bar{B} C_{in} + \bar{A} B \bar{C}_{in} + A \bar{B} \bar{C}_{in} + A B C_{in}$$

$$C_{out} = \bar{A} B C_{in} + A \bar{B} C_{in} + A B \bar{C}_{in} + A B C_{in}$$

■ Product term (or minterm)

- ANDed product of literals – input combination for which output is true
- Each variable appears exactly once, in true or inverted form (but not both)



Simplify Boolean Expressions




$$\begin{aligned} \text{Cout} &= \overline{A} B C_{in} + A \overline{B} C_{in} + A B \overline{C_{in}} + A B C_{in} \\ &= \overline{A} B C_{in} + A B C_{in} + A \overline{B} C_{in} + A B C_{in} + A B \overline{C_{in}} + A B C_{in} \\ &= (\overline{A} + A) B C_{in} + A (\overline{B} + B) C_{in} + A B (\overline{C_{in}} + C_{in}) \\ &= B C_{in} + A C_{in} + A B \\ &= (B + A) C_{in} + A B \end{aligned}$$

$$\begin{aligned} S &= \overline{A} \overline{B} C_{in} + \overline{A} B \overline{C_{in}} + A \overline{B} \overline{C_{in}} + A B C_{in} \\ &= (\overline{A} \overline{B} + A B) C_{in} + (A \overline{B} + \overline{A} B) \overline{C_{in}} \\ &= \overline{(A \oplus B)} C_{in} + (A \oplus B) \overline{C_{in}} \\ &= A \oplus B \oplus C_{in} \end{aligned}$$



Sum-of-Products & Product-of-Sum

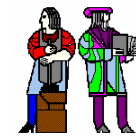

- Product term** (or minterm): ANDed product of literals – input combination for which output is true

A	B	C	minterms	
0	0	0	$\overline{A} \overline{B} \overline{C}$	m0
0	0	1	$\overline{A} \overline{B} C$	m1
0	1	0	$\overline{A} B \overline{C}$	m2
0	1	1	$\overline{A} B C$	m3
1	0	0	$A \overline{B} \overline{C}$	m4
1	0	1	$A \overline{B} C$	m5
1	1	0	$A B \overline{C}$	m6
1	1	1	$A B C$	m7

short-hand notation form in terms of 3 variables

F in canonical form:

$$F(A, B, C) = \sum m(1,3,5,6,7)$$

$$= m1 + m3 + m5 + m6 + m7$$

$$F = \overline{A} \overline{B} C + \overline{A} B \overline{C} + A \overline{B} C + A B \overline{C} + ABC$$

canonical form \neq minimal form

$$F(A, B, C) = \overline{A} \overline{B} C + \overline{A} B \overline{C} + A \overline{B} C + ABC + ABC \overline{C}$$

$$= (\overline{A} \overline{B} + \overline{A} B + A \overline{B} + AB)C + ABC \overline{C}$$

$$= ((\overline{A} + A)(\overline{B} + B))C + ABC \overline{C}$$

$$= C + ABC \overline{C} = ABC \overline{C} + C = AB + C$$

- Sum term** (or maxterm) - ORed sum of literals – input combination for which output is false

A	B	C	maxterms	
0	0	0	$A + B + C$	M0
0	0	1	$A + B + \overline{C}$	M1
0	1	0	$A + \overline{B} + C$	M2
0	1	1	$A + \overline{B} + \overline{C}$	M3
1	0	0	$\overline{A} + B + C$	M4
1	0	1	$\overline{A} + B + \overline{C}$	M5
1	1	0	$\overline{A} + \overline{B} + C$	M6
1	1	1	$\overline{A} + \overline{B} + \overline{C}$	M7

short-hand notation for maxterms of 3 variables

F in canonical form:

$$F(A, B, C) = \prod M(0,2,4)$$

$$= M0 \cdot M2 \cdot M4$$

$$= (A + B + C) (A + \overline{B} + C) (\overline{A} + B + C)$$

canonical form \neq minimal form

$$F(A, B, C) = (A + B + C) (A + \overline{B} + C) (\overline{A} + B + C)$$

$$= (A + B + C) (A + \overline{B} + C)$$

$$(A + B + C) (\overline{A} + B + C)$$

$$= (A + C) (B + C)$$



Mapping Between Forms



1. **Minterm to Maxterm conversion:**
rewrite minterm shorthand using maxterm shorthand
replace minterm indices with the indices not already used

$$\text{E.g., } F(A,B,C) = \Sigma m(3,4,5,6,7) = \Pi M(0,1,2)$$

2. **Maxterm to Minterm conversion:**
rewrite maxterm shorthand using minterm shorthand
replace maxterm indices with the indices not already used

$$\text{E.g., } F(A,B,C) = \Pi M(0,1,2) = \Sigma m(3,4,5,6,7)$$

3. **Minterm expansion of F to Minterm expansion of F':**
in minterm shorthand form, list the indices not already used in F

$$\begin{array}{lcl} \text{E.g., } F(A,B,C) = \Sigma m(3,4,5,6,7) & \longrightarrow & F'(A,B,C) = \Sigma m(0,1,2) \\ & \longrightarrow & = \Pi M(3,4,5,6,7) \\ & & = \Pi M(0,1,2) \end{array}$$

4. **Minterm expansion of F to Maxterm expansion of F':**
rewrite in Maxterm form, using the same indices as F


$$\begin{array}{lcl} \text{E.g., } F(A,B,C) = \Sigma m(3,4,5,6,7) & \longrightarrow & F'(A,B,C) = \Pi M(3,4,5,6,7) \\ & \longrightarrow & = \Sigma m(0,1,2) \\ & & = \Pi M(0,1,2) \end{array}$$



The Uniting Theorem



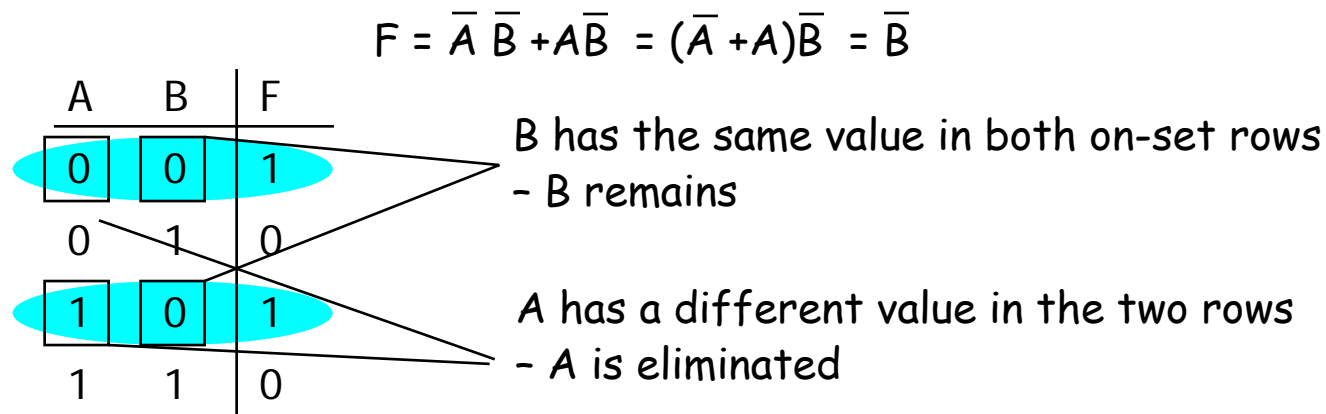- Key tool to simplification: $A(\bar{B} + B) = A$
- Essence of simplification of two-level logic
 - Find two element subsets of the ON-set where only one variable changes its value – this single varying variable can be eliminated and a single product term used to represent both elements









Boolean Cubes




    - Just another way to represent truth table
- Visual technique for identifying when the uniting theorem can be applied
- n input variables = n -dimensional "cube"






Mapping truth tables onto Boolean cubes

 

■ Uniting theorem

A	B	F
0	0	1
0	1	0
1	0	1
1	1	0

 

Circled group of the on-set is called the *adjacency plane*. Each adjacency plane corresponds to a product term.

ON-set = solid nodes
OFF-set = empty nodes


A varies within face, B does not
this face represents the literal \bar{B}

■ Three variable example: Binary full-adder carry-out logic

A	B	Cin	Cout
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$(\bar{A}+A)BCin$$

$$AB(\bar{Cin}+Cin)$$

 


$$Cout = BCin + AB + ACin$$

$$A(B+\bar{B})Cin$$

The on-set is completely covered by the combination (OR) of the subcubes of lower dimensionality - note that "111" is covered three times



Higher Dimension Cubes

 

$$F(A,B,C) = \sum m(4,5,6,7)$$

on-set forms a square
i.e., a cube of dimension 2 (2-D adjacency plane)

represents an expression in one variable
i.e., 3 dimensions - 2 dimensions

A is asserted (true) and unchanged
B and C vary

This subcube represents the literal A

- In a 3-cube (three variables):

- 0-cube, i.e., a single node, yields a term in 3 literals
- 1-cube, i.e., a line of two nodes, yields a term in 2 literals
- 2-cube, i.e., a plane of four nodes, yields a term in 1 literal
- 3-cube, i.e., a cube of eight nodes, yields a constant term "1"

- In general,

- m-subcube within an n-cube ($m < n$) yields a term with $n - m$ literals



Karnaugh Maps



- Alternative to truth-tables to help visualize adjacencies
 - Guide to applying the uniting theorem - On-set elements with only one variable changing value are adjacent unlike in a linear truth-table

	A	0	1
B	0	1	1
	1	0	0
		1	3

A	B	F
0	0	1
0	1	0
1	0	1
1	1	0

- Numbering scheme based on Gray-code

- e.g., 00, 01, 11, 10 (only a single bit changes in code for adjacent map cells)

2-variable K-map

	A	0	1
B	0	0	2
	1	1	3


3-variable K-map

	AB	00	01	11	10
C	0	0	2	6	4
	1	1	3	7	5


	AB	00	01	11	10
CD	00	0	4	12	8
	01	1	5	13	9
	11	3	7	15	11
	10	2	6	14	10



K-Map Examples

 


Cout =

 


$$F(A,B,C) = \sum m(0,4,5,7)$$

F =

 

F(A,B,C) =

 


F' simply replace 1's with 0's and vice versa

$$F'(A,B,C) = \sum m(1,2,3,6)$$

F' =




Four Variable Karnaugh Map

 

$$F(A,B,C,D) = \sum m(0,2,3,5,6,7,8,10,11,14,15)$$

$$F = C + \bar{A} B D + \bar{B} \bar{D}$$

 
Find the smallest number of the largest possible subcubes that cover the ON-set



K-map Corner Adjacency Illustrated in the 4-Cube



K-Map Example: Don't Cares

 

Don't Cares can be treated as 1's or 0's if it is advantageous to do so

AB		A			
		00	01	11	10
C	CD	00	01	11	10
	00	0	0	X	0
	01	1	1	X	1
	11	1	1	0	0
	10	0	X	0	0

$$F(A,B,C,D) = \sum m(1,3,5,7,9) + \sum d(6,12,13)$$

$$F = \bar{A} D + \bar{B} \bar{C} D \text{ w/o don't cares}$$

$$F = \bar{C} D + \bar{A} D \text{ w/ don't cares}$$

By treating this DC as a "1", a 2-cube can be formed rather than one 0-cube

In PoS form: $F = D (\bar{A} + \bar{C})$

Equivalent answer as above,
but fewer literals

AB		A			
		00	01	11	10
C	CD	00	01	11	10
	00	0	0	X	0
	01	1	1	X	1
	11	1	1	0	0
	10	0	X	0	0




Hazards




Static Hazards: Consider this function:

$$F = A * \bar{C} + B * C$$

 


		AB			
		00	01	11	10
C	0	0	0	1	1
	1	0	1	1	0

$A = B = 1$

 

Implemented with MSI gates:

 




Fixing Hazards



 The glitch is the result of timing differences in parallel data paths. It is associated with the function jumping between groupings or product terms on the K-map. To fix it, cover it up with another grouping or product term!



		AB			
		00	01	11	10
C	0	0	0	1	1
	1	0	1	1	0

$$F = A * \bar{C} + B * C + A * B$$

- In general, it is difficult to avoid hazards – need a robust design methodology to deal with hazards.