



L12: Reconfigurable Logic Architectures



Acknowledgements:

R. Katz, “*Contemporary Logic Design*”, Addison Wesley Publishing Company, Reading, MA, 1993.

Frank Honore



History of Computational Fabrics



- Discrete devices: relays, transistors (1940s-50s)
- Discrete logic gates (1950s-60s)
- Integrated circuits (1960s-70s)
 - e.g. TTL packages: Data Book for 100's of different parts
- Gate Arrays (IBM 1970s)
 - Transistors are pre-placed on the chip & Place and Route software puts the chip together automatically – only program the interconnect (mask programming)
- Software Based Schemes (1970's- present)
 - Run instructions on a general purpose core
- ASIC Design (1980's to present)
 - Turn Verilog directly into layout using a library of standard cells
 - Effective for high-volume and efficient use of silicon area
- Programmable Logic (1980's to present)
 - A chip that be reprogrammed after it has been fabricated
 - Examples: PALs, EPROM, EEPROM, PLDs, FPGAs
 - Excellent support for mapping from Verilog



Reconfigurable Logic



■ Logic blocks


- To implement combinational and sequential logic

■ Interconnect

- Wires to connect inputs and outputs to logic blocks


■ I/O blocks

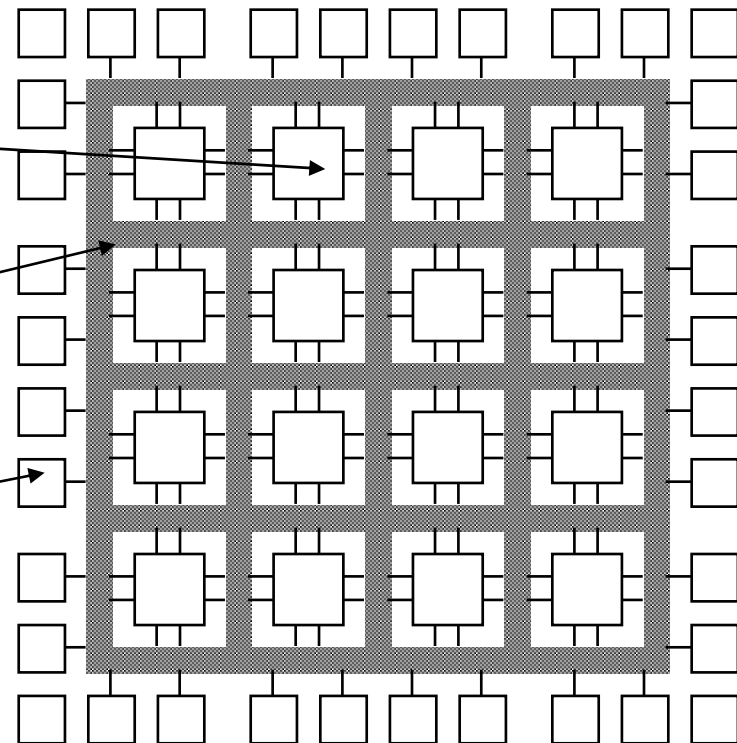- Special logic blocks at periphery of device for external connections



■ Key questions:

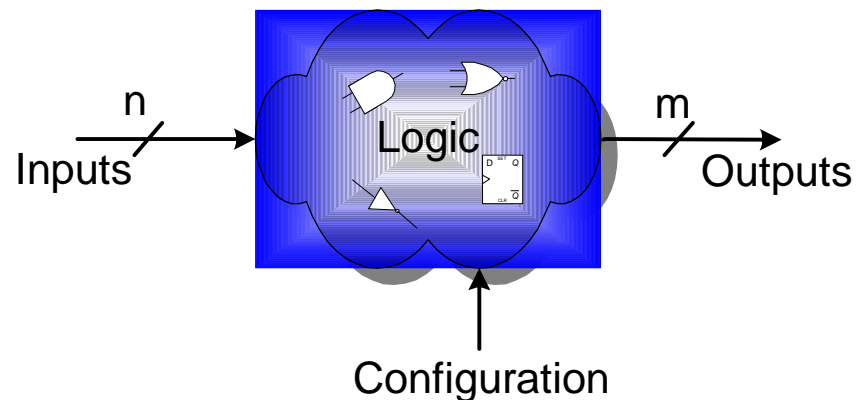- How to make logic blocks programmable? (after chip has been fabbed!)
- What should the logic granularity be?
- How to make the wires programmable? (after chip has been fabbed!)
- Specialized wiring structures for local vs. long distance routes?
- How many wires per logic block?






Programmable Array Logic (PAL)



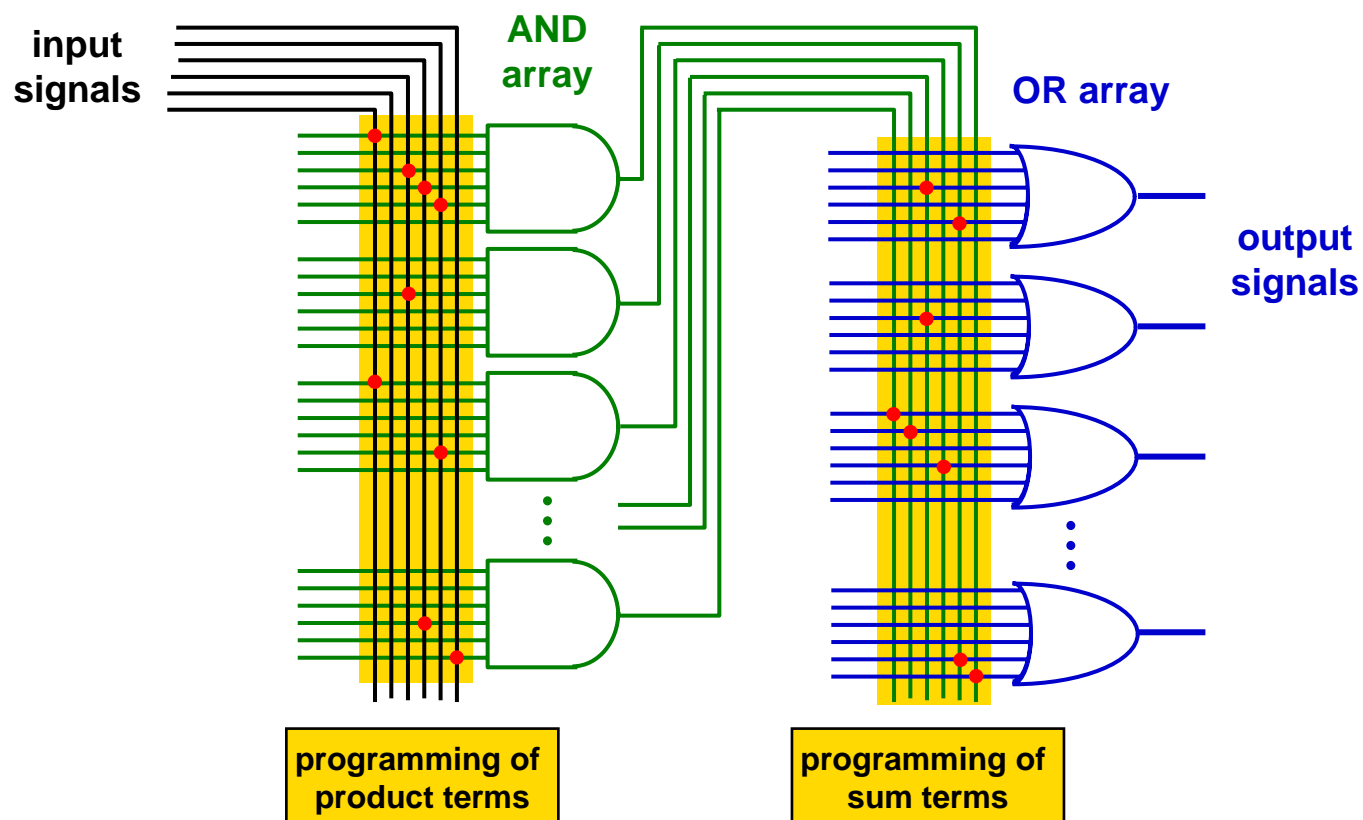- Based on the fact that any combinational logic can be realized as a sum-of-products
- PALs feature an array of AND-OR gates with programmable interconnect






Inside the 22v10 PAL



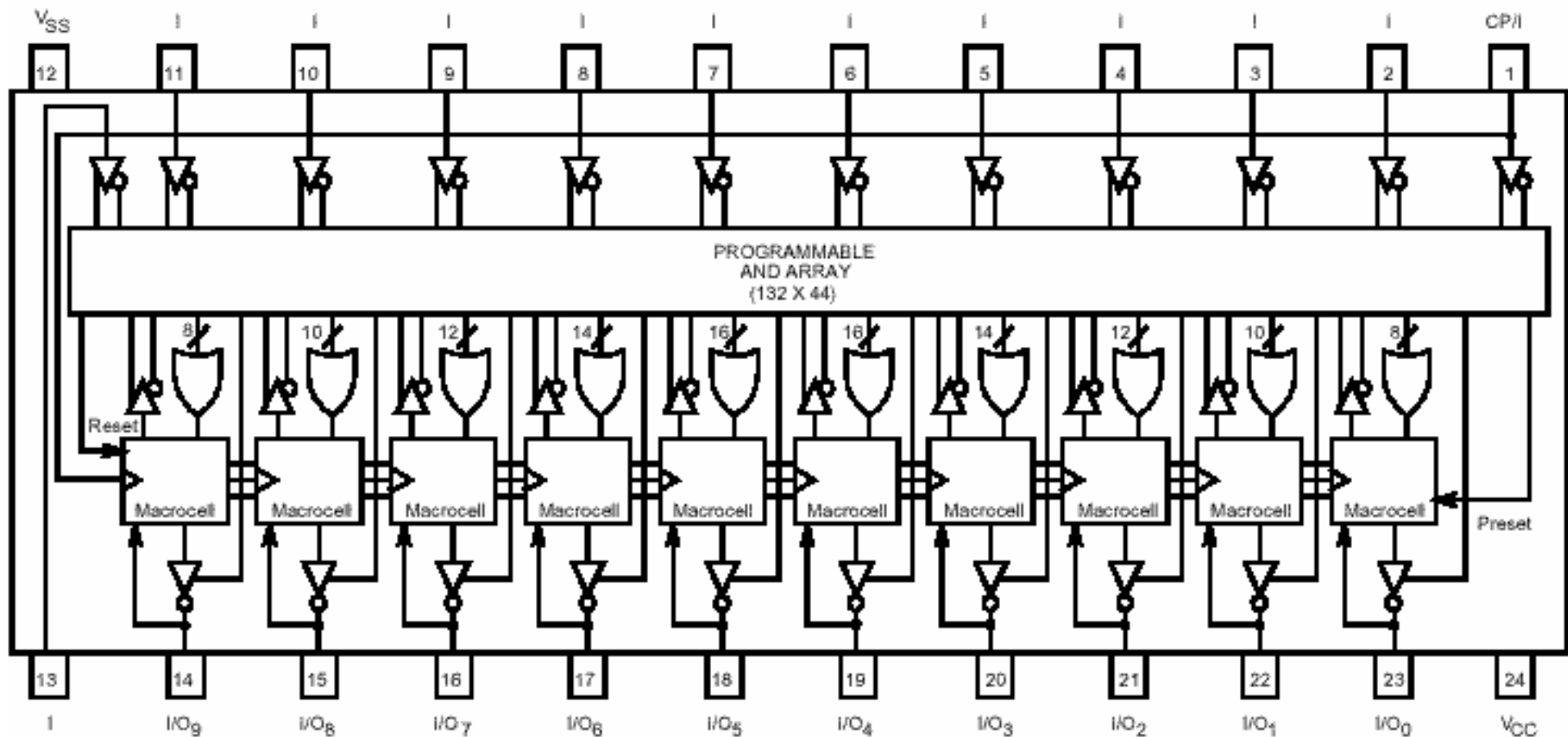- Each input pin (and its complement) sent to the AND array
- OR gates for each output can take 8-16 product terms, depending on output pin
- “Macrocell” block provides additional output flexibility...






Inside the 22v10 “Macrocell” Block







From Lattice Semiconductor

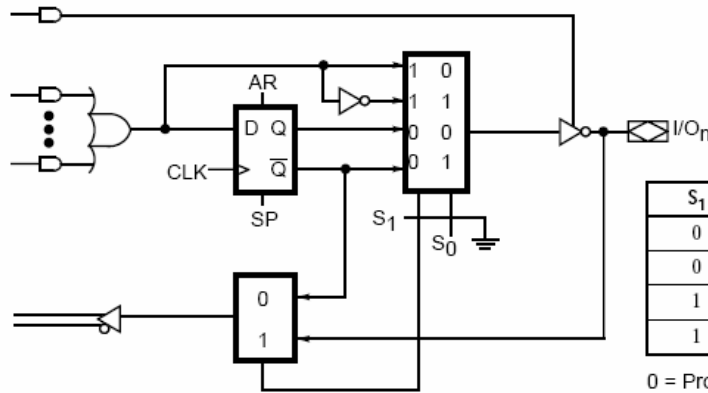

S_1	S_0	Output Configuration
0	0	Registered/Active Low
0	1	Registered/Active High
1	0	Combinational/active low
1	1	Combinational/active high

0 = Programmed EE bit
1 = Erased (charged) EE bit

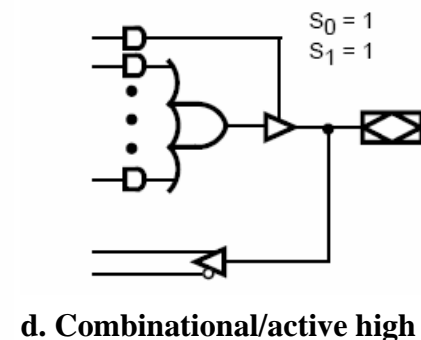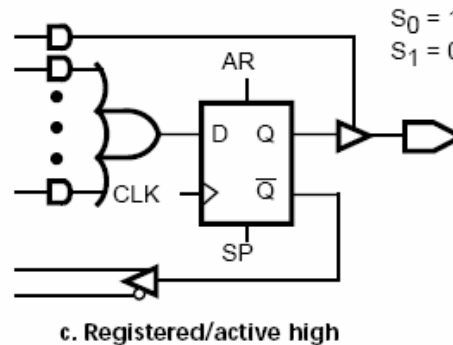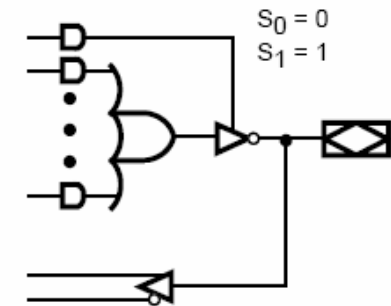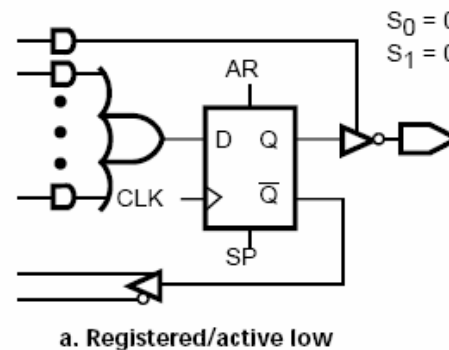- Outputs may be registered or combinational, positive or inverted
- Registered output may be fed back to AND array for FSMs, etc.






Cypress PAL CE22V10




Functional Logic Diagram for PALCE22V10

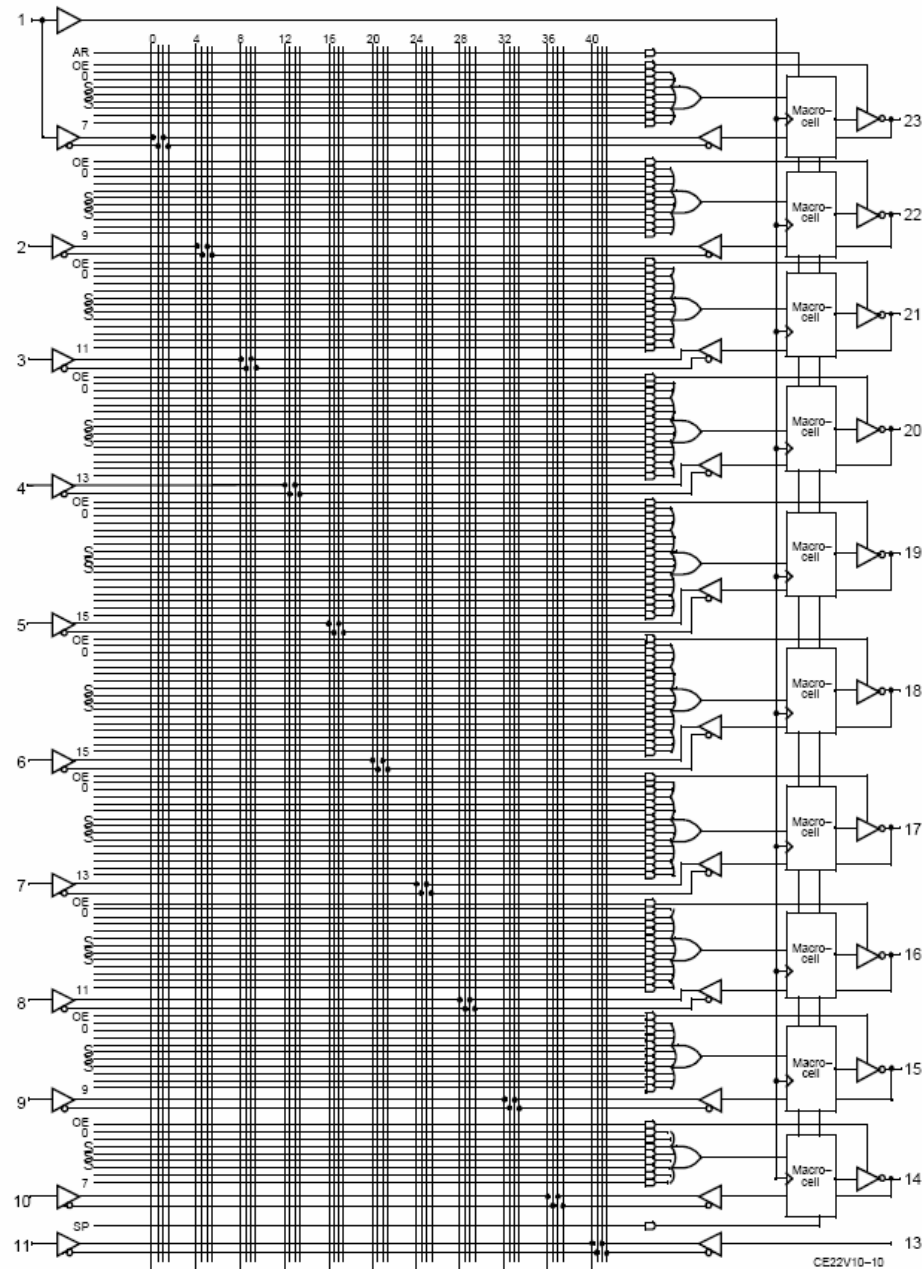



Anti-Fuse-Based Approach (Actel)

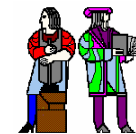


Rows of programmable
logic building blocks


+

rows of interconnect

**Anti-fuse Technology:
Program Once**

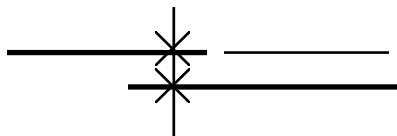

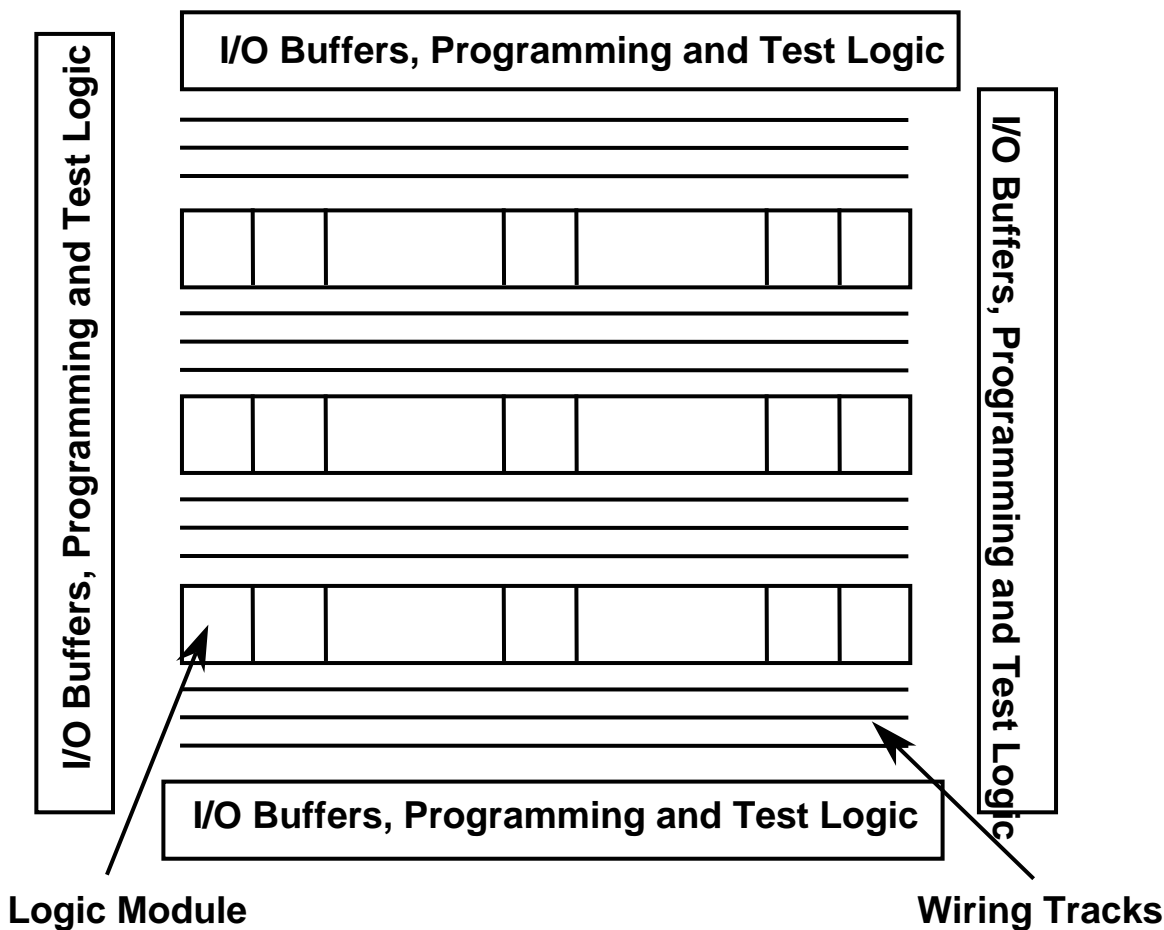Use Anti-fuses to build
up long wiring runs from
short segments



8 input, single output combinational logic blocks


FFs constructed from discrete cross coupled gates






Actel Logic Module



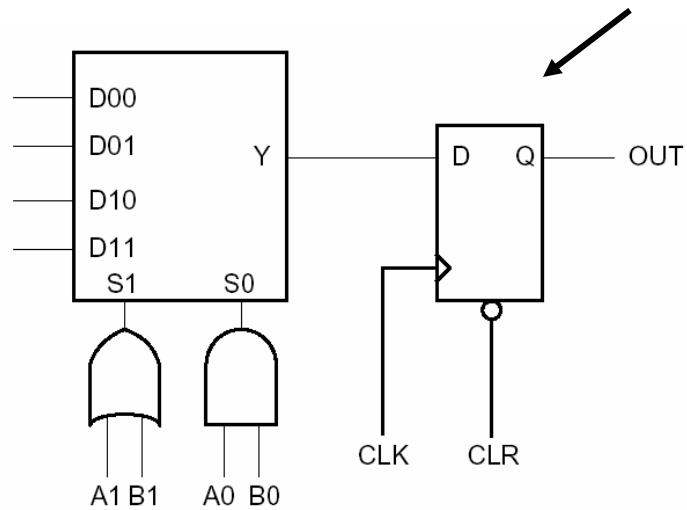
Combinational block does not have the output FF



Example Gate Mapping

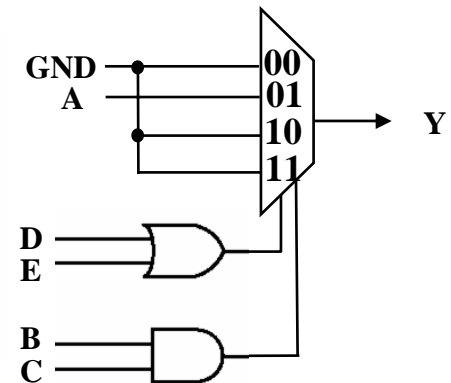
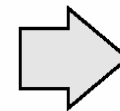
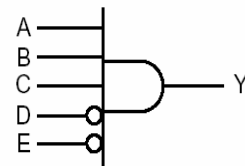


S-R Flip-Flop

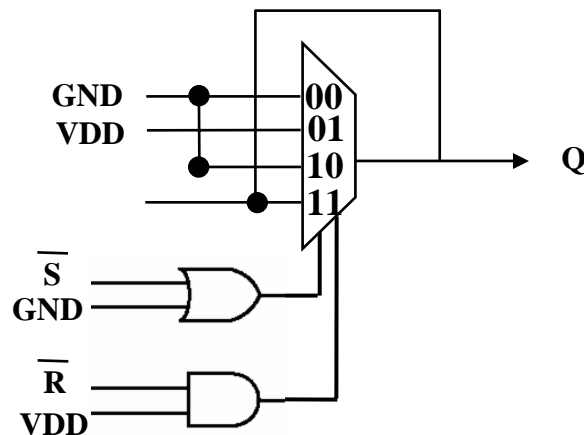





Actel Routing & Programming

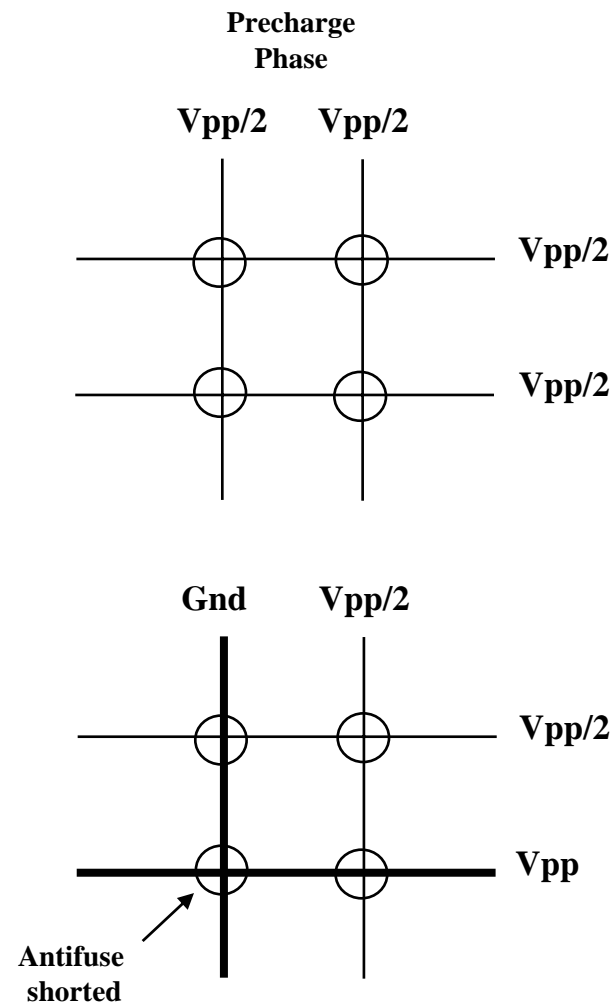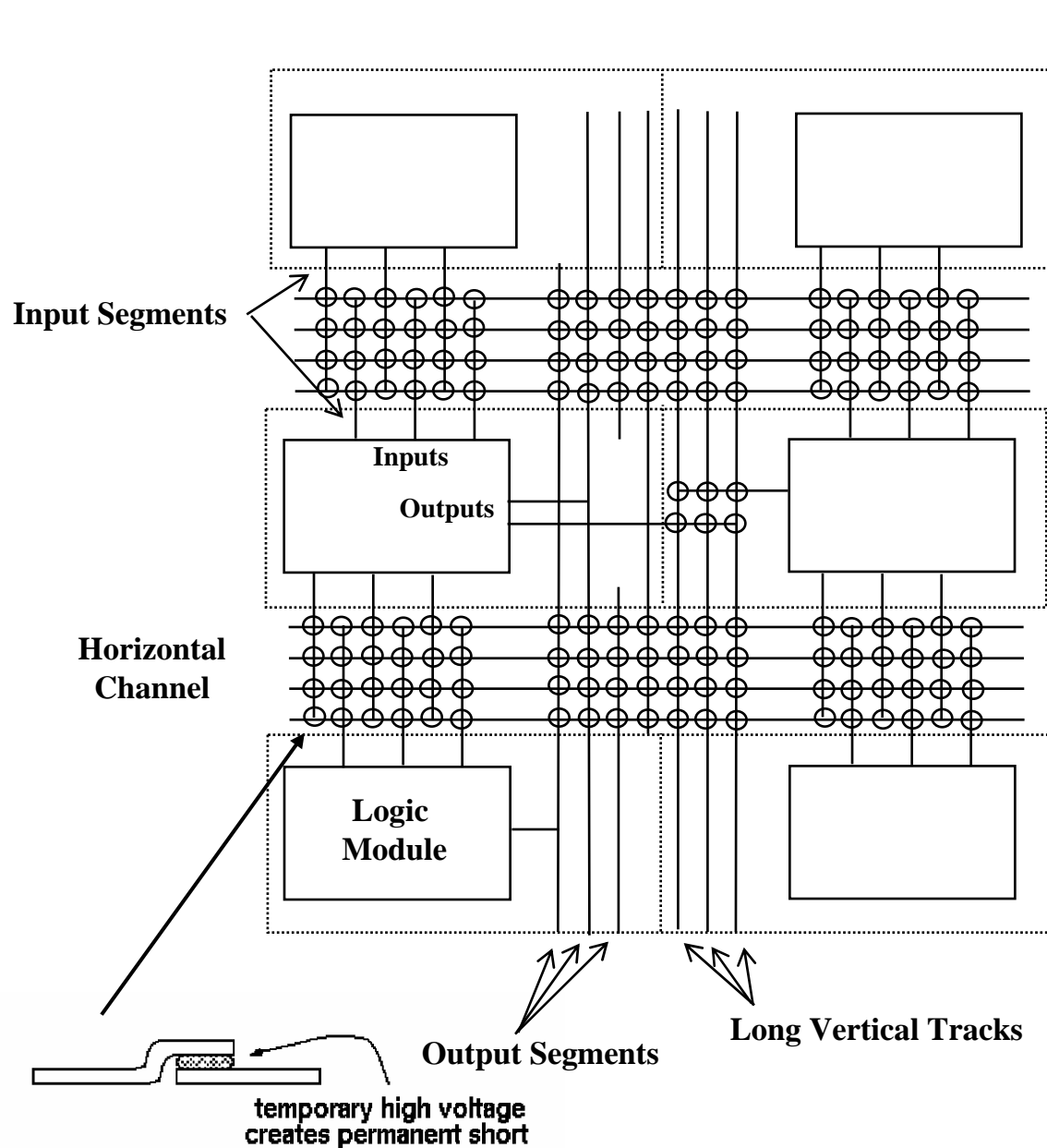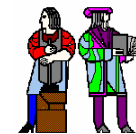

Programming an Antifuse




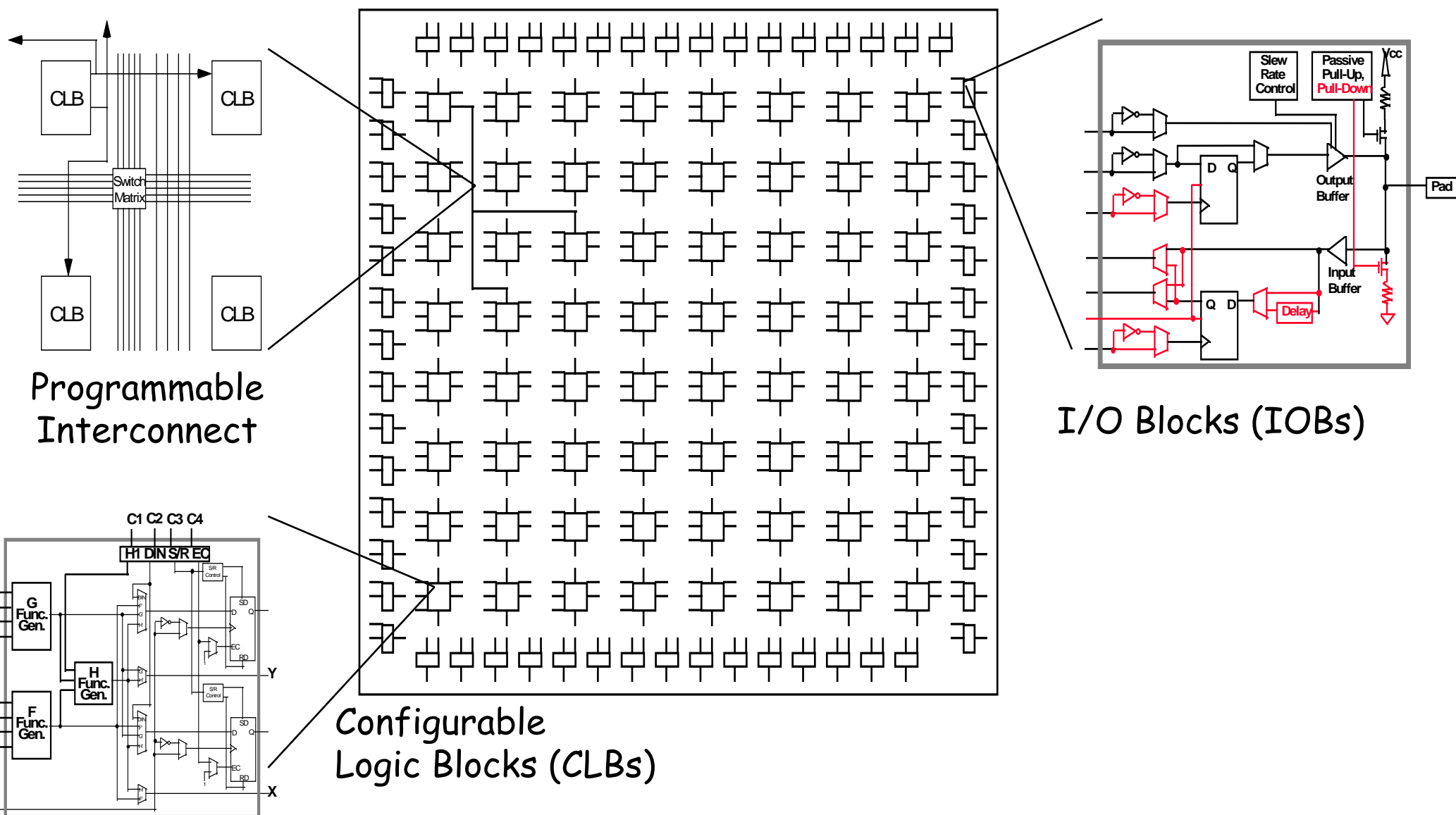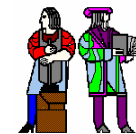RAM Based Field Programmable Logic - Xilinx






The Xilinx 4000 CLB

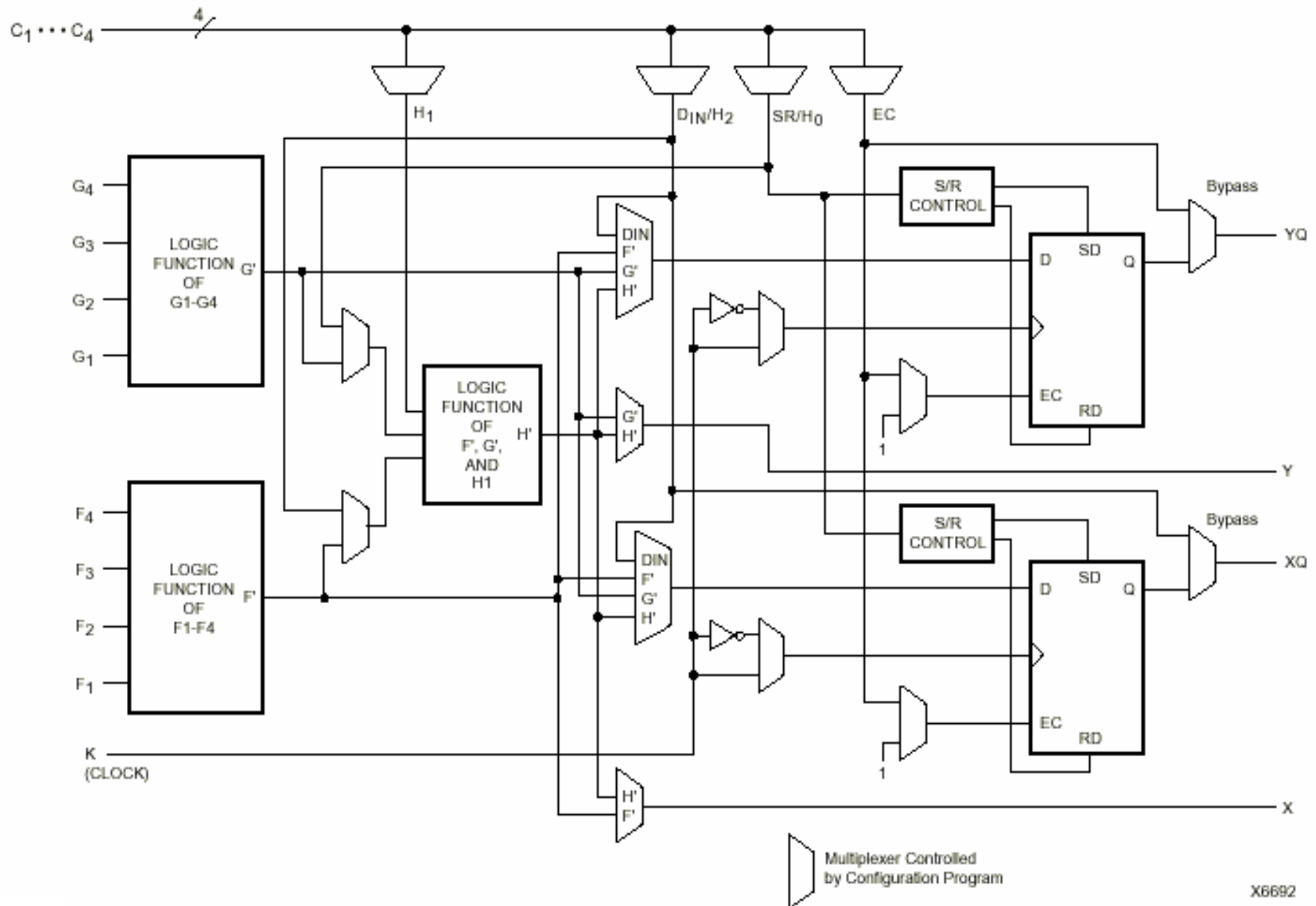


Simplified Block Diagram of XC4000 Series CLB (RAM and Carry Logic functions not shown)



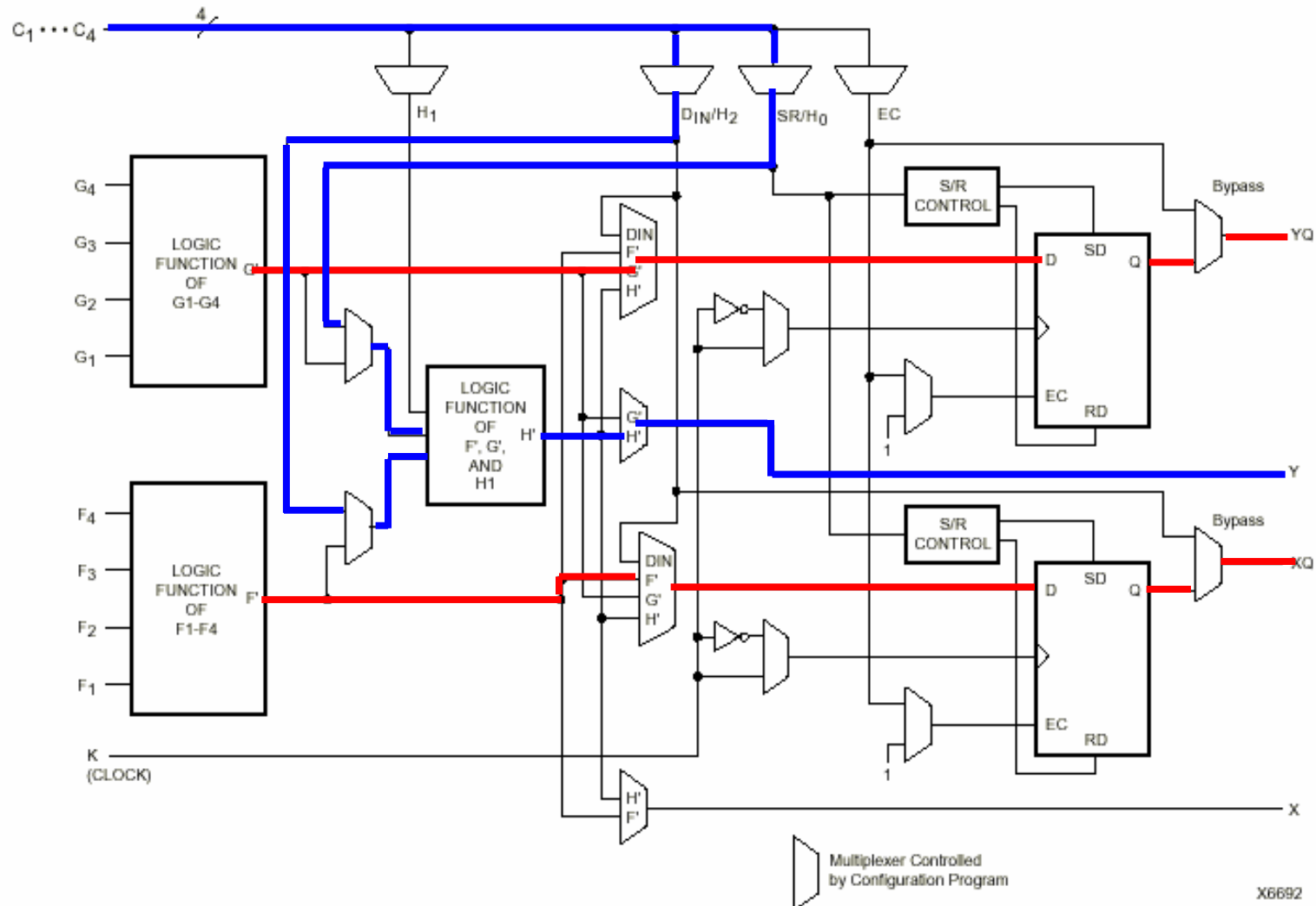Two 4-input Functions, Registered Output and a Two Input Function



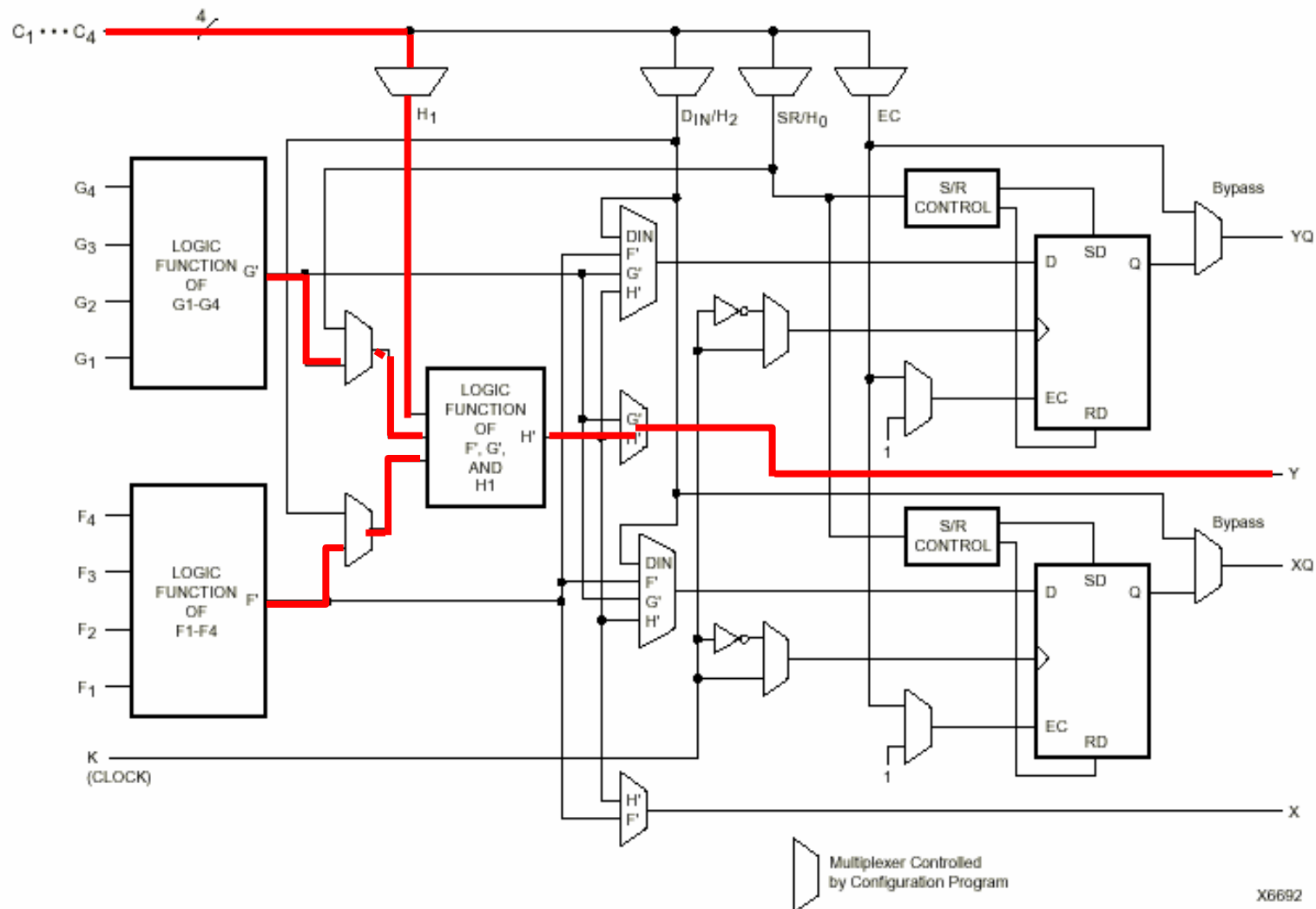Simplified Block Diagram of XC4000 Series CLB (RAM and Carry Logic functions not shown)




L12: 6.111 Spring 2005



LUT Mapping



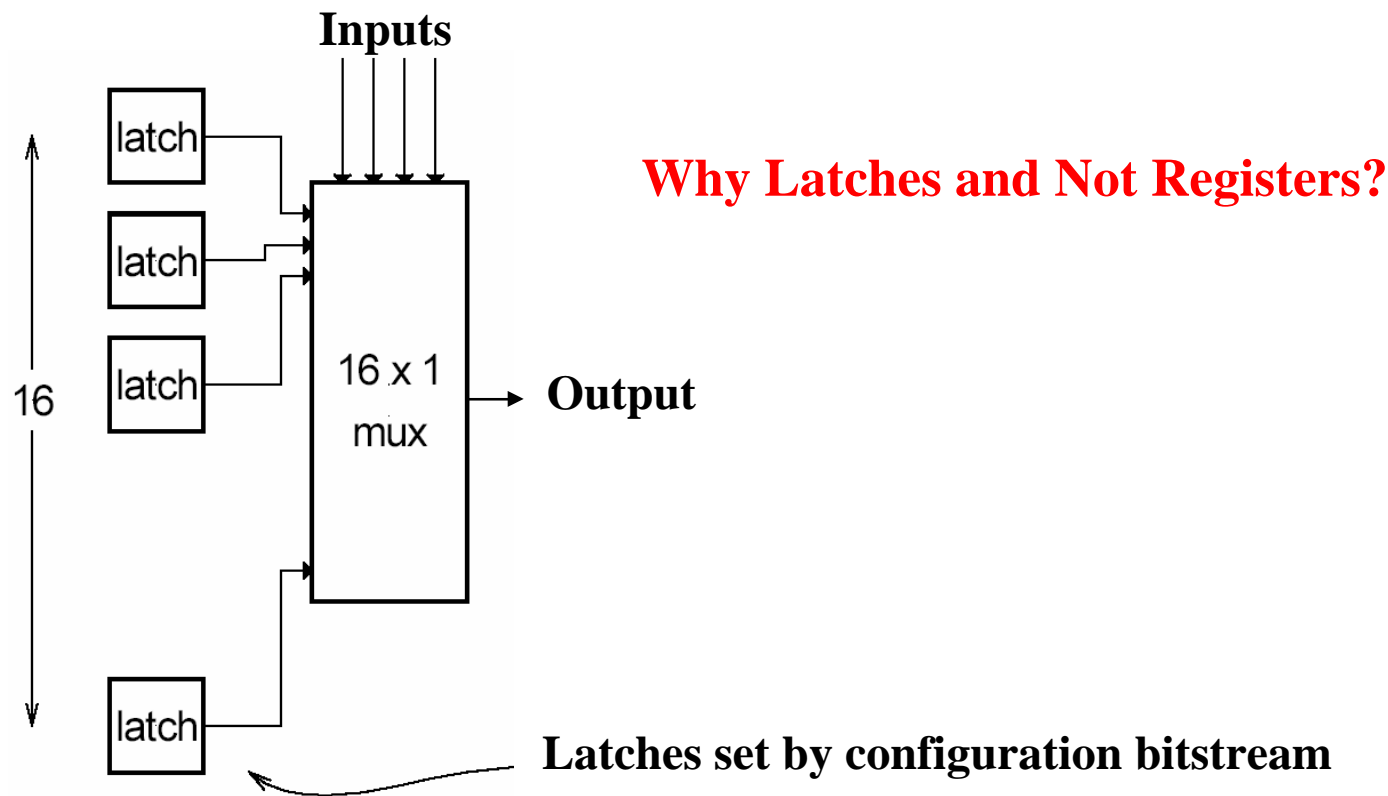
- N-LUT direct implementation of a truth table: any function of n-inputs.
- N-LUT requires 2^N storage elements (latches)
- N-inputs select one latch location (like a memory)



4LUT example




Configuring the CLB as a RAM

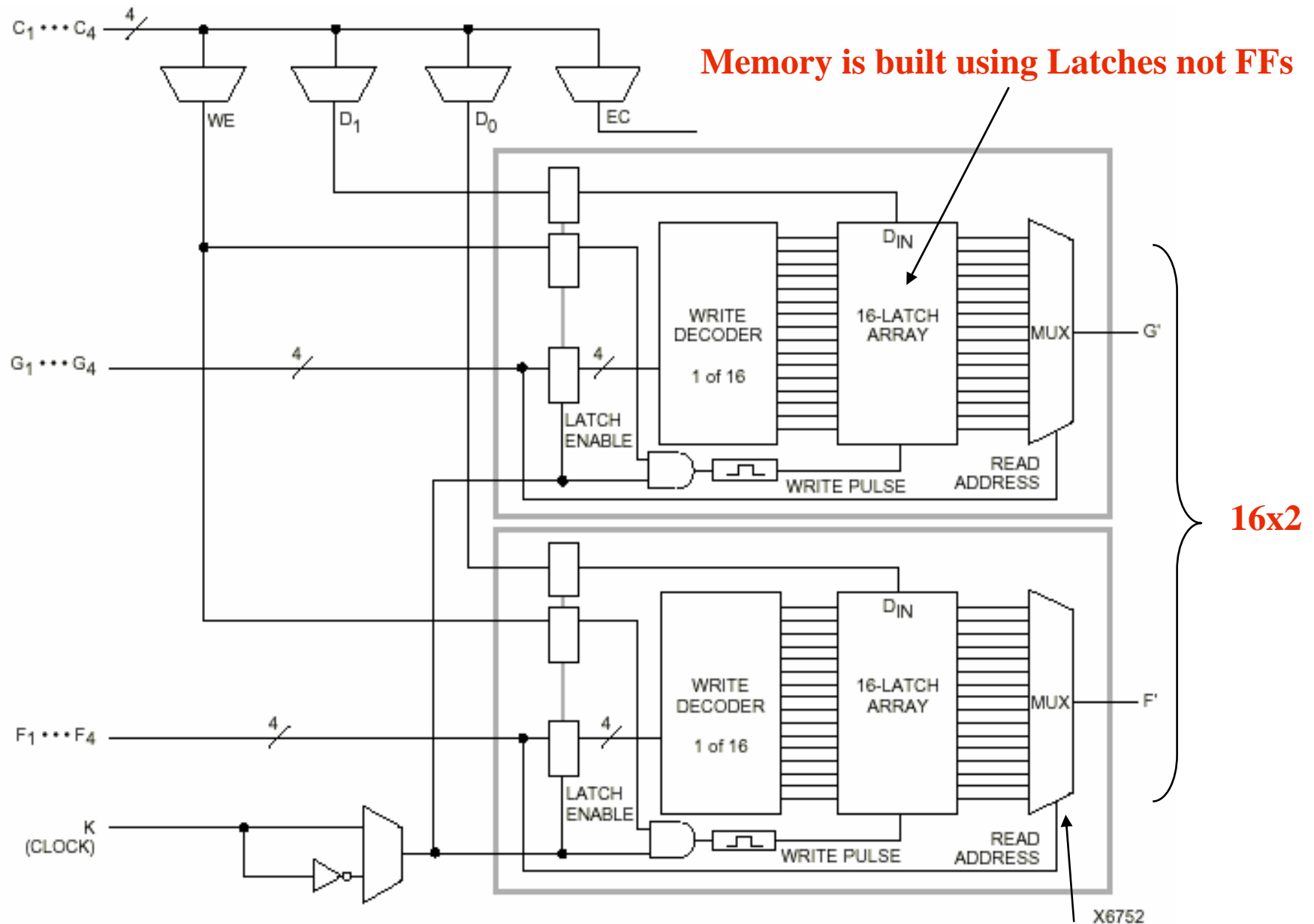

Read is same a LUT Function!





Xilinx 4000 Interconnect

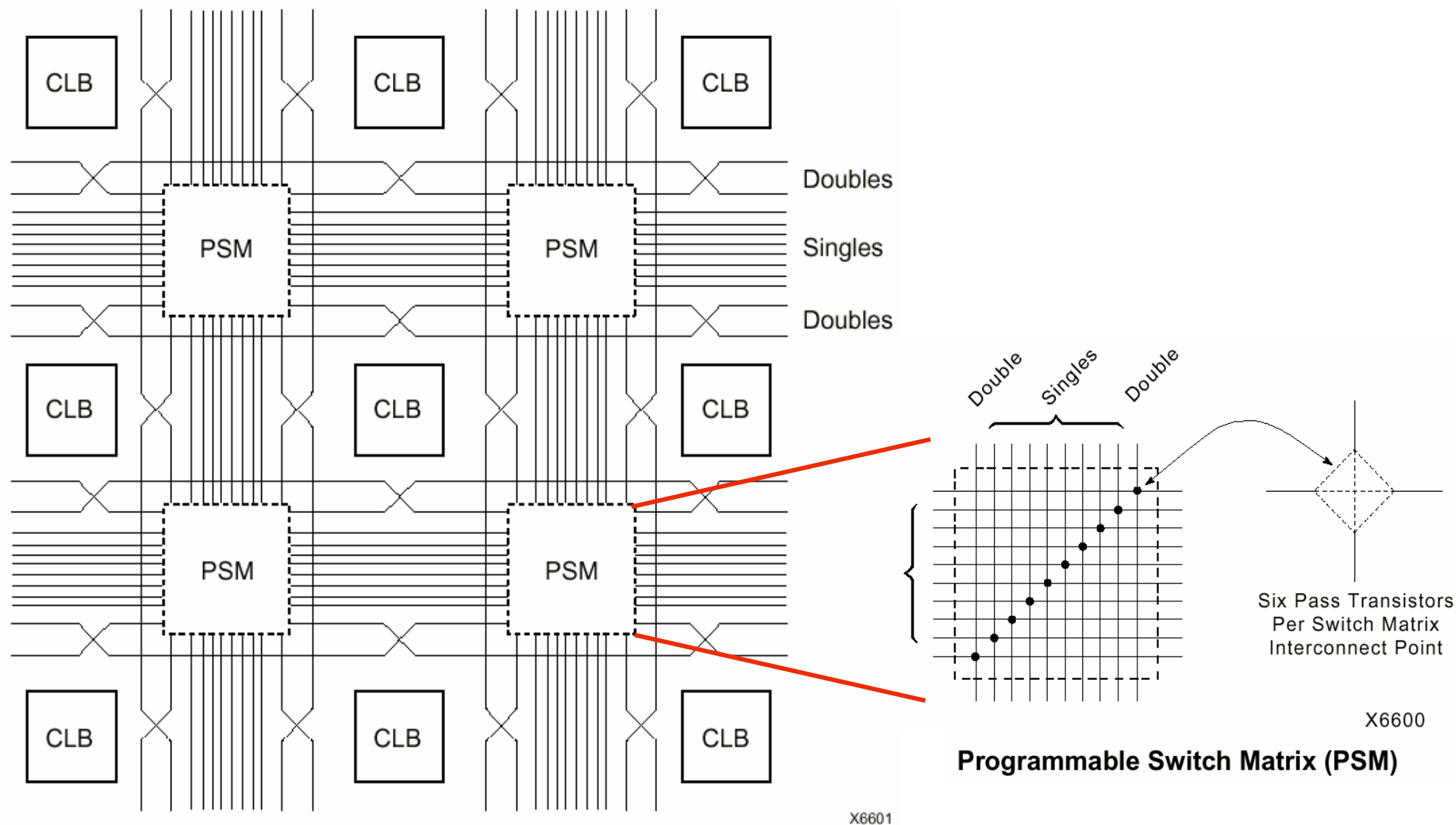

Single- and Double-Length Lines, with Programmable Switch Matrices (PSMs)





Xilinx 4000 Interconnect Details

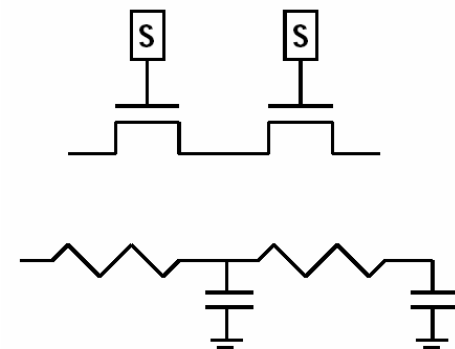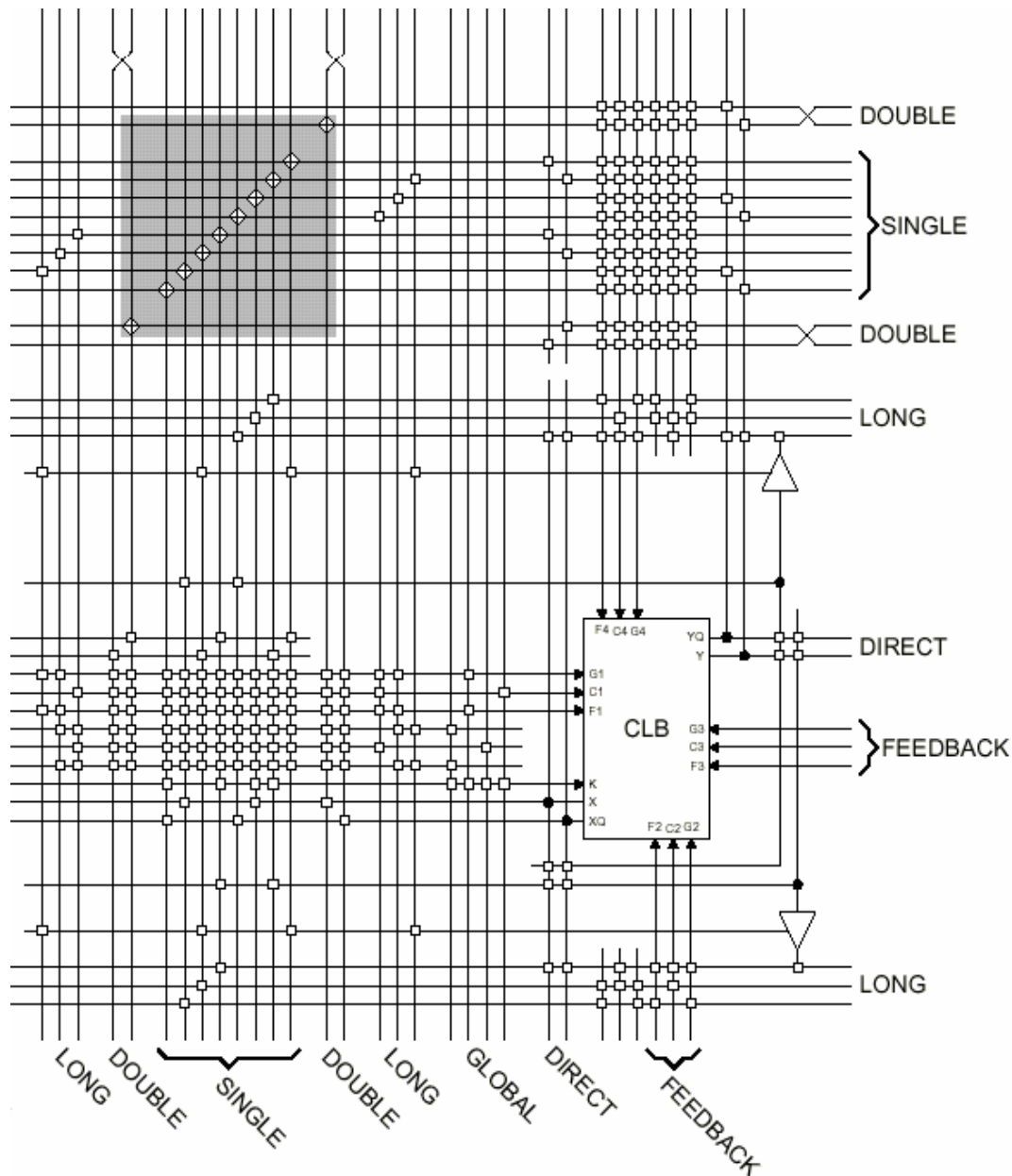

Wires are not ideal!





Add Bells & Whistles

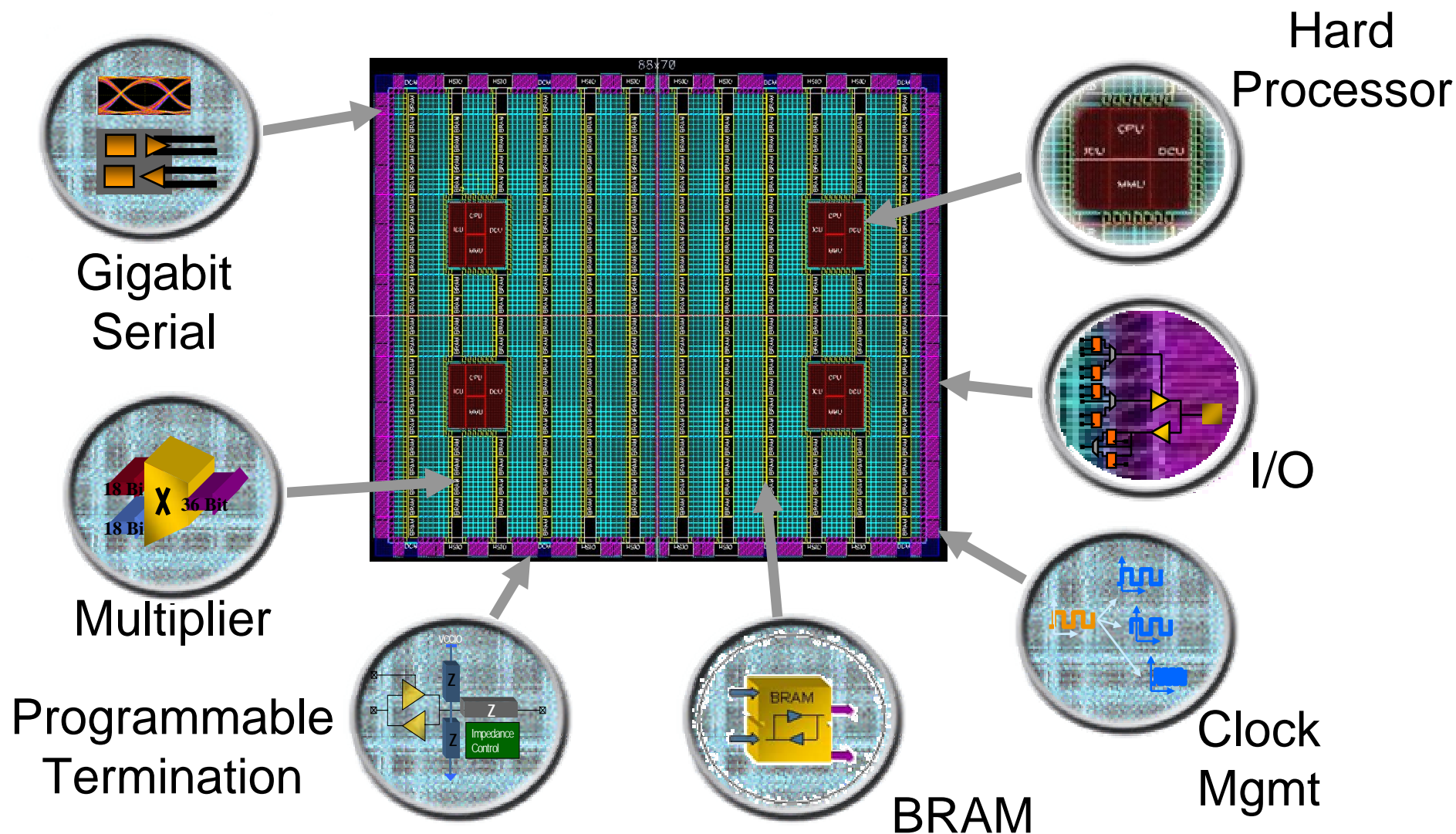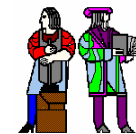

Courtesy of David B. Parlour, ISSCC 2004 Tutorial,
“The Reality and Promise of Reconfigurable Computing in Digital Signal Processing”




Xilinx 4000 Flexible IOB

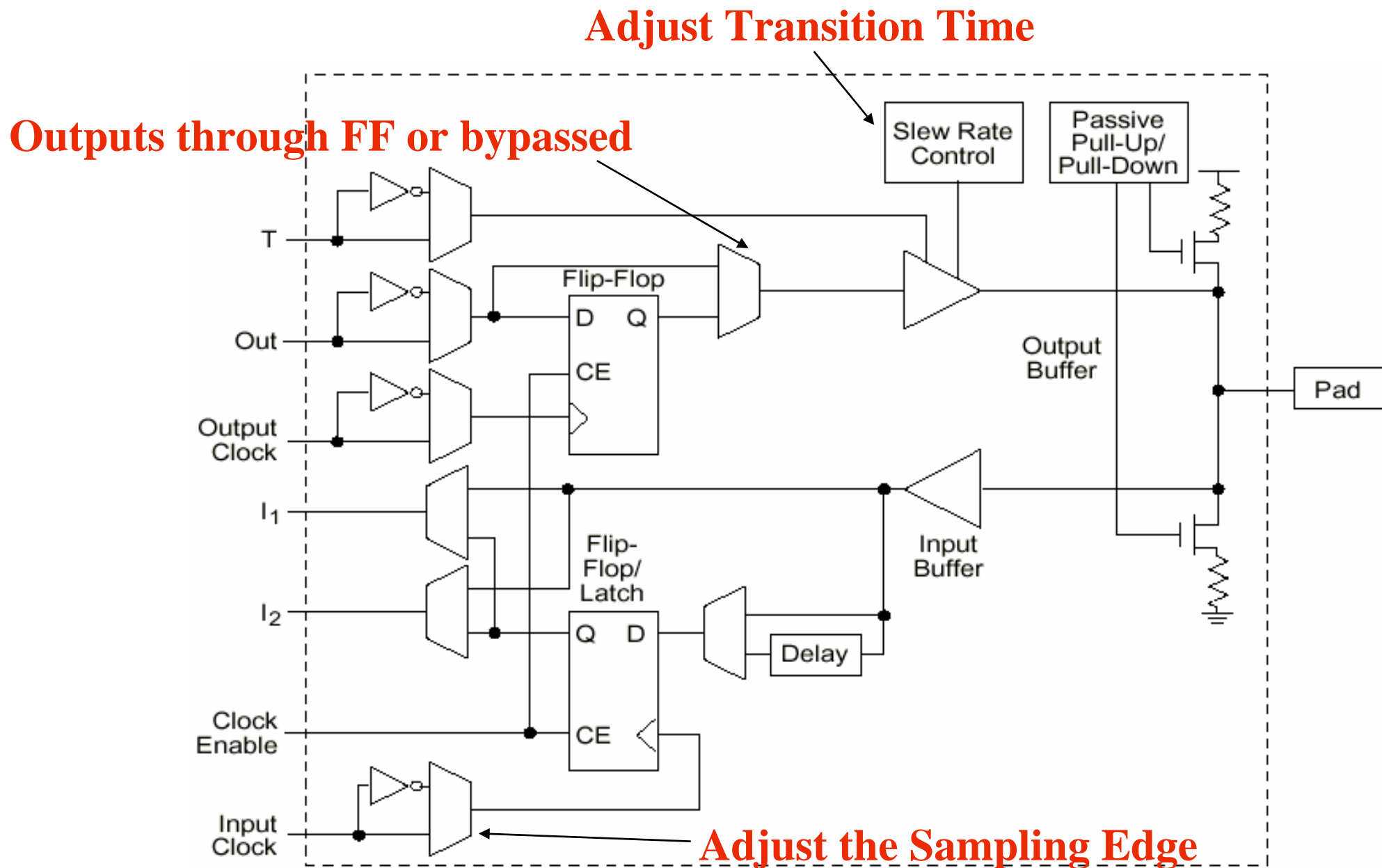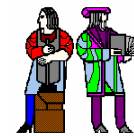




The Virtex II CLB (Half Slice Shown)

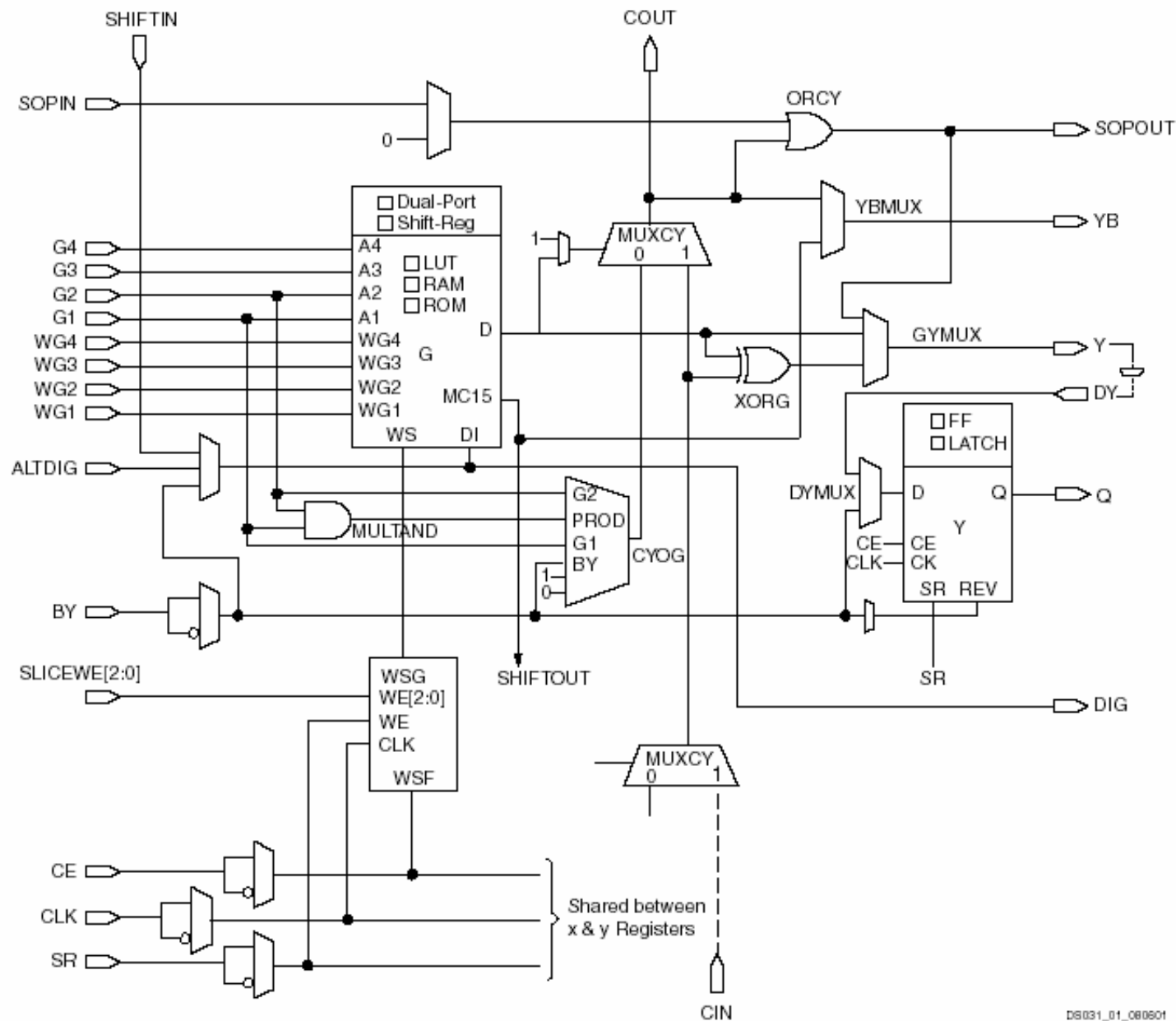

DS031_01_080601




DS031_01_080601

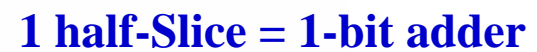





Carry Chain

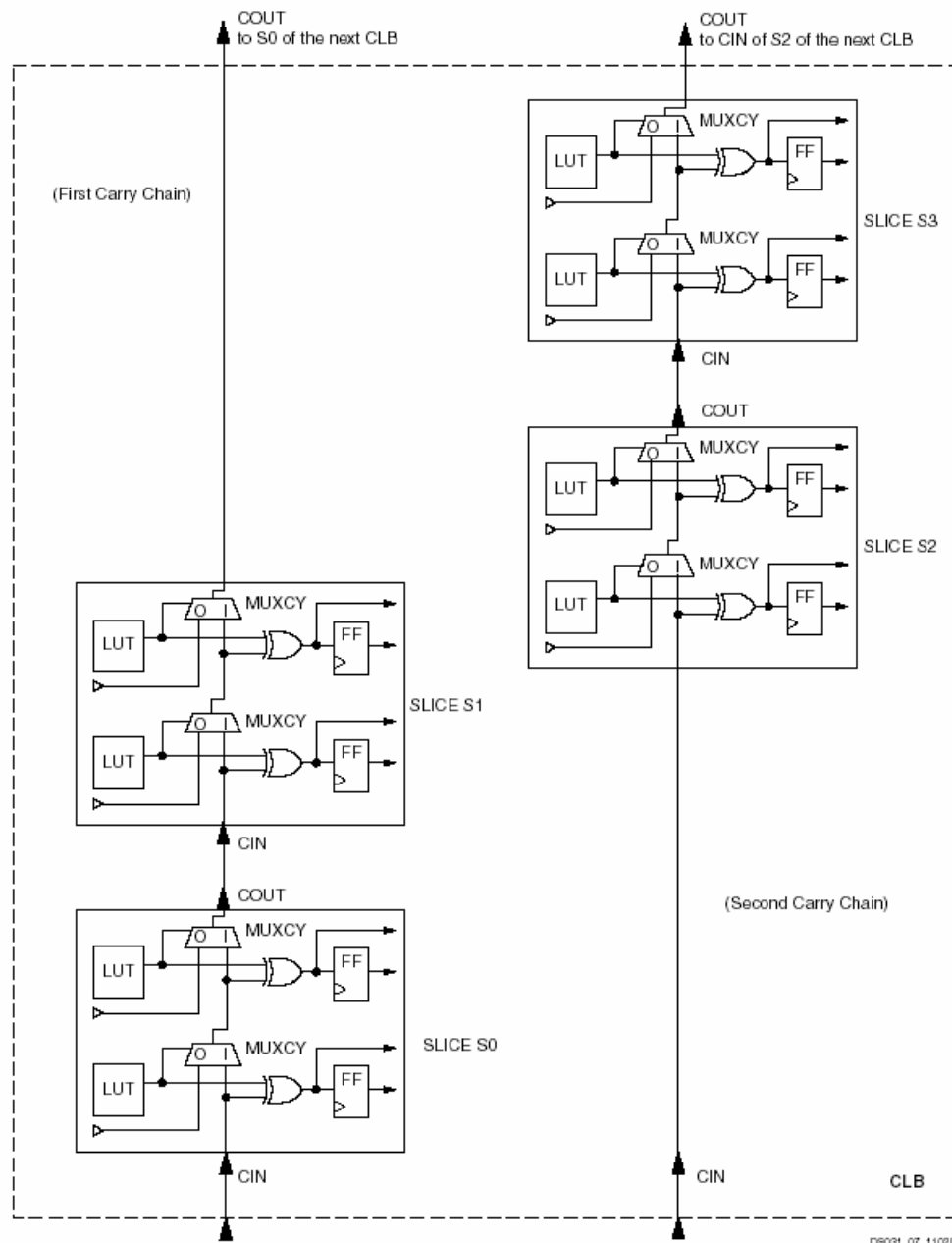

1 CLB = 4 Slices = 2, 4-bit adders


64-bit Adder: 16 CLBs

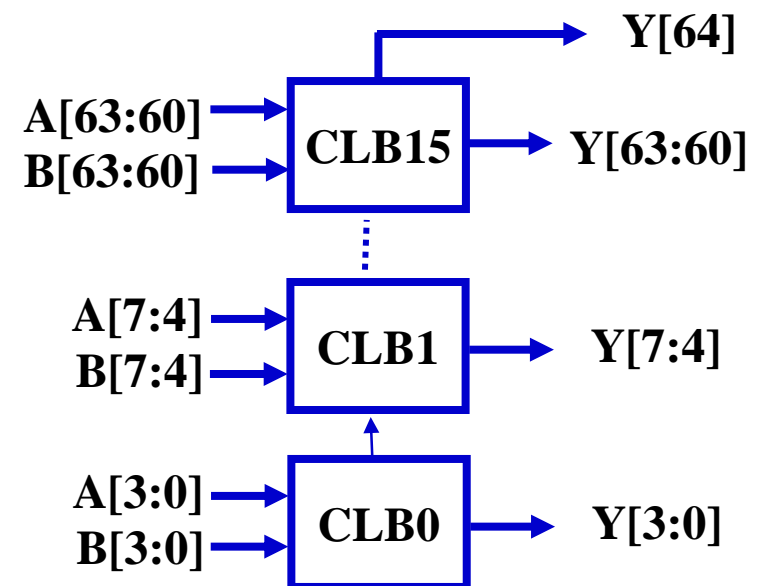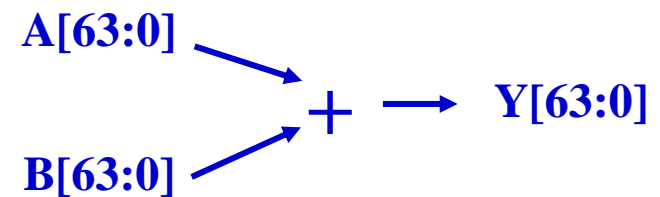


CLBs must be in same column




Virtex II Features

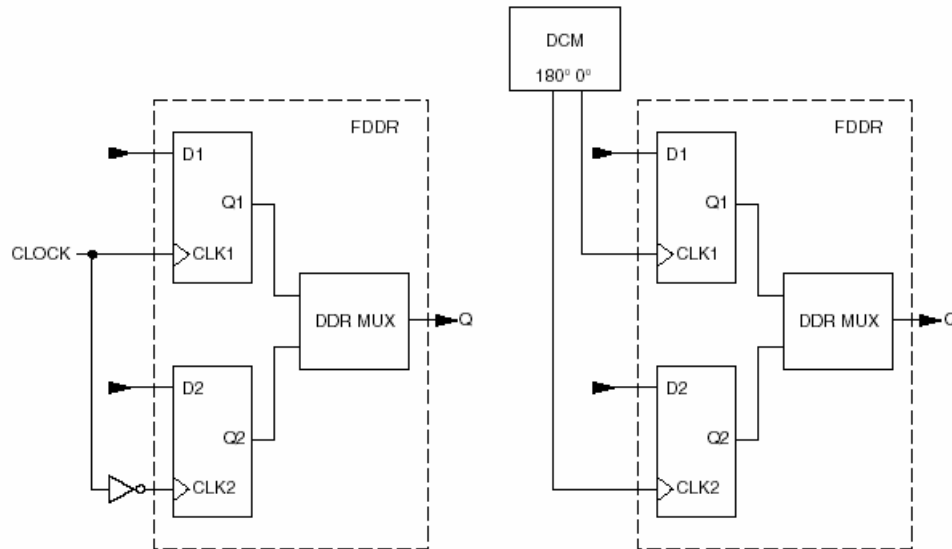


Double Data Rate registers

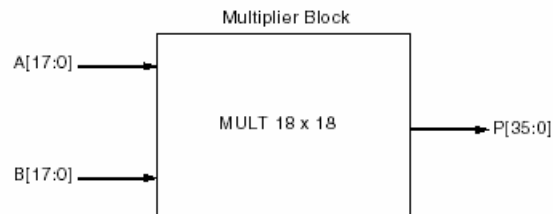

Embedded Multiplier

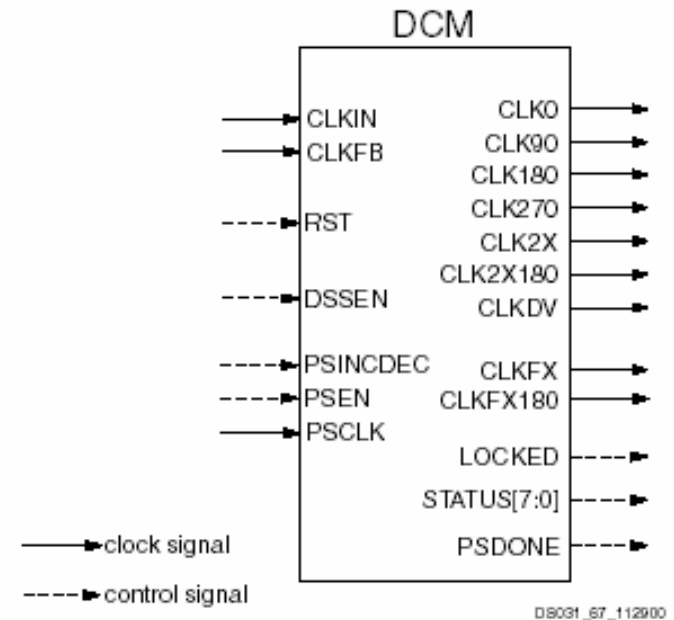



Digital Clock Manager

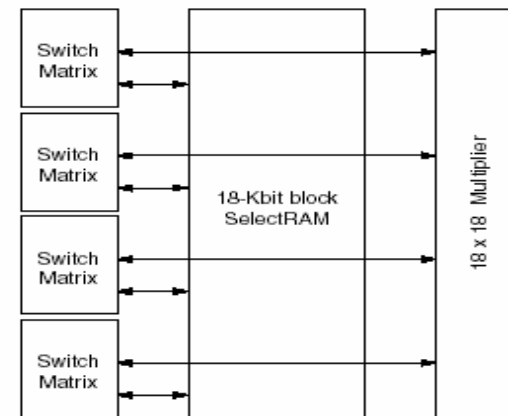

Block SelectRAM




The Latest Generation: Virtex-II Pro

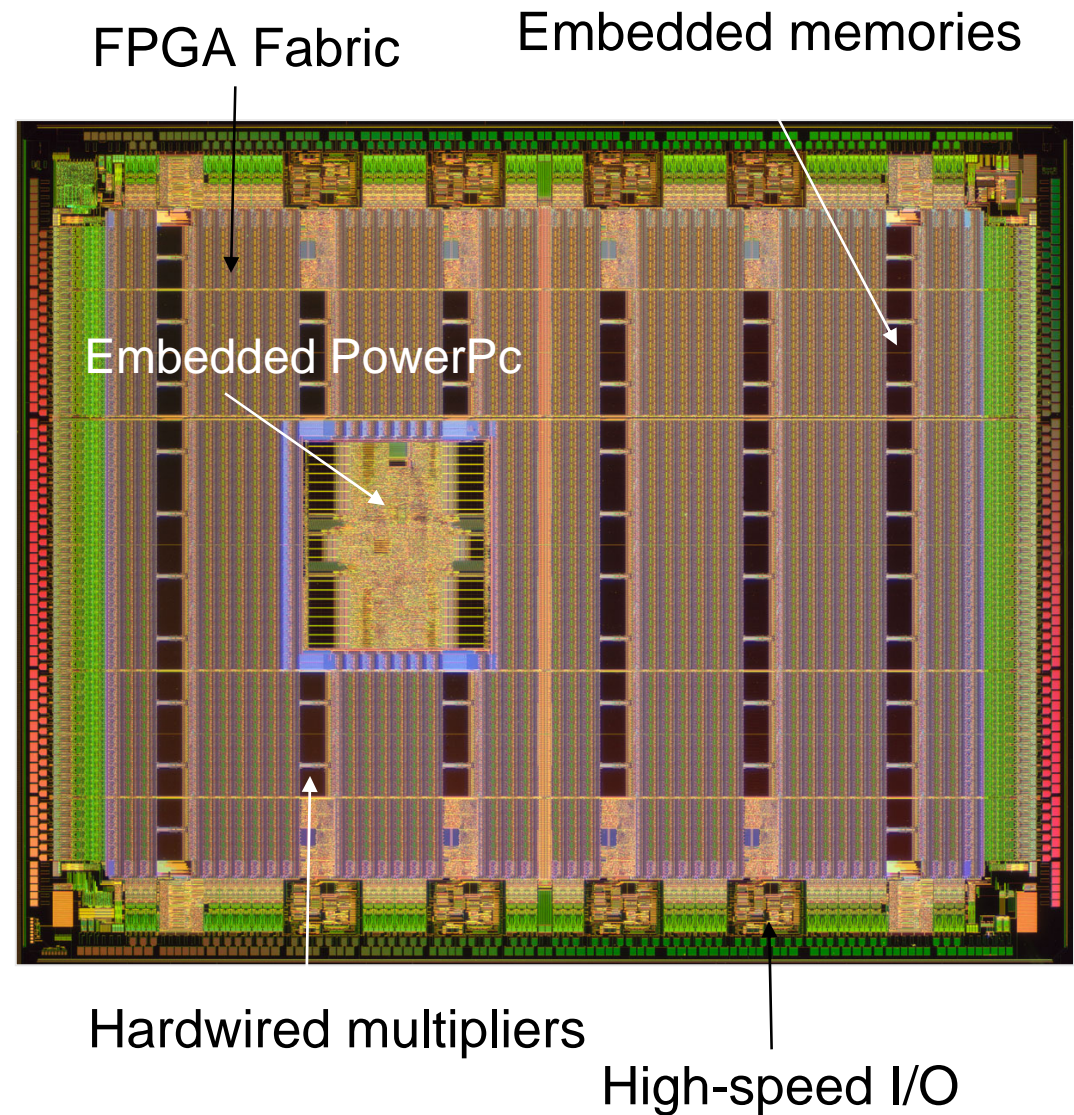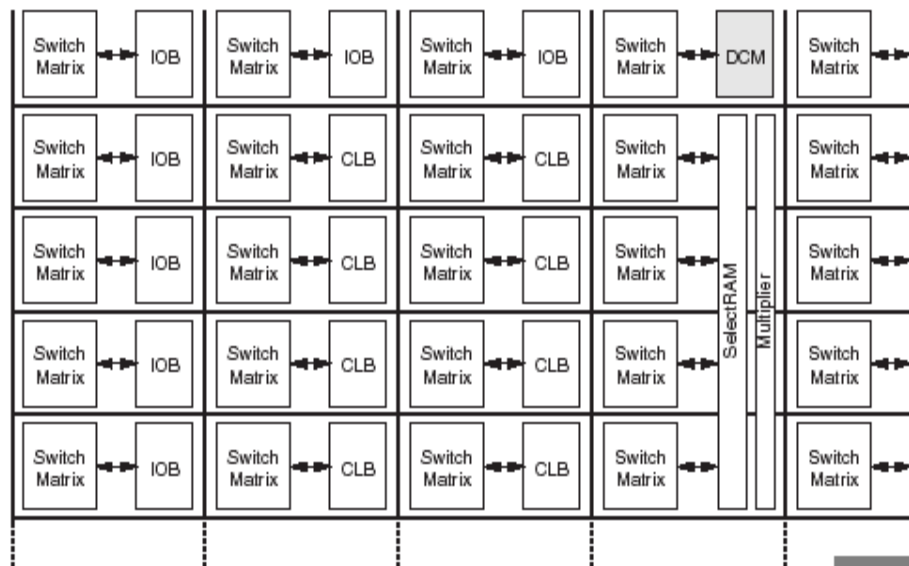

Courtesy Xilinx




Altera FLEX 10K Family

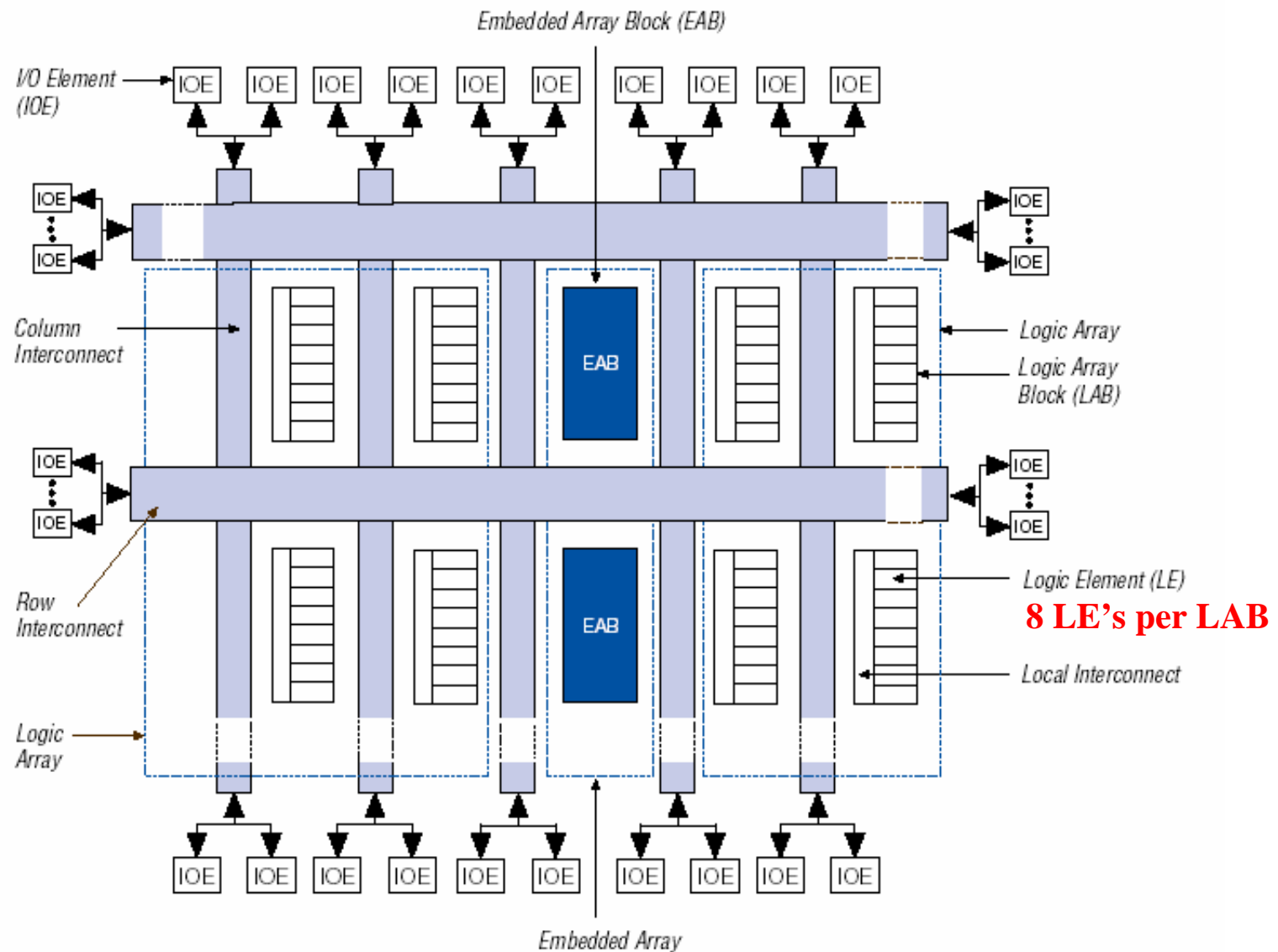

SRAM-based programming




Altera Logic Element

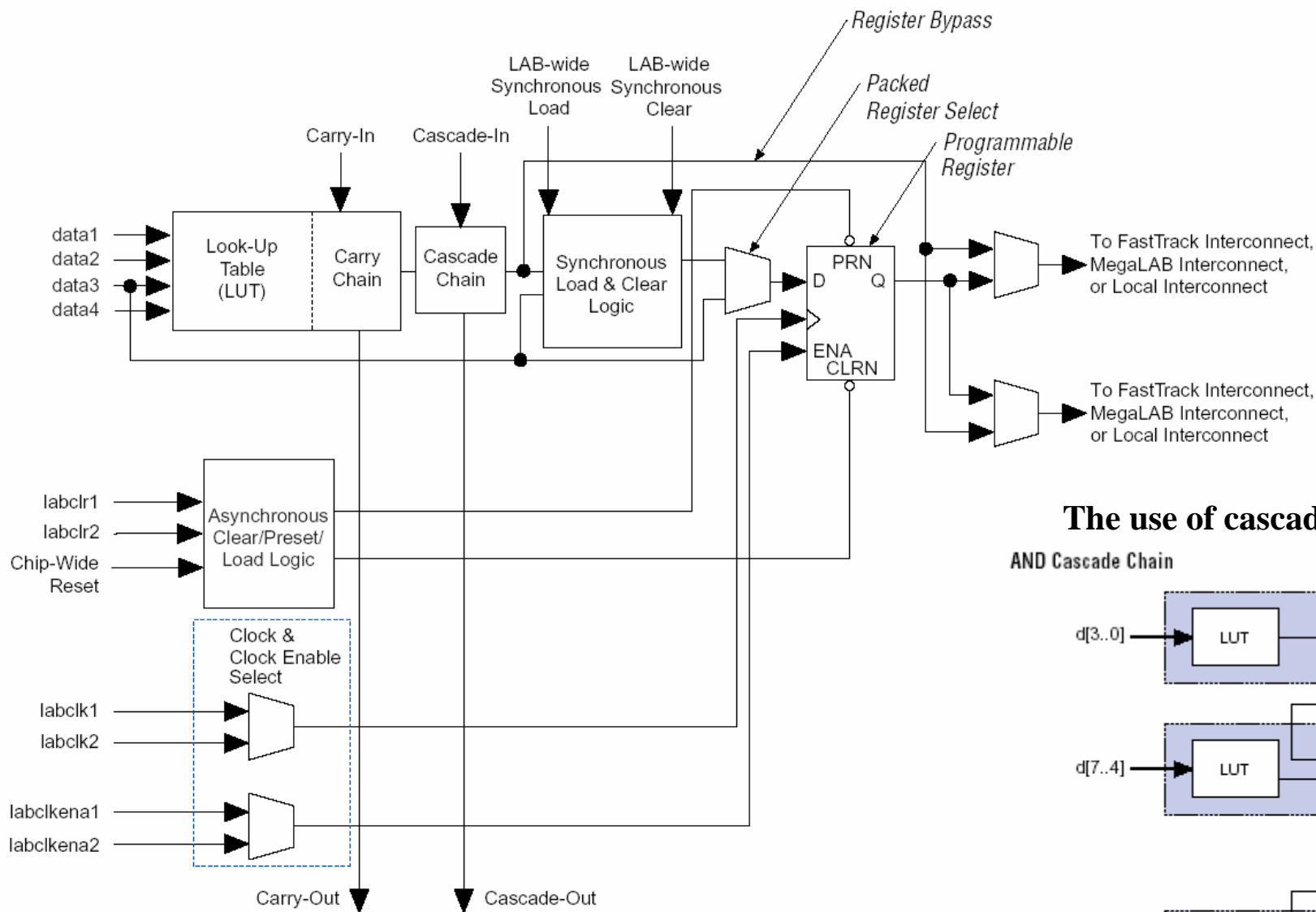


The use of cascade chain

AND Cascade Chain

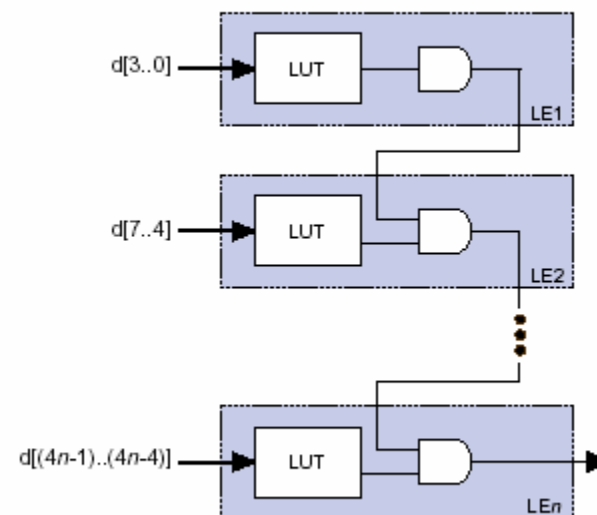




FLEX 10K Logic Array Block

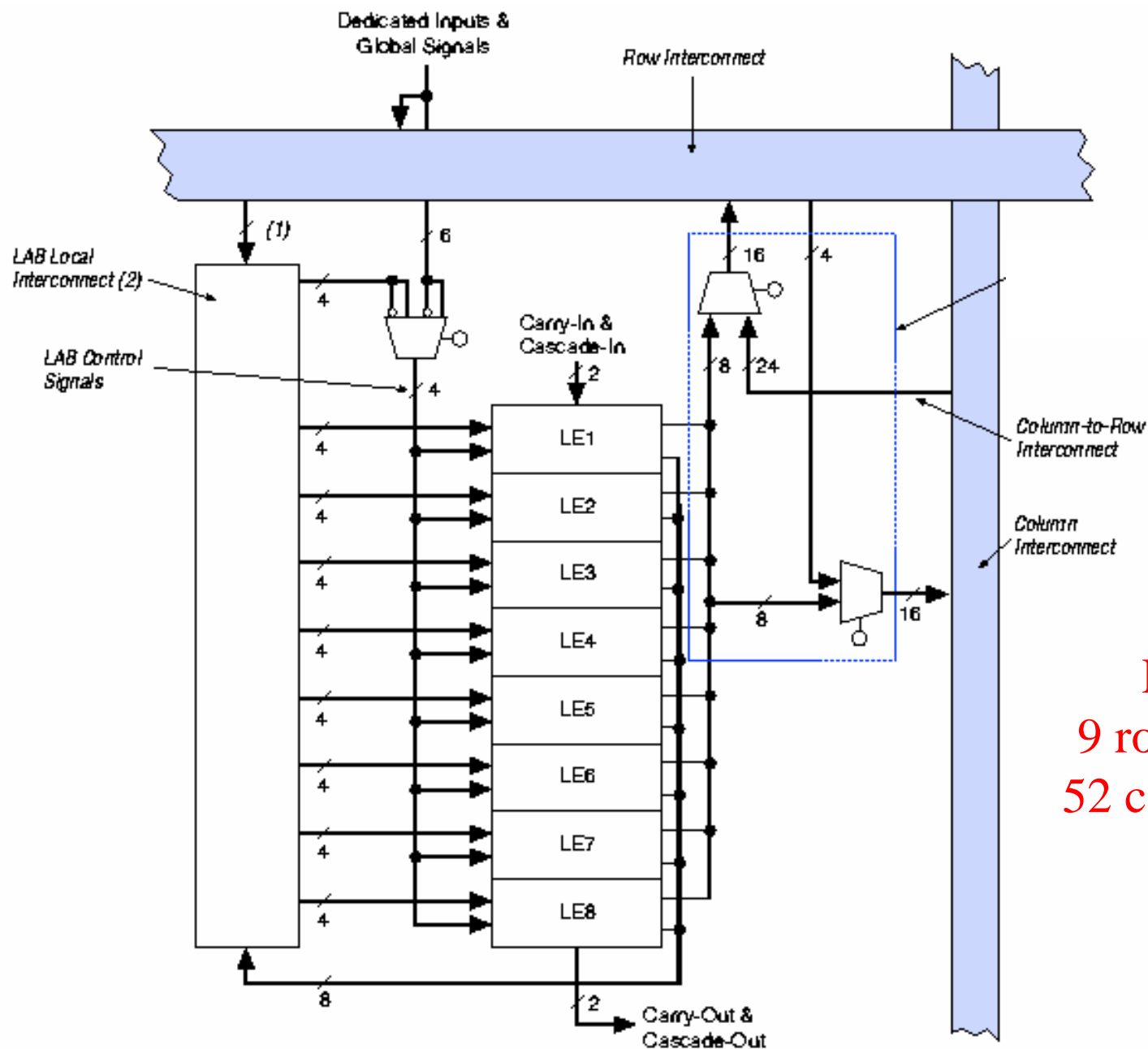

FLEX 10K70:
9 rows (312 chan/row),
52 columns (24 chan/col)




FLEX 10K Embedded Array Block

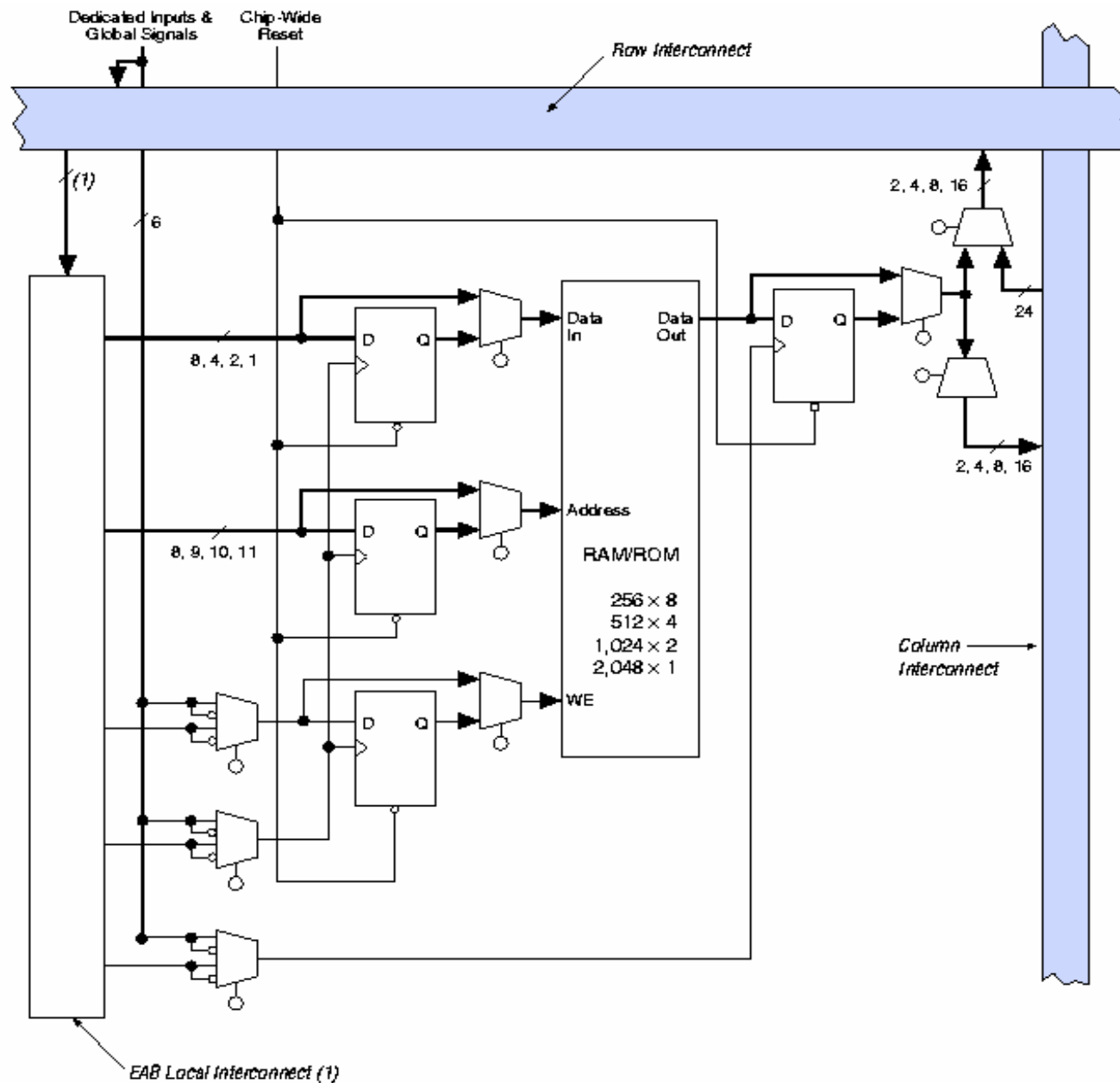



Altera's New Stratix Architecture

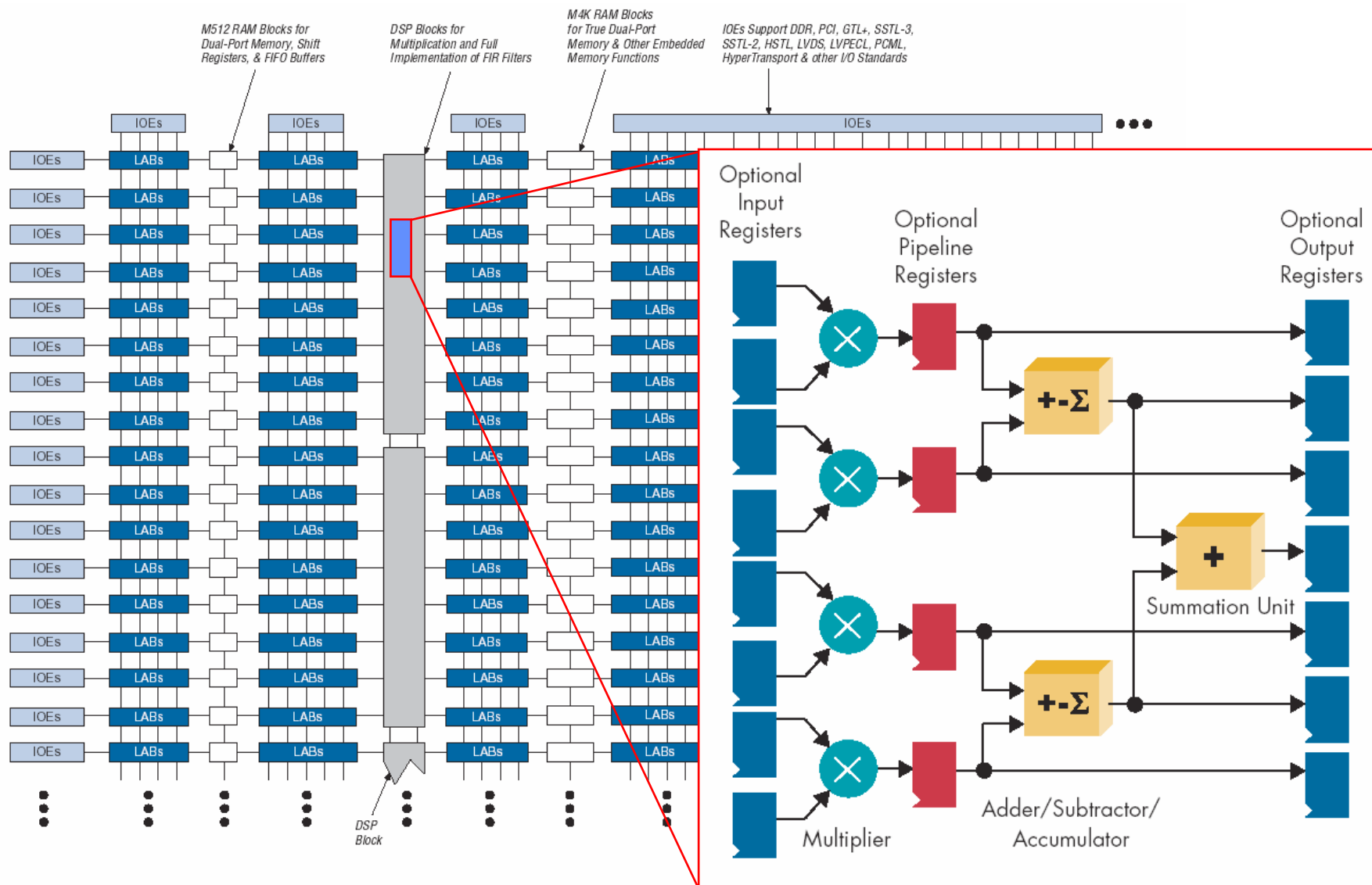

Up to 11,310 LE's, 10Mbits RAM
10 LE's per LAB


Embedded DSP feature: 9x9, 18x18, 36x36 with 52-bit accumulator



Design Flow - Mapping



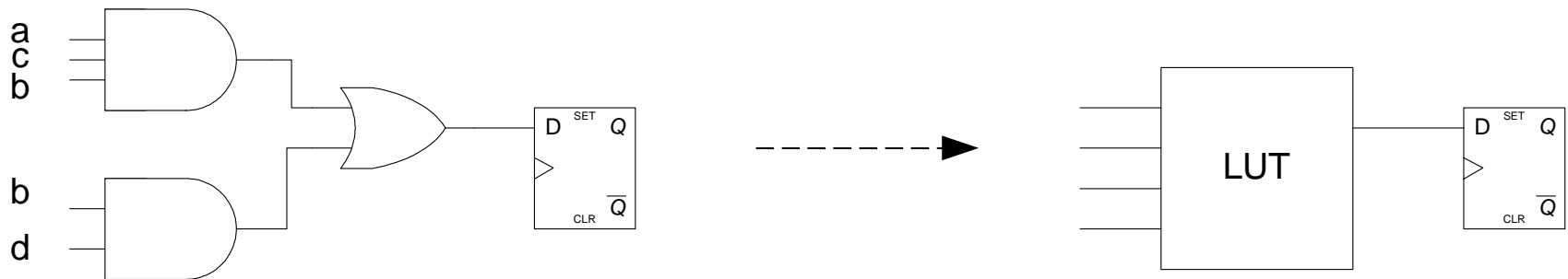- **Technology Mapping: Schematic/HDL to Physical Logic units**
- **Compile functions into basic LUT-based groups (function of target architecture)**




```
always @(posedge Clock or negedge Reset)
begin
  if (! Reset)
    q <= 0;
  else
    q <= (a & b & c) | (b & d);
end
```




Design Flow – Placement & Route



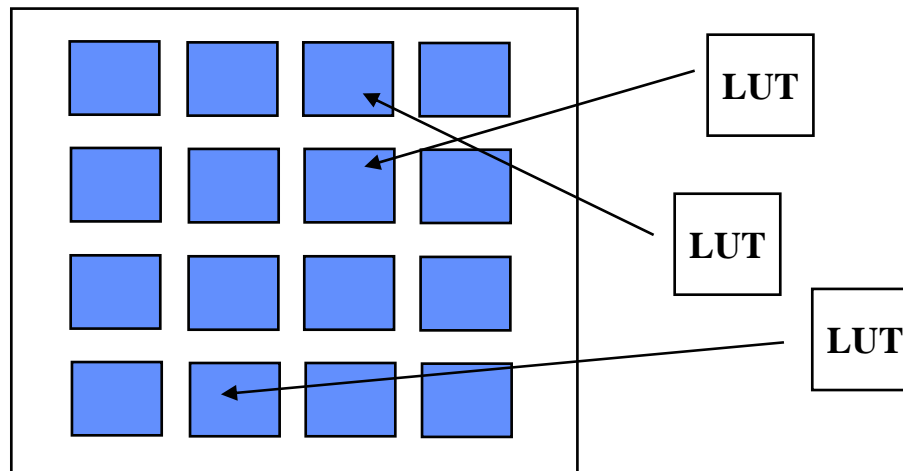- **Placement** – assign logic location on a particular device



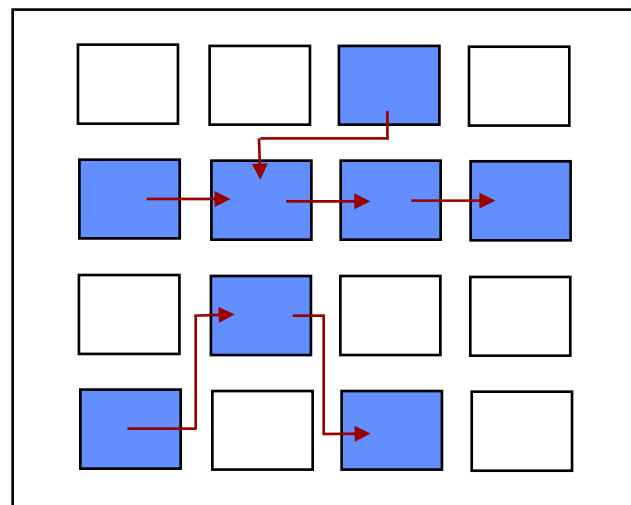- **Routing** – iterative process to connect CLB inputs/outputs and IOBs. Optimizes critical path delay – can take hours or days for large, dense designs



Iterate placement if timing not met

Satisfy timing? → Generate Bitstream to config device

Challenge! Cannot use full chip for reasonable speeds (wires are not ideal).

Typically no more than 50% utilization.




Example: Verilog to FPGA




```
module adder64 (a, b, sum);  
  input [63:0] a, b;  
  output [63:0] sum;  
  
  assign sum = a + b;  
endmodule
```

- 
- Synthesis
 - Tech Map
 - Place&Route

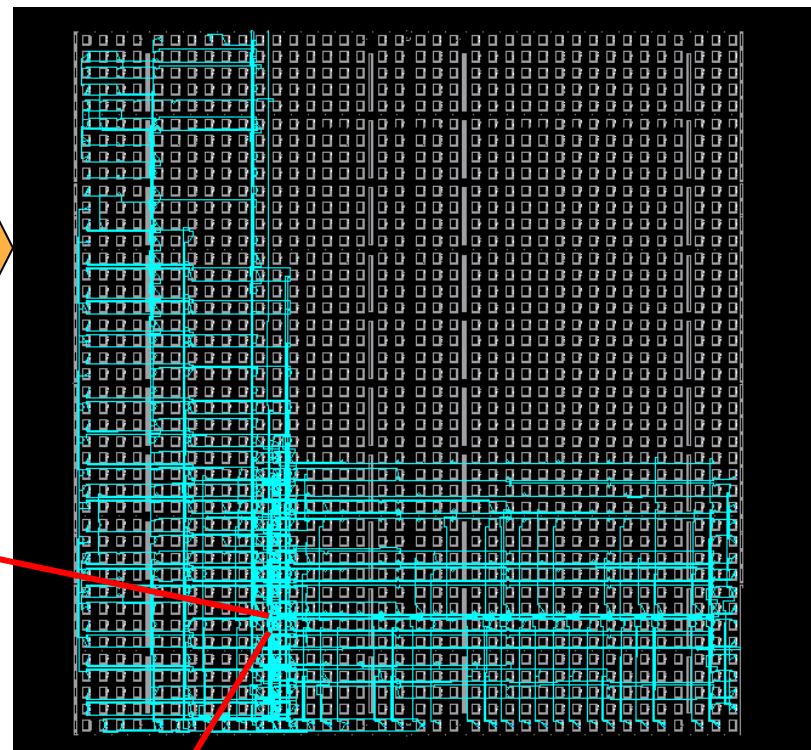

Virtex II – XC2V2000

64-bit Adder Example

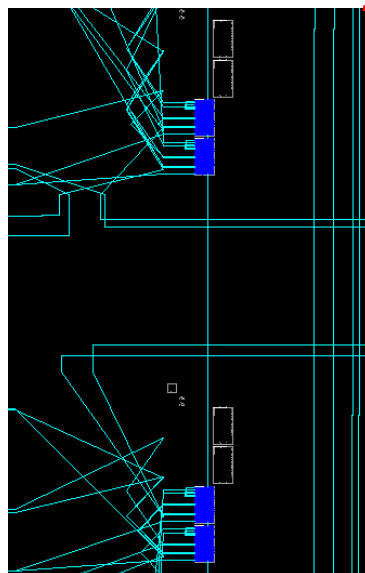




How are FPGAs Used?



Logic Emulation

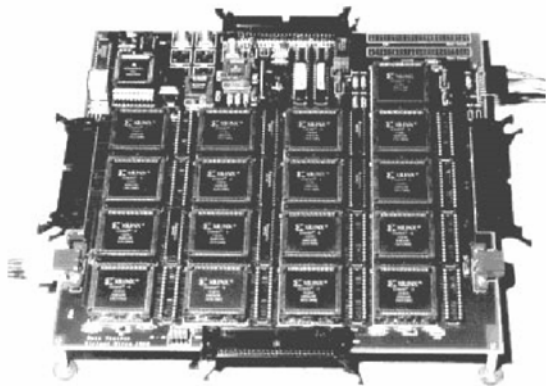

■ Prototyping


- Ensemble of gate arrays used to emulate a circuit to be manufactured
- Get more/better/faster debugging done than with simulation

■ Reconfigurable hardware

- One hardware block used to implement more than one function

■ Special-purpose computation engines

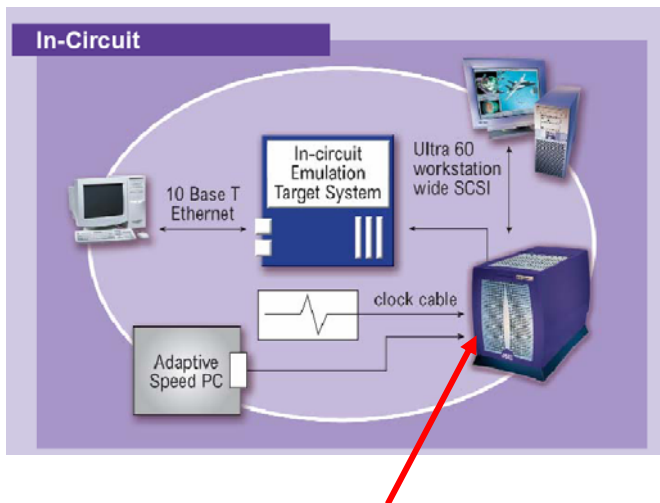- Hardware dedicated to solving one problem (or class of problems)
- Accelerators attached to general-purpose computers (e.g., in a cell phone!)



FPGA-based Emulator
(courtesy of IKOS)



Summary



- **FPGA provide a flexible platform for implementing digital computing**
- **A rich set of macros and I/Os supported (multipliers, block RAMS, ROMS, high-speed I/O)**
- **A wide range of applications from prototyping (to validate a design before ASIC mapping) to high-performance spatial computing**
- **Interconnects are a major bottleneck (physical design and locality are important considerations)**

“College students will study concurrent programming instead of “C” as their first computing experience.”

-- David B. Parlour, ISSCC 2004 Tutorial