
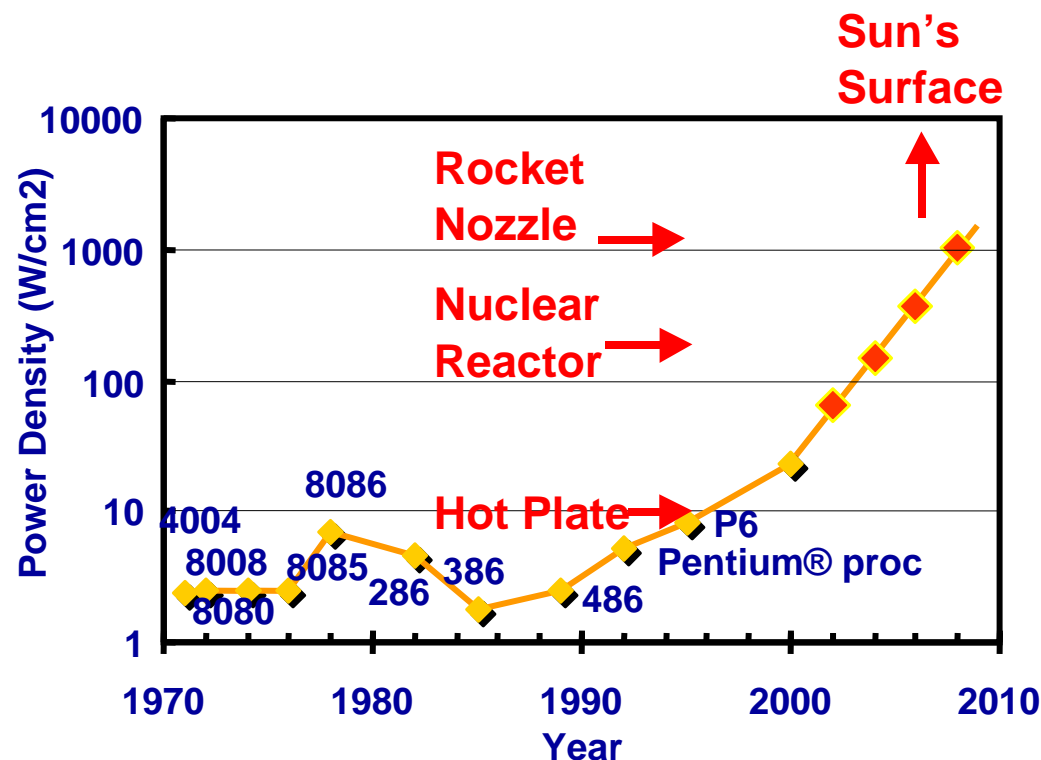


L16: Power Dissipation in Digital Systems


Acknowledgements:

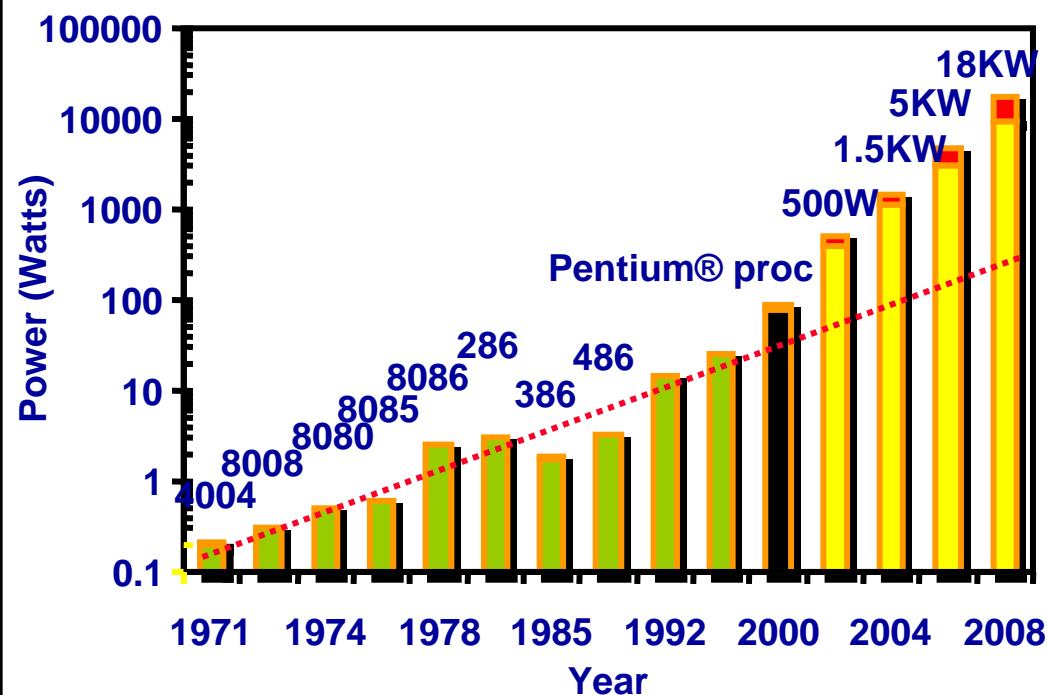
Lecture prepared by Professor Anantha Chandrakasan




Courtesy Intel (S. Borkar)

How do you cool these chips??

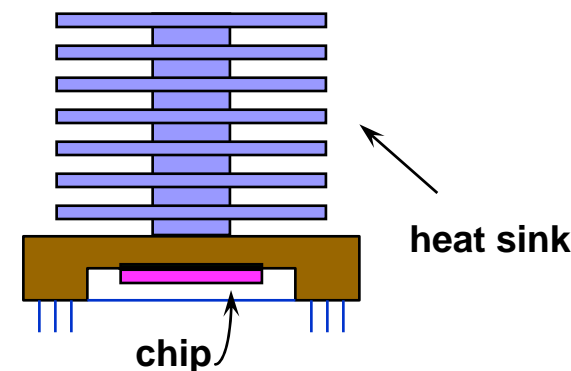

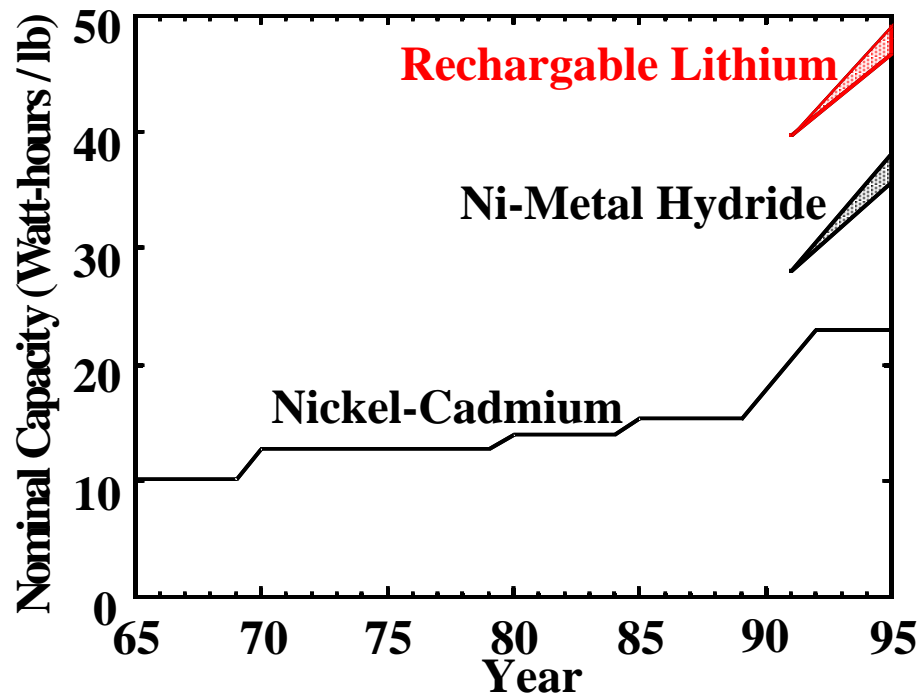

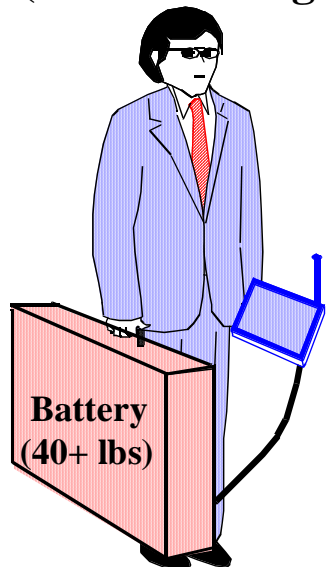(from Jon Eager, Gates Inc. , S. Watanabe, Sony Inc.)



The Energy Problem




**7.5 cm³
AA battery**

**Alkaline:
~10,000J**

*What can **One Joule**
of energy do?*



**Mow your
lawn for
1 ms**

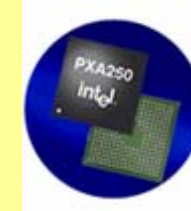


**Operate a
processor
for ~ 7s**




**Send a 1
Megabyte
file over
802.11b**

No Moore's law for batteries...
**Today: Understand where power goes
and ways to manage it**

Charging

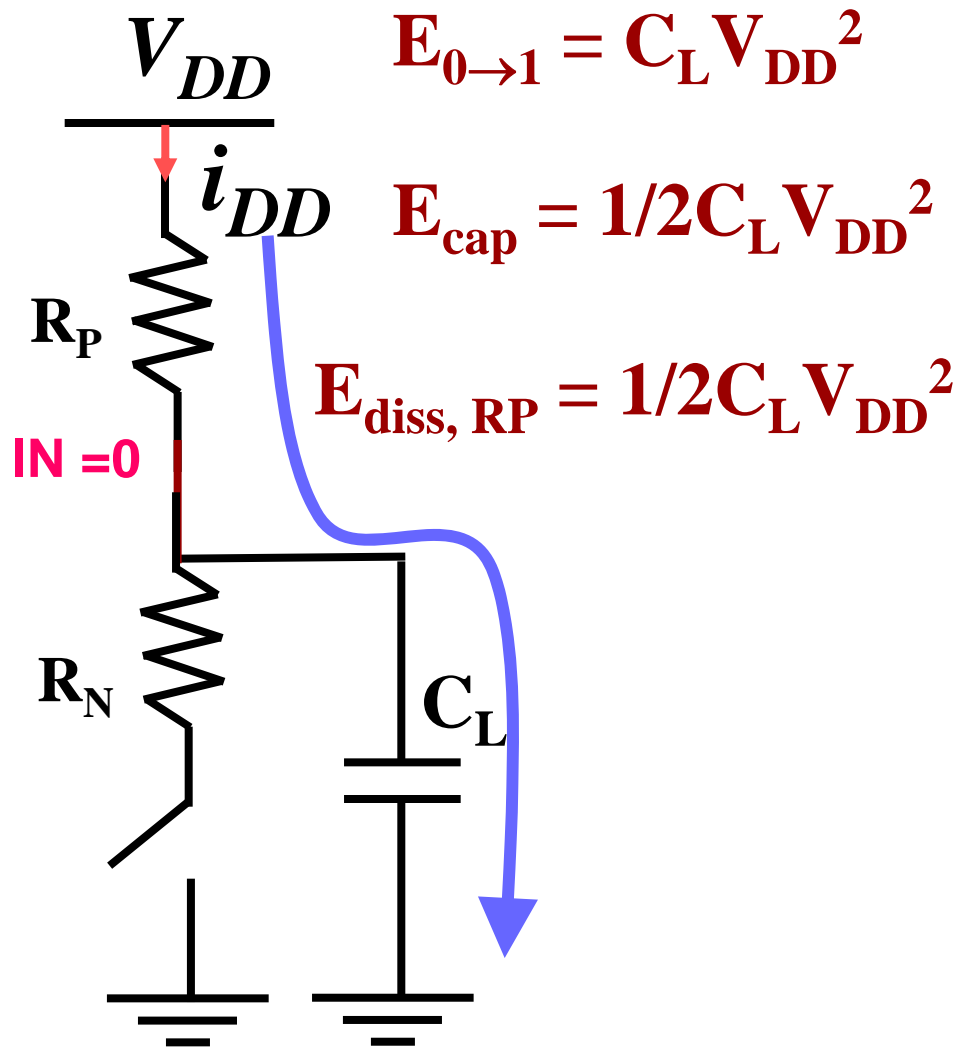


Discharging

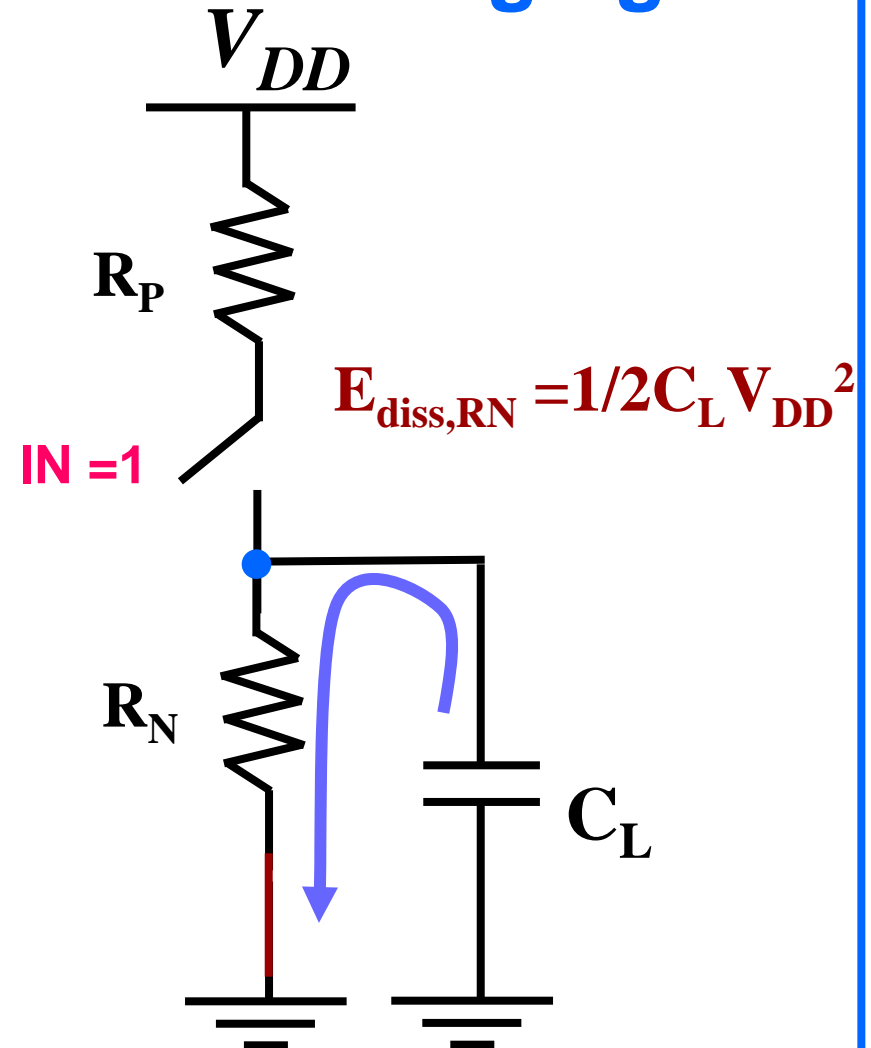

$$P = C_L V_{DD}^2 f_{clk}$$

| Current Input | Next Input | Output Transition |
|---------------|------------|-------------------|
| 00 | 00 | 1 \rightarrow 1 |
| 00 | 01 | 1 \rightarrow 1 |
| 00 | 10 | 1 \rightarrow 1 |
| 00 | 11 | 1 \rightarrow 0 |
| 01 | 00 | 1 \rightarrow 1 |
| 01 | 01 | 1 \rightarrow 1 |
| 01 | 10 | 1 \rightarrow 1 |
| 01 | 11 | 1 \rightarrow 0 |
| 10 | 00 | 1 \rightarrow 1 |
| 10 | 01 | 1 \rightarrow 1 |
| 10 | 10 | 1 \rightarrow 1 |
| 10 | 11 | 1 \rightarrow 0 |
| 11 | 00 | 0 \rightarrow 1 |
| 11 | 01 | 0 \rightarrow 1 |
| 11 | 10 | 0 \rightarrow 1 |
| 11 | 11 | 0 \rightarrow 0 |

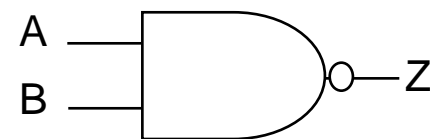


Assume inputs (A,B) arrive at f and are uniformly distributed

What is the average power dissipation?

$$\alpha_{0 \rightarrow 1} = 3/16$$


$$P = \alpha_{0 \rightarrow 1} C_L V_{DD}^2 f$$

Simple Scenario

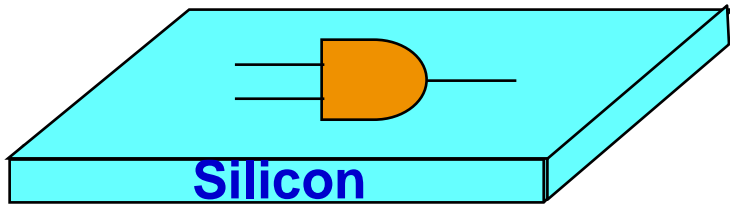

$$T_j - T_a = R_{\theta JA} P_D$$


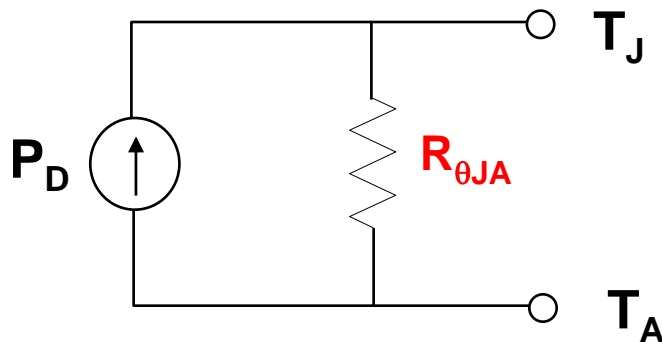
$R_{\theta JA}$ is the thermal resistance between silicon and Ambient



$$T_j = T_a + R_{\theta JA} P_D$$

Make this as low as possible


Realistic Scenario

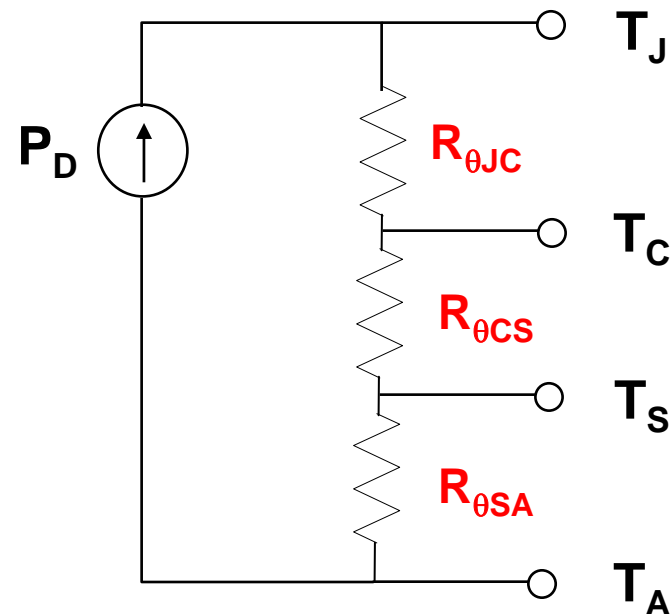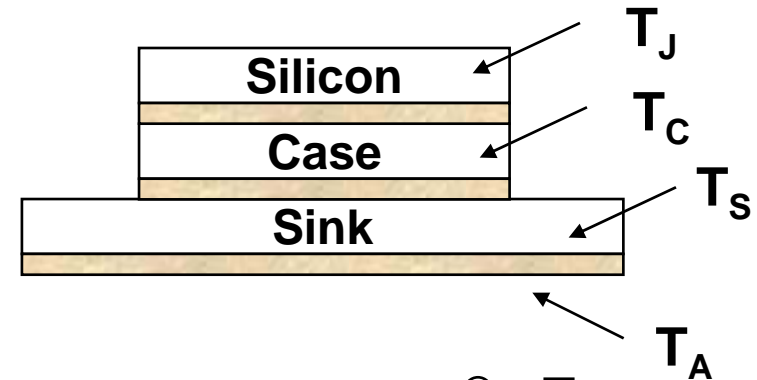


$$R_{\theta CA} = R_{\theta CS} + R_{\theta SA}$$

is minimized by facilitating heat transfer
(bolt case to extended metal surface – heat sink)

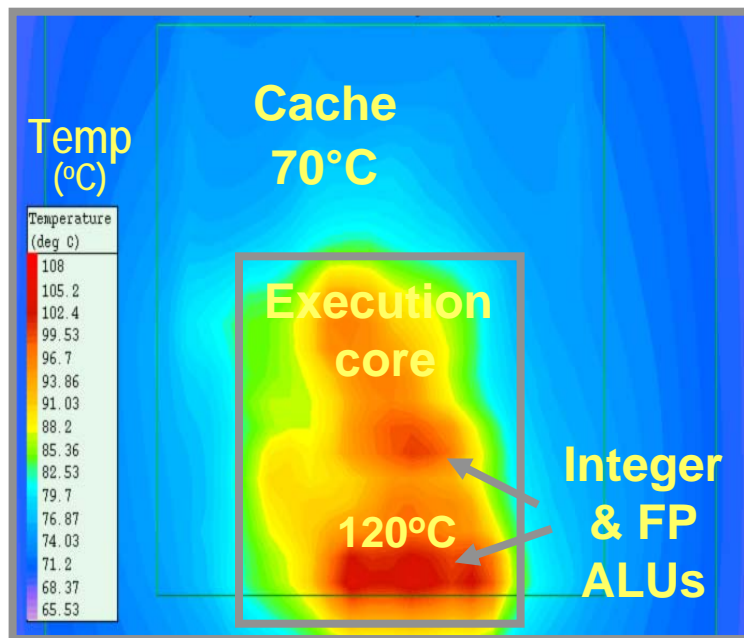- Pentium 4 @ 3.06 GHz dissipates 81.8W!
- Maximum $T_C = 69^\circ\text{C}$
- $R_{CA} < 0.23^\circ\text{C/W}$ for 50°C ambient
- Typical chips dissipate 0.5-1W (cheap packages without forced air cooling)



Courtesy of Intel
(Ram Krishnamurthy)

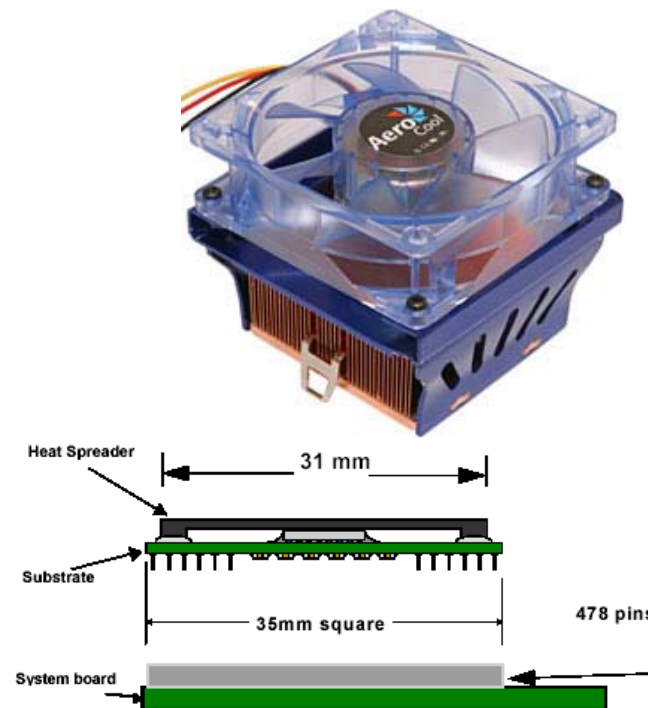


| Processor and Core Frequency | Thermal Design Power ^{1,2} (W) |
|-------------------------------|---|
| Processors with VID=1.500V | |
| 2 GHz | 52.4 |
| 2.20 GHz | 55.1 |
| 2.26 GHz | 56.0 |
| 2.40 GHz | 57.8 |
| 2.50 GHz | 59.3 |
| 2.53 GHz | 59.3 |
| Processors with VID=1.525V | |
| 2 GHz | 54.3 |
| 2.20 GHz | 57.1 |
| 2.26 GHz | 58.0 |
| 2.40 GHz | 59.8 |
| 2.50 GHz | 61.0 |
| 2.53 GHz | 61.5 |
| 2.60 GHz | 62.6 |
| 2.66 GHz | 66.1 |
| 2.80 GHz | 68.4 |
| Processors with multiple VIDs | |
| 2 GHz | 54.3 |
| 2.20 GHz | 57.1 |
| 2.26 GHz | 58.0 |
| 2.40 GHz | 59.8 |
| 2.50 GHz | 61.0 |
| 2.53 GHz | 61.5 |
| 2.60 GHz | 62.6 |
| 2.66 GHz | 66.1 |
| 2.80 GHz | 68.4 |
| 3.06 GHz | 81.8 |

$$P = \alpha_{0 \rightarrow 1} C_L V_{DD}^2 f$$

- Reduce Transition Activity or Switching Events
- Reduce Capacitance (e.g., keep wires short)
- Reduce Power Supply Voltage
- Frequency is typically fixed by the application, though this can be adjusted to control power


Optimize at all levels of design hierarchy

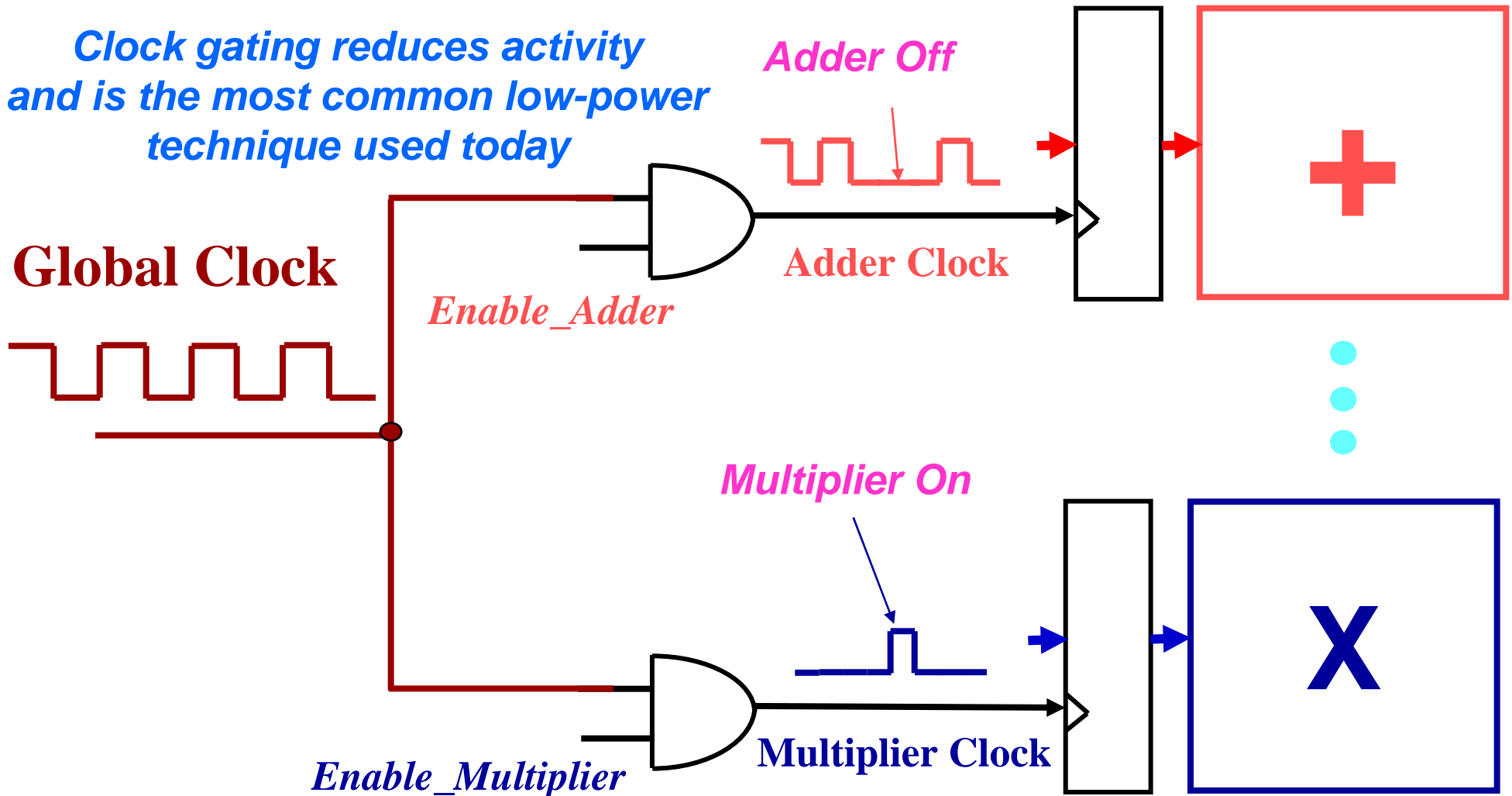Clock gating reduces activity and is the most common low-power technique used today




100's of different clocks in a microprocessor

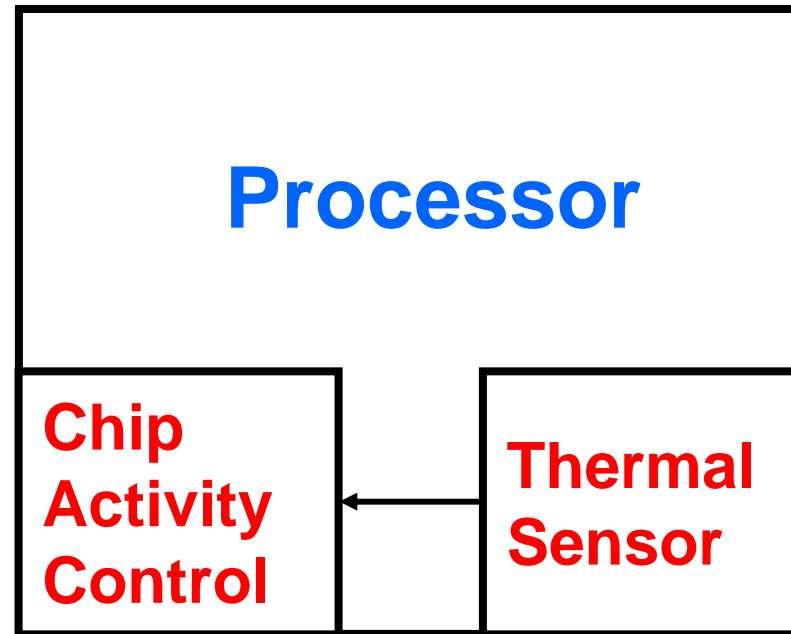Clock Gating Reduces Energy, does it reduce Power?






- Note that there is a difference between average and peak power
- On-chip thermal sensor (diode based), measures the silicon temperature
- If the silicon junction gets too hot (say 125 °C), then the activity is reduced (e.g., reduce clock rate or use clock gating)

Use of Thermal Feedback

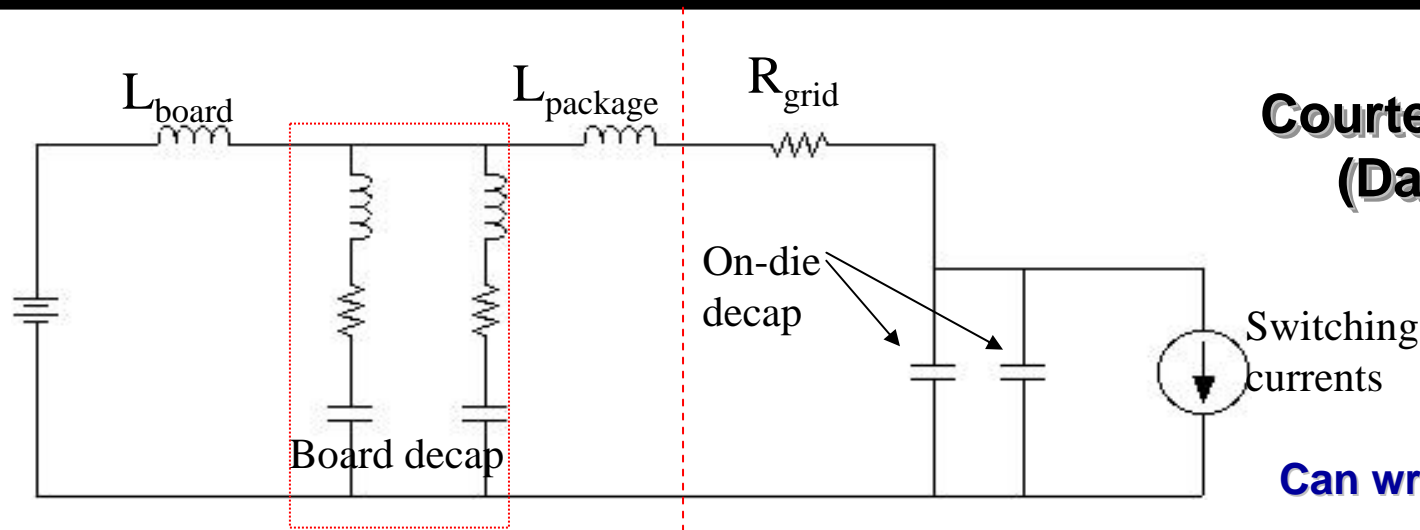


Courtesy of Motorola
(David Blaauw)

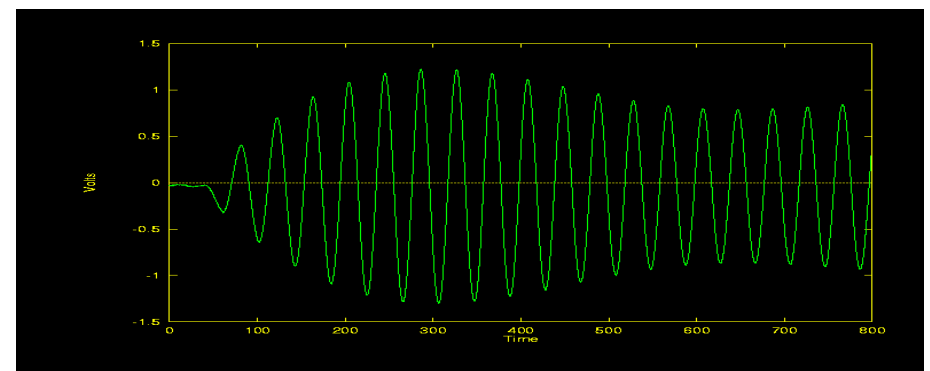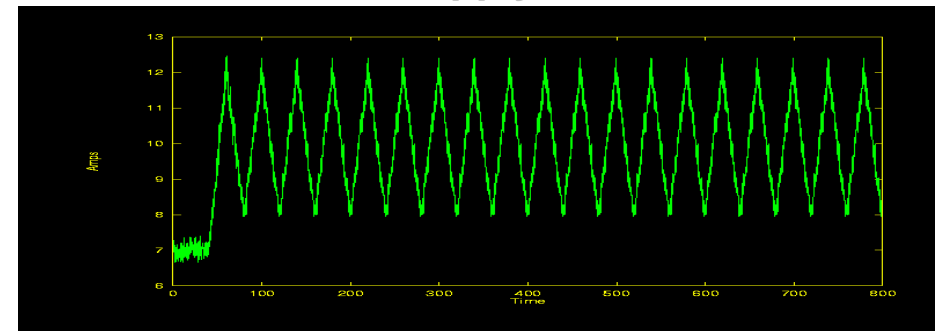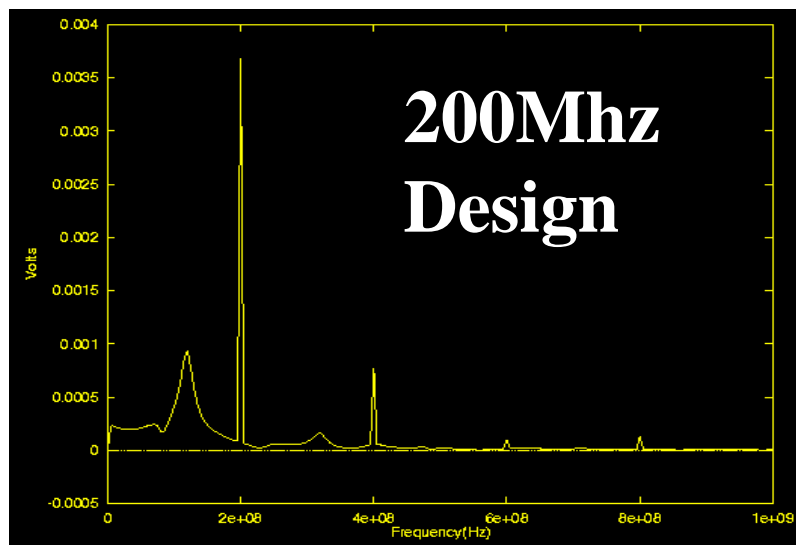Can write a Virus to Activate
Power Supply Resonance!




Number Representation: Two's Complement vs. Sign Magnitude


Two's complement

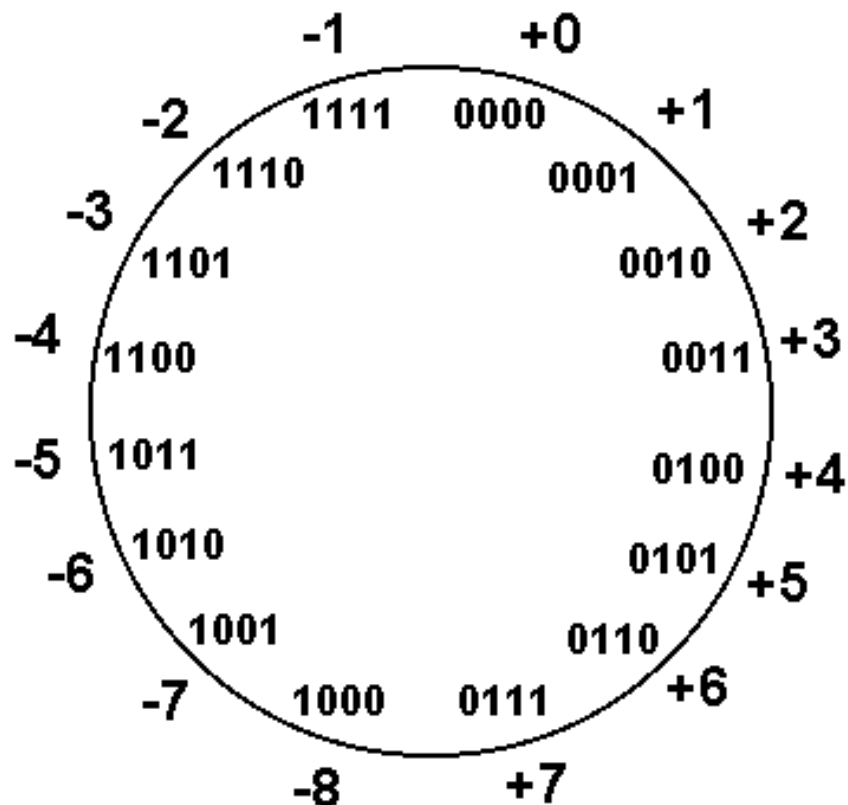

Sign-Magnitude


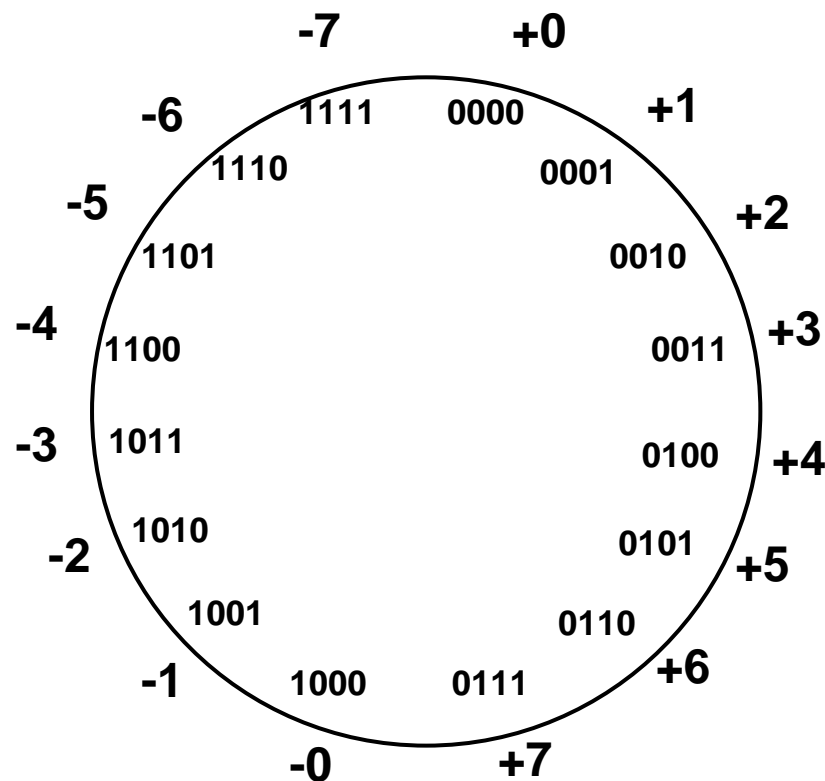


Consider a 16 bit bus where inputs toggles between +1 and -1 (i.e., a small noise input)
Which representation is more energy efficient?


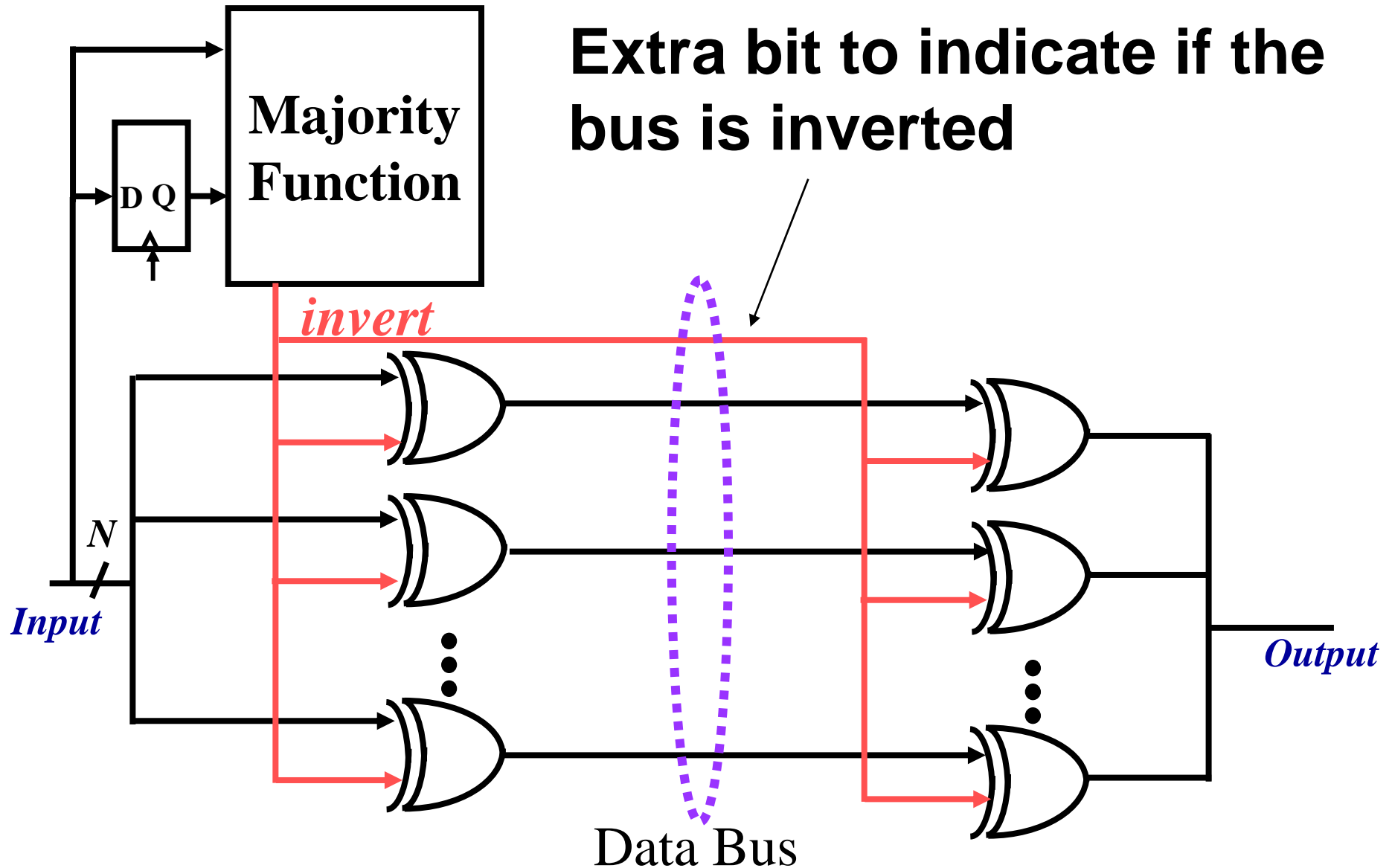


[Stan94]


Parallel busses for I,Q

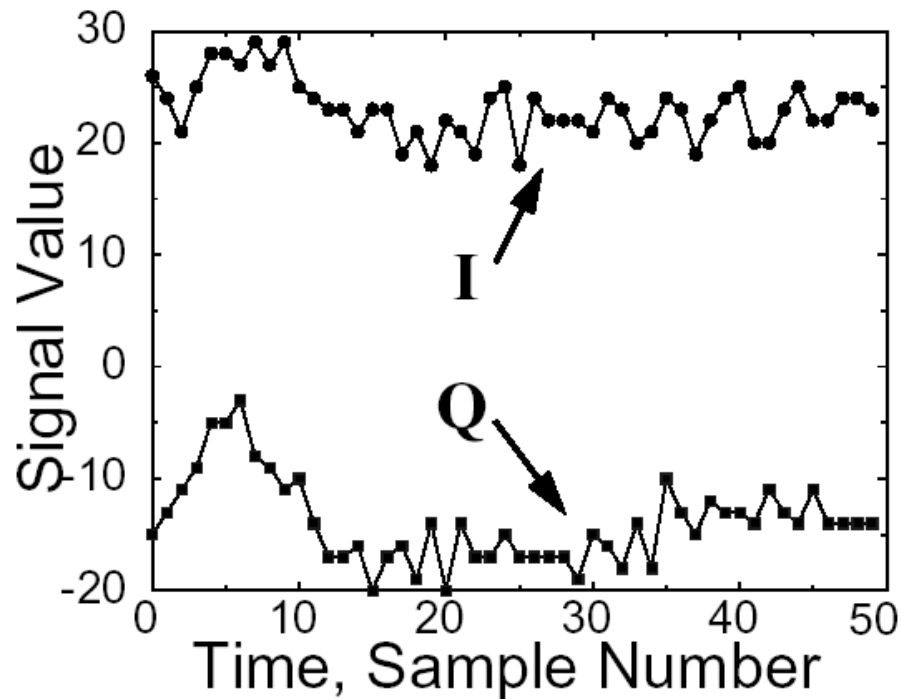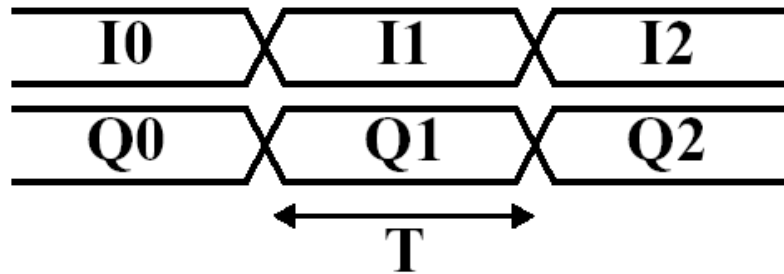

Time-shared bus for I,Q

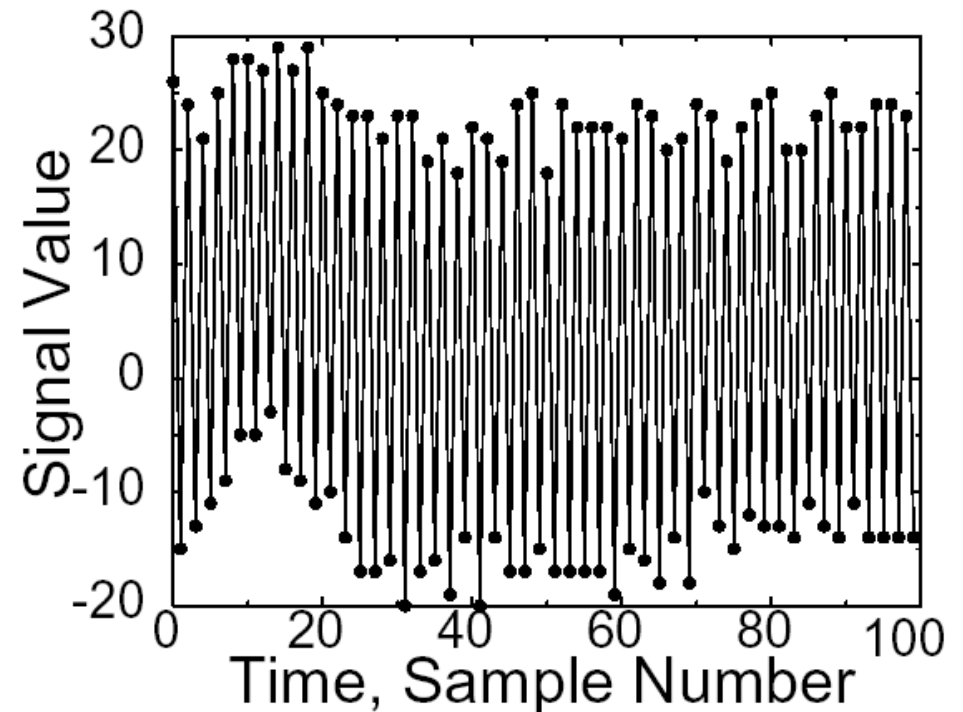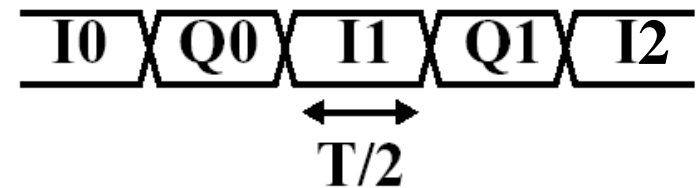

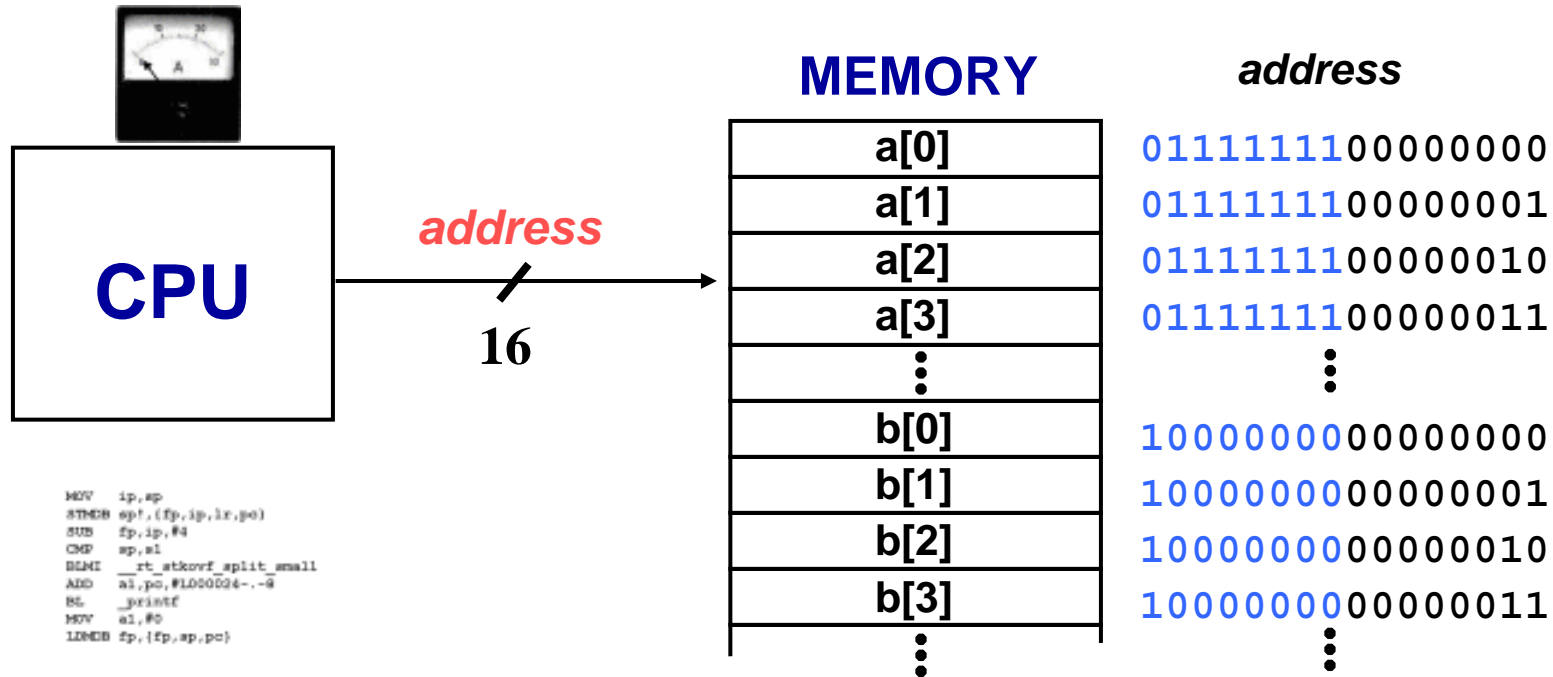Time Sharing Increases Switching Activity



float a [256], b[256];
float pi= 3.14;

```

for (i = 0; i < 255; i++) {
    a[i] = sin(pi * i /256);
    b[i] = cos(pi * i /256);
}
    
```

512(8)+2+4+8+16+32+64+128+256
= **4607 bit transitions**


float a [256], b[256];
float pi= 3.14;

```

for (i = 0; i < 255; i++) {a[i] = sin(pi * i /256);}
for (i = 0; i < 255; i++) {b[i] = cos(pi * i /256);}
    
```


2(8)+2(2+4+8+16+32+64+128+256)
= **1030 transitions**

Chain Topology

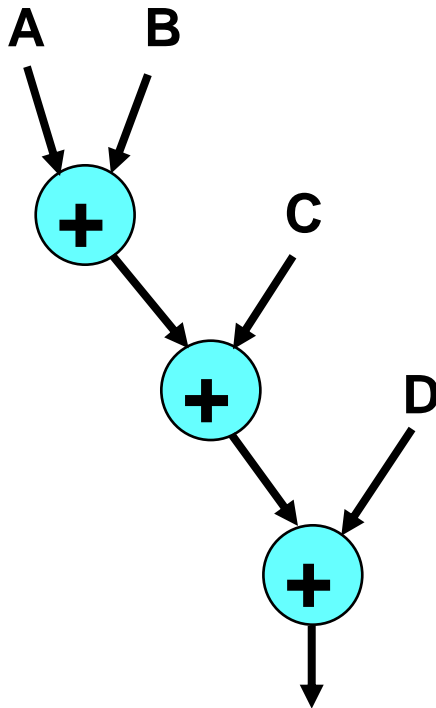



$$(((A+B) + C)+D)$$

Tree Topology

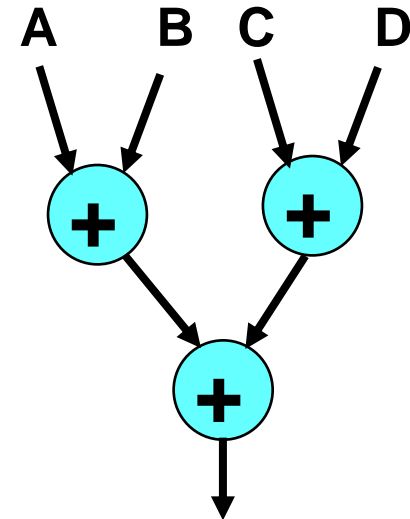

$$(A+B) + (C+D)$$

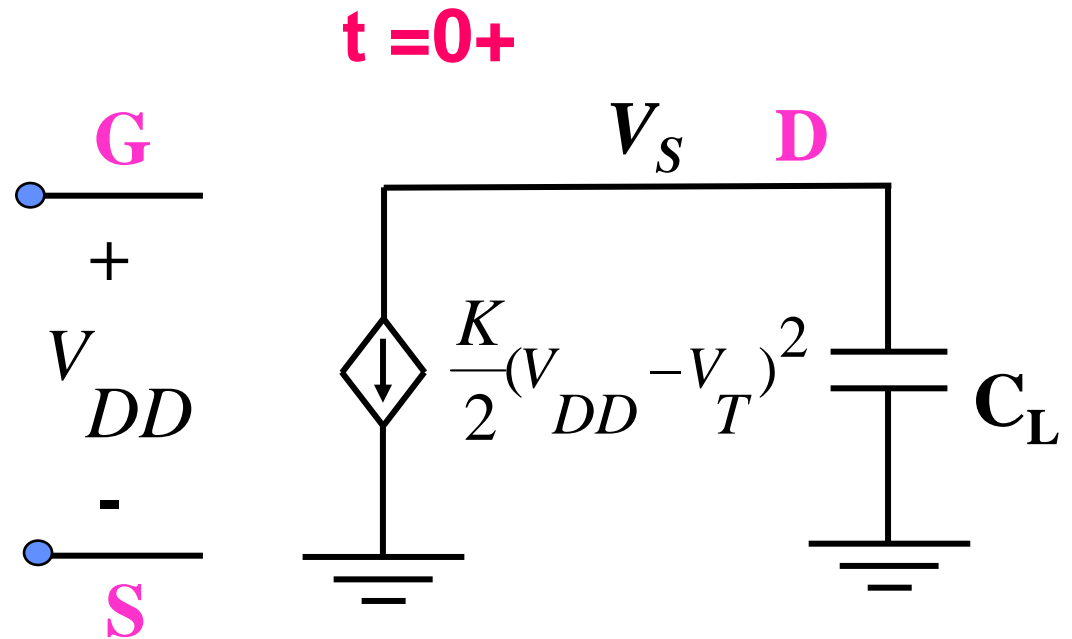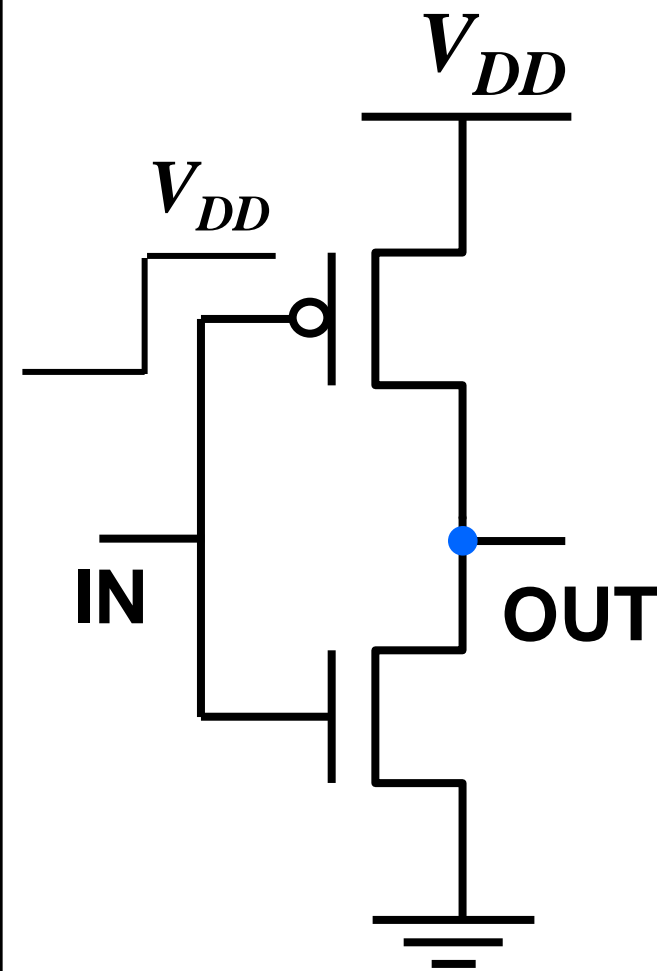- Balancing paths reduces glitching transitions
- Structures such as multipliers have lot of glitching transitions
- Keeping logic depths short (e.g., pipelining) reduces glitching




$$Delay = \frac{C_L \cdot \Delta V}{i_D} = \frac{C_L \cdot \frac{V_{DD}}{2}}{\frac{k}{2} (V_{DD} - V_T)^2} \propto \frac{V_{DD}}{(V_{DD} - V_T)^2} \approx \frac{1}{V_{DD}}$$

V_{DD} from 2V to 1V, **energy** ↓ by **x4**, **delay** ↑ **x2**

Transistors Are Free...


(What do you do with a Billion Transistors?)

$f=1\text{GHz}$
 $V_{DD}=2\text{V}$


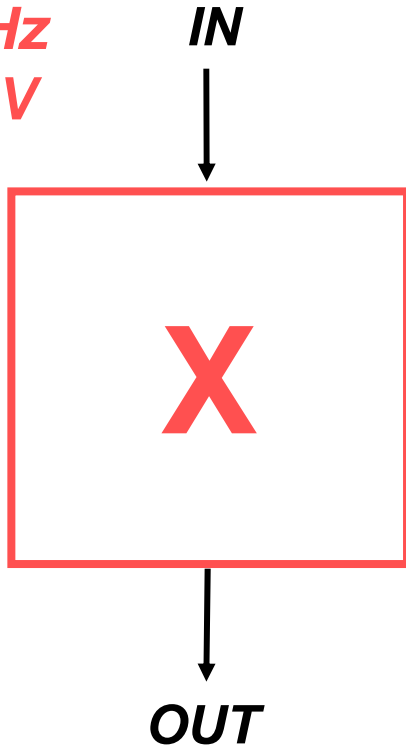


$$P_{\text{serial}} = C_{\text{mult}} 2^2 f$$

$f=500\text{Mhz}$
 $V_{DD}=1\text{V}$

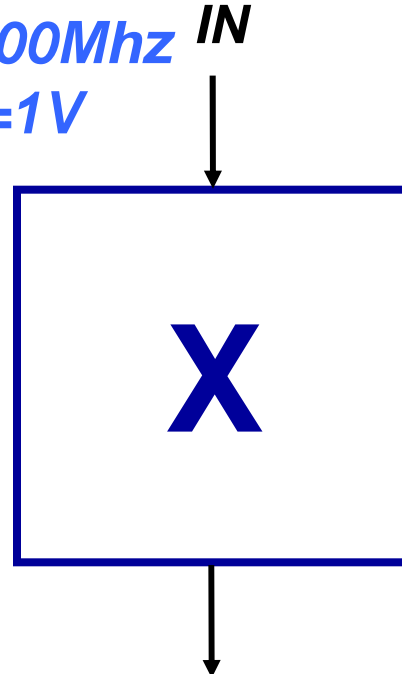


$f=500\text{Mhz}$
 $V_{DD}=1\text{V}$

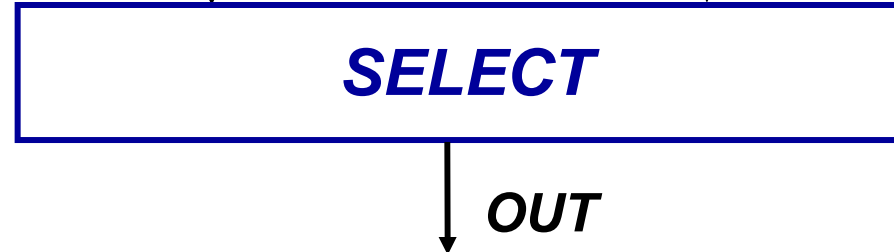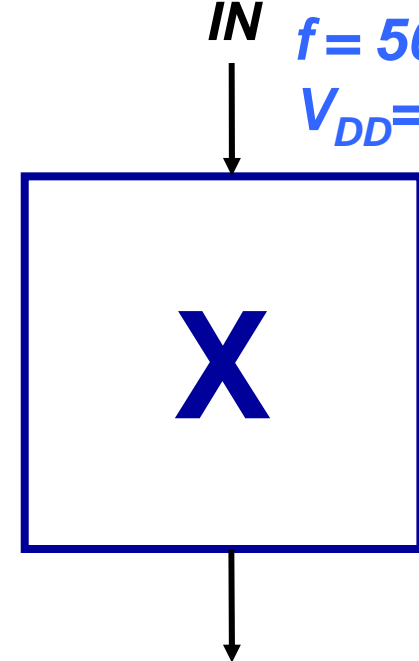

$$P_{\text{parallel}} = (2C_{\text{mult}} 1^2 f / 2) = P_{\text{serial}} / 4$$

Trade Area for Low Power

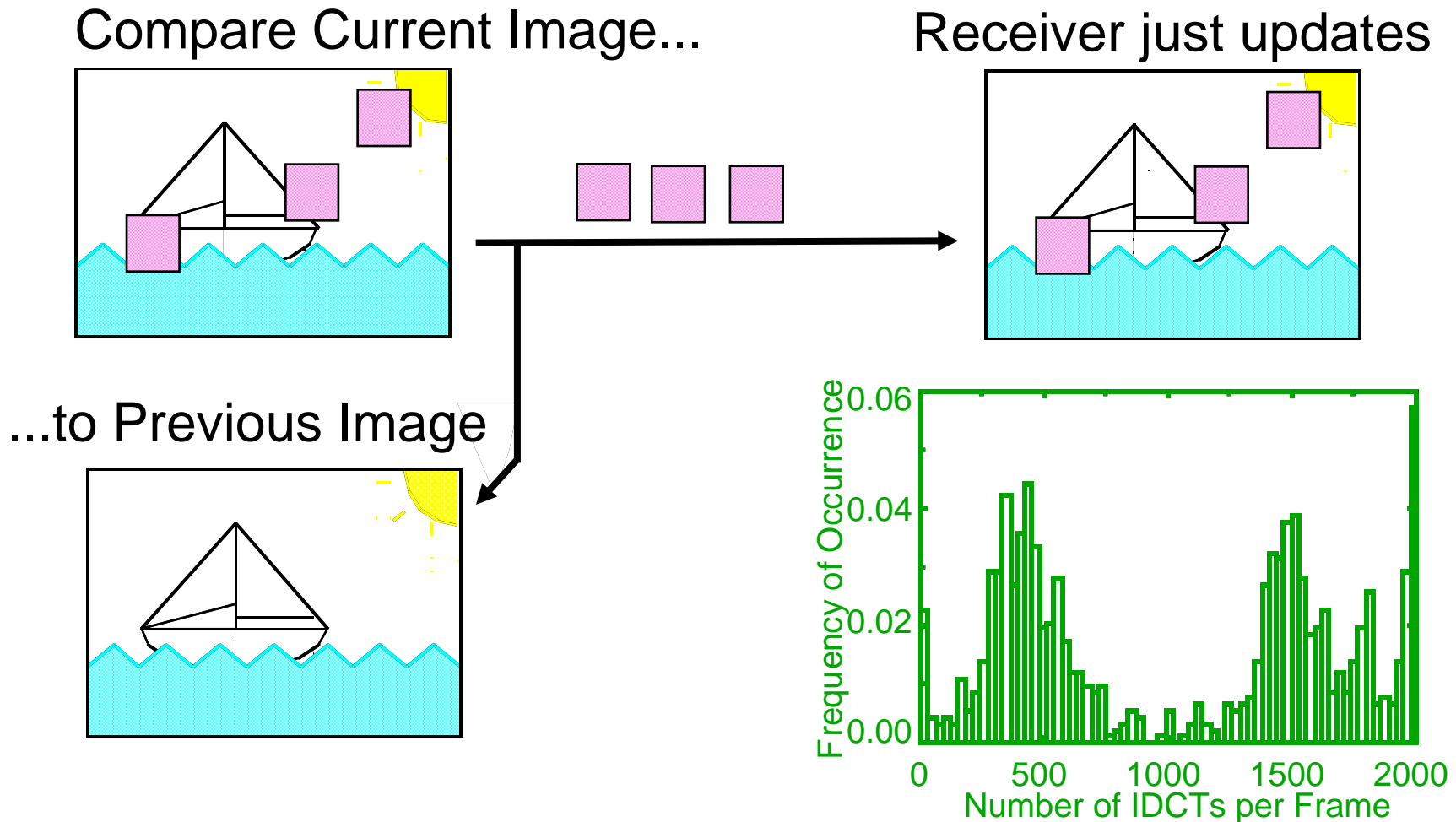

***Exploit Time Varying Algorithmic Workload
To Vary the Power Supply Voltage***

Fixed Power Supply


ACTIVE**IDLE**

$$E_{\text{FIXED}} = \frac{1}{2} C V_{\text{DD}}^2$$

Variable Power Supply

ACTIVE



$$E_{\text{VARIABLE}} = \frac{1}{2} C (V_{\text{DD}}/2)^2 = E_{\text{FIXED}} / 4$$

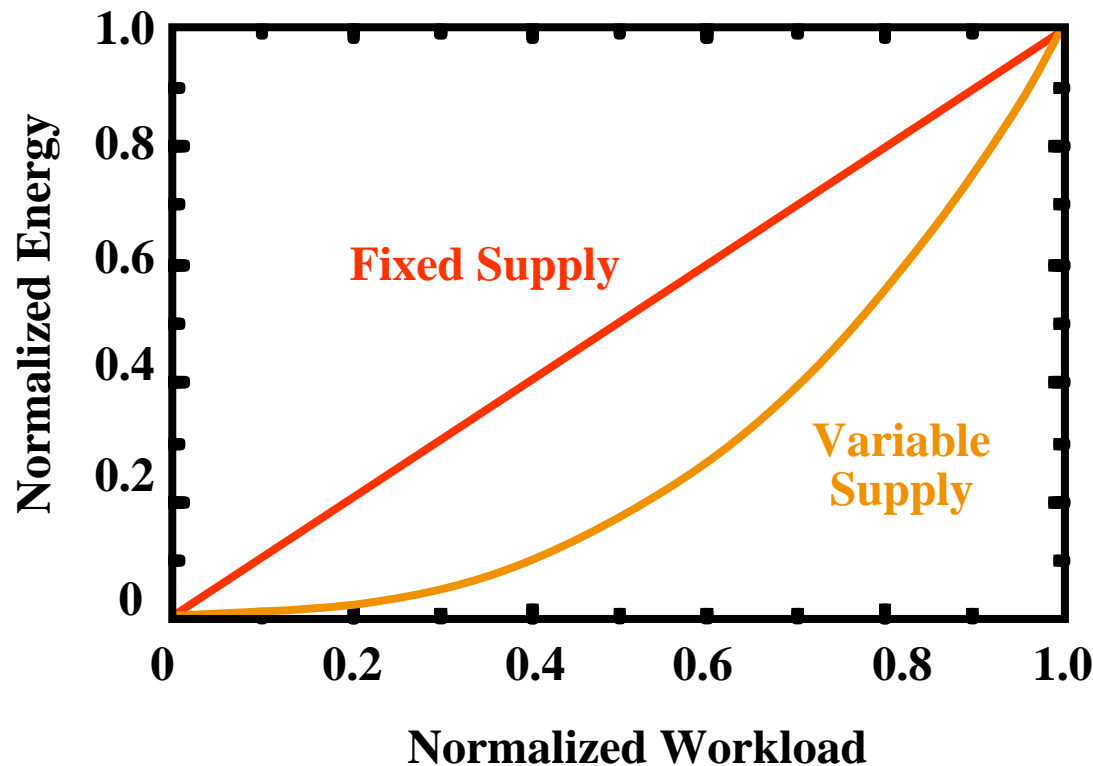


[Gutnik97]





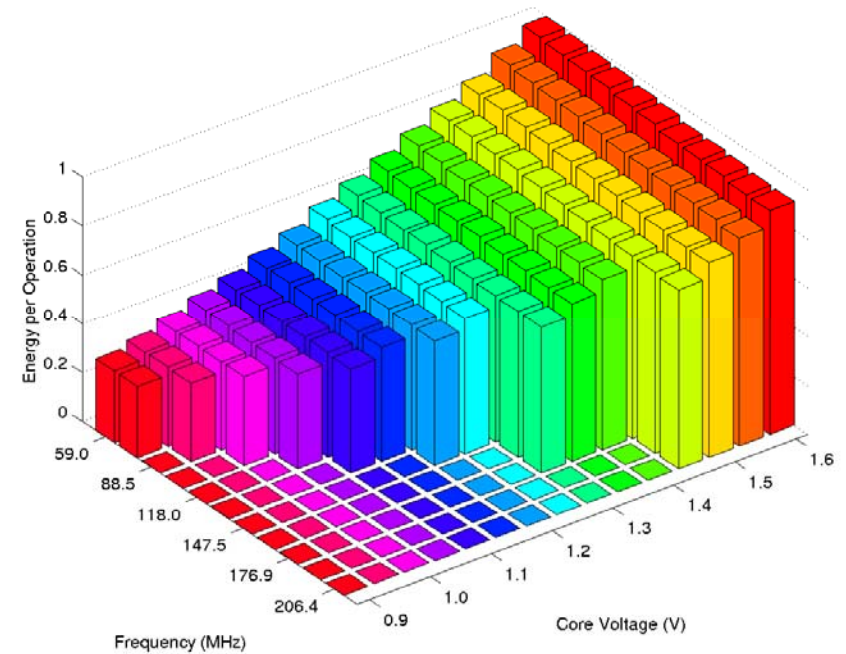
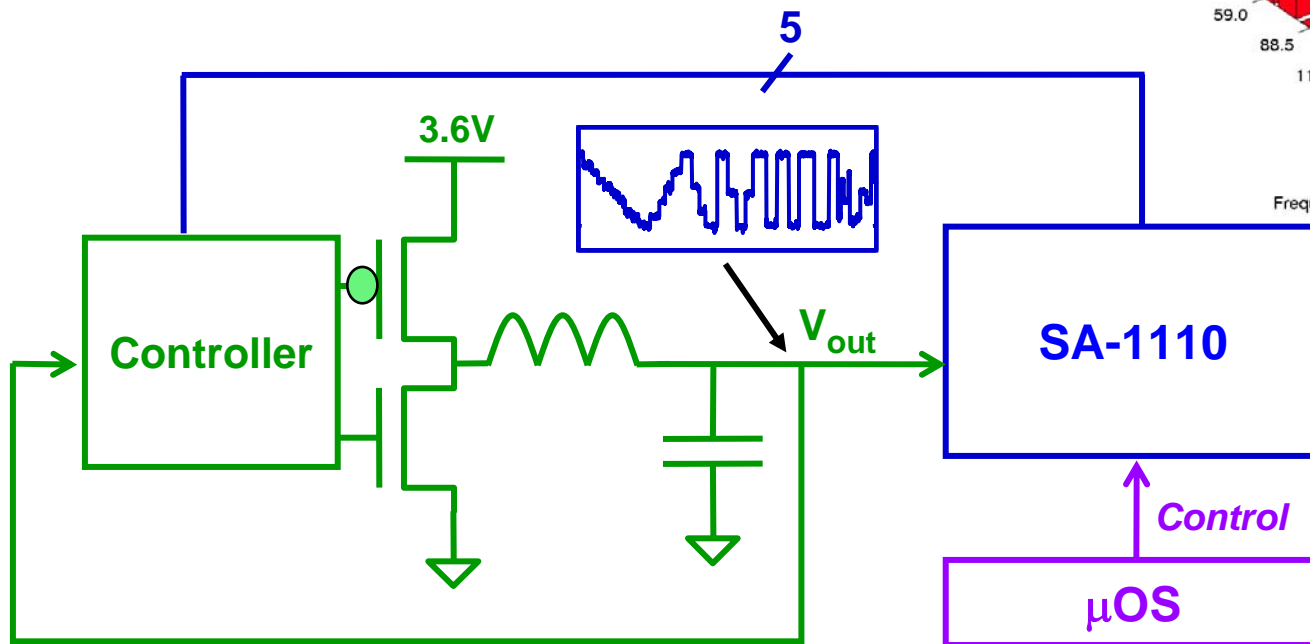
Digitally adjustable DC-DC converter powers SA-1110 core




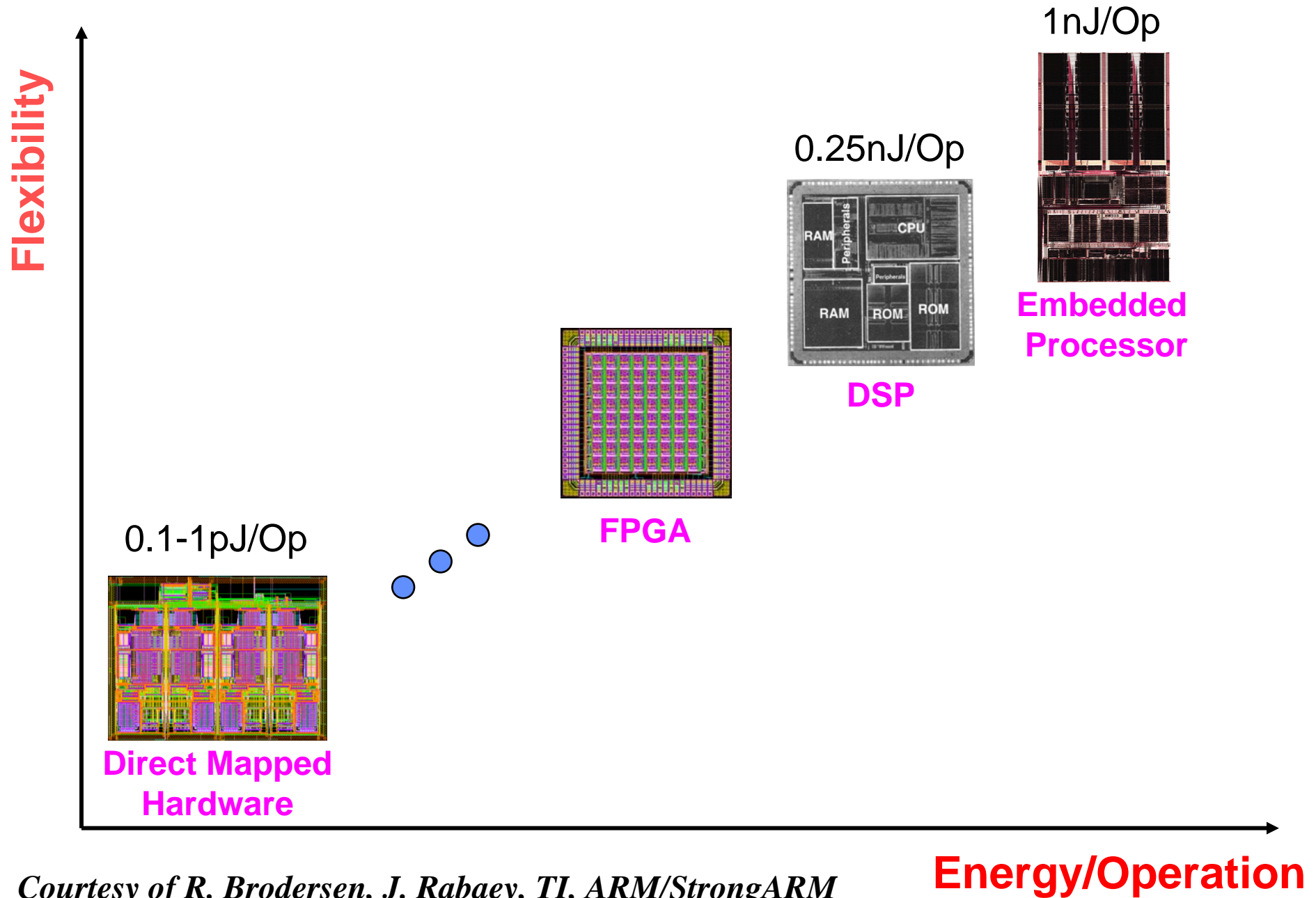
μ OS selects appropriate clock frequency based on workload and latency constraints




FPGA (Xilinx)

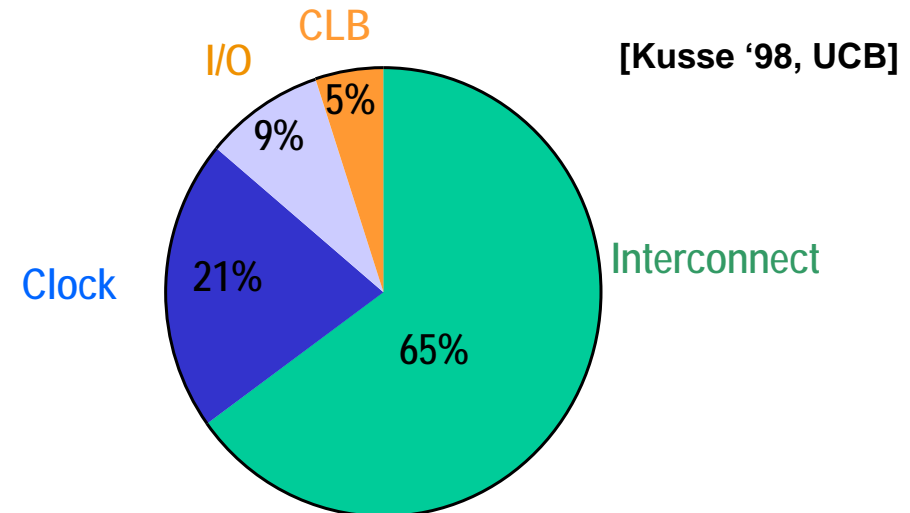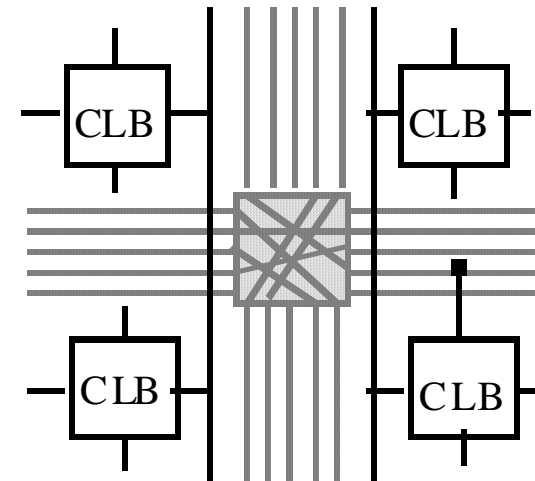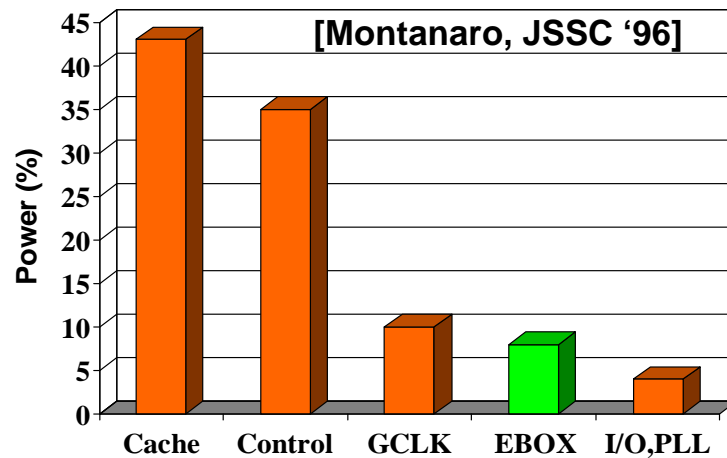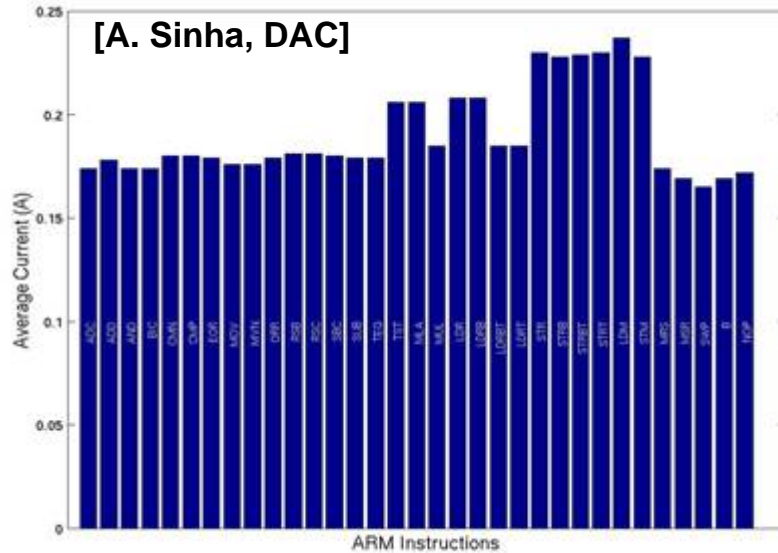

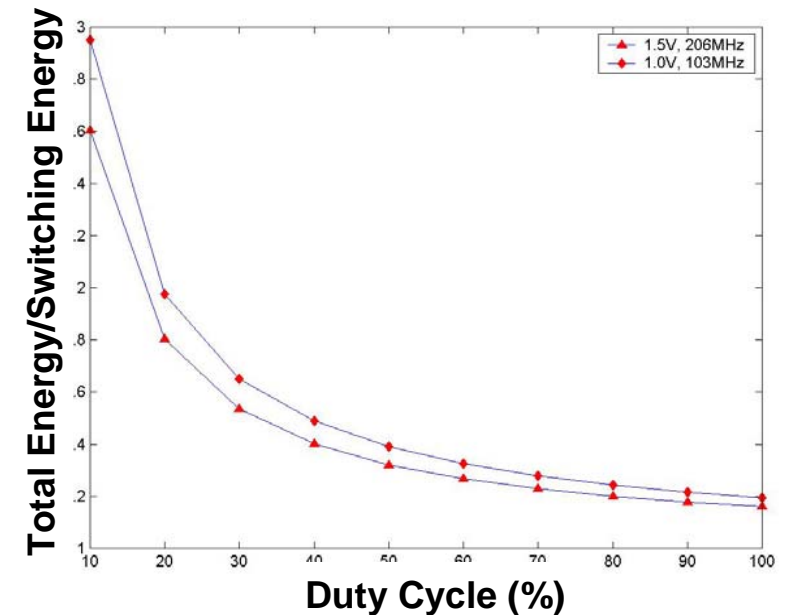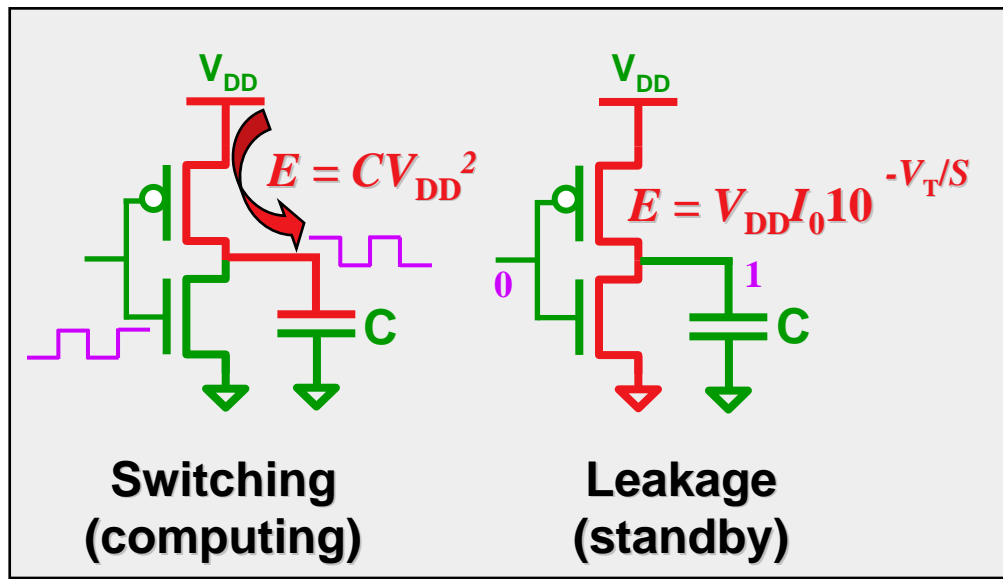“Software” Energy Dissipation has Large Overhead





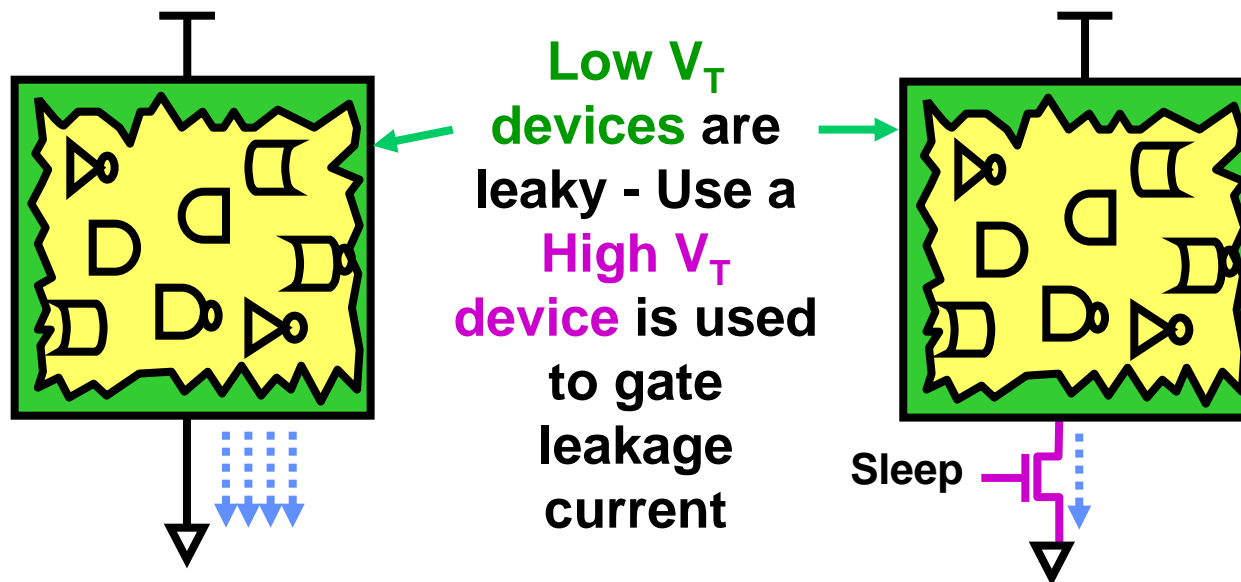In today's 65nm CMOS Technology : 30-50% of power is leakage!




Strong Inversion Operation: fast, power-hungry

$$V_{DD} = 0.18V$$

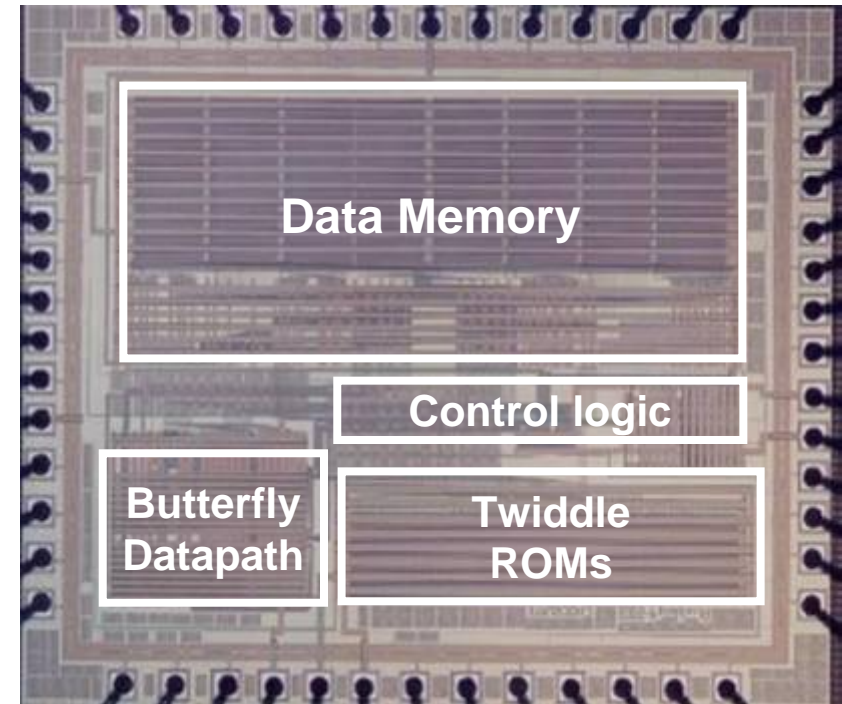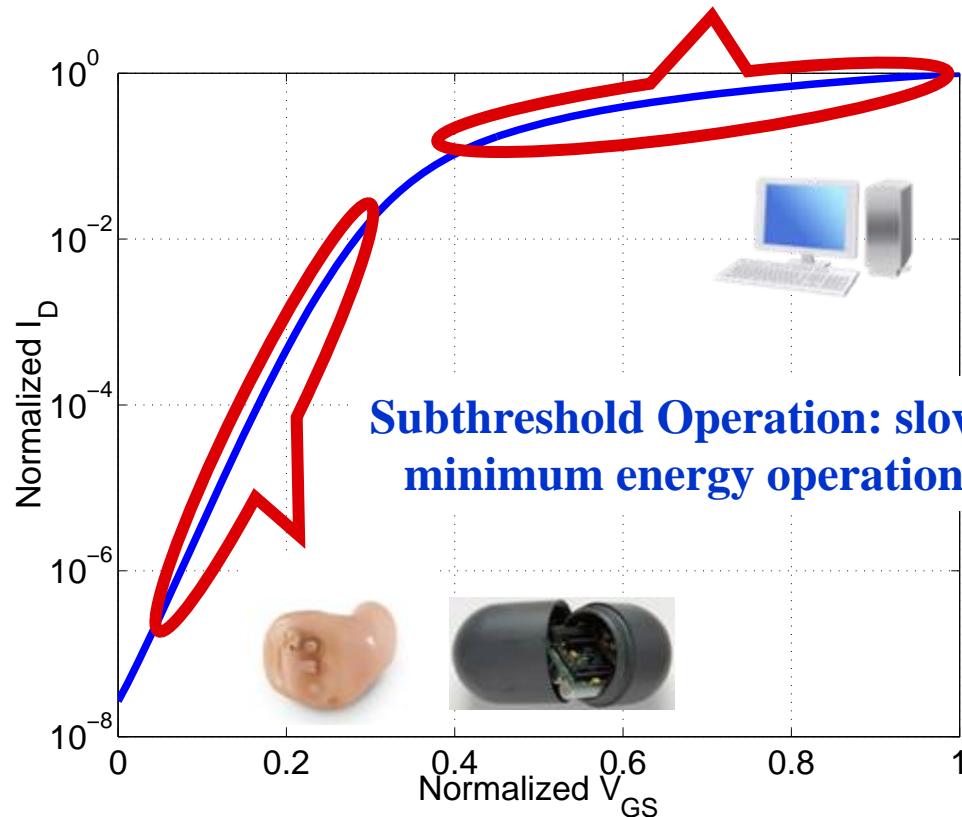

***Exploit Sub-threshold Operation ($V_{DD} < V_T$)
for Sensor Circuits***

MEMS Generator

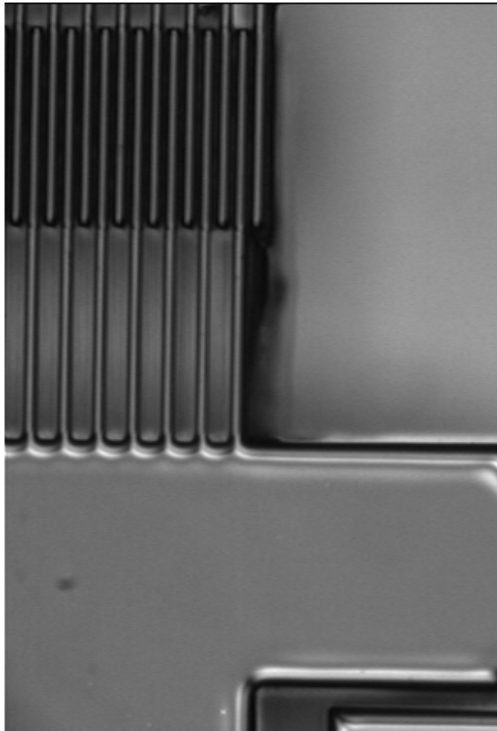

Jose Mur Miranda/
Jeff Lang

Vibration-to-Electric
Conversion

$\sim 10\mu\text{W}$

Power Harvesting Shoes



Joe Paradiso
(Media Lab)

After 3-6 steps, it provides 3 mA
for 0.5 sec

$\sim 10\text{mW}$