

L2: Combinational Logic Design


(Construction and Boolean Algebra)

Acknowledgements:

Lecture material adapted from Chapter 2 of R. Katz, G. Borriello, “*Contemporary Logic Design*” (second edition), Pearson Education, 2005.



Some lecture material adapted from J. Rabaey, A. Chandrakasan, B. Nikolic, “*Digital Integrated Circuits: A Design Perspective*” Copyright 2003 Prentice Hall/Pearson.

 Lecture Based on Notes by Professor Anantha Chandrakasan



Truth Table






IN	OUT
0	1
1	0

  



$$NM_L = V_{IL} - V_{OL}$$

$$NM_H = V_{OH} - V_{IH}$$

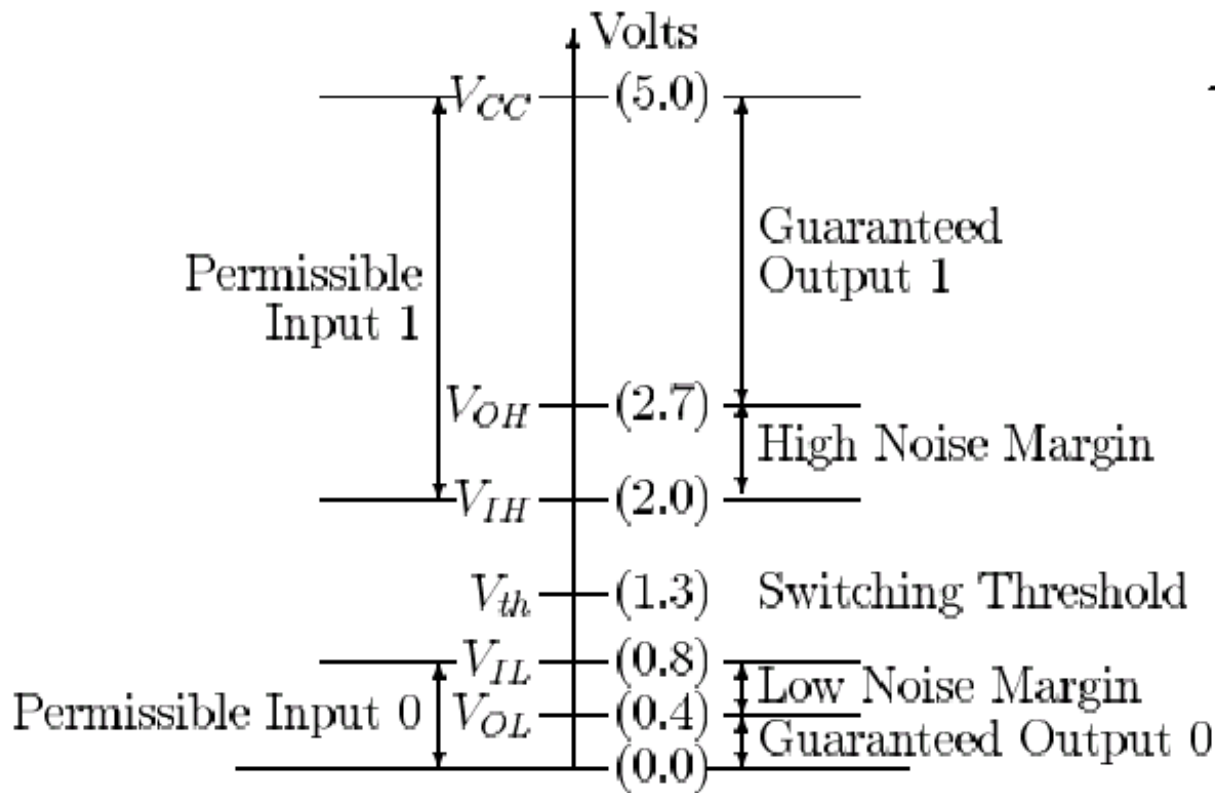    - Large noise margins protect against various noise sources




74LS04
(courtesy TI)

  


Switch Model




OFF

 



ON

 



NMOS ON when Switch Input is High

   

  - **MOS is a very non-linear.**
- **Switch-resistor model sufficient for first order analysis.**





Switch Model


 
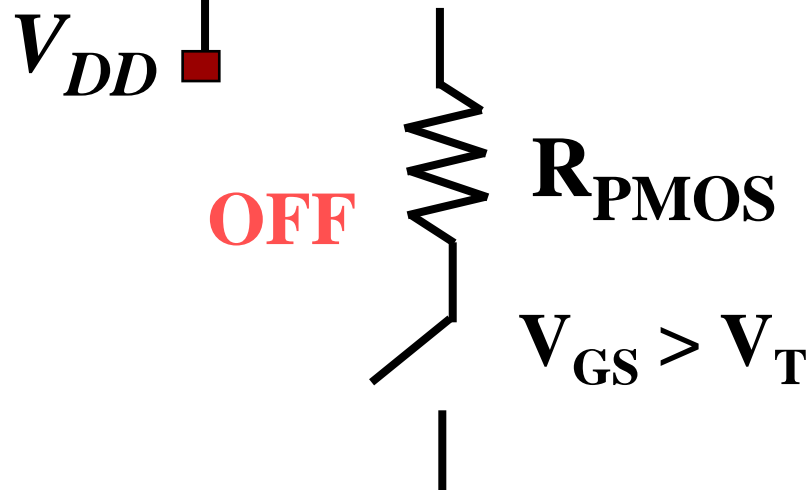


PMOS ON when Switch Input is Low

Switch Model

  


Rail-to-rail Swing in CMOS

  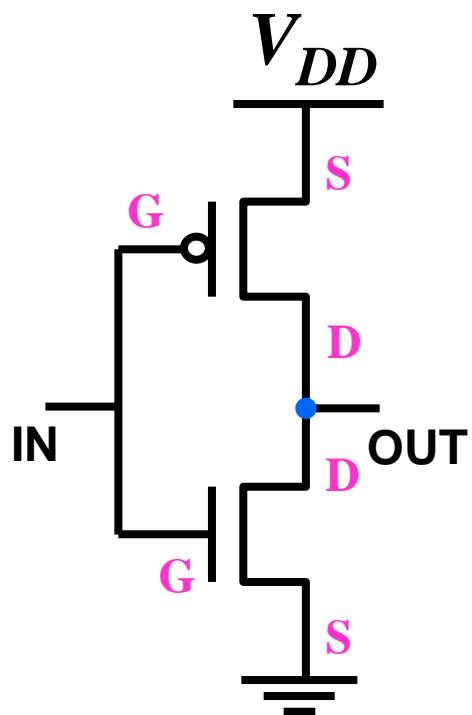

CMOS gates have:

- Rail-to-rail swing (0V to V_{DD})
- Large noise margins
- **“zero” static power dissipation**

 There are 16 possible functions of 2 input variables:



X	Y	16 possible functions (F_0 – F_{15})																
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	1

Labels for functions (indicated by lines pointing to specific output columns):
 - Column 2: 0 → X AND Y
 - Column 4: 1 → X
 - Column 6: 1 → Y
 - Column 8: 0 → X XOR Y
 - Column 10: 0 → X OR Y
 - Column 11: 0 → X NOR Y
 - Column 12: 1 → NOT (X OR Y)
 - Column 13: 0 → X = Y
 - Column 14: 0 → NOT Y
 - Column 15: 1 → NOT X
 - Column 17: 0 → X NAND Y
 - Column 18: 1 → NOT (X AND Y)

In general, there are $2^{(2^n)}$ functions of n inputs


Gate

Symbol

Truth-Table

Expression


NAND

 

X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

$$Z = \overline{X \cdot Y}$$


AND

 

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

$$Z = X \cdot Y$$


NOR

 

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0

$$Z = \overline{X + Y}$$


OR

 

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

$$Z = X + Y$$


XOR
($X \oplus Y$)

 

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0

$Z = X \bar{Y} + \bar{X} Y$
X or Y but not both
("inequality", "difference")


XNOR
($X \oplus Y$)

 


X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	1

$Z = \bar{X} \bar{Y} + X Y$
X and Y the same
("equality")

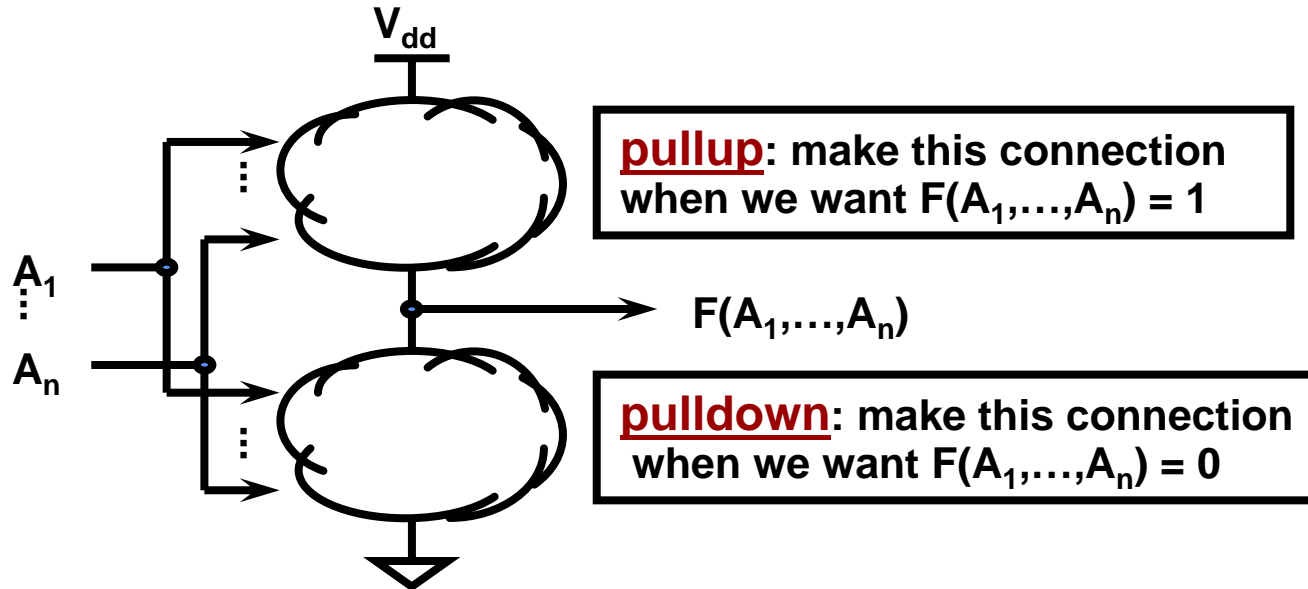Widely used in arithmetic structures such as adders and multipliers



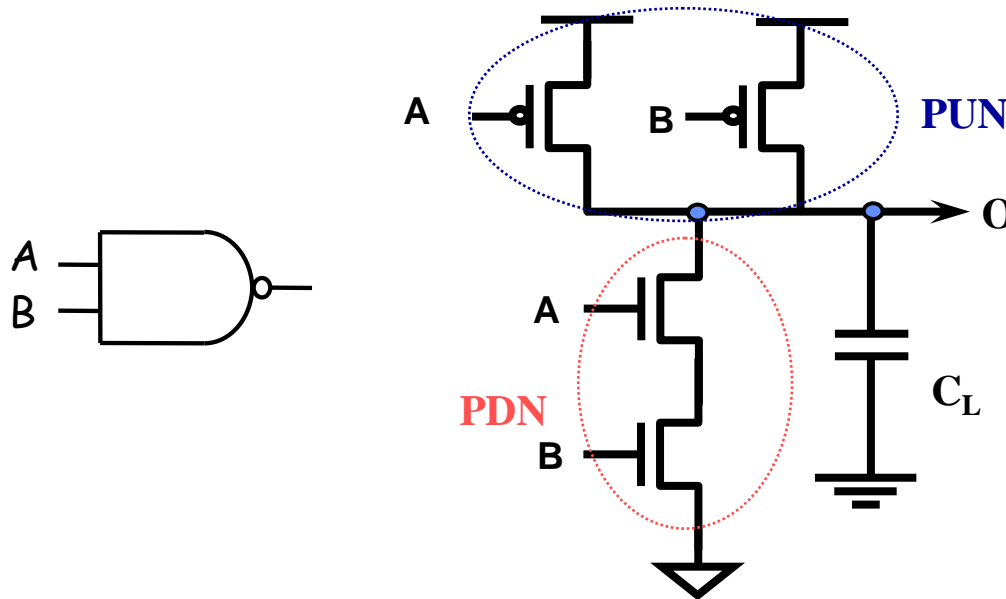Note: CMOS gates result in inverting functions!
 (easier to build NAND vs. AND)



A	B	PDN	PUN	O
0	0	Off	On	1
0	1	Off	On	1
1	0	Off	On	1
1	1	On	Off	0

How do you build a 2-input NOR Gate?

■ Elementary

$$1. X + 0 = X$$

$$2. X + 1 = 1$$

$$3. X + X = X$$

$$4. \overline{\overline{X}} = X$$

$$5. X + \overline{X} = 1$$

$$1D. X \cdot 1 = X$$

$$2D. X \cdot 0 = 0$$

$$3D. X \cdot X = X$$

$$5D. X \cdot \overline{X} = 0$$

■ Commutativity:

$$6. X + Y = Y + X$$

$$6D. X \cdot Y = Y \cdot X$$

■ Associativity:

$$7. (X + Y) + Z = X + (Y + Z)$$

$$7D. (X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$$

■ Distributivity:

$$8. X \cdot (Y + Z) = (X \cdot Y) + (X \cdot Z)$$

$$8D. X + (Y \cdot Z) = (X + Y) \cdot (X + Z)$$

■ Uniting:

$$9. X \cdot Y + X \cdot \overline{Y} = X$$

$$9D. (X + Y) \cdot (X + \overline{Y}) = X$$

■ Absorption:

$$10. X + X \cdot Y = X$$

$$10D. X \cdot (X + Y) = X$$

$$11. (X + \overline{Y}) \cdot Y = X \cdot Y$$

$$11D. (X \cdot \overline{Y}) + Y = X + Y$$

■ Factoring:

$$12. (X \cdot Y) + (X \cdot Z) = X \cdot (Y + Z)$$

$$12D. (X + Y) \cdot (X + Z) = X + (Y \cdot Z)$$

■ Consensus:

$$13. (X \cdot Y) + (Y \cdot Z) + (\bar{X} \cdot Z) = X \cdot Y + \bar{X} \cdot Z$$

$$13D. (X + Y) \cdot (Y + Z) \cdot (\bar{X} + Z) = (X + Y) \cdot (\bar{X} + Z)$$

■ De Morgan's:

$$14. \overline{(X + Y + \dots)} = \bar{X} \cdot \bar{Y} \cdot \dots$$

$$14D. \overline{(X \cdot Y \cdot \dots)} = \bar{X} + \bar{Y} + \dots$$

■ Generalized De Morgan's:

$$15. \overline{f(X_1, X_2, \dots, X_n, 0, 1, +, \cdot)} = f(\bar{X}_1, \bar{X}_2, \dots, \bar{X}_n, 1, 0, \cdot, +)$$


■ Duality

□ Dual of a Boolean expression is derived by replacing \cdot by $+$, $+$ by \cdot , 0 by 1, and 1 by 0, and leaving variables unchanged

$$\square f(X_1, X_2, \dots, X_n, 0, 1, +, \cdot) \Leftrightarrow f(X_1, X_2, \dots, X_n, 1, 0, \cdot, +)$$

■ 1-bit binary adder

 - inputs: A, B, Carry-in
- outputs: Sum, Carry-out



A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Sum-of-Products Canonical Form

$$S = \bar{A} \bar{B} C_{in} + \bar{A} B \bar{C}_{in} + A \bar{B} \bar{C}_{in} + A B C_{in}$$

$$C_{out} = \bar{A} B C_{in} + A \bar{B} C_{in} + A B \bar{C}_{in} + A B C_{in}$$

■ Product term (or minterm)

- ANDed product of literals – input combination for which output is true
- Each variable appears exactly once, in true or inverted form (but not both)

$$\begin{aligned}
 \text{Cout} &= \overline{A} B C_{in} + A \overline{B} C_{in} + A B \overline{C_{in}} + A B C_{in} \\
 &= \overline{A} B C_{in} + A B C_{in} + A \overline{B} C_{in} + A B C_{in} + A B \overline{C_{in}} + A B C_{in} \\
 &= (\overline{A} + A) B C_{in} + A (\overline{B} + B) C_{in} + A B (\overline{C_{in}} + C_{in}) \\
 &= B C_{in} + A C_{in} + A B \\
 &= (B + A) C_{in} + A B
 \end{aligned}$$

$$\begin{aligned}
 S &= \overline{A} \overline{B} C_{in} + \overline{A} B \overline{C_{in}} + A \overline{B} \overline{C_{in}} + A B C_{in} \\
 &= (\overline{A} \overline{B} + A B) C_{in} + (A \overline{B} + \overline{A} B) \overline{C_{in}} \\
 &= \overline{(A \oplus B)} C_{in} + (A \oplus B) \overline{C_{in}} \\
 &= A \oplus B \oplus C_{in}
 \end{aligned}$$

- Product term** (or minterm): ANDed product of literals – input combination for which output is true

A	B	C	minterms	
0	0	0	$\overline{A} \overline{B} \overline{C}$	m0
0	0	1	$\overline{A} \overline{B} C$	m1
0	1	0	$\overline{A} B \overline{C}$	m2
0	1	1	$\overline{A} B C$	m3
1	0	0	$A \overline{B} \overline{C}$	m4
1	0	1	$A \overline{B} C$	m5
1	1	0	$A B \overline{C}$	m6
1	1	1	$A B C$	m7

short-hand notation form in terms of 3 variables

F in canonical form:

$$F(A, B, C) = \sum m(1,3,5,6,7)$$

$$= m1 + m3 + m5 + m6 + m7$$

$$F = \overline{A} \overline{B} C + \overline{A} B \overline{C} + A \overline{B} C + A B \overline{C} + ABC$$

canonical form \neq minimal form

$$F(A, B, C) = \overline{A} \overline{B} C + \overline{A} B \overline{C} + A \overline{B} C + ABC + ABC \overline{C}$$

$$= (\overline{A} \overline{B} + \overline{A} B + A \overline{B} + AB)C + ABC \overline{C}$$

$$= ((\overline{A} + A)(\overline{B} + B))C + ABC \overline{C}$$

$$= C + ABC \overline{C} = ABC \overline{C} + C = AB + C$$

- Sum term** (or maxterm) - ORed sum of literals – input combination for which output is false

A	B	C	maxterms	
0	0	0	$A + B + C$	M0
0	0	1	$A + B + \overline{C}$	M1
0	1	0	$A + \overline{B} + C$	M2
0	1	1	$A + \overline{B} + \overline{C}$	M3
1	0	0	$\overline{A} + B + C$	M4
1	0	1	$\overline{A} + B + \overline{C}$	M5
1	1	0	$\overline{A} + \overline{B} + C$	M6
1	1	1	$\overline{A} + \overline{B} + \overline{C}$	M7

short-hand notation for maxterms of 3 variables

F in canonical form:

$$F(A, B, C) = \prod M(0,2,4)$$

$$= M0 \cdot M2 \cdot M4$$

$$= (A + B + C) (A + \overline{B} + C) (\overline{A} + B + C)$$

canonical form \neq minimal form


$$F(A, B, C) = (A + B + C) (A + \overline{B} + C) (\overline{A} + B + C)$$

$$= (A + B + C) (A + \overline{B} + C)$$





$$(A + B + C) (\overline{A} + B + C)$$

$$= (A + C) (B + C)$$

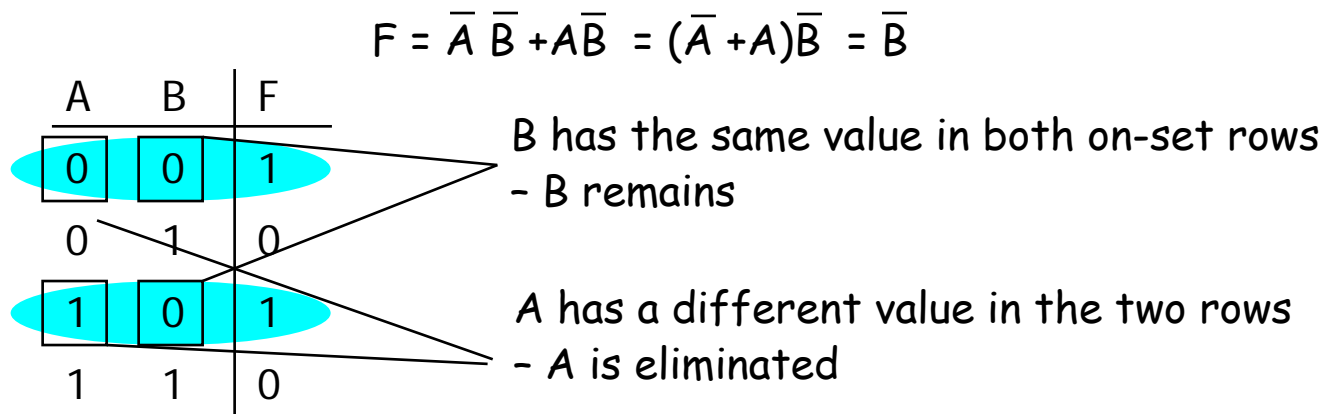- Key tool to simplification: $A(\bar{B} + B) = A$
- Essence of simplification of two-level logic
 - Find two element subsets of the ON-set where only one variable changes its value – this single varying variable can be eliminated and a single product term used to represent both elements



    
- Just another way to represent truth table
- Visual technique for identifying when the uniting theorem can be applied
- n input variables = n -dimensional "cube"



Mapping Truth Tables onto Boolean Cubes

■ Uniting theorem

A	B	F
0	0	1
0	1	0
1	0	1
1	1	0

 

Circled group of the on-set is called the *adjacency plane*. Each adjacency plane corresponds to a product term.

ON-set = solid nodes
OFF-set = empty nodes


A varies within face, B does not
this face represents the literal \bar{B}

■ Three variable example: Binary full-adder carry-out logic

A	B	Cin	Cout
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$(\bar{A}+A)BCin$$


$$AB(\bar{Cin}+Cin)$$

 

$$Cout = BCin + AB + ACin$$

$$A(B+\bar{B})Cin$$

 The on-set is completely covered by the combination (OR) of the subcubes of lower dimensionality - note that "111" is covered three times



$$F(A,B,C) = \sum m(4,5,6,7)$$

on-set forms a square
i.e., a cube of dimension 2 (2-D adjacency plane)

represents an expression in one variable
i.e., 3 dimensions - 2 dimensions

A is asserted (true) and unchanged
B and C vary

This subcube represents the literal A

■ In a 3-cube (three variables):

- 0-cube, i.e., a single node, yields a term in 3 literals
- 1-cube, i.e., a line of two nodes, yields a term in 2 literals
- 2-cube, i.e., a plane of four nodes, yields a term in 1 literal
- 3-cube, i.e., a cube of eight nodes, yields a constant term "1"

■ In general,

- m-subcube within an n-cube ($m < n$) yields a term with $n - m$ literals

- Alternative to truth-tables to help visualize adjacencies
 - Guide to applying the uniting theorem - On-set elements with only one variable changing value are adjacent unlike in a linear truth-table

	A	0	1
B		0	1
0		0	1
1		1	3

A	B	F
0	0	1
0	1	0
1	0	1
1	1	0

- Numbering scheme based on Gray-code

- e.g., 00, 01, 11, 10 (only a single bit changes in code for adjacent map cells)

2-variable K-map


	A	0	1
B		0	1
0		0	2
1		1	3

3-variable K-map


		AB	00	01	11	10
C			0	1	6	4
0			0	2	6	4
1			1	3	7	5

		AB	00	01	11	10
CD			00	01	11	10
00			0	4	12	8
01			1	5	13	9
11			3	7	15	11
10			2	6	14	10

4-variable K-map

 


Cout =

 


$$F(A,B,C) = \sum m(0,4,5,7)$$

F =

 


F(A,B,C) =

 

F' simply replace 1's with 0's and vice versa

$$F'(A,B,C) = \sum m(1,2,3,6)$$


F' =

 

$$F(A,B,C,D) = \Sigma m(0,2,3,5,6,7,8,10,11,14,15)$$

$$F = C + \bar{A} B D + \bar{B} \bar{D}$$

 Find the smallest number of the largest possible subcubes that cover the ON-set



K-map Corner Adjacency Illustrated in the 4-Cube

Don't Cares can be treated as 1's or 0's if it is advantageous to do so

AB		A			
		00	01	11	10
CD	00	0	0	X	0
	01	1	1	X	1
	11	1	1	0	0
	10	0	X	0	0

Annotations: A bracket above the 11 and 10 columns; a bracket below the 01 and 11 columns; a bracket to the right of the 01 and 11 rows; a bracket to the left of the 11 and 10 rows.

$$F(A,B,C,D) = \sum m(1,3,5,7,9) + \sum d(6,12,13)$$

$$F = \bar{A} D + \bar{B} \bar{C} D \text{ w/o don't cares}$$

$$F = \bar{C} D + \bar{A} D \text{ w/ don't cares}$$

By treating this DC as a "1", a 2-cube can be formed rather than one 0-cube

In PoS form: $F = D (\bar{A} + \bar{C})$


Equivalent answer as above,
but fewer literals

AB		A			
		00	01	11	10
CD	00	0	0	X	0
	01	1	1	X	1
	11	1	1	0	0
	10	0	X	0	0

Annotations: A bracket above the 11 and 10 columns; a bracket below the 01 and 11 columns; a bracket to the right of the 01 and 11 rows; a bracket to the left of the 11 and 10 rows.


Static Hazards: Consider this function:

$$F = A * \bar{C} + B * C$$

 


		AB			
		00	01	11	10
C	0	0	0	1	1
	1	0	1	1	0


$A = B = 1$

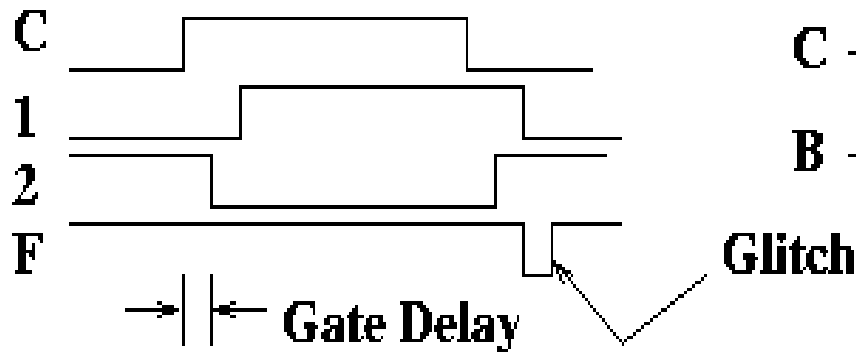

Implemented with MSI gates:

 

 The glitch is the result of timing differences in parallel data paths. It is associated with the function jumping between groupings or product terms on the K-map. To fix it, cover it up with another grouping or product term!



		AB			
		00	01	11	10
C	0	0	0	1	1
	1	0	1	1	0

$$F = A * \bar{C} + B * C + A * B$$

- In general, it is difficult to avoid hazards – need a robust design methodology to deal with hazards.