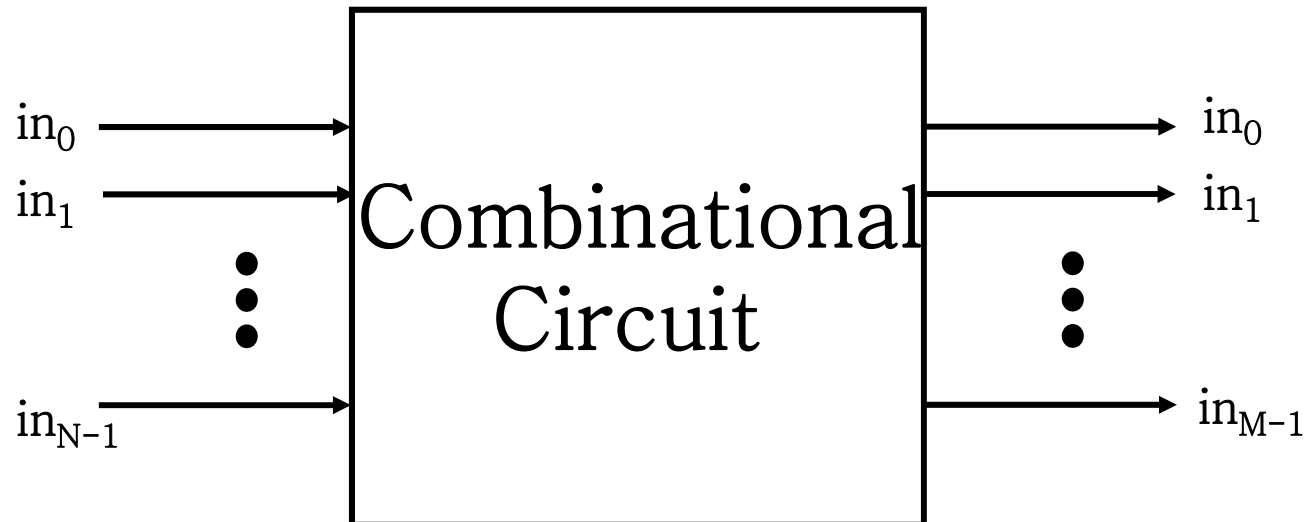



L4: Sequential Building Blocks (Flip-flops, Latches and Registers)

Acknowledgements:

- Lecture material adapted from R. Katz, G. Borriello, “Contemporary Logic Design” (second edition), Prentice-Hall/Pearson Education, 2005.
- Lecture material adapted from J. Rabaey, A. Chandrakasan, B. Nikolic, “Digital Integrated Circuits: A Design Perspective” Copyright 2003 Prentice Hall/Pearson.
- Lecture notes prepared by Professor Anantha Chandrakasan




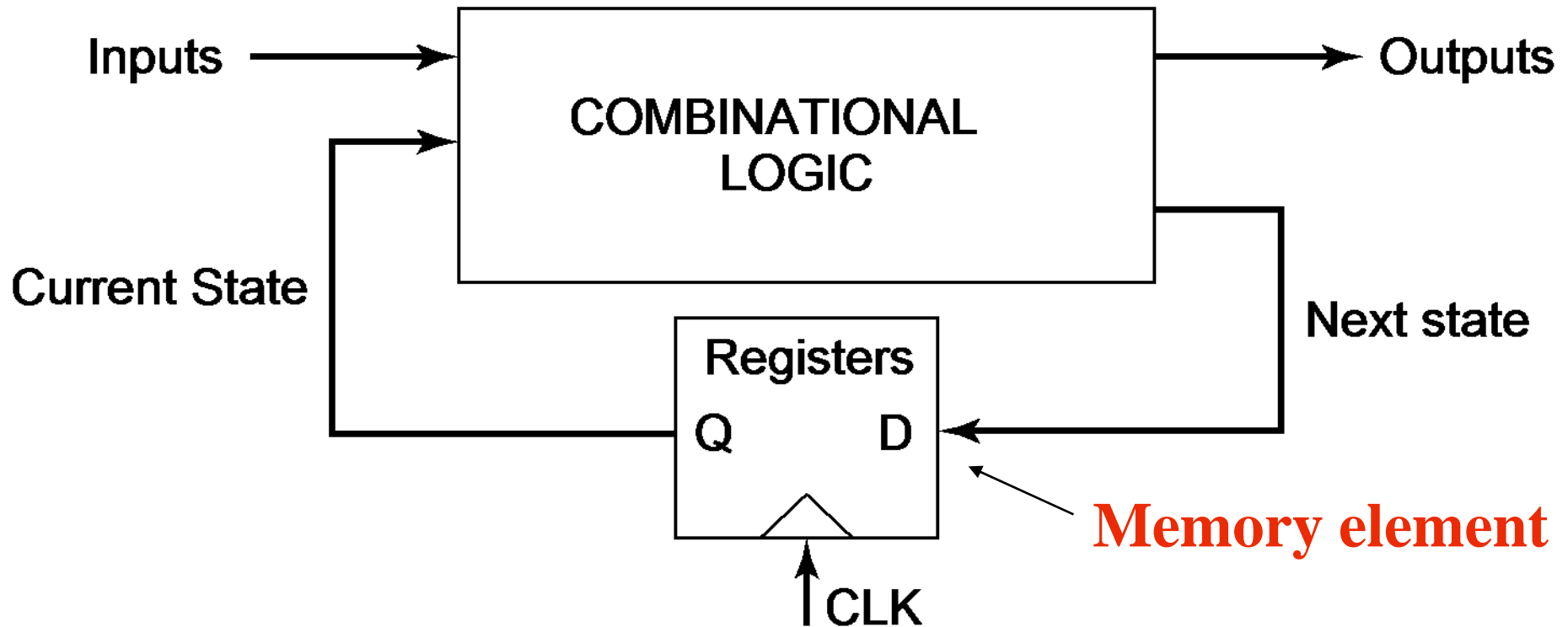- **Combinational logic circuits are memoryless**
- **No feedback in combinational logic circuits**
- **Output assumes the function implemented by the logic network, assuming that the switching transients have settled**
- **Outputs can have multiple logical transitions before settling to the correct value**








- Sequential circuits have memory (i.e., remember the past)
- The current state is “held” in memory and the next state is computed based the current state and the current inputs
- In a synchronous systems, the **clock signal** orchestrates the sequence of events



Adding N inputs (N-1 Adders)

 

Using a sequential (serial) approach


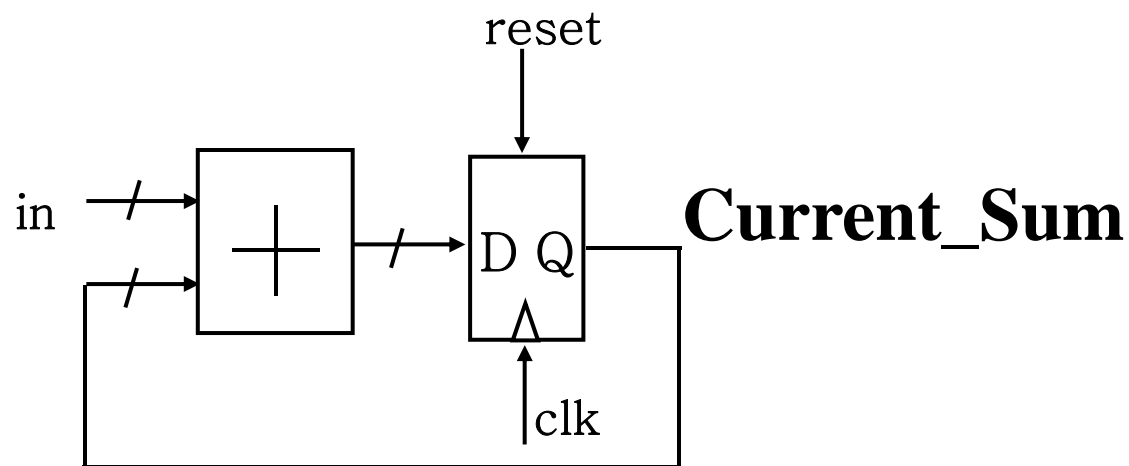


    

  


S	R	Q	\bar{Q}
0	0	Q	\bar{Q}
1	0	1	0
0	1	0	1
1	1	0	0

Forbidden State

  


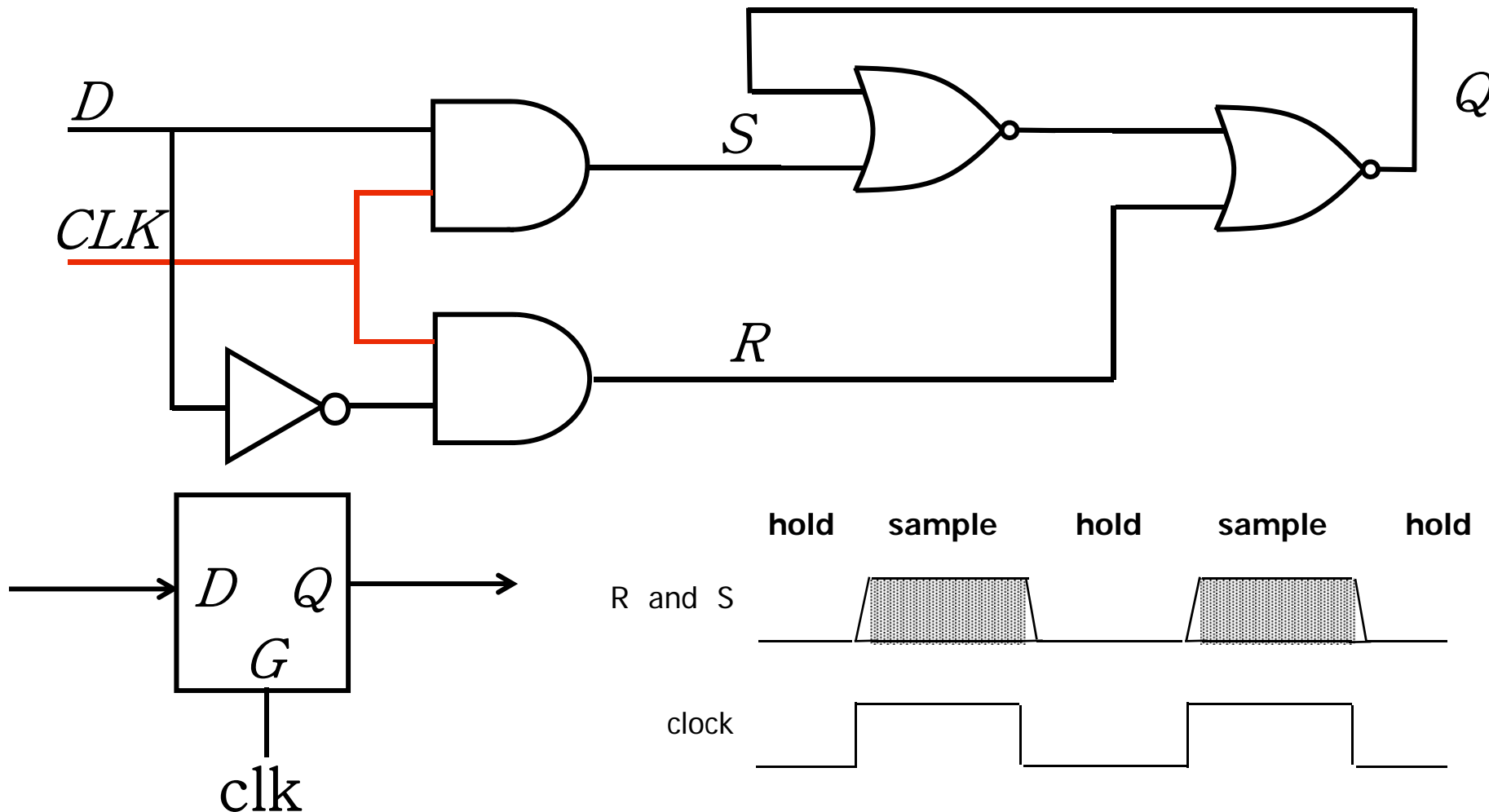- Flip-flop refers to a bi-stable element (edge-triggered registers are also called flip-flops) – this circuit is not clocked and outputs change “asynchronously” with the inputs




- **A Positive D-Latch:** Passes input D to output Q when CLK is high and holds state when clock is low (i.e., ignores input D)
- **A Latch is level-sensitive:** invert clock for a negative latch



2:1 multiplexer

 


Positive Latch

 


Negative Latch

  

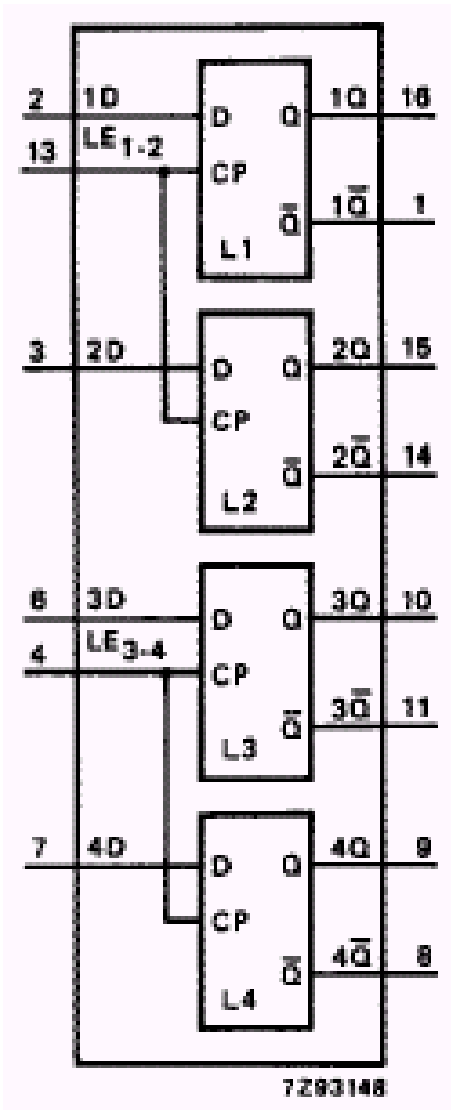

OPERATING MODES	INPUTS		OUTPUTS	
	LE_{n-n}	nD	nQ	$n\bar{Q}$
data enabled	H	L	L	H
	H	H	H	L
data latched	L	X	q	\bar{q}

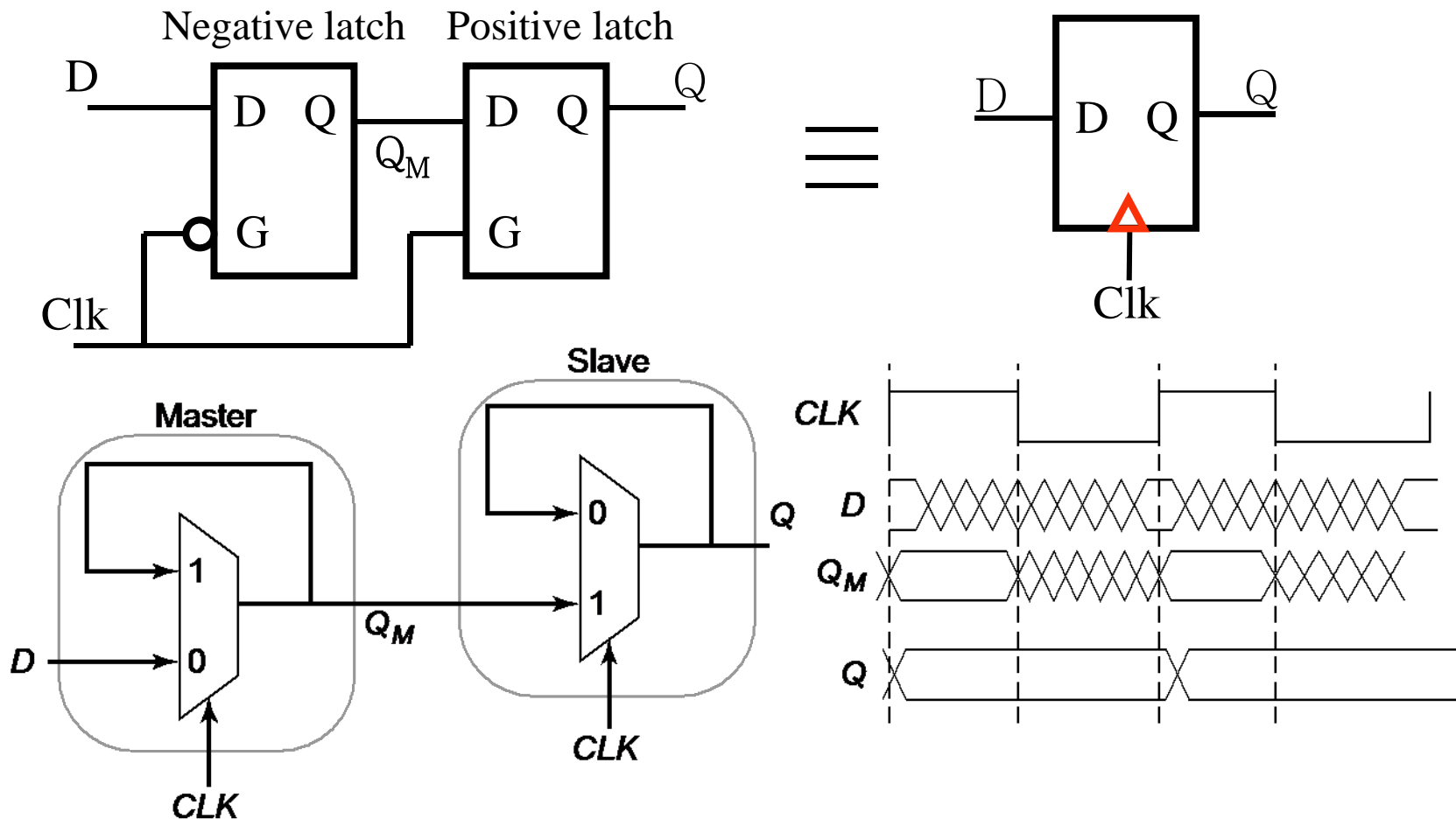

■ Master-Slave Register

- Use negative clock phase to latch inputs into first latch
- Use positive clock to change outputs with second latch


■ View pair as one basic unit

- master-slave flip-flop twice as much logic


Edge triggered device sample inputs on the event edge

Transparent latches sample inputs as long as the clock is asserted


Timing Diagram:

 

 Behavior the same unless input changes while the clock is high




Positive edge-triggered register

 

Level-sensitive latch

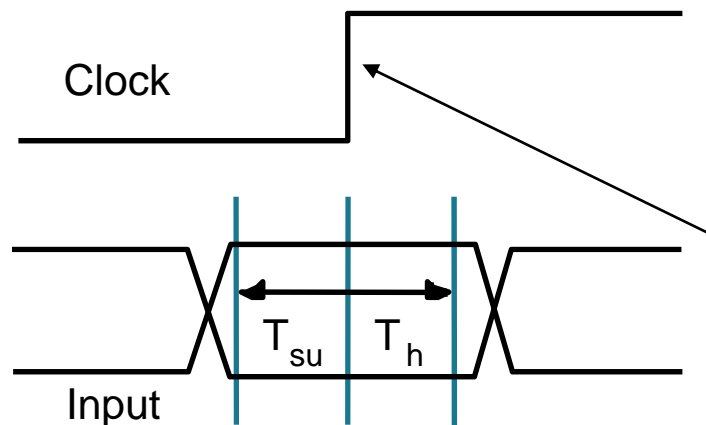Bubble here for negative edge triggered register



Clock:

Periodic Event, causes state of memory element to change

memory element can be updated on the: rising edge, falling edge, high level, low level

Setup Time (T_{su})

Minimum time before the clocking event by which the input must be stable

Hold Time (T_h)



Minimum time after the clocking event during which the input must remain stable

Propagation Delay (T_{cq} for an edge-triggered register and T_{dq} for a latch)

Delay overhead of the memory element

There is a timing "window" around the clocking event during which the input must remain stable and unchanged in order to be recognized

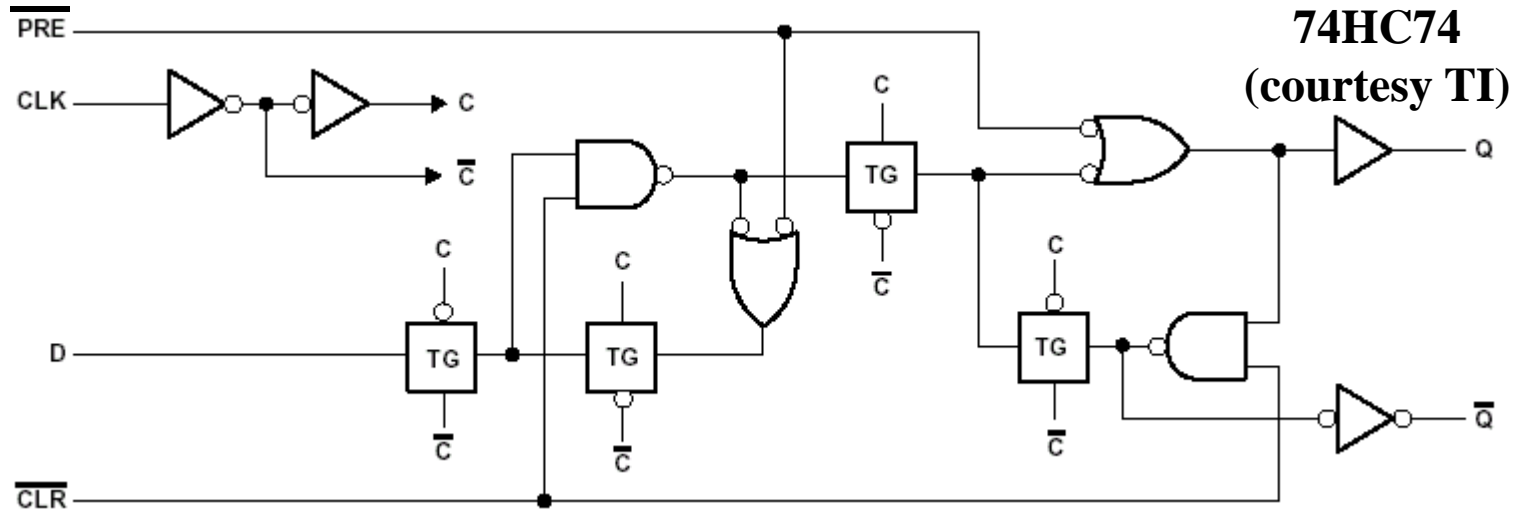 74HC74 (Positive Edge-Triggered Register)





FUNCTION TABLE

INPUTS				OUTPUTS	
$\overline{\text{PRE}}$	$\overline{\text{CLR}}$	CLK	D	Q	$\overline{\text{Q}}$
L	H	X	X	H	L
H	L	X	X	L	H
L	L	X	X	$\text{H}\uparrow$	$\text{H}\uparrow$
H	H	\uparrow	H	H	L
H	H	\uparrow	L	L	H
H	H	L	X	Q_0	$\overline{\text{Q}}_0$

D-FF with preset and clear

		V_{CC}	$T_A = 25^\circ\text{C}$		SN54HC74		SN74HC74		UNIT
			MIN	MAX	MIN	MAX	MIN	MAX	
f_{clock}	Clock frequency	2 V	0	6	0	4.2	0	5	MHz
		4.5 V	0	31	0	21	0	25	
		6 V	0	36	0	25	0	29	
t_w	Pulse duration	$\overline{\text{PRE}}$ or $\overline{\text{CLR}}$ low	2 V	100	150	125	ns		
			4.5 V	20	30	25			
			6 V	17	25	21			
		CLK high or low	2 V	80	120	100			
			4.5 V	16	24	20			
			6 V	14	20	17			
t_{su}	Setup time before $\text{CLK}\uparrow$	Data	2 V	100	150	125	ns		
			4.5 V	20	30	25			
			6 V	17	25	21			
		$\overline{\text{PRE}}$ or $\overline{\text{CLR}}$ inactive	2 V	25	40	30			
			4.5 V	5	8	6			
			6 V	4	7	5			
t_h	Hold time, data after $\text{CLK}\uparrow$	2 V	0	0	0	ns			
		4.5 V	0	0	0				
		6 V	0	0	0				


 
 


J	K	Q ₊	\overline{Q}_+
0	0	Q	\overline{Q}
0	1	0	1
1	0	1	0
1	1	\overline{Q}	Q




- Eliminate the forbidden state of the SR Flip-flop
- Use output feedback to guarantee that R and S are never both one

Sample inputs while clock high


Sample inputs while clock low

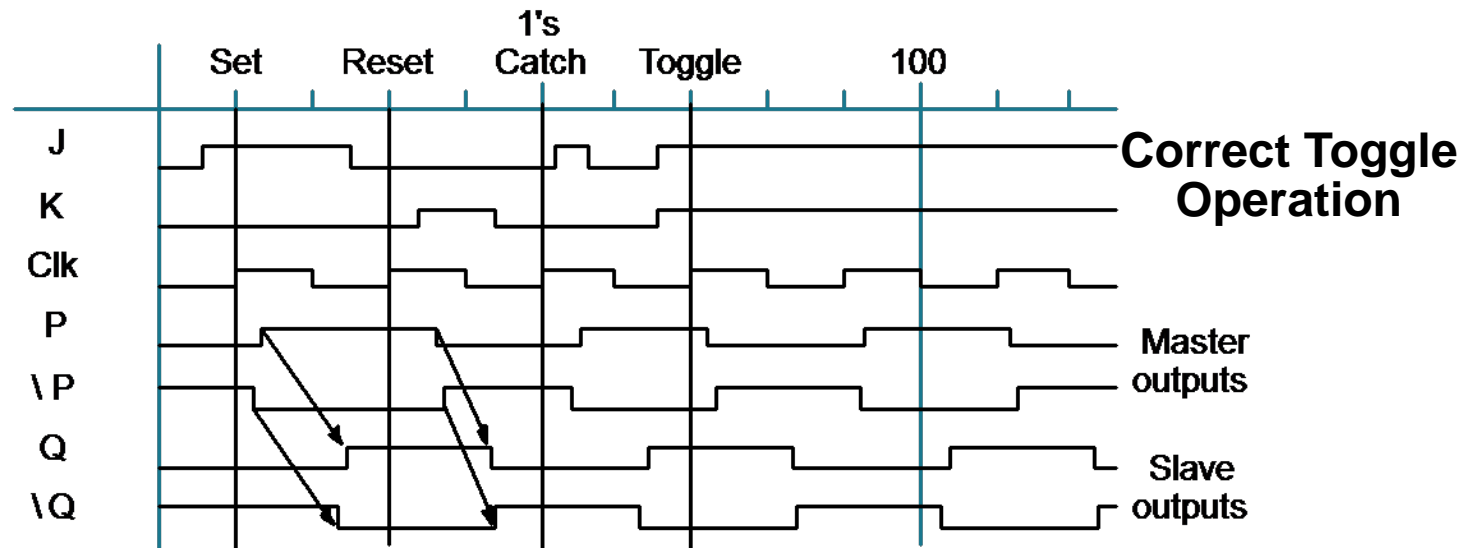 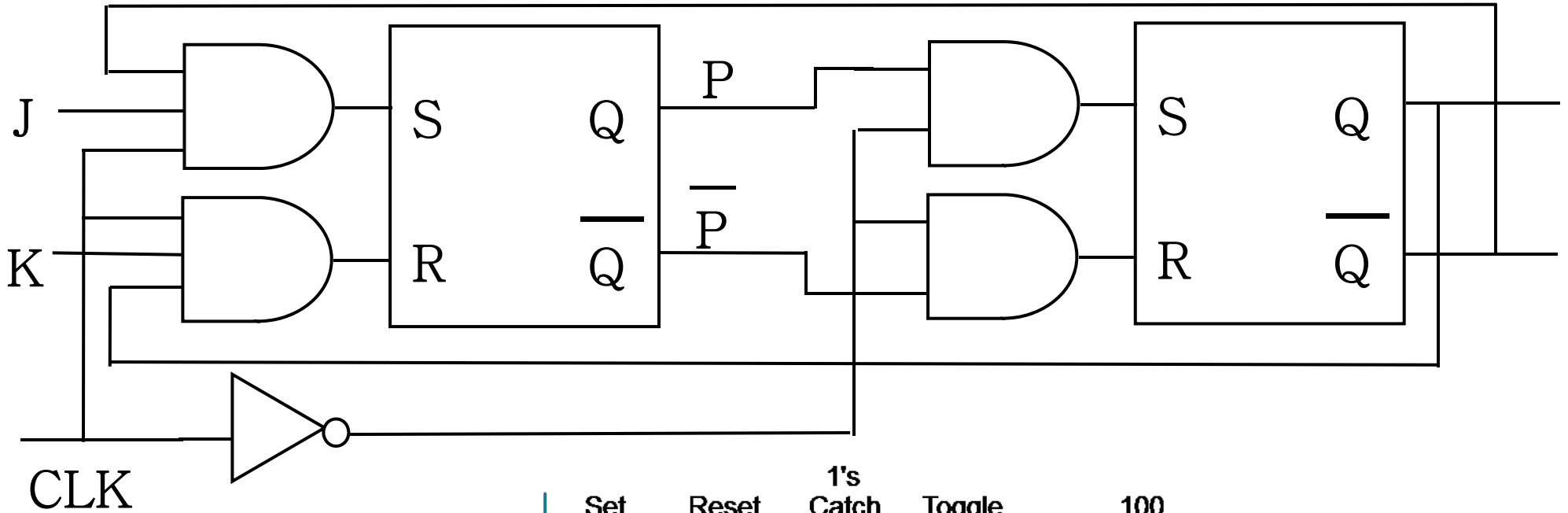

Is there a problem with this circuit?

   


JK Register Schematic

 


JK Register Logic Symbol

Ways to design an edge-triggered sequential cell:

Master-Slave Latches

 


Pulse-Based Register


 


Short pulse around clock edge

 
- **Pulse registers are widely used in high-performance microprocessor chips (Sun Microsystems, AMD, Intel, etc.)**
- **The can have a negative setup time!**



D	Q_N
0	0
1	1

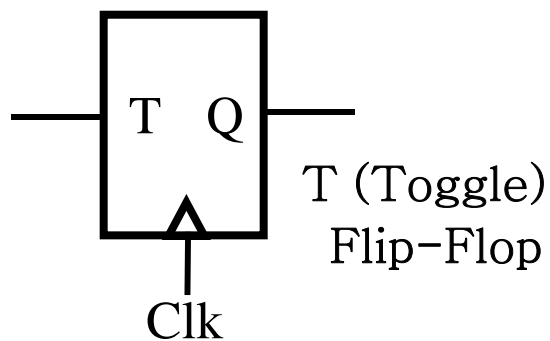 

T	Q_N
0	Q_{N-1}
1	$\overline{Q_{N-1}}$

 

Characteristic Equations


D: $Q_+ = D$

J-K: $Q_+ = J \bar{Q} + \bar{K} Q$


T: $Q_+ = T \bar{Q} + \bar{T} Q$

E.g., J=K=0, then $Q_+ = Q$
 J=1, K=0, then $Q_+ = 1$
 J=0, K=1, then $Q_+ = \bar{Q}$
 J=1, K=1, then $Q_+ = \bar{Q}$

Implementing One FF in Terms of Another

 

D implemented with J-K

 

J-K implemented with D

Excitation Tables: What are the necessary inputs to cause a particular kind of change in state?

Q	Q+	J	K	T	D
0	0	0	X	0	0
0	1	1	X	1	1
1	0	X	1	1	0
1	1	X	0	0	1

Implementing D FF with a J-K FF:

- 1) Start with K-map of $Q^+ = f(D, Q)$
- 2) Create K-maps for J and K with same inputs (D, Q)
- 3) Fill in K-maps with appropriate values for J and K to cause the same state changes as in the original K-map

	D	0	1
Q	0	0	1
	1	0	1

$Q^+ = D$

E.g., $D = Q = 0$, $Q^+ = 0$
then $J = 0$, $K = X$

	D	0	1
Q	0	0	1
	1	X	X

$J = D$

	D	0	1
Q	0	X	X
	1	1	0

$K = \bar{D}$

Implementing J-K FF with a D FF:


1) K-Map of $Q^+ = F(J, K, Q)$

2,3) Revised K-map using D's excitation table
 its the same! that is why design procedure with D FF is simple!

		JK			
				J	
	Q	00	01	11	10
0		0	0	1	1
1		1	0	0	1
		K			

$$Q^+ = D = J\bar{Q} + \bar{K}Q$$

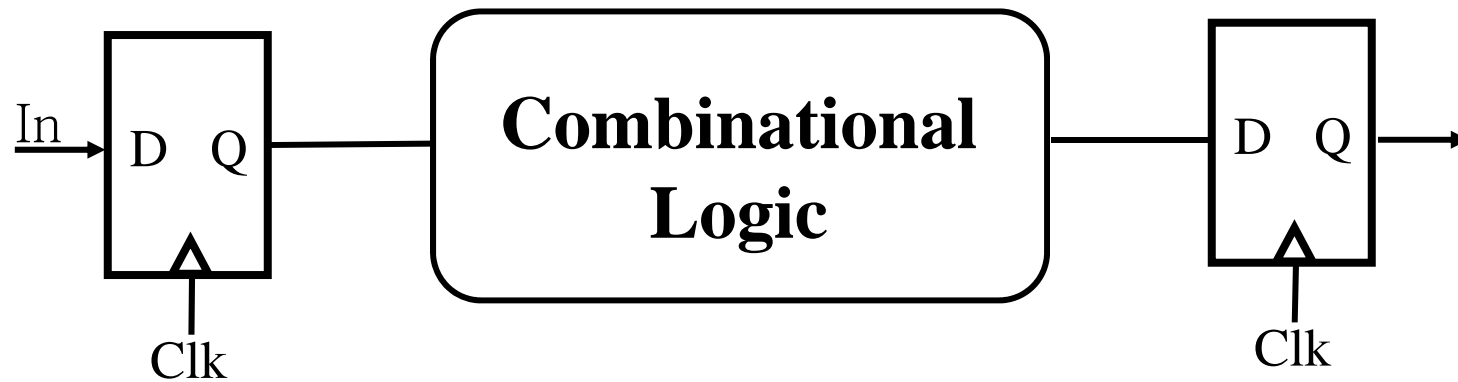Resulting equation is the combinational logic input to D to cause same behavior as J-K FF. Of course it is identical to the characteristic equation for a J-K FF.



Register Timing Parameters

T_{cq} : worst case rising edge
clock to q delay

$T_{cq, cd}$: contamination or
minimum delay from
clock to q


T_{su} : setup time

T_h : hold time


Logic Timing Parameters

T_{logic} : worst case delay
through the
combinational logic
network

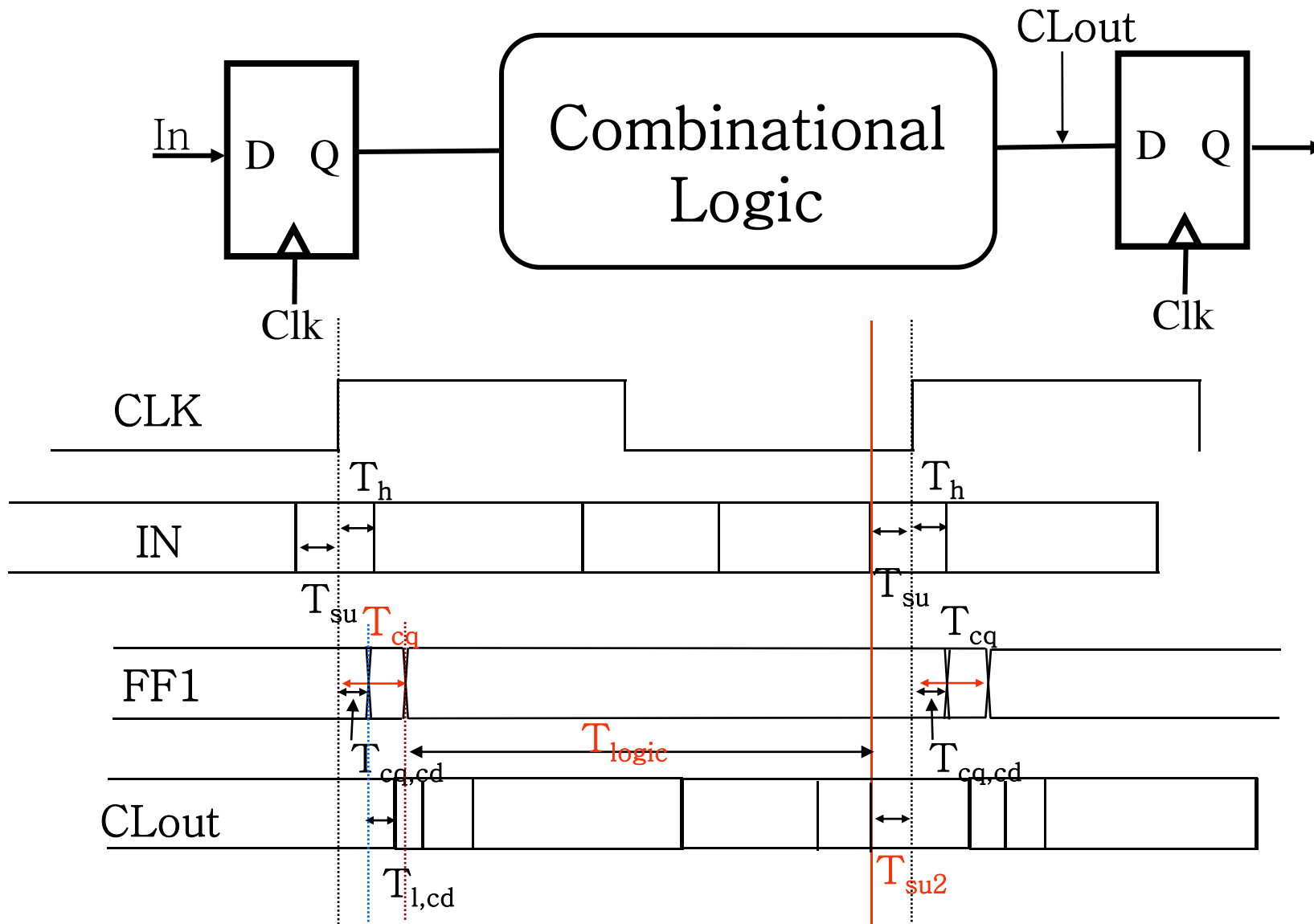$T_{logic, cd}$: contamination or
minimum delay
through logic network




$$T > T_{cq} + T_{logic} + T_{su}$$

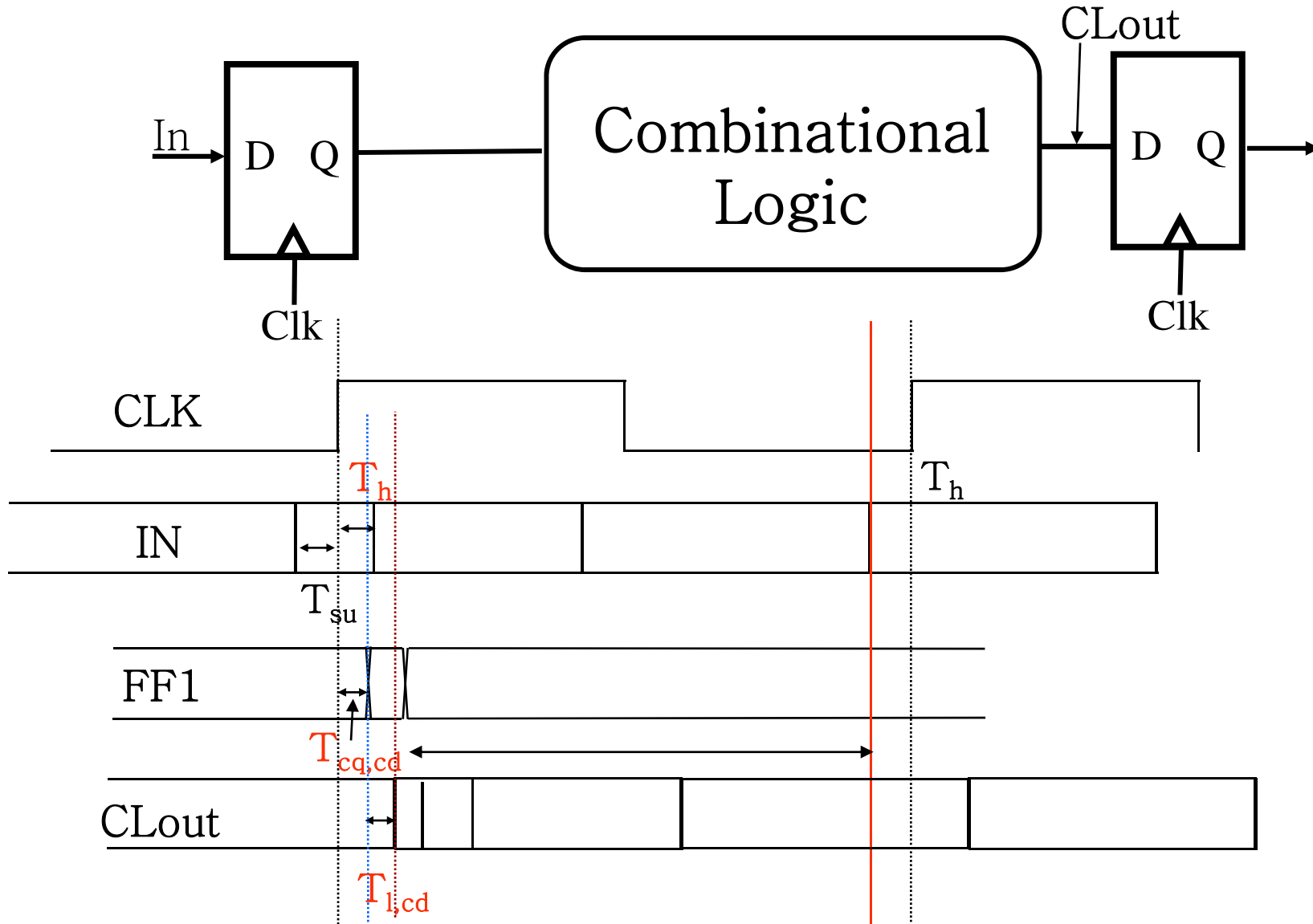

$$T_{cq,cd} + T_{logic,cd} > T_{hold}$$

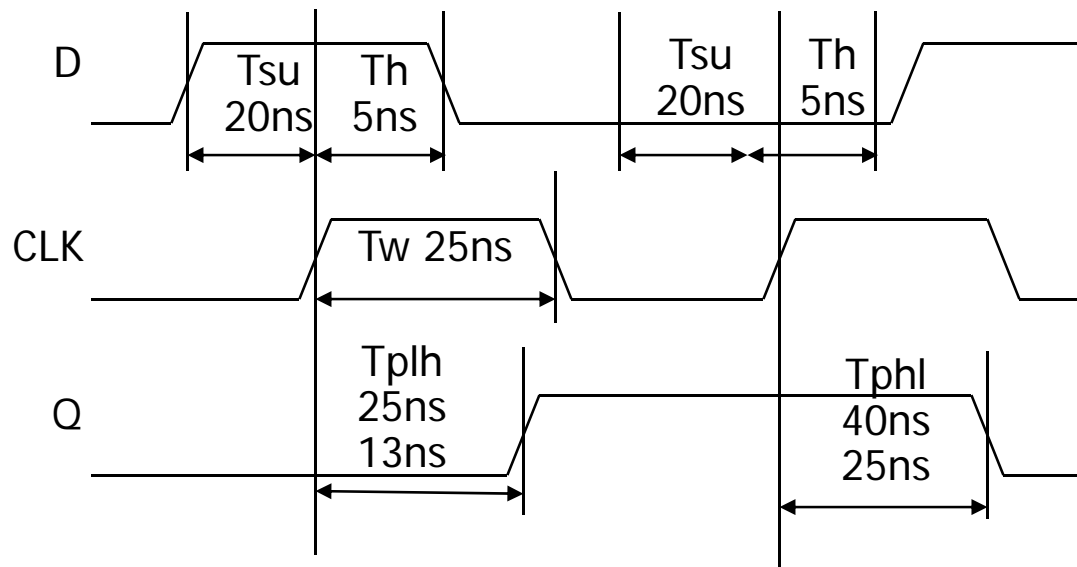■ Typical parameters for Positive edge-triggered D Register



all measurements are made from the clocking event that is, the rising edge of the clock

■ Shift-register

