 


PROBLEM 1

#1	a	b	c	d	f
	0	0	0	0	0
	0	0	0	1	1
	0	0	1	0	0
	0	0	1	1	0
	0	1	0	0	0
	0	1	0	1	1
	0	1	1	0	0
	0	1	1	1	0
	1	0	0	0	0
	1	0	0	1	0
	1	0	1	0	0
	1	0	1	1	0
	1	1	0	0	0
	1	1	0	1	0
	1	1	1	0	1
	1	1	1	1	0



$$SOP = \bar{a} \cdot \bar{c} \cdot d + a \cdot b \cdot c \cdot \bar{d}$$

$$POS = (\bar{a} + \bar{d})(c + d)(\bar{a} + b)(a + \bar{c})$$

#2  $f = \overline{(w+x)}(z\bar{y}+x) = \overline{(w+x)} + \overline{(z\bar{y}+x)}$   
 $= (\bar{w} \cdot \bar{x}) + ((\bar{z} + y) \cdot \bar{x}) = \bar{w}x + \bar{x}\bar{z} + \bar{x}y$

w	x	y	z	f
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

wx \ yz	00	01	11	10
00	1	0	1	1
01	1	1	1	1
11	0	0	0	0
10	1	0	1	1

SOP =  $\bar{w}x + \bar{x}\bar{z} + \bar{x}y$

POS =  $(\bar{w} + \bar{x})(x + y + \bar{z})$

PROBLEM 2

#1

		ab			
	cd	00	01	11	10
00		X	0	0	1
01		1	0	0	X
11		0	X	0	1
10		0	0	0	1

i) min SOP =  $a\bar{b} + \bar{c}\bar{b}$

ii) min POS =  $\bar{b} \cdot (a + \bar{c})$

iii) Yes

iv) Yes

#2

		ab			
	cd	00	01	11	10
00		1	X	0	1
01		1	1	1	0
11		0	0	X	0
10		X	0	1	1

i) min SOP =  $abc + \bar{b}\bar{d} + \bar{a}\bar{c} + b\bar{c}\bar{d}$

ii) min POS =  $(c+d+\bar{b})(a+\bar{c})(\bar{a}+b+\bar{d})$

iii) POS is unique, but SOP is not

e.g.  $\bar{a}\bar{c} + \bar{b}\bar{c}\bar{d} + a\bar{c}\bar{d} + \bar{b}\bar{d}$

iv) NO

← This grouping is redundant

PROBLEM 3


#1  $\overline{(a+d)(\bar{b}+c)} = (a+d) + (\bar{b}+c)$

#2  $\overline{(a \cdot b \cdot \bar{c}) + (\bar{c} \cdot d)} = (a \cdot b \cdot \bar{c}) \cdot (\bar{c} \cdot d)$   
 $= a \cdot b \cdot \bar{c} \cdot d$


#3  $\overline{\bar{a}+d} \cdot \overline{b+\bar{c}} \cdot \overline{\bar{c}+d} = (a \cdot \bar{d}) \cdot (\bar{b} \cdot c) \cdot (c \cdot \bar{d})$   
 $= a \cdot \bar{b} \cdot c \cdot \bar{d}$

PROBLEM 4

#1

 

#2

 

PROBLEM 5

5/5

#1

$$t_{\text{setup}} = 0$$

$t_{\text{hold}} = 2 t_{\text{inv}}$  ( to ensure stability, we want the signal to propagate through  $I_1$  &  $I_2$  before  $\bar{G}$  is asserted ).

#2

Master-Slave positive-edge triggered register (or flip flop)

#3

$t_{\text{setup}} = 2 t_{\text{inv}}$  ( before rising edge of the clk, the data must propagate through both inverters ).

$$t_{\text{hold}} = 0$$

(@ rising edge, the inverter feedback loop is stable so no need to hold data)

$t_{c \rightarrow a} = 2 t_{\text{inv}}$  ( looking @ the second D-flip flop )

Note: since we have a positive-edge triggered register, the timing parameters are calculated with respect to the rising (i.e. low-to-high transition) of the clock.