

Lecture 2

Intermediate circuit theory, nonlinear components

Graphics used with permission from AspenCore (<http://electronics-tutorials.ws>)

Agenda



1. Lab 1 review: RC circuits
2. Nonlinear components: diodes, BJTs and MOSFETs
3. Operational amplifiers (op-amps)
4. Audio amplification
5. Lab 2 overview: components and specifications

Lab 1 review

Resistor-capacitor (RC) circuits

RC charging response

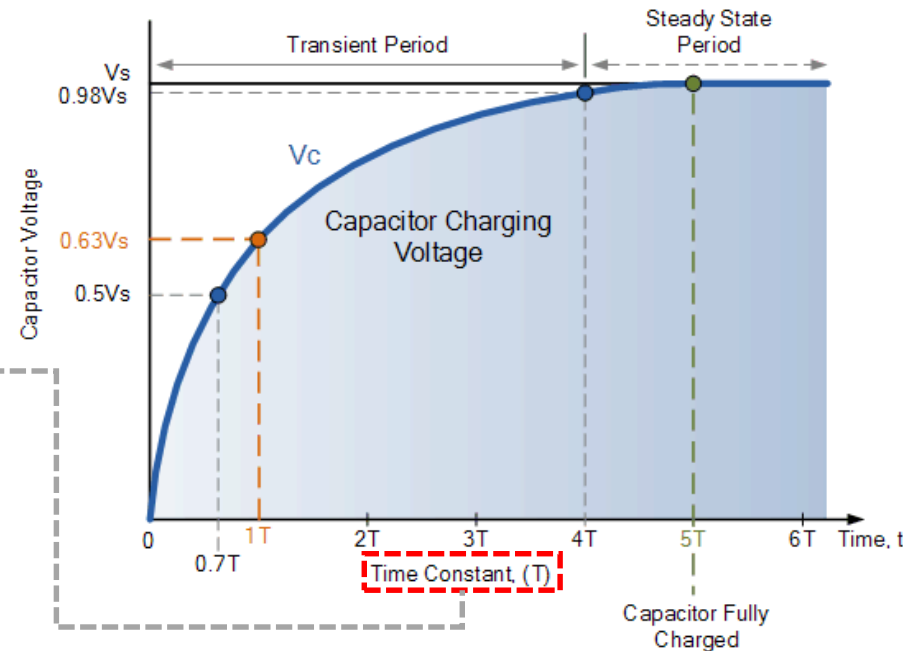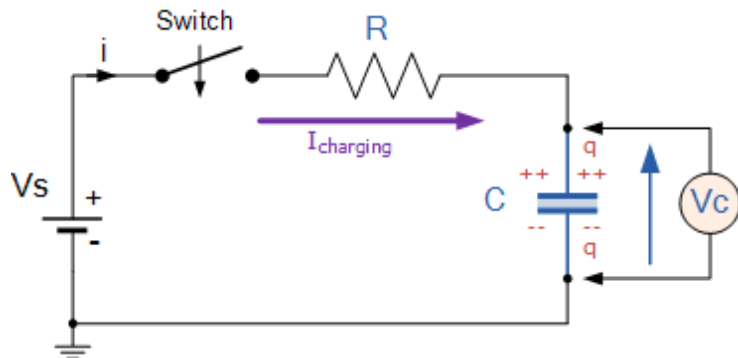- Capacitor voltage V_C grows **exponentially** close to V_S
- Rate of exponential growth defined by resistor value (smaller resistor = faster charging)





RC time constant $\tau \equiv R \times C$

Capacitor voltage $V_C = V_S (1 - e^{-(t/RC)})$

RC discharging response

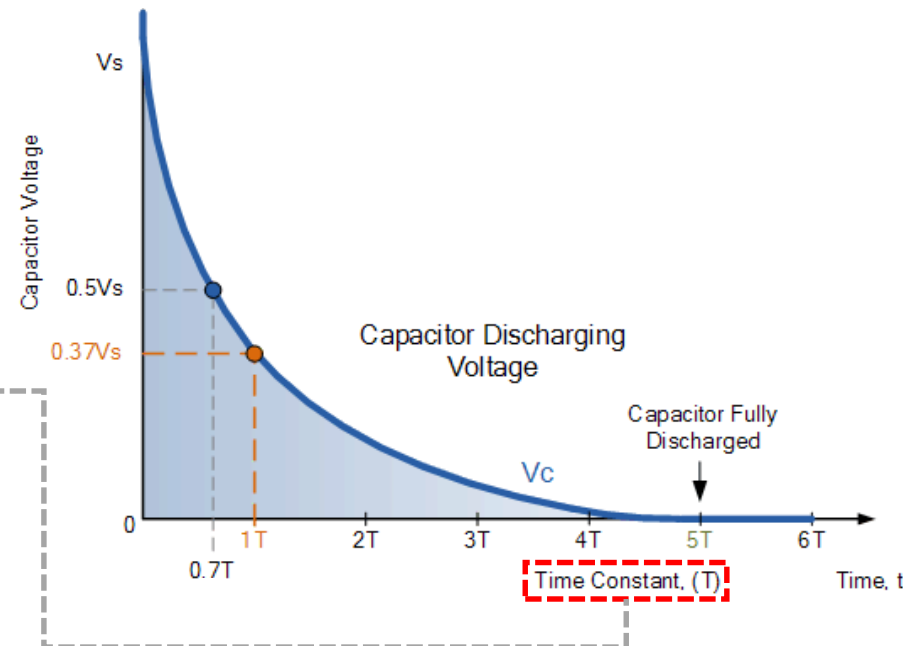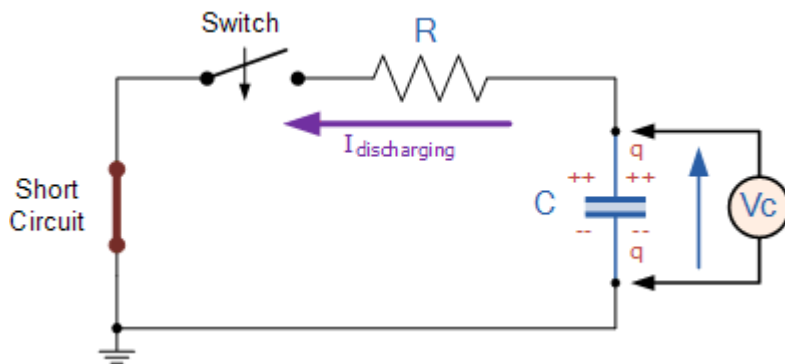
- Capacitor voltage V_C decays **exponentially** to 0
- Rate of exponential decay defined by resistor value (smaller resistor = faster discharging)



RC time constant $\tau \equiv R \times C$



Capacitor voltage $V_C = V_s \times e^{-t/RC}$

RC transient response

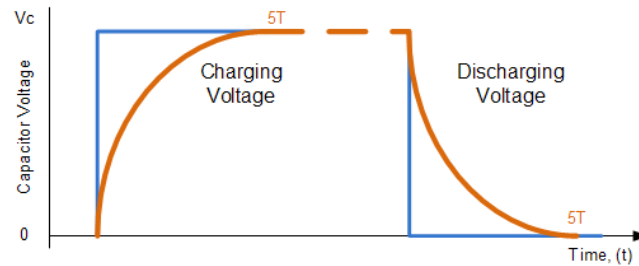

Slower oscillations

Faster oscillations

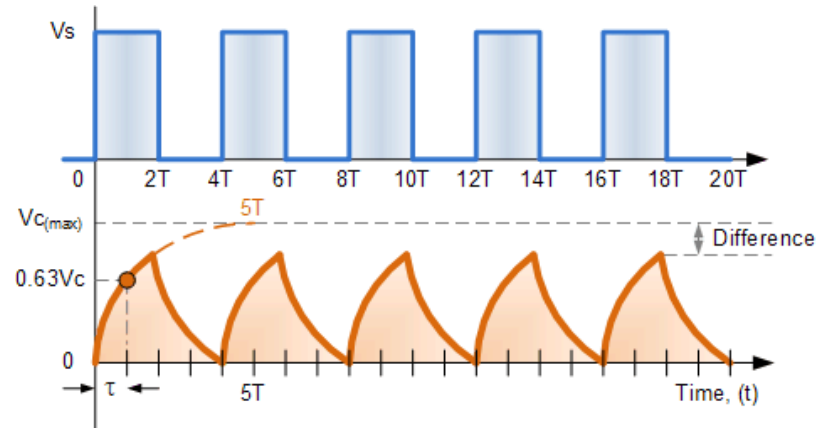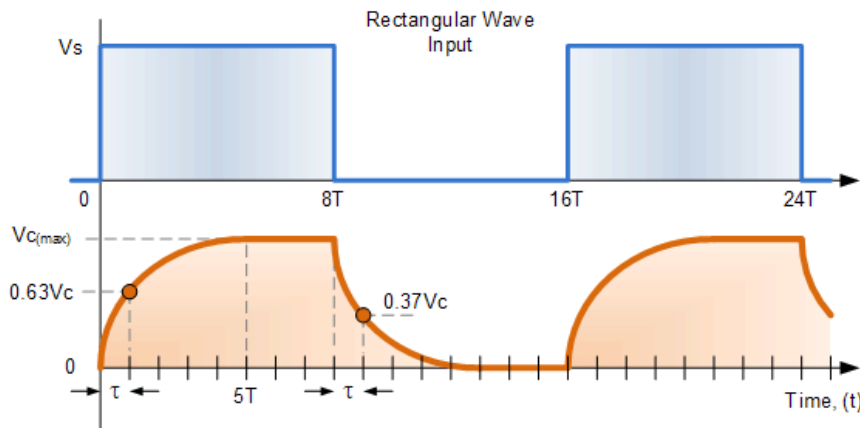

RC Time constant tables

Charging



Time Constant	Percentage of applied voltage
0.5	39.3%
0.7	50.3%
1	63.2%
2	86.5%
3	95.0%
4	98.2%
5	99.3%

Discharging

Time Constant	Percentage of applied voltage
0.5	60.7%
0.7	49.7%
1	36.8%
2	13.5%
3	5.0%
4	1.8%
5	0.7%



Filtering

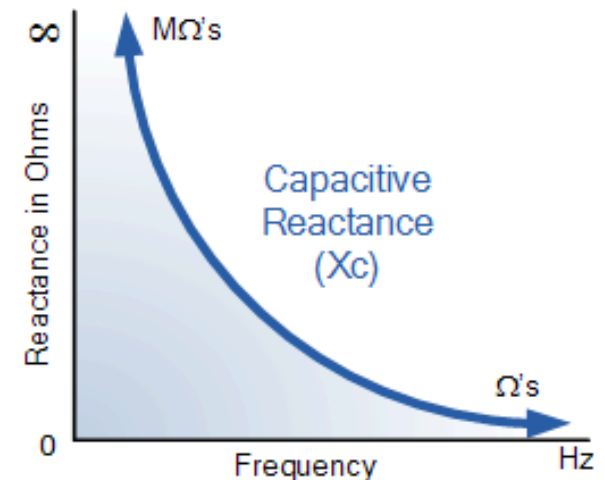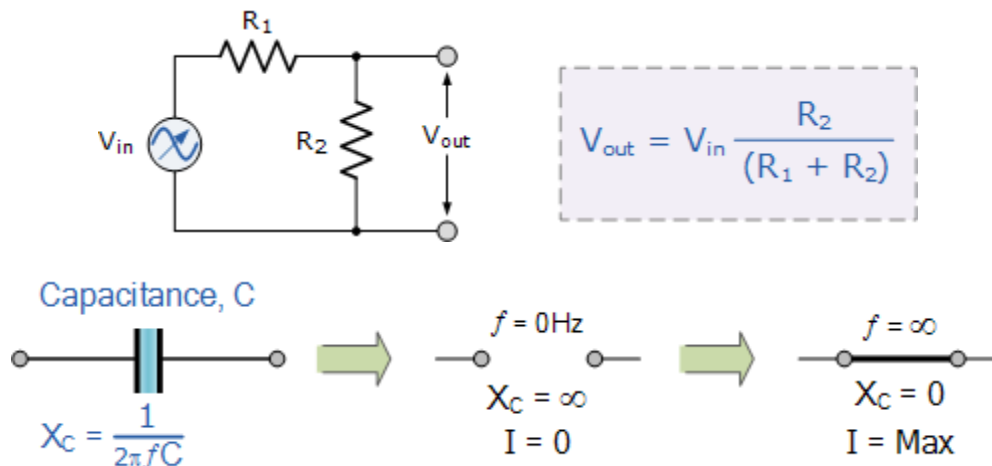- **Filter:** Circuit whose response depends on the frequency of the input
- **Reactance:** “Effective resistance” of a capacitor, varies inversely with frequency
- Can construct a voltage divider using a capacitor as a “resistor” to exploit this property





Types of filters

LPF

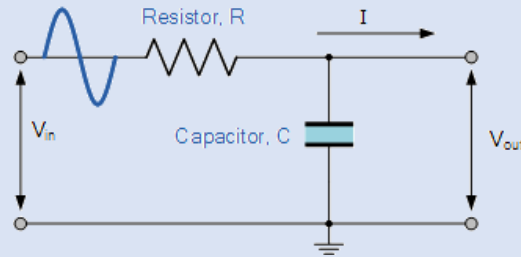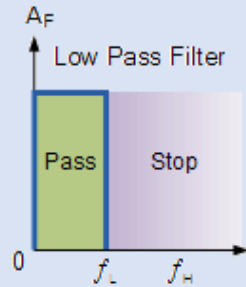



$$f_c = \frac{1}{2\pi RC} \text{ Hz}$$

HPF

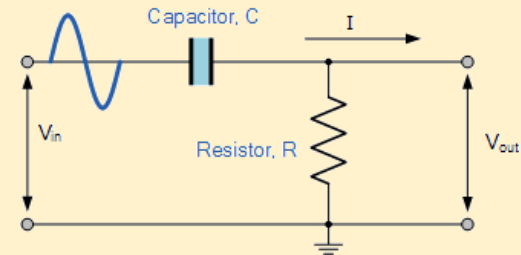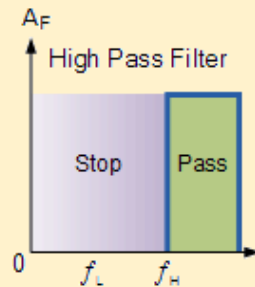

$$f_c = \frac{1}{2\pi RC} \text{ Hz}$$

BPF

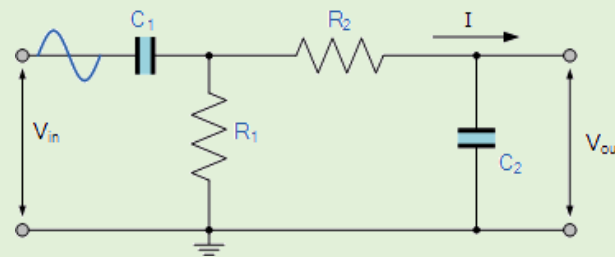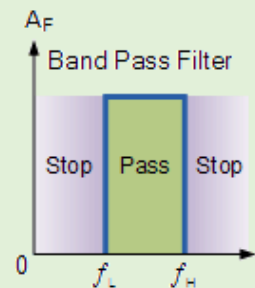

$$f_H = \frac{1}{2\pi R_1 C_1} \text{ Hz}$$
$$f_L = \frac{1}{2\pi R_2 C_2} \text{ Hz}$$


Nonlinear components

Diodes, BJTs and MOSFETs


Linear vs. nonlinear components

- **I-V curve:** Relates current through a device to voltage across the device
- **Nonlinear components** have nonlinear I-V curves

I-V curve of linear component (resistor)

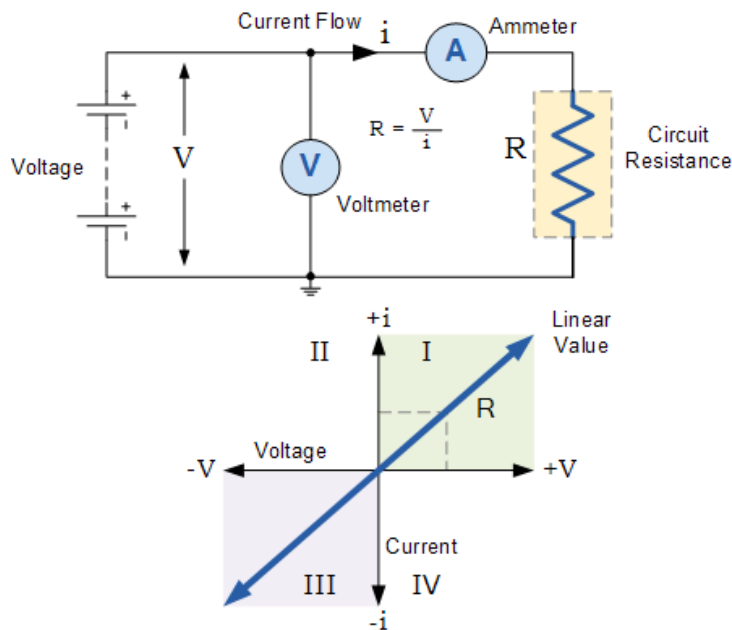


I-V curve of nonlinear component (diode)

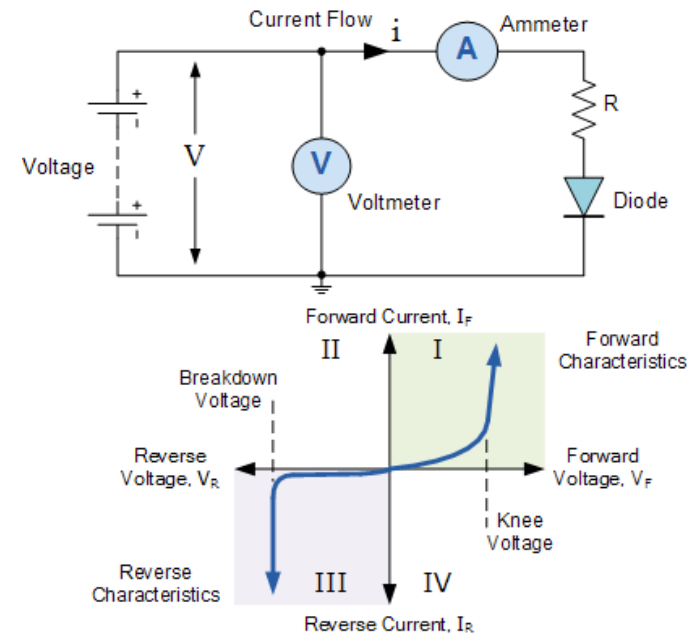


Diodes

- **Diode:** only allows current to flow one way
- Can be modeled by a **switch** in series with a voltage source
- Important to ensure proper **polarity** when prototyping





Diode symbol and I-V characteristic

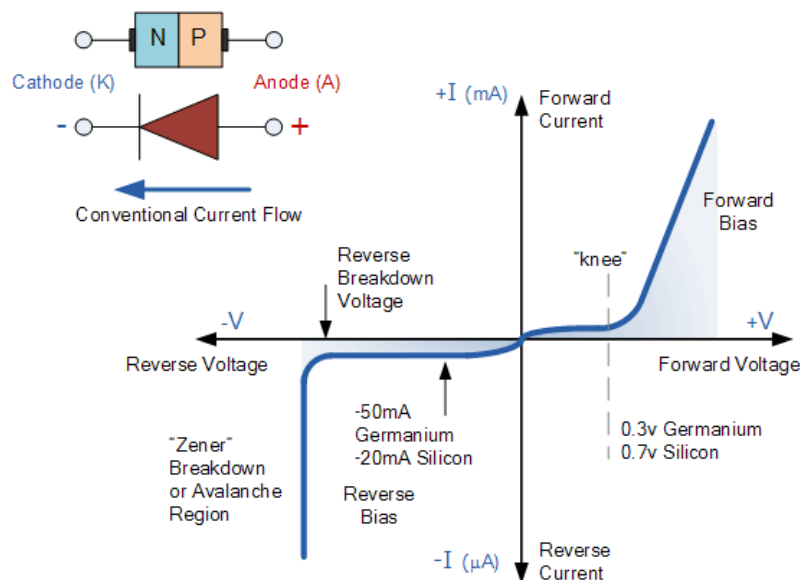



Ideal vs. real diode characteristics

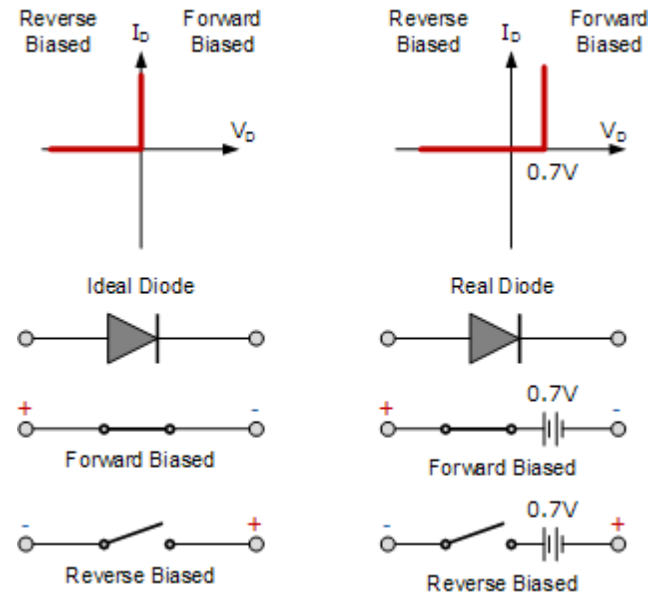

Example diode circuits

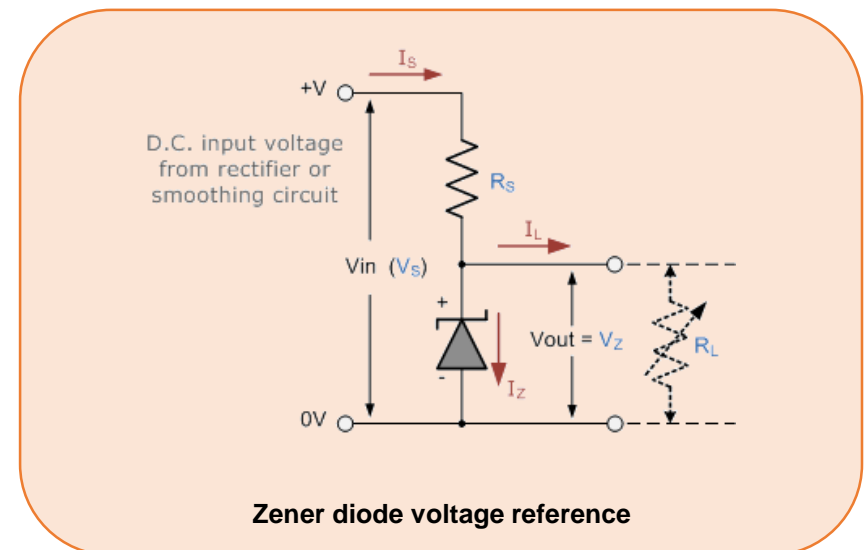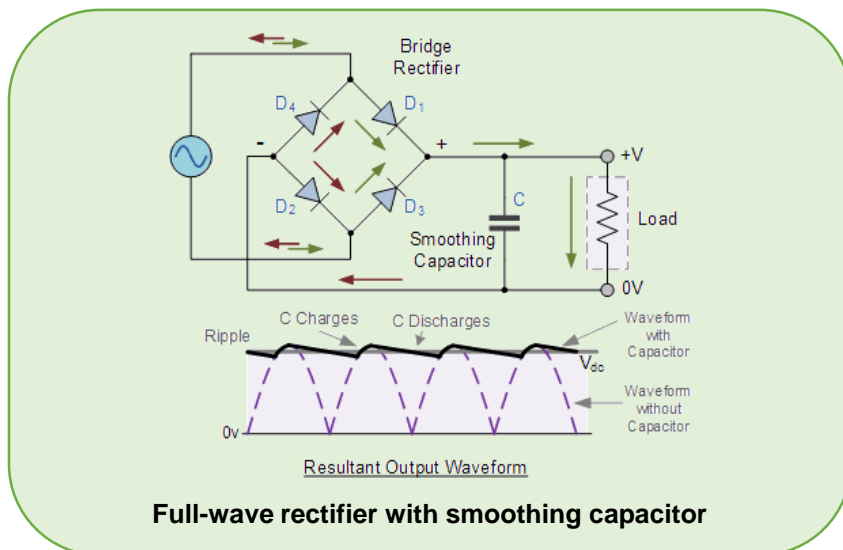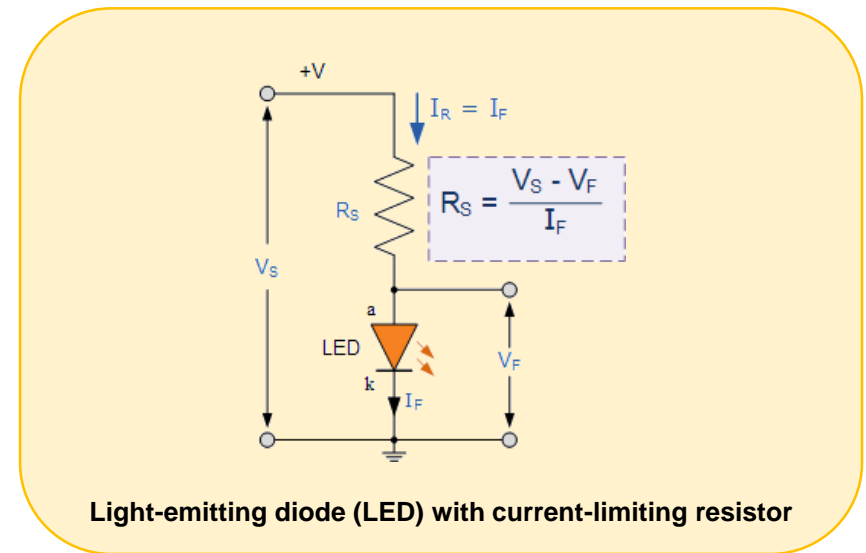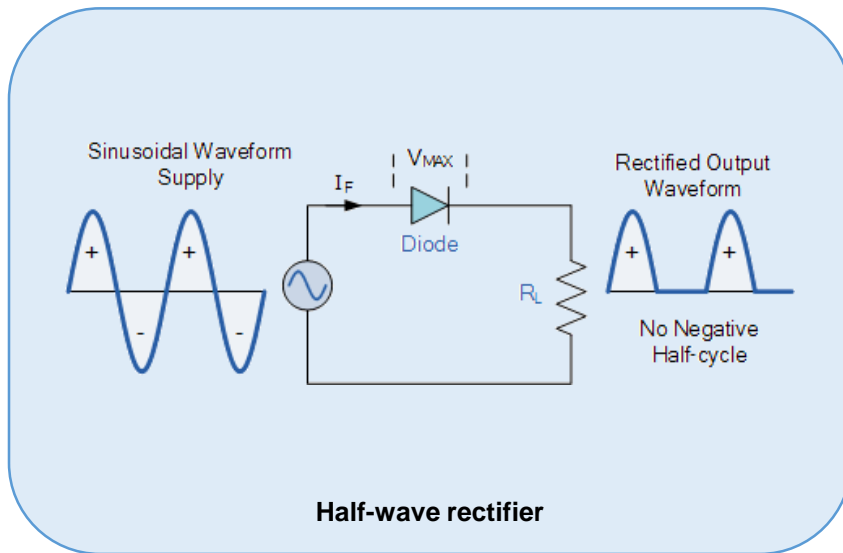



Diodes

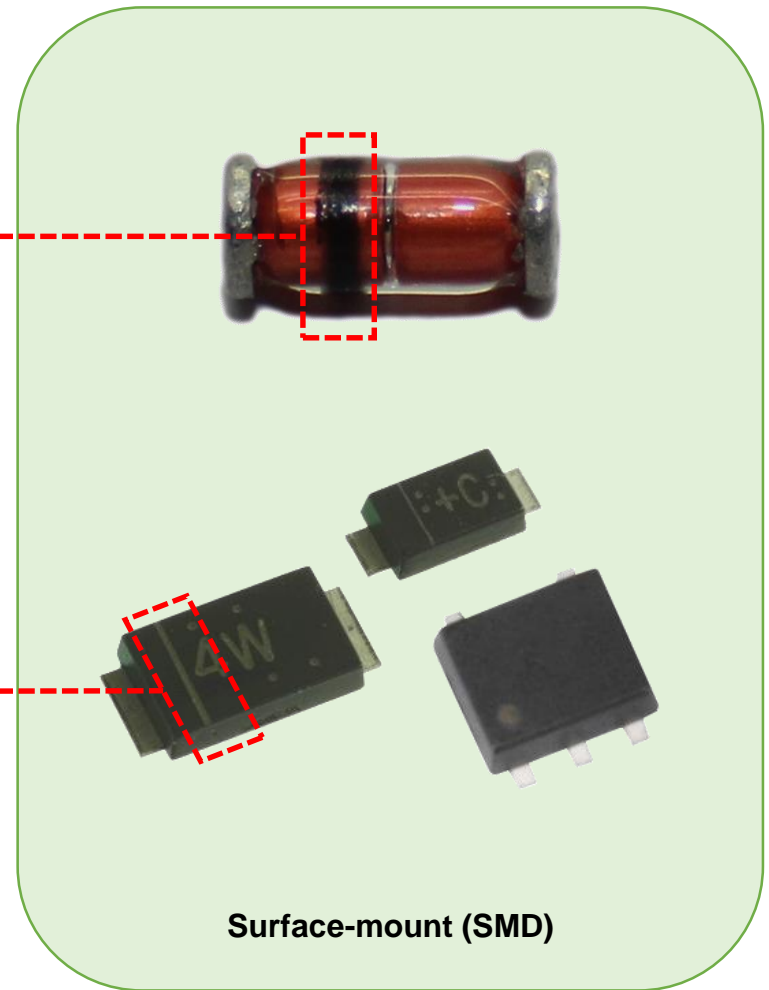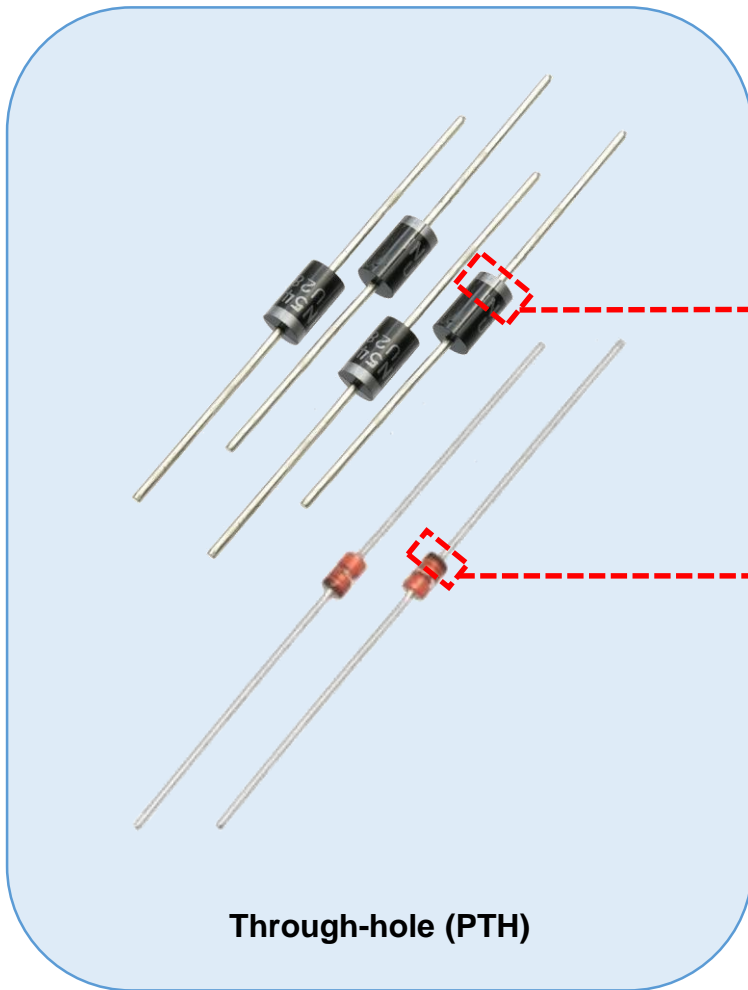




Pay attention to polarity: the striped side is always the cathode (K)

BJTs

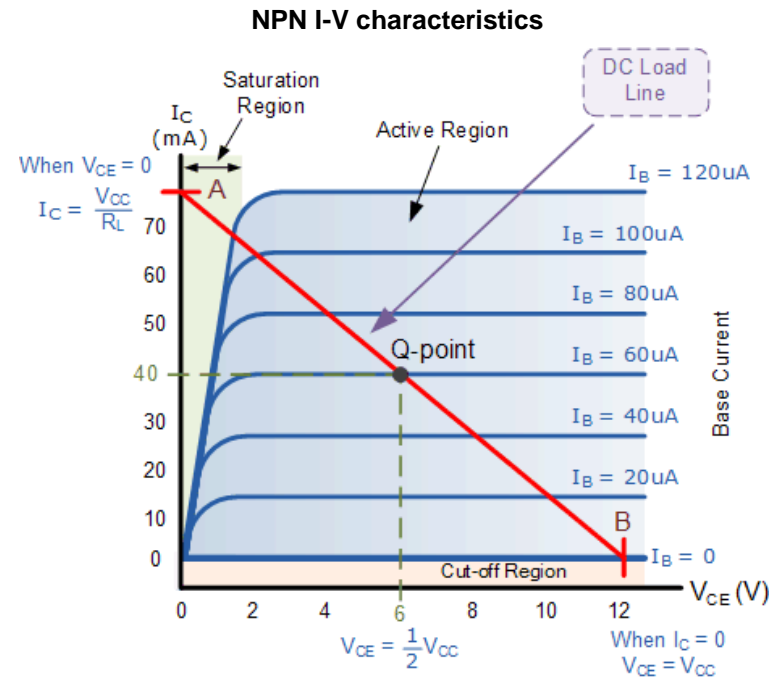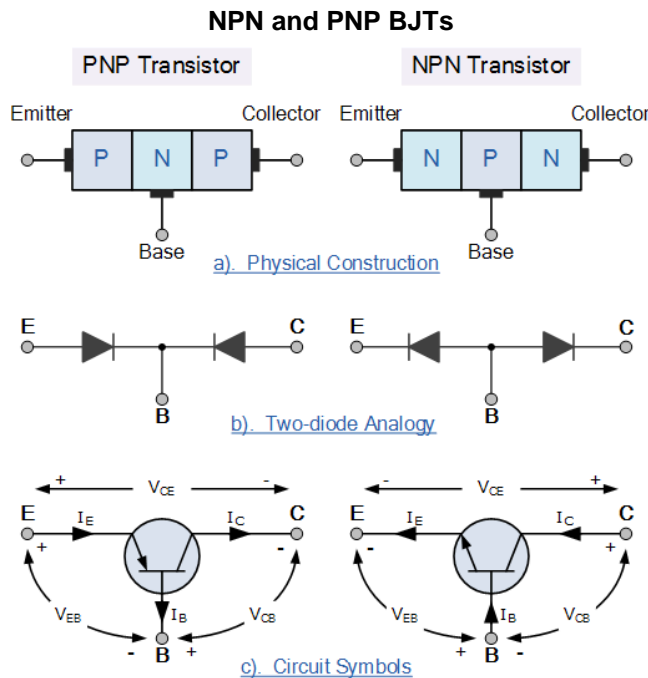- **BJT (bipolar junction transistor):** Current-driven amplifier
- Two types: NPN and PNP
- **Base** controls current from **emitter** to **collector**




BJT amplifier circuits

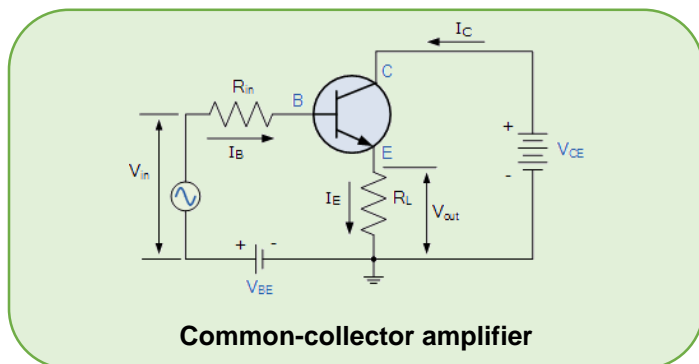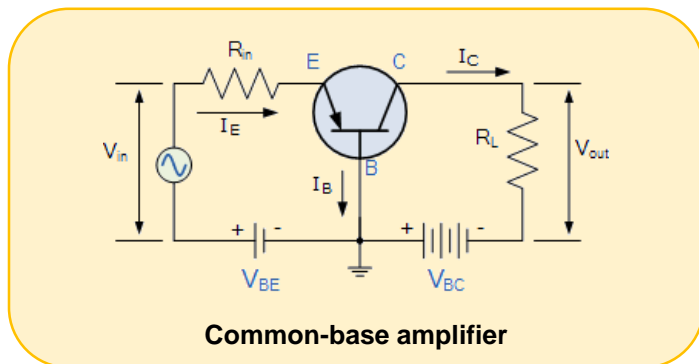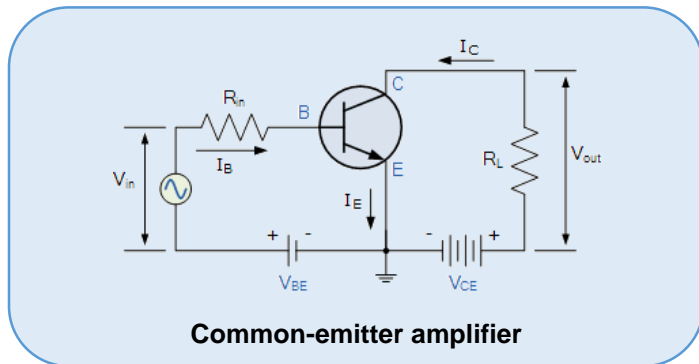


Characteristic	Common Base	Common Emitter	Common Collector
Input Impedance	Low	Medium	High
Output Impedance	Very High	High	Low
Phase Shift	0°	180°	0°
Voltage Gain	High	Medium	Low
Current Gain	Low	Medium	High
Power Gain	Low	Very High	Medium

BJTs

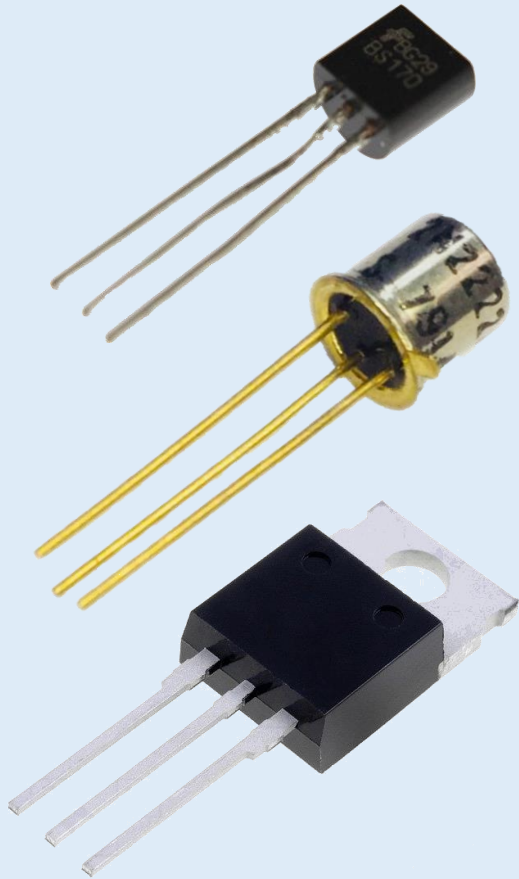



Through-hole (PTH)

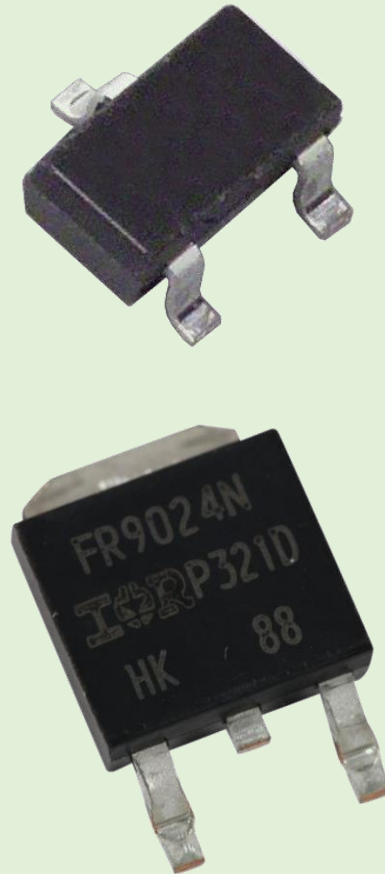

Surface-mount (SMD)


MOSFETs

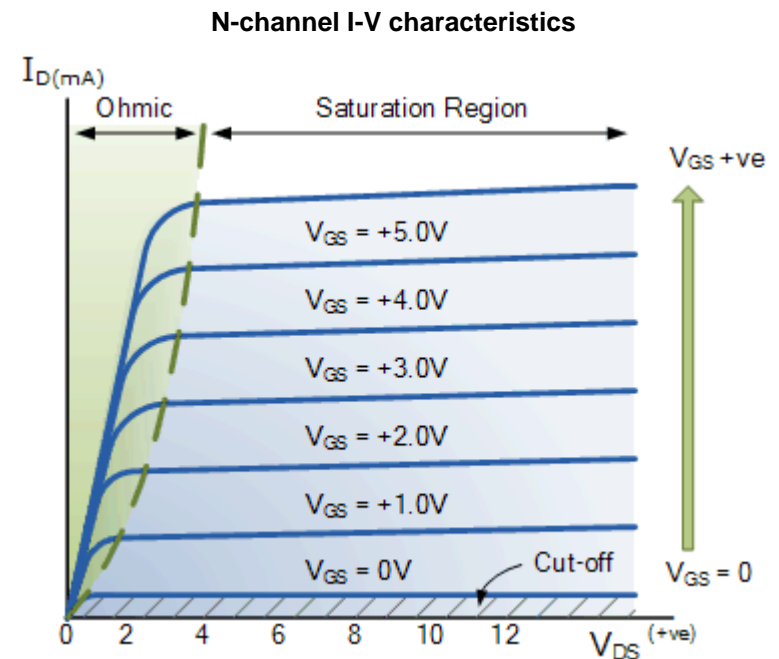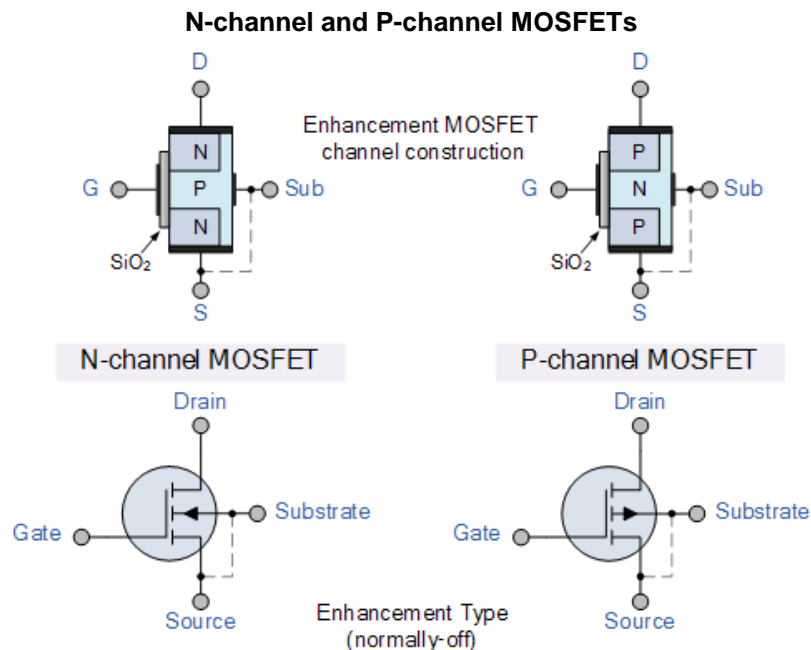- **MOSFET:** Metal-oxide-semiconductor field effect transistor
- Typically used as a **voltage-controlled** switch
- **Gate** controls current from **drain** to **source**




MOSFET as a switch

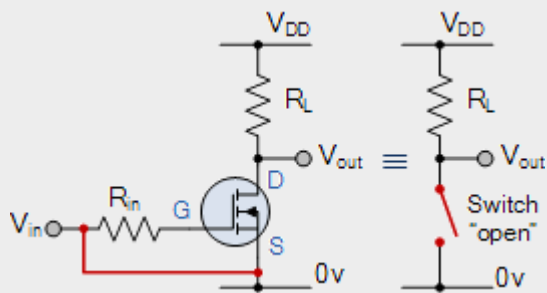- Drain-source junction conducts when **gate voltage** (V_{GS}) exceeds the **threshold voltage** (V_T)
- N-channel MOSFETS are **low-side** switches
- P-channel MOSFETS are **high-side** switches




$V_{GS} = 0$: Switch "open"

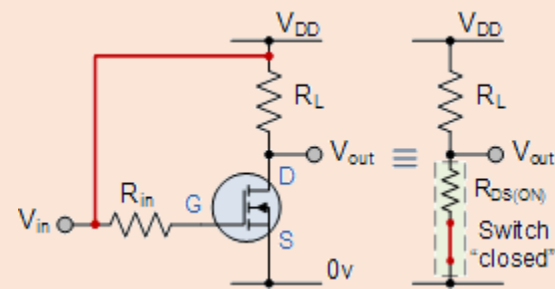


$V_{GS} = V_{DD}$: Switch "closed"

MOSFETs

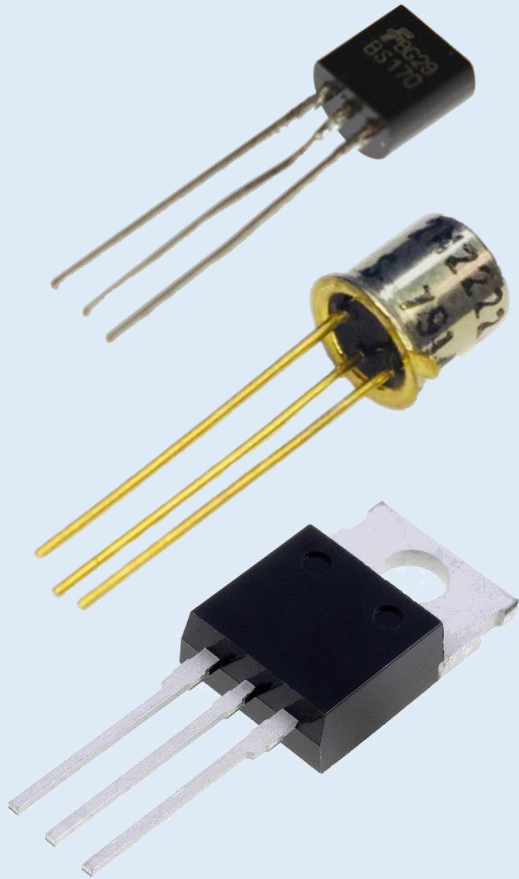

Through-hole (PTH)

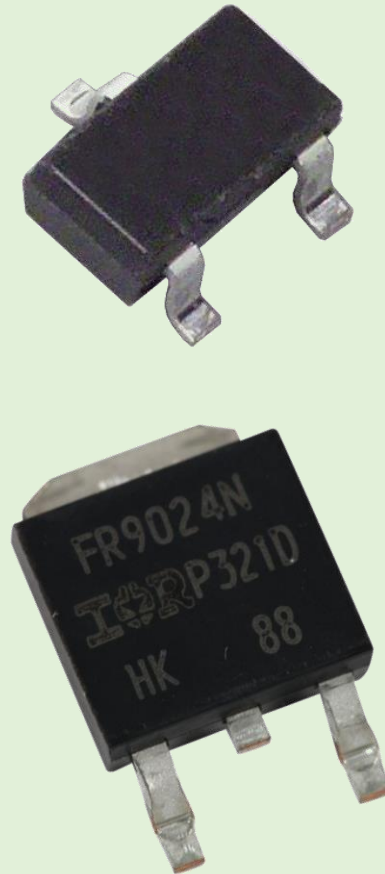


Surface-mount (SMD)


Operational amplifiers (op-amps)

Operational amplifiers

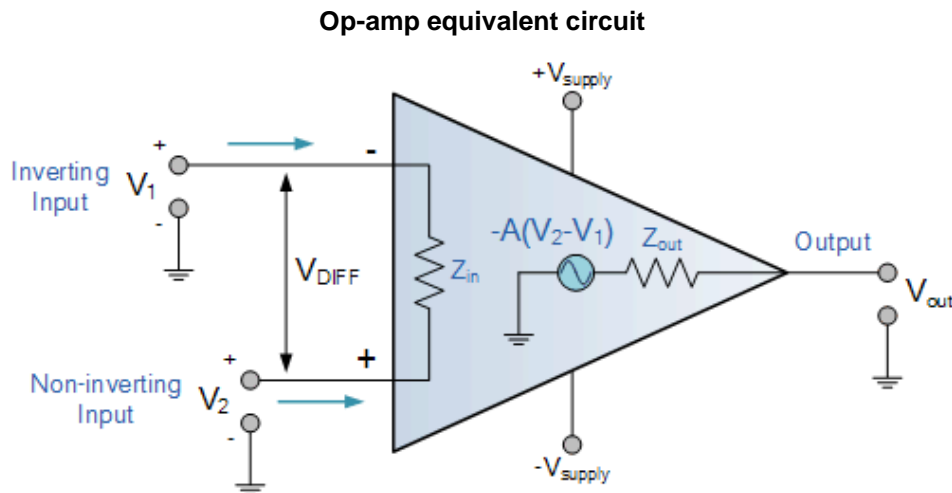- **Operational amplifier (op-amp):** Amplifies the difference between two voltages
- “Operational”: can be used for arithmetic operations (addition, subtraction, multiplication by a constant)
- Many common circuits can be enhanced with op-amps



μ A741 / LM741 pinout diagram

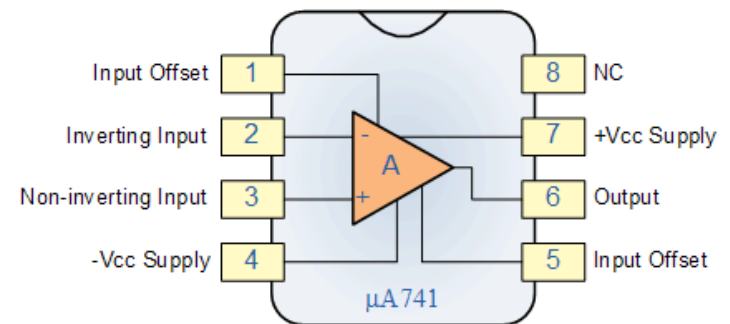

Ideal op-amp properties



Two “golden rules”¹ of op-amps:

1. In a **closed loop** the output attempts to do whatever is necessary to make the voltage difference between the inputs zero.
2. The inputs draw no current.

¹ Horowitz, Paul; Hill, Winfield (1989). *The Art of Electronics*.

Inverting amplifier

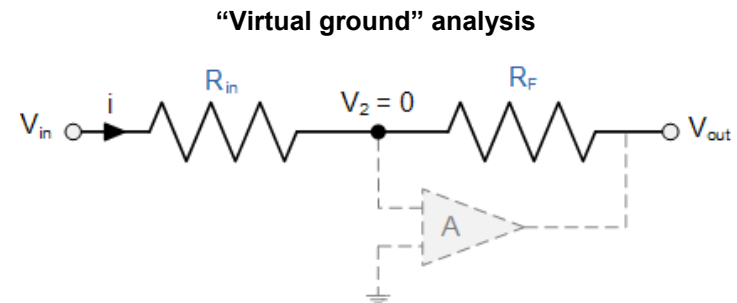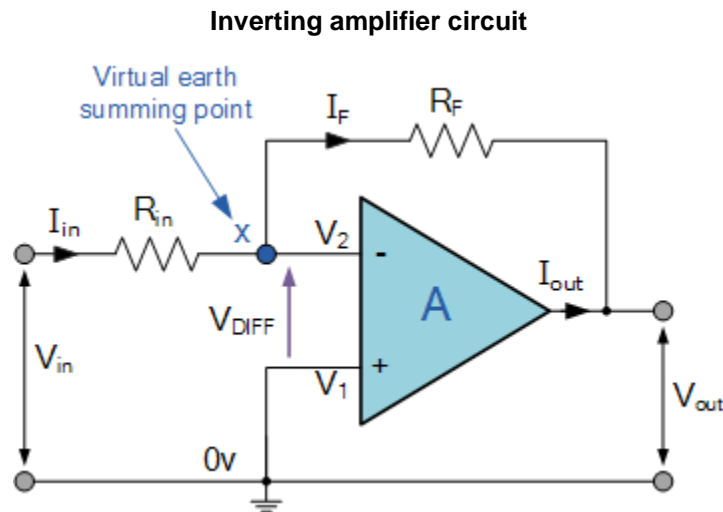- **Inverting amplifier:** Multiplies input by a negative constant (A_V)
- To solve for voltage gain, assume the output forces the difference ($V_1 - V_2$) to 0




$$\text{Gain } (A_V) = \frac{V_{out}}{V_{in}} = -\frac{R_f}{R_{in}}$$


Non-inverting amplifier

- **Non-inverting amplifier:** Multiplies input by a positive constant (A_V)
- Voltage gain can be derived from “golden rules” and resistor divider formula

Non-inverting amplifier circuit

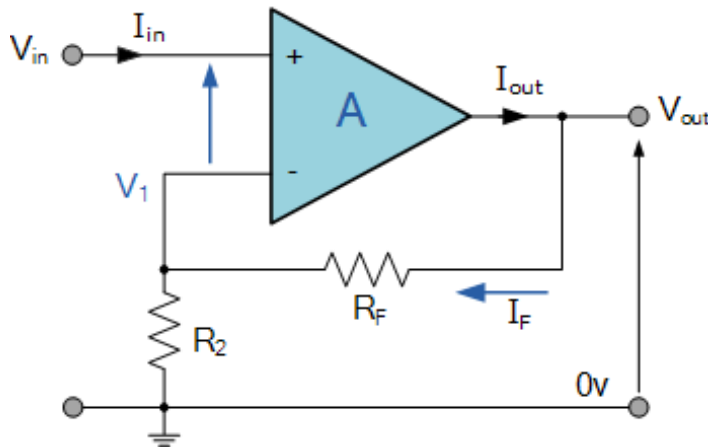



Voltage gain derivation

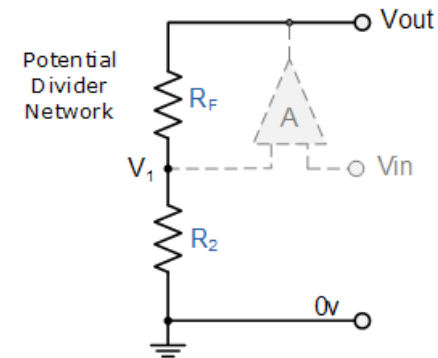

$$A_{(v)} = 1 + \frac{R_F}{R_2}$$


Op-amp LPF and HPF

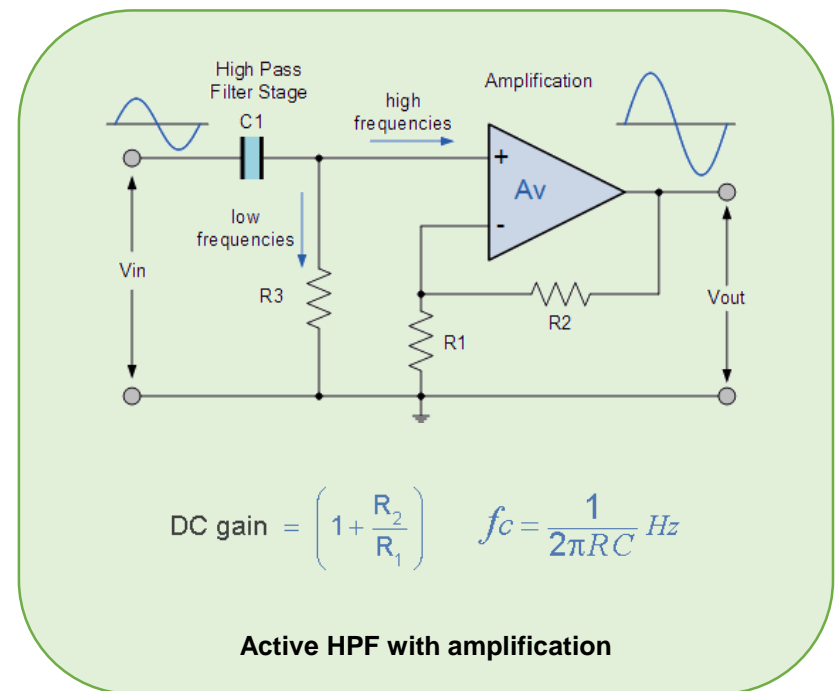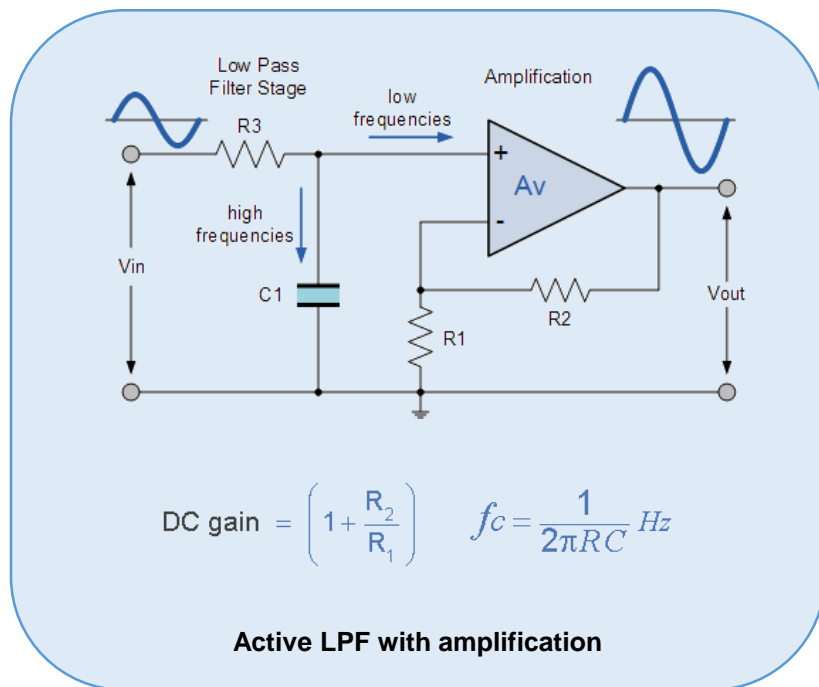- Same function as passive LPF and HPF
- Adds **amplification**, which is useful for small or high-impedance inputs



Op-amp BPF

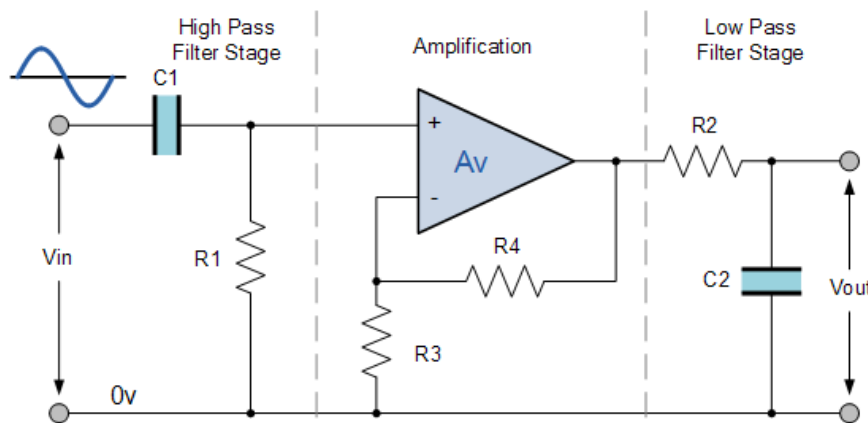- Same function as passive BPF
- Adds **amplification**, which is useful for small or high-impedance inputs
- Adds **isolation** between HPF and LPF stage





$$f_H = \frac{1}{2\pi R_1 C_1} \text{ Hz}$$

$$f_L = \frac{1}{2\pi R_2 C_2} \text{ Hz}$$

$$A_V = 1 + \frac{R_4}{R_3}$$



Comparator

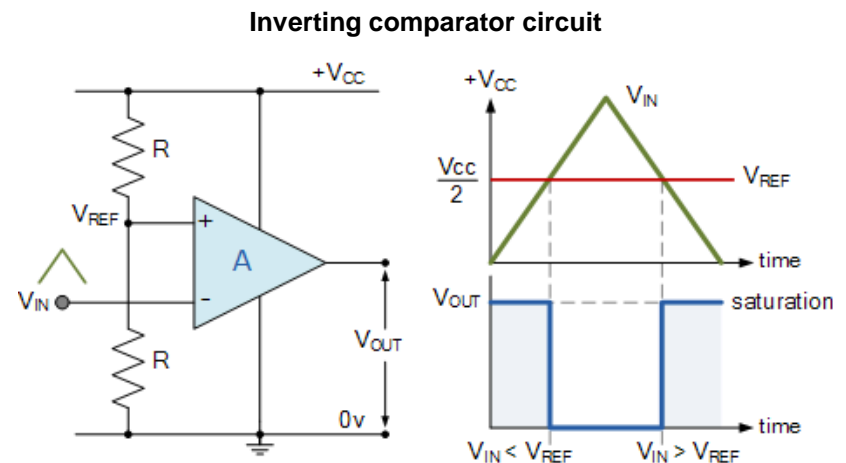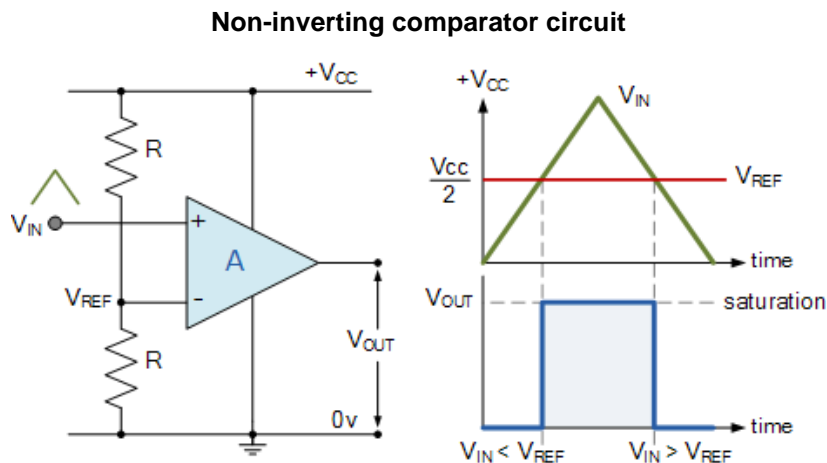- **Comparator:** Compares input voltage (V_{IN}) with reference voltage (V_{REF})
- Exploits “infinite” gain to produce **binary output**
- Most op-amps cannot operate **rail-to-rail**



Comparator with hysteresis

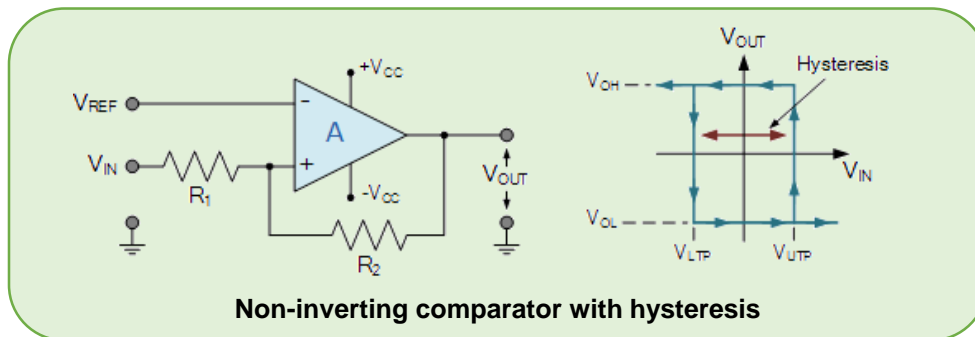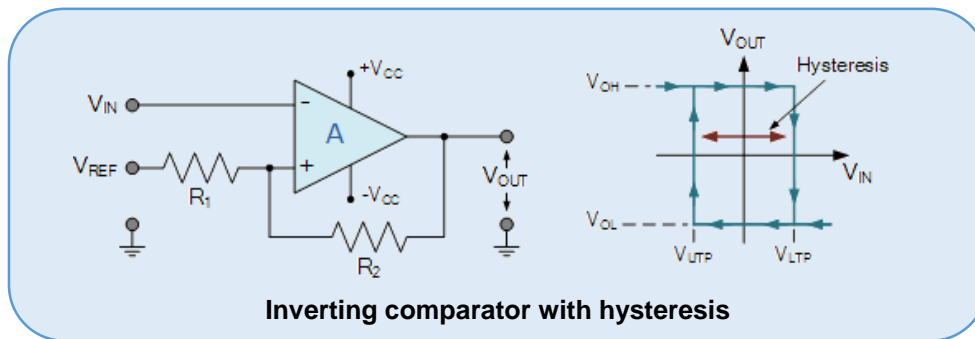- **Hysteresis:** Removes noise from comparator output
- Creates upper and lower “trip points” (V_{UTP} and V_{LTP})
- Amount of hysteresis determined by R_1 and R_2



$$\beta = \frac{R_1}{R_1 + R_2}$$

$$V_{HYSTERESIS} = V_{UTP} - V_{LTP}$$


$$V_{HYSTERESIS} = +\beta V_{CC} - (-\beta V_{CC})$$

$$\therefore V_{HYSTERESIS} = 2\beta V_{CC}$$

Audio amplification


Class A amplifier

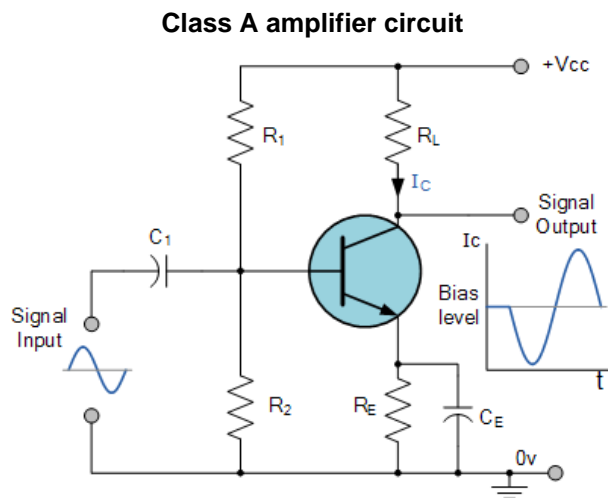- **Class A amplifier:** Uses BJT to “pull down” output
- Value of **load resistor** (R_L) determines voltage gain
- Commonly used on input stage for **high voltage gain**
- Not ideal as a power amplifier due to **low efficiency**





Class A amplifier voltage gain and efficiency
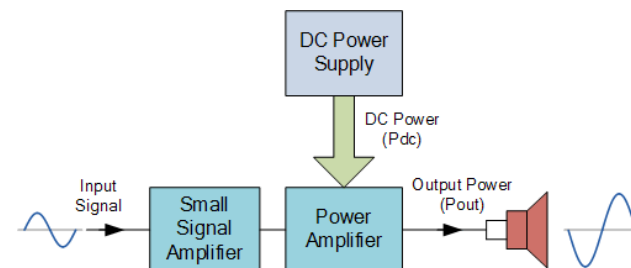
$$\text{Voltage Gain} = \frac{V_{out}}{V_{in}} = \frac{\Delta V_L}{\Delta V_B} = -\frac{R_L}{R_E}$$




Class B amplifier

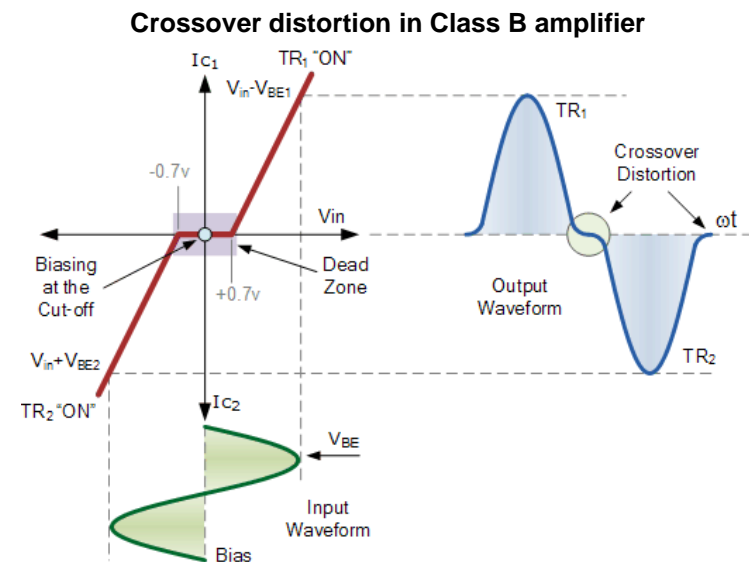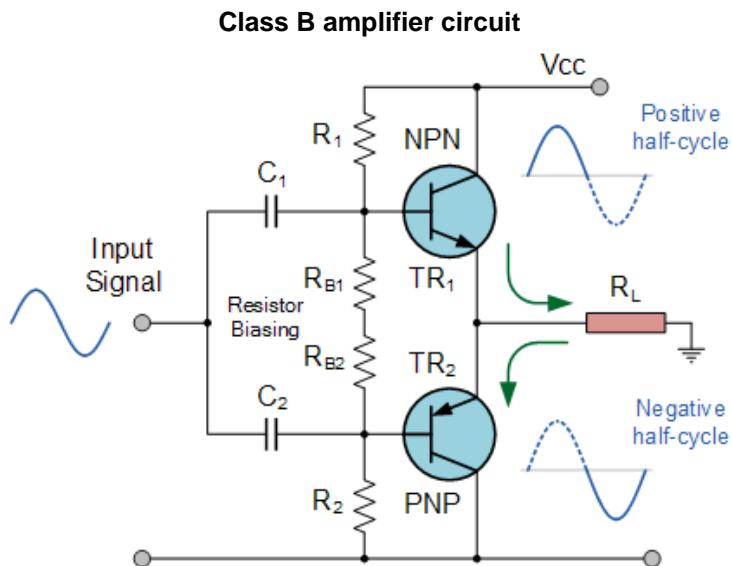- **Class B amplifier:** Much more efficient than Class A
- Uses “**push-pull**” output: only one BJT on at a time
- Introduces **crossover distortion** in the output signal




Distortion

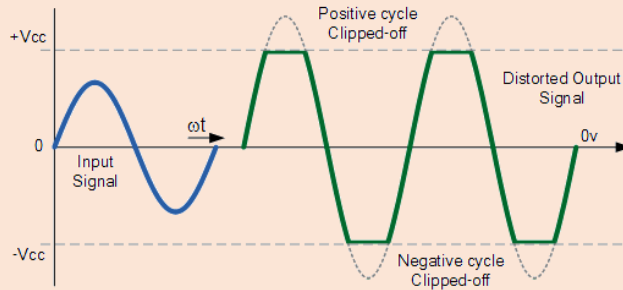


Amplitude distortion

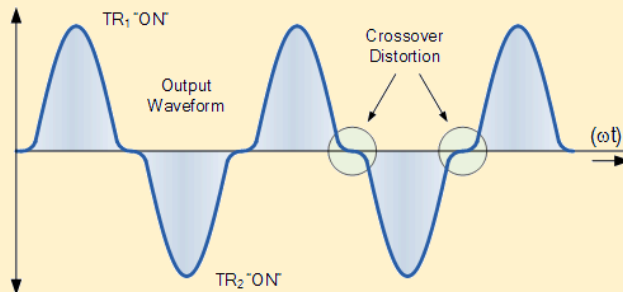- Caused when signal “clips” above or below the power supply rails
- Detrimental to signal quality
- Eliminate by increasing power supply voltage or decreasing input



Crossover distortion

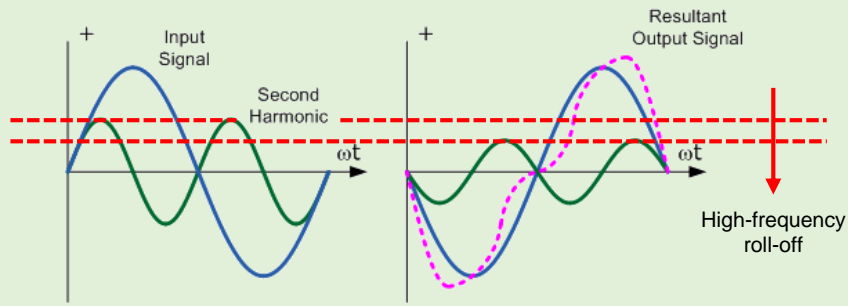- Caused when output signal crosses through 0 volts
- Can have significant effects when input is small
- Eliminate by biasing output stage slightly on at all times (Class AB)





Frequency distortion

- Caused when amplifier frequency response is nonlinear
- Minimal effects on signal quality
- Eliminate by using transistors with lower input/output capacitance

Class AB amplifier

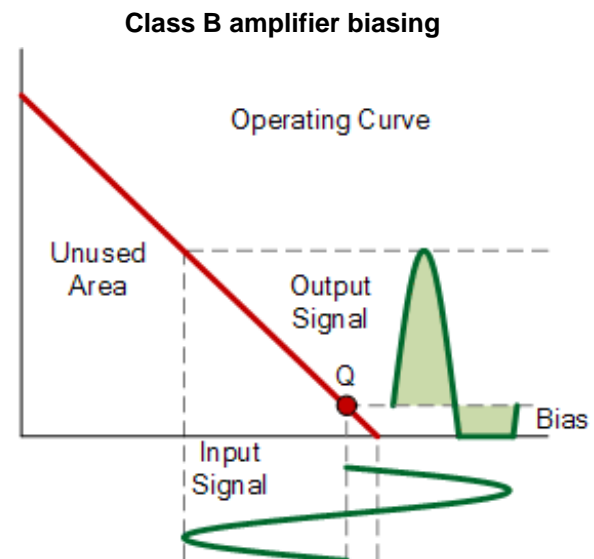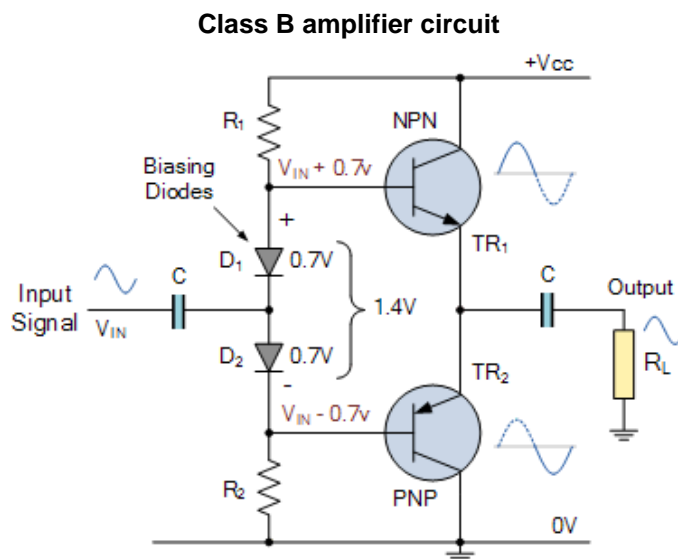
- Same principle as Class B, but with added **bias voltage**
- **Biassing diodes** keep both output transistors on slightly after the input crosses 0 volts
- Result: minimal **crossover distortion**, less efficient



Summary of amplifier classes

- **Class A:** High quality, low efficiency
- **Class B:** Low quality, high efficiency
- **Class AB:** High quality, average efficiency

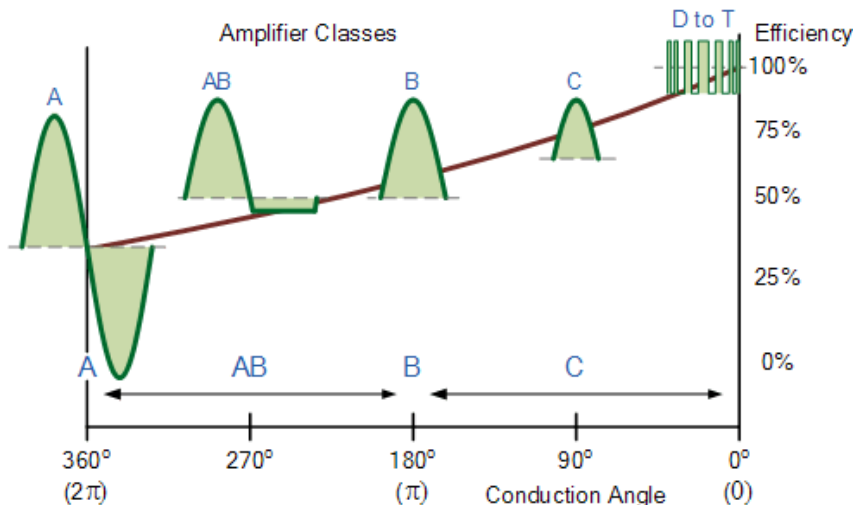Conduction angle and efficiency comparison



Summary of characteristics

Characteristic	Class A	Class B	Class AB
Signal quality	High	Low	High
Efficiency	Low	High	Medium
Conduction angle	360°	180°	180° – 360°
Output impedance	High	Medium	Low

Lab 2 overview

Components and specifications

Exercise 1: Op-amps

- **Goal:** Build and test basic op-amp circuits
- **New parts:** LM741 op-amp
- **Power pins are hidden** on schematic by convention but must be connected
- Be extremely careful not to switch **positive and negative power supplies**

LM741

Supply voltage: Most op-amps rated for dual-supply operation

Short circuit duration: Very tolerant of breadboard accidents

Input offset voltage: Should be low for high-precision applications

Input bias current: Higher for bipolar devices (LM741), lower for JFET devices (LF356)

Slew rate: Important if used in high-frequency circuits


6.1 Absolute Maximum Ratings

over operating free-air temperature range (unless otherwise noted)⁽¹⁾⁽²⁾⁽³⁾

		MIN	MAX	UNIT
Supply voltage	LM741, LM741A		±22	V
	LM741C		±18	V
Power dissipation ⁽⁴⁾			500	mW
Differential input voltage			±30	V
Input voltage ⁽⁵⁾			±15	V
Output short circuit duration			Continuous	
Operating temperature	LM741, LM741A	-50	125	°C
	LM741C	0	70	°C
Junction temperature	LM741, LM741A		150	°C
	LM741C		100	°C
Soldering information	PDIP package (10 seconds)		260	°C
	CDIP or TO-99 package (10 seconds)		300	°C
Storage temperature, T _{stg}		-65	150	°C

6.5 Electrical Characteristics, LM741⁽¹⁾

PARAMETER	TEST CONDITIONS		MIN	TYP	MAX	UNIT
Input offset voltage	R _S ≤ 10 kΩ	T _A = 25°C T _{AMIN} ≤ T _A ≤ T _{AMAX}		1	5	mV
Input offset voltage adjustment range	T _A = 25°C, V _S = ±20 V			±15		mV
Input offset current	T _A = 25°C			20	200	nA
Input bias current	T _{AMIN} ≤ T _A ≤ T _{AMAX} T _A = 25°C			85	500	nA
Input resistance	T _{AMIN} ≤ T _A ≤ T _{AMAX} T _A = 25°C, V _S = ±20 V		0.3	2		MΩ
Input voltage range	T _{AMIN} ≤ T _A ≤ T _{AMAX}		±12	±13		V
Large signal voltage gain	V _S = ±15 V, V _O = ±10 V, R _L ≥ 2 kΩ	T _A = 25°C T _{AMIN} ≤ T _A ≤ T _{AMAX}	50	200		V/mV
Output voltage swing	V _S = ±15 V	R _L ≥ 2 kΩ	±12	±14		V
Output short circuit current	T _A = 25°C			25		mA
Common-mode rejection ratio	R _S ≤ 10 Ω, V _{CM} = ±12 V, T _{AMIN} ≤ T _A ≤ T _{AMAX}		80	95		dB
Supply voltage rejection ratio	V _S = ±20 V to V _S = ±5 V, R _S ≤ 10 Ω, T _{AMIN} ≤ T _A ≤ T _{AMAX}		86	96		dB
Transient response	Rise time	T _A = 25°C, unity gain		0.3		μs
	Overshoot			5%		
Slew rate	T _A = 25°C, unity gain			0.5		V/μs
Supply current	T _A = 25°C		1.7	2.8		mA
Power consumption	V _S = ±15 V	T _A = 25°C	50	85		mW
		T _A = T _{AMIN}	60	100		
		T _A = T _{AMAX}	45	75		

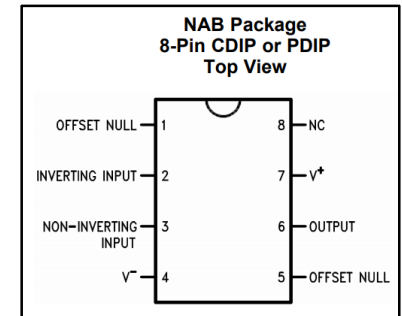

Offset adjustment: Offset can be “nulled” with a potentiometer connected from pin 1 to pin 5

Voltage gain: Nearly infinite (200 V / mV = 200,000 V / V)

Output swing: Most op-amps will not operate “rail-to-rail”

Exercise 2: LED driver

- **Goal:** use BJT and function generator to drive an LED
- **New parts:** 2N3904 BJT (NPN)
- Very important to check **orientation** of transistors

2N3904

Pin diagram: Pinning for 2N3904 is like "ABC" (actually EBC)

"Absolute maximum" ratings: Values outside these ranges will cause permanent damage to the device

Maximum voltages: Limited by power supply (V_{CEO} , V_{CBO}) or input range (V_{EBO})


Maximum current: Limited by load impedance

Gain-bandwidth product: Defines maximum gain in an amplifier

Small-signal gain: Ratio of collector current to base current

MAXIMUM RATINGS

Rating	Symbol	Value	Unit
Collector - Emitter Voltage	V_{CEO}	40	Vdc
Collector - Base Voltage	V_{CBO}	60	Vdc
Emitter - Base Voltage	V_{EBO}	6.0	Vdc
Collector Current - Continuous	I_C	200	mAdc
Total Device Dissipation @ $T_A = 25^\circ\text{C}$ Derate above 25°C	P_D	625	mW
		5.0	mW/ $^\circ\text{C}$
Total Device Dissipation @ $T_C = 25^\circ\text{C}$ Derate above 25°C	P_D	1.5	W
		12	mW/ $^\circ\text{C}$
Operating and Storage Junction Temperature Range	T_J, T_{stg}	-55 to +150	$^\circ\text{C}$

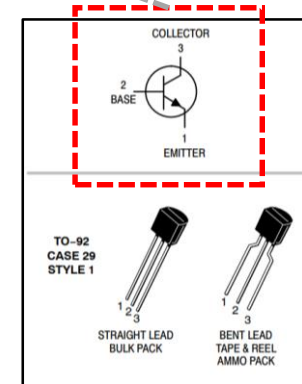

SMALL-SIGNAL CHARACTERISTICS

Characteristic	2N3903	2N3904	f_T	250	300	—	—	MHz
Current - Gain - Bandwidth Product ($I_C = 10$ mAdc, $V_{CE} = 20$ Vdc, $f = 100$ MHz)	2N3903	2N3904	f_T	250	300	—	—	MHz
Output Capacitance ($V_{CB} = 5.0$ Vdc, $I_E = 0$, $f = 1.0$ MHz)			C_{obo}	—	—	4.0	—	pF
Input Capacitance ($V_{EB} = 0.5$ Vdc, $I_C = 0$, $f = 1.0$ MHz)			C_{ibo}	—	—	8.0	—	pF
Input Impedance ($I_C = 1.0$ mAdc, $V_{CE} = 10$ Vdc, $f = 1.0$ kHz)	2N3903	2N3904	h_{ie}	1.0	1.0	8.0	10	k Ω
Voltage Feedback Ratio ($I_C = 1.0$ mAdc, $V_{CE} = 10$ Vdc, $f = 1.0$ kHz)	2N3903	2N3904	h_{re}	0.1	0.5	5.0	8.0	$\times 10^{-4}$
Small-Signal Current Gain ($I_C = 1.0$ mAdc, $V_{CE} = 10$ Vdc, $f = 1.0$ kHz)	2N3903	2N3904	h_{fe}	50	100	200	400	—
Output Admittance ($I_C = 1.0$ mAdc, $V_{CE} = 10$ Vdc, $f = 1.0$ kHz)			h_{oe}	1.0	—	40	—	μmhos
Noise Figure ($I_C = 100$ μAdc , $V_{CE} = 5.0$ Vdc, $R_S = 1.0$ k Ω , $f = 1.0$ kHz)	2N3903	2N3904	NF	—	—	6.0	5.0	dB

Source: <https://www.onsemi.com/pub/Collateral/2N3903-D.PDF>

Exercise 3: Audio amplifier

- **Goal:** Build a high-quality, high-efficiency audio amplifier
- **New parts:** TIP41, TIP42 complementary power BJTs
- Don't force large pins into breadboard, look at the holes and **make sure the pins line up**
- Make sure **output capacitor** is oriented correctly

TIP41, TIP42

Collector-emitter voltage: Capable of switching high voltages

Packaging: Collector electrically connected to case


Collector current: Capable of driving high-current loads

Power dissipation: Capable of dissipating much more power than small-signal devices (2N3904)

DC current gain: Much lower current gain than small-signal devices

MAXIMUM RATINGS


Rating	Symbol	Value	Unit
Collector-Emitter Voltage TIP41, TIP42 TIP41A, TIP42A TIP41B, TIP42B TIP41C, TIP42C	V_{CEO}	40 60 80 100	Vdc
Collector-Base Voltage TIP41, TIP42 TIP41A, TIP42A TIP41B, TIP42B TIP41C, TIP42C	V_{CB}	40 60 80 100	Vdc
Emitter-Base Voltage	V_{EB}	5.0	Vdc
Collector Current- Continuous Peak	I_C	6.0 10	Adc
Base Current	I_B	2.0	Adc
Total Power Dissipation @ $T_C = 25^\circ\text{C}$ Derate above 25°C	P_D	65 0.52	W W/ $^\circ\text{C}$
Total Power Dissipation @ $T_A = 25^\circ\text{C}$ Derate above 25°C	P_D	2.0 0.016	W W/ $^\circ\text{C}$
Unclamped Inductive Load Energy (Note 1)	E	62.5	mJ
Operating and Storage Junction, Temperature Range	T_J, T_{stg}	-65 to +150	$^\circ\text{C}$

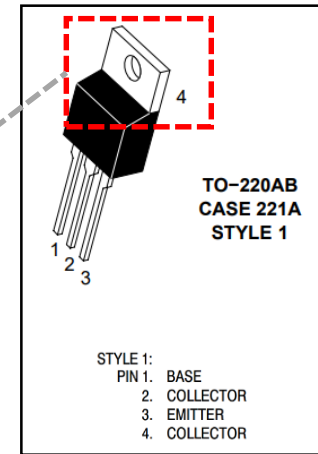

ELECTRICAL CHARACTERISTICS ($T_C = 25^\circ\text{C}$ unless otherwise noted)

Characteristic	Symbol	Min	Max	Unit
OFF CHARACTERISTICS				
Collector-Emitter Sustaining Voltage (Note 2) ($I_C = 30 \text{ mAdc}, I_B = 0$)	$V_{CEO(sus)}$	40 60 80 100	- - - -	Vdc
Collector Cutoff Current ($V_{CE} = 30 \text{ Vdc}, I_B = 0$) ($V_{CE} = 60 \text{ Vdc}, I_B = 0$)	I_{CEO}	- -	0.7 0.7	mAdc
Collector Cutoff Current ($V_{CE} = 40 \text{ Vdc}, V_{EB} = 0$) ($V_{CE} = 60 \text{ Vdc}, V_{EB} = 0$) ($V_{CE} = 80 \text{ Vdc}, V_{EB} = 0$) ($V_{CE} = 100 \text{ Vdc}, V_{EB} = 0$)	I_{CES}	- - - -	400 400 400 400	μAdc
Emitter Cutoff Current ($V_{BE} = 5.0 \text{ Vdc}, I_C = 0$)	I_{EBO}	-	1.0	mAdc
ON CHARACTERISTICS (Note 2)				
DC Current Gain ($I_C = 0.3 \text{ Adc}, V_{CE} = 4.0 \text{ Vdc}$) ($I_C = 3.0 \text{ Adc}, V_{CE} = 4.0 \text{ Vdc}$)	h_{FE}	30 15	- 75	-
Collector-Emitter Saturation Voltage ($I_C = 6.0 \text{ Adc}, I_B = 600 \text{ mAdc}$)	$V_{CE(sat)}$	-	1.5	Vdc
Base-Emitter On Voltage ($I_C = 6.0 \text{ Adc}, V_{CE} = 4.0 \text{ Vdc}$)	$V_{BE(on)}$	-	2.0	Vdc

Audio amplifier analysis

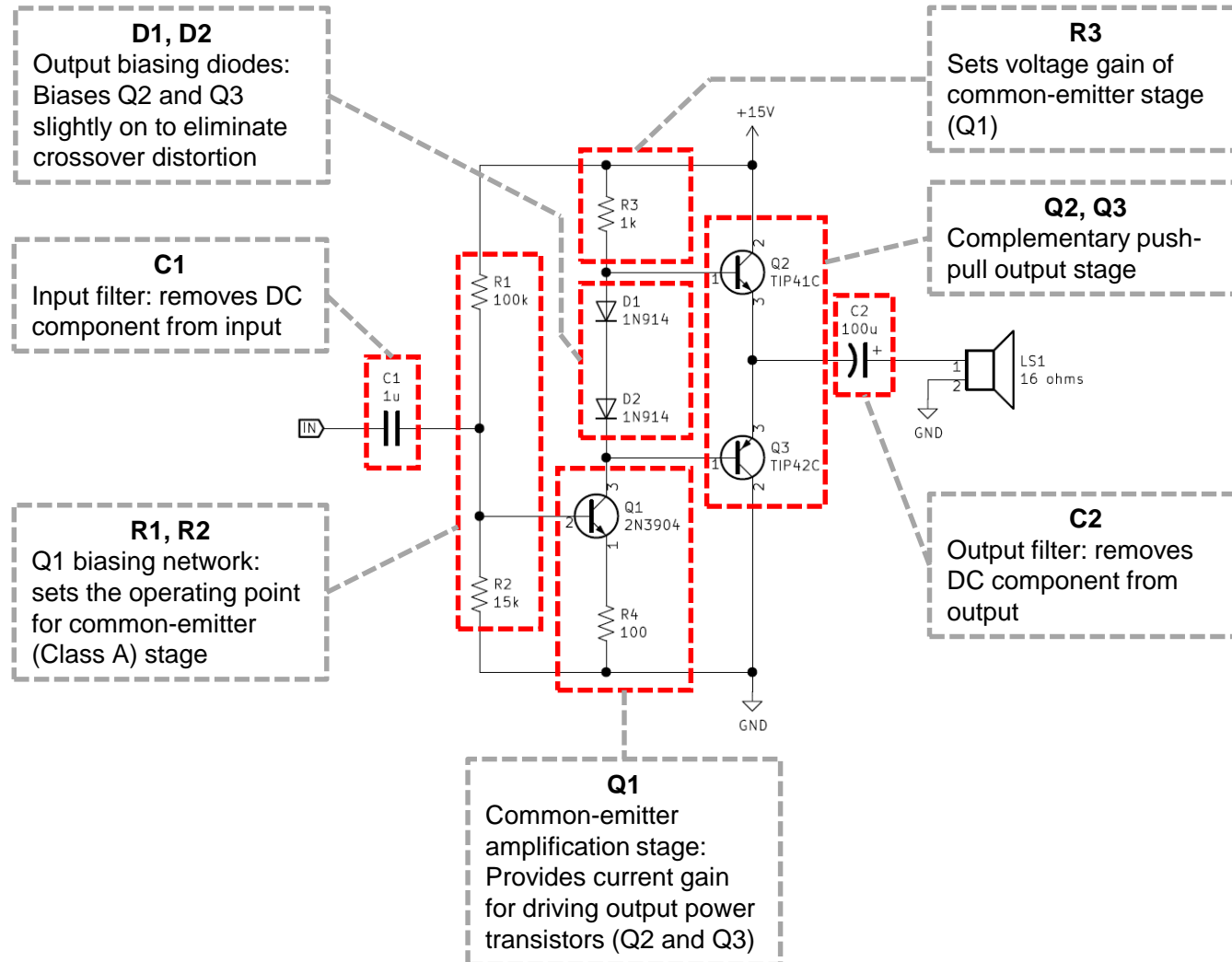

Further reading

- Filter design tool:
<http://sim.okawa-denshi.jp/en/Fkeisan.htm>
- Advanced BJT theory (from 6.012 course notes):
https://ocw.mit.edu/courses/electrical-engineering-and-computer-science/6-012-microelectronic-devices-and-circuits-spring-2009/lecture-notes/MIT6_012S09_lec17.pdf
- Overview of amplifier classes:
<https://www.maximintegrated.com/en/design/technical-documents/tutorials/5/5590.html>