

	Specification	Calculated	Simulated
Open-loop transimpedance	$> 200 \text{ k}\Omega$	$500 \text{ k}\Omega$	$800 \text{ k}\Omega$
Input common mode	$\pm 10 \text{ V}$	$\pm 13.8 \text{ V}$	$14.8 \text{ V}$
Output swing	$\pm 10 \text{ V}$	$\pm 13.8 \text{ V}$	$\pm 14.3 \text{ V}$
Output current	$\pm 10 \text{ mA}$	-	$\pm 250 \text{ mA}$
Power consumption	$< 250 \text{ mW}$	$210 \text{ mW}$	$205 \text{ mW}$
Phase margin	$> 70^\circ$		$74^\circ$

# Design Process

The three key components of the transimpedance amplifier are the input buffer, current mirror, and output buffer stages. The input buffer is provided for us as a diamond buffer configuration. This leaves the current mirror and output buffer design.

For the current mirror, we want a mirror with low error and a high output resistance. This output resistance will form the transimpedance of the amplifier, and thus needs to be sufficiently large (greater than 200 k $\Omega$ ). Using a Wilson current mirror, we achieve very low error ( $\frac{2}{\beta^2}$ ) and a high output resistance ( $\frac{\beta r_o}{2}$ ).

For the output buffer, we use the same structure as the input buffer, a diamond buffer. This buffer has low offset, due to the matching  $V_{be}$  drops, and a current gain of  $\beta^2$ . The buffer also has a large input impedance to create the high impedance node.

## Design Calculations

### Open-loop transimpedance

PNP Wilson mirror:  $R_{O,PNP} = \frac{\beta r_o}{2} = 625 \text{ k}\Omega$

NPN Wilson mirror:  $R_{O,NPN} = \frac{\beta r_o}{2} = 5 \text{ M}\Omega$

Output buffer:  $R_I = (r_{\pi,NPN} + \beta_{NPN}(r_{\pi,PNP} + \beta_{PNP}1\text{k}\Omega)) || (r_{\pi,PNP} + \beta_{PNP}(r_{\pi,NPN} + \beta_{NPN}1\text{k}\Omega))$   
 $R_I = 5.1 \text{ M}\Omega$

$Z = 500 \text{ k}\Omega$

### Input and output range

Our input and output buffers are designed to go nearly rail to rail, requiring only the 0.6 V margin for the  $V_{be}$  drops. However, the current mirror adds an extra  $V_{be}$  drop, so our final input and output swings are  $\pm 13.8 \text{ V}$ .

### Output current

Since our output buffer has a current gain of  $\beta_{NPN}\beta_{PNP} = 1000$ , we need an input current of only 10  $\mu\text{A}$  to produce an output current of 10 mA.

## Power consumption

Our power consumption is made up of the 4 current sources driving our diamond buffers, and the current that is mirrored in the second half of the buffers and in the current mirror. If we drive the buffer with a current  $I$ , we have a total current draw of  $7I$ , so we set  $I$  to 1 mA, setting a power consumption of 210 mW, which is below our specification of 250 mW.

# Spice Deck

```
*6.301 Design Project
*Transconductance Amplifier

.option post
.OP
**For AC Sweep
.AC DEC 100 1e3 1e9
.print ac vm(out) vp(out)
**For DC Sweep (output swing and current)
*.DC Vin -15 15 0.1
*.print dc v(out)

*Compensation test circuit
Vhigh vcc 0 DC 15
Vlow vee 0 DC -15
Vin 1 comm AC 1 0
R1 1 minus 1k
R2 out 0 1k
Voffs plus comm DC -12.7m
Vcm comm 0 DC 0
Xamp plus minus out vcc vee transamp

**Amplifier test - gain=11
*Vhigh vcc 0 DC 15
*Vlow vee 0 DC -15
*Vin plus 0 AC 1 0
*R1 out minus 1k
*R2 minus 0 100
*Xamp plus minus out vcc vee transamp

**Buffer test - measure common mode
*Vhigh vcc 0 DC 15
*Vlow vee 0 DC -15
*Vin plus 0 AC 1 0
*Rout out 0 1k
*Xamp plus out out vcc vee transamp

.SUBCKT transamp in.p in.m out vcc vee
```

```
*input diamond buffer
Q1 vee in.p 1 qnpn
Q2 3 1 in.m qnpn
Q3 vcc in.p 2 qnpn
Q4 5 2 in.m qnpn
I1 vcc 1 DC 1m
I2 2 vee DC 1m

*upper current mirror
Q5 3 4 vcc qnpn
Q6 4 4 vcc qnpn
Q7 7 3 4 qnpn

*lower current mirror
Q8 5 6 vee qnpn
Q9 6 6 vee qnpn
Q10 7 5 6 qnpn

*compensation capacitor
Cc 7 0 3pF


*output diamond buffer
Q11 vee 7 8 qnpn
Q12 vcc 8 out qnpn
Q13 vcc 7 9 qnpn
Q14 vee 9 out qnpn
I3 vcc 8 DC 1m
I4 9 vee DC 1m
.ENDS transamp

.MODEL qnpn npn
+ is=150fA bf=200
+ vaf=50 cje=10p
+ tf=750p cjc=1p


.MODEL qpnp pnp
+ is=150fA bf=50
+ vaf=25 cje=10p
+ tf=750p cjc=1p

.END
```



## Simulation Results

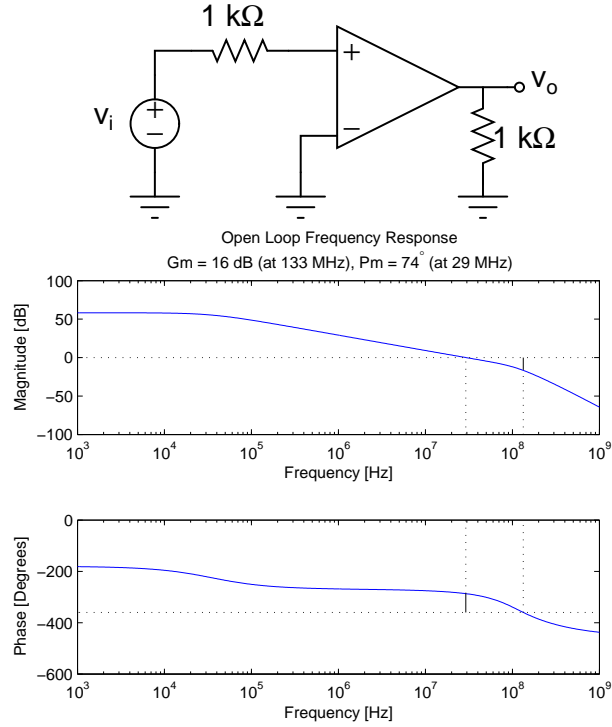


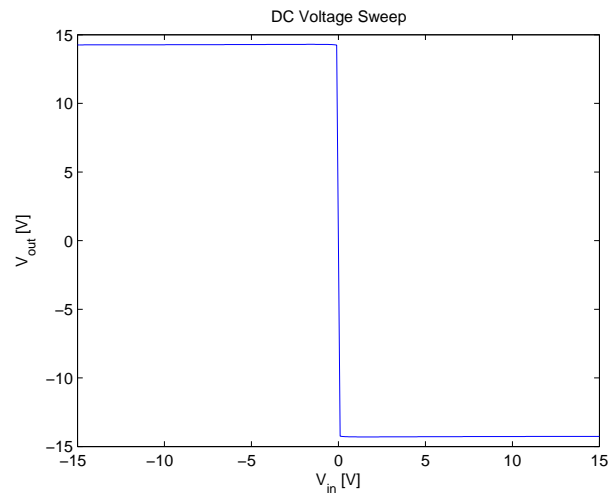
In the graph above, we see the results of simulating the amplifier running open loop. The low frequency gain 58 dB implies an open-loop transimpedance of  $800\text{ k}\Omega$ . To achieve the required phase margin, a  $3\text{ pF}$  capacitor is connected to the high impedance node in the amplifier, raising the phase margin to  $74^\circ$ .



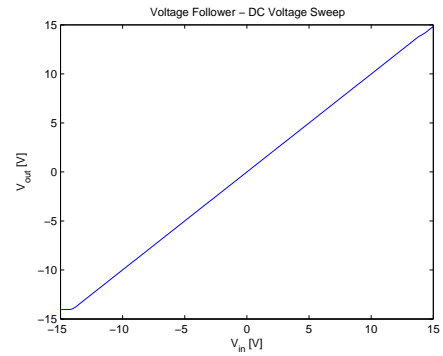 The DC sweep shows that the output swing is  $\pm 14.3\text{ V}$ , and that the output current is  $\pm 14.3\text{ mA}$ . By decreasing the load resistor to  $10\text{ }\Omega$ , we find that the maximum output current is  $\pm 250\text{ mA}$ .



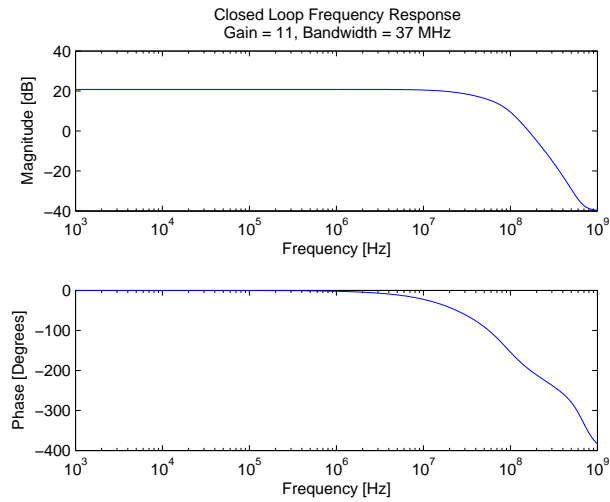 By using a voltage buffer, we can show that the amplifier can handle common mode inputs sweeping almost from rail to rail, with a common mode range of  $\pm 14.8\text{ V}$ .



The frequency response of the closed loop system shows that we achieve the expected gain of 11 from the amplifier, with a bandwidth of 37 MHz.