
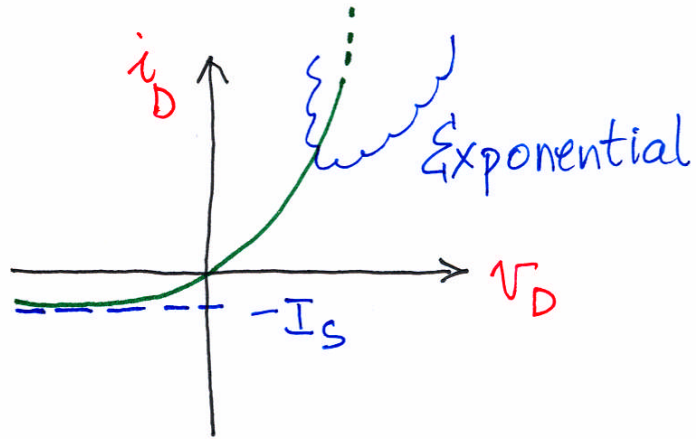


6.002 - Lecture 4

Circuits With Nonlinear Resistors

- Nonlinear Resistor Example $\Rightarrow$ Diode
- Circuits With Nonlinear Resistors
- Analysis Options:
 - Closed-Form (Difficult)
 - Numerical (Mention Only)
 - Graphical (Provides Intuition)
 - Piecewise Linear Approximation (Later)
 - Linearized/Incremental (Mainstay)

Exponential Diode

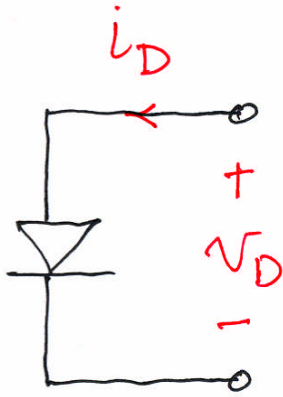

$$i_D = I_S \left(e^{\frac{V_D}{K T / q}} - 1 \right)$$



$$\frac{K T}{q} \approx 26 \text{ mV @ } 300 \text{ C}$$

$$I_S \approx 10^{-13} \text{ A} \dots 10^{-9} \text{ A}$$

(Signal) (Power)

- Common in communication, power and lighting applications.
- Solar cells, LEDs, and many rectifiers and photodetectors are diodes.

Circuits With Nonlinear Resistors

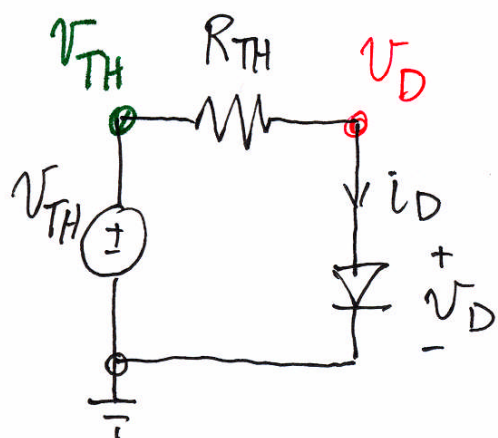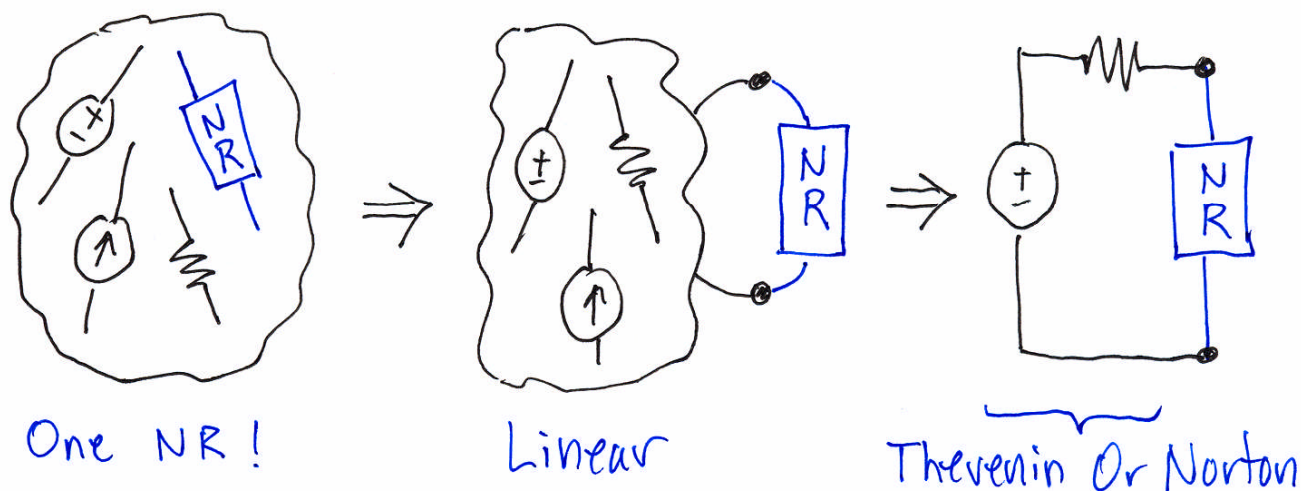


Node method still works!

$$\frac{V_D - V_{TH}}{R_{TH}} + I_S \left(e^{\frac{V_D}{kT/q}} - 1 \right) = 0$$

No closed-form solution, so:


- numerical analysis;
- graphical analysis;
- approximate analysis;
- linearized/incremental analysis.

Graphical (Load-Line) Analysis

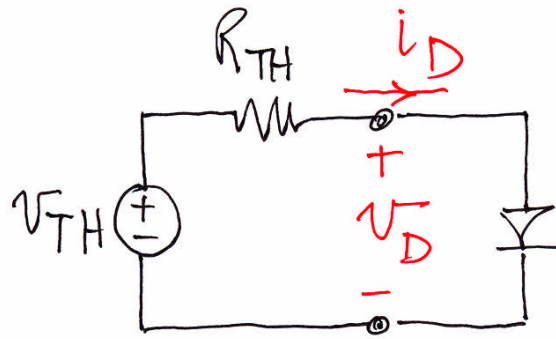


Thevenin: $V_D = V_{TH} - R_D i_D$


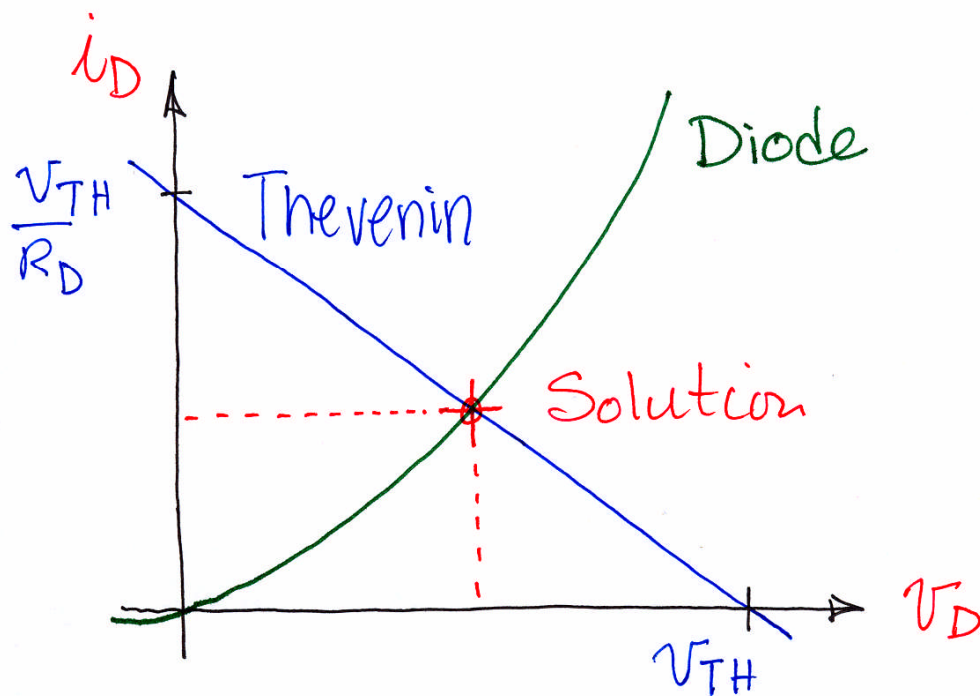
Diode: $i_D = I_s (e^{\frac{V_D}{K T / q}} - 1)$



Motivating Small Signals

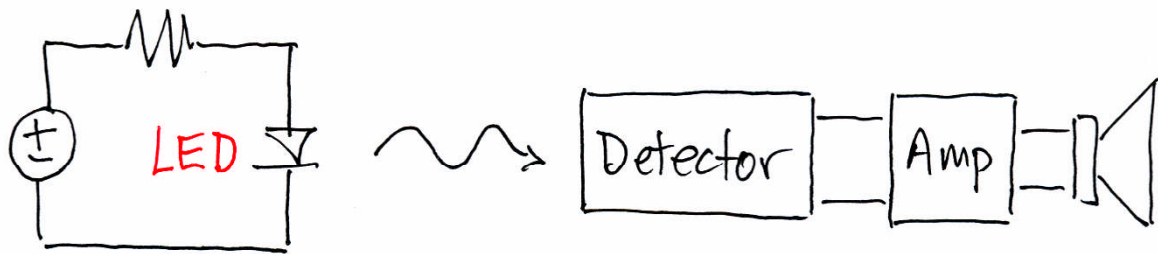

Small-Signal Analysis (I)

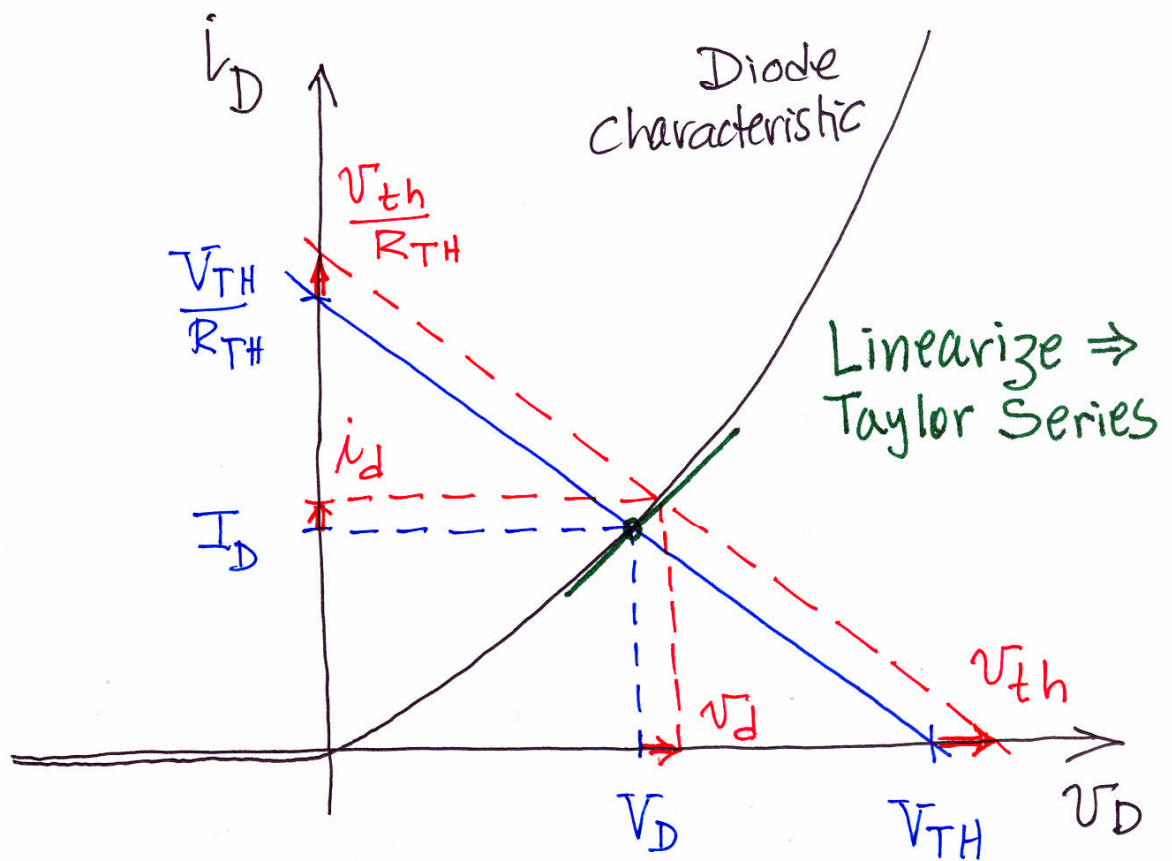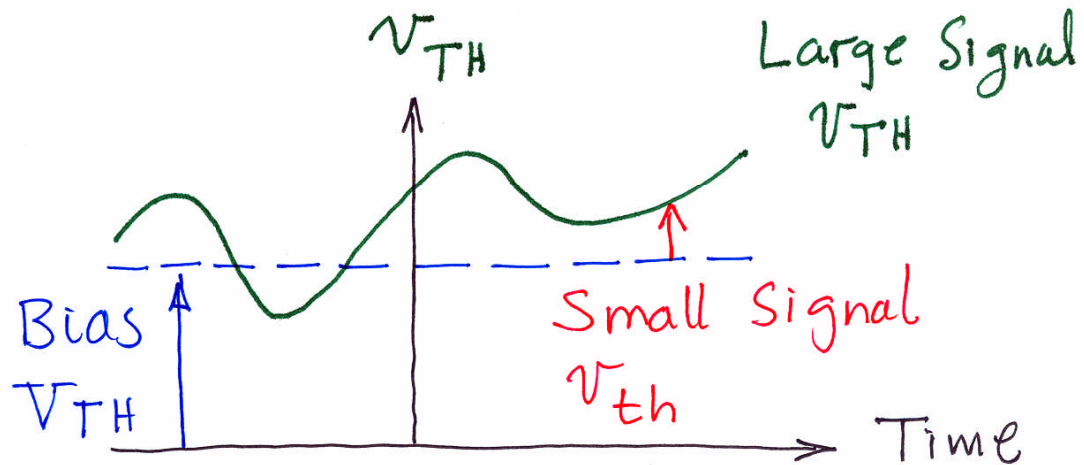

Small-Signal Analysis (II)

Signal Components:

$$\begin{aligned} V_{TH} &= V_{TH} + v_{th} \\ V_D &= V_D + v_d \\ i_D &= I_D + i_d \end{aligned}$$

Totals Biases Increments

Biases:

$$\frac{V_D - V_{TH}}{R_{TH}} + \underbrace{I_S \left(e^{\frac{V_D}{K T / q}} - 1 \right)}_{I_D} = 0$$

Totals:

$$\frac{V_D + v_d - V_{TH} - v_{th}}{R_{TH}} + \underbrace{I_S \left(e^{\frac{V_D + v_d}{K T / q}} - 1 \right)}_{i_D = I_D + i_d} = 0$$

Small-Signal Analysis (III)

Linearize: $f(v_D = \bar{V}_D + v_d) \approx f(\bar{V}_D) + \frac{df}{dv_D}(\bar{V}_D) \cdot v_d$

Linearized to take:

$$\frac{\bar{V}_D + v_d - V_{TH} - v_{th}}{R_{TH}} + I_D + \underbrace{\frac{I_S}{KT/q} e^{\frac{V_D}{KT/q}}}_{i_d} v_d \approx 0$$

Biases Cancel $\approx I_D$

Small Signals:

$$\frac{v_d - v_{TH}}{R_{TH}} + \frac{I_D}{KT/q} v_d \approx 0$$

$$v_d \approx \frac{1}{1 + R_{TH} I_D / \frac{KT}{q}} v_{th}$$

$$i_d \approx \frac{di_D}{dv_D}(\bar{V}_D) v_d \approx \frac{I_D}{KT/q} v_d$$