 


6.002 - Lecture 5


Digital Logic Gates

- Electrical Requirements
- Electronic Switch
- MOSFET Switch
- Gate Design & Operation


Static Discipline



Inverter Electrical Requirements

 



IN	OUT
L	H
H	L

 


$$0 \leq V_{OL} < V_{IL} < V_{IH} < V_{OH} \leq V_S$$

$$|\text{Slope}| \geq \frac{V_{OH} - V_{OL}}{V_{IH} - V_{IL}} > 1 \Rightarrow \text{Need new device!}$$

Three - Terminal Electronic Switch

 
 


Inverter Design

 


$$V_{IN} \leq \bar{V}_T$$

$$V_{IN} > \bar{V}_T$$

  


Inverter Analysis


 


$$\begin{array}{ccccccc}
 \underbrace{V_L}_{\text{Noise Margin}} & & \underbrace{\text{Noise Margin}} & & \underbrace{\text{Noise Margin}} & & \underbrace{V_H} \\
 0 \leq \frac{R_{ON} V_S}{R_{ON} + R_{PU}} \leq V_{OL} < V_{IL} < V_T < V_{IH} < V_{OH} \leq V_S \leq V_S \\
 \uparrow \quad \quad \uparrow \quad \quad \uparrow \quad \quad \uparrow \quad \quad \uparrow \quad \quad \uparrow \quad \quad \uparrow \\
 \text{Free} \quad \text{Design} \quad \text{Static Discipline} \quad \text{Design} \quad \text{Design} \quad \text{Design} \quad \text{Free}
 \end{array}$$

n-Channel MOSFET As A Switch

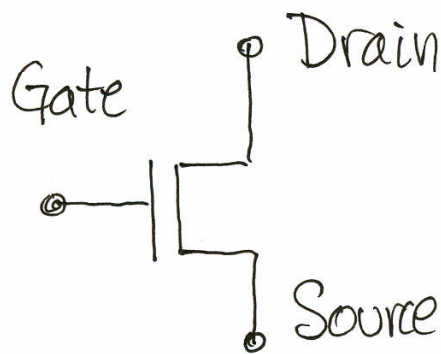


Defn $\Rightarrow V_{DS} \geq 0$

  


$\Rightarrow$ Switch - Resistor Model For Logic

Digital Gates (NMOS)

 

Inverter

IN	OUT
L	H
H	L

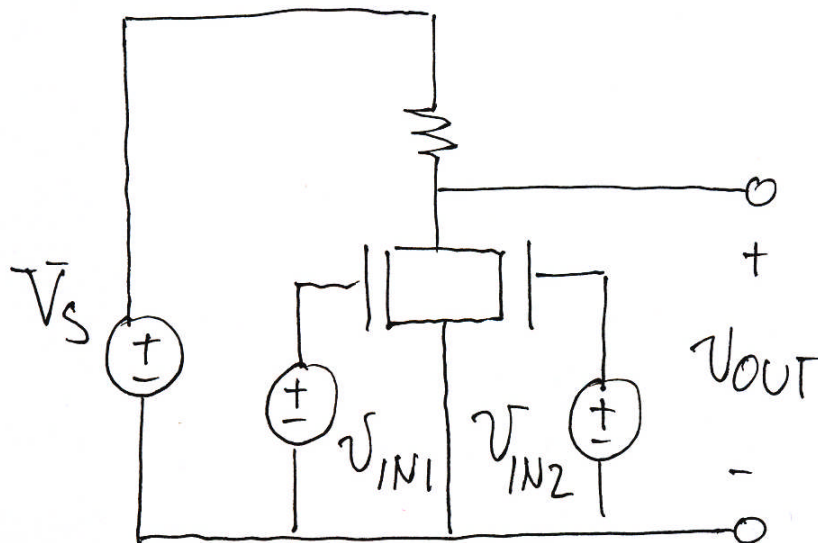

NOR Gate

IN1	IN2	OUT
L	L	H
L	H	L
H	L	L
H	H	L