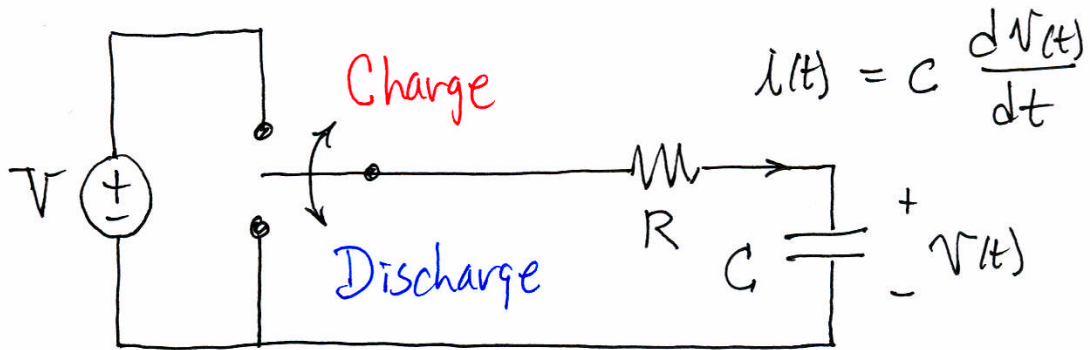


6.002 - Lecture 12


Power Dissipation In Logic

- Energy Accounting During RC Transients
- Power Dissipation In NMOS Logic
- CMOS Logic & Power Dissipation
- p-Channel MOSFET




RC Transients



Charge At $t=0$

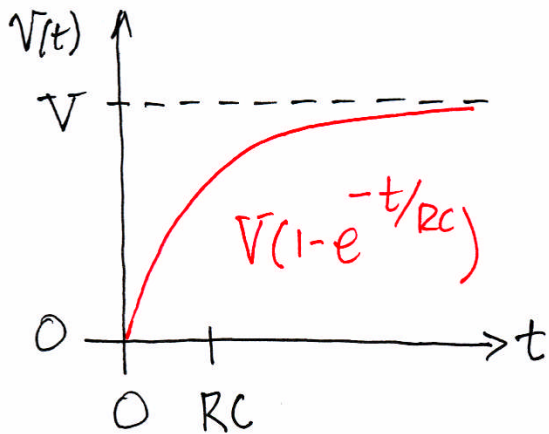

Discharge At $t=0$

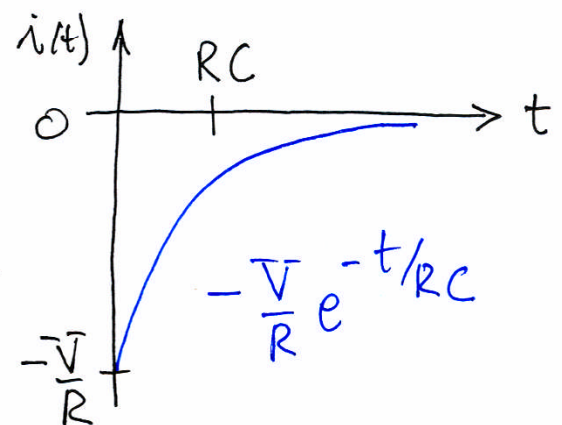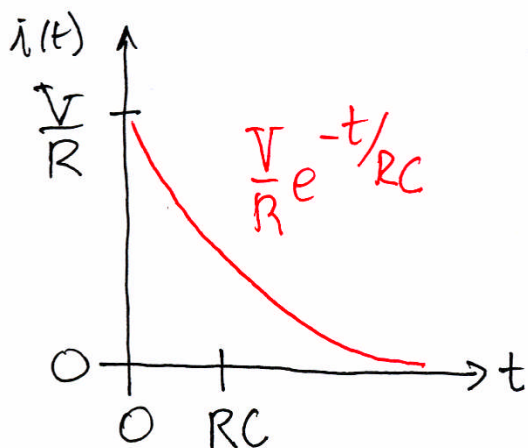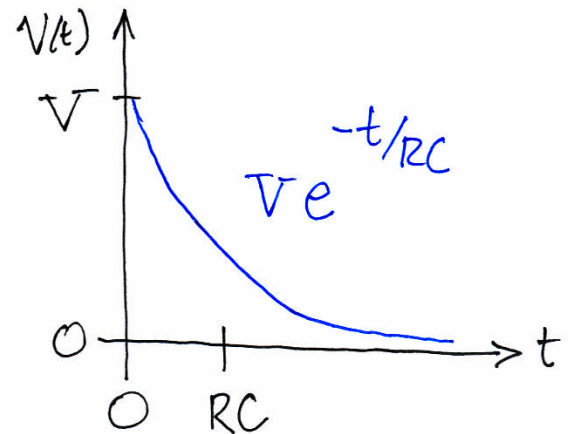

Charge & Energy Conservation

$$\int_0^{\infty} i(t) dt = \int_0^{\infty} \pm \frac{V}{R} e^{-t/RC} dt = \pm CV$$

Charging: Source charges capacitor plates to $\pm CV$.

Discharging: Resistor discharges capacitor plates.

$$\int_0^{\infty} R i^2(t) dt = \int_0^{\infty} \frac{V^2}{R} e^{-\frac{2t}{RC}} dt = \frac{1}{2} CV^2$$

Charging $CV \cdot V = CV^2$ from source


Energy: $\frac{1}{2} CV^2$ to capacitor (storage)

$\frac{1}{2} CV^2$ to resistor (loss)

Discharging $\frac{1}{2} CV^2$ from capacitor


Energy: $\frac{1}{2} CV^2$ to resistor (loss)

NMOS Logic Operation

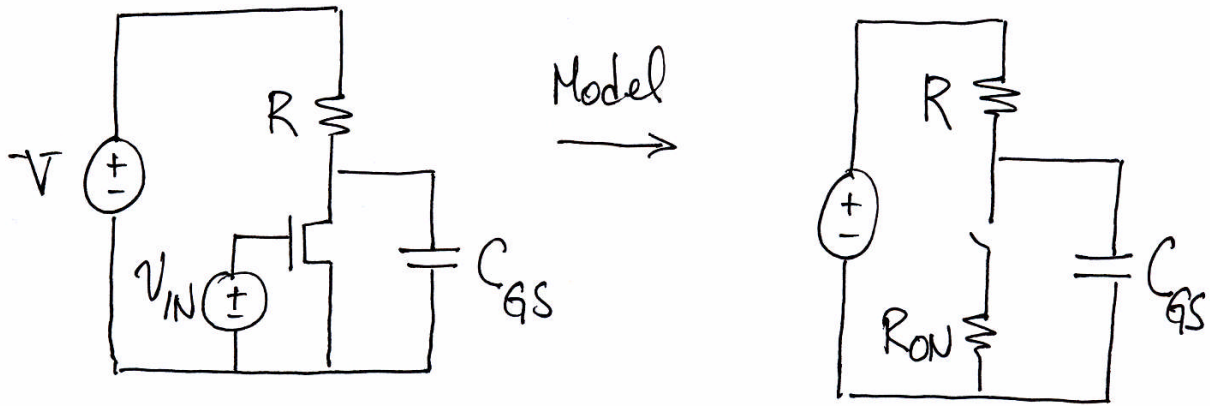


$V_{IN} = \text{Low}$
MOSFET = Off

$V_{IN} = \text{High}$
MOSFET = On

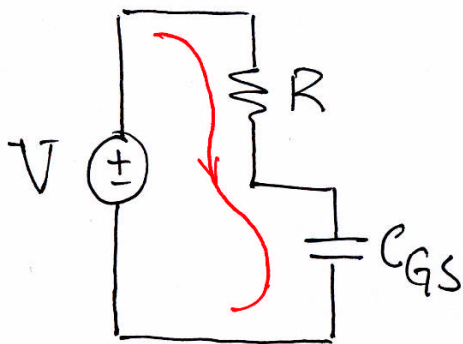

C_{GS} Charges

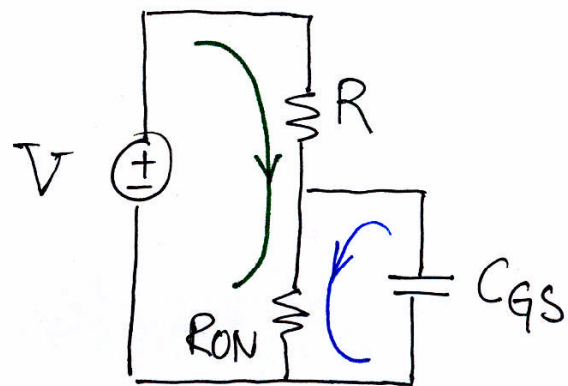


C_{GS} Discharges ($R_{ON} \ll R$)

R Conducts

N MOS Power Dissipation

Assume: * $V_{IN}(t)$

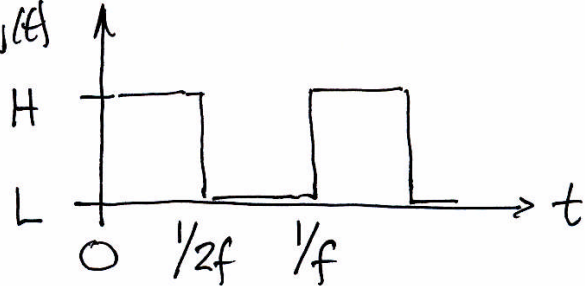

$$* R_{ON} \ll R \quad \& \quad RC_{GS} \ll 1/2f$$

$$V_{IN} \text{ } H \rightarrow L : \text{Dissipation} = \frac{1}{2} C_{GS} V^2 f$$

$$V_{IN} \text{ } L \rightarrow H : \text{Dissipation} = \frac{1}{2} C_{GS} V^2 f + \frac{V^2}{2R}$$

$$\text{Total Dissipation} = \underbrace{C_{GS} V^2 f}_{\text{Dynamic Loss}} + \underbrace{\frac{V^2}{2R}}_{\text{Static Loss}}$$

$$\frac{\text{Static Loss}}{\text{Dynamic Loss}} = \frac{1/2f}{RC_{GS}} \gg 1$$

Examples

Pentium III: $n \approx 10^7$ Gates (Excluding Memory)

$$f \approx 10^9 \text{ Hz}$$

$$C \approx 10^{-14} \text{ F} \quad (\text{Mostly Interconnect})$$


$$V \approx 1.8 \text{ V}$$

Too high since
gates often
idle $\longrightarrow$

$$n C V^2 f \approx 324 \text{ W} !!$$


Demo:
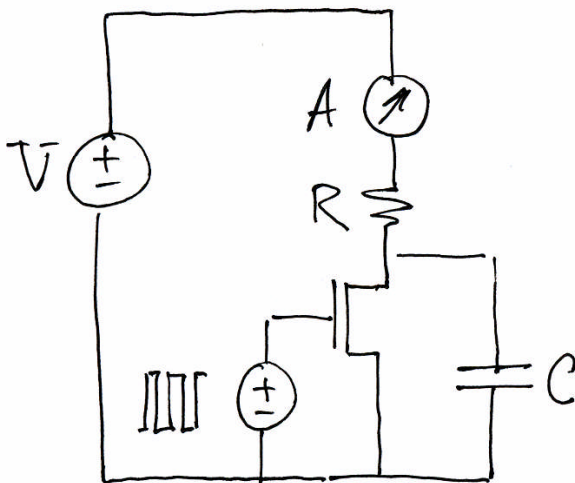
$$\text{Avg Dissipation} = V \left[\frac{V}{2R} + C V f \right]$$




Average current
measured by
electromechanical
ammeter.

Trends

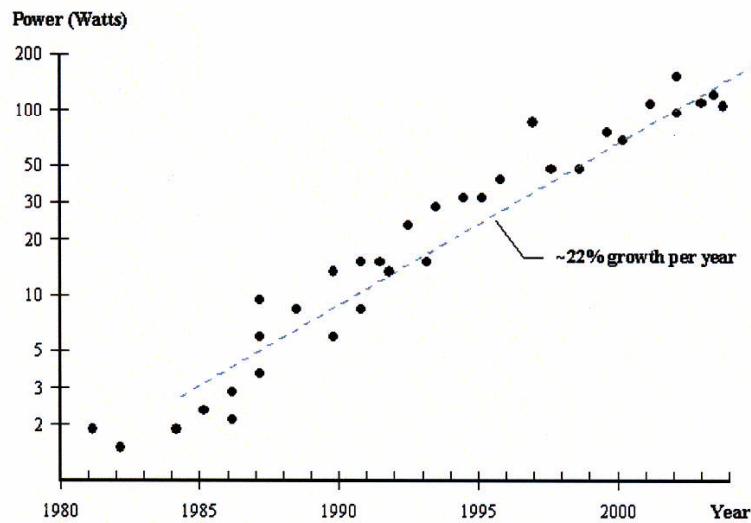

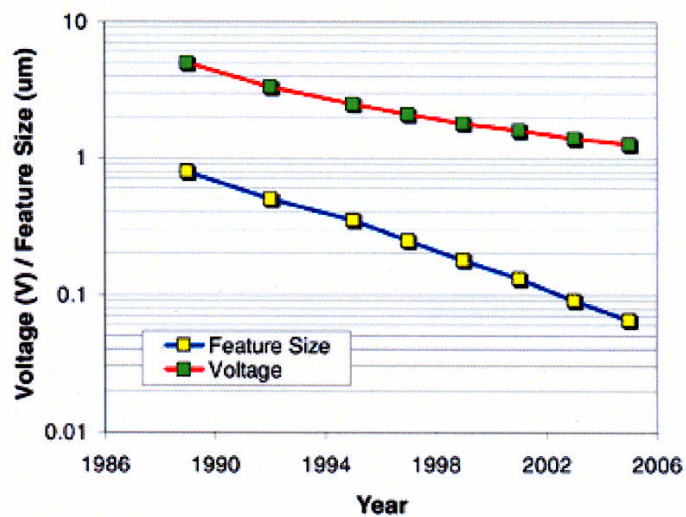
<http://www.realworldtech.com/page.cfm?ArticleID=RWT062004172947&p=3>



http://www.intel.com/technology/itj/2005/volume09issue04/art02_powerdelivery/figures/figure_3.gif


CMOS

NMOS

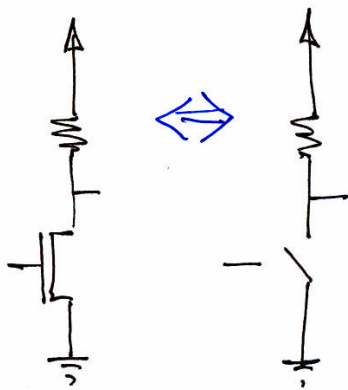


Better

No
Static
Loss

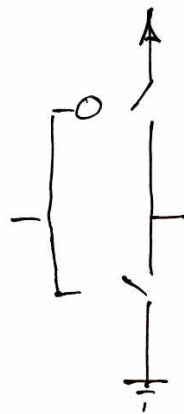


Complementary


CMOS

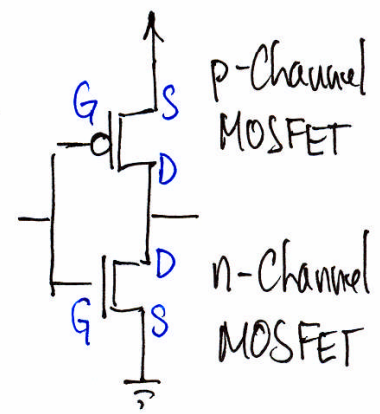


NMOS

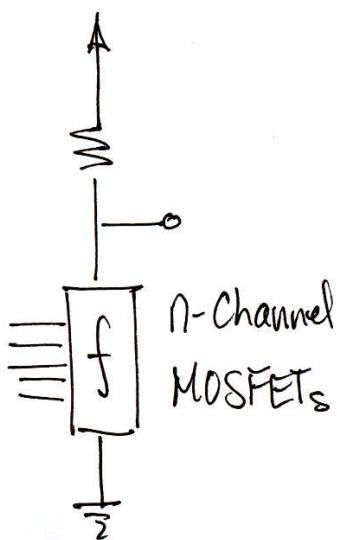


PMOS

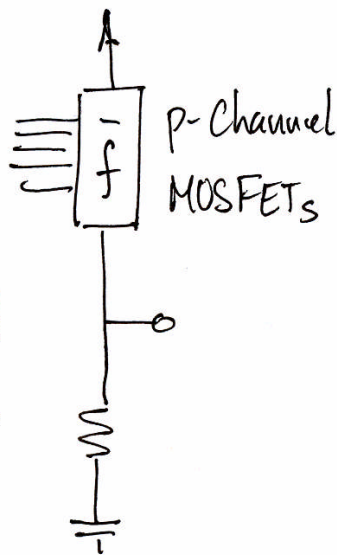

CMOS

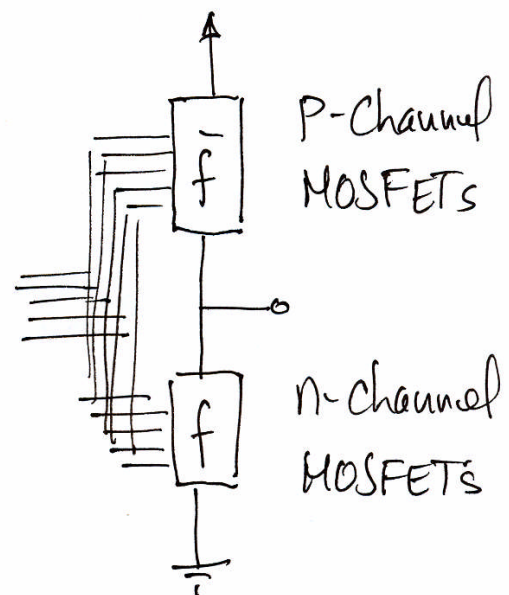


CMOS Dissipation Demo

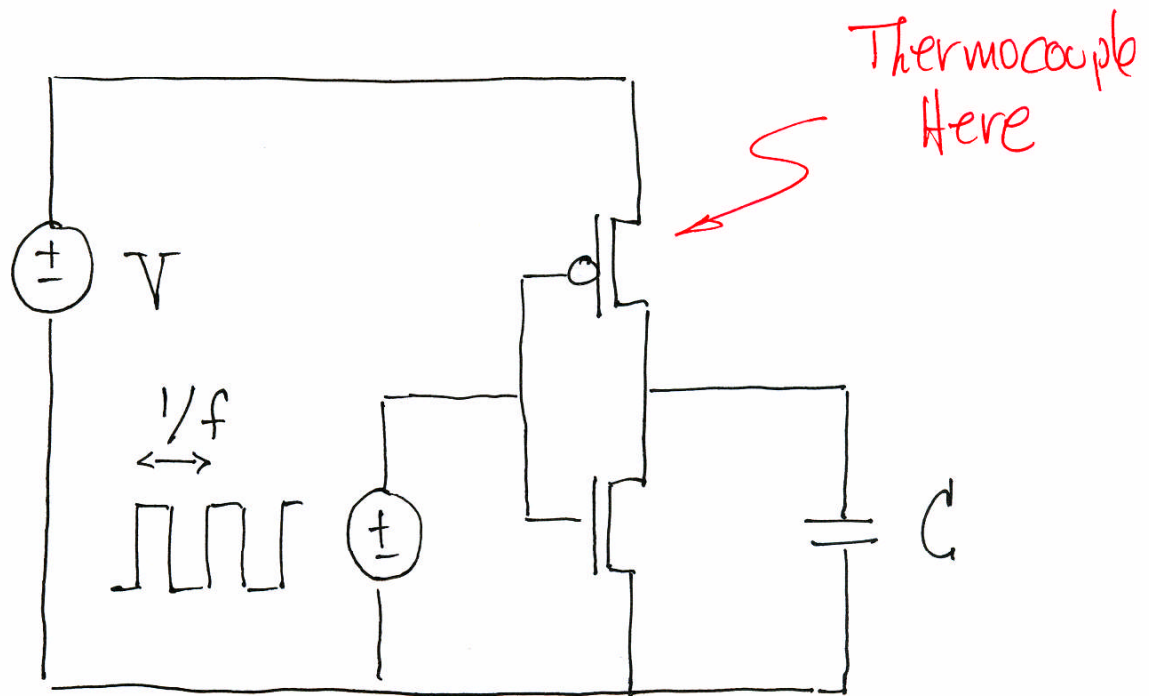

$$\left. \begin{array}{l} V = 10\text{V} \\ C = 1\mu\text{F} \\ f = 1\text{kHz} \end{array} \right\} \text{Dissipation} = 0.1\text{W}$$

p-Channel MOSFET

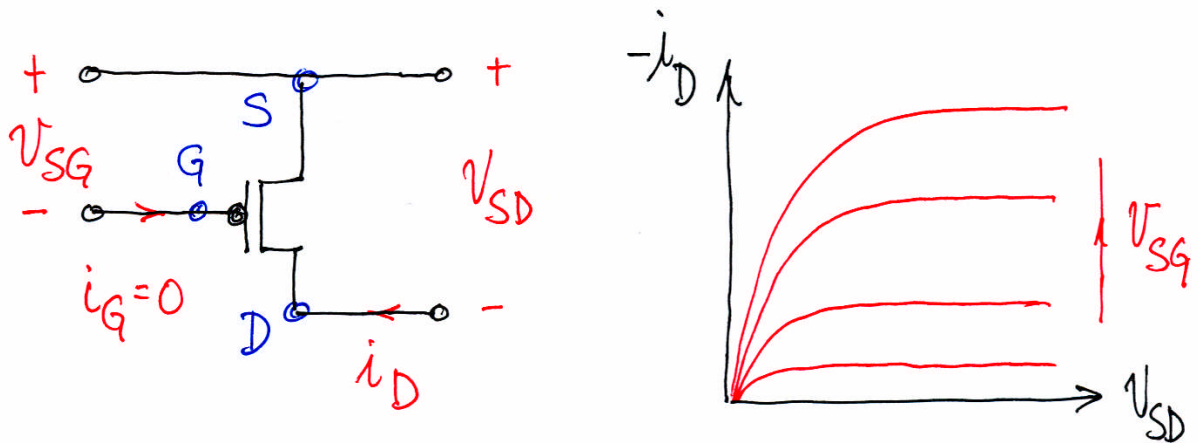

p-Channel MOSFET permits CMOS logic, and more interesting amplifiers, for example.

