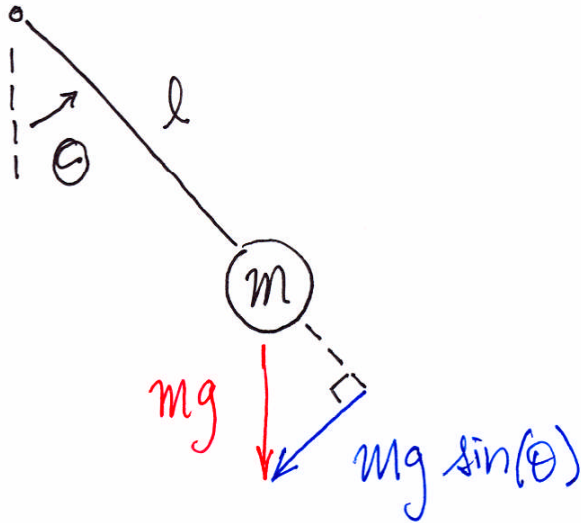


6.002 - Lecture 15

Clocks

- Mechanical clocks
- Phase - Plane Analysis
- Electrical Clocks
- LC Oscillations Can Be Good

Pendulum



Damping:
Bearing Loss
Windage

$$m l^2 \frac{d^2 \theta}{dt^2} = -m g l \sin(\theta) - b \frac{d\theta}{dt}$$

$$\frac{d^2 \theta}{dt^2} + \boxed{\frac{b}{m l^2}} \frac{d\theta}{dt} + \boxed{\frac{g}{l}} \theta \approx 0 \quad \left. \begin{array}{l} \text{ } \end{array} \right\} \theta \ll \frac{\pi}{2}$$

2α ω_0^2

$$\theta \sim e^{st} \Rightarrow s = -\alpha \pm j\sqrt{\omega_0^2 - \alpha^2} \approx -\alpha \pm j\omega_0$$

$$\text{Low Loss} \Rightarrow \alpha \ll \omega_0 \quad \uparrow$$

Trajectories

$$\Theta(t) \approx \Theta \cos(\omega_0 t) e^{-\alpha t}$$

$$\Omega(t) \equiv \frac{d\Theta(t)}{dt}$$

$$\approx -\omega_0 \Theta \sin(\omega_0 t) e^{-\alpha t} - \alpha \Theta \cos(\omega_0 t) e^{-\alpha t}$$

$$\approx -\omega_0 \Theta \sin(\omega_0 t) e^{-\alpha t}$$


$\underbrace{\hspace{10em}}$

$$\alpha \ll \omega_0$$

$\Downarrow$

Small

States

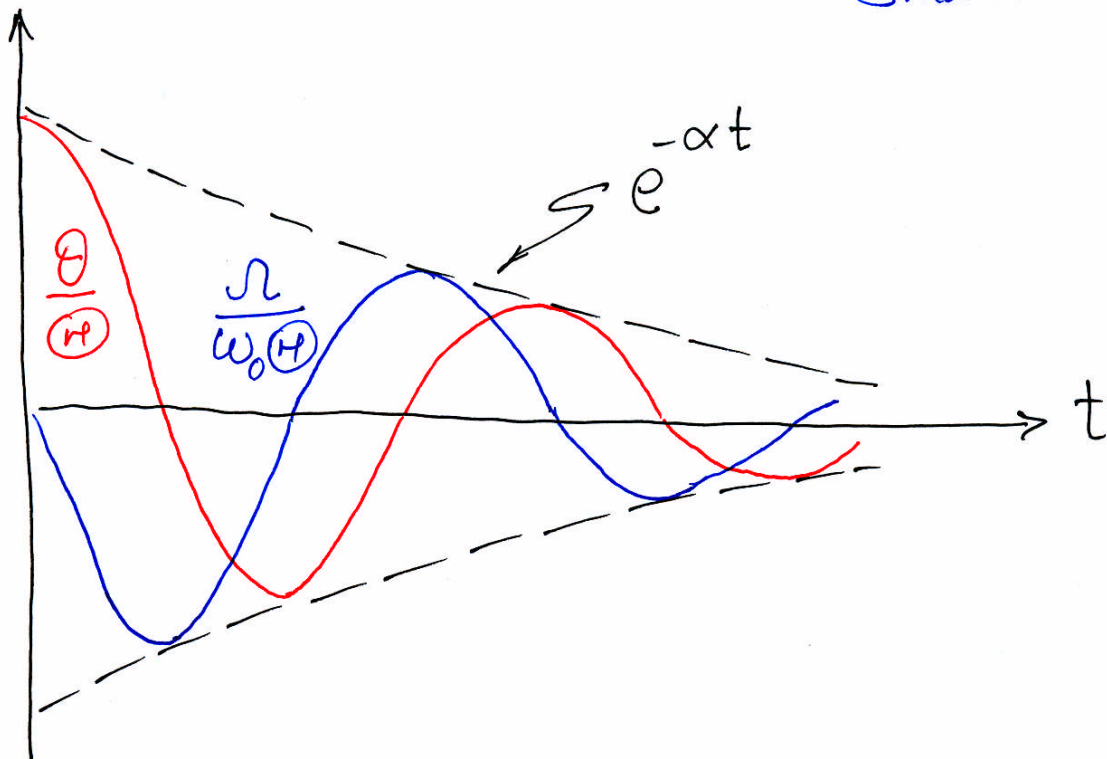


Θ - Ω Phase Plane

Phase - Plane Coordinates: $\frac{\Theta(t)}{\omega} , \frac{\Omega(t)}{\omega_0 \omega}$


Phase - Plane Angle: $\frac{\Omega(t)/\omega_0 \omega}{\Theta(t)/\omega} = \tan^{-1}(-\omega t)$

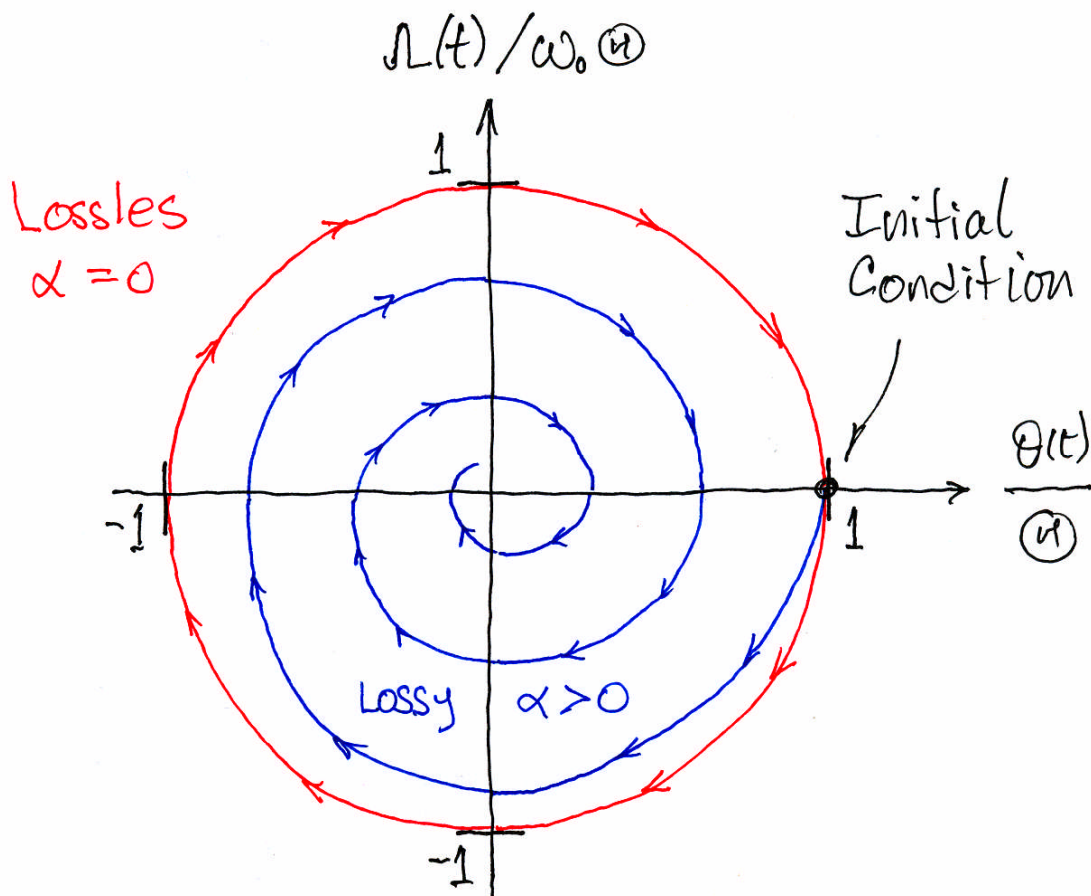Phase - Plane Radius: $\left(\frac{\Theta(t)}{\omega}\right)^2 + \left(\frac{\Omega(t)}{\omega_0 \omega}\right)^2 = e^{-2\alpha t}$




Loss Mitigation

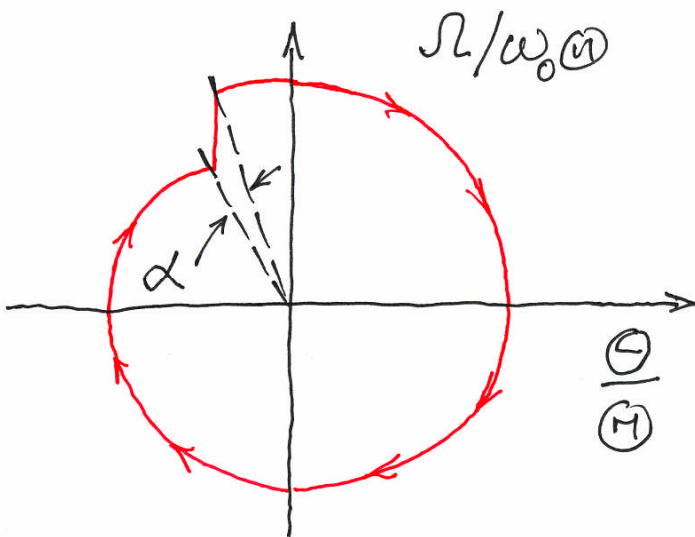Add kinetic energy (via a force impulse and a momentum step) when the pendulum velocity is at a peak.




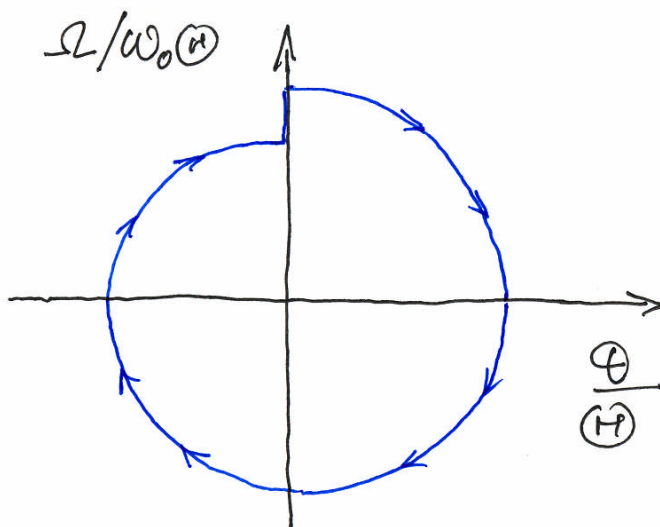This period differs from 2π by α , which depends on the velocity step.
Not good!



This period is 2π , independent of the velocity step. Good!




Escapement Mechanism

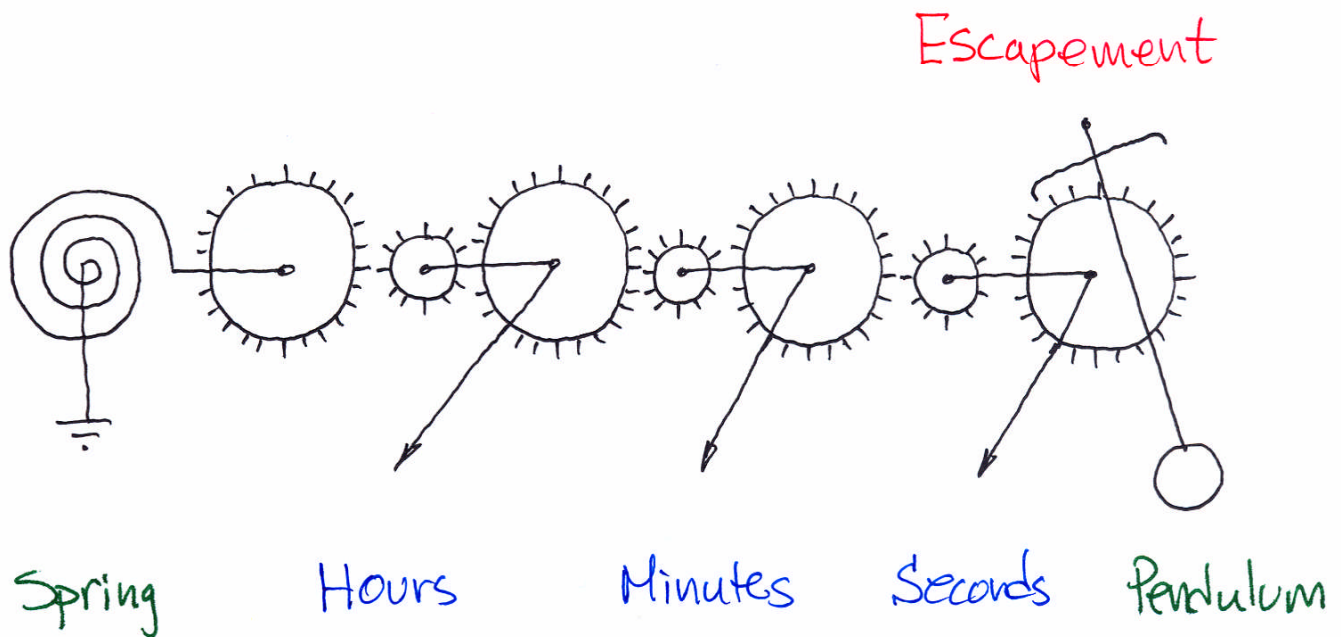

Escapement mechanism:

- (1) synchronizes gear motion to the pendulum;
- (2) delivers a force impulse to the pendulum when $\theta = 0$.

Pendulum Clocks

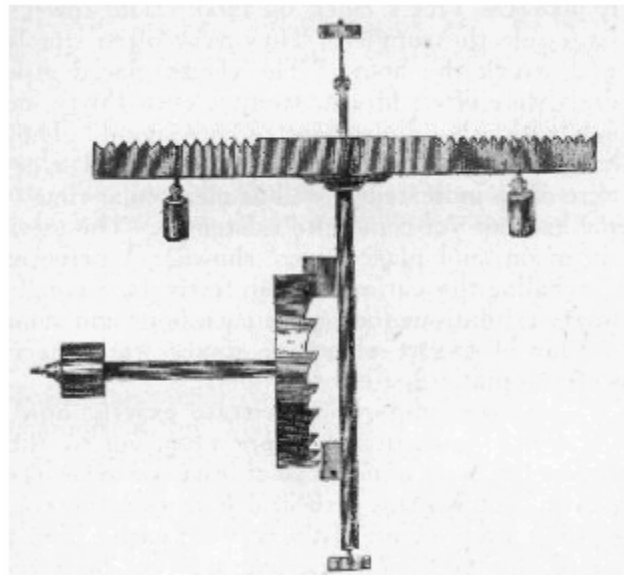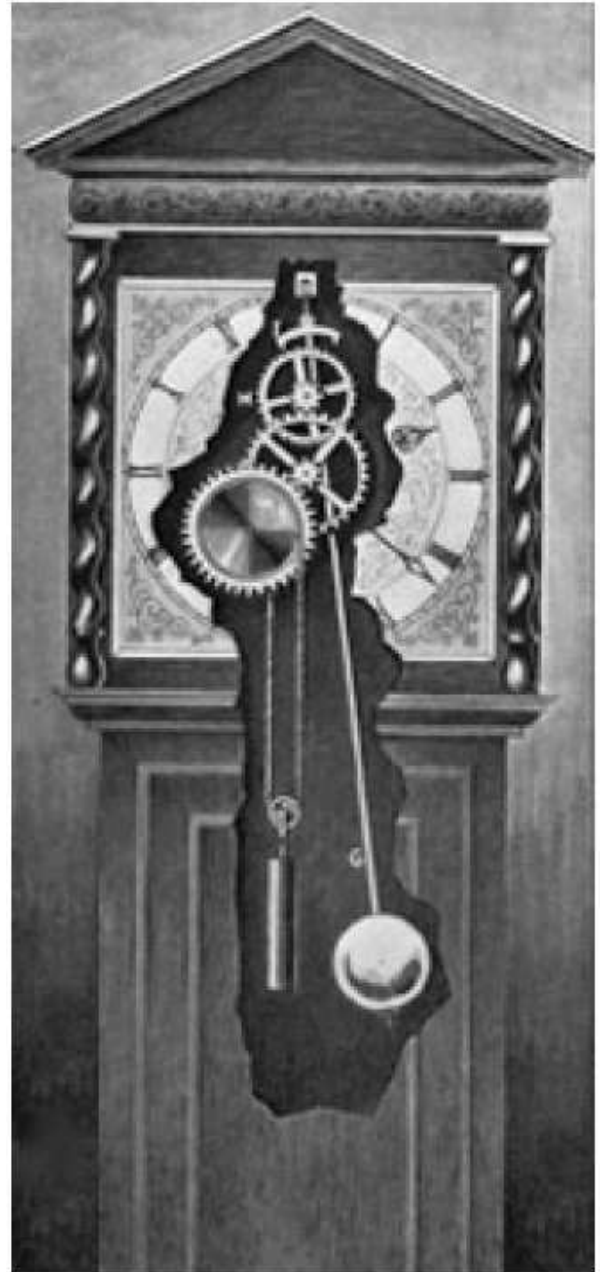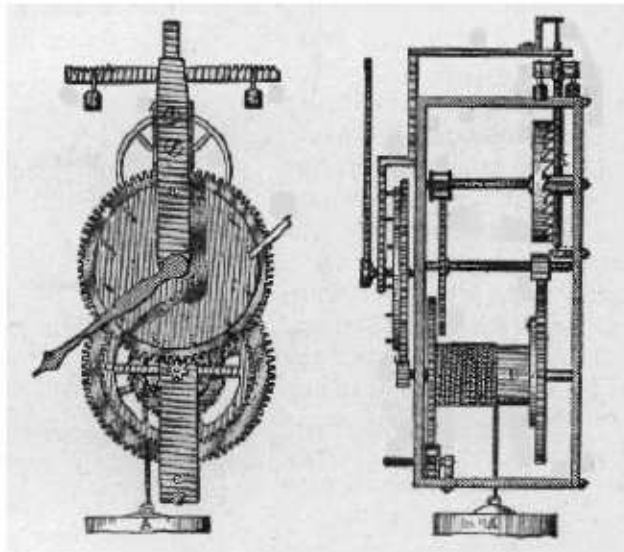


Christiaan Huygens (1629-1695)

- Mathematician
- Astronomer
- Engineer
- Inventor of Pendulum Clock




LC Clock I

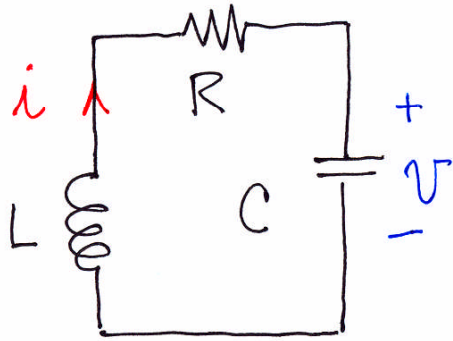

$$L \frac{di}{dt} + Ri + V = 0$$

$$i = C \frac{dV}{dt}$$

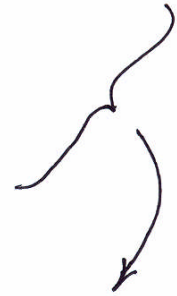

$$\frac{d^2 V(t)}{dt^2} + \underbrace{\left[\frac{R}{L} \right]}_{2\alpha} \frac{dV(t)}{dt} + \underbrace{\left[\frac{1}{LC} \right]}_{\omega_0^2} V(t) = 0$$




$$R \ll \sqrt{\frac{L}{C}} \Rightarrow \alpha \ll \omega_0 \Rightarrow e^{st}, \quad s \approx \alpha \pm j\omega_0$$

$$V(t) \approx V_0 \sin(\omega_0 t) e^{-\alpha t}$$

$$i(t) \approx \frac{V_0}{\sqrt{LC}} \cos(\omega_0 t) e^{-\alpha t}$$

} Similar
to the
pendulum!

LC Clock II

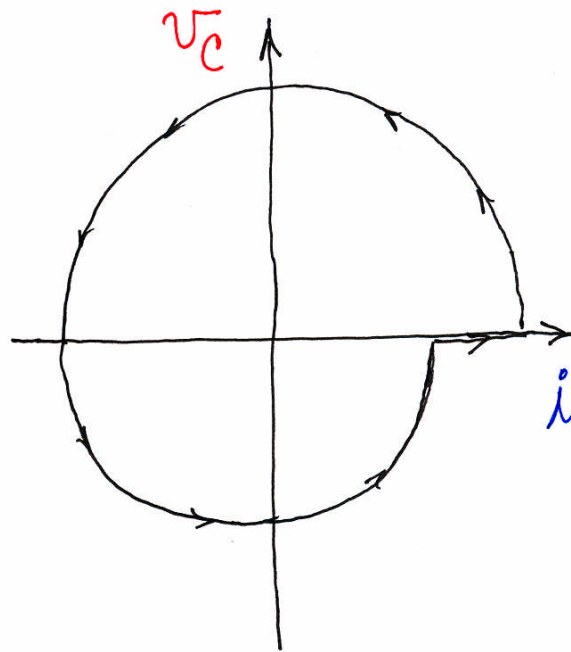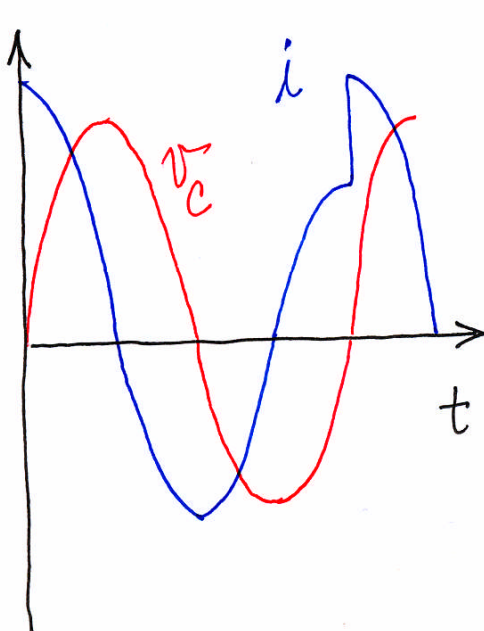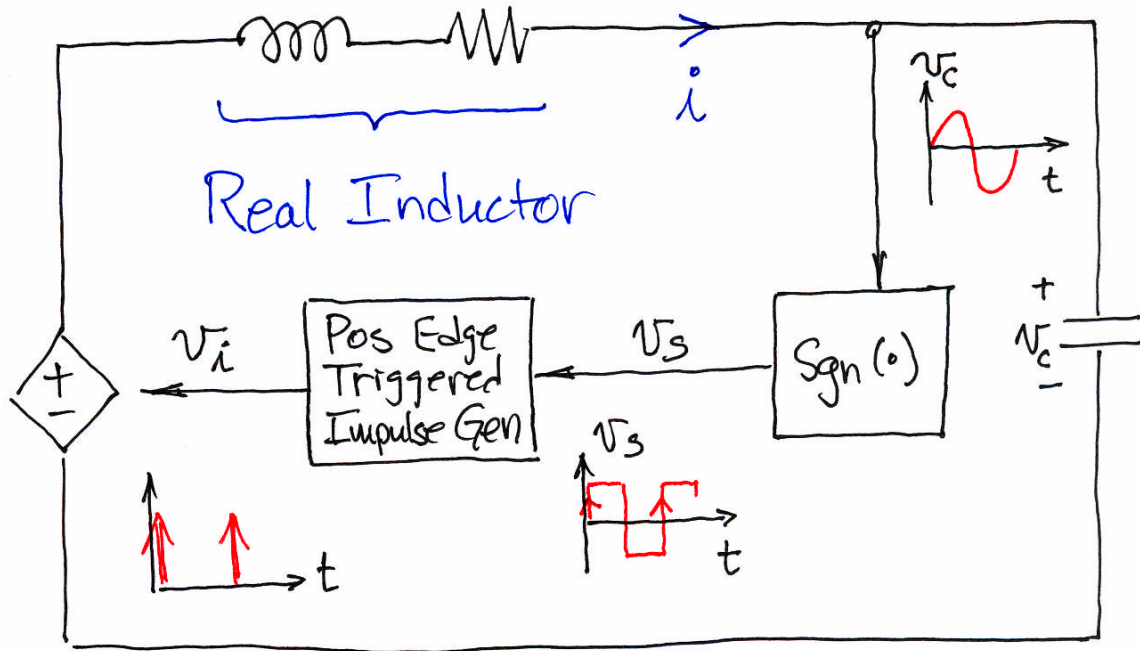

LC Clock III

Suppose voltage impulse has area Λ .

$$i(t) \approx I \cos(\omega_0 t) e^{-\alpha t} \quad 0 \leq t < \frac{2\pi}{\omega}$$

$$i\left(\frac{2\pi}{\omega_0}^-\right) = I e^{-\frac{2\pi\alpha}{\omega_0}}$$



$$i\left(\frac{2\pi}{\omega_0}^+\right) = i\left(\frac{2\pi}{\omega_0}^-\right) + \frac{\Lambda}{L}$$

$$I = \frac{\Lambda/L}{1 - e^{-\frac{2\pi\alpha}{\omega_0}}}$$

The amplitude I falls with Λ , perhaps due to decaying power supply, but the frequency remains $\approx \omega_0$.

LC Clock IV

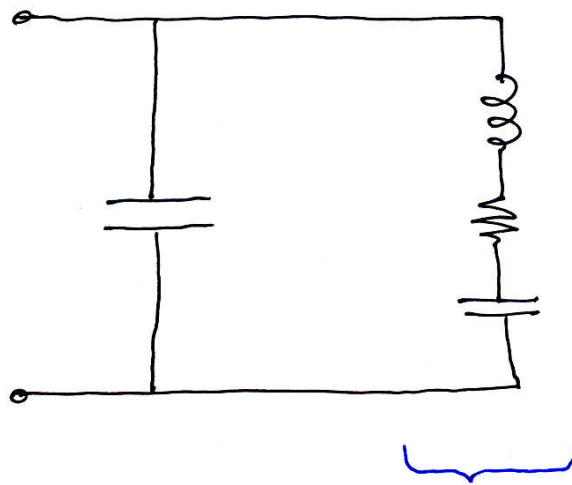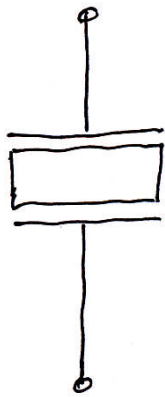Use a quartz crystal as a very - low - loss resonator.



Mechanical resonator
with piezoelectric
electromechanical
coupling.