
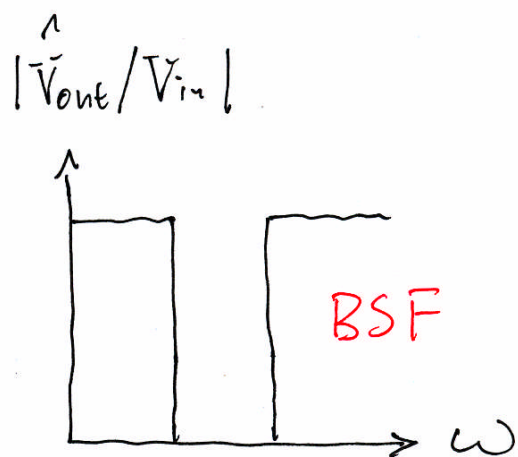
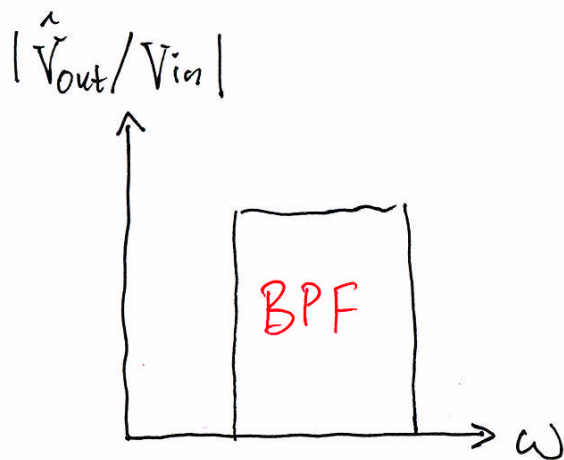
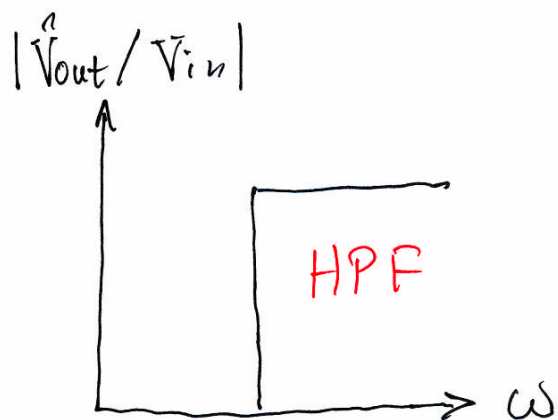
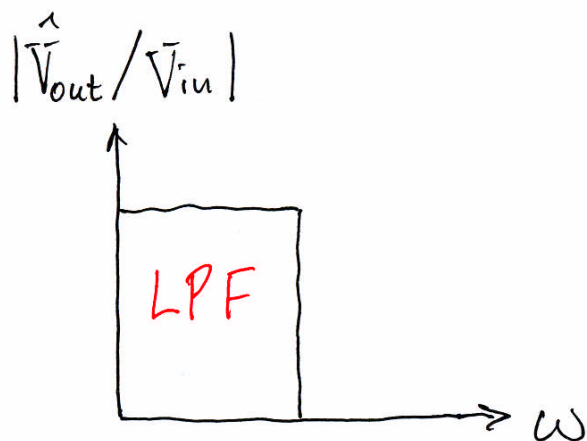


6.002 - Lecture 18


Filtering

- Simple Objectives :
(LPF, HPF, BPF, BSF)
- Simple Synthesis
- LC Resonators
- Radio Examples



Simple Filtering Objectives

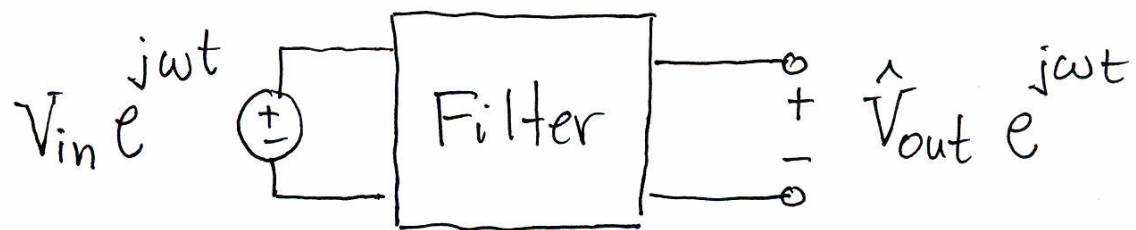




Simple Filtering Synthesis

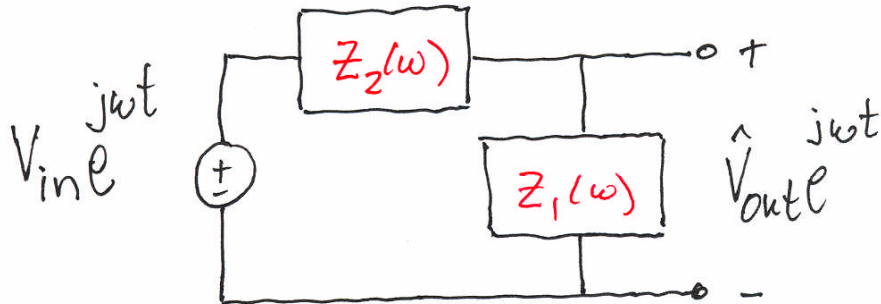


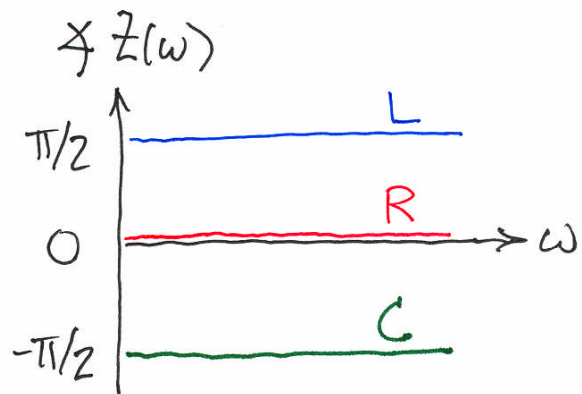
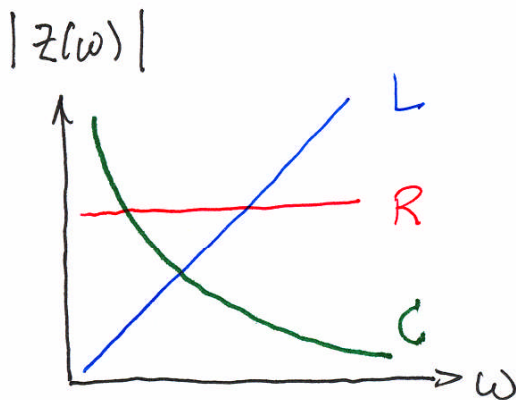
$$\frac{\hat{V}_{out}}{V_{in}} = \frac{Z_1(\omega)}{Z_2(\omega) + Z_1(\omega)}$$




LPF:

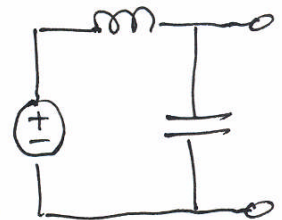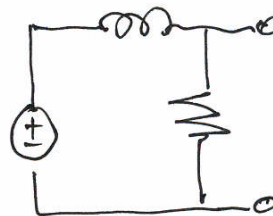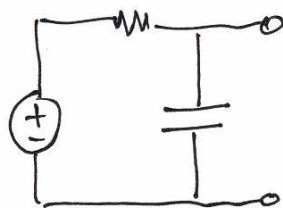



HPF:

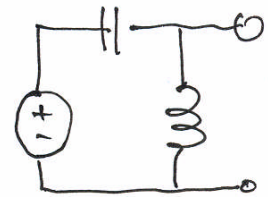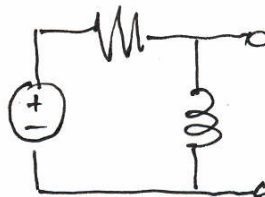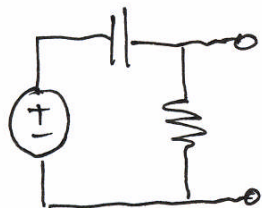


Parallel LC Resonator

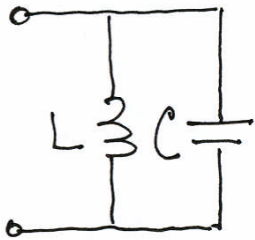

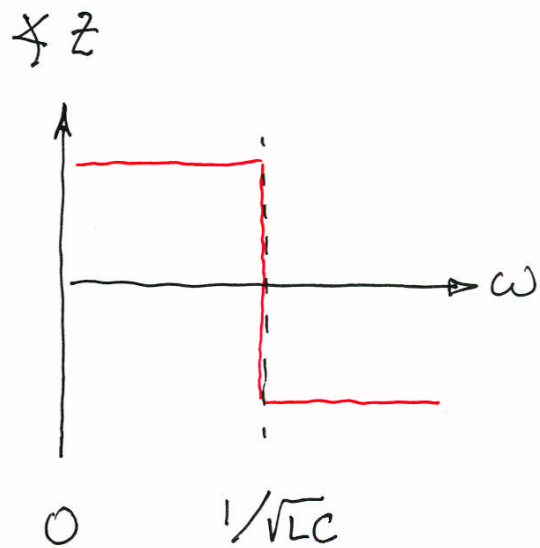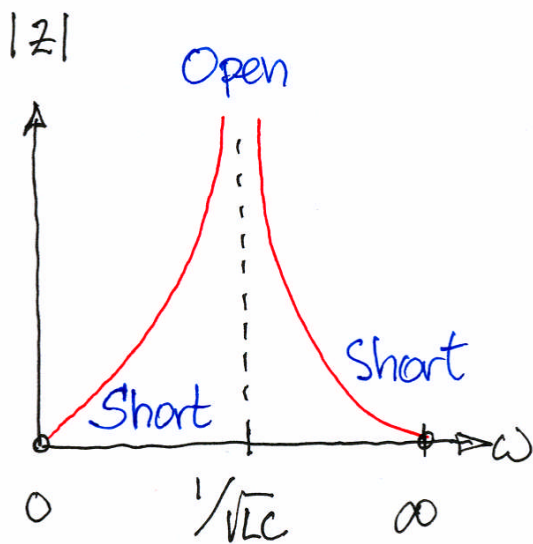
$$Z = \frac{j\omega L \cdot \frac{1}{j\omega C}}{j\omega L + \frac{1}{j\omega C}} = \frac{j\omega L}{1 - \omega^2 LC}$$




BPF:

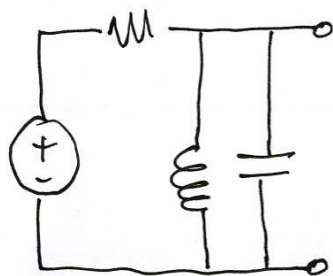





BSF:

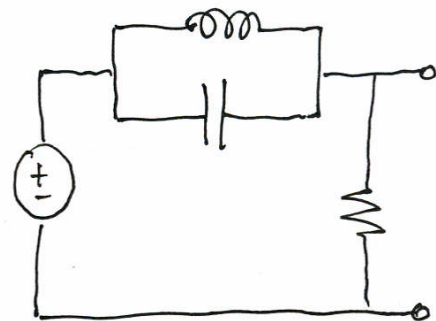


Series LC Resonator

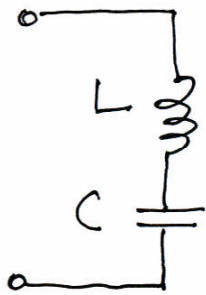
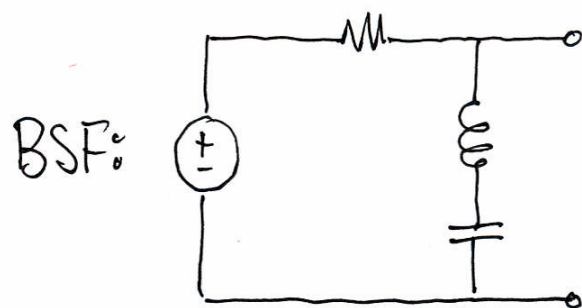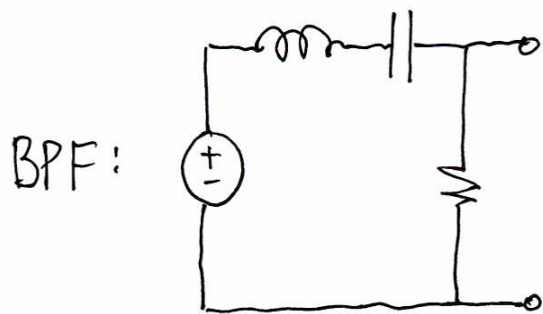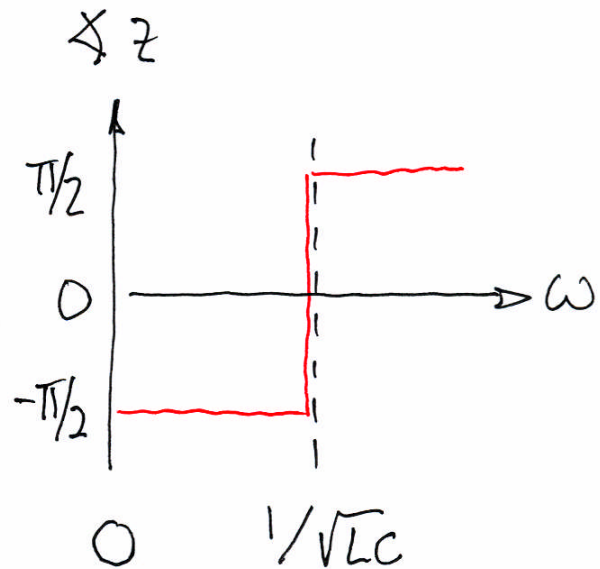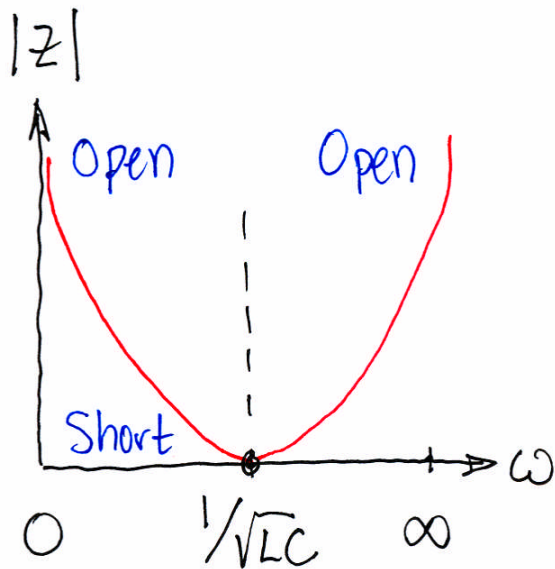
$$Z = j\omega L + \frac{1}{j\omega C} = \frac{1 - \omega^2 LC}{j\omega C}$$




BPF Example

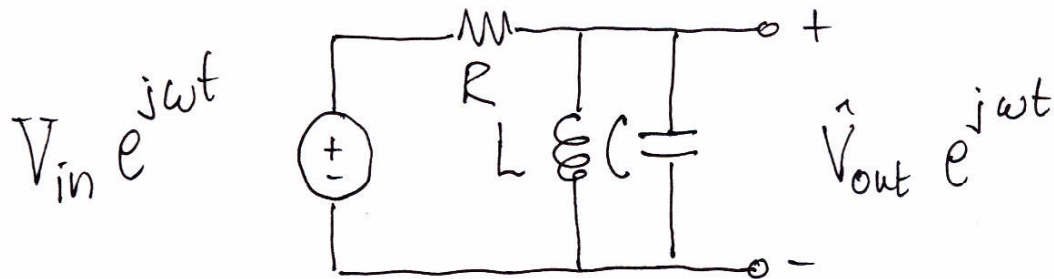

$$\frac{\hat{V}_{out}}{V_{in}} = \frac{1/R}{1/R + 1/j\omega L + j\omega C} = \frac{j\omega L/R}{1 - \omega^2 LC + j\omega L/R}$$

$$\left| \frac{\hat{V}_{out}}{V_{in}} \right| = \frac{(\omega L/R)}{\sqrt{(1 - \omega^2 LC)^2 + (\omega L/R)^2}}$$

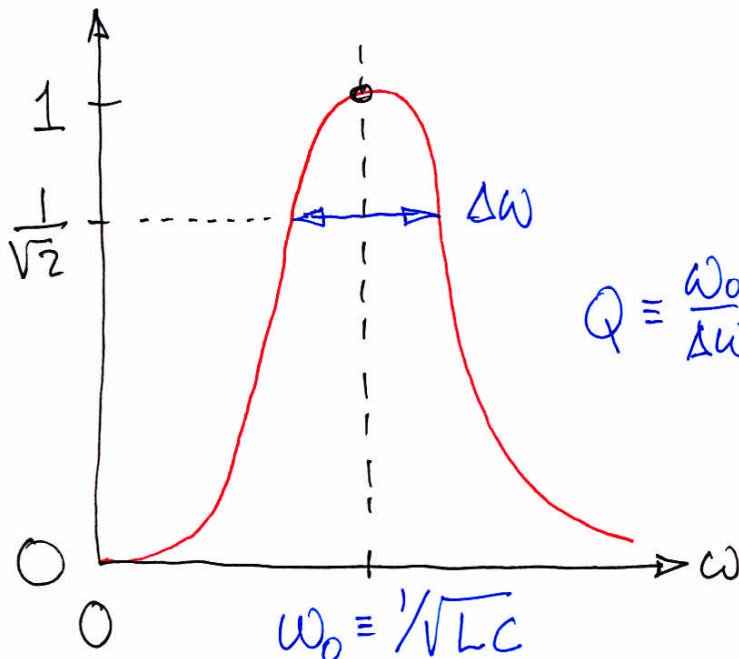

Numbers:

$$L = 0.1 \text{ H}$$

$$C = 0.25 \mu\text{F}$$


$$R = 10 \text{ k}\Omega$$

$$\frac{1}{2\pi\sqrt{LC}} = 1 \text{ kHz}$$

$$\sqrt{L/C} = 632 \Omega$$


$$Q = 16$$

BSF Example

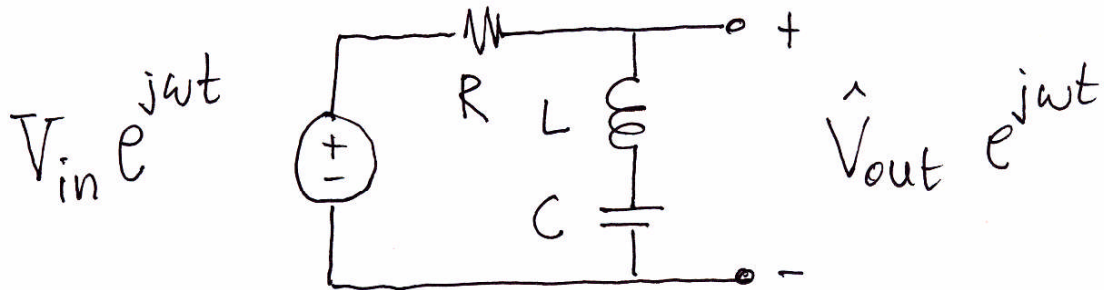

$$\frac{\hat{V}_{out}}{\hat{V}_{in}} = \frac{j\omega L + 1/j\omega C}{R + j\omega L + 1/j\omega C} = \frac{1 - \omega^2 LC}{1 - \omega^2 LC + j\omega RC}$$

$$\left| \frac{\hat{V}_{out}}{\hat{V}_{in}} \right| = \frac{1 - \omega^2 LC}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}}$$

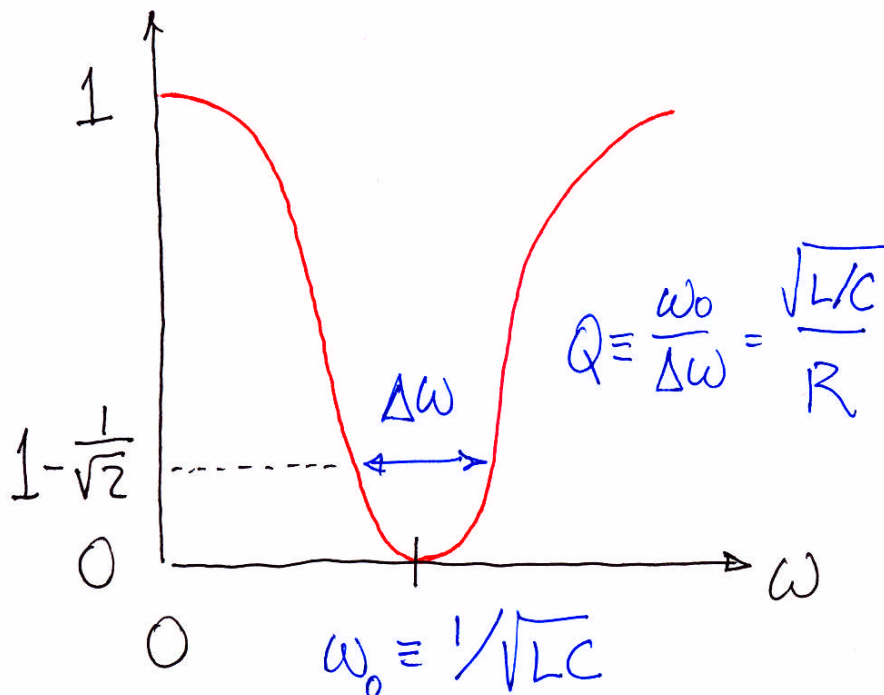

Numbers :

$$L = 0.1 \text{ H}$$

$$C = 0.25 \mu\text{F}$$


$$R = 100 \Omega$$

$$\frac{1}{2\pi\sqrt{LC}} = 1 \text{ kHz}$$

$$\sqrt{L/C} = 632 \Omega$$

$$Q = 6.3$$

A More Complex Filter

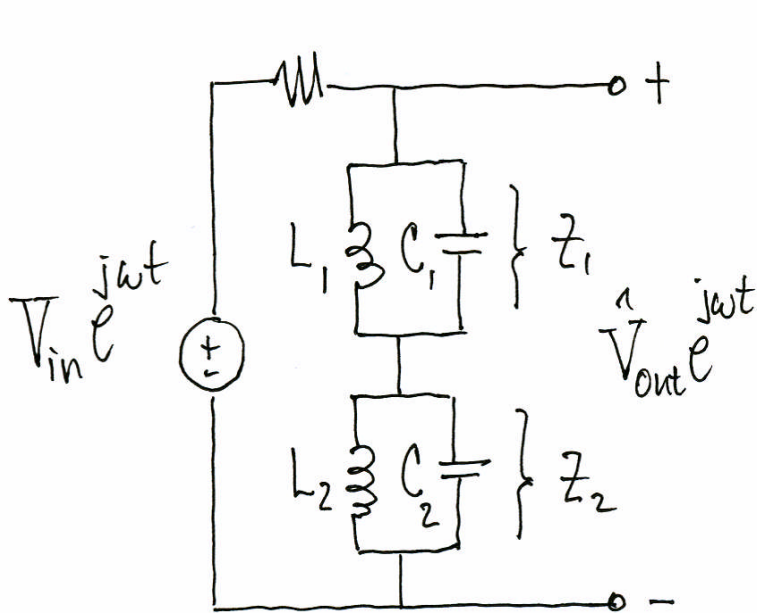


$$z_1 = \text{Open at } \omega = \frac{1}{\sqrt{L_1 C_1}}$$


$$z_2 = \text{Open at } \omega = \frac{1}{\sqrt{L_2 C_2}}$$

$$z_1 + z_2 = \text{Short at } \omega = 0, \infty$$

and between the two opens

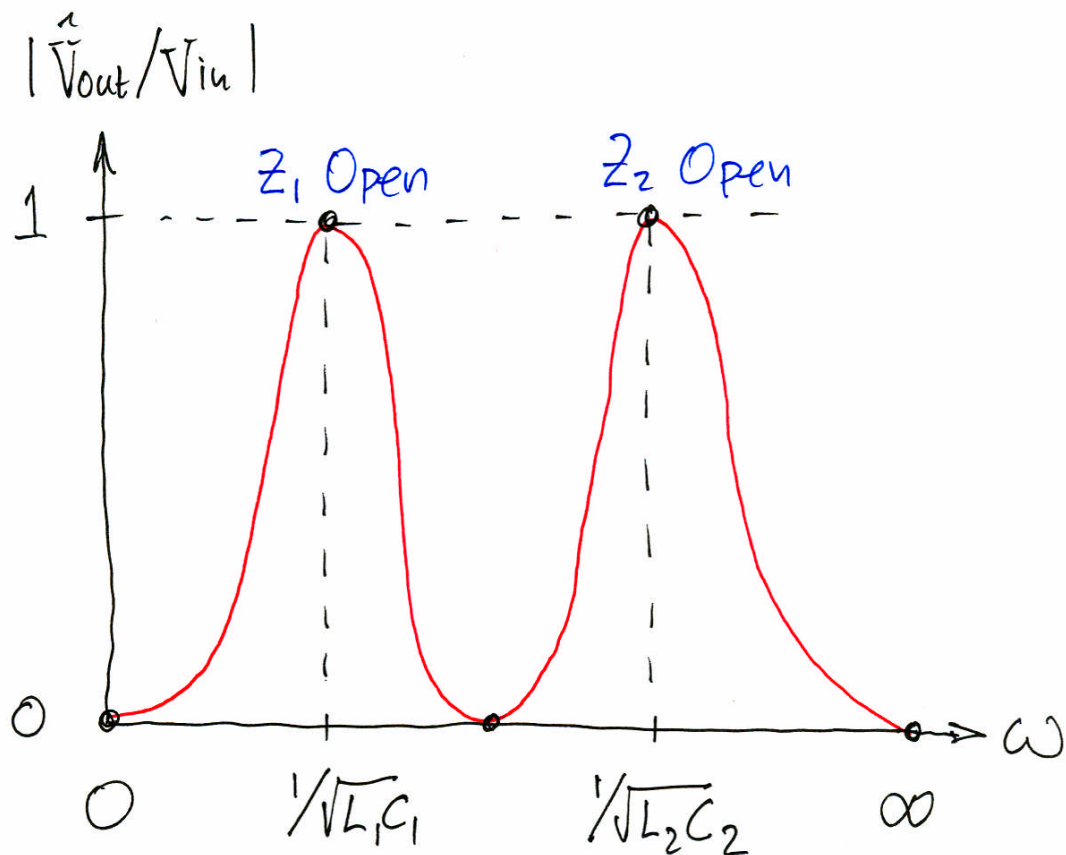



AM Radio Transmission

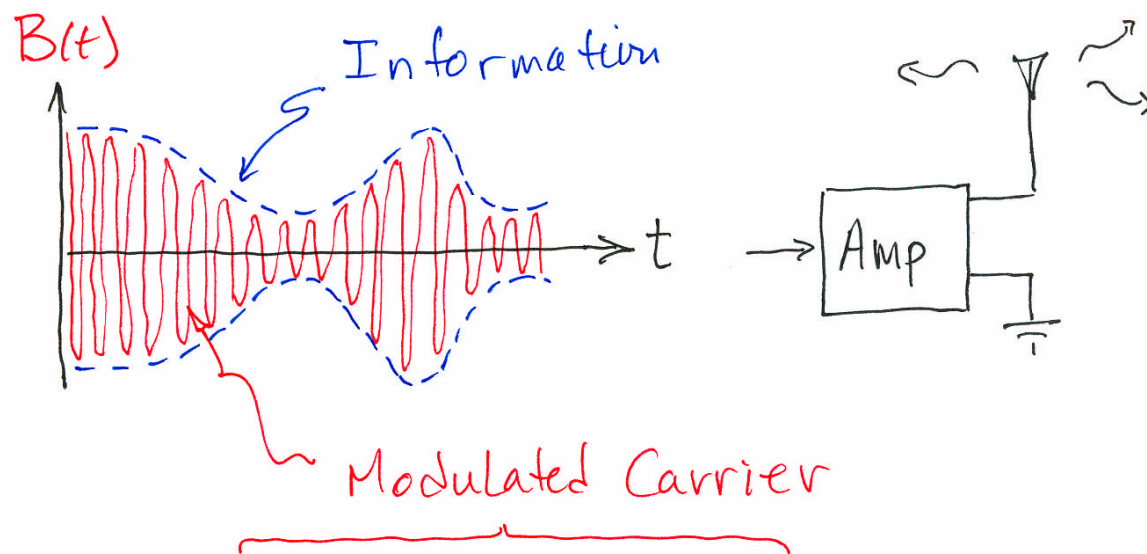


$$B(t) = (1 + \underbrace{S(t)}_{\text{Information}}) \underbrace{\cos(\omega_c t)}_{\text{Carrier}} \quad |S(t)| < 1$$

Suppose $S(t) = \alpha \cos(\omega_m t)$ $|\alpha| < 1$

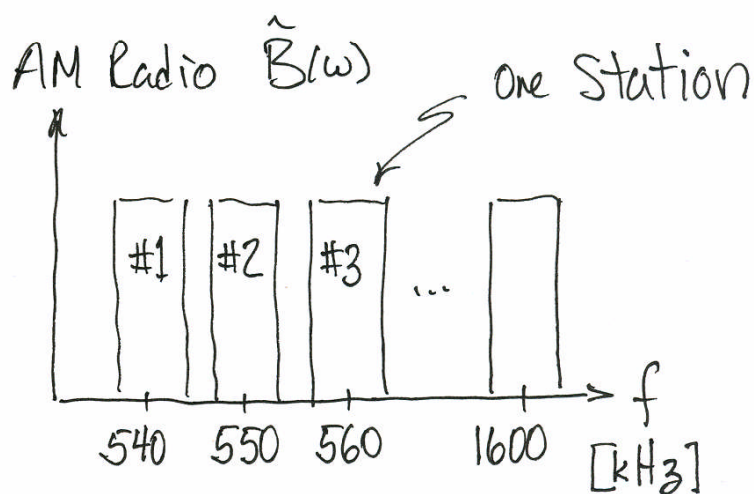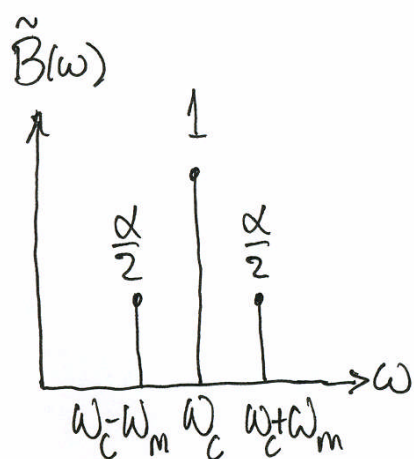Then $B(t) = \cos(\omega_c t) + \frac{\alpha}{2} (\cos((\omega_c + \omega_m)t) + \cos((\omega_c - \omega_m)t))$



AM Radio Transmitter

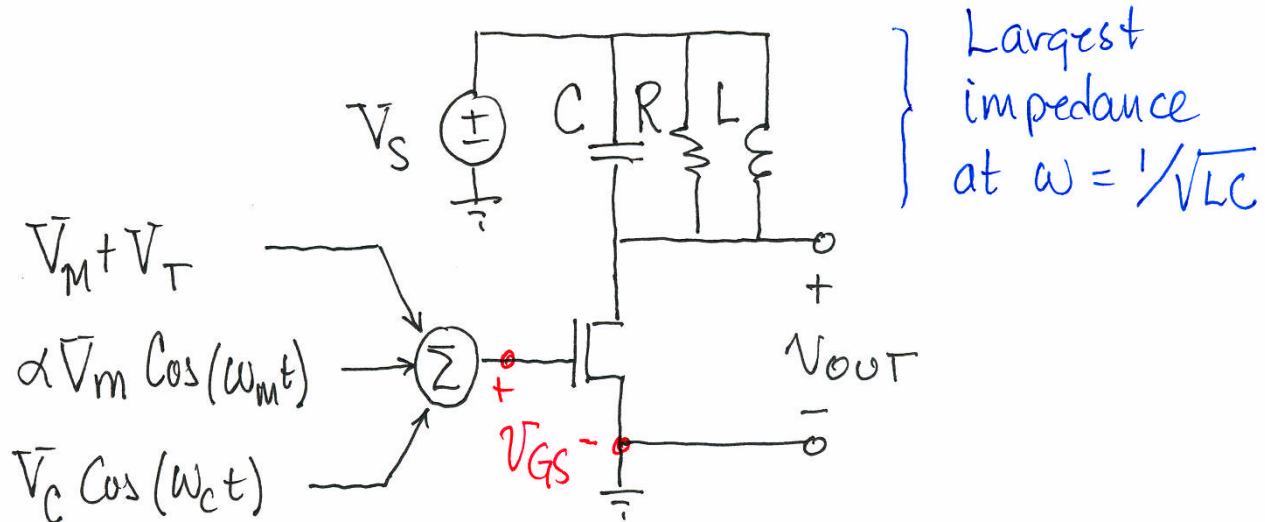


$$C \frac{d}{dt} (V_{out} - \bar{V}_s) + \frac{1}{R} (V_{out} - \bar{V}_s) + \frac{1}{L} \int_{-\infty}^t (V_{out} - \bar{V}_s) dt + \frac{K}{2} (V_{GS} - \bar{V}_T)^2 = 0$$


$$LC \frac{d^2 V_{out}}{dt^2} + \frac{L}{R} \frac{dV_{out}}{dt} + V_{out} = \bar{V}_s - K L (V_{GS} - \bar{V}_T) \frac{dV_{GS}}{dt}$$

$$\begin{aligned}
 - (V_{GS} - \bar{V}_T) \frac{dV_{GS}}{dt} &= \omega_c \bar{V}_m \bar{V}_c (1 + \alpha \cos(\omega_m t)) \sin(\omega_c t) && \text{Desired} \\
 &+ \alpha \omega_m \bar{V}_m \bar{V}_c \sin(\omega_m t) \cos(\omega_c t) && \text{Small For } \omega_m \ll \omega_c \\
 &+ \omega_c \bar{V}_c^2 \sin(\omega_c t) \cos(\omega_c t) && \text{Filtered Out} \\
 &+ \alpha \omega_m \bar{V}_m^2 (1 + \alpha \cos(\omega_m t)) \sin(\omega_m t) && \text{Filtered Out}
 \end{aligned}$$

AM Radio Receiver

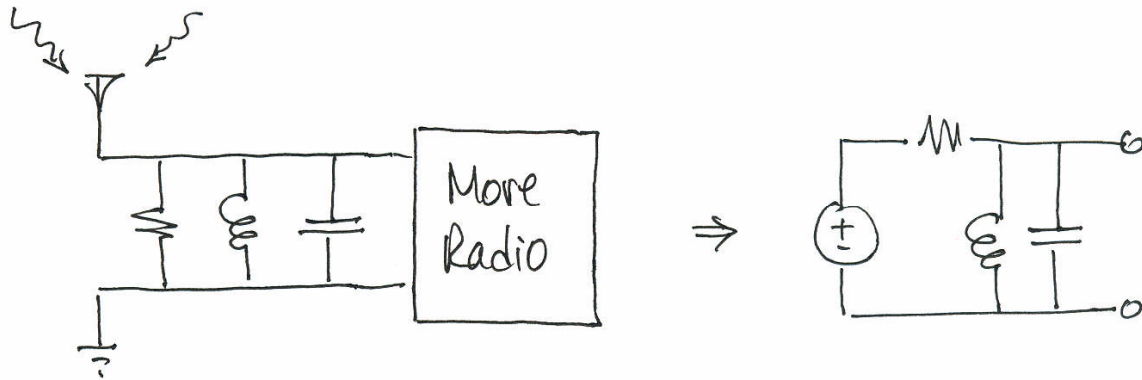


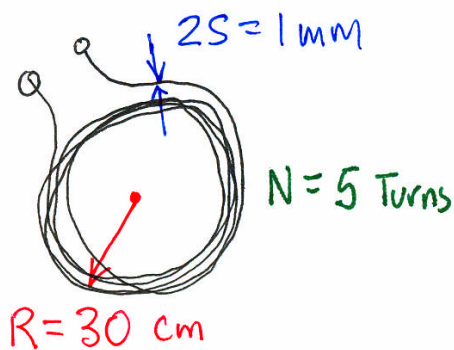RLC Filter $\Rightarrow$ BPF around $\omega = 1/\sqrt{LC}$



$$L = \mu_0 N^2 R \left(\ln \left(\frac{8R}{S} \right) - 2 \right)$$
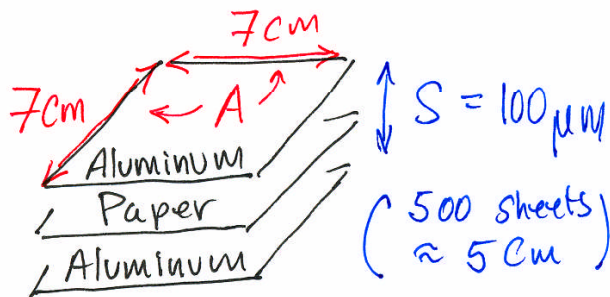
$$= 61 \mu H \quad (\text{Actually } 52 \mu H)$$



$$C = \frac{\epsilon_0 A}{S} = 434 \text{ pF}$$

$$+ 150 \text{ pF}$$

$$\hline 584 \text{ pF}$$

$\omega = 1/\sqrt{LC} \dots 910 \text{ kHz as measured}$

Parasitic