


# 6.002 - Lecture 20

## Analog Signal Processing


- Addition & Subtraction
- Integration & Differentiation
- Analog Computers
- Filter Synthesis

# Addition

$$\frac{R_2 V_1 + R_1 V_2}{R_1 + R_2}$$

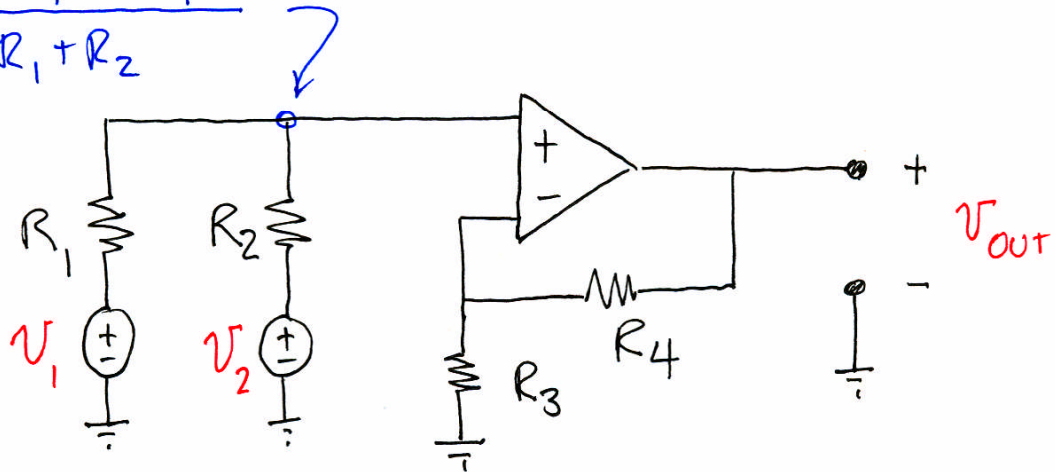

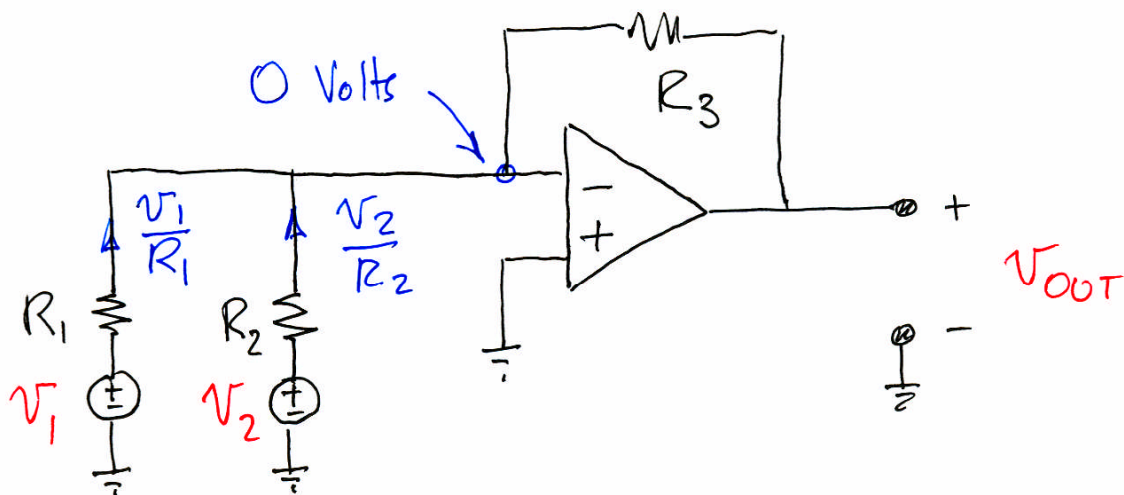
$$V_{out} = \frac{R_4 + R_3}{R_3} \left[ \frac{R_2 V_1 + R_1 V_2}{R_1 + R_2} \right]$$



$$V_{out} = -R_3 \left[ \frac{V_1}{R_1} + \frac{V_2}{R_2} \right]$$

# Subtraction

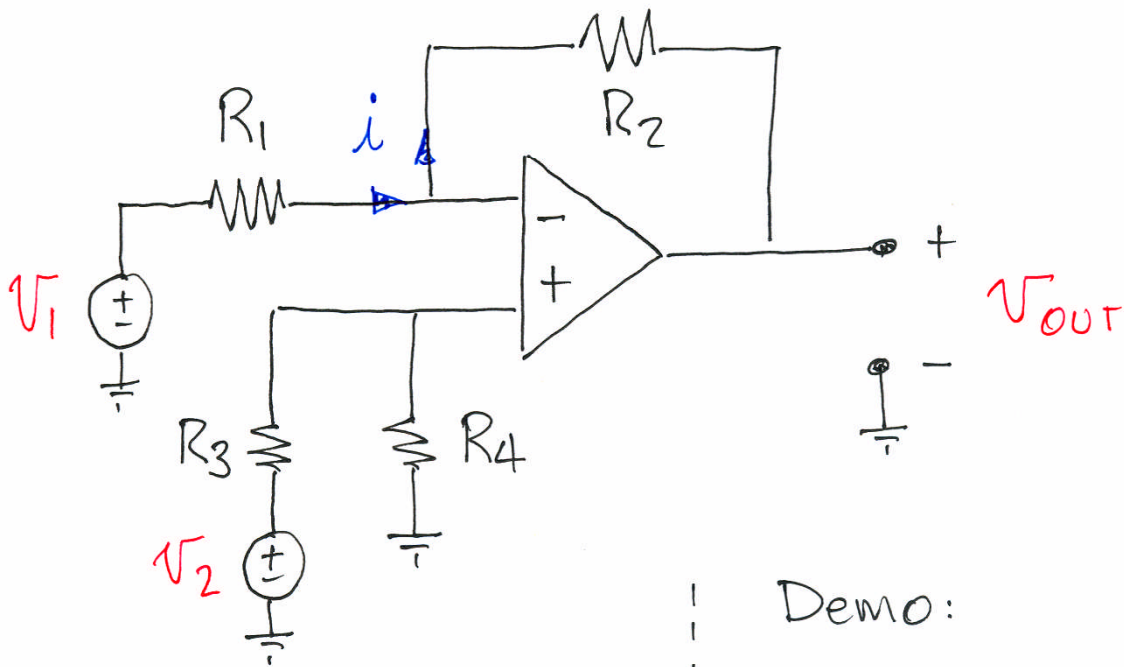


$$V_- \approx V_+ = \frac{R_4}{R_3 + R_4} V_2$$

$$i = \frac{V_1 - V_-}{R_1}$$



$$V_{out} = V_- - R_2 i$$

$$V_{out} = \frac{R_4}{R_3 + R_4} \cdot \frac{R_1 + R_2}{R_1} V_2 - \frac{R_2}{R_1} V_1$$

Demo:

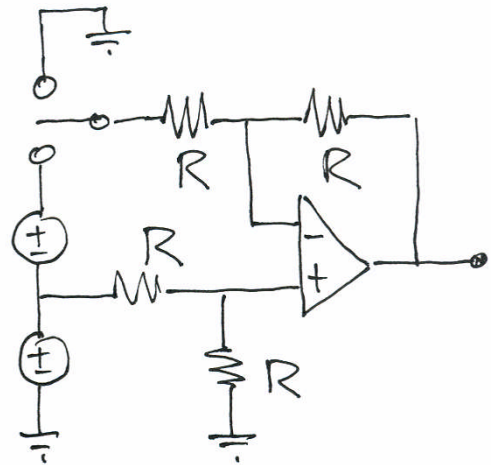


# Superposition

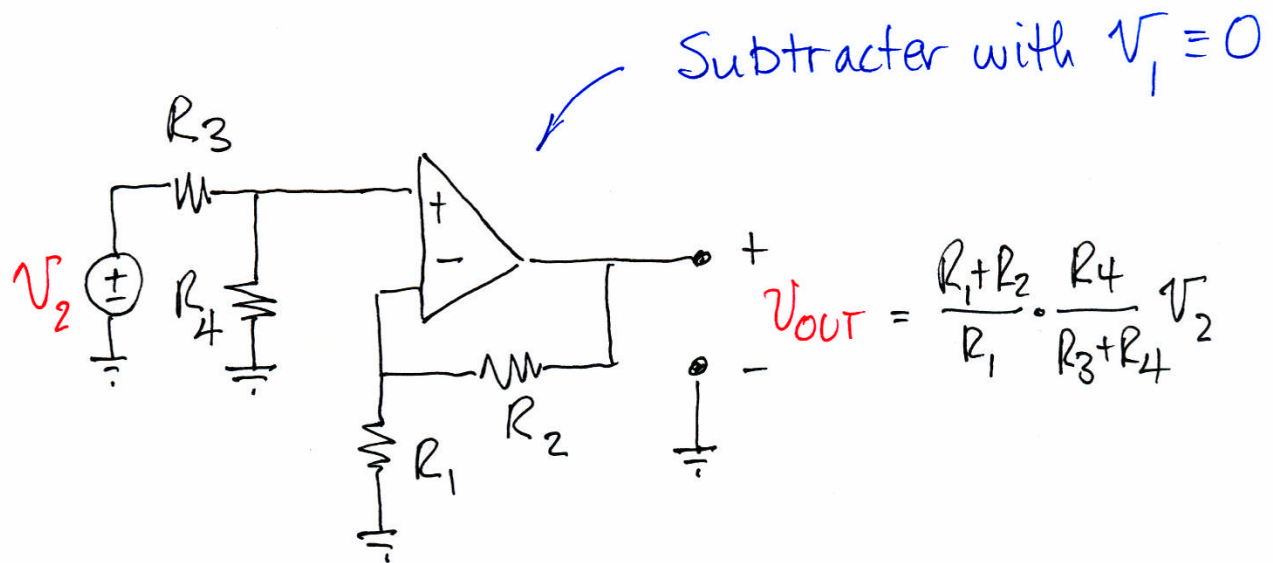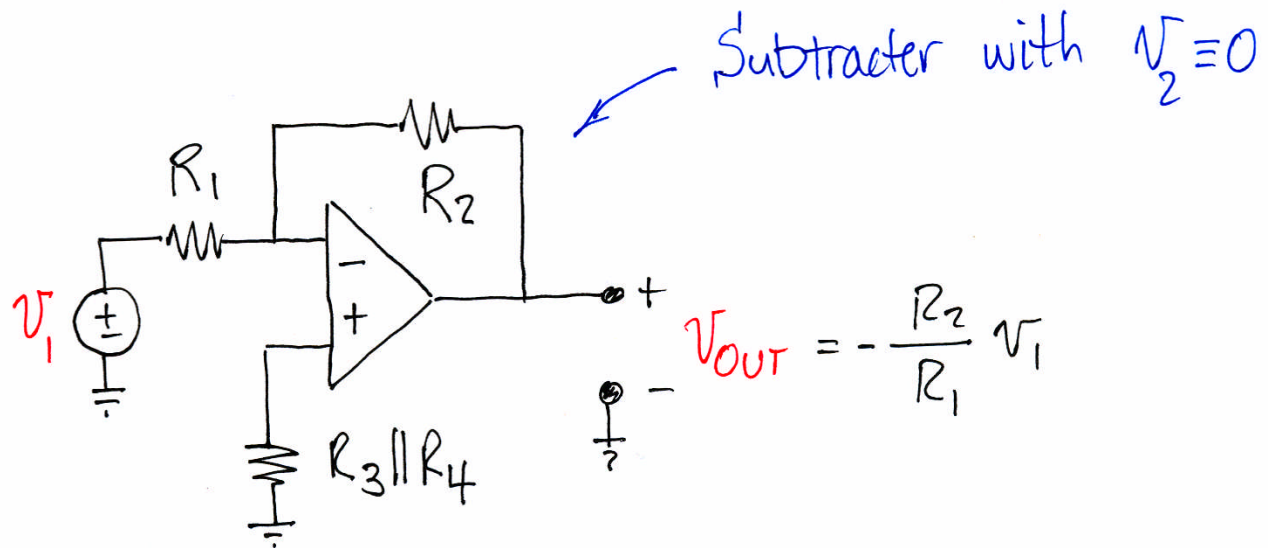


Subtractor: 
$$V_{OUT} = \frac{R_1 + R_2}{R_1} \cdot \frac{R_4}{R_3 + R_4} V_2 - \frac{R_2}{R_1} V_1$$





# Differential Instrumentation Amplifier

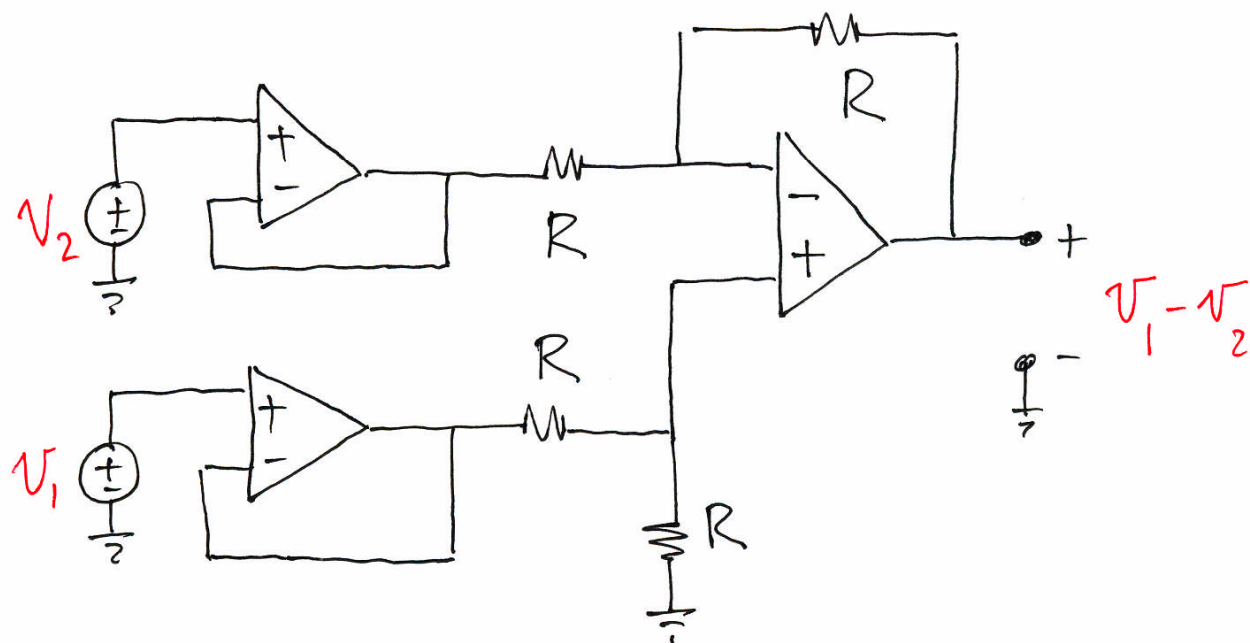

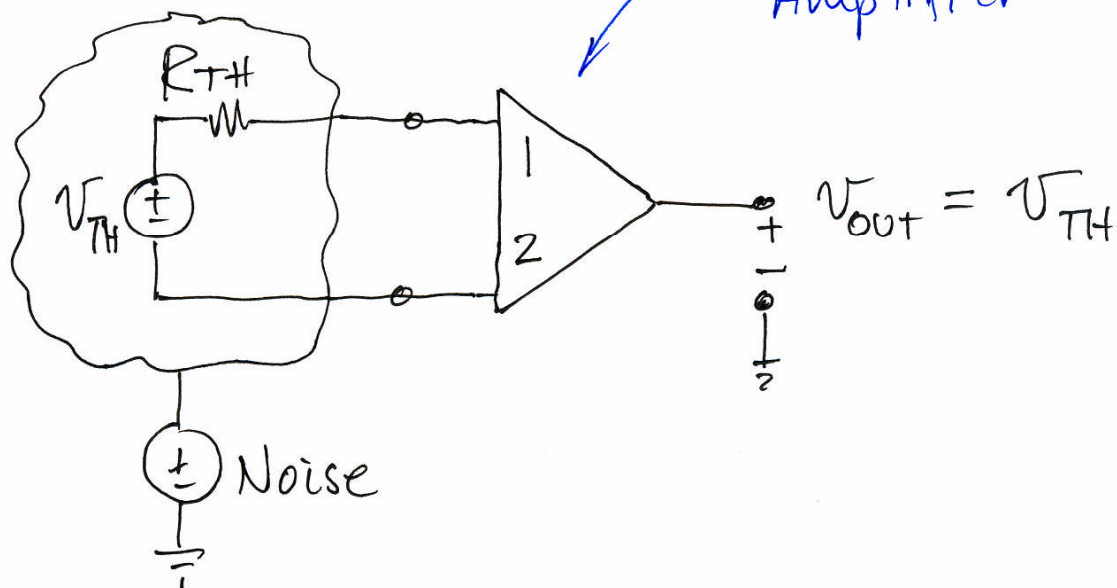Differential  
Instrumentation  
Amplifier



# Differentiation & Integration I

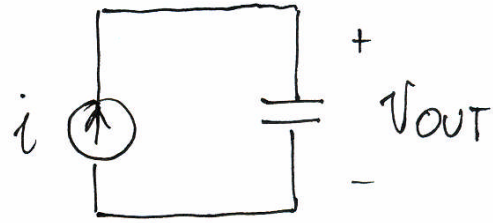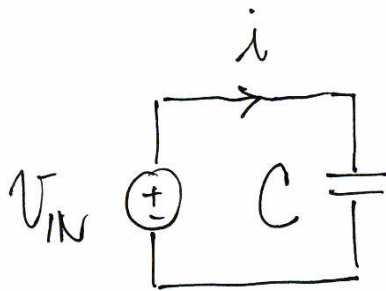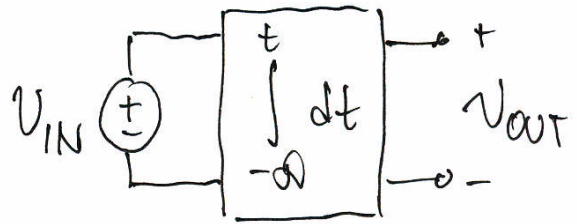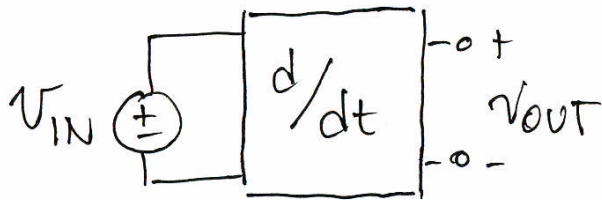

$$i = C \frac{dv}{dt}$$


$$v_{OUT} = \frac{1}{C} \int_{-\infty}^t i dt$$

Needs conversion  
from  $i$  to  $v_{OUT}$ .

Needs conversion  
from  $v_{IN}$  to  $i$ .

(Inductors are generally not used because they are too big and too lossy.)

# Differentiation & Integration II

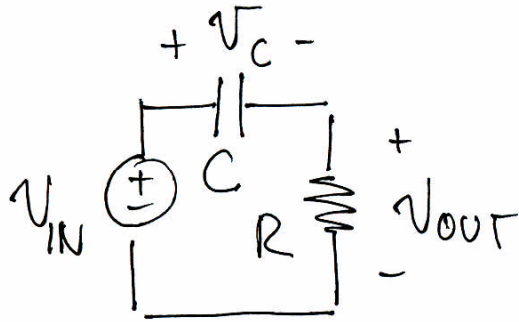

Resistor converts  
current to voltage.

Good Differentiation

↓


$$V_C \gg V_{OUT}$$

↓

$$V_C \gg RC \frac{dV_C}{dt}$$

↓

$$\omega \ll \frac{1}{RC}$$

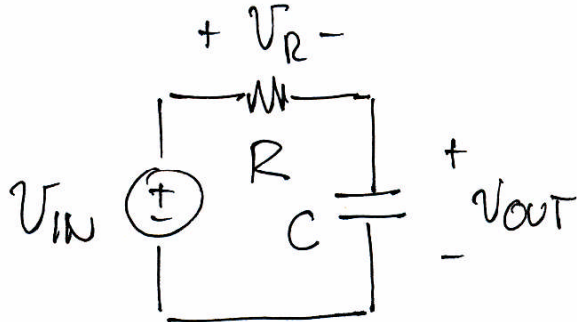

Resistor converts  
voltage to current.

Good Integration

↓

$$V_R \gg V_{OUT}$$


↓

$$RC \frac{dV_{OUT}}{dt} \gg V_{OUT}$$


↓

$$\omega \gg \frac{1}{RC}$$


# Better Converters

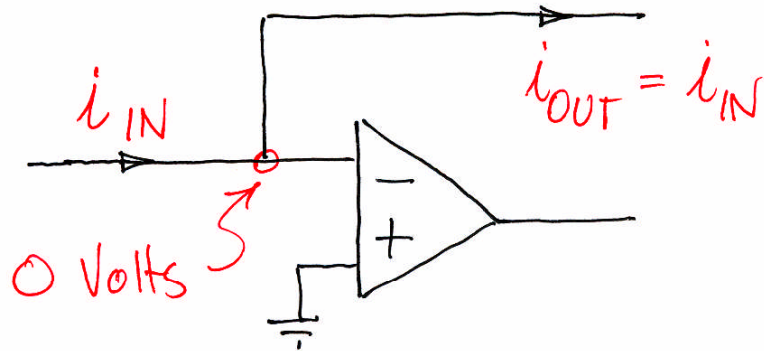


Current - To - Voltage  
Converter

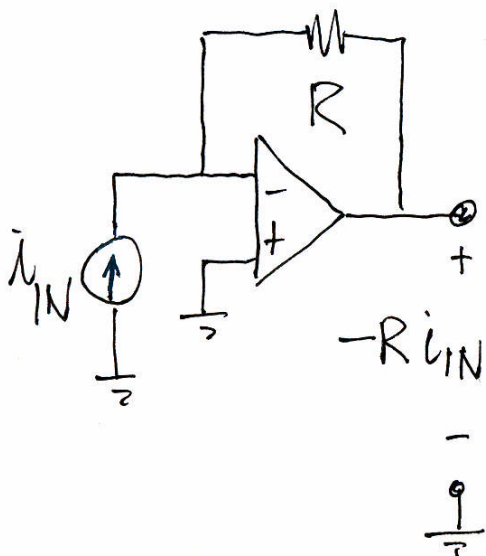

Voltage - To - Current  
Converter

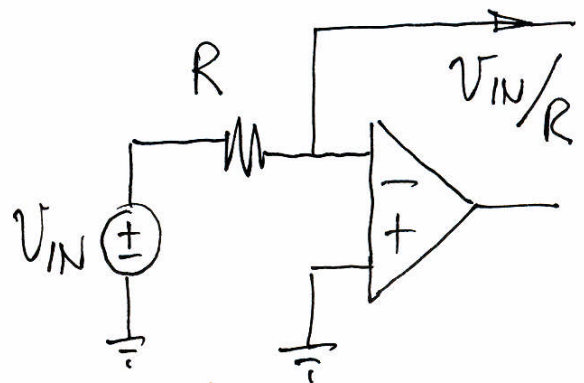

## Differentiation III

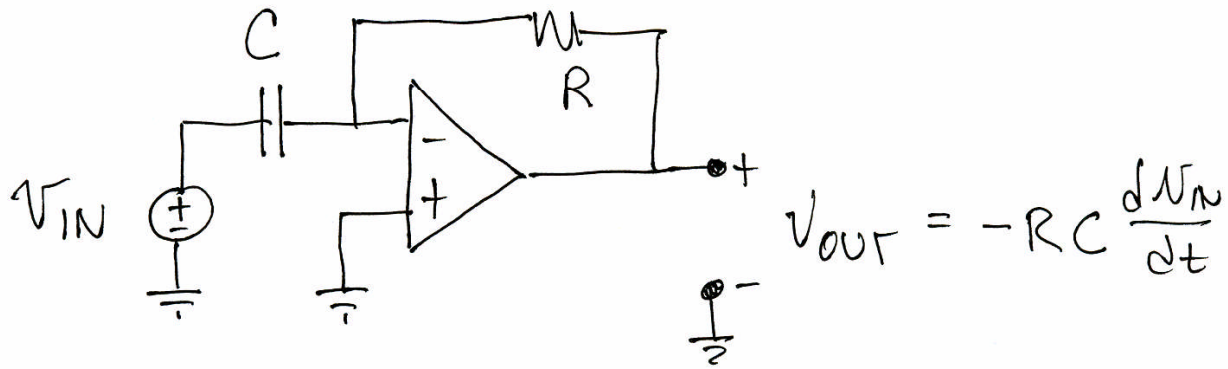

Good Differentiation

$$\downarrow$$
$$v_{IN} \gg v_- = -\frac{v_{OUT}}{A}$$

$$\downarrow$$
$$v_{IN} \gg \frac{RC}{A} \frac{dv_{IN}}{dt}$$

$$\downarrow$$
$$\omega \ll \frac{A}{RC}$$

Numbers:

$$R = 1 \text{ k}\Omega$$


$$C = 0.01 \mu\text{F}$$

$$A = 10^6$$

$$\omega \ll 10^4 \frac{\text{rad}}{\text{s}}$$

Op Amp is  
probably too  
slow!!

# Integration III

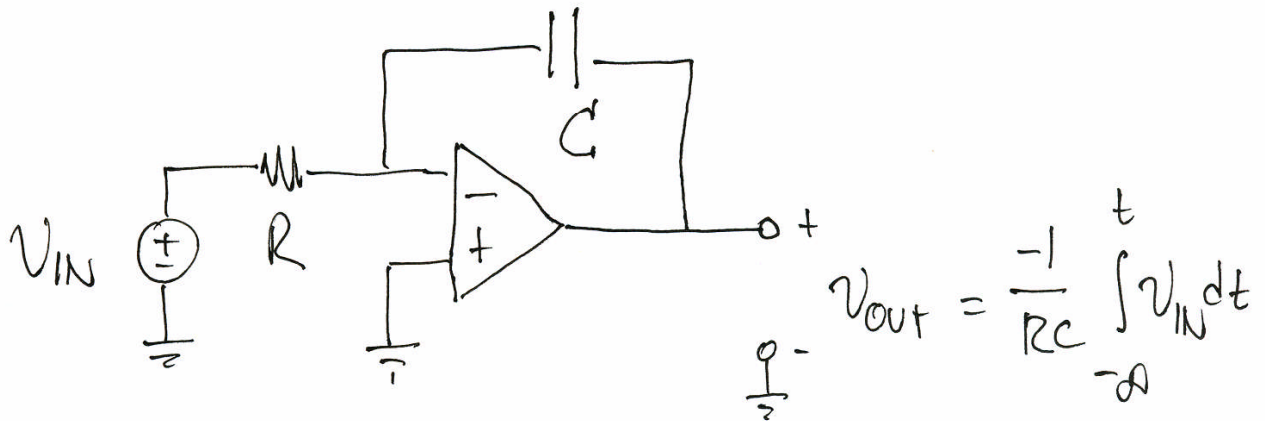

Good Integration

↓

$$V_{IN} \gg V_- = -\frac{V_{OUT}}{A}$$

↓

$$V_{IN} \gg \frac{1}{ARC} \int_{-\infty}^t V_{IN} dt$$

↓

$$\omega \gg \frac{1}{ARC}$$

Numbers:

$$R = 1 \text{ k}\Omega$$


$$C = 0.01 \mu\text{F}$$

$$A = 10^6$$

$$\omega \gg 10^{-1} \frac{\text{rad}}{\text{s}}$$

Beware of offsets!


# Integration IV (Offsets)

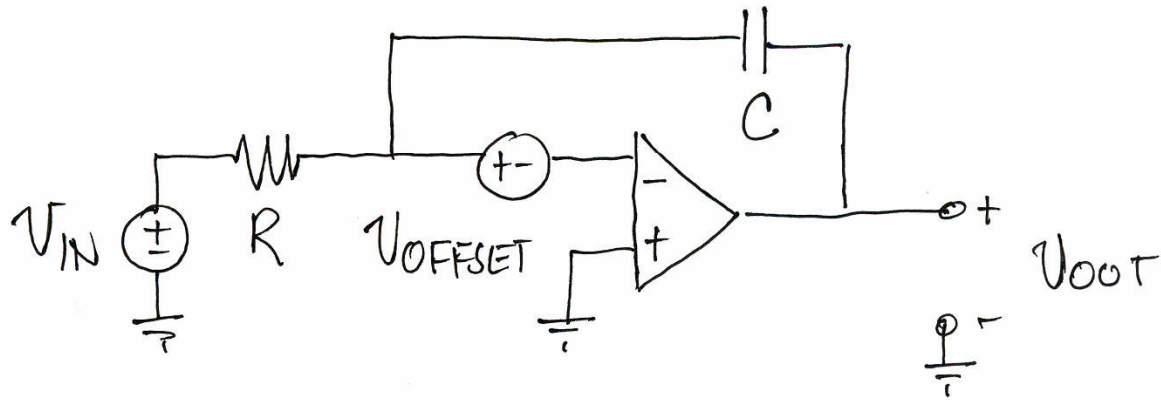


$$V_{OUT} = V_{OFFSET} + \frac{1}{RC} \int_{-\infty}^t (V_{OFFSET} - V_{IN}) dt$$

$V_{OFFSET}$  must be balanced, otherwise  $V_{OUT} \rightarrow \pm \infty$  even when  $V_{IN} \equiv 0$ .

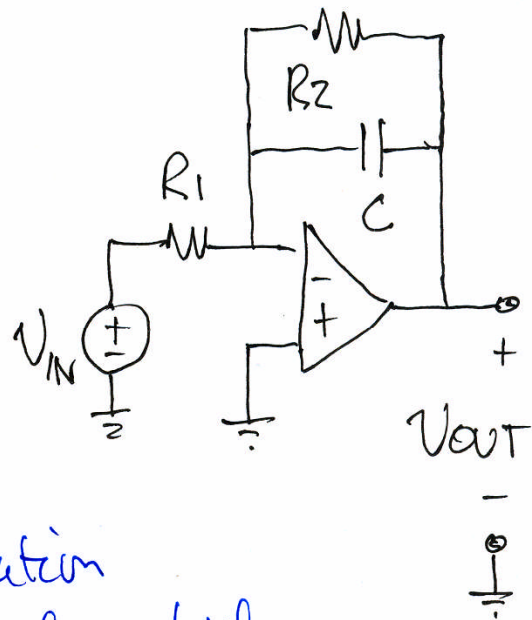Use the circuit to the right, for example, for which good integration  $\Rightarrow \omega \gg 1/R_2C$ , but for which  $V_{OUT} \approx \frac{R_2 + R_1}{R_1} V_{OFFSET}$  when  $V_{IN} \equiv 0$ .



# Analog Computers

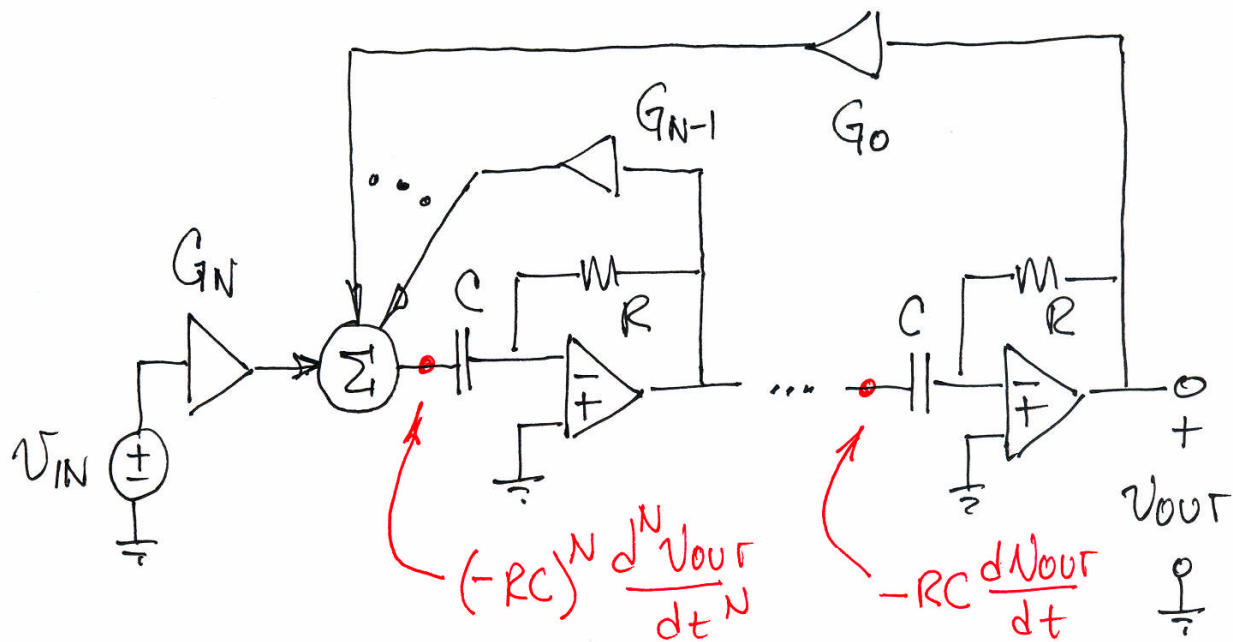


←  $N$  Integrators →

$$(-RC)^N \frac{d^N V_{OUT}}{dt^N} = G_{N-1} (-RC)^{N-1} \frac{d^{N-1} V_{OUT}}{dt^{N-1}} + \dots + G_0 V_{OUT} + G_N V_{IN}$$

Note that  $V_{IN}$  can also be injected along the integrator string so as to inject its derivatives.

# Filter Synthesis I

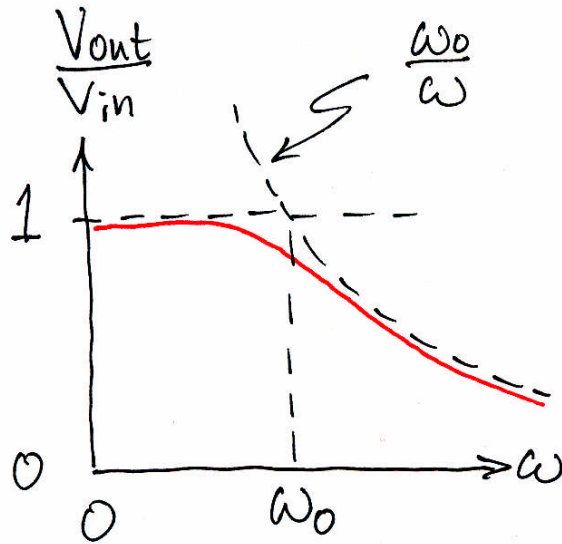

$$\Rightarrow \frac{\tilde{V}_{out}}{V_{in}} = \frac{1}{1 + j\omega/\omega_0}$$


$$\tilde{V}_{out} (1 + j\omega/\omega_0) = V_{in}$$

$$j\omega \rightarrow \frac{d}{dt}$$

$$V_{out} + \frac{1}{\omega_0} \frac{dV_{out}}{dt} = V_{in}$$

Construct an "analog computer" from the differential equation.

## Filter Synthesis II

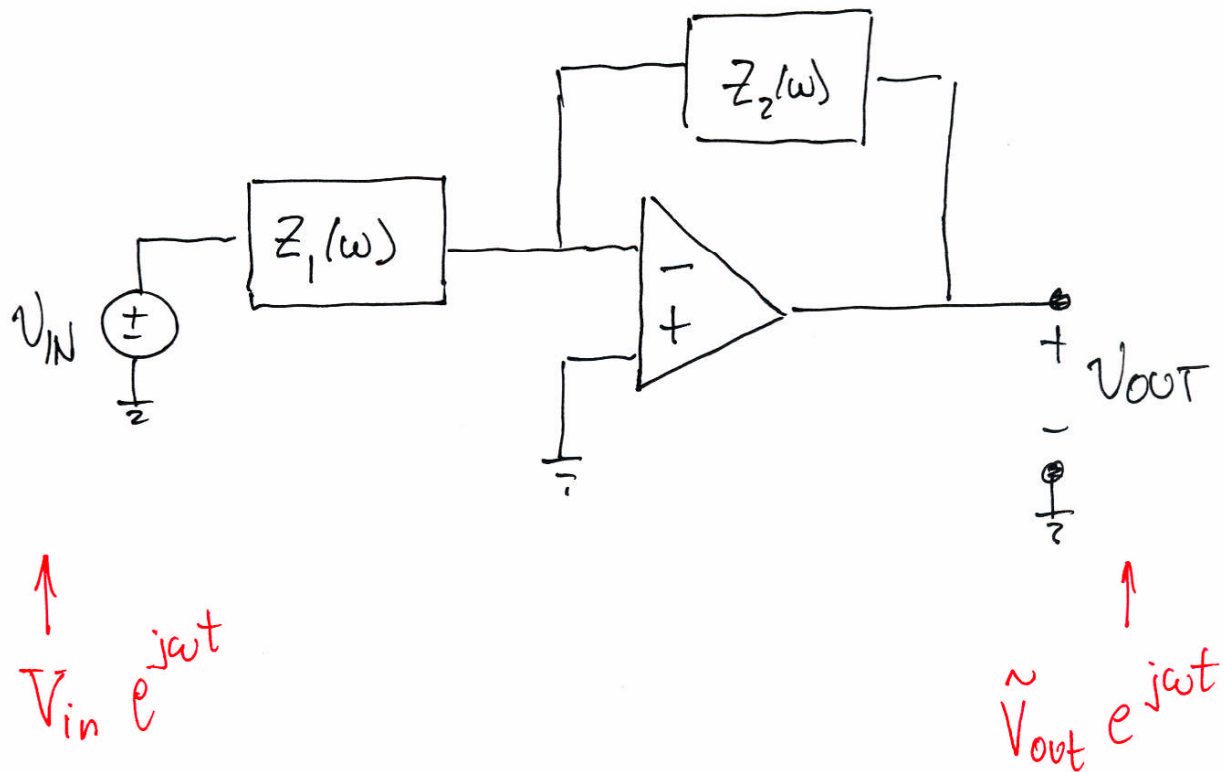

$$\tilde{V}_{out} = \frac{Z_2(\omega)}{Z_1(\omega)} V_{in}$$

Use parallel and series stages to obtain more complex filter.