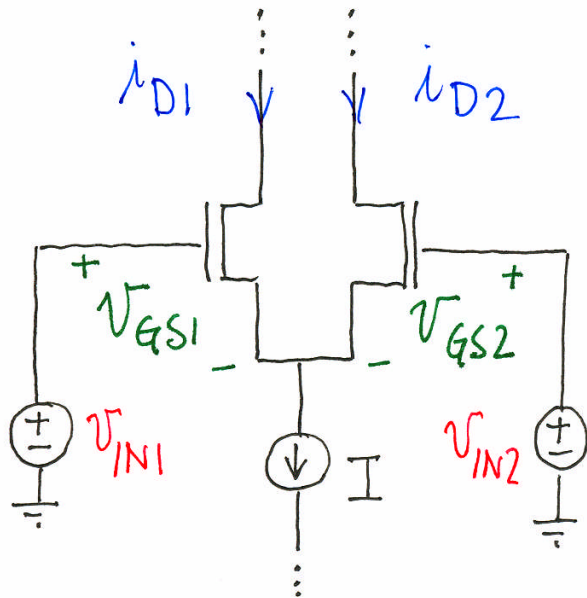


6.002 - Lecture 22

Op Amp Details

- MOSFET Review
- Differential Amplifier
- An Operational Amplifier
- Small-Signal Analysis

Differential Amplifier



$$i_{D1} + i_{D2} = I$$

$$i_{D1} = \frac{K}{2} (V_{GS1} - V_T)^2$$

$$i_{D2} = \frac{K}{2} (V_{GS2} - V_T)^2$$


$$V_{IN1} - V_{GS1} + V_{GS2} - V_{IN2} = 0$$

$$i_{D1} + \frac{K}{2} (V_{GS2} - V_T)^2 = I$$


$$i_{D1} + \frac{K}{2} (V_{IN2} - V_{IN1} + V_{GS1} - V_T)^2 = I$$

$$i_{D1} + \frac{K}{2} (V_{IN2} - V_{IN1} + \sqrt{\frac{2i_{D1}}{K}})^2 = I$$

$$i_{D1} = \text{Function}(V_1 - V_2)$$

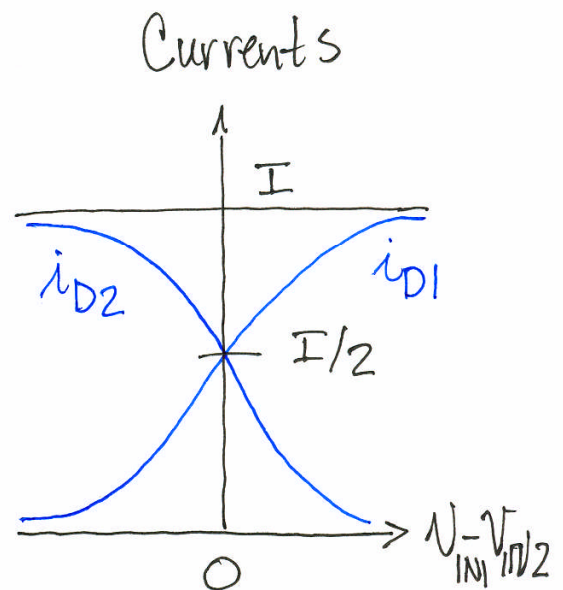


An Op-Amp

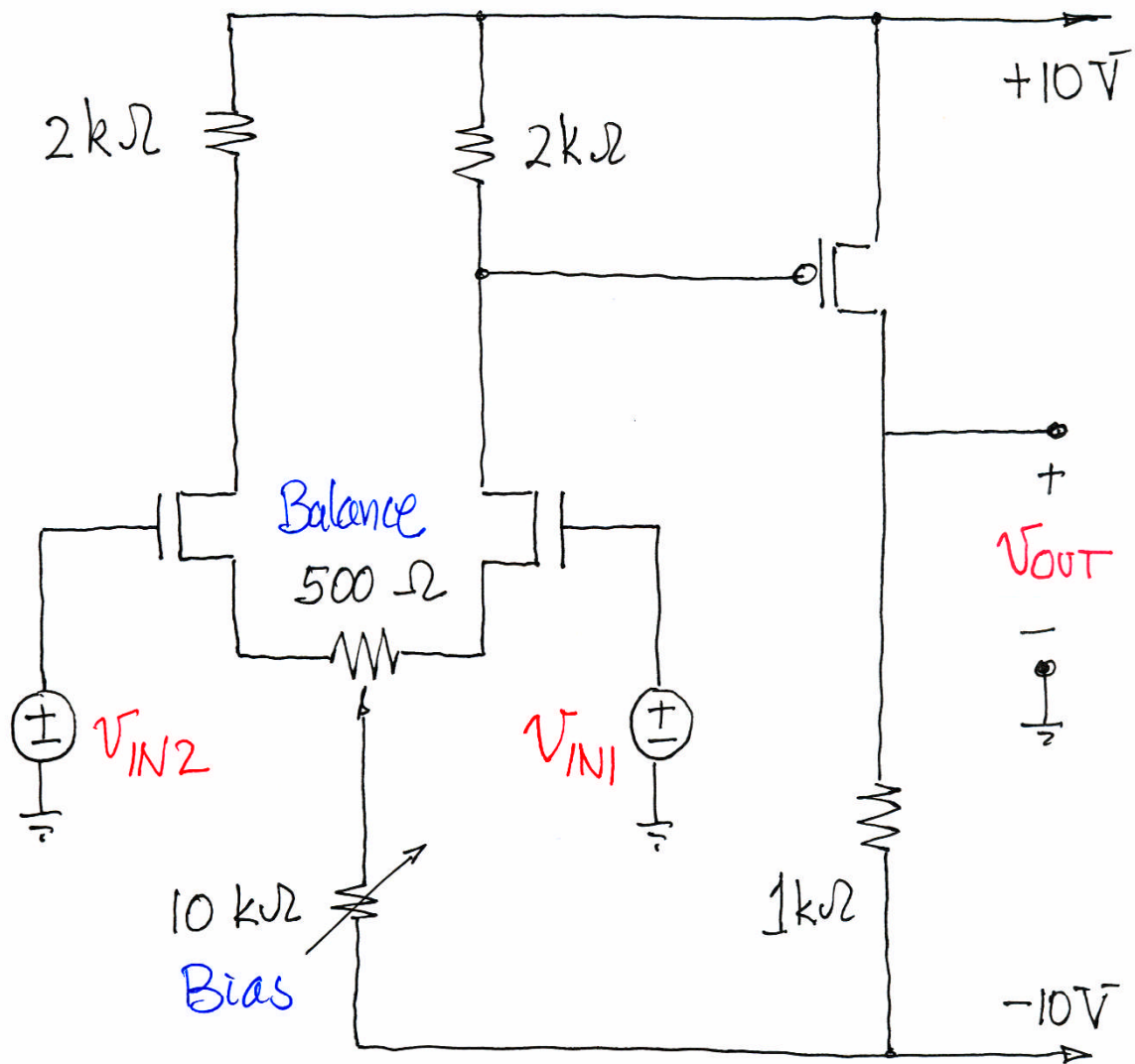


Adjust balance and bias for balanced currents and zero output when $V_{IN1} = V_{IN2} = 0$.

Approximate Biasing

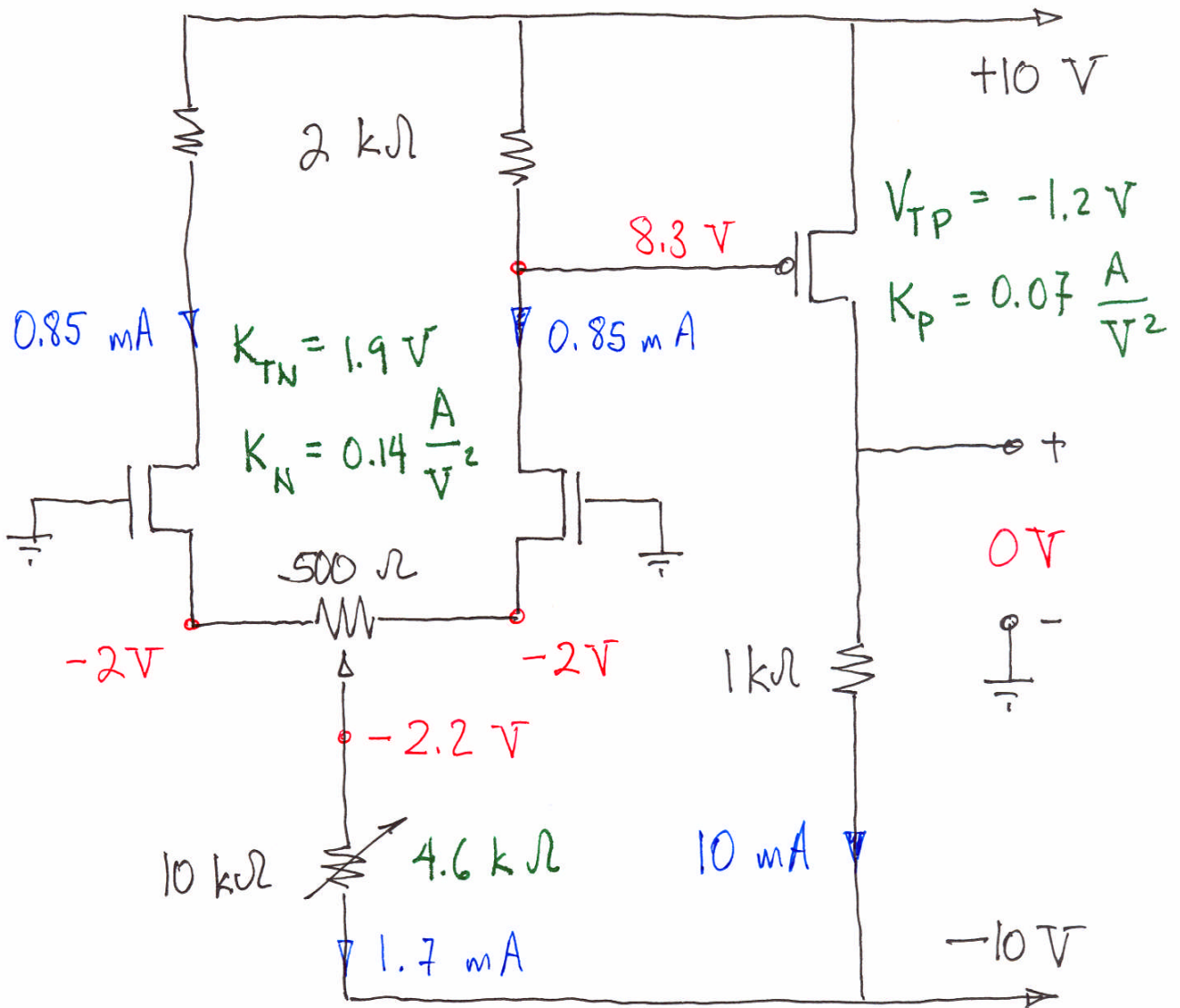


Small-Signal Model

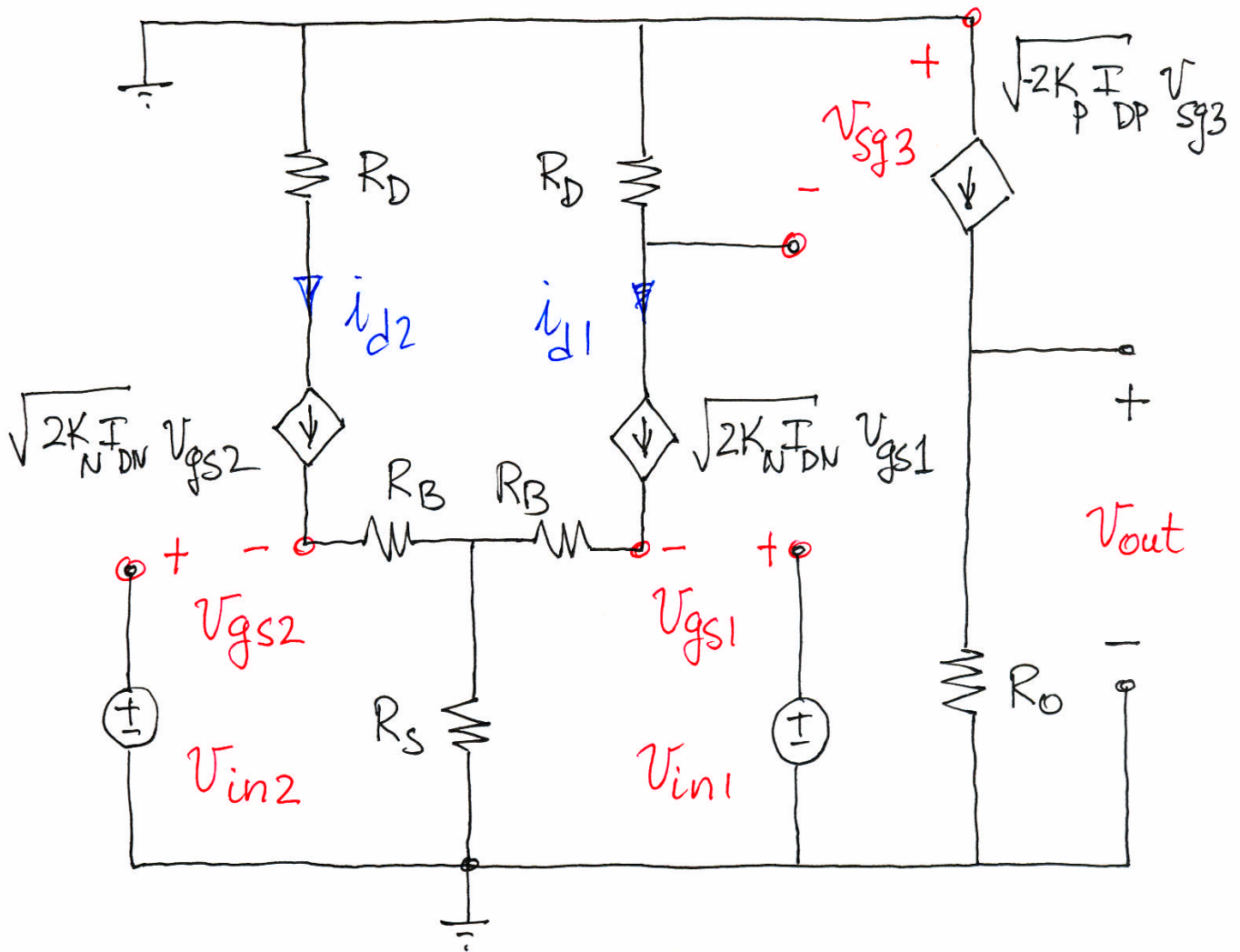

(N) $i_D = \frac{K_N}{2} (V_{GS} - V_{TN})^2 \Rightarrow i_d = K_N (V_{GS} - V_{TN}) v_{gs} = \sqrt{2K_N I_{DN}} v_{gs}$

(P) $-i_D = \frac{K_P}{2} (V_{SG} + V_{TP})^2 \Rightarrow -i_d = K_P (V_{SG} + V_{TP}) v_{sg} = \sqrt{2K_P I_{DP}} v_{sg}$

Modes

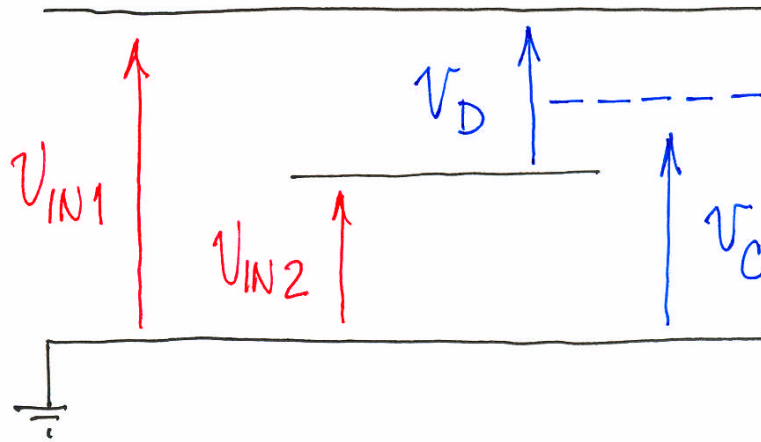

$$v_D \equiv v_{IN1} - v_{IN2} \equiv \text{Difference Mode}$$

$$v_C \equiv \frac{v_{IN1} + v_{IN2}}{2} \equiv \text{Common Mode}$$

$$v_{IN1} = v_C + \frac{v_D}{2}$$

$$v_{IN2} = v_C - \frac{v_D}{2}$$

Same for large and small signals

Difference Mode

$$V_c \equiv 0 \quad V_{in1} = -V_{in2} = V_d/2$$

$$\text{Symmetry} \Rightarrow \begin{aligned} V_{gs2} &= -V_{gs1} & i_d &= 0 \\ i_{d2} &= -i_{d1} & R_S i_s &= 0 \end{aligned}$$

$$i_{d1} R_B + V_{gs1} = V_{in1}$$

$$i_{d1} = \sqrt{2K_N I_{DN}} V_{gs1}$$

$$i_{d1} (R_B + 1/\sqrt{2K_N I_{DN}}) = V_{in1} = V_d/2$$

$$i_{d1} = \frac{\sqrt{2K_N I_{DN}} V_d}{2(1 + R_B \sqrt{2K_N I_{DN}})}$$

$$V_{out} = \frac{R_o \sqrt{2K_P I_{DP}} R_D \sqrt{2K_N I_{DN}}}{2(1 + R_B \sqrt{2K_N I_{DN}})} V_d$$

$$\underbrace{\frac{R_o \sqrt{2K_P I_{DP}} R_D \sqrt{2K_N I_{DN}}}{2(1 + R_B \sqrt{2K_N I_{DN}})}}_{\text{Difference Mode Gain}} \equiv G_D$$

Common Mode

$$V_d \equiv 0 \quad V_{in1} = V_{in2} = V_c$$

$$\text{Symmetry} \Rightarrow V_{gs1} = V_{gs2} \quad i_{d1} = i_{d2}$$

$$2R_s i_{d1} + R_B i_{d1} + V_{gs1} = V_{in1}$$

$$i_{d1} = \sqrt{2K_N I_{DN}} V_{gs1}$$

$$i_{d1} (2R_s + R_B + 1/\sqrt{2K_N I_{DN}}) = V_{in1} = V_c$$

$$i_{d1} = \frac{\sqrt{2K_N I_{DN}} V_c}{1 + (2R_s + R_B) \sqrt{2K_N I_{DN}}}$$

$$V_{out} = \frac{R_o \sqrt{2K_p I_{DP}} R_D \sqrt{2K_N I_{DN}}}{1 + (2R_s + R_B) \sqrt{2K_N I_{DN}}} V_c$$

$$\text{Common Mode Gain} = G_c$$

Gain Summary

Combine difference and common mode analyses using superposition.

$$V_{out} = G_D (V_{IN1} - V_{IN2}) + G_C \left(\frac{V_{IN1} + V_{IN2}}{2} \right)$$

$$= \underbrace{\left(G_D + \frac{G_C}{2} \right)}_{G_1} V_{IN1} - \underbrace{\left(G_D - \frac{G_C}{2} \right)}_{G_2} V_{IN2}$$

From
Non-Inverting
Input " V_+ "

From
Inverting
Input " V_- "

Numbers

$$R_B = 250 \, \Omega$$

$$R_S = 4600 \, \Omega$$

$$R_D = 2000 \, \Omega$$

$$R_O = 1000 \, \Omega$$

$$I_{DN} = 0.85 \, \text{mA}$$

$$-I_{DP} = 10 \, \text{mA}$$

$$K_N = 0.14 \, \text{A/V}^2$$

$$K_P = 0.07 \, \text{A/V}^2$$

$$\sqrt{2K_N I_{DN}} = 0.015 \, \text{A/V}$$

$$\sqrt{-2K_P I_{DP}} = 0.037 \, \text{A/V}$$


$$G_D = 117$$

$$G_C = 8$$

$$G_1 = 121 \quad (\text{From non-inverting input})$$

$$G_2 = 113 \quad (\text{From inverting input})$$

Applications

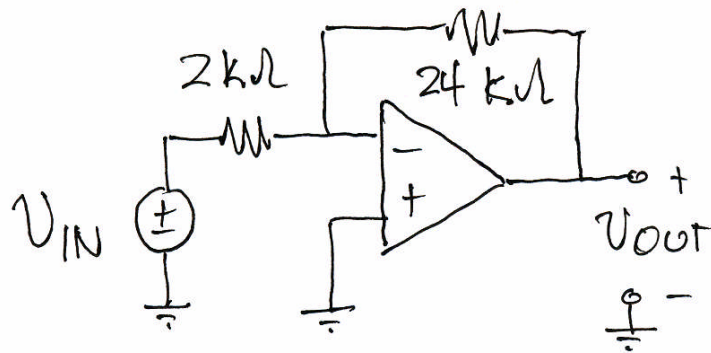

$$\frac{AG}{A+G} = \frac{121 \cdot 12}{121 + 12} = 10.9$$

$$\text{Let } A = G_2.$$

