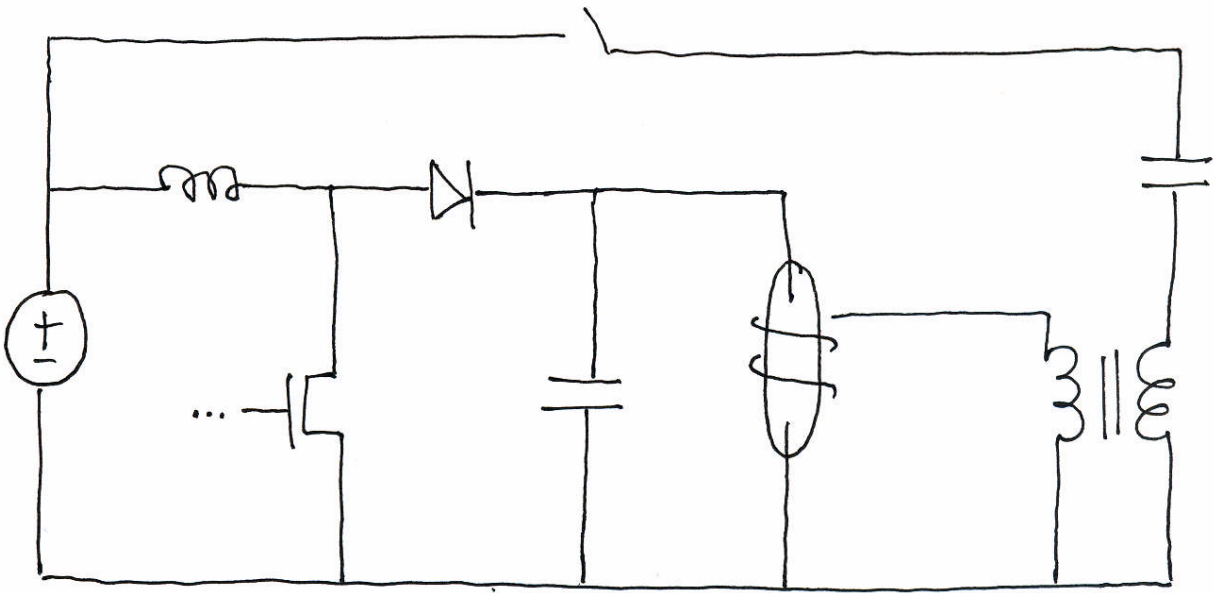


6.002 - Lecture 24

Diodes & LC Networks

- Review of LC Networks
- Diodes As Uncontrolled Switches
- Energy Processing & Conservation
- Preview of Power Electronics
- Voltage Pump Example

Camera Flash Circuit




Voltage Pump

Flash


Igniter

Typical Operation: 1.5 V @ Battery
 300 V @ Capacitor
 10 kV @ Igniter


Voltage Pump (Boost Converter)

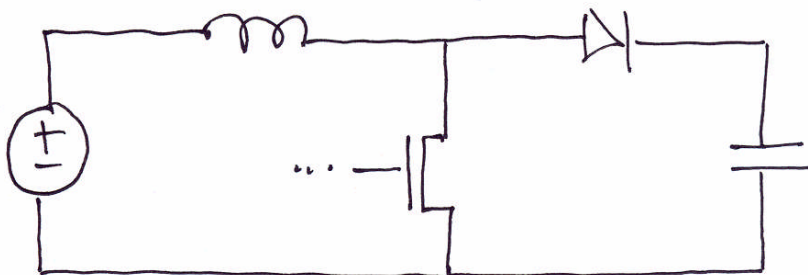


State I
MOSFET On
Diode Off

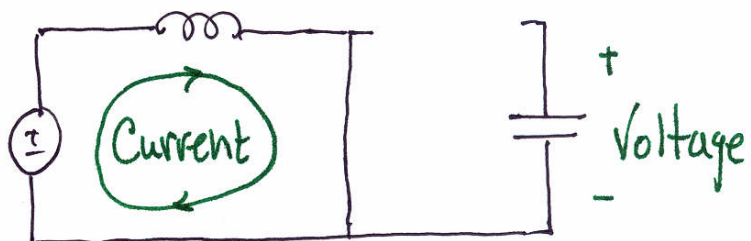

State II
MOSFET Off
Diode On

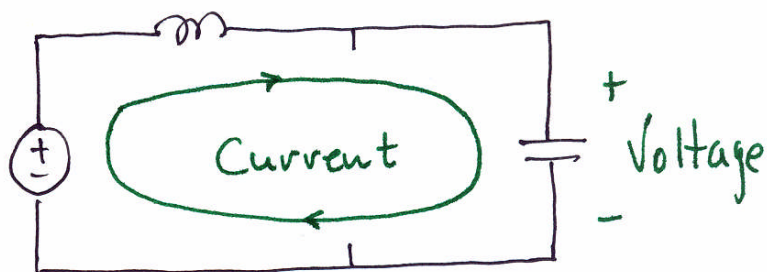

State III
MOSFET off
Diode Off

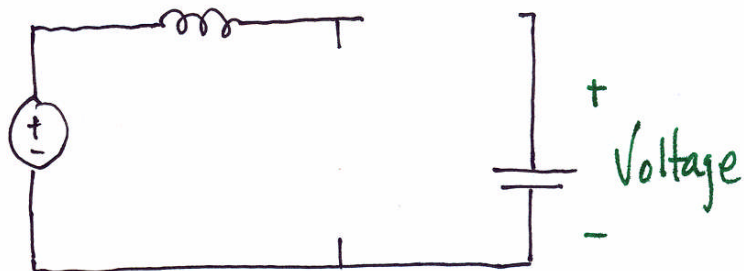


Observations

- MOSFET $\Rightarrow$ Ideal controlled switch
- Diode $\Rightarrow$ Ideal uncontrolled switch
- Inductor $\Rightarrow$ Energy storage
- Capacitor $\Rightarrow$ Energy storage
- No use for lossy resistors

Power electronics preview!

State I

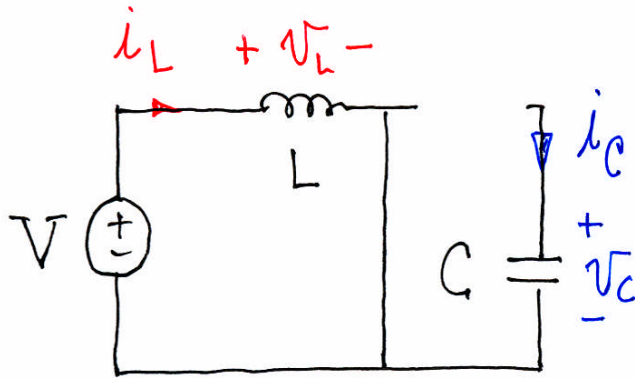


$$-T \leq t \leq 0$$

$$i_L(-T) = 0$$


$$v_C(-T) = \text{Given}$$

$$V = v_L = L \frac{di_L}{dt} \Rightarrow i_L(t) = \frac{V}{L} (t+T)$$

$$0 = i_C = C \frac{dv_C}{dt} \Rightarrow v_C(t) = v_C(-T)$$

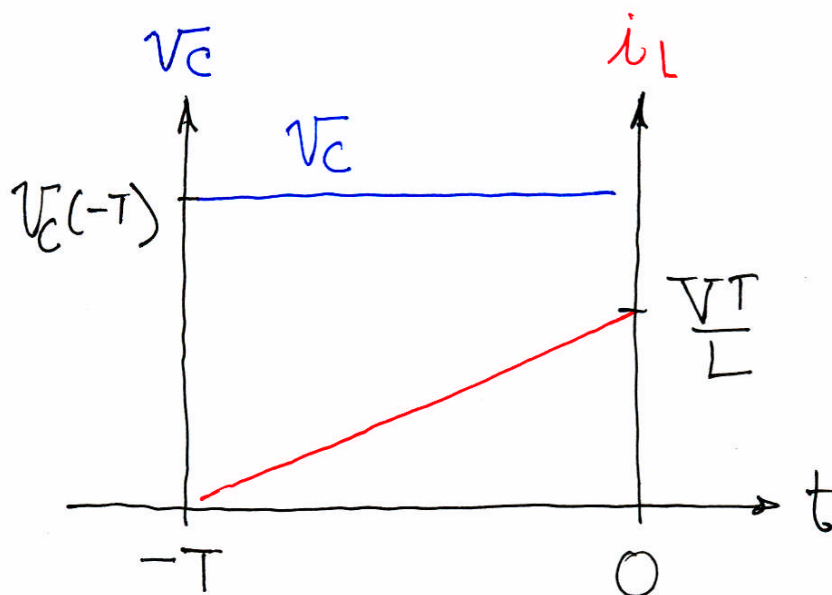

State II

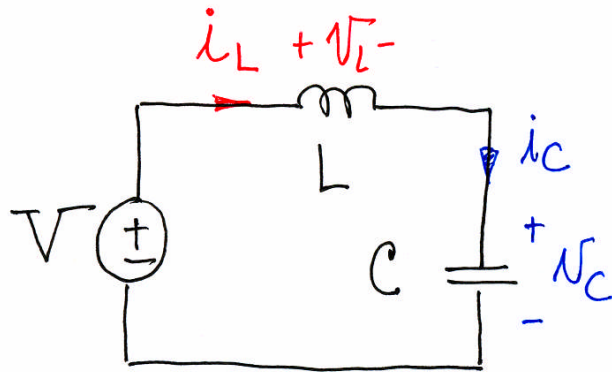

$0 \leq t \leq \text{Diode Turn Off}$

$$i_L(0) = \text{Given}$$

$$V_C(0) = \text{Given}$$

$$V = LC \frac{d^2 V_C}{dt^2} + V_C \quad \& \quad i_C = C \frac{dV_C}{dt}$$

$$V_C = V + A \sin\left(\frac{t}{\sqrt{LC}}\right) + B \cos\left(\frac{t}{\sqrt{LC}}\right)$$


$$i_L = C \frac{dV_C}{dt} = \sqrt{\frac{C}{L}} A \cos\left(\frac{t}{\sqrt{LC}}\right) - \sqrt{\frac{C}{L}} B \sin\left(\frac{t}{\sqrt{LC}}\right)$$

$$V_C = V + \sqrt{\frac{L}{C}} i_L(0) \sin\left(\frac{t}{\sqrt{LC}}\right) + (V_C(0) - V) \cos\left(\frac{t}{\sqrt{LC}}\right)$$

$$i_L = i_L(0) \cos\left(\frac{t}{\sqrt{LC}}\right) - \sqrt{\frac{C}{L}} (V_C(0) - V) \sin\left(\frac{t}{\sqrt{LC}}\right)$$

Demo

Ideal:

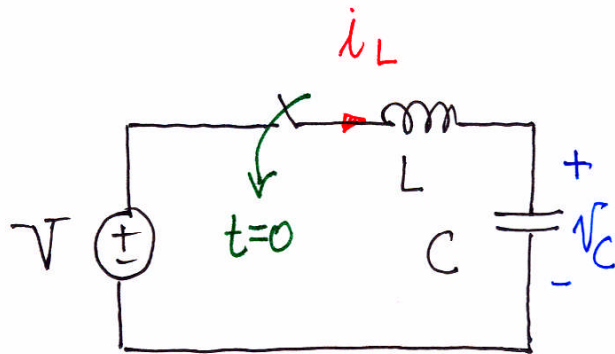

$$i_L(0) = 0$$

$$V_C(0) = 0$$


$$V_C = V \left(1 - \cos\left(\frac{t}{\sqrt{LC}}\right) \right)$$

$$i_L = \sqrt{\frac{C}{L}} V \sin\left(\frac{t}{\sqrt{LC}}\right)$$

Actual:

Sig Gen

Inductor

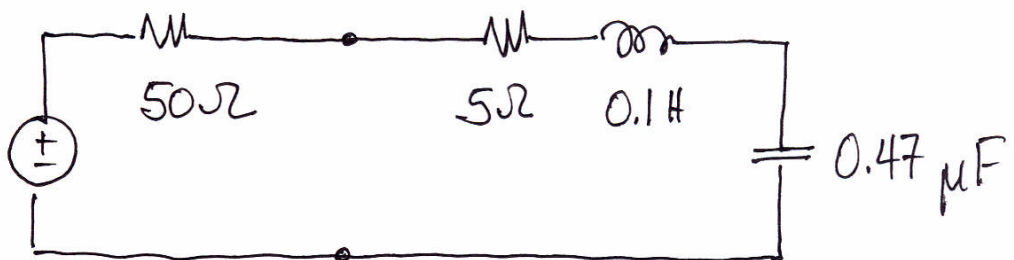

$$2\pi\sqrt{LC} = 1.3 \text{ } \mu\text{s}$$

$$\frac{\pi}{2}\sqrt{LC} = 0.34 \text{ } \mu\text{s}$$

$$Q = \frac{\sqrt{L/C}}{R} = \frac{461 \text{ } \Omega}{55 \text{ } \Omega} = 8.4 \Rightarrow \text{Underdamped}$$

$$e^{-\frac{Rt}{2L}} \Rightarrow 50\% \text{ Decay Over } 2.5 \text{ } \mu\text{s}$$


All States Together

State II Review:



$\phi = \text{Positive}$

$$V_C(t) = V + \sqrt{(V_C(0) - V)^2 + \frac{L}{C} i_L^2(0)} \cos\left(\frac{t}{\sqrt{LC}} - \tan^{-1}\left(\sqrt{\frac{L}{C}} \frac{i_L(0)}{V_C(0) - V}\right)\right)$$
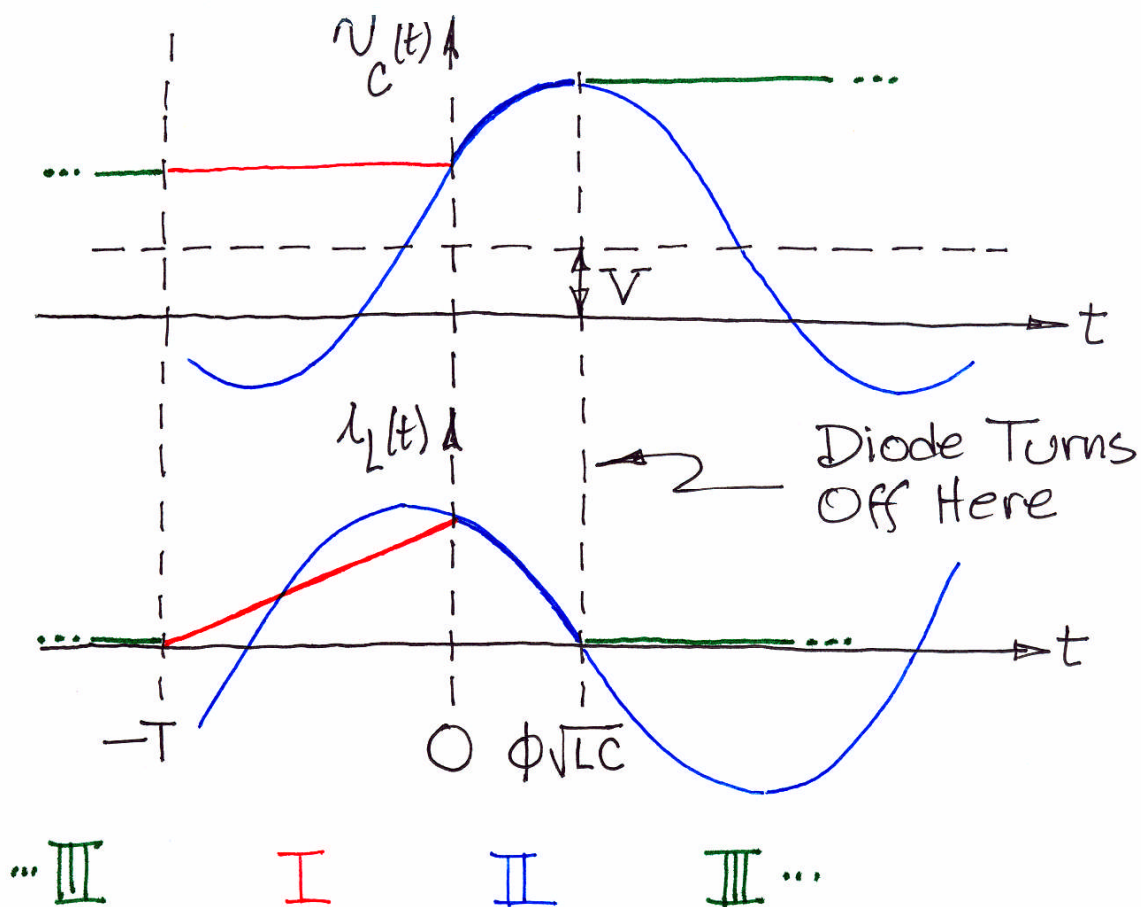
$$i_L(t) = -\sqrt{\frac{C}{L}(V_C(0) - V)^2 + i_L^2(0)} \sin\left(\frac{t}{\sqrt{LC}} - \tan^{-1}\left(\sqrt{\frac{L}{C}} \frac{i_L(0)}{V_C(0) - V}\right)\right)$$



Cycle Analysis

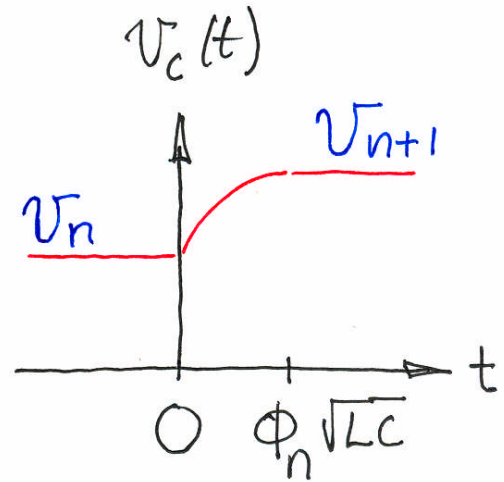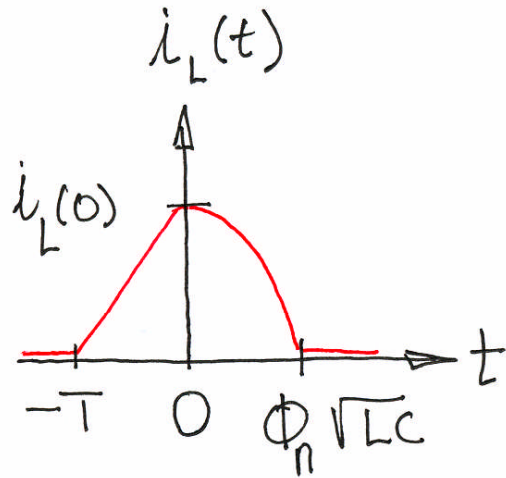

$$\begin{aligned}
 v_{n+1} &= V + \sqrt{(v_n - V)^2 + \frac{L}{C} i_L^2(0)} \\
 &= V + \sqrt{(v_n - V)^2 + \frac{V^2 T^2}{LC}}
 \end{aligned}$$

$$(v_{n+1} - V)^2 = (v_n - V)^2 + \frac{V^2 T^2}{LC} \quad (v_0 - V)^2 = 0$$

$$v_n = V + V \sqrt{\frac{n T^2}{LC}}$$

Cycle Analysis Via Energy Conservation

Conservation: $\Delta W_C = -\Delta W_B + W_L$

Capacitor: $\Delta W_C = \frac{1}{2} C v_{n+1}^2 - \frac{1}{2} C v_n^2$

Inductor: $W_L = \frac{1}{2} L i_L^2(0)$

Battery: $-\Delta W_B = V \Delta Q$



Charge: $\Delta Q = C v_{n+1} - C v_n$

$$\frac{C}{2} v_{n+1}^2 - \frac{C}{2} v_n^2 = C V v_{n+1} - C V v_n + \frac{L}{2} i_L^2(0)$$

$$v_{n+1}^2 - 2V v_{n+1} + V^2 = v_n^2 - 2V v_n + V^2 + \frac{L}{C} i_L^2(0)$$

$$(v_{n+1} - V)^2 = (v_n - V)^2 + \frac{L}{C} i_L^2(0) \quad \dots \text{As Before!}$$

Demo

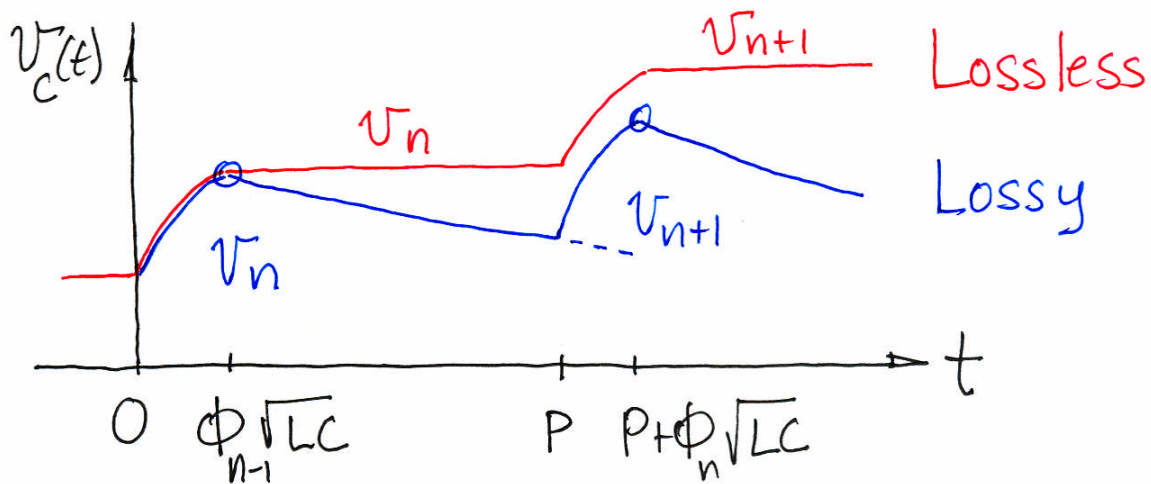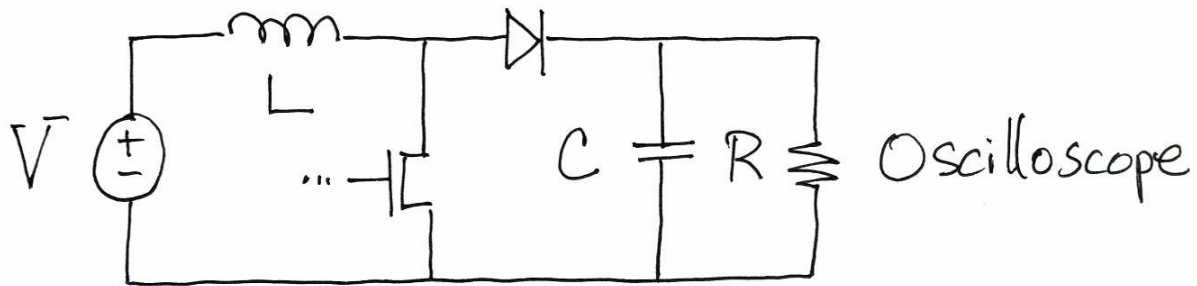

Assume $P \gg \phi_n \sqrt{LC} \Rightarrow V_n \rightarrow V_n e^{-P/RC}$
during energy conservation argument.

$$(V_{n+1} - V)^2 = (V_n e^{-P/RC} - V)^2 + \frac{L}{C} i_L^2(0)$$

$$V_n = V + \sqrt{(V_{n-1} e^{-P/RC} - V)^2 + \frac{V^2 T^2}{LC}}$$

↑ Except $n=1$.

Demo Numbers

$$L = 0.1 \text{ H}$$

$$V = 5.1 \text{ V}$$

$$C = 0.47 \text{ }\mu\text{F}$$

$$R = 10 \text{ M}\Omega$$

$$2\pi\sqrt{LC} = 1.36 \text{ ms}$$

$$T \approx 0.75 \text{ ms}$$

$$\sqrt{L/C} = 460 \text{ }\Omega$$

$$P = 50 \text{ ms}$$

n	Predicted V_n [V]	Measured V_n [V]
0	5.1	5.1
1	23	24
2	30	30
3	35	35
4	40	39
5	44	42
6	47	44 (Clipped)