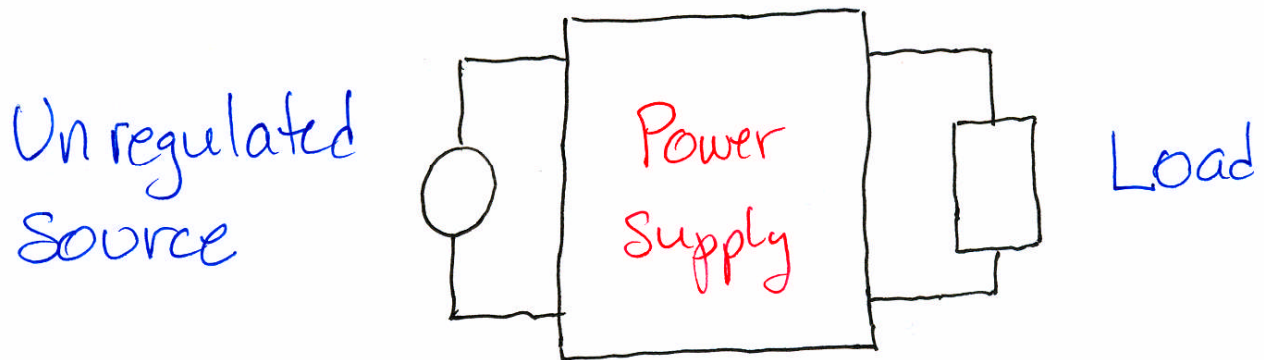


6.002 - Lecture 26

Power Electronics


- Introduction To Power Electronics
- Power Supplies
- Example: Solar-Powered Motor Drive

Power Supply Objectives



- Regulated load voltage or current despite an unregulated source.
- High efficiency.
- AC/DC source and AC/DC load.

Linear Power Supply Example

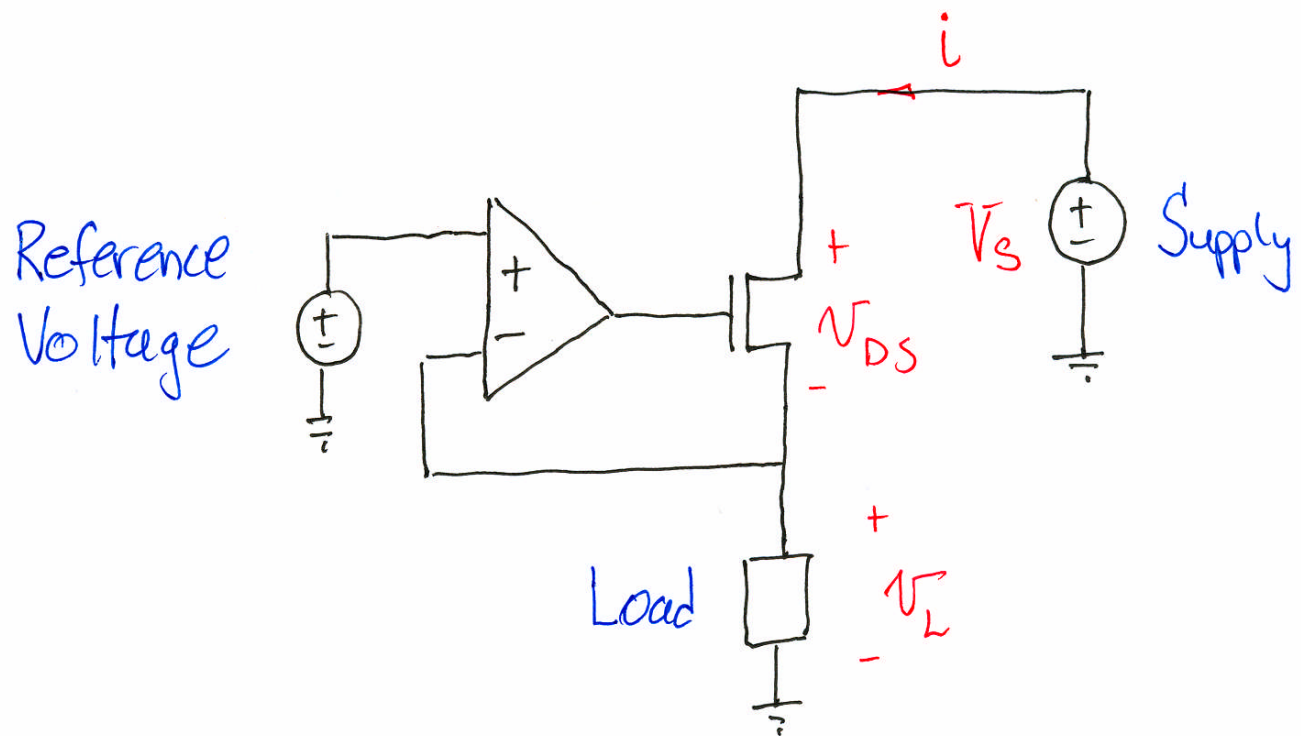


$$\underbrace{V_S i}_{\text{Power From Supply}} = \underbrace{V_{DS} i}_{\text{Power Lost In MOSFET}} + \underbrace{V_L i}_{\text{Power Into Load}}$$

Suppose: $V_S = 12 \dots 6$ Volts, $V_L = 5V$ and $i = 1A$.

Then, for $V_S = 12$ Volts, $P_L = 5W$, $P_{\text{MOSFET}} = 7W$,
and efficiency = 47%. Not good!

MOSFET Losses

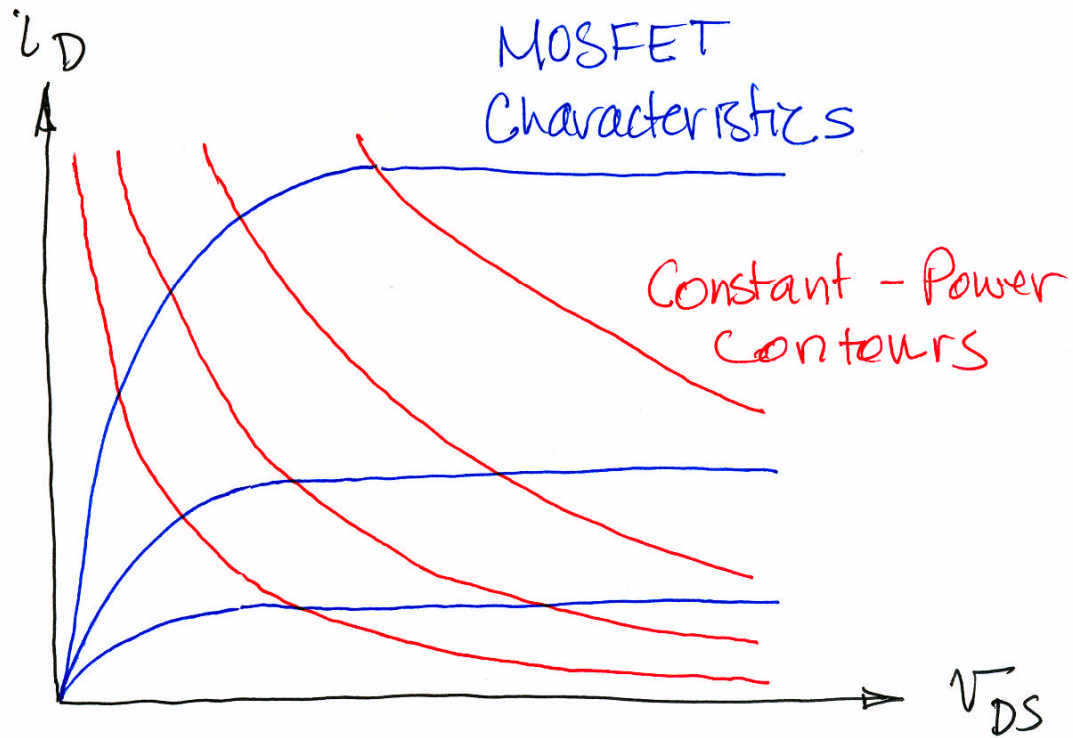

- Transistors are lossy valves.
- Loss $\Rightarrow$ lost energy $\Rightarrow$ lost fuel \$.
- Loss $\Rightarrow$ heat $\Rightarrow$ heat management \$.
- Least loss occurs during cut off ($i_D = 0$) and deep within the triode region ($V_{DS} \approx 0$).

Power Electronics


- Power electronics are not necessarily "powerful" electronics.
- Power electronics denotes a design paradigm targeting circuits that process energy with very high efficiency.

Transistors/Diodes $\Rightarrow$ Ideal switches:
either on or off.

Capacitors/Inductors $\Rightarrow$ Used for energy
Storage and filtering.

Resistors $\Rightarrow$ No first-order use.

Solar - Powered Motor Drive

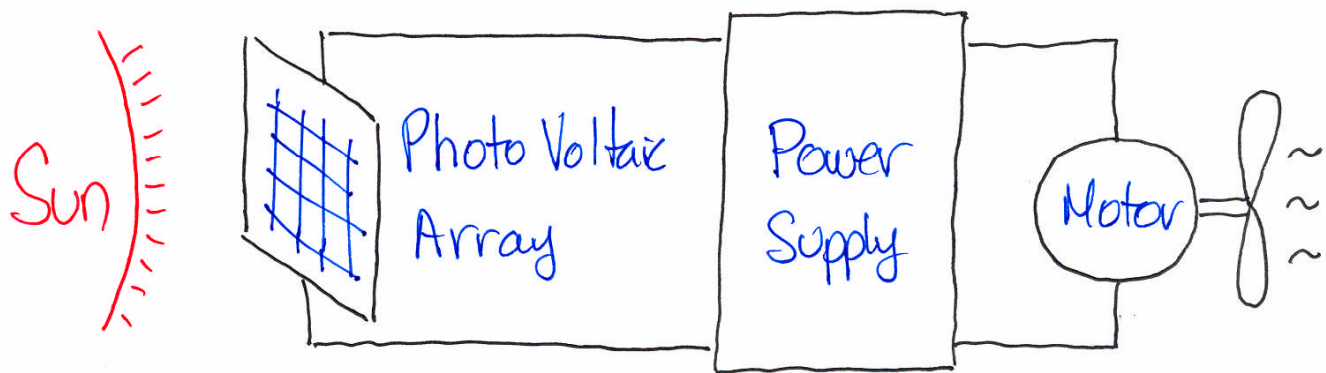

Energy
Source



Energy
Conversion

Energy
Processor


Working
Load

Demo Solar PVA $\Rightarrow 9\text{ V}$ at maximum power
 Demo Motor $\Rightarrow 27\text{ V}$ at the same power } $\left. \begin{array}{l} 3:1 \text{ Voltage} \\ \text{boost desired} \end{array} \right\}$


PVA

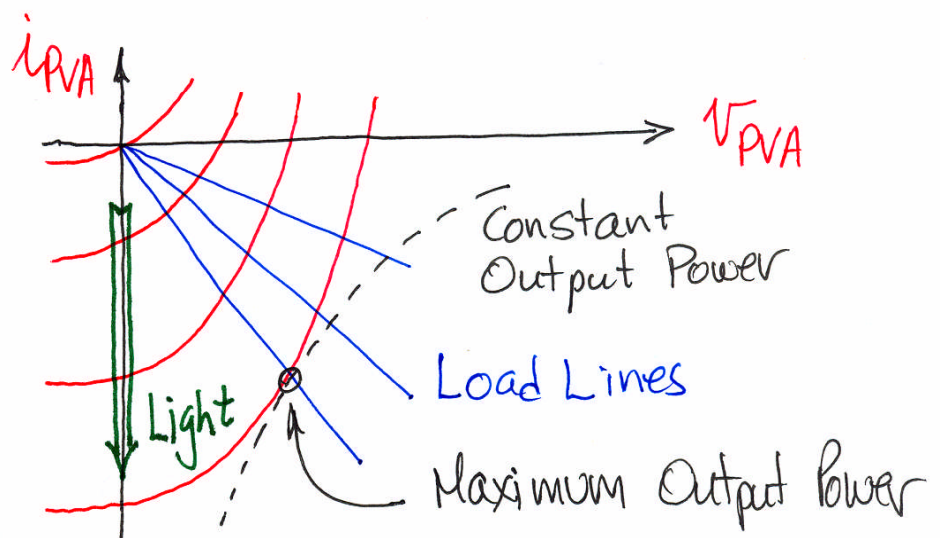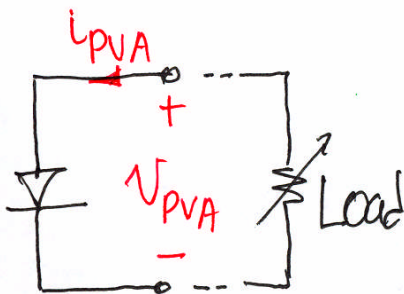


Boost Converter

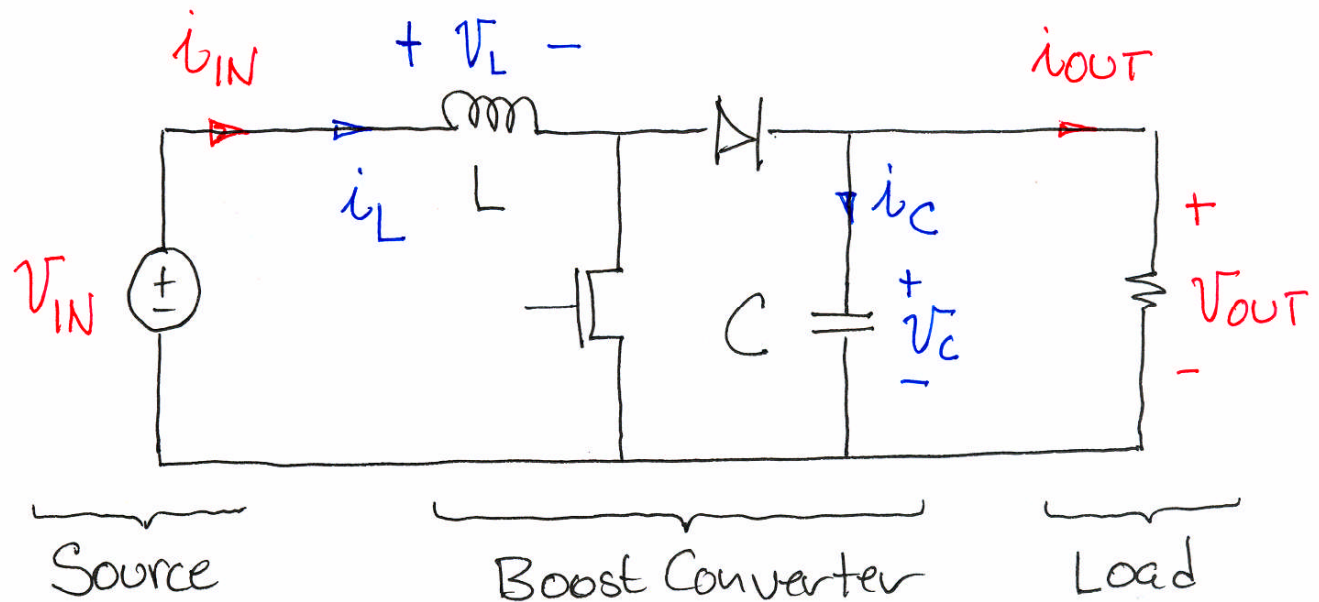

MOSFET On
Diode Off

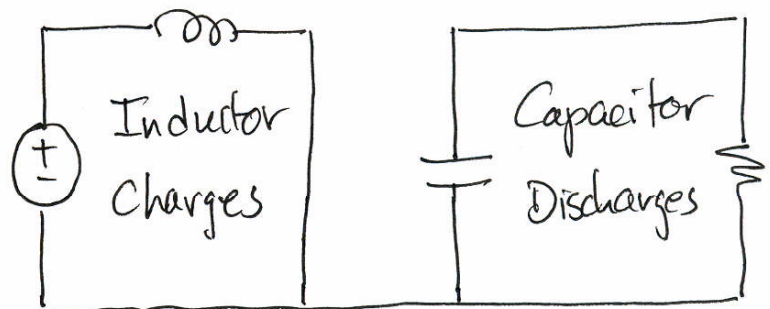

MOSFET Off
Diode On

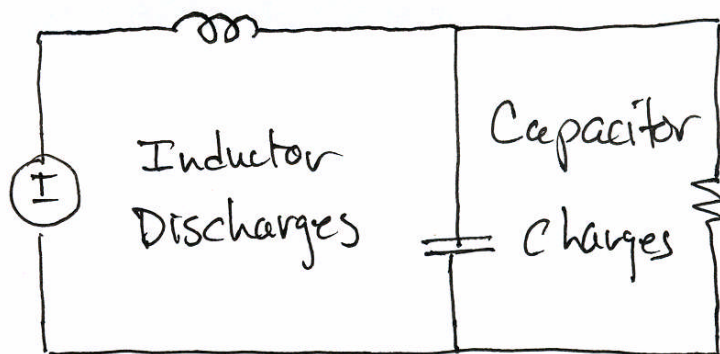


Waveforms I

$D \equiv$ Duty Cycle (MOSFET On)

$T \equiv$ Switching Period

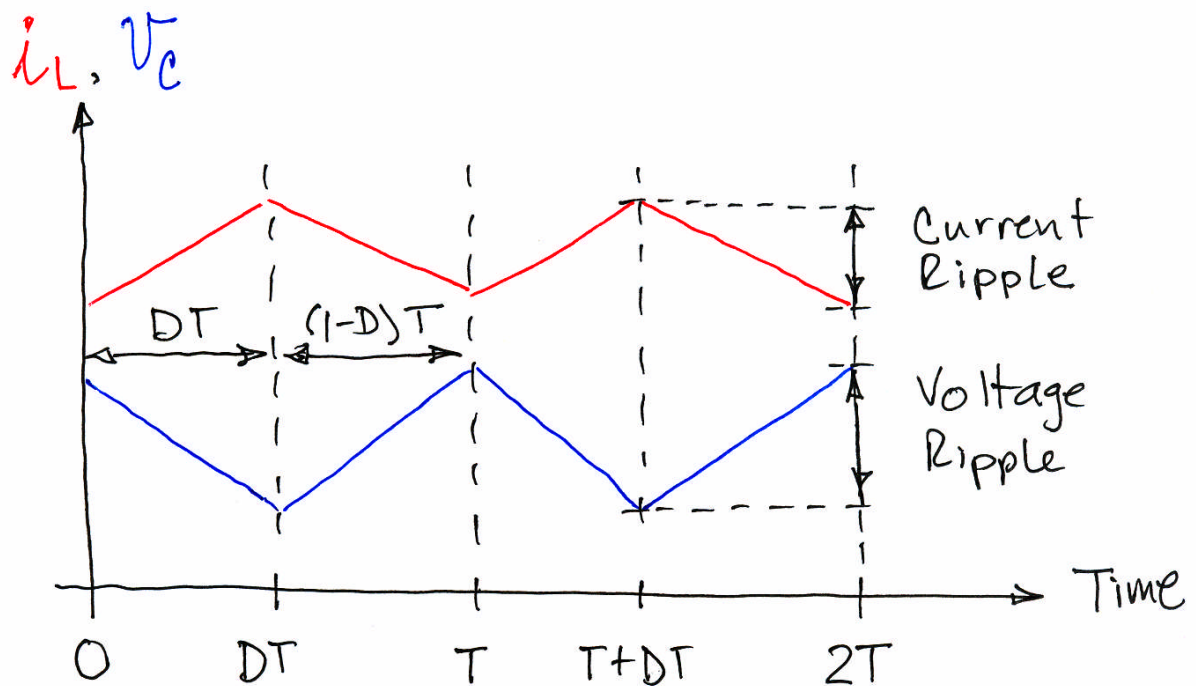$\frac{1}{T} \equiv$ Switching Frequency (1 kHz ... 100 kHz)



High $1/T \Rightarrow$ Smaller ripple, smaller
L & C, larger switching losses.

Waveforms II

Ignore ripple and focus on averages.

$$\text{Inductor: } \int_0^T v_L dt = \int_0^T L \frac{di_L}{dt} dt = L (i_L(t) - i_L(0)) = 0$$

Cyclic $\downarrow$

$$\Rightarrow D V_{IN} + (1-D)(V_{IN} - V_{OUT}) = 0 \Rightarrow V_{OUT} = \frac{V_{IN}}{1-D}$$

$$\text{Capacitor: } \int_0^T i_C dt = \int_0^T C \frac{dV_C}{dt} dt = C (V_C(t) - V_C(0)) = 0$$

Cyclic $\downarrow$

$$\Rightarrow -D i_{OUT} + (1-D)(i_{IN} - i_{OUT}) = 0 \Rightarrow i_{OUT} = (1-D) i_{IN}$$

$$\text{Energy Conservation: } V_{OUT} i_{OUT} = V_{IN} i_{IN}$$

In theory, no losses; same behavior as an ideal transformer.

Waveforms III

V_{out} Ripple: $i_{out} \approx C \frac{\Delta V_{out}}{DT}$... MOSFET On

$$\Delta V_{out} \approx \frac{DT}{C} i_{out}$$

Use small T and large C
for small voltage ripple.


i_{in} Ripple: $V_{in} \approx L \frac{\Delta i_{in}}{DT}$... MOSFET On

$$\Delta i_{in} \approx \frac{DT}{L} V_{in}$$


Use small T and Large L
for small current ripple.

More Examples

Buck Converter

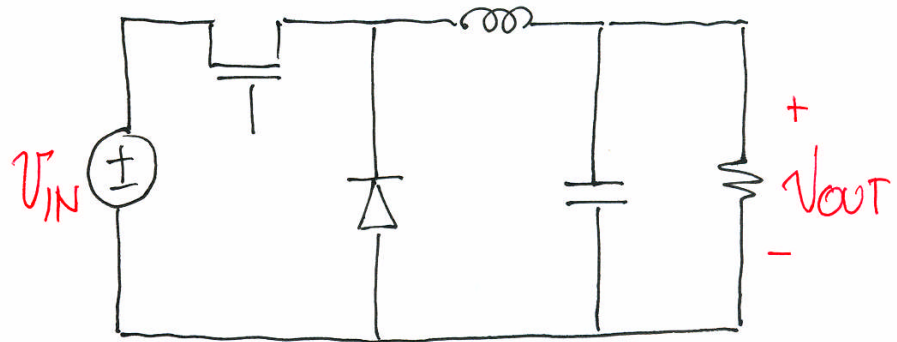

Buck/Boost Converter

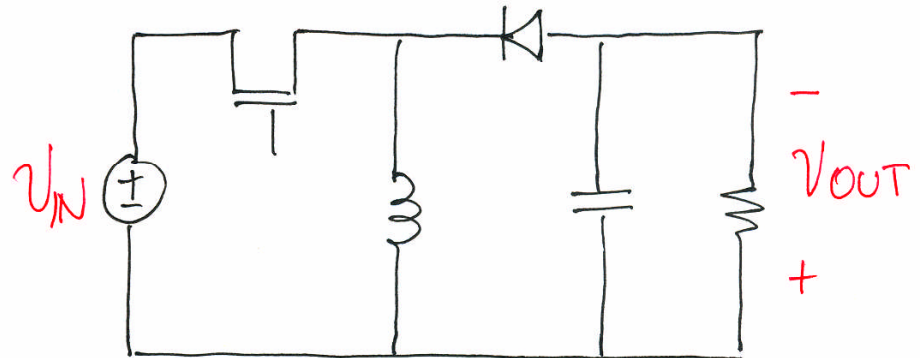

Current Chopper

