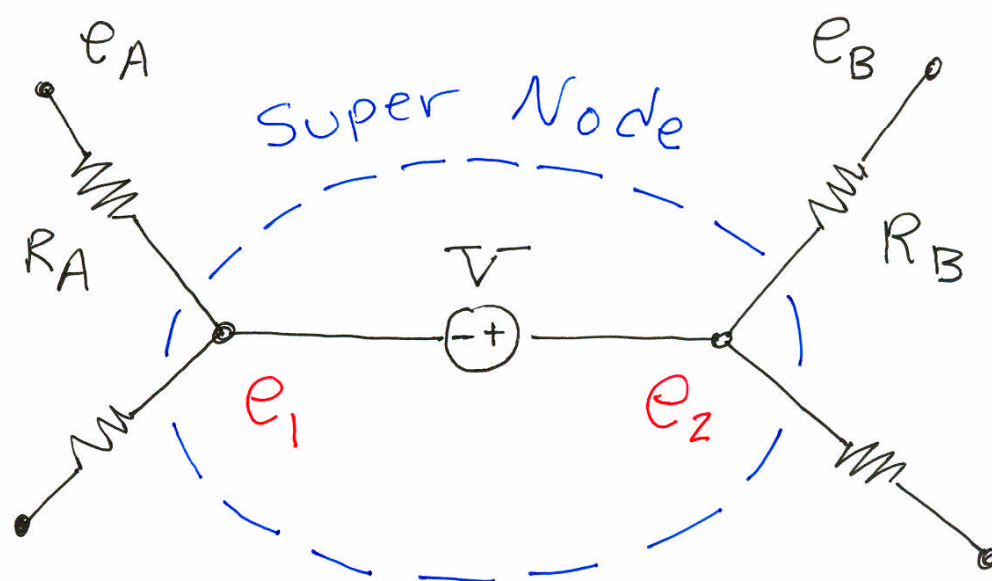


G.002 - Lecture 3

Circuit Analysis Simplifications

- Superposition
- Thevenin & Norton Equivalence

Node Analysis & Floating Voltage Sources




$$e_2 = e_1 + V$$

Write only one KCL for each super node.

$$\frac{e_1 - e_A}{R_A} + \frac{\overbrace{e_1 + V}^{e_2} - e_B}{R_B} + \dots = 0$$

Simple Analysis Example

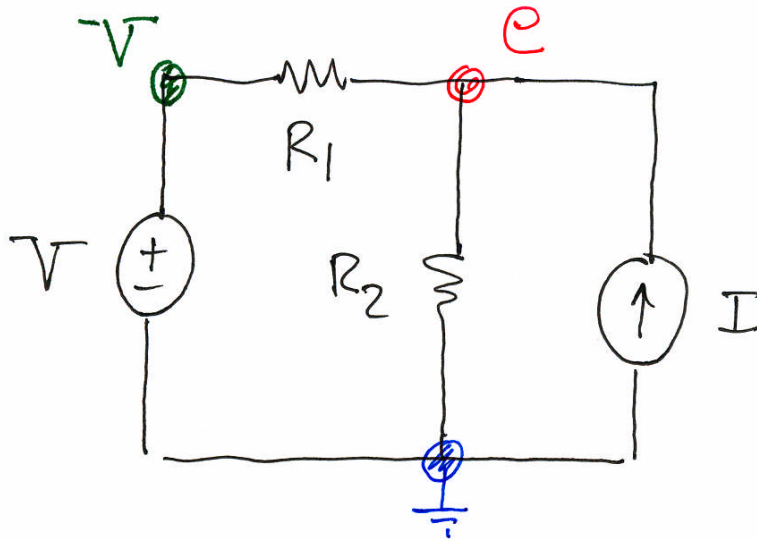

Linear in $\bar{e}$ and $\bar{I}$.

$$\frac{e - V}{R_1} + \frac{e}{R_2} - I = 0$$

$$e \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V}{R_1} + I$$

$$e = \frac{R_2}{R_1 + R_2} V + \frac{R_1 R_2}{R_1 + R_2} I$$

Conductance
Matrix



$$G \bar{e} = H \bar{I}$$



Node
Voltage
Vector

Coefficient
Matrix



Source
Vector

Linearity $\Rightarrow$ Homogeneity & Superposition

Homogeneity: If $\bar{X} \rightarrow \boxed{\text{Linear System}} \rightarrow \bar{Y}$

Then $\alpha \bar{X} \rightarrow \boxed{\text{Linear System}} \rightarrow \alpha \bar{Y}$

Superposition: If $\bar{X}_1 \rightarrow \boxed{\text{Linear System}} \rightarrow \bar{Y}_1$


$\bar{X}_2 \rightarrow \boxed{\text{Linear System}} \rightarrow \bar{Y}_2$

Then $\bar{X}_1 + \bar{X}_2 \rightarrow \boxed{\text{Linear System}} \rightarrow \bar{Y}_1 + \bar{Y}_2$

Divide & Conquer


Use superposition to analyze a linear circuit one source at a time. (All sources except one are set to zero each time.)

How to set a source to zero?

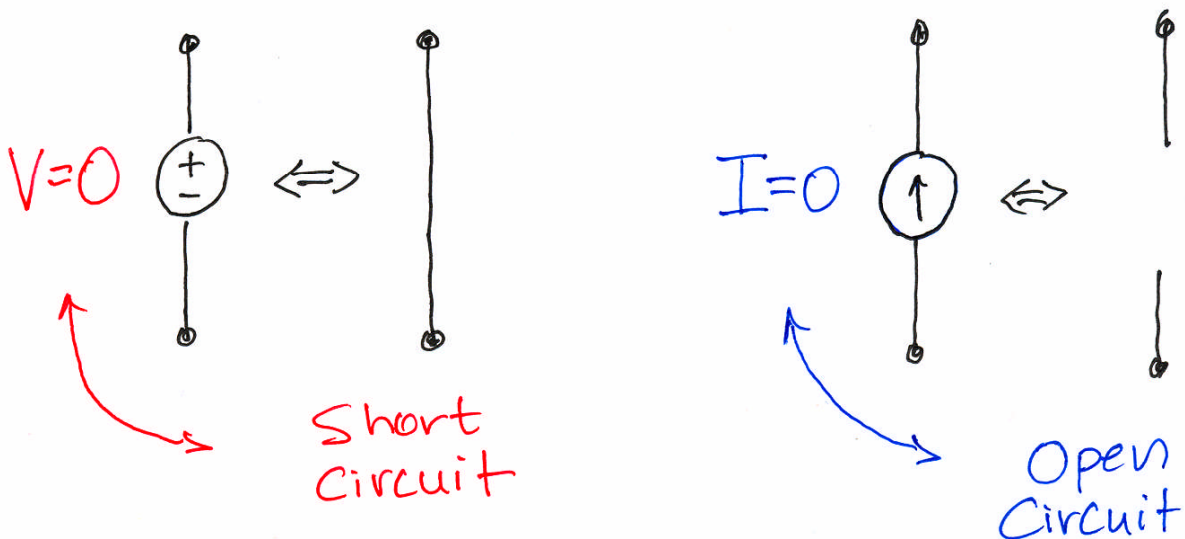

Linear Networks & Systems

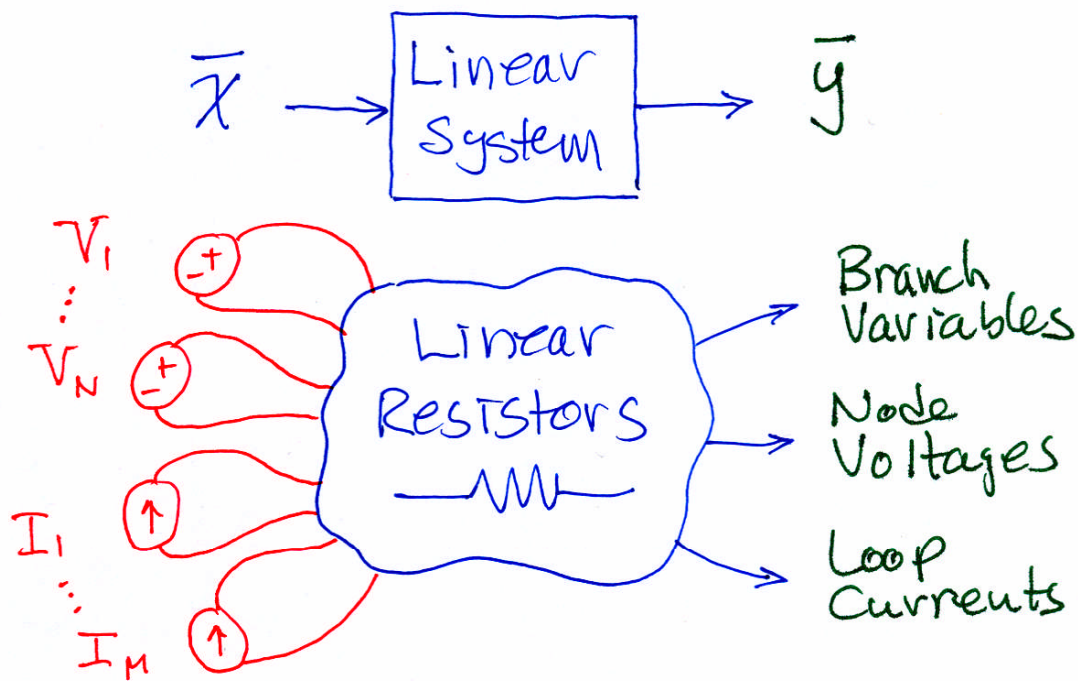
Linear system $\Rightarrow$ all stimuli are external inputs. For example, $y = x_1 + x_2$ is linear from $\bar{x} \rightarrow y$, but $y = x_1 + x_2 + 1$ is not.



No source should be left within the network for the purposes of superposition. Superposition is carried out over all sources.

No Superposition For Power

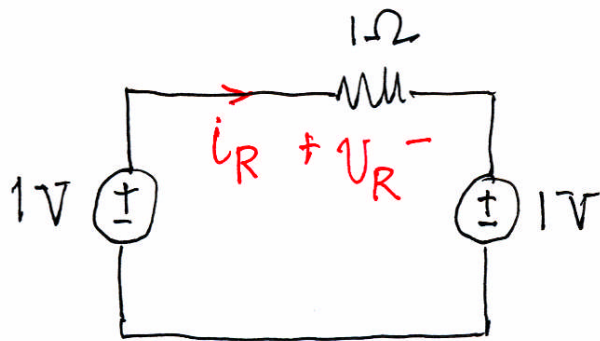
Power is a **nonlinear** network property, and so the superposition of power is not possible.



$$v_R = 0 \text{ V}$$

$$i_R = 0 \text{ A}$$


$$v_R i_R = 0 \text{ W}$$

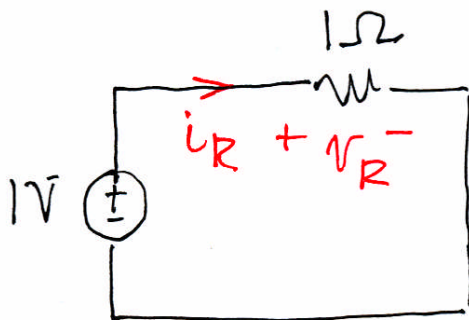

$$v_R = 1 \text{ V}$$

$$i_R = 1 \text{ A}$$

$$v_R i_R = 1 \text{ W}$$


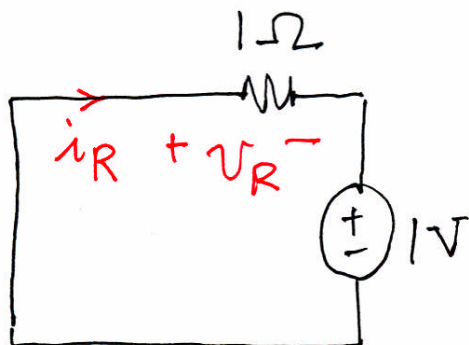


$$v_R = -1 \text{ V}$$

$$i_R = -1 \text{ A}$$


$$v_R i_R = 1 \text{ W}$$

Superposition Examples

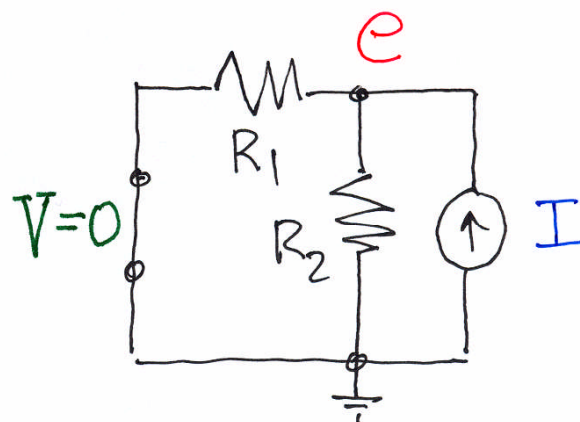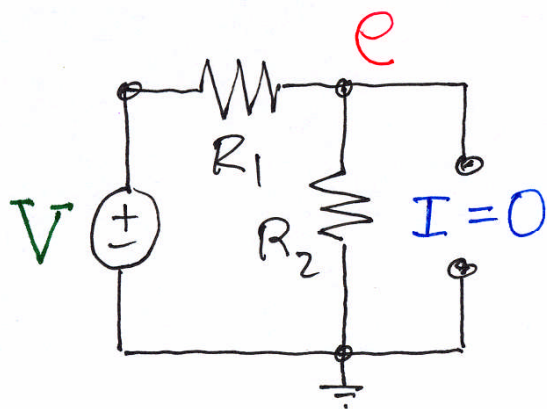


$$e = \frac{R_2}{R_1 + R_2} V$$


$$e = \frac{R_1 R_2}{R_1 + R_2} I$$

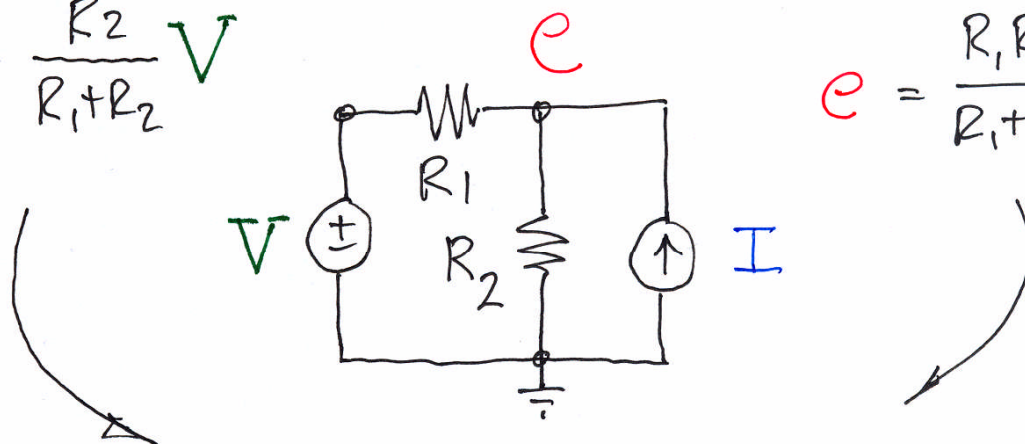
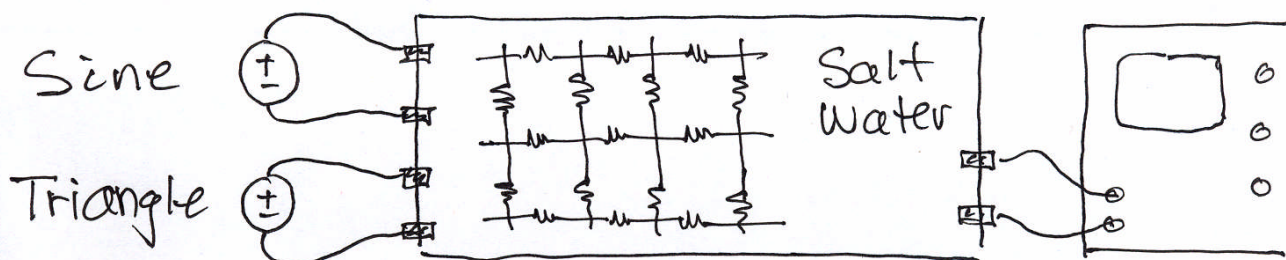
$$e = \frac{R_2}{R_1 + R_2} V + \frac{R_1 R_2}{R_1 + R_2} I$$




Thevenin & Norton Equivalence

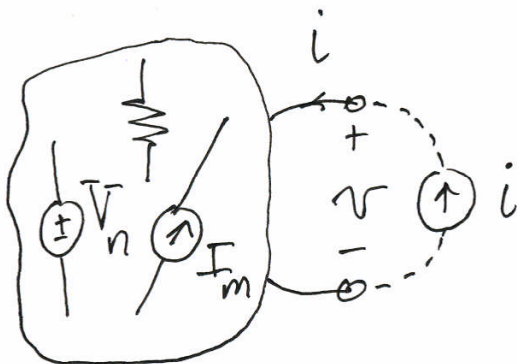

Linear
Network

$$v = \sum_n \alpha_n V_n + \sum_m \beta_m I_m + R_{TH} i$$

Superposition

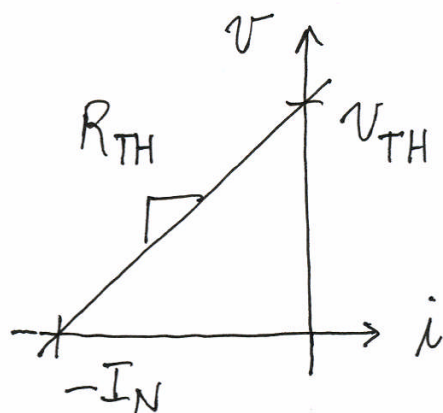


Open
Circuit
($i=0$)


$$\Rightarrow V_{TH} = \sum_n \alpha_n V_n + \sum_m \beta_m I_m$$

Short
Circuit
($v=0$)

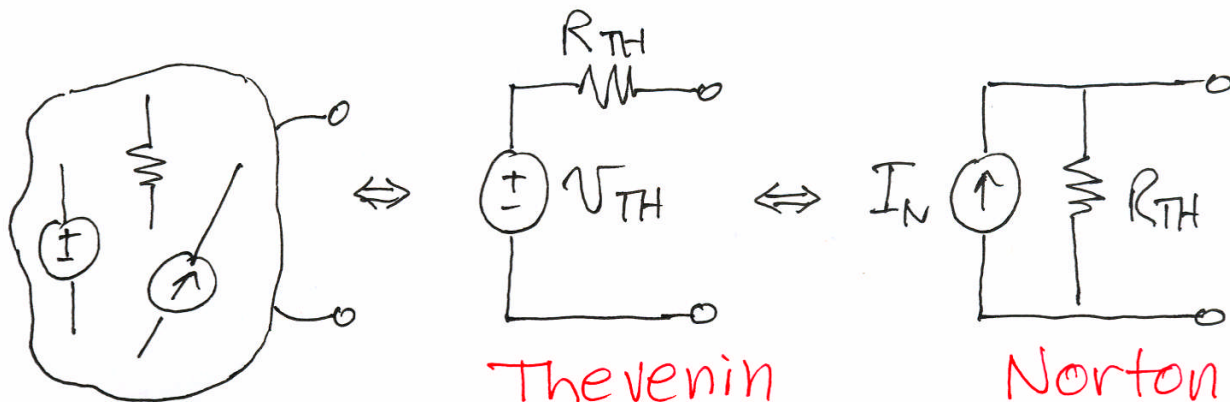
$$\Rightarrow I_N = \frac{V_{TH}}{R_{TH}}$$





THEVENIN / NORTON EXAMPLE

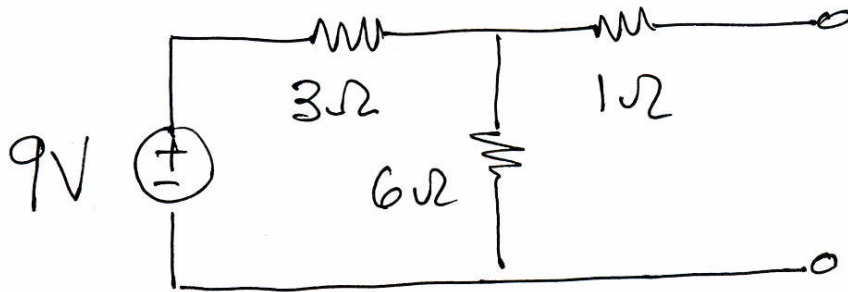

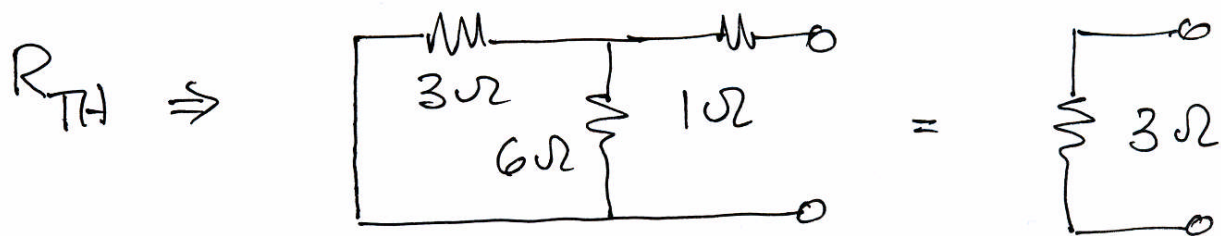Open-circuit voltage = 6 V via
voltage divider $\Rightarrow V_{TH} = 6 V$



$$I_N = V_{TH} / R_{TH} = 2 A$$

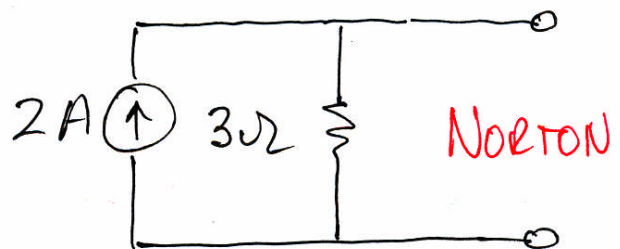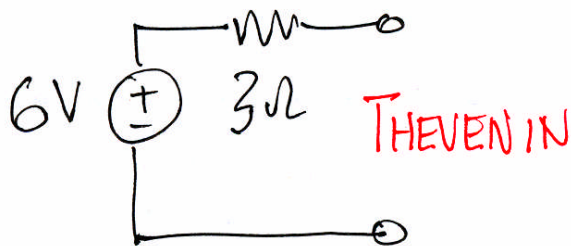

3 - Lecture Summary

- Two-terminal devices : V, I, R
- KCL and KVL
- Brute-force analysis
- Node analysis
- Parallel and series reductions
- Voltage and current dividers
- Superposition
- Thevenin and Norton equivalence