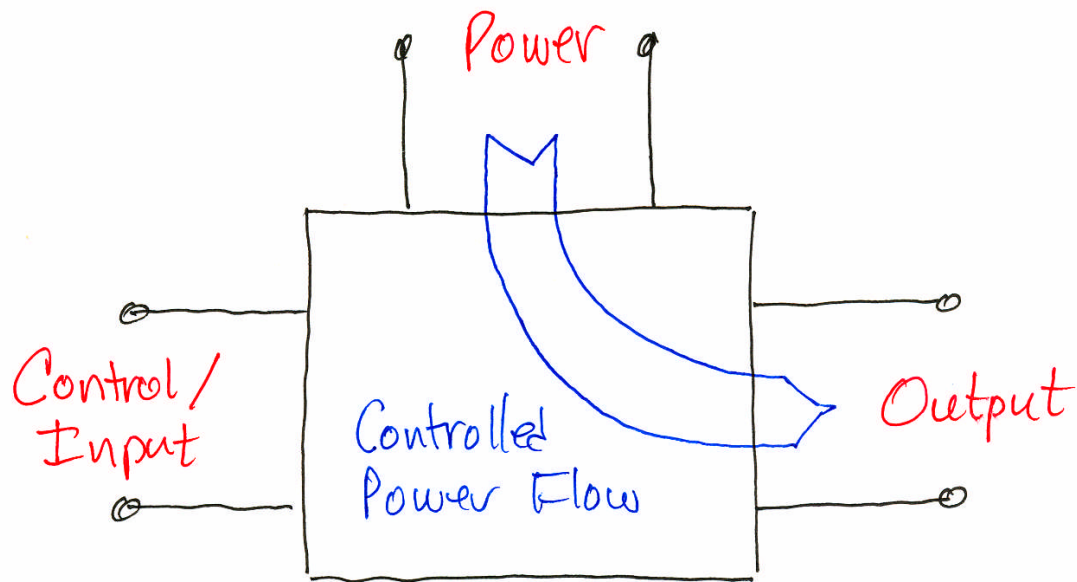


6.002 - Lecture 6

Amplifiers

- Amplifiers
- Review Of Digital Inverter
- Review Of MOSFET Characteristics
- Dependent Sources
- Amplifier Implementation

Amplifiers



- An amplifier is a three-port device.
- Ubiquitous use to improve signal strength, improve signal-to-noise ratio, and provide power gain.
- Examples found in electronics, mechanics, pneumatics, hydraulics, economics, society ...

Some Amplifier Properties

Gain: Voltage, Current, Power

Equivalence: Input, Output

Bandwidth



Noise

Stability

Dissipation

Load Dependence


NMOS Inverter

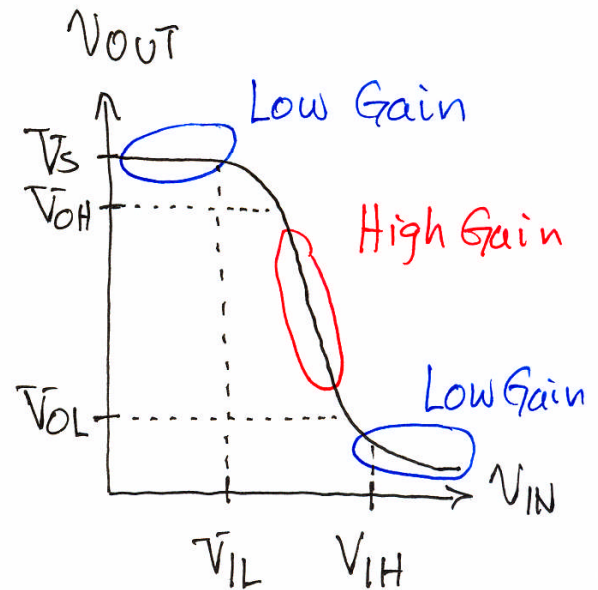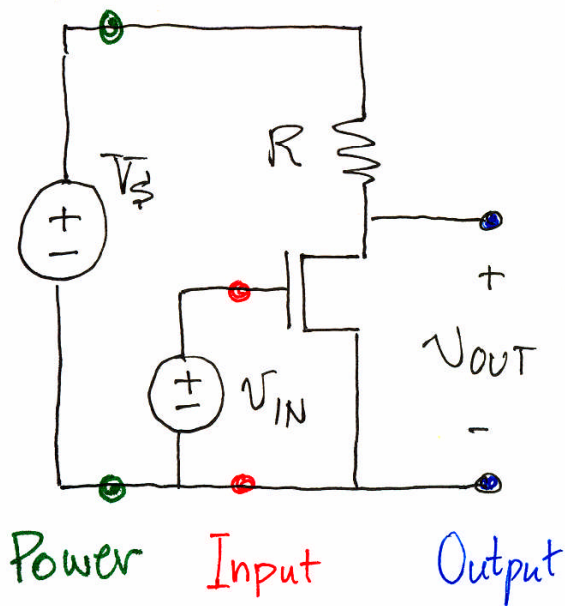

Low Gain $\Rightarrow$ Output is insensitive to input. Perfect for digital logic operation.

High Gain $\Rightarrow$ Output is very sensitive to input. Perfect for amplification.

MOSFET Characteristics

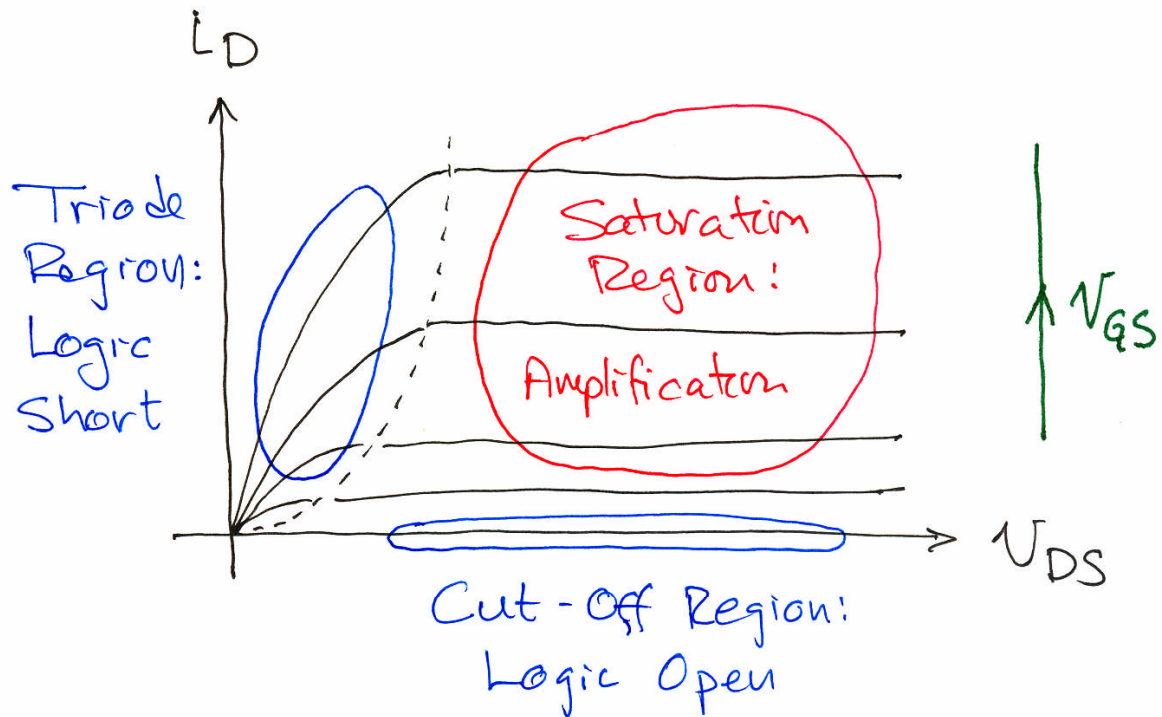


Saturation Region: I_D depends (to first order) only on V_{GS} , and not on V_{DS} ! Model this region with a voltage-dependent current source.

Independent & Dependent Sources


Independent Sources (ϕ) are external inputs and are independent of all other signals.

Dependent Sources ($\diamond$) are internal sources having values that depend on other internal branch variables.


Dependent
Voltage Source

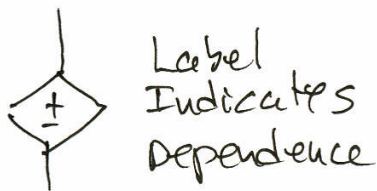


Dependent
Current Source

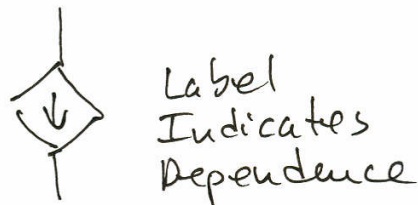

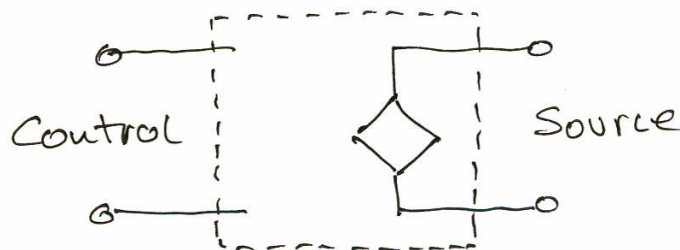Dependent sources are at least two-port devices, and are three-port devices if they can source power.



Network Example (Node Method)

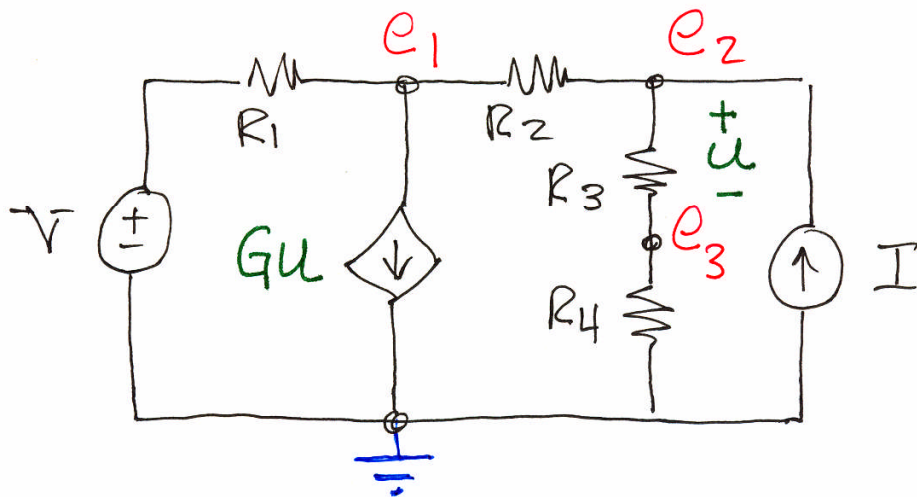

Node 1: $G_1(e_1 - V) + G(e_2 - e_3) + G_2(e_1 - e_2) = 0$

Node 2: $G_2(e_2 - e_1) + G_3(e_2 - e_3) - I = 0$


Node 3: $G_3(e_3 - e_2) + G_4(e_3) = 0$

$$\begin{bmatrix} G_1 + G_2 & G - G_2 & -G \\ -G_2 & G_2 + G_3 & -G_3 \\ 0 & -G_3 & G_3 + G_4 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} = \begin{bmatrix} G_1 & 0 \\ 0 & 1 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} V \\ I \end{bmatrix}$$


- Dependent source properties appear in coefficient matrices.
- The network remains linear if the dependent sources are linear.

Superposition

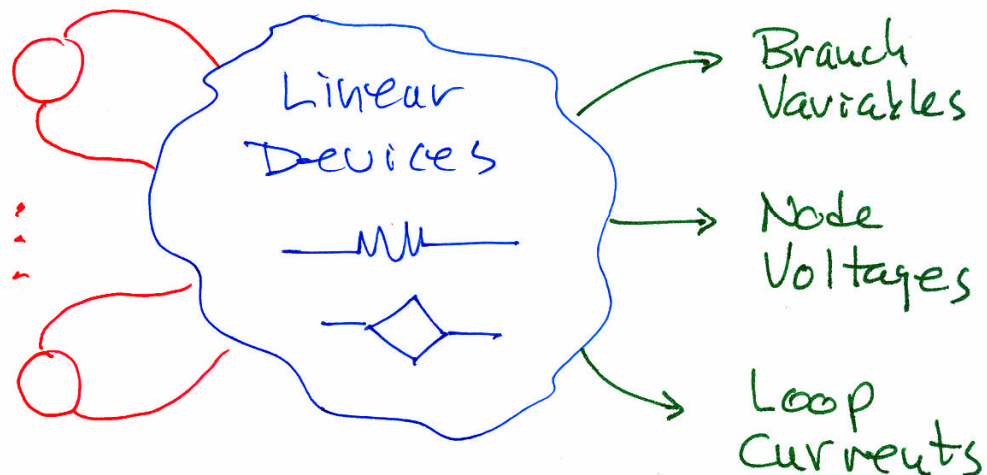Dependent sources are part of the network/system, not part of the independent inputs. Carry out superposition only over the independent sources.




Thevenin & Norton Equivalence

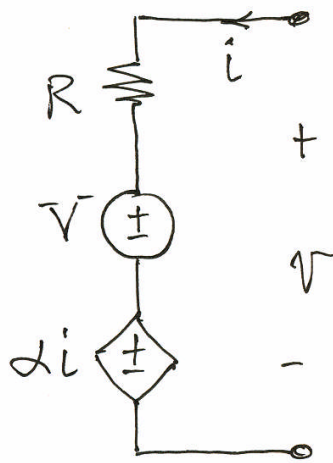


$$v = \alpha i + V + Ri$$

$$= V + (\alpha + R)i$$

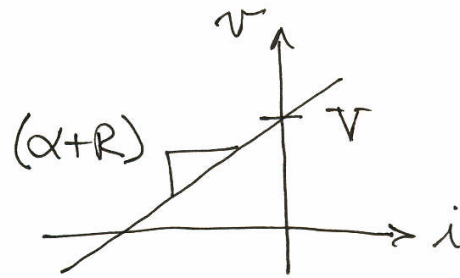


The dependent source is acting like a

resistor:

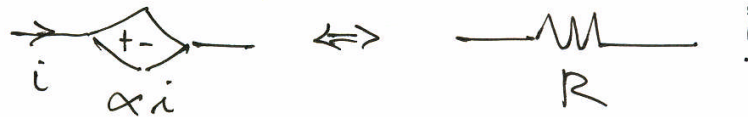


- Independent sources can only bias the $i-v$ relation at a port.
- Dependent sources can also change the slope of the $i-v$ relation.
- Dependent sources are part of the network, and so must be part of a Thevenin resistance calculation.

Amplifier Implementation

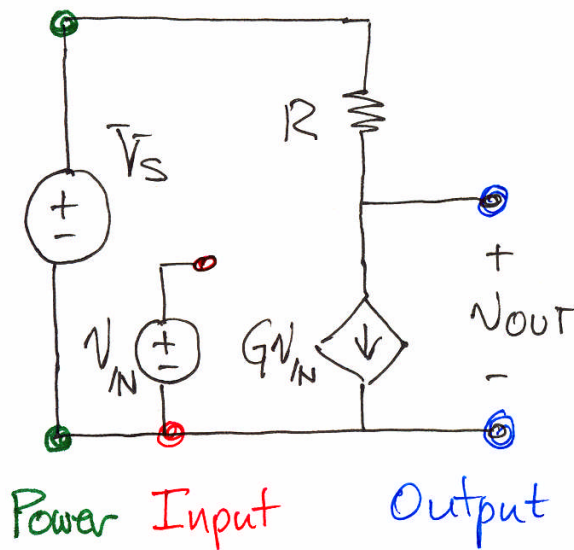


$$\frac{V_{OUT} - \bar{V}_S}{R} + G V_{IN} = 0$$

$$V_{OUT} = \bar{V}_S - R G V_{IN}$$

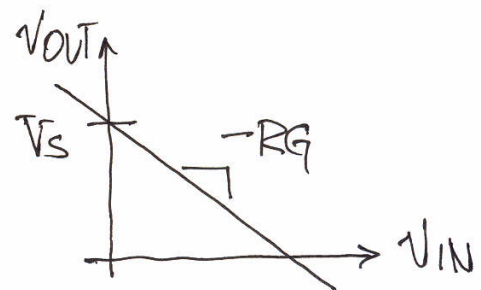

Thevenin Equivalent:

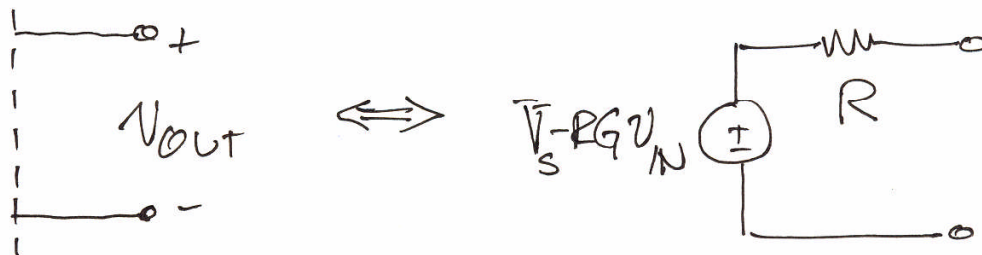


Dependent Source Power


$$\text{Voltage} = V_S - R_G V_{IN}$$

$$\text{Current} = G V_{IN}$$
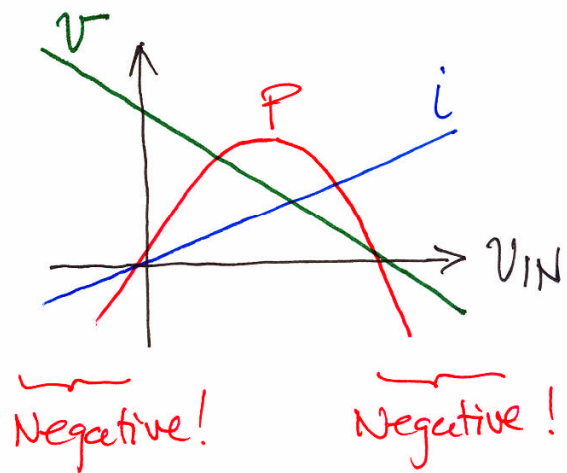
$$\text{Power In} = \text{Voltage} \cdot \text{Current}$$



Dependent Source $\Rightarrow$

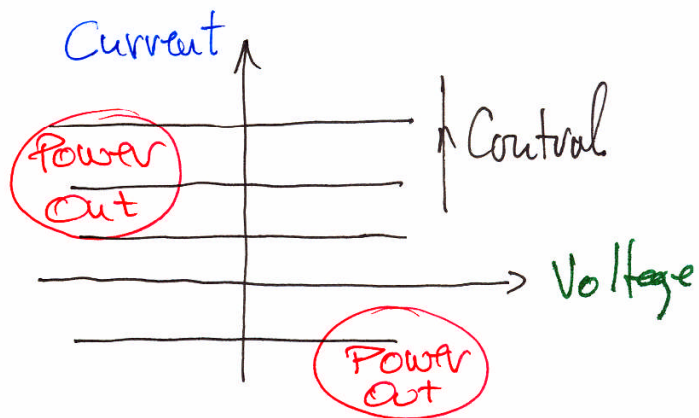

MOSFET:

