
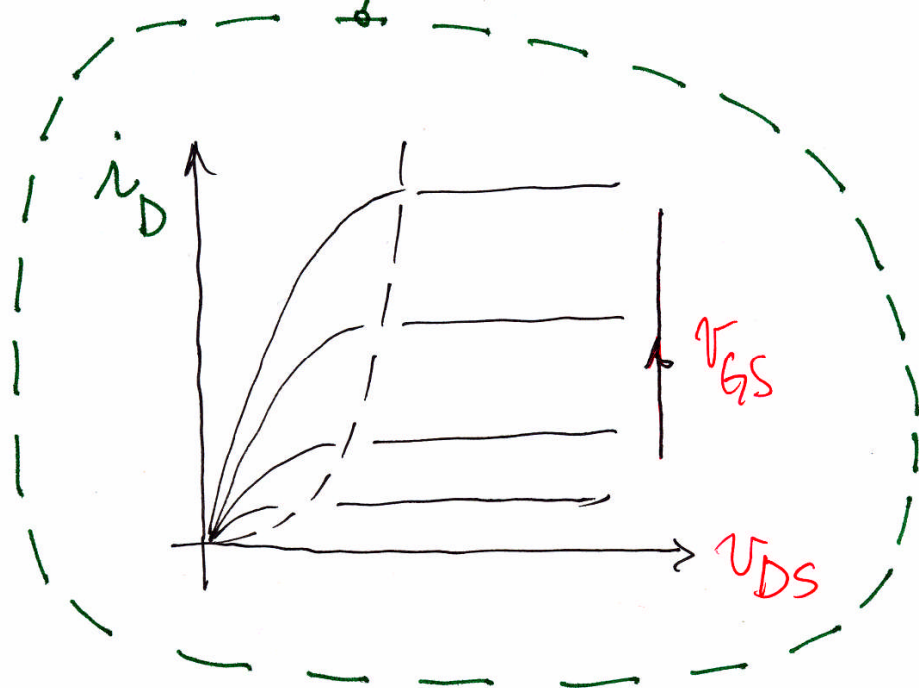


6.002 - Lecture 7

MOSFET Amplifiers

- Graphical Analysis
- MOSFET Details
- Closed-Form Analysis

MOSFET Amplifier

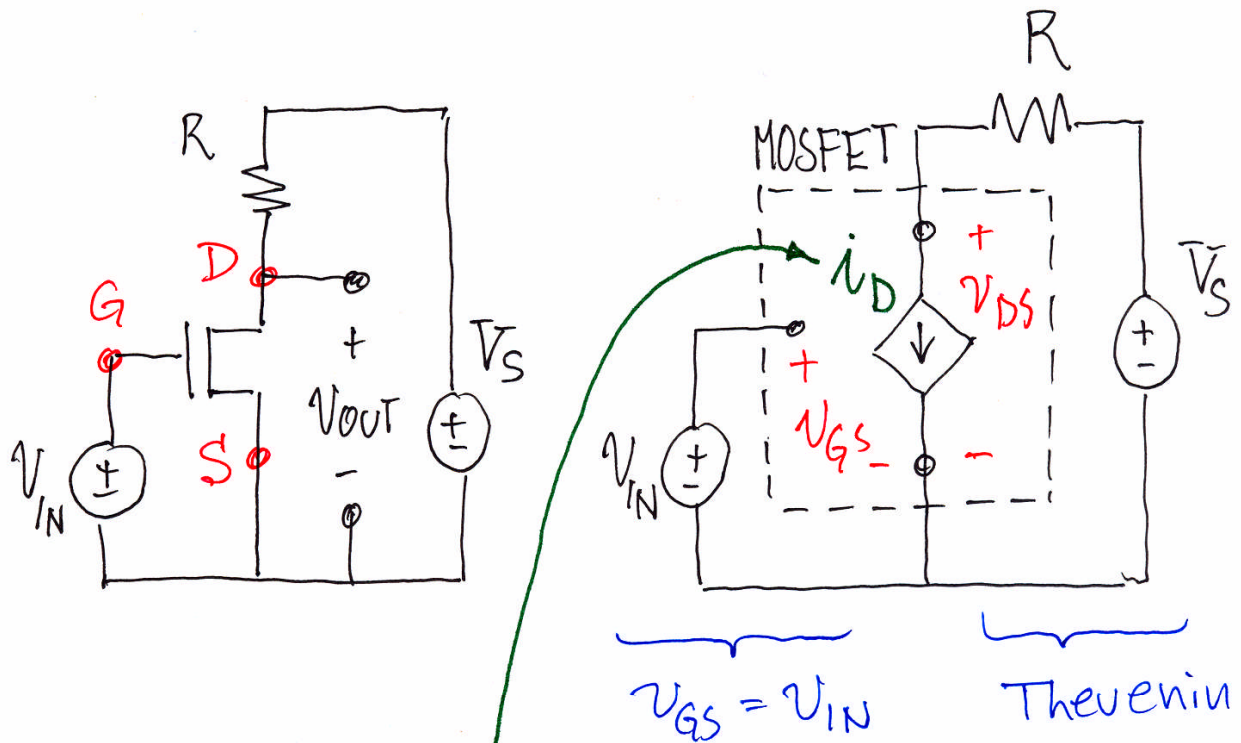



Graphical Analysis I

Thevenin:



$$V_S = V_{DS} + R i_D$$

MOSFET:


$$i_D(V_{DS}, V_{GS} = V_{IN})$$

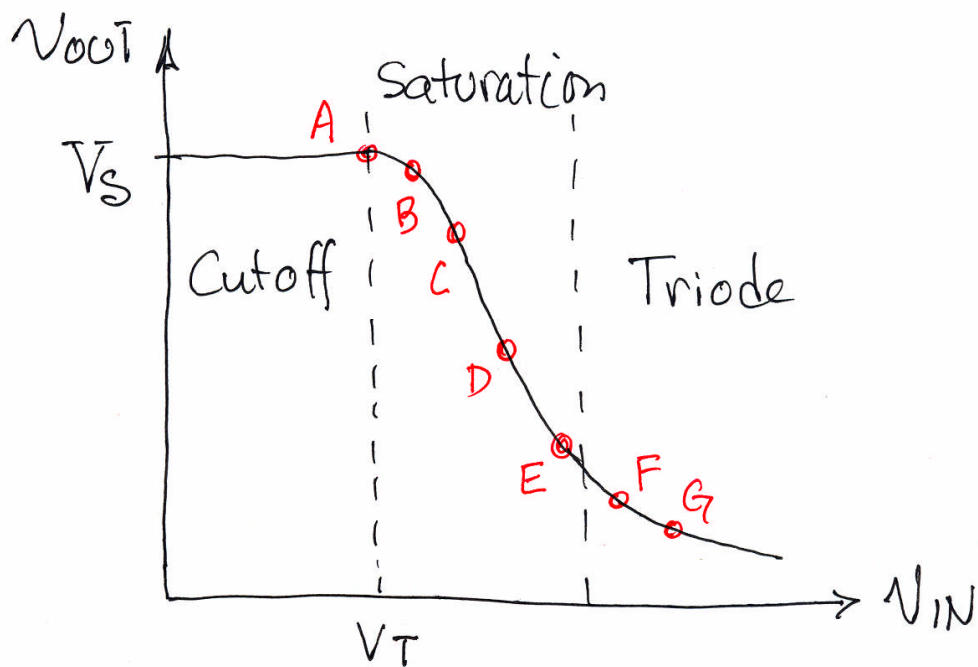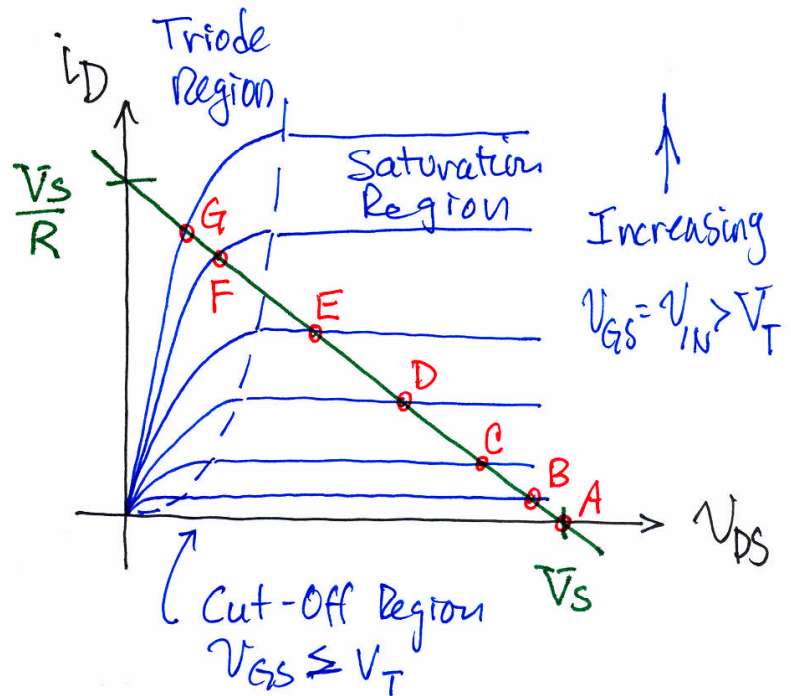

Graphical Analysis II

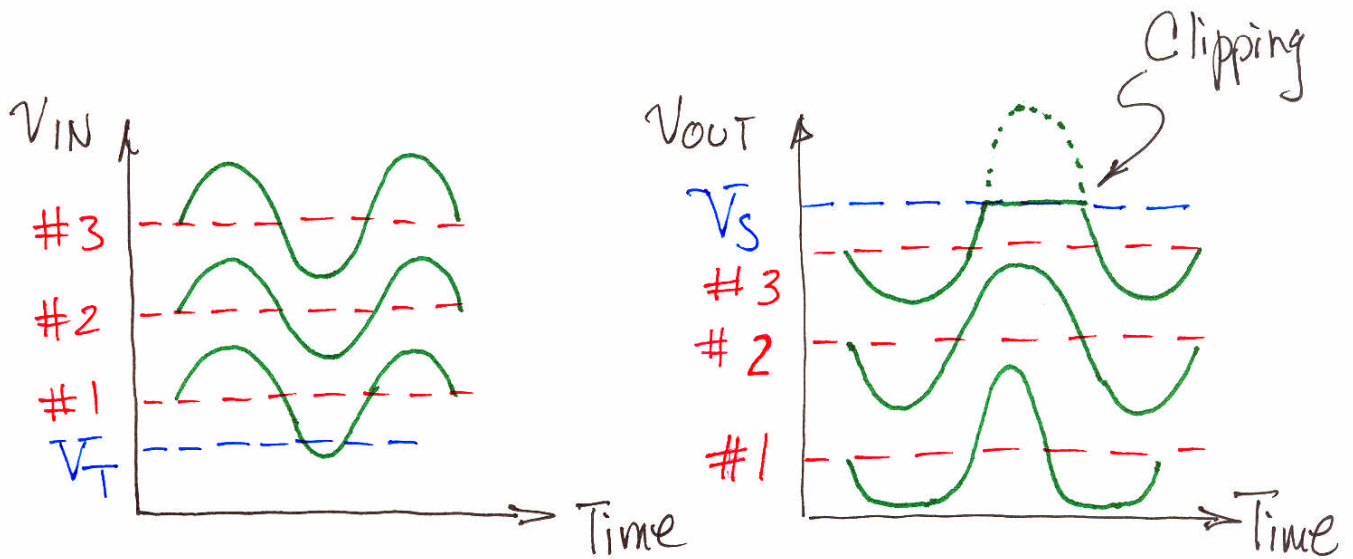
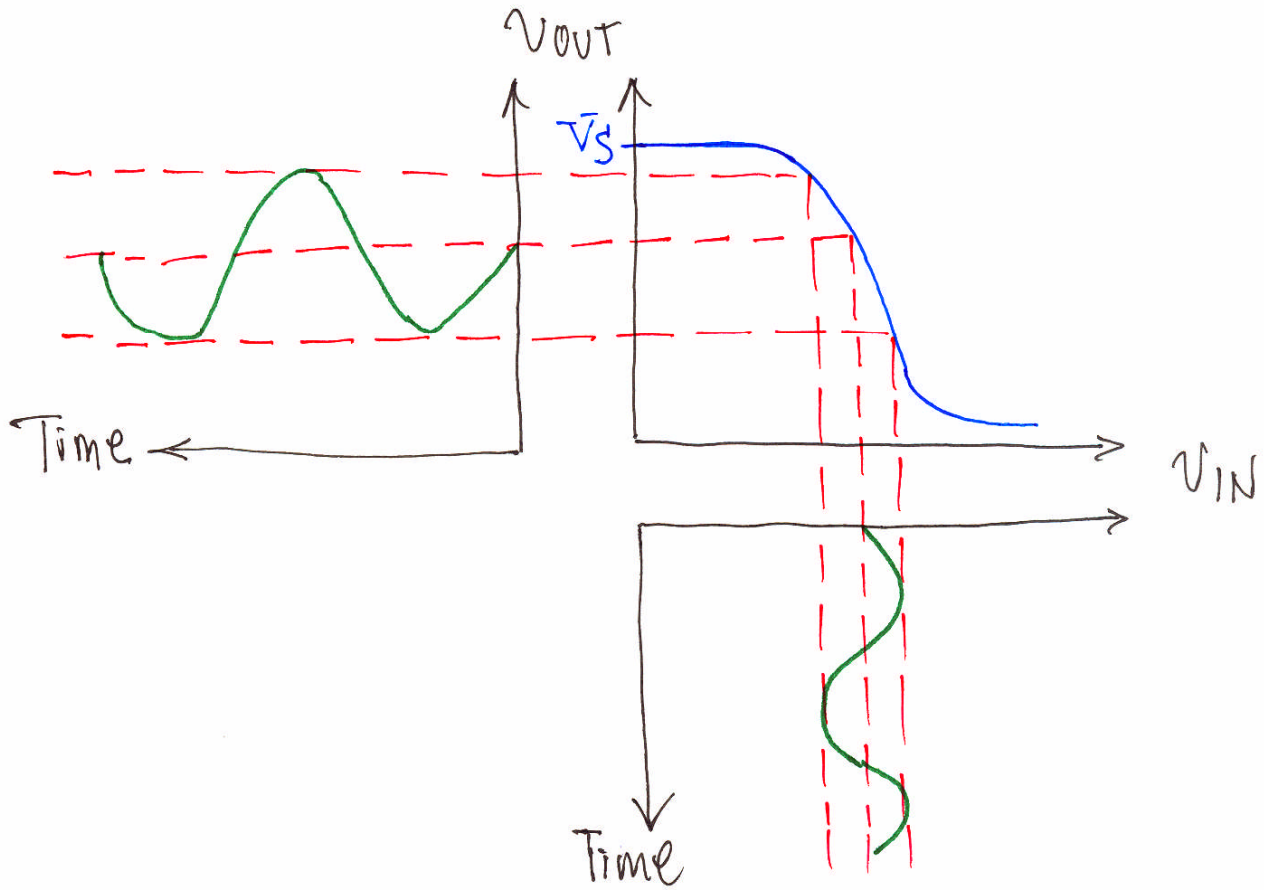


MOSFET Details

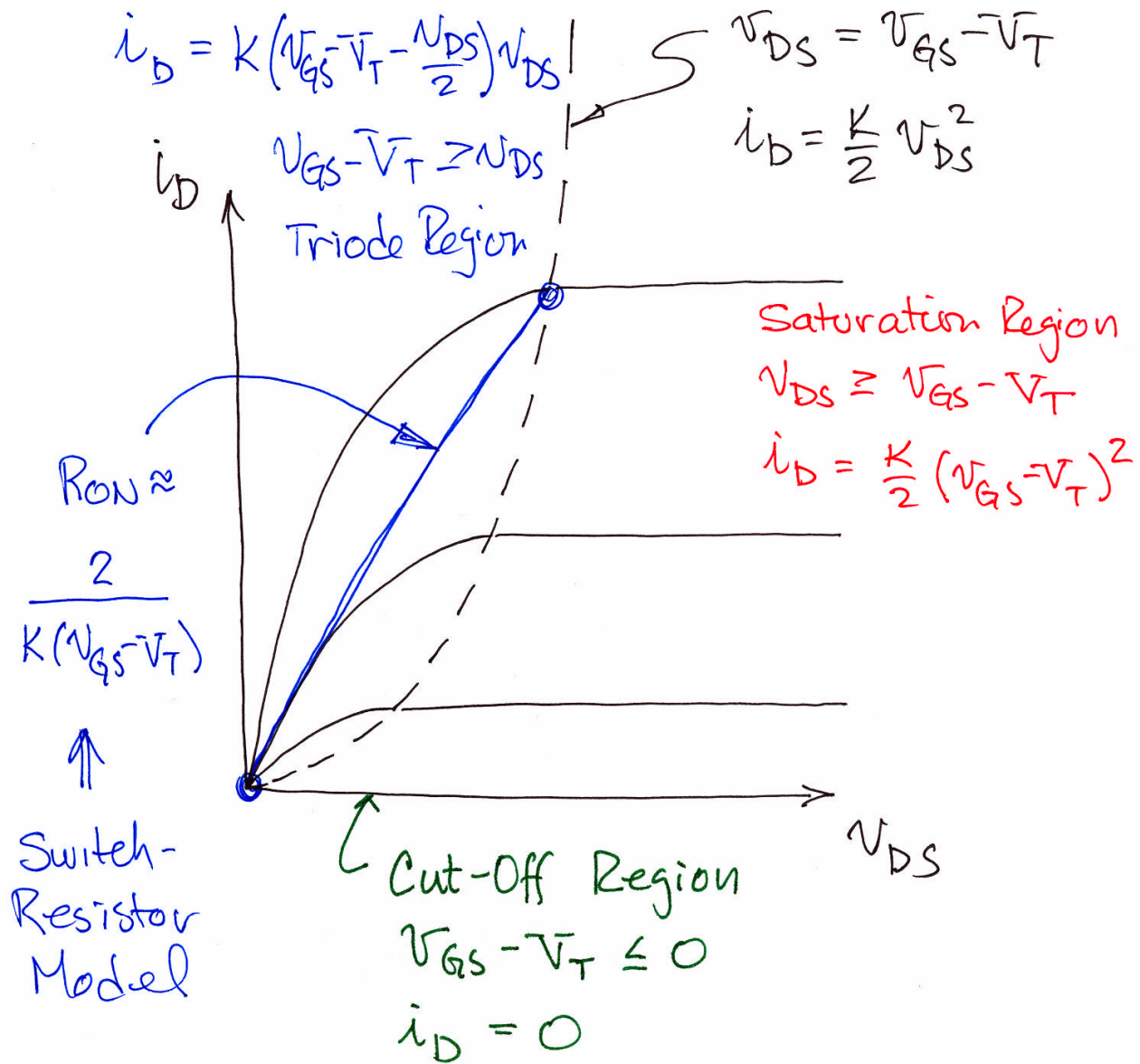


Also, $i_G \equiv 0$!

MOSFET Summary

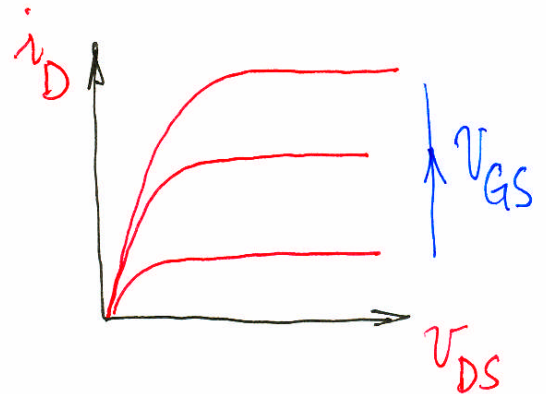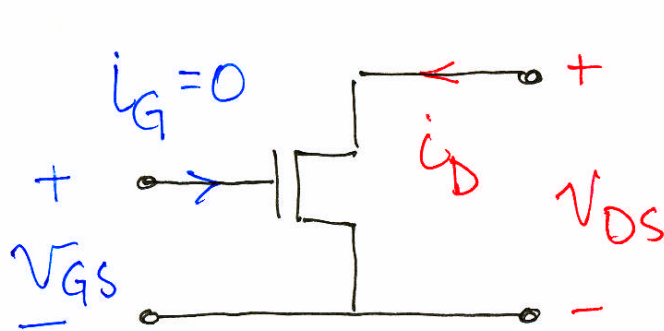


Cut-off

$$V_{GS} - V_T \leq 0$$

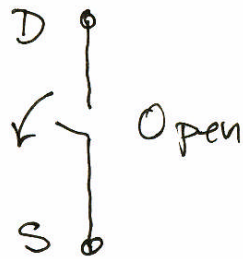


Saturation

$$0 \leq V_{GS} - V_T \leq V_{DS}$$

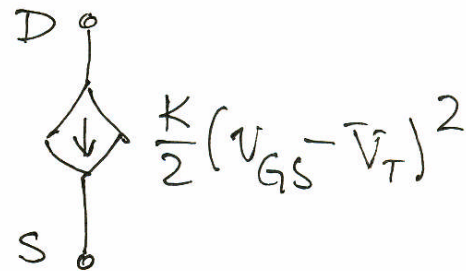


Triode (Amp)

$$V_{DS} \leq V_{GS} - V_T$$

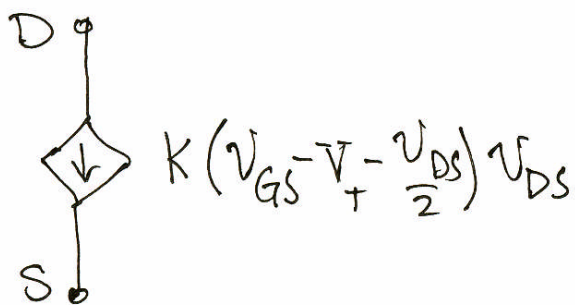


Triode (Logic)

$$V_{DS} \leq V_{GS} - V_T$$

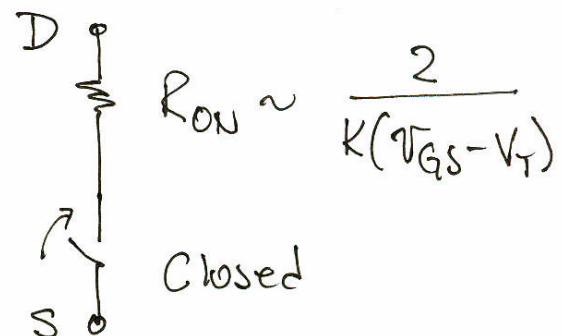

iLab MOSFET Data

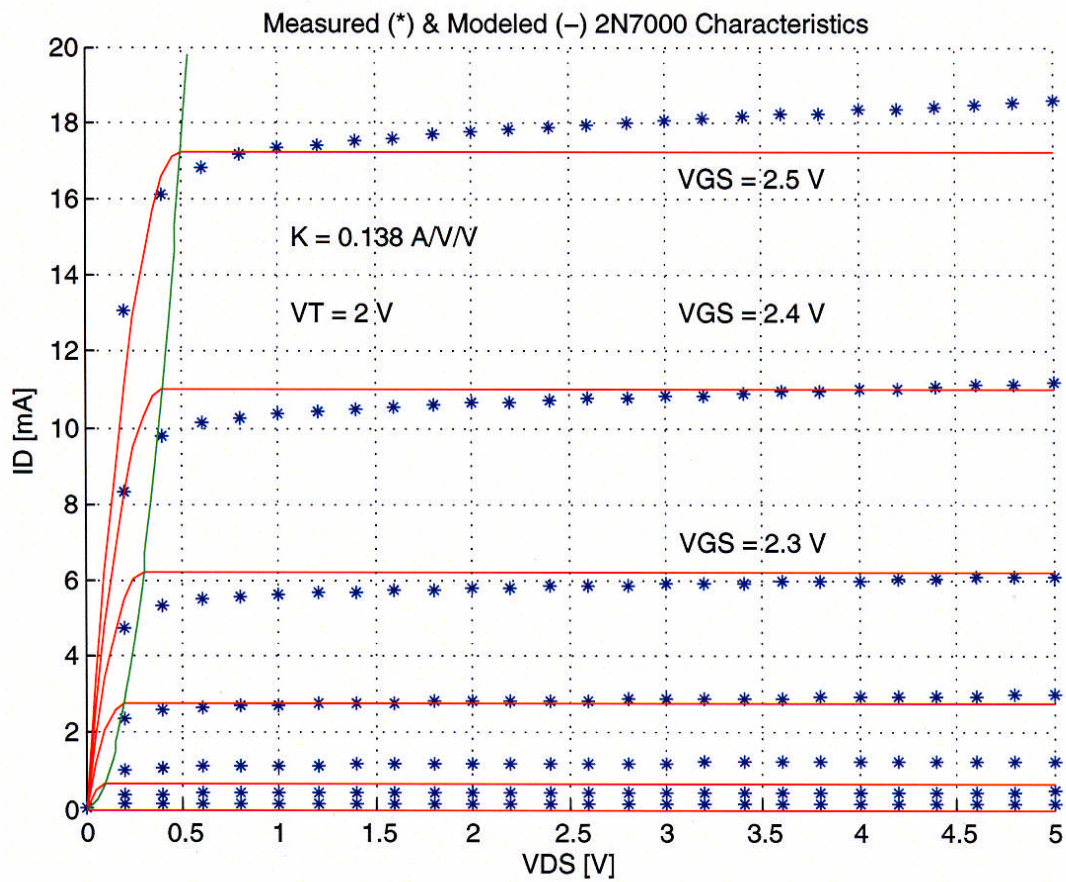


Graphical Analysis III

Cut-Off
Region

$$V_{GS} - V_T \leq 0$$


$$\uparrow V_{IN}$$

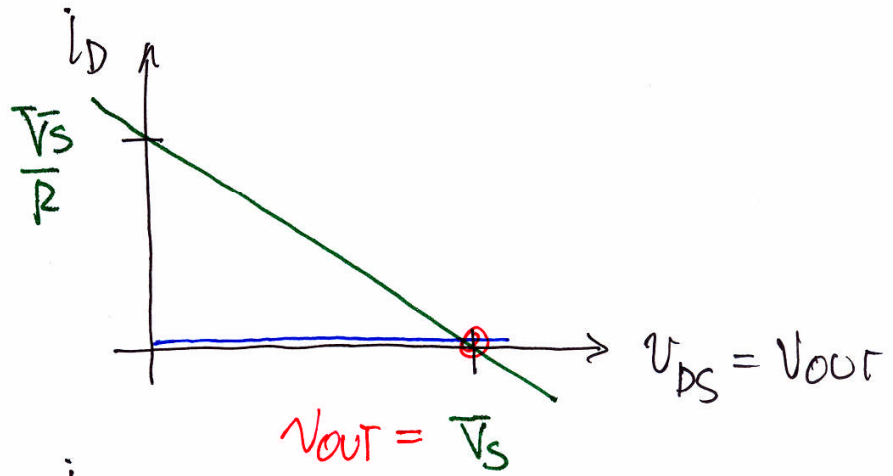

Saturation
Region

$$0 \leq V_{GS} - V_T \leq v_{DS}$$


$$\uparrow V_{IN}$$

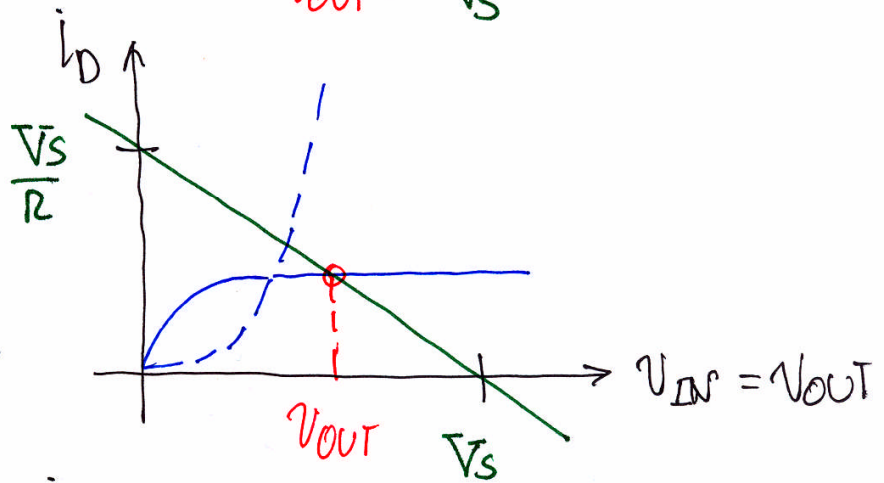


Triode
Region

$$v_{DS} \leq V_{GS} - V_T$$

$$\uparrow V_{IN}$$

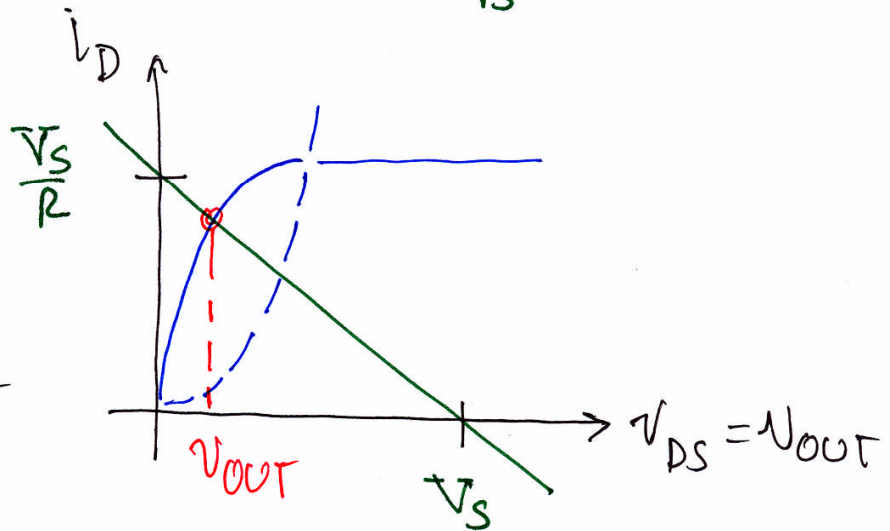

Saturation Region:

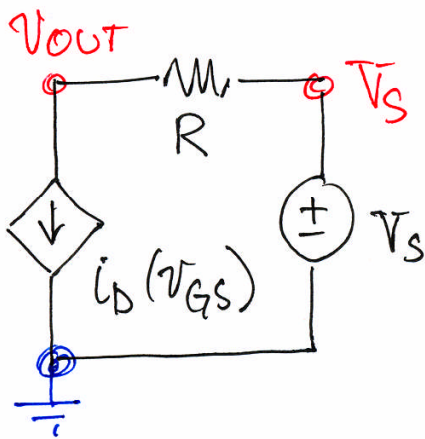

$$i_D = \frac{K}{2} (v_{GS} - V_T)^2$$

$$\frac{v_{OUT} - V_S}{R} + \frac{K}{2} (v_{IN} - V_T)^2 = 0$$

$$v_{OUT} = V_S - \frac{RK}{2} (v_{IN} - V_T)^2$$

Boundaries:

$$v_{DS} \geq v_{GS} - V_T \geq 0$$

$$v_{OUT} \geq v_{IN} - V_T \geq 0$$

Triode Cut-off

$$\frac{\sqrt{2RK\bar{V}_S + 1} - 1}{RK} \geq v_{IN} - \bar{V}_T \geq 0$$

$$\frac{\sqrt{2RK\bar{V}_S + 1} - 1}{RK} \leq v_{OUT} \leq \bar{V}_S$$

Triode/Saturation
Boundary $\Rightarrow$

$$v_{OUT} = v_{IN} - V_T$$

$$v_{OUT} = \bar{V}_S - \frac{RK}{2} v_{OUT}^2$$

$$v_{OUT} = \frac{\sqrt{2RK\bar{V}_S + 1} - 1}{RK}$$

Closed-Form Analysis

