

6.002 - Lecture 9

Small-Signal Models

- Small-Signal Analysis Problem
- Small-Signal Model Solution
- Small-Signal MOSFET Model
- S-S MOSFET Amplifier Model


The Problem

- Small-signal analysis yields valuable insight. But ...
- Small-signal analysis via expansion or differentiation requires a complete closed-form nonlinear analysis.
- The expansion or differentiation can be very complex for a large circuit.
- Numerical analysis is possible but it yields little insight.

The Solution

- Rather than analyze first and then linearize the analysis, **linearize first and then analyze.**
- Remove the biases from the linearization to uncover the **small-signal model.**
- The linearization still requires an operating point, but it can come from a non-linear analysis, a numerical analysis, an approximate analysis, or an experiment.

Mathematical Example

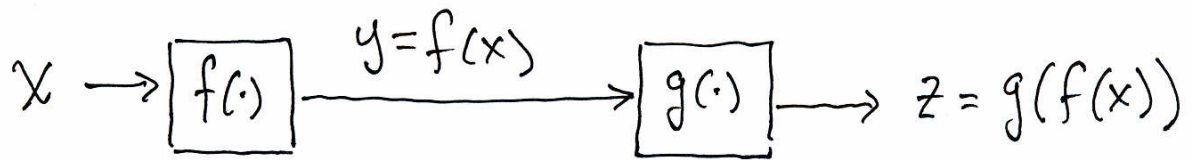

Bias: $Y = f(X)$, $Z = g(Y) = g(f(X))$

Analyze
First:

$$\Delta z = \left. \frac{d}{dx} (g(f(x))) \right|_X \cdot \Delta x$$
$$\approx \left. \frac{dg}{dy} \right|_Y \cdot \left. \frac{dy}{dx} \right|_X \cdot \Delta x$$

$$z \approx Z + \left. \frac{dg}{dy} \right|_Y \cdot \left. \frac{dy}{dx} \right|_X \cdot \Delta x = Z + \Delta z$$





Linearize
First:

$$\Delta y \approx \left. \frac{df}{dx} \right|_X \Delta x \quad , \quad \Delta z = \left. \frac{dg}{dy} \right|_Y \Delta y$$



$$z \approx Z + \Delta z = Z + \left. \frac{dg}{dy} \right|_Y \cdot \left. \frac{df}{dx} \right|_X \Delta x$$

For circuit analysis, f and g represent KCL, KVL and the device laws.


Small-Signal-Model Method

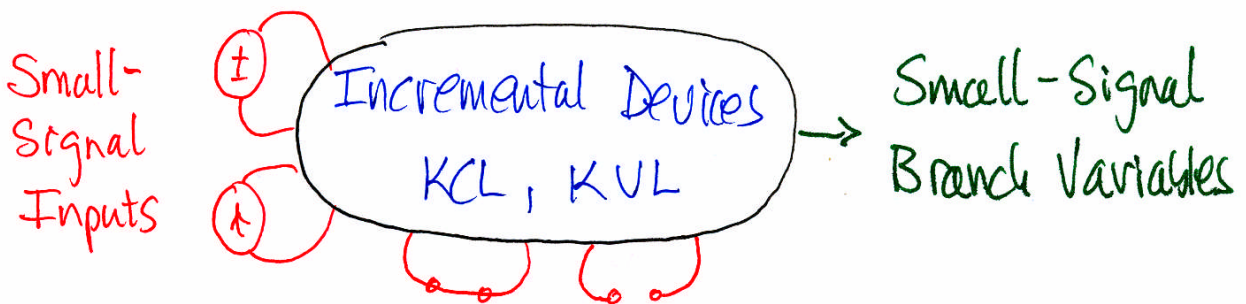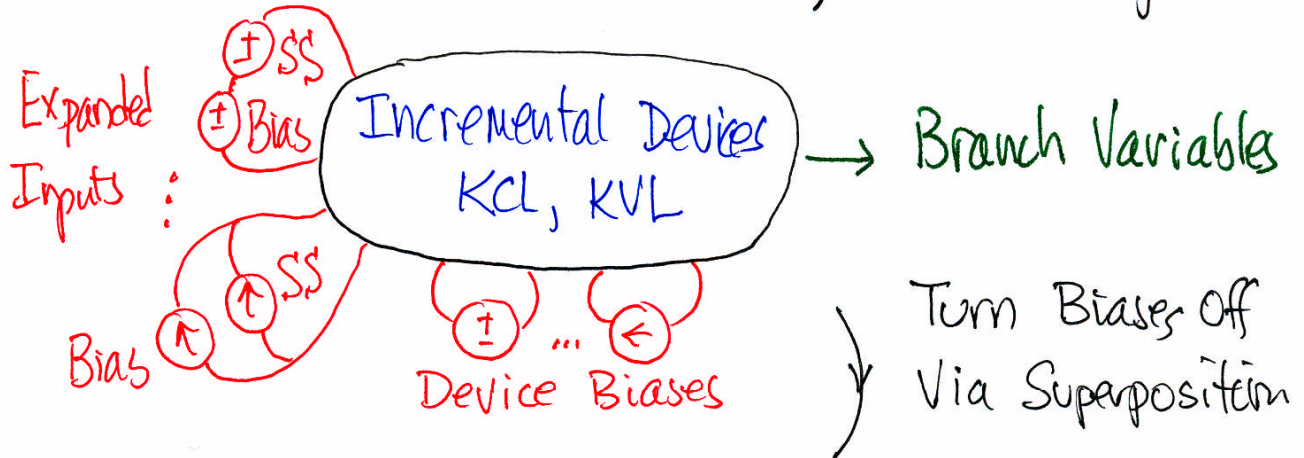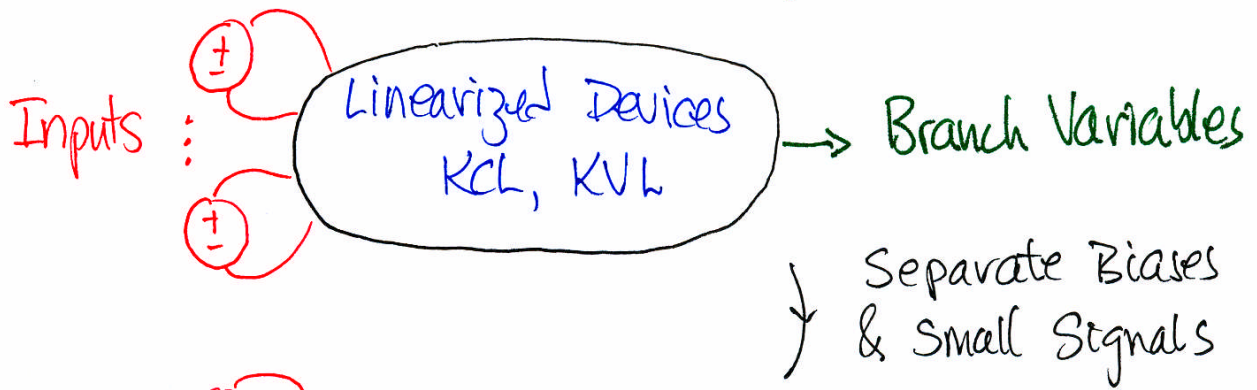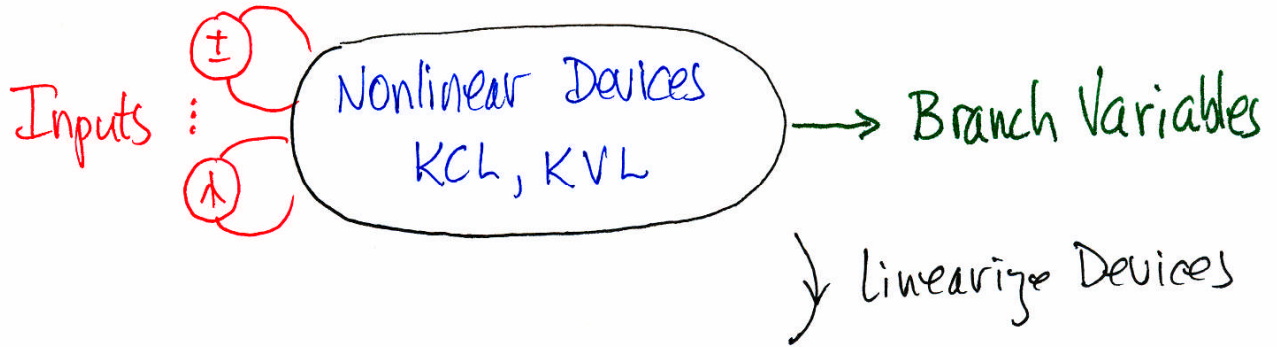


Treatment Of Independent Sources

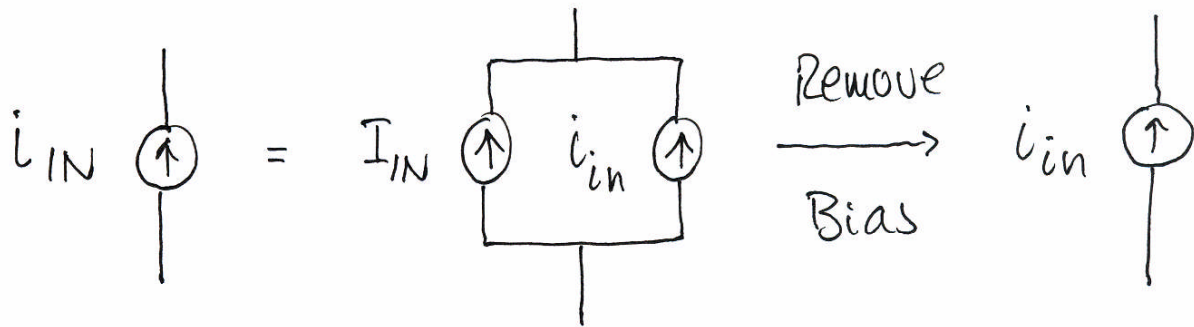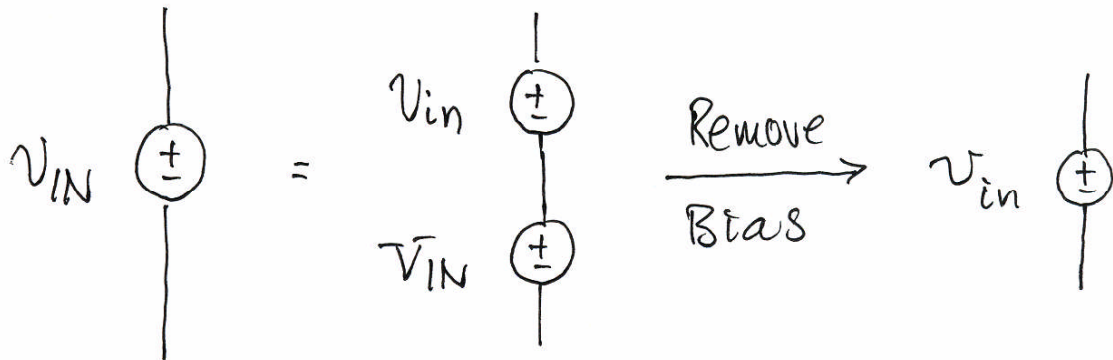

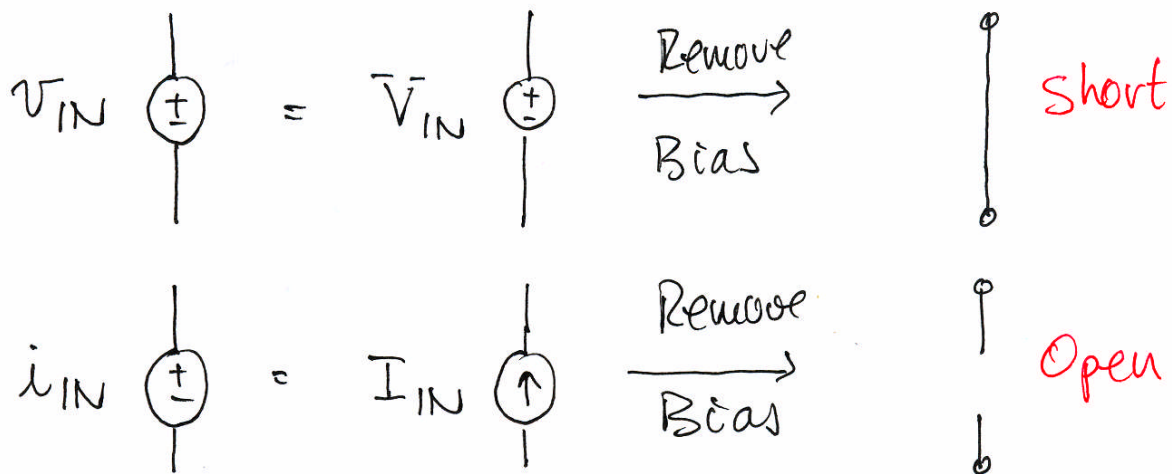If the independent source has no small-signal component, then ...



Linearizing A Nonlinear Resistor

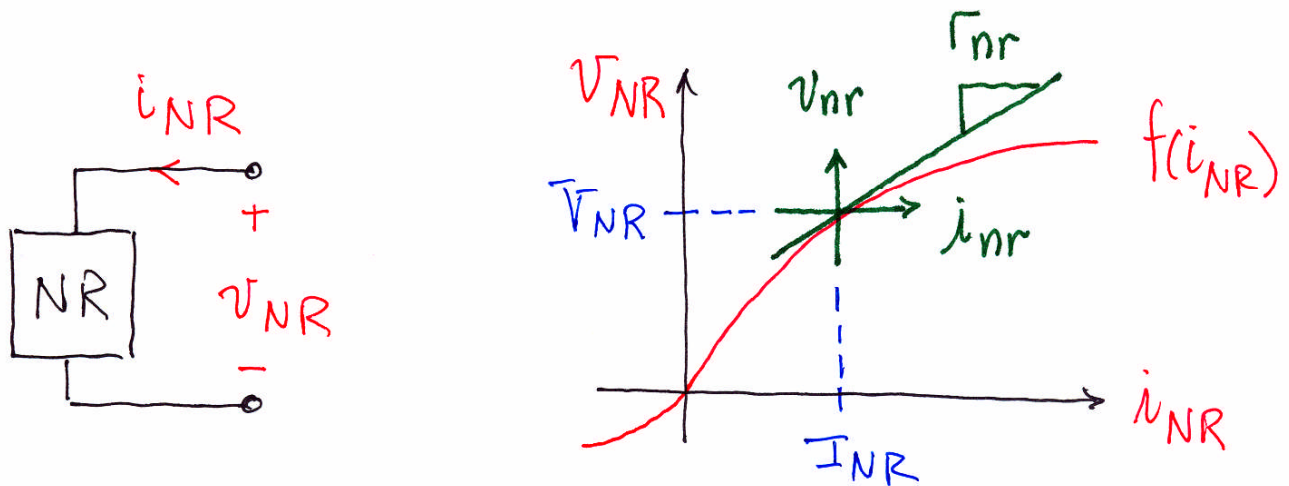


Bias: $V_{NR} = f(I_{NR})$


Off Bias:
$$\begin{aligned} v_{NR} &= f(i_{NR}) \\ &= V_{NR} + v_{nr} \\ &= f(I_{NR} + i_{nr}) \\ &\approx f(I_{NR}) + \left. \frac{df}{di_{NR}} \right|_{I_{NR}} \cdot i_{nr} \\ &= V_{NR} + r_{nr} \cdot i_{nr} \\ &= V_{NR} + r_{nr} (i_{NR} - I_{NR}) \end{aligned}$$

Nonlinear-Resistor Small-Signal Model
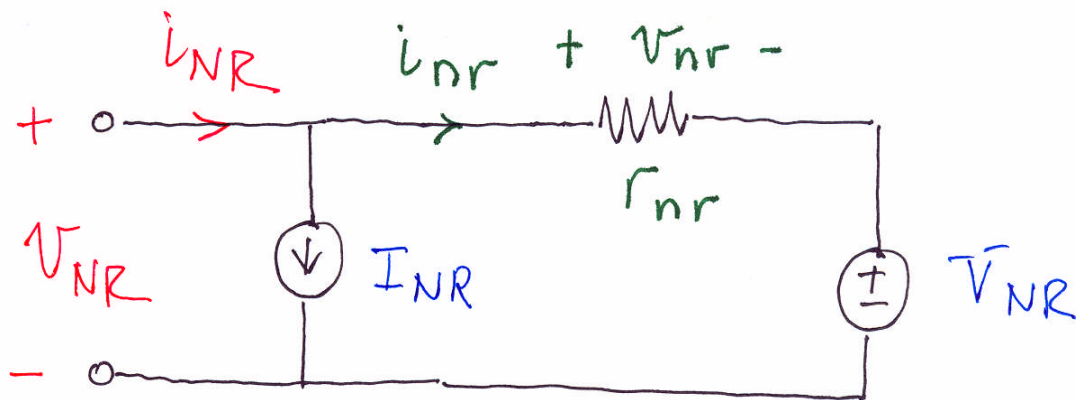
$$V_{NR} = \bar{V}_{NR} + r_{nr} (i_{nr} - I_{NR})$$




↓ Set Biases
To zero

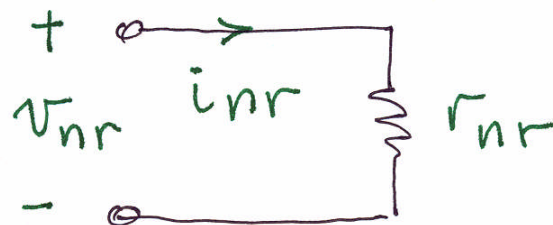

Alternatively: $V_{NR} + v_{nr} = \bar{V}_{NR} + r_{nr} i_{nr}$

↑ ↑
Bias Cancels

Linearizing A Dependent Source

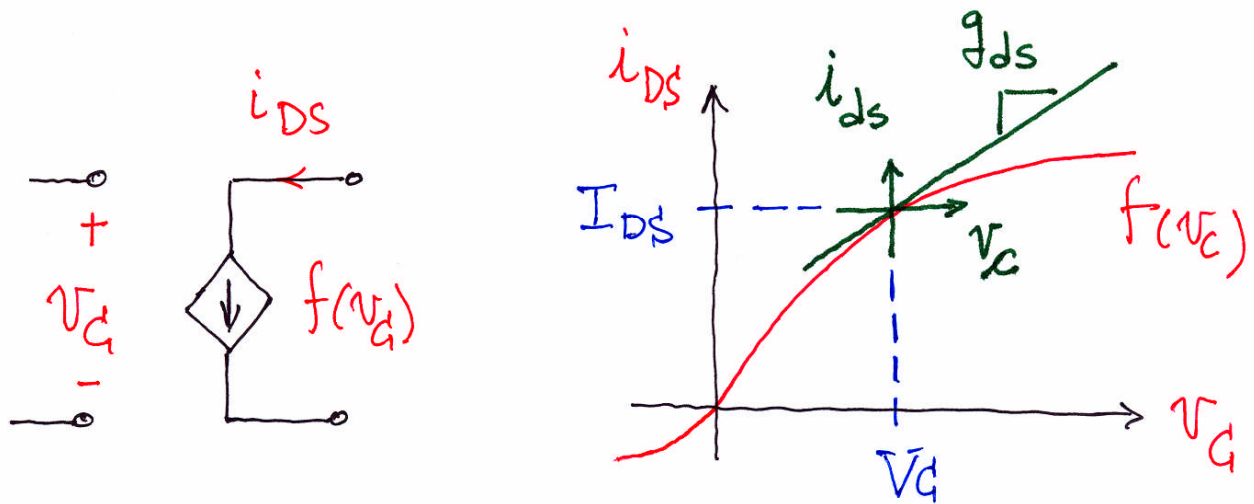


Bias: $I_{DS} = f(V_G)$

Off Bias: $i_{DS} = f(v_G)$


$$\begin{aligned} &= I_{DS} + i_{ds} \\ &= f(V_G + v_c) \\ &\approx f(V_G) + \left. \frac{df}{dv_G} \right|_{V_G} \cdot v_c \\ &= I_{DS} + g_{DS} \cdot v_c \\ &= I_{DS} + g_{DS} (v_c - V_G) \end{aligned}$$

Dependent - Source Small-Signal Model

$$i_{DS} = I_{DS} + g_{ds} (v_G - V_G)$$

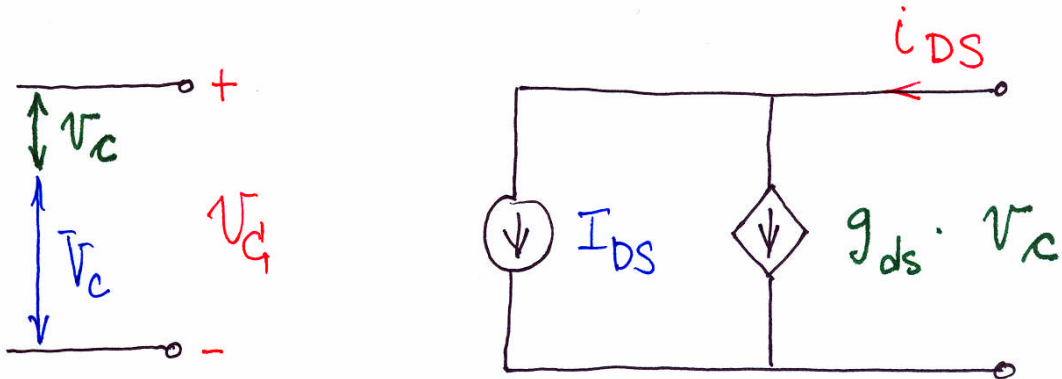


Set Biases
To zero

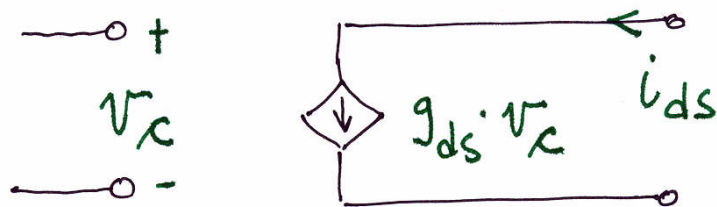


Alternatively: $I_{DS} + i_{ds} = I_{DS} + g_{ds} v_c$

$\underbrace{\hspace{10em}}_{\text{Biases Cancel}}$

MOSFET Small-Signal Model

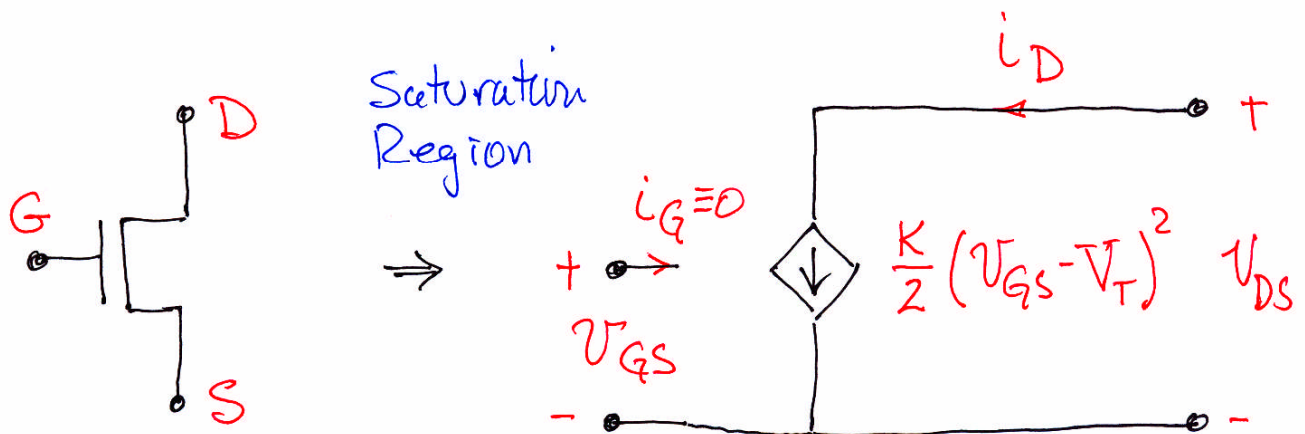


Small-Signal Model

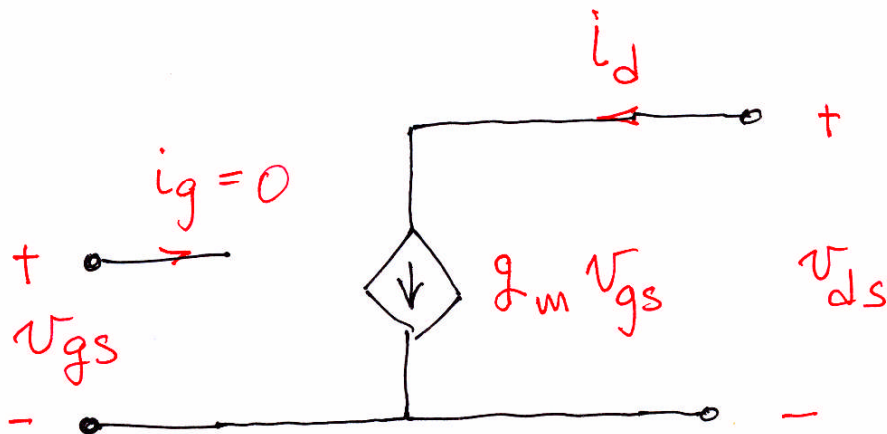


$$g_m = K (V_{GS} - V_T)$$

MOSFET Amplifier S-S Model

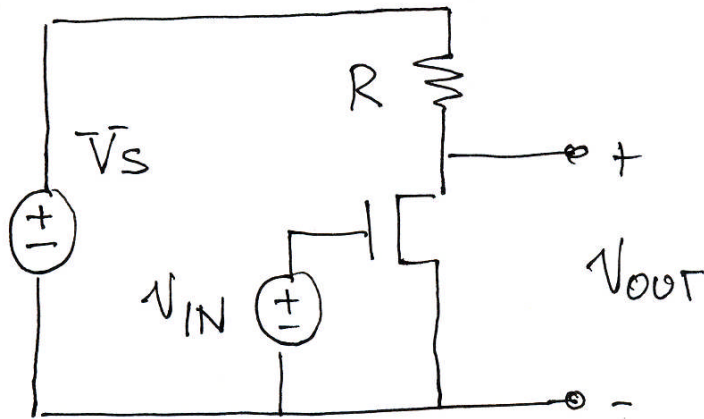

Use
Small-Signal
Device Models

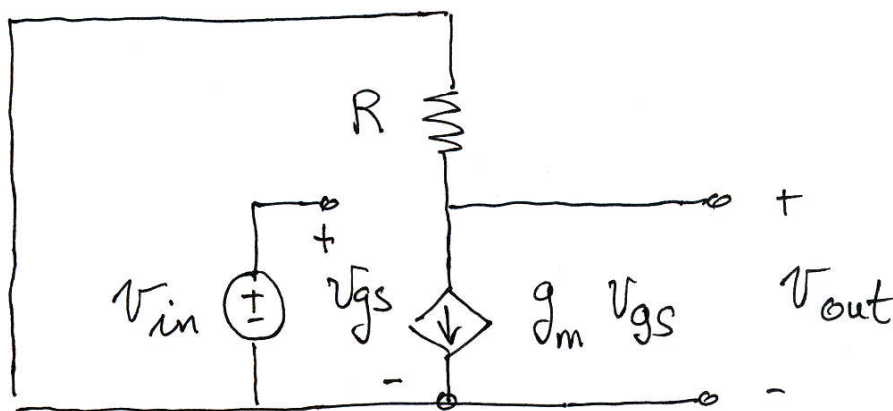

Re-draw

