

Calculate Frequency of Damped RLC Oscillator

$$\omega' = \sqrt{\omega^2 - (R/2L)^2}$$

$$\omega' = \sqrt{\left(\frac{1}{\sqrt{LC}}\right)^2 - (R/2L)^2}$$

where L=90mH

C=.6μF

R=60Ω + 4.5Ω (R_{inductor @ 90mH}) + 50Ω (output impedance

R_{tot}=114.5Ω

of F.G.)

$$\frac{\omega'}{2\pi} = 677.37 \text{ Hz} \quad T = 1.4\text{ms}$$

Calculate Time of Oscillation Envelope Decay

How long will it take envelope to decay to 1/e of its initial value?

$$e^{\frac{-Rt}{2L}} = 1/e$$

$$\frac{-Rt}{2L} = -1$$

$$t = 2L/R$$

$$t = 1.57\text{ms}$$