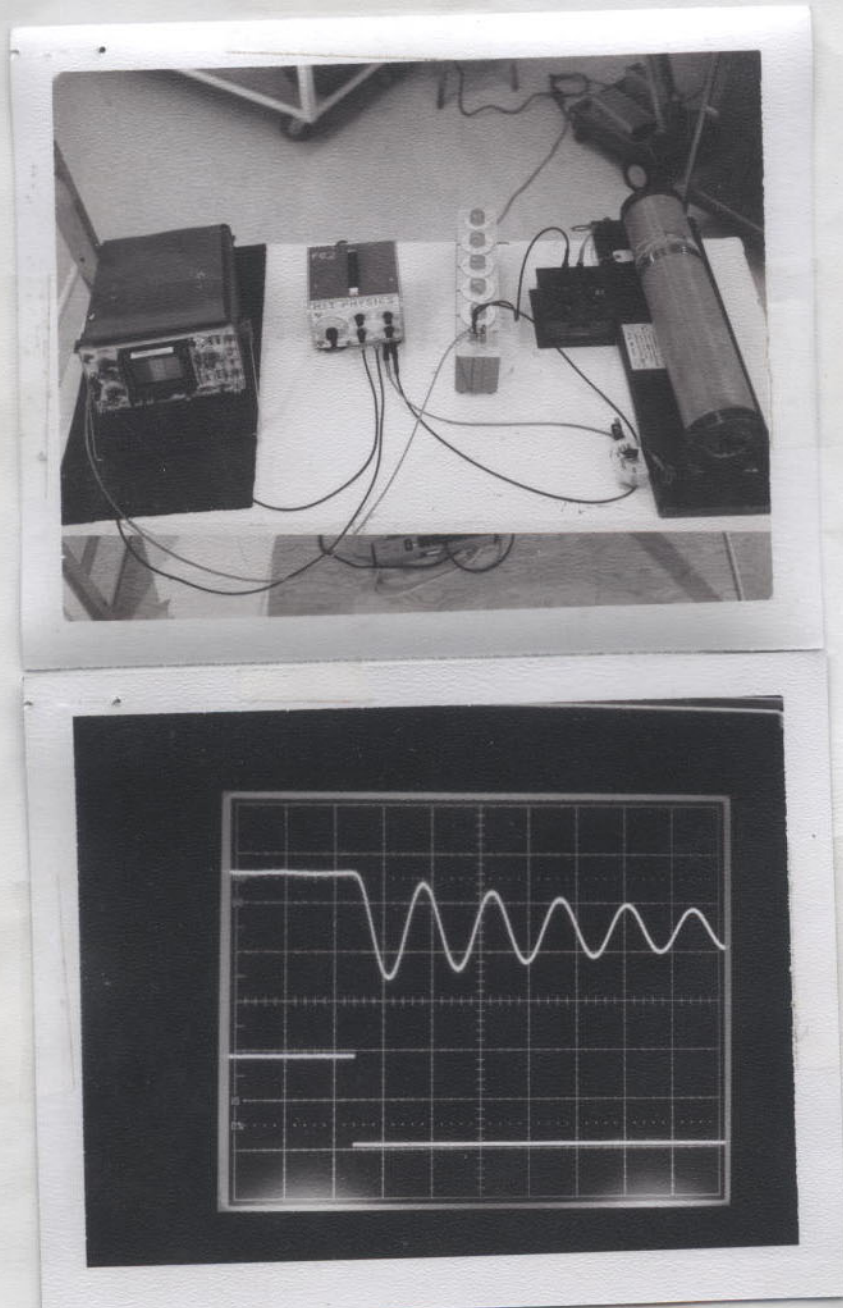


**LC & RLC CIRCUITS - Damped Oscillations**

A series circuits consisting of a decade resistor, a decade capacitor, and a variable inductor are driven by a square wave generator. The damped signal across any of the circuit components can be displayed on an oscilloscope.





H. Bradt  
September 3, 1987

### X80. Damping in LC(R) Circuit; CRT - 10M

*Purpose:* Show the effect (damping) of resistance in an LC (R) circuit.. Display waveforms on a CRT.

*Equipment:* LC circuit (values??); square wave generator; CRT

#### *Procedure:*

The intrinsic R does the damping.

Pulse (or 'excite') the LRC Circuit with edges of pulse from square wave generator.

Set decay time to be a lot less than time between edges.

Show square wave on scope.


Show multiple excitations in LRC circuit

Each excitation damps out rather quickly

Increase sweep speed to show decay from one excitation.

Could compare decay time to that predicted by theory (approx. equal to RC)

B80

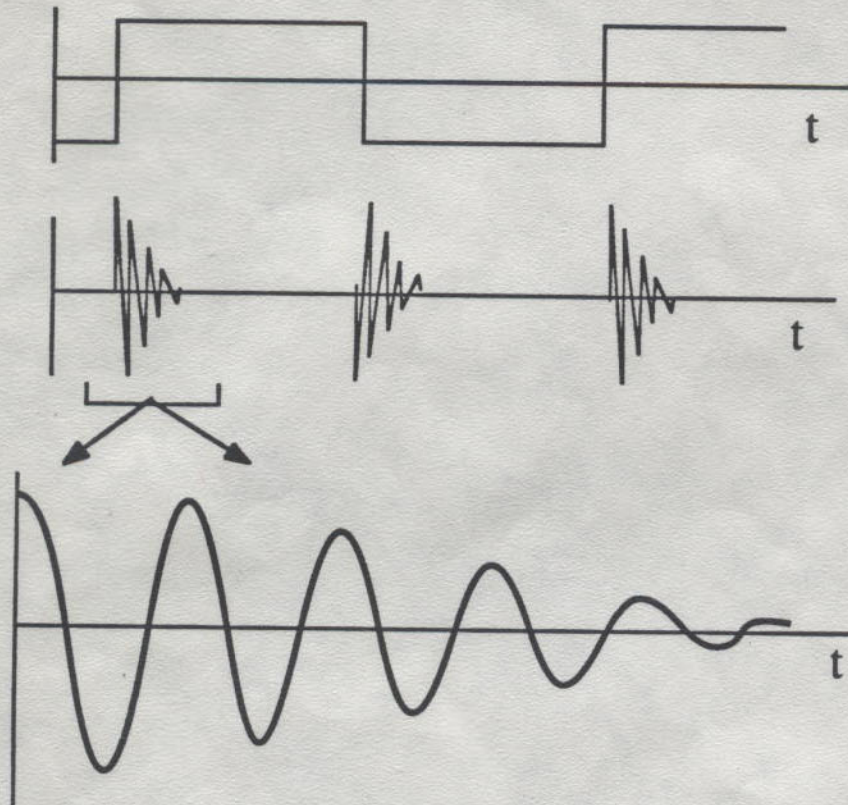






L2a

## DAMPED RLC CIRCUIT (ACROSS RESISTOR)

L2
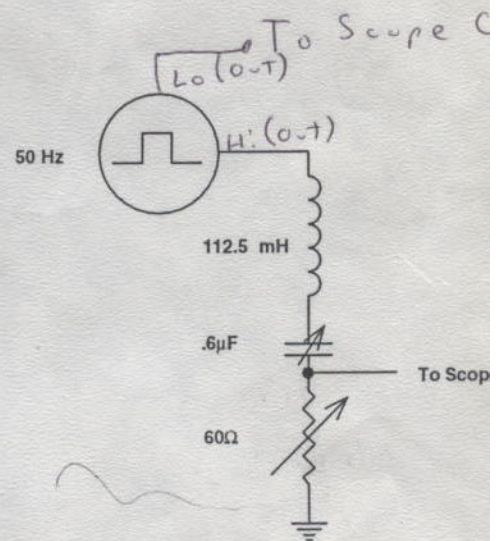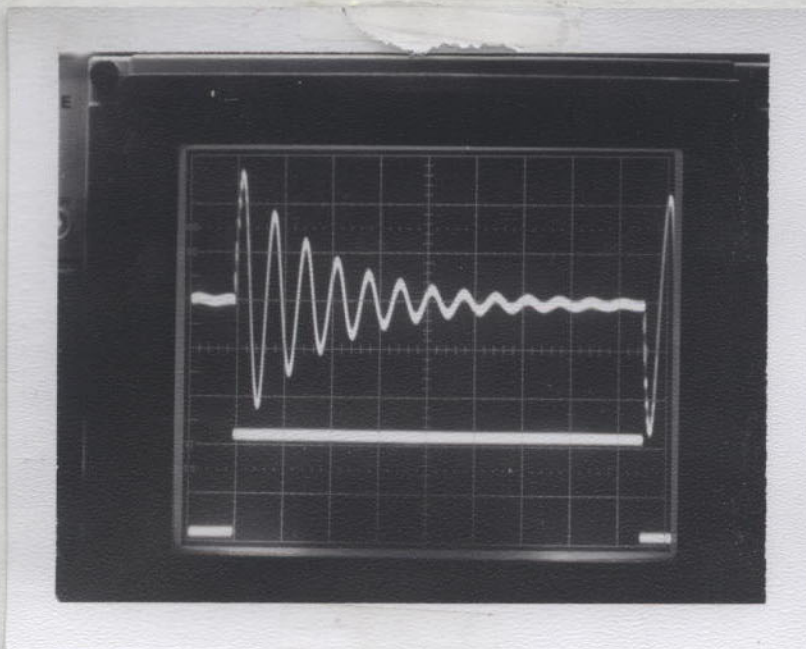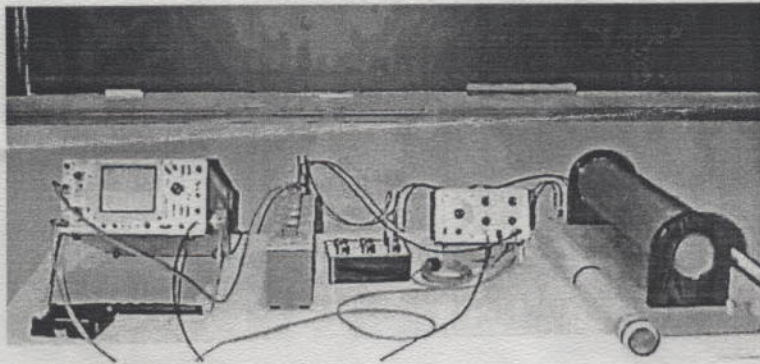
### DAMPED OSCILLATIONS - Damped RLC Circuit


A series circuit consisting of a decade resistor, decade capacitor and a variable inductor driven by a square wave generator. The damped signal across any of the circuit components are displayed on an oscilloscope.





# DAMPED RLC CIRCUIT

L2

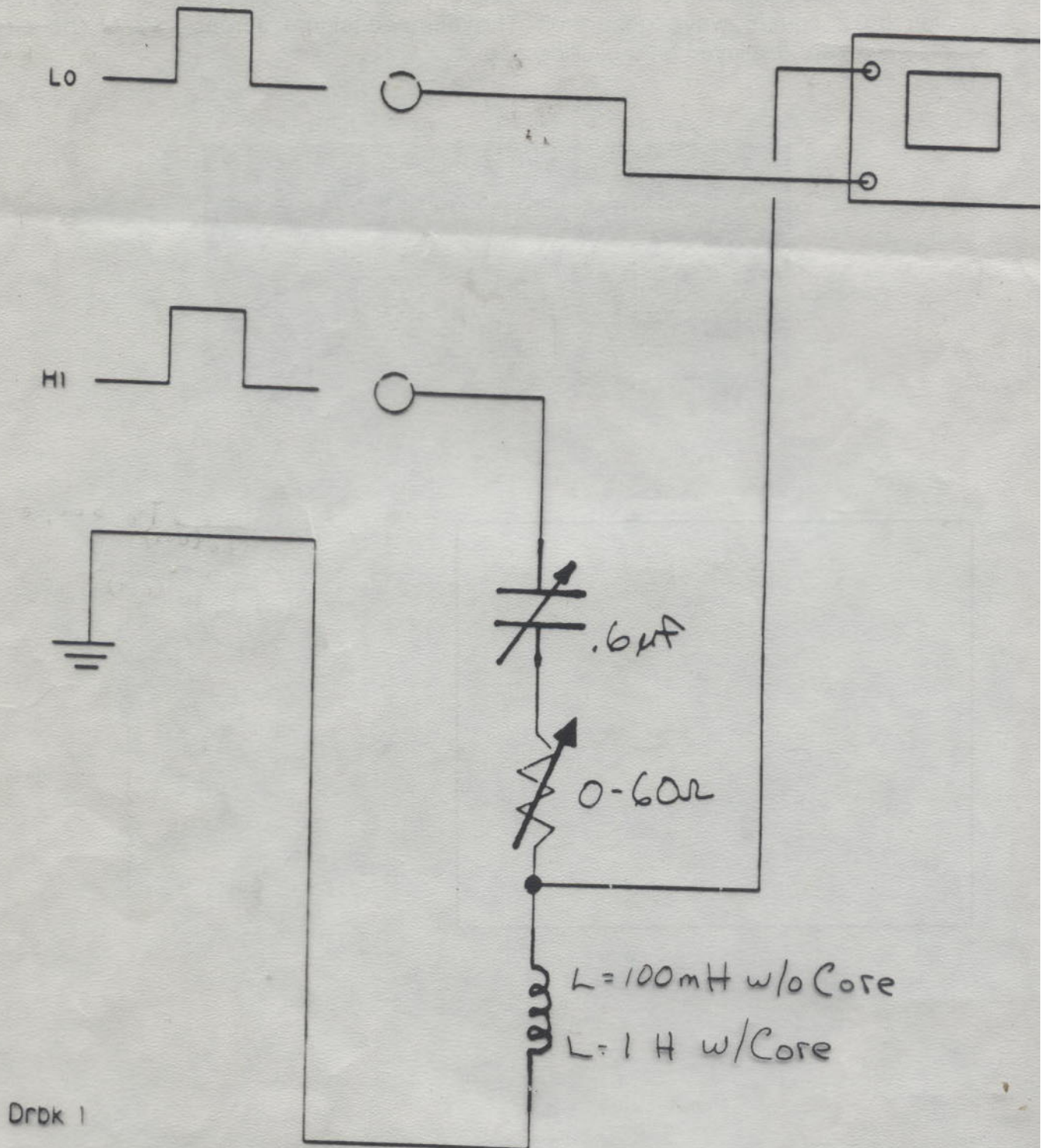



L2b

## DAMPED RLC CIRCUIT (ACROSS CAPACITOR)

L2b
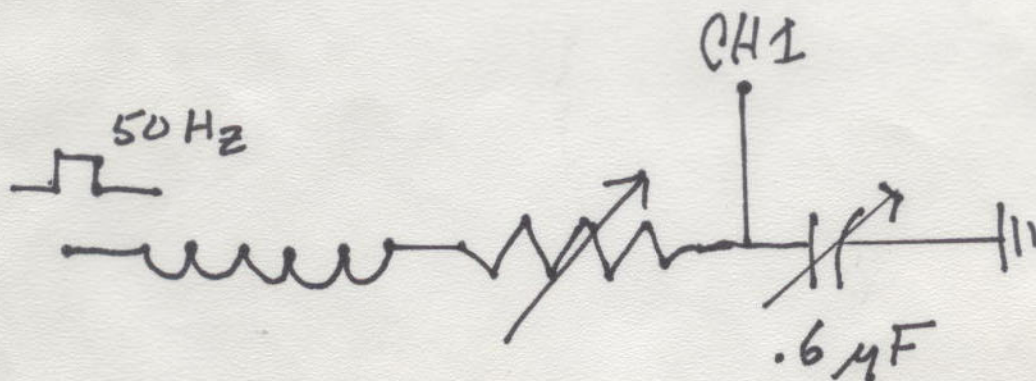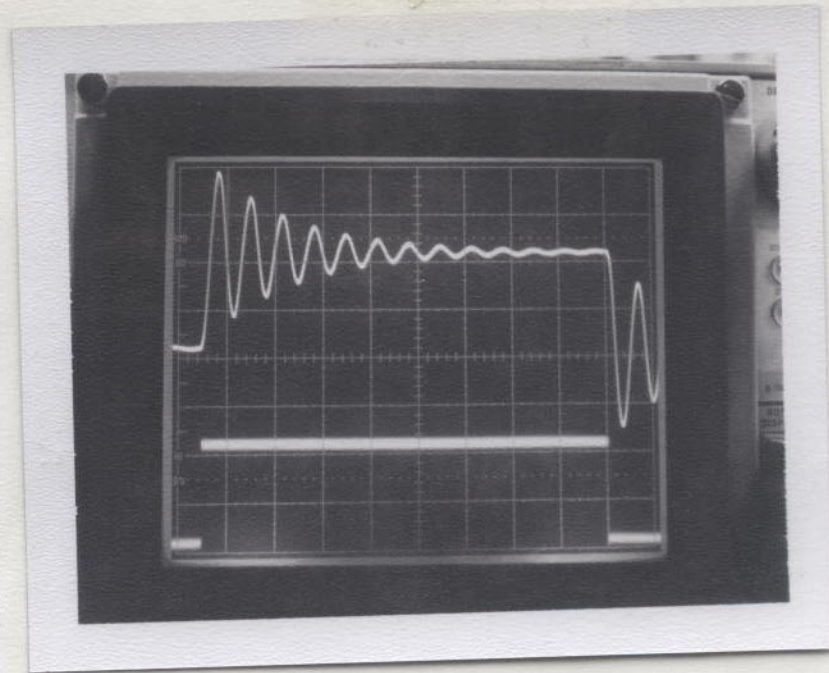
### DAMPED OSCILLATIONS - Damped RLC Circuit

A series circuit consisting of a decade resistor, decade capacitor and a variable inductor driven by a square wave generator. The damped signal across any of the circuit components are displayed on an oscilloscope.





L2b


# DAMPED RLC ACROSS CAPACITOR

$$T = 2\pi \sqrt{LC}$$

(read across C)

## 1. Circuit Set Up:

Function Gen (FG2)

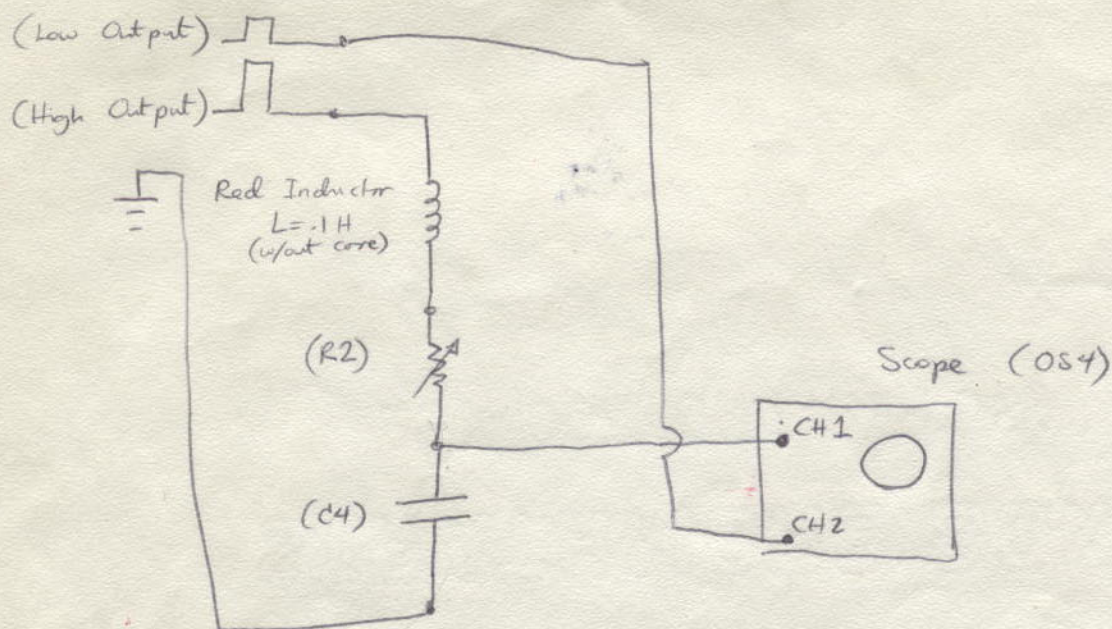

## 2. Specifications:

### ● FG2:

- Function: SQ
- Range: ~~10~~ 10 ; knob < 5
- DC offset: 0
- Sync Output: → to scope A Trigger
- High Output Level: → to Inductor
- Low Output Level: → to scope Ch.2

### ● R2:

- Originally set @ 0.52





L2c

## DAMPED RLC CIRCUIT (ACROSS INDUCTOR)

L2c
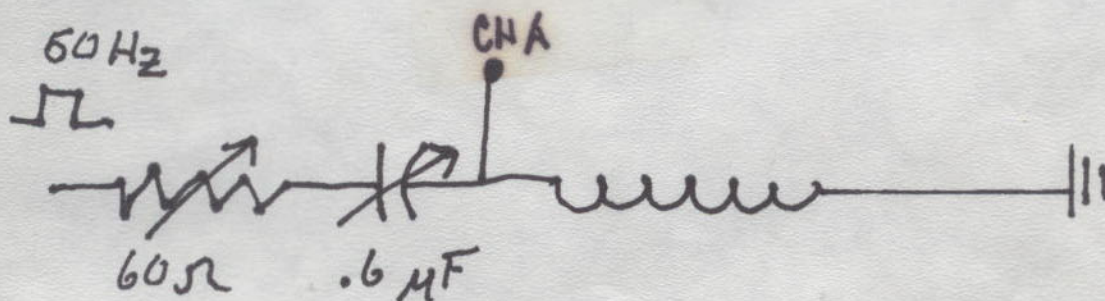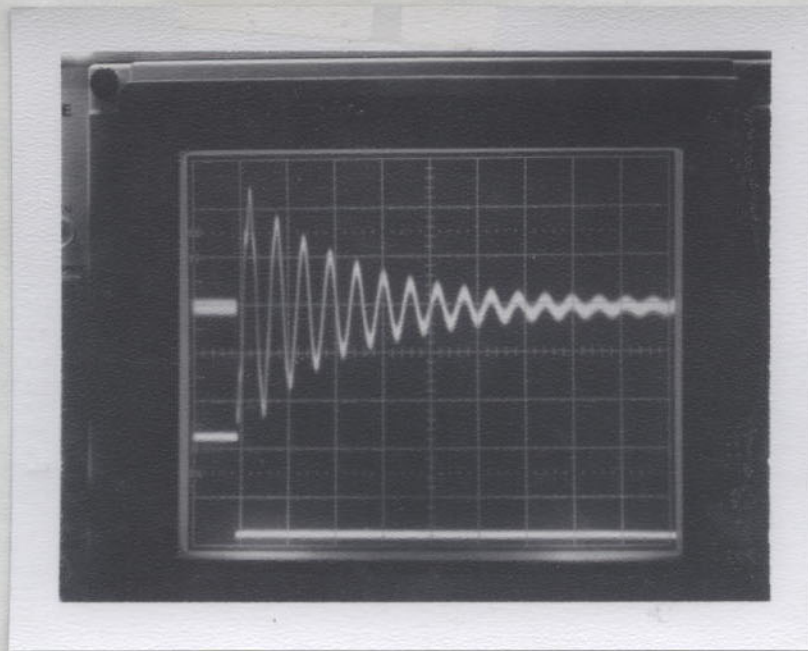
### DAMPED OSCILLATIONS - Damped RLC Circuit

A series circuit consisting of a decade resistor, decade capacitor and a variable inductor driven by a square wave generator. The damped signal across any of the circuit components are displayed on an oscilloscope.





L2d

## DAMPED RLC CIRCUIT (SERIES / PARALLEL)

L2

### DAMPED OSCILLATIONS - Damped RLC Circuit

A series circuit consisting of a decade resistor, decade capacitor and a variable inductor driven by a square wave generator. The damped signal across any of the circuit components are displayed on an oscilloscope.

