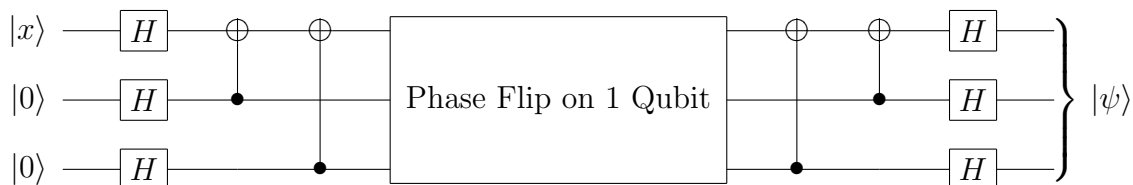


## 2.111J/18.435J Quantum Computation Problem Set 8

(Due: Tuesday, December 6, 2005)

1) Verify that the following circuit is the appropriate encoder/decoder circuit for the 3 qubit phase flip code.



In other words, exhibit a measurement on the two ancillae in the circuit's output  $|\psi\rangle$  that will detect whether a phase flip error occurred and locate the phase flip if it did occur. Then, exhibit an operation based on the above measurement that will correct the phase flip.

---

2) Construct an encoding circuit and a decoding circuit for the 9 qubit Shor code

$$|0\rangle \rightarrow \frac{1}{2\sqrt{2}}(|000\rangle + |111\rangle) \otimes (|000\rangle + |111\rangle) \otimes (|000\rangle + |111\rangle)$$


$$|1\rangle \rightarrow \frac{1}{2\sqrt{2}}(|000\rangle - |111\rangle) \otimes (|000\rangle - |111\rangle) \otimes (|000\rangle - |111\rangle).$$

---

3) Verify that the 9 qubit Shor code corrects a bit and/or phase flip on any 1 of the 9 qubits.

---


4) What is the output  $|\psi\rangle$  of the following circuit, which is the encoder for the Laflamme-Miquel-Paz-Zurek perfect 5 qubit code?

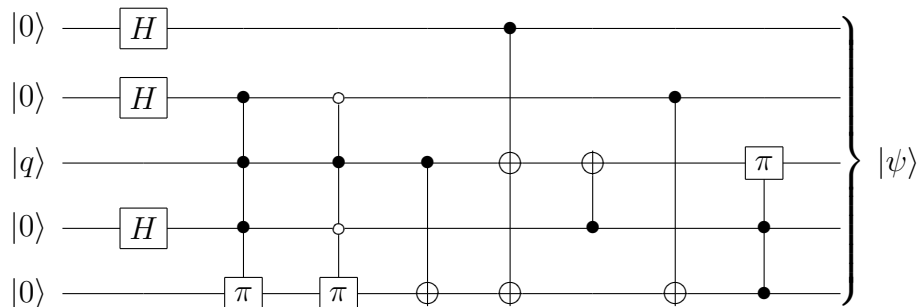

Note the following definitions. The single qubit gates are (in the  $\sigma_z$  eigenbasis):

$$\text{---} \boxed{H} \text{---} = \frac{1}{\sqrt{2}} \begin{pmatrix} 1 & 1 \\ 1 & -1 \end{pmatrix}; \quad \text{---} \boxed{\pi} \text{---} = e^{i\pi\mathbb{I}} = \begin{pmatrix} -1 & 0 \\ 0 & -1 \end{pmatrix}; \quad \text{---} \oplus \text{---} = \begin{pmatrix} 0 & 1 \\ 1 & 0 \end{pmatrix}.$$

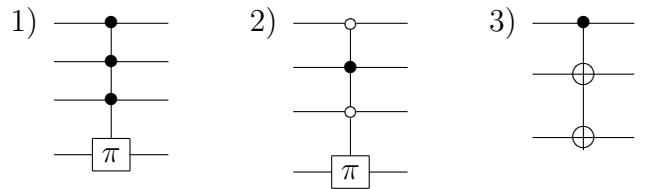Our more complicated controlled gates, for example



work as follows (in the tensor product  $\sigma_z$  eigenbasis):

- (1) does nothing to the first 3 qubits and imparts a  $-1$  phase factor to the 4th qubit if and only if the first 3 qubits are in the state  $|111\rangle$ .
- (2) does nothing to the first 3 qubits and imparts a  $-1$  phase factor to the 4th qubit if and only if the first 3 qubits are in the the state  $|010\rangle$ .
- (3) does nothing to the 1st qubit and applies  $\oplus$ -gates to both the 2nd and 3rd qubits only if the 1st qubit is in the state  $|1\rangle$ .

---

5) Verify that the decoder of the above circuit allows one to correct a bit and/or phase flip on any 1 of the 5 qubits.

---

6) Consider the code  $|0\rangle_{en} = \frac{1}{\sqrt{2}}(|01\rangle - |10\rangle)$ ;  $|1\rangle_{en} = \frac{1}{\sqrt{2}}(|01\rangle + |10\rangle)$ . Show that an arbitrary superposition of encoded states  $\alpha|0\rangle_{en} + \beta|1\rangle_{en}$  is robust against errors of the form  $e^{-i\theta\sigma_z/2} \otimes e^{-i\theta\sigma_z/2}$ .