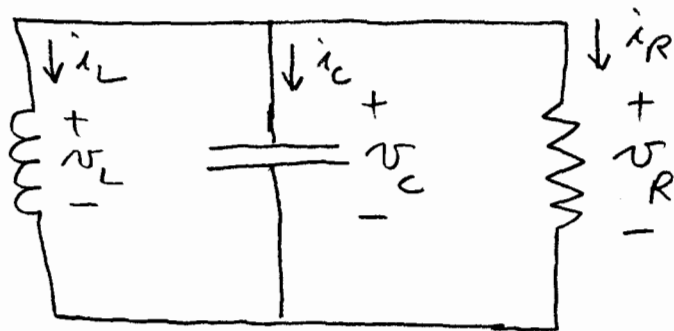


(E1)

The electrical circuit shown below can be described by a 2nd-order homogeneous differential equation. We will see that it exhibits responses which are analogous to the 2nd order mechanical system studied earlier



First, recall the constitutive relationships

$$v_R = i_R R$$

$$v_L = L \frac{di_L}{dt}$$

$$i_C = C \frac{dv_C}{dt}$$

The three elements are in parallel, and thus have equal voltages

$$v_L = v_C = v_R \stackrel{\Delta}{=} v$$

Also, currents entering (leaving) a node must sum to zero. Counting entering as positive, the currents at the upper node sum as

$$-i_L - i_C - i_R = 0$$

Now we have $i_R = \frac{v}{R}$

$$i_C = C \frac{dv}{dt}$$

$$i_L = \frac{1}{L} \int v dt$$

Substituting into the previous result gives

$$\frac{1}{L} \int v dt + C \frac{dv}{dt} + \frac{1}{R} v = 0$$

Taking the derivative of each term yields

$$LC \frac{dv^2}{dt^2} + \frac{L}{R} \frac{dv}{dt} + v = 0$$

Compare with the canonical 2nd-order form to give

$$\omega_n = \frac{1}{\sqrt{LC}}$$

$$\zeta = \frac{1}{2R} \sqrt{\frac{L}{C}}$$

The associated initial conditions are

$$v(0) = v_C(0)$$

and

$$\begin{aligned} \dot{v}(0) &= \frac{dv_C(0)}{dt} = \frac{i_C(0)}{C} = \frac{1}{C} (-i_L(0) - i_R(0)) \\ &= \frac{1}{C} (-i_L(0) - \frac{v_C(0)}{R}) \end{aligned}$$