

Lecture 10

MOSFET (III)

MOSFET Equivalent Circuit Models

Outline


- Low-frequency small-signal equivalent circuit model
- High-frequency small-signal equivalent circuit model

Reading Assignment:

Howe and Sodini; Chapter 4, Sections 4.5-4.6

Summary of Key Concepts

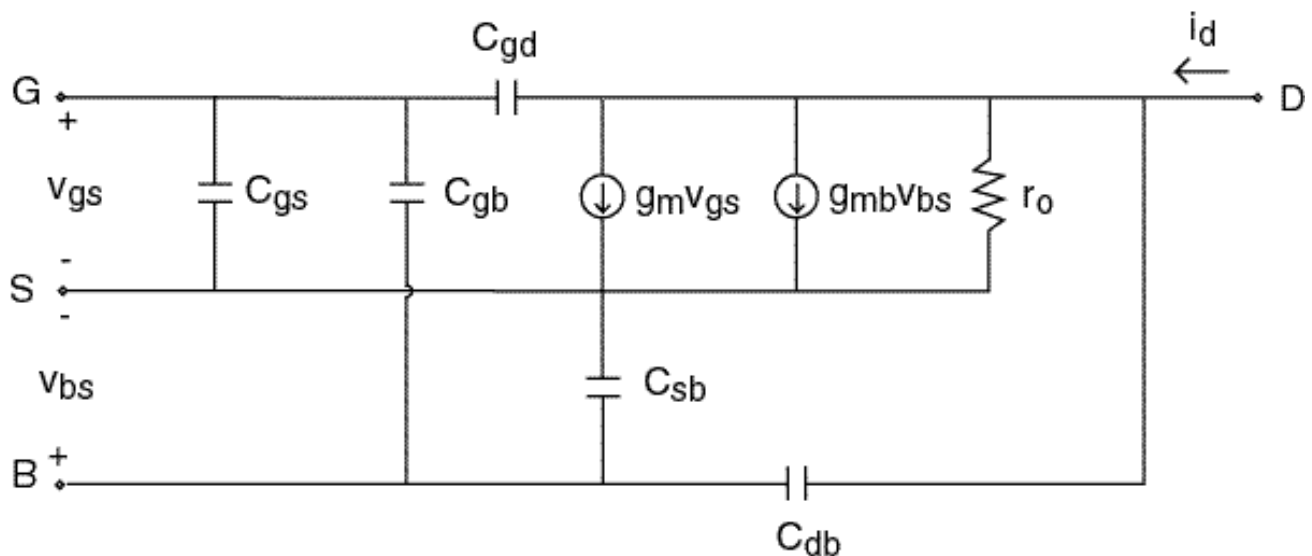High-frequency small-signal equivalent circuit model of MOSFET



In saturation:


$$g_m \propto \sqrt{\frac{W}{L}} I_D$$

$$r_o \propto \frac{L}{I_D}$$

$$C_{gs} \propto WLC_{ox}$$

1. Low-frequency small-signal equivalent circuit model

Regimes of operation of MOSFET:

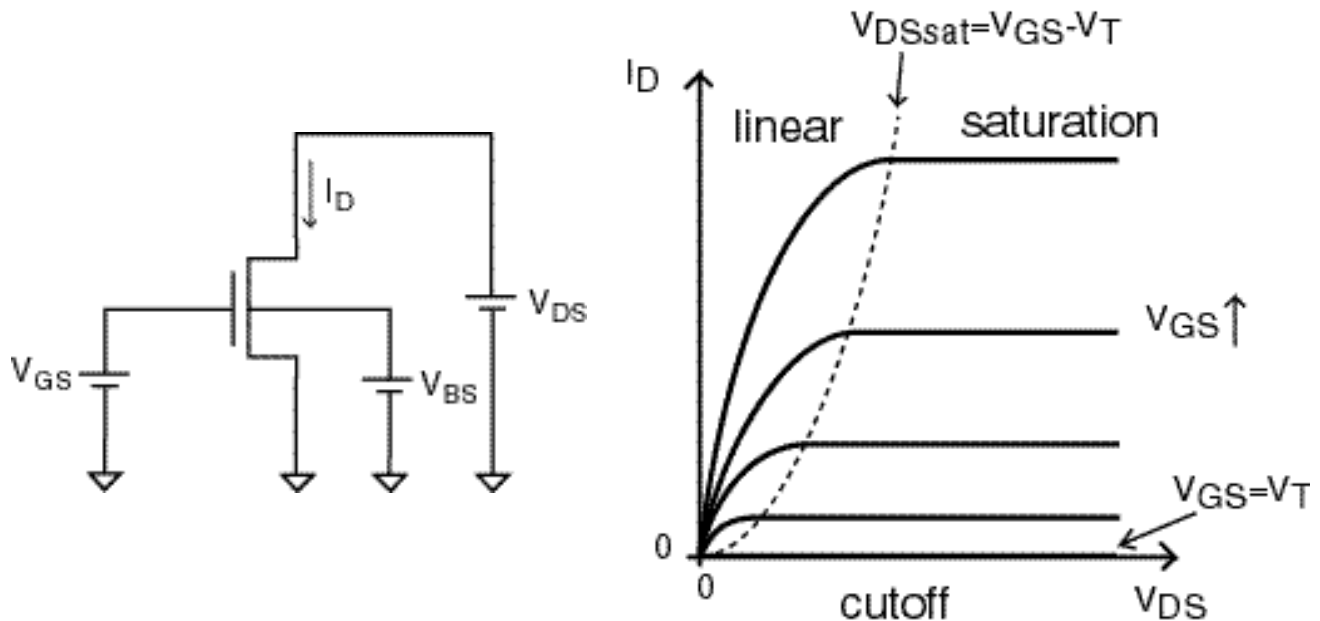

- Cut-off

$$I_D = 0$$

- Linear / Triode:

$$I_D = \frac{W}{L} m_h C_{ox} \left[V_{GS} - \frac{V_{DS}}{2} - V_T \right] \cdot V_{DS}$$

- Saturation


$$I_D = I_{Dsat} = \frac{W}{2L} m_h C_{ox} [V_{GS} - V_T]^2 \cdot [1 + I(V_{DS} - V_{DSsat})]$$

Effect of back bias

$$V_T(V_{BS}) = V_{To} + g \left[\sqrt{-2f_p - V_{BS}} - \sqrt{-2f_p} \right]$$

Small-signal device modeling

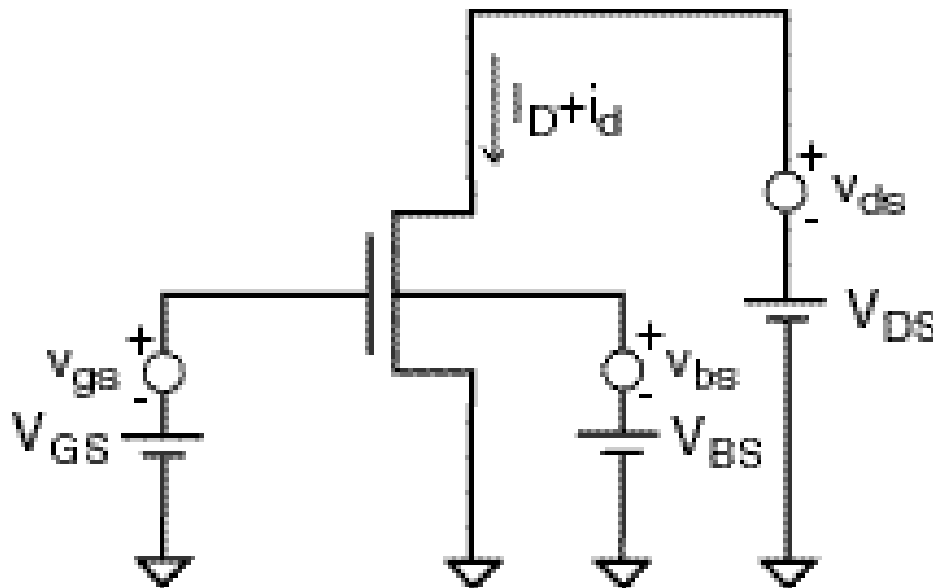In many applications, we are only interested in the response of device to *small-signal* applied on top of a bias.



Key Points:

- Small-signal is *small*
 - \Rightarrow response of non-linear components becomes linear
- Since response is linear, *superposition* can be used
 - \Rightarrow effects of different small signals are independent from each other.

Mathematically:

$$\mathbf{i}_D(\mathbf{V}_{GS}, \mathbf{V}_{DS}, \mathbf{V}_{BS}; \mathbf{v}_{gs}, \mathbf{v}_{ds}, \mathbf{v}_{bs}) \approx \mathbf{I}_D(\mathbf{V}_{GS}, \mathbf{V}_{DS}, \mathbf{V}_{BS}) + \mathbf{i}_d(\mathbf{v}_{gs}, \mathbf{v}_{ds}, \mathbf{v}_{bs})$$

With \mathbf{i}_d linear on small-signal drives:

$$\mathbf{i}_d \approx \mathbf{g}_m \mathbf{v}_{gs} + \mathbf{g}_o \mathbf{v}_{ds} + \mathbf{g}_{mb} \mathbf{v}_{bs}$$

Define:

$$\mathbf{g}_m \equiv \textit{transconductance} \text{ [S]}$$

$$\mathbf{g}_o \equiv \textit{output or drain conductance} \text{ [S]}$$

$$\mathbf{g}_{mb} \equiv \textit{backgate transconductance} \text{ [S]}$$

Approach to computing \mathbf{g}_m , \mathbf{g}_o , and \mathbf{g}_{mb} .

$$\mathbf{g}_m \approx \left. \frac{\mathbf{i}_D}{\mathbf{v}_{GS}} \right|_Q$$

$$\mathbf{g}_o \approx \left. \frac{\mathbf{i}_D}{\mathbf{v}_{DS}} \right|_Q$$

$$\mathbf{g}_{mb} \approx \left. \frac{\mathbf{i}_D}{\mathbf{v}_{BS}} \right|_Q$$

$$\mathbf{Q} \equiv [\mathbf{v}_{GS} = \mathbf{V}_{GS}, \mathbf{v}_{DS} = \mathbf{V}_{DS}, \mathbf{v}_{BS} = \mathbf{V}_{BS}]$$

Transconductance

In saturation regime:


$$i_D = \frac{W}{2L} m_n C_{ox} [v_{GS} - V_T]^2 \cdot [1 + \lambda (v_{DS} - V_{DSsat})]$$

Then (neglecting channel length modulation) the transconductance is:


$$g_m = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_Q \approx \frac{W}{L} m_n C_{ox} (V_{GS} - V_T)$$

Rewrite in terms of I_D :
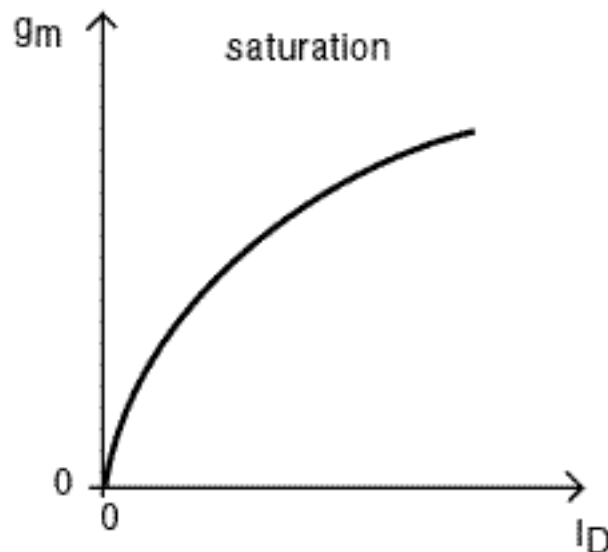
$$g_m = \sqrt{2 \frac{W}{L} m_n C_{ox} I_D}$$




Transconductance (contd.)

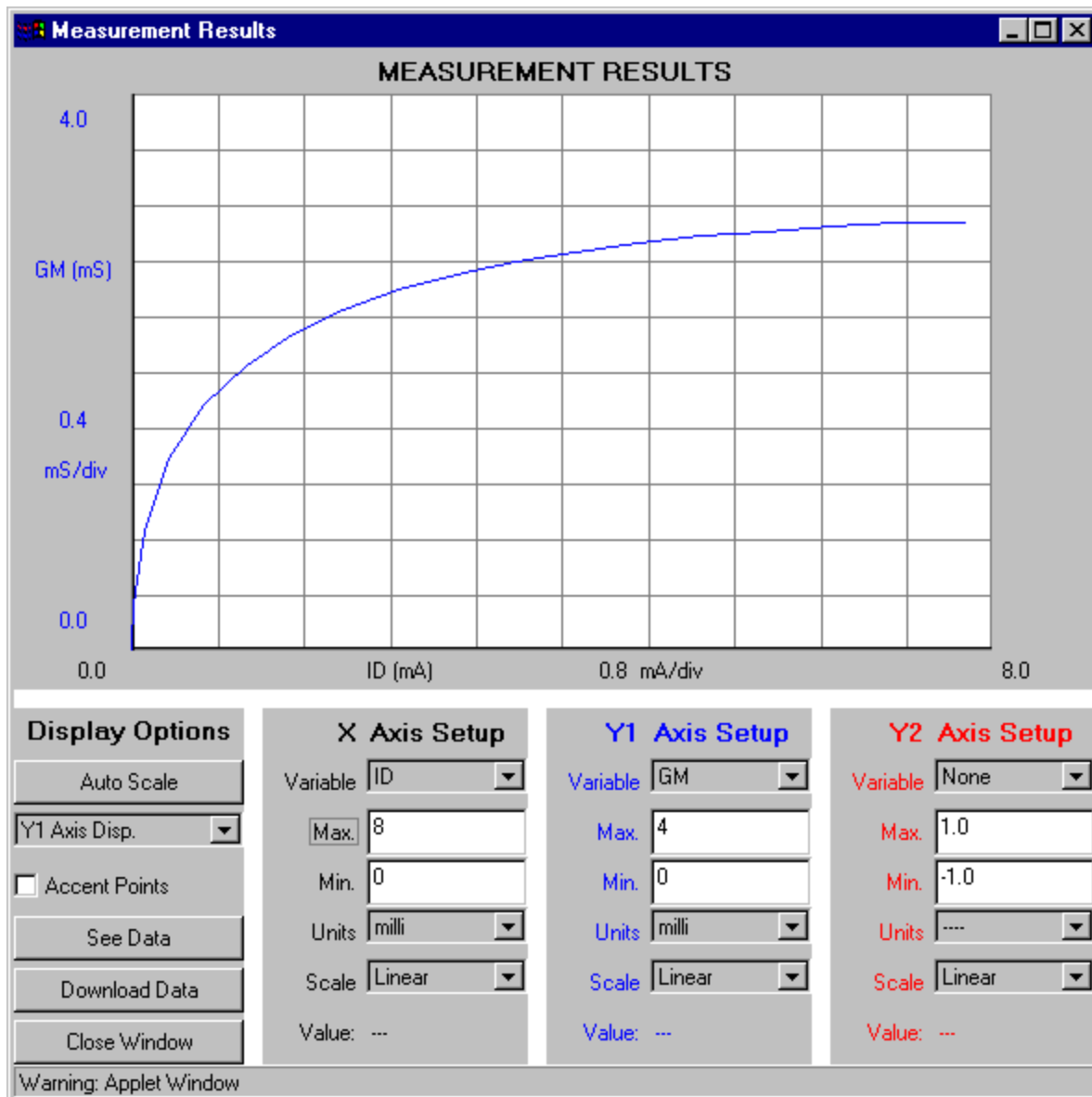

Transconductance (contd.)

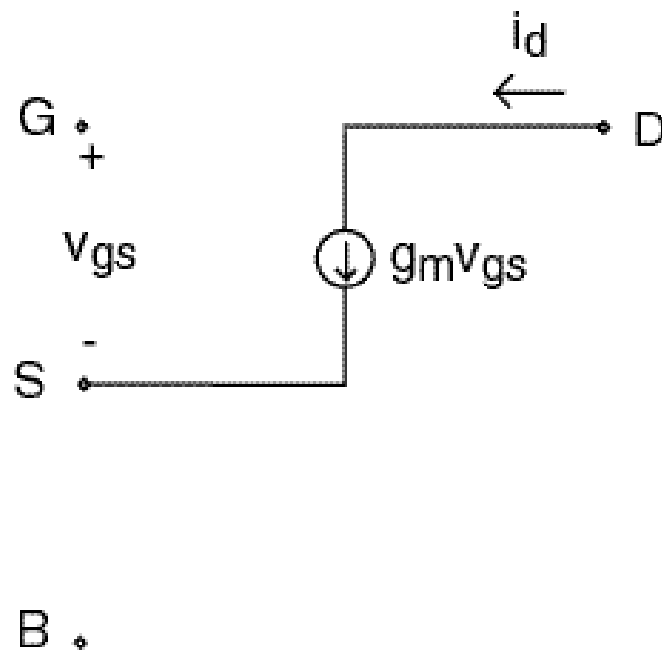Equivalent circuit model representation of g_m :



Output conductance

In saturation regime:

$$i_D = \frac{W}{2L} m_n C_{ox} [v_{GS} - V_T]^2 \cdot [1 + \lambda (v_{DS} - V_{DSsat})]$$

Then:

$$g_o = \left. \frac{\partial i_D}{\partial v_{DS}} \right|_Q = \frac{W}{2L} m_n C_{ox} (V_{GS} - V_T)^2 \cdot \lambda \approx \lambda I_D$$

Output resistance is the inverse of output conductance:

$$r_o = \frac{1}{g_o} = \frac{1}{\lambda I_D}$$


Remember also:

$$\lambda \propto \frac{1}{L}$$

Hence:


$$r_o \propto L$$

Output conductance (contd.)

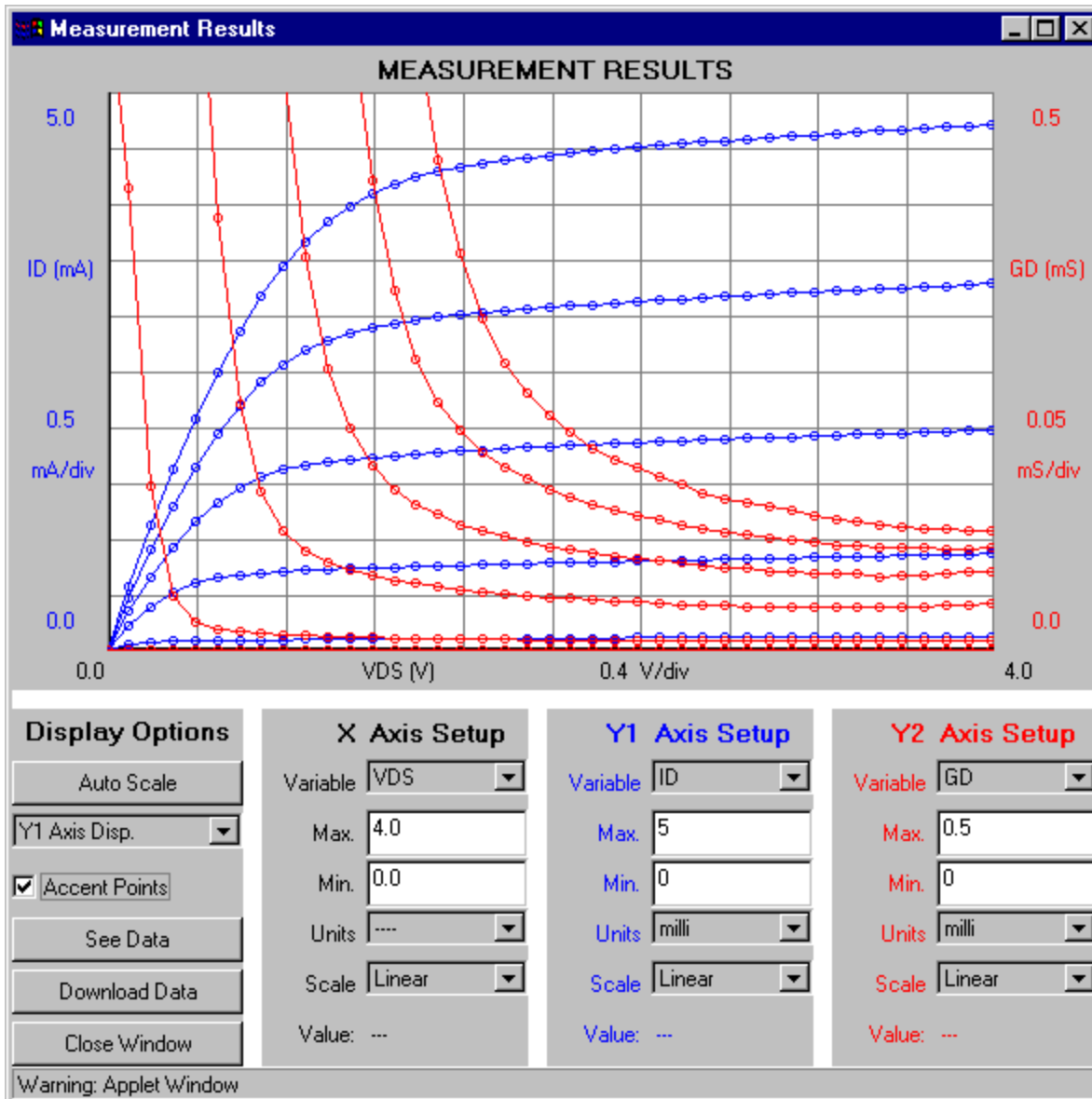

Output conductance (contd.)

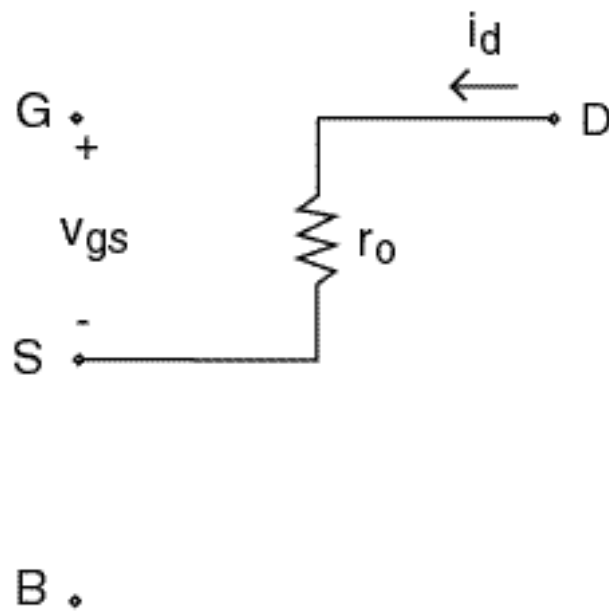Equivalent circuit model representation of g_o :



Backgate transconductance

In saturation regime (neglect channel length modulation):

$$i_D \approx \frac{W}{2L} m_h C_{ox} [v_{GS} - V_T]^2$$

Then:

$$g_{mb} = \left. \frac{\partial i_D}{\partial v_{BS}} \right|_Q = -\frac{W}{L} m_h C_{ox} (V_{GS} - V_T) \cdot \left(\left. \frac{\partial V_T}{\partial v_{BS}} \right|_Q \right)$$

Since:

$$V_T(v_{BS}) = V_{T0} + g \left[\sqrt{-2f_p - v_{BS}} - \sqrt{-2f_p} \right]$$

Then :

$$\left. \frac{\partial V_T}{\partial v_{BS}} \right|_Q = \frac{-g}{2\sqrt{-2f_p - V_{BS}}}$$


Hence:

$$g_{mb} = \frac{g g_m}{2\sqrt{-2f_p - V_{BS}}}$$

Backgate transconductance (contd.)


Another way to write this (see book):
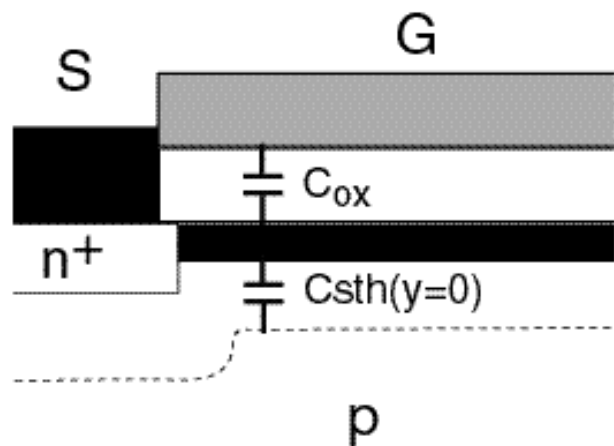
$$\frac{g_{mb}}{g_m} = \frac{C_b(y=0)}{C_{ox}}$$




Ratio of backgate transconductance to transconductance is equal to the ratio of depletion capacitance at source to oxide capacitance.

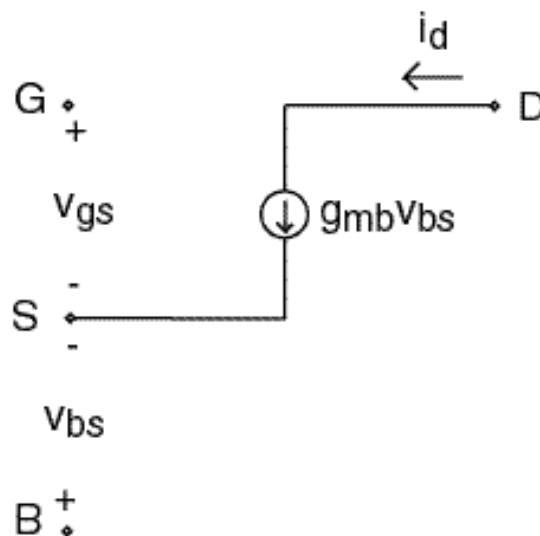Equivalent circuit representation of g_{mb} :




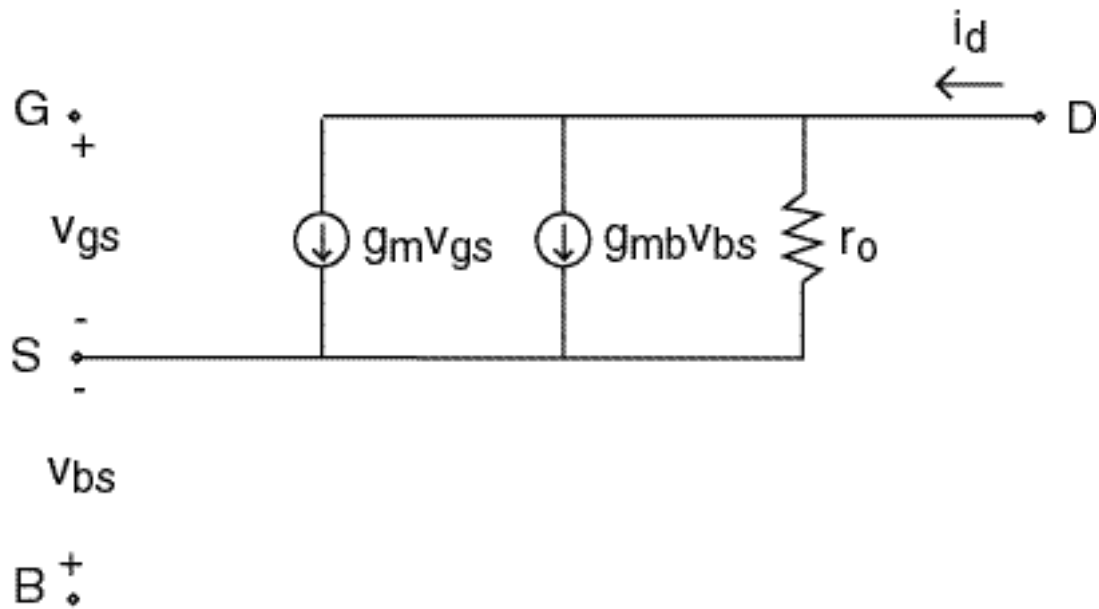Complete MOSFET small-signal equivalent circuit model for low frequency:



2. High-frequency small-signal equivalent circuit model

Need to add capacitances. In saturation:

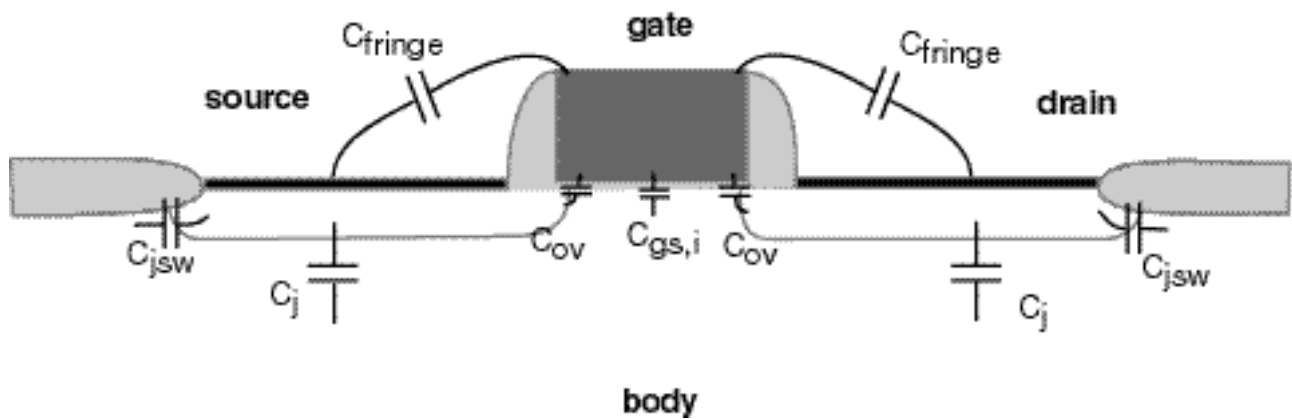

$C_{gs} \equiv$ channel charge + overlap capacitance, C_{ov}


$C_{gd} \equiv$ overlap capacitance, C_{ov}

$C_{gb} \equiv$ only parasitic capacitance

$C_{sb} \equiv$ source junction depletion capacitance (+sidewall)

$C_{db} \equiv$ drain junction depletion capacitance (+sidewall)

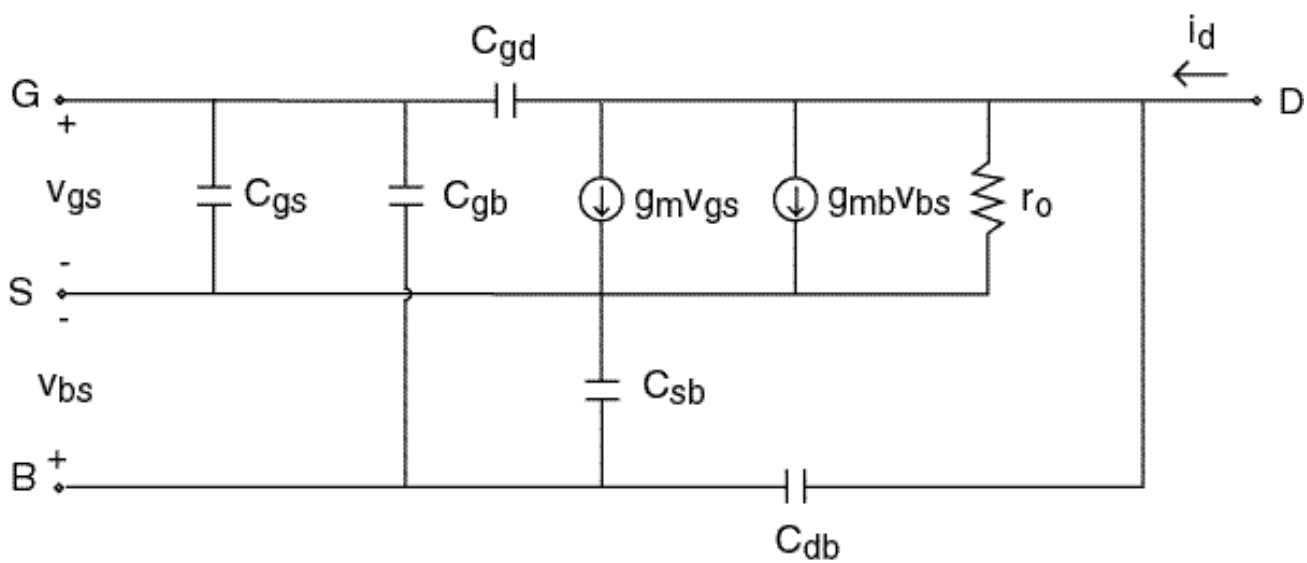Complete MOSFET high-frequency small-signal equivalent circuit model:



Inversion layer charge in saturation

$$q_N(v_{GS}) = W \int_0^L Q_n(y) dy = W \int_0^{v_{GS}-V_T} Q_n(y) \cdot \frac{dy}{dv_C} \cdot dv_C$$

Note that q_N is total inversion charge in the channel & $v_C(y)$ is the channel voltage. But:

$$\frac{dv_C}{dy} = -\frac{i_D}{W m_n Q_n(y)}$$

Then:

$$q_N(v_{GS}) = -\frac{W^2 L m_n}{i_D} \cdot \int_0^{v_{GS}-V_T} [Q_n(y)]^2 \cdot dv_C$$

Remember:

$$Q_n(v_C) = -C_{ox} [v_{GS} - v_C(y) - V_T]$$

Then:

$$q_N(v_{GS}) = -\frac{W^2 L m_n}{i_D} \cdot \int_0^{v_{GS}-V_T} [v_{GS} - v_C(y) - V_T]^2 \cdot dv_C$$

Inversion layer charge in saturation (contd.)

Do integral, substitute i_D in saturation and get:

$$q_N(v_{GS}) = -\frac{2}{3} WLC_{ox}(v_{GS} - V_T)$$

Gate charge:

$$q_G(v_{GS}) = -q_N(v_{GS}) - Q_{B,max}$$

Intrinsic gate-to-source capacitance:

$$C_{gs,i} = \frac{dq_G}{dv_{GS}} = \frac{2}{3} WLC_{ox}$$


Must add overlap capacitance:

$$C_{gs} = \frac{2}{3} WLC_{ox} + WC_{ov}$$

Gate-to-drain capacitance — only overlap capacitance:

$$C_{gd} = WC_{ov}$$

Other capacitances

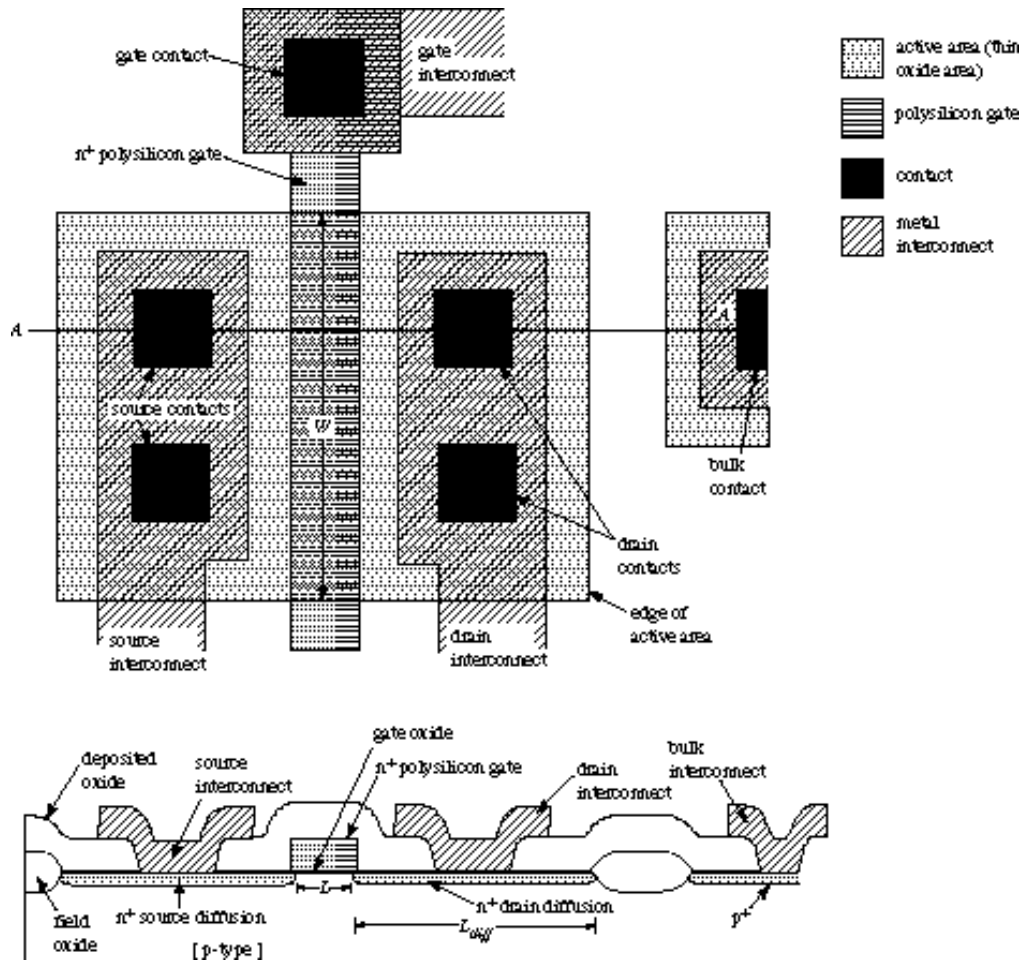

Body-to-source capacitance = source junction capacitance:

$$C_{bs} = C_j + C_{jsw} = WL_{diff} \sqrt{\frac{qe_s N_a}{2(f_B - V_{BS})}} + (2L_{diff} + W)C_{Jsw}$$


Body-to-drain capacitance = drain junction capacitance:

$$C_{bd} = C_j + C_{jsw} = WL_{diff} \sqrt{\frac{qe_s N_a}{2(f_B - V_{BS})}} + (2L_{diff} + W)C_{Jsw}$$

What did we learn today?

Summary of Key Concepts

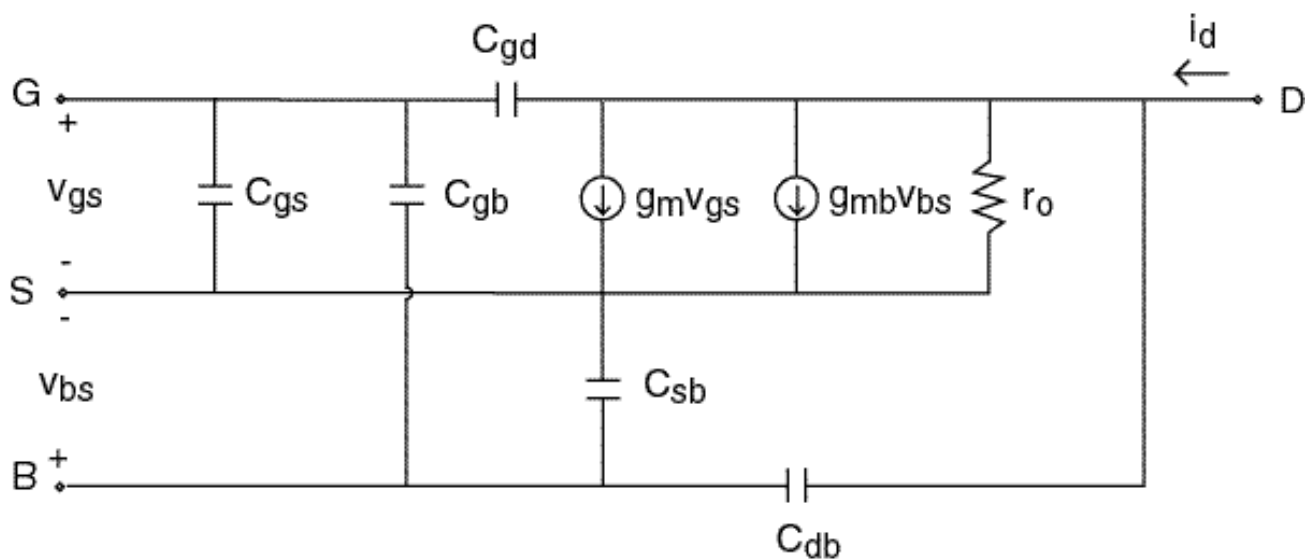High-frequency small-signal equivalent circuit model of MOSFET



In saturation:

$$g_m \propto \sqrt{\frac{W}{L}} I_D$$

$$r_o \propto \frac{L}{I_D}$$

$$C_{gs} \propto WLC_{ox}$$