

Lecture 13

Digital Circuits (III)

CMOS CIRCUITS

Outline

- Complementary MOS (CMOS) Inverter: **introduction**
- CMOS inverter: **noise margins**
- CMOS Inverter: **propagation delay**

Reading Assignment:

Howe and Sodini; Chapter 5, Sections 5.4, 5.5 & 5.7

Summary of Key Concepts

Key features of CMOS inverter:

- No current between power supply and ground while inverter is idle in any logic state
- “rail-to-rail” logic
 - Logic levels are 0 and V_{DD} .
- High $|A_v|$ around the logic threshold
 - Good noise margins.

CMOS inverter logic threshold and noise margins engineered through W_n/L_n and W_p/L_p .

Key dependencies of propagation delay:

- V_{DD} t_p
- L t_p

1. Complementary MOS (CMOS) Inverter


Circuit schematic:

- $V_{IN} = 0$ $V_{OUT} = V_{DD}$
 - $V_{GSn} = 0$ ($< V_{Tn}$) **NMOS OFF**
 - $V_{SGp} = V_{DD}$ ($> -V_{Tp}$) **PMOS ON**
- $V_{IN} = V_{DD}$ $V_{OUT} = 0$
 - $V_{GSn} = V_{DD}$ ($> V_{Tn}$) **NMOS ON**
 - $V_{SGp} = 0$ ($< -V_{Tp}$) **PMOS OFF**

No power consumption while idle in any logic state!

CMOS Inverter (Contd.):

 Output characteristics of both transistors:




Note:

$$V_{IN} = V_{GSn} = V_{DD} - V_{SGp} \quad V_{GSp} = V_{DD} - V_{IN}$$

$$V_{OUT} = V_{DSn} = V_{DD} - V_{SDp} \quad V_{SDp} = V_{DD} - V_{OUT}$$

$$I_{Dn} = -I_{Dp}$$

 Combine into single diagram of I_D vs. V_{OUT} with V_{IN} as parameter




- *No current while idle in any logic state*

Inverter Characteristics:



- *“rail-to-rail” logic: logic levels are 0 and V_{DD}*
- *High $|A_v|$ around logic threshold
good noise margins*

2. CMOS inverter: noise margins

 

- Calculate V_M
- Calculate $A_v(V_M)$
- Calculate NM_L and NM_H

Calculate V_M ($V_M = V_{IN} = V_{OUT}$)

At V_M both transistors are saturated:

$$I_{Dn} = \frac{W_n}{2L_n} \mu_n C_{ox} (V_M - V_{Tn})^2$$

$$-I_{Dp} = \frac{W_p}{2L_p} \mu_p C_{ox} (V_{DD} - V_M + V_{Tp})^2$$

CMOS inverter: noise margins (contd.)

Define:

$$k_n = \frac{W_n}{L_n} \mu_n C_{ox}; \quad k_p = \frac{W_p}{L_p} \mu_p C_{ox}$$

Since :

$$I_{Dn} = -I_{Dp}$$

Then:

$$\frac{1}{2} k_n (V_M - V_{Tn})^2 = \frac{1}{2} k_p (V_{DD} - V_M + V_{Tp})^2$$

Solve for V_M :

$$V_M = \frac{V_{Tn} + \sqrt{\frac{k_p}{k_n}} (V_{DD} + V_{Tp})}{1 + \sqrt{\frac{k_p}{k_n}}}$$

Usually, V_{Tn} and V_{Tp} fixed and $V_{Tn} = -V_{Tp}$
 V_M engineered through k_p/k_n ratio.

CMOS inverter: noise margins (contd..)

- **Symmetric case:** $k_n = k_p$

$$V_M = \frac{V_{DD}}{2}$$

This implies:

$$\frac{k_p}{k_n} = 1 = \frac{\frac{W_p}{L_p} \mu_p C_{ox}}{\frac{W_n}{L_n} \mu_n C_{ox}} = \frac{\frac{W_p}{L_p} \mu_p}{\frac{W_n}{L_n} 2\mu_p} = \frac{W_p}{L_p} = 2 \frac{W_n}{L_n}$$

Since usually $L_p = L_n$ $W_p = 2W_n$

- **Asymmetric case:** $k_n \gg k_p$, or $\frac{W_n}{L_n} \gg \frac{W_p}{L_p}$

$$V_M = V_{Tn}$$

NMOS turns on as soon as V_{IN} goes above V_{Tn} .

- **Asymmetric case:** $k_n \ll k_p$, or $\frac{W_n}{L_n} \ll \frac{W_p}{L_p}$



$$V_M = V_{DD} + V_{Tp}$$

PMOS turns on as soon as V_{IN} goes below $V_{DD} + V_{Tp}$.

CMOS inverter: noise margins (contd...)

Calculate $A_v(V_M)$


- Small signal model:

  

$$\mathbf{A}_v = -(\mathbf{g}_{mn} + \mathbf{g}_{mp})(\mathbf{r}_{on} // \mathbf{r}_{op})$$

This can be rather large.

 CMOS inverter: calculate noise margins (contd.)



- Noise-margin low, NM_L :

$$|A_v| = \frac{V_{DD} - V_M}{V_M - V_{IL}}$$

Then:

$$V_{IL} = V_M - \frac{V_{DD} - V_M}{|A_v|}$$

Therefore:

$$NM_L = V_{IL} - V_{OL} = V_{IL} = V_M - \frac{V_{DD} - V_M}{|A_v|}$$

In the limit of $|A_v| \rightarrow \infty$:

$$NM_L \rightarrow V_M$$

CMOS inverter: calculate noise margins (contd.)

- Noise-margin-high, NM_H :

$$|A_v| = \frac{V_M}{V_{IH} - V_M}$$

Then:

$$V_{IH} = V_M \left(1 + \frac{1}{|A_v|} \right)$$

Therefore:

$$NM_H = V_{OH} - V_{IH} = V_{DD} - V_M \left(1 + \frac{1}{|A_v|} \right)$$

In the limit of $|A_v| \rightarrow \infty$:

$$NM_H \rightarrow V_{DD} - V_M$$


3. CMOS inverter: Propagation delay

Inverter propagation delay: time delay between input and output signals; figure of merit of logic speed.

Typical propagation delays: <1 ns.

Complex logic system has 10-50 propagation delays per clock cycle.

 Estimation of t_p : use square-wave at input




Average propagation delay:

$$t_p = \frac{1}{2} (t_{PHL} + t_{PLH})$$

CMOS inverter:

Propagation delay high-to-low

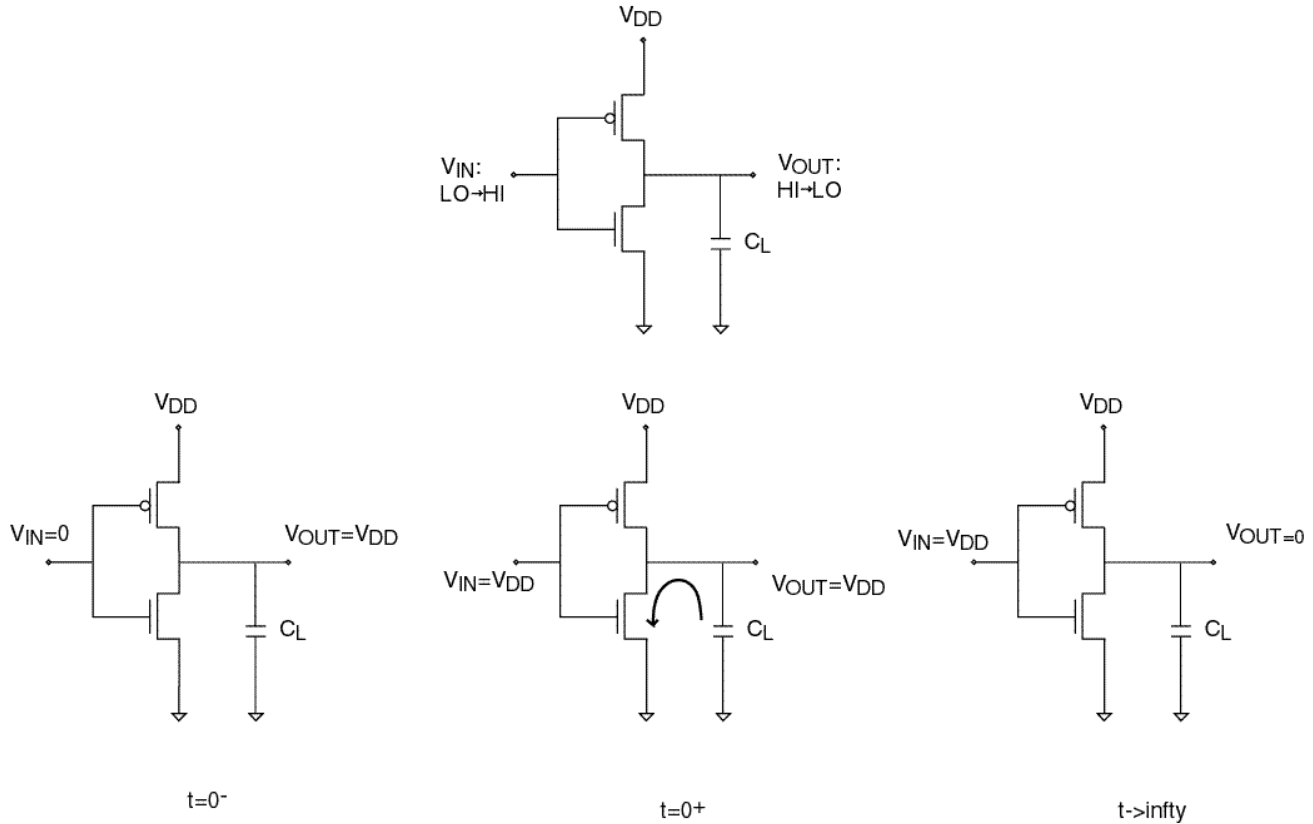

During early phases of discharge, NMOS is saturated and PMOS is cut-off.

Time to discharge *half* of charge stored in C_L :

$$t_{pHL} = \frac{\frac{1}{2} \text{ charge on } C_L \text{ @ } t = 0^-}{\text{discharge current}}$$

CMOS inverter:

Propagation delay high-to-low (contd.)

Charge in C_L at $t=0^-$:

$$Q_L(t = 0^-) = C_L V_{DD}$$

Discharge Current (NMOS in saturation):


$$I_{Dn} = \frac{W_n}{2L_n} \mu_n C_{ox} (V_{DD} - V_{Tn})^2$$

Then:

$$t_{PHL} = \frac{C_L V_{DD}}{\frac{W_n}{L_n} \mu_n C_{ox} (V_{DD} - V_{Tn})^2}$$

CMOS inverter:

Propagation delay low-to-high

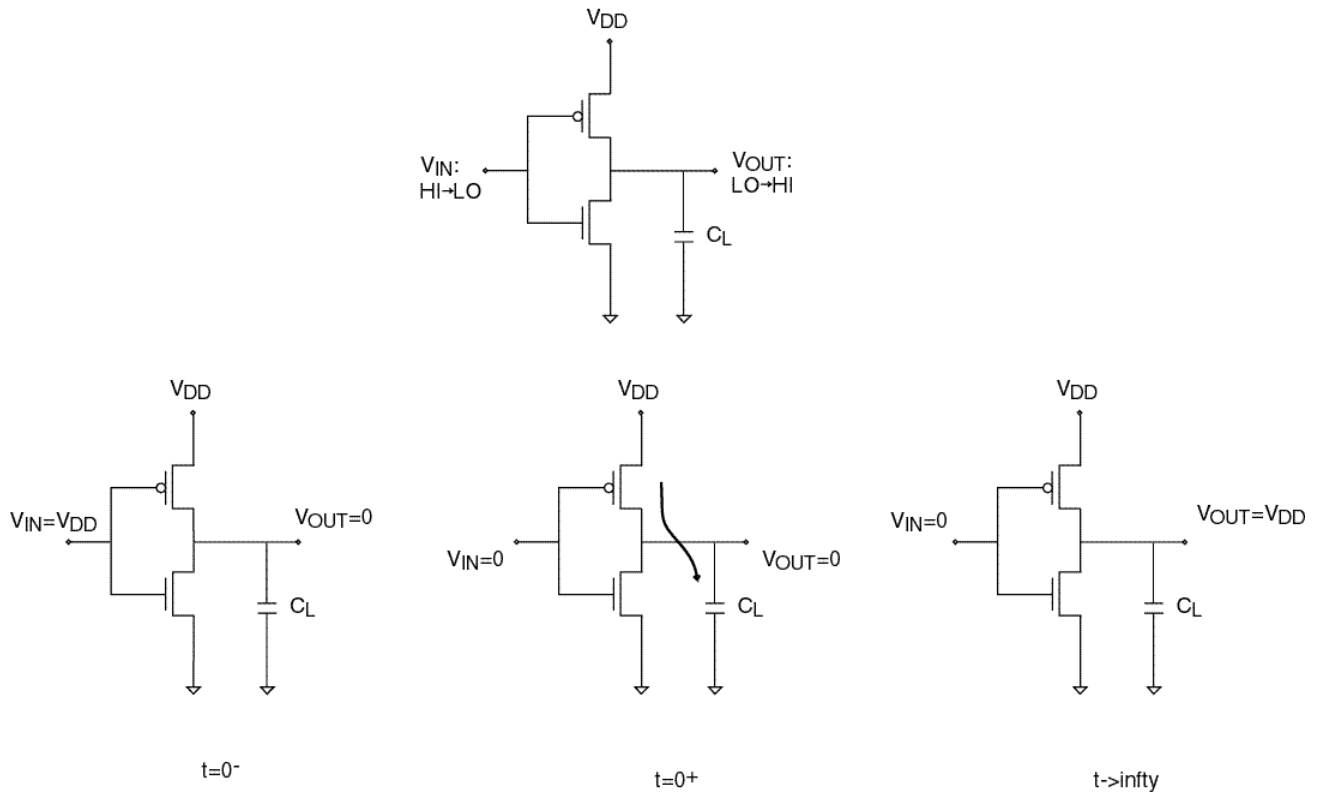

During early phases of discharge, PMOS is saturated and NMOS is cut-off.

Time to charge to *half* of final charge on C_L :

$$t_{PLH} = \frac{\frac{1}{2} \text{ charge on } C_L \text{ @ } t =}{\text{charge current}}$$

CMOS inverter:

Propagation delay high-to-low (contd.)

Charge in C_L at $t = t_p$:

$$Q_L(t = t_p) = C_L V_{DD}$$

Charge Current (PMOS in saturation):

$$-I_{Dp} = \frac{W_p}{2L_p} \mu_p C_{ox} (V_{DD} + V_{Tp})^2$$

Then:

$$t_{PLH} = \frac{C_L V_{DD}}{\frac{W_p}{L_p} \mu_p C_{ox} (V_{DD} + V_{Tp})^2}$$

Key dependencies of propagation delay:

- $V_{DD} \propto t_p$
 - Reason: $V_{DD} \propto Q(C_L) / I_D$, but also $I_D \propto V_{DD}^2$
 - Trade-off: $V_{DD} \propto t_p$ more power consumed.
- $L \propto t_p$
 - Reason: $L \propto I_D$
 - Trade-off: manufacturing cost!

Components of load capacitance C_L :

- *Following logic gates*: must add capacitance of each gate of every transistor the output is connected to.
- *Interconnects wire* that connects output to input of following logic gates
- *Own drain-to-body capacitances*

$$C_L = C_G + C_{\text{wire}} + C_{\text{DBn}} + C_{\text{DBp}}$$

See details in Howe & Sodini Section 5.4.3

What did we learn today?

Summary of Key Concepts

Key features of CMOS inverter:

- No current between power supply and ground while inverter is idle in any logic state
- “rail-to-rail” logic
 - Logic levels are 0 and V_{DD} .
- High $|A_v|$ around the logic threshold
 - Good noise margins.

CMOS inverter logic threshold and noise margins engineered through W_n/L_n and W_p/L_p .

Key dependencies of propagation delay:

- V_{DD} t_p
- L t_p