

# Lecture 22

## Frequency Response of Amplifiers (II)

### VOLTAGE AMPLIFIERS

### Outline

1. Full Analysis
2. Miller Approximation
3. Open Circuit Time Constant

#### **Reading Assignment:**

Howe and Sodini, Chapter 10, Sections 10.1-10.4

# Summary of Key Concepts

- Full Analysis

- Assumes that  $\tau_1 + \tau_2 \approx \tau_1$

$$\omega_{3dB} \approx \frac{1}{\tau_1} = \frac{1}{\mathbf{R}'_{out} C_{\mu} + \mathbf{R}'_{in} C_{\mu} (1 + \mathbf{g}_m \mathbf{R}'_{out}) + \mathbf{R}'_{in} C_{\pi}}$$

- Miller Approximation

- Does not take into account  $\mathbf{R}'_{out}$


$$\omega_3 = \left[ \frac{1}{\mathbf{R}'} \right] \left[ \frac{1}{C_{\pi} + (1 + \mathbf{g}'_{out}) C_{\mu}} \right]$$

- Open Circuit Time Constant (OCT)

- Assumes a dominant pole as full analysis


$$\omega_{3dB} \approx \frac{1}{b_1} = \frac{1}{\mathbf{R}'_{out} C_{\mu} + \mathbf{R}'_{in} C_{\mu} (1 + \mathbf{g}_m \mathbf{R}'_{out}) + \mathbf{R}'_{in} C_{\pi}}$$

# Common Emitter Amplifier

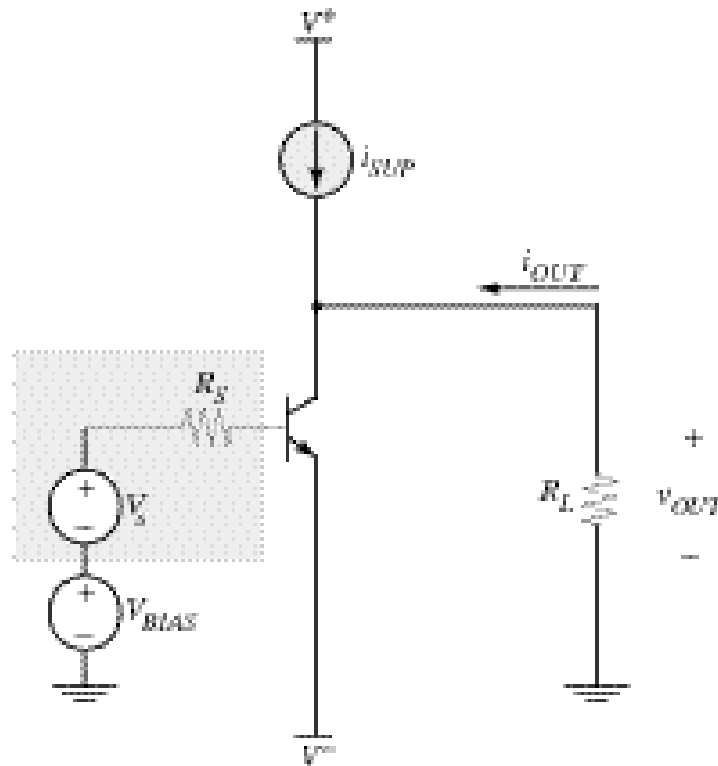


- Operating Point Analysis
  - $v_s=0, R_S = 0, r_o \rightarrow \infty, r_{oc} \rightarrow \infty, R_L \rightarrow \infty$
  - Find  $V_{BIAS}$  such that  $I_C=I_{SUP}$  with the BJT in the forward active region
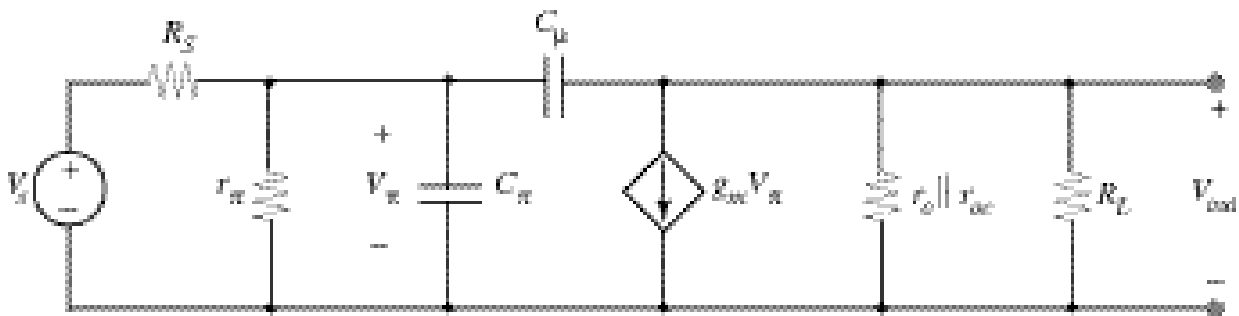
# Frequency Response Analysis of the Common Emitter Amplifier




- Frequency Response
  - Set  $V_{BIAS} = 0$ .
  - Substitute BJT small signal model (with capacitors) including  $R_S$ ,  $R_L$ ,  $r_o$ ,  $r_{oc}$
  - Perform impedance analysis
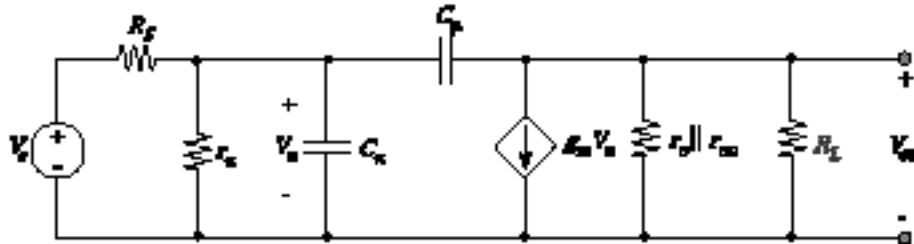
# 1. Full Analysis of CE Voltage Amplifier



Replace source voltage and resistance with source current and conductance

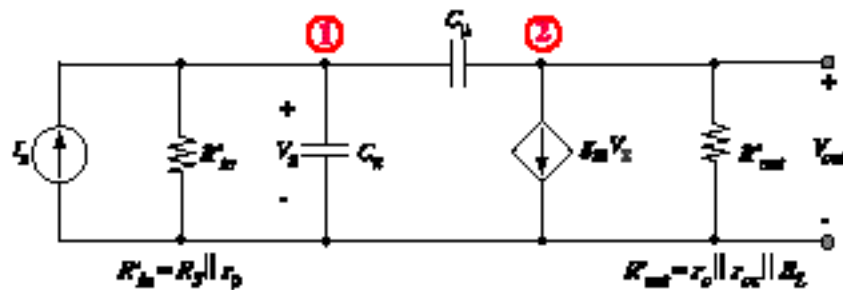

**Node 1:**

$$\mathbf{I}_s = \frac{\mathbf{V}_\pi}{\mathbf{R}'_{in}} + \mathbf{j}\omega\mathbf{C}_\pi \mathbf{V}_\pi + \mathbf{j}\omega\mathbf{C}_\mu (\mathbf{V}_\pi - \mathbf{V}_{out})$$

**Node 2:**

$$\mathbf{g}_m \mathbf{V}_\pi + \frac{\mathbf{V}_{out}}{\mathbf{R}'_{out}} = \mathbf{j}\omega\mathbf{C}_\mu (\mathbf{V}_\pi - \mathbf{V}_{out})$$

## Full Frequency Response Analysis (contd.)

- Re-arranging **2** and obtain an expression for  $V_\pi$
- Substituting it into **1** and with some manipulation, we can obtain an expression for  $V_{out} / I_s$ :

$$\frac{V_{out}}{I_s} = \frac{-R'_{in} R'_{out} (g_m - j\omega C_\mu)}{1 + j\omega(R'_{out} C_\mu + R'_{in} C_\mu + R'_{in} C_\pi + g_m R'_{out} R'_{in} C_\mu) - \omega^2 R'_{out} R'_{in} C_\mu C_\pi}$$

Changing input current source back to a voltage source:

$$\frac{V_{out}}{V_s} = \frac{-g_m R'_{out} \left( \frac{r_\pi}{R_S + r_\pi} \right) \left( 1 - j\omega \frac{C_\mu}{g_m} \right)}{1 + j\omega(R'_{out} C_\mu + R'_{in} C_\mu (1 + g_m R'_{out}) + R'_{in} C_\pi) - \omega^2 R'_{out} R'_{in} C_\mu C_\pi}$$

where  $R'_{in} = R_S \parallel r_\pi$  and  $R'_{out} = r_o \parallel r_{oc} \parallel R_L$


We can ignore zero at  $g_m/C_\mu$  because it is higher than  $f_T$ .

The gain can be expressed as:

$$\frac{V_{out}}{V_s} = \frac{A_v}{(1 + j\omega\tau_1)(1 + j\omega\tau_2)} = \frac{A_v}{(1 - \omega^2\tau_1\tau_2) - j\omega(\tau_1 + \tau_2)}$$

where  $A_v$  is the DC gain and  $\tau_1$  and  $\tau_2$  are the two time constants associated with the capacitors
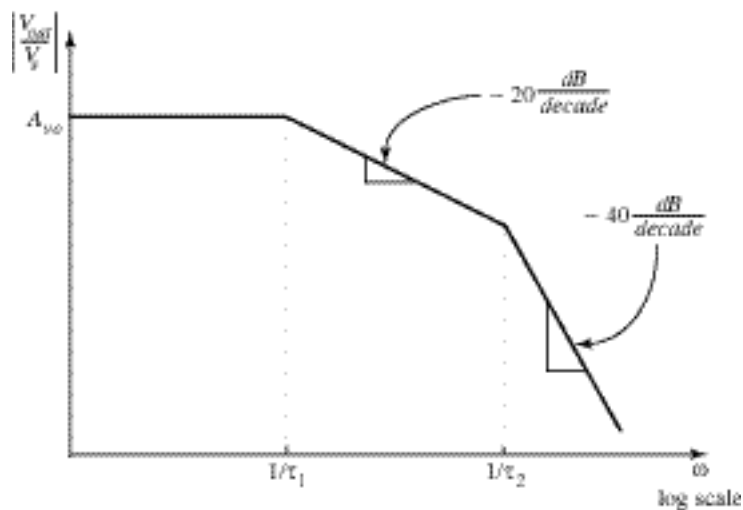
## Denominator of the System Transfer Function



$$\tau_1 + \tau_2 = \mathbf{R}'_{out} \mathbf{C}_\mu + \mathbf{R}'_{in} \mathbf{C}_\mu (1 + \mathbf{g}_m \mathbf{R}'_{out}) + \mathbf{R}'_{in} \mathbf{C}_\pi$$

$$\tau_1 \cdot \tau_2 = \mathbf{R}'_{out} \mathbf{R}'_{in} \mathbf{C}_\mu \mathbf{C}_\pi$$

We could solve for  $\tau_1$  and  $\tau_2$  but is algebraically complex.

- However, if we assume that  $\tau_1 \gg \tau_2 \Rightarrow \tau_1 + \tau_2 \approx \tau_1$ .
- This is a conservative estimate since  $\tau_1$  is actually smaller.


$$\tau_1 \approx \mathbf{R}'_{in} [\mathbf{C}_\pi + \mathbf{C}_\mu (1 + \mathbf{g}_m \mathbf{R}'_{out})] + \mathbf{R}'_{out} \mathbf{C}_\mu$$

Then:

$$\omega_{3dB} = \frac{1}{\tau_1} = \frac{1}{\mathbf{R}'_{in} [\mathbf{C}_\pi + \mathbf{C}_\mu (1 + \mathbf{g}_m \mathbf{R}'_{out})] + \mathbf{R}'_{out} \mathbf{C}_\mu}$$
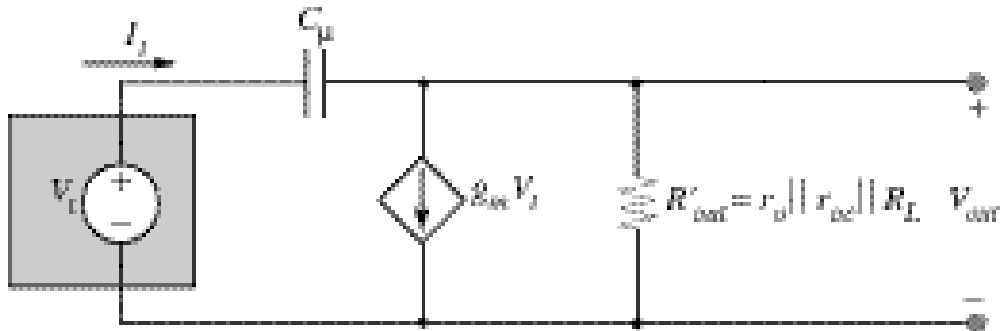
## 2. The Miller Approximation

Effect of  $C_\mu$  on the Input Impedance:



The input impedance  $Z_i$  is determined by applying a test voltage  $V_t$  to the input and measuring  $I_t$ :

$$V_{out} = -g_m V_t R'_{out} + I_t R'_{out}$$

The Miller Approximation assumes that current through  $C_\mu$  is small compared to the transconductance generator

$$I_t \ll |g_m V_t|$$

$$V_{out} \approx -g_m V_t R'_{out}$$

We can relate  $V_t$  and  $V_{out}$  by

$$V_t - V_{out} = \frac{I_t}{j\omega C_\mu}$$


## The Miller Approximation (contd.)

After some Algebra:

$$\frac{V_t}{I_t} = Z_{i,\text{eff}} = \frac{1}{j\omega C_\mu (1 + g_m R'_{\text{out}})} = \frac{1}{j\omega C_\mu (1 - A_{vC_\mu})}$$

The effect of  $C_\mu$  at input is that  $C_\mu$  is “Miller multiplied” by  $(1 - A_{vC_\mu})$


### Generalized “Miller Effect”

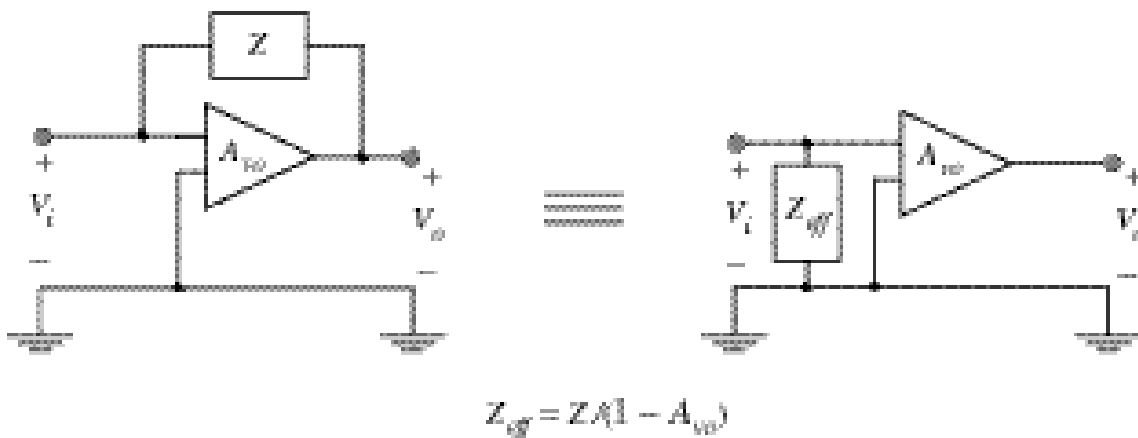

- An impedance connected across an amplifier with voltage gain  $A_{v_o}$  can be replaced by an impedance to ground ... divided by  $(1 - A_{v_o})$
- $A_{v_o}$  is large and negative for common-emitter and common-source amplifiers
- Capacitance at input is magnified.

$$Z_{\text{eff}} = \frac{Z}{(1 - A_{v_o})}$$
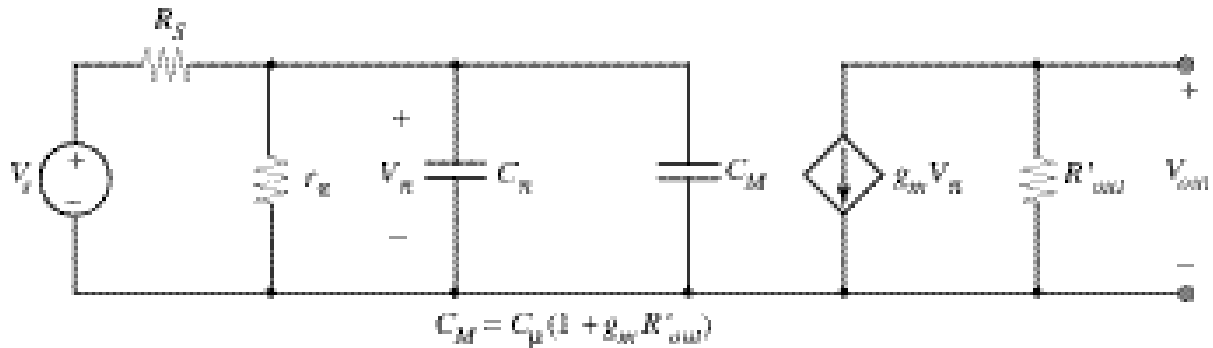
## Frequency Response of the CE Voltage Amplifier Using Miller Approximation



- The Miller capacitance is lumped together with  $C_\pi$ , which results in a single pole low pass filter at the input

$$\frac{V_{out}}{V_s} = -g_m \left( \frac{r_\pi}{r_\pi + R_S} \right) R'_{out} \left[ \frac{1}{1 + j\omega(C_\pi + C_M)(R_S \parallel r_\pi)} \right]$$

- At DC the small signal voltage gain is

$$\frac{V_{out}}{V_s} = -g_m \left( \frac{r_\pi}{r_\pi + R_S} \right) R'_{out}$$

- The frequency at which the magnitude of the voltage gain is reduced by  $1/\sqrt{2}$  is

$$\omega_{3dB} = \frac{1}{(R_S \parallel r_\pi)(C_\pi + C_M)} = \left[ \frac{1}{(R_S \parallel r_\pi)} \right] \left[ \frac{1}{C_\pi + (1 + g_m R'_{out})C_\mu} \right]$$

### 3. Open Circuit Time Constant Analysis

#### Assumptions:

- No zeros
- One “dominant” pole ( $1/\tau_1 \ll 1/\tau_2, 1/\tau_3 \dots 1/\tau_n$ )
- N capacitors

$$\frac{V_{\text{out}}}{V_s} = \frac{A_v}{(1 + j\omega\tau_1)(1 + j\omega\tau_2)\dots(1 + j\omega\tau_n)}$$

The example shows a voltage gain; however, it could be  $I_{\text{out}}/V_s$  or  $V_{\text{out}}/I_s$ .

Multiplying out the denominator:

$$\frac{V_{\text{out}}}{V_s} = \frac{A_v}{1 + \mathbf{b}_1(j\omega) + \mathbf{b}_2(j\omega)^2 + \dots + \mathbf{b}_n(j\omega)^n}$$

$$\text{where } \mathbf{b}_1 = \tau_1 + \tau_2 + \tau_3 + \dots + \tau_n$$

It can be shown that the coefficient  $\mathbf{b}_1$  can be found exactly [see Gray & Meyer, 3<sup>rd</sup> Edition, pp. 502-506]

$$\mathbf{b}_1 = \left( \sum_{i=1}^N \mathbf{R}_{T_i} C_i \right) = \left( \sum_i \tau_{C_{i_o}} \right)$$

- $\tau_{C_{i_o}}$  is the open-circuit time constant for capacitor  $C_i$
- $C_i$  is the  $i^{\text{th}}$  capacitor and  $\mathbf{R}_{T_i}$  is the Thevenin resistance across the  $i^{\text{th}}$  capacitor terminals (with all capacitors open-circuited)

# Open Circuit Time Constant Analysis

## Estimating the Dominant Pole

The dominant pole of the system can be estimated by:


$$b_1 = \tau_1 + \tau_2 + \tau_3 + \dots + \tau_n$$

$$b_1 = \left( \sum_{i=1}^N R_{Ti} C_i \right) \approx \tau_1 = \frac{1}{\omega_1}$$


$R_{Ti} C_i$  is the **open-circuit time constant** for capacitor  $C_i$
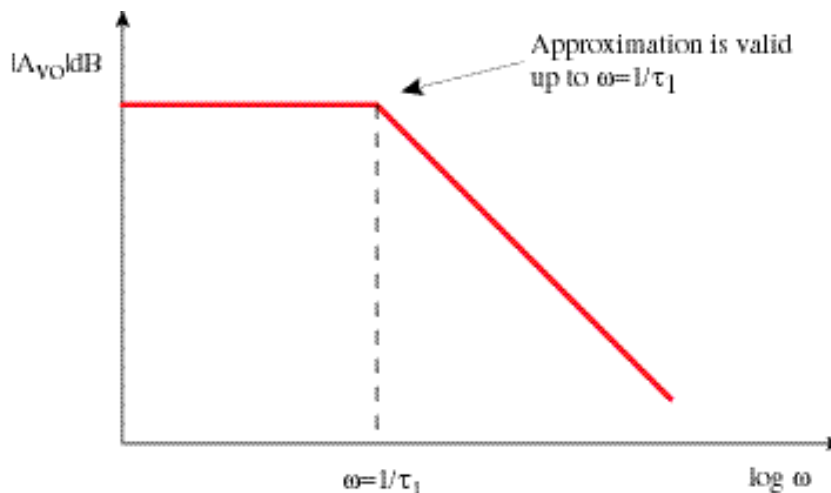
## Power of the Technique:

- Estimates the contribution of each capacitor to the dominant pole frequency separately
- Enables the designer to understand what part of a complicated circuit is responsible for limiting the bandwidth of amplifier
- The approximate magnitude of the Bode Plot is


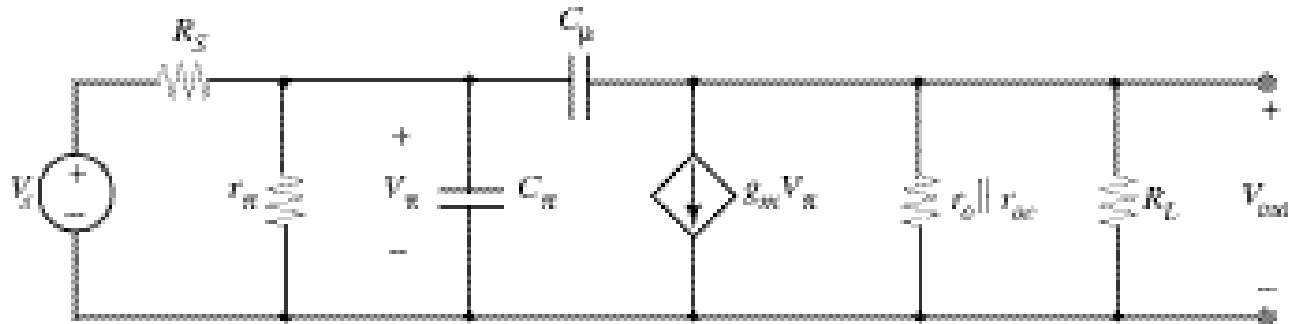
# Common Emitter Amplifier Analysis Using OCT



From the Full Analysis

$$\frac{V_{out}}{V_s} = \frac{-g_m R'_{out} \left( \frac{r_\pi}{R_S + r_\pi} \right) \left( 1 - j\omega \frac{C_\mu}{g_m} \right)}{1 + j\omega (R'_{out} C_\mu + R'_{in} C_\mu (1 + g_m R'_{out}) + R'_{in} C_\pi) - \omega^2 R'_{out} R'_{in} C_\mu C_\pi}$$

where  $R'_{in} = R_S \parallel r_\pi$  and  $R'_{out} = r_o \parallel r_{oc} \parallel R_L$


$$b_1 = R'_{out} C_\mu + R'_{in} C_\mu (1 + g_m R'_{out}) + R'_{in} C_\pi$$

$$\omega_{3dB} \approx \frac{1}{b_1} = \frac{1}{R'_{out} C_\mu + R'_{in} C_\mu (1 + g_m R'_{out}) + R'_{in} C_\pi}$$

# Common Emitter Amplifier Analysis Using OCT—Procedure

1. Eliminate all independent sources [e.g.  $V_s \rightarrow 0$ ]
2. Open-circuit all capacitors
3. Find the Thevenin resistance by applying  $i_t$  and measuring  $v_t$ .

## Time Constant for $C_\pi$

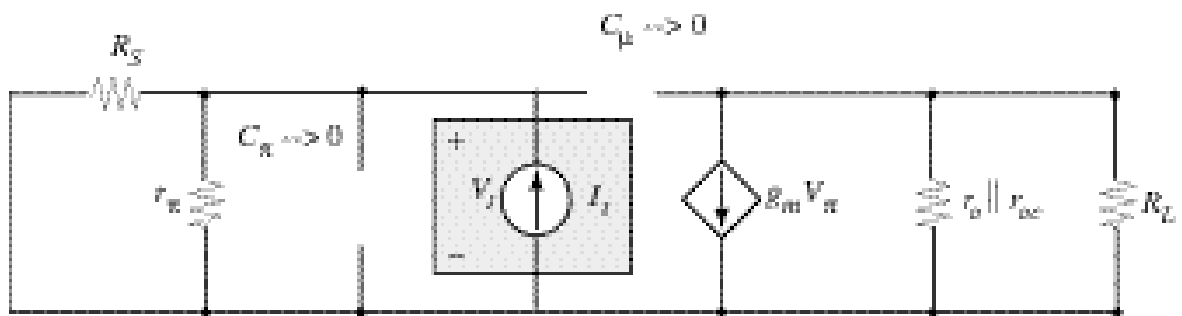


Result obtained by inspection

$$\mathbf{R}_{T\pi} = \mathbf{R}_S \parallel \mathbf{r}_\pi$$


$$\tau_{C_{\pi 0}} = \mathbf{R}_{T\pi} \mathbf{C}_\pi$$

# Common Emitter Amplifier Analysis Using OCT—Time Constant for $C_\mu$

Using the same procedure

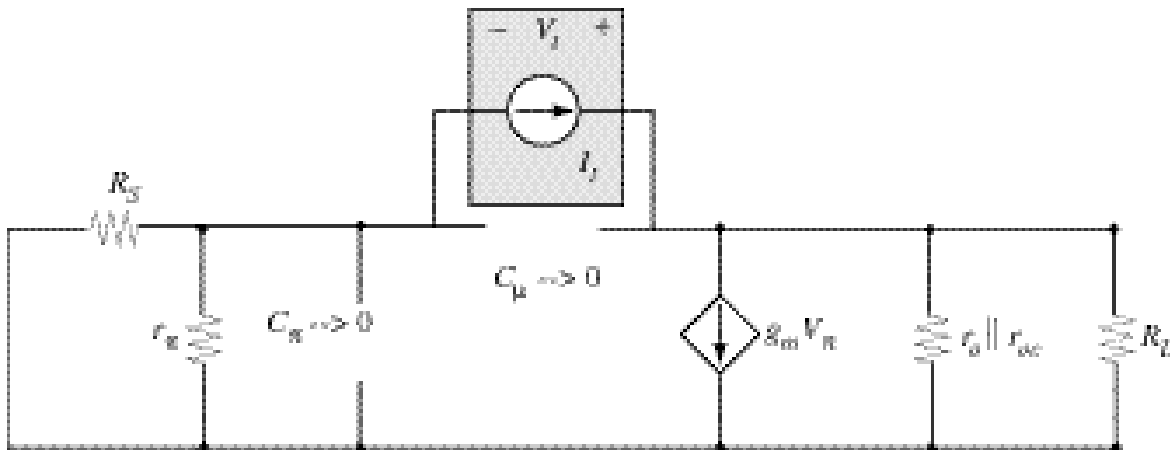

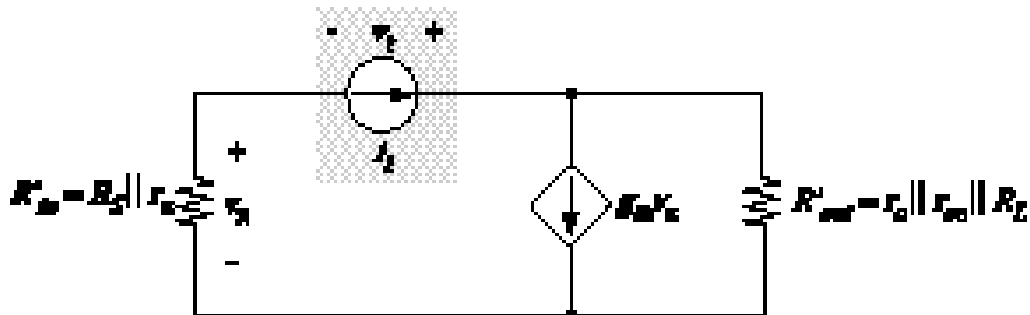Let  $R'_{in} = R_S \parallel r_\pi$  and  $R'_{out} = r_o \parallel r_{oc} \parallel R_L$



$$-i_t = \frac{V_\pi}{R'_{in}}$$

$$i_t = \frac{V_t + V_\pi}{R'_{out}} + g_m V_\pi$$

Eliminate  $V_\pi$ :

$$\frac{V_t}{i_t} = R_{T\mu} = R'_{out} + R'_{in} (1 + g_m R'_{out})$$

$$\tau_{C_{\mu o}} = R_{T\mu} C_\mu = [R'_{out} + R'_{in} (1 + g_m R'_{out})] C_\mu$$

# Common Emitter Amplifier Analysis Using OCT—Dominant Pole

Summing individual time constants

$$\mathbf{b}_1 = \mathbf{R}_{T\pi} \mathbf{C}_\pi + \mathbf{R}_{T\mu} \mathbf{C}_\mu$$

$$\mathbf{b}_1 = \mathbf{R}'_{\text{out}} \mathbf{C}_\mu + \mathbf{R}'_{\text{in}} \mathbf{C}_\mu (1 + \mathbf{g}_m \mathbf{R}'_{\text{out}}) + \mathbf{R}'_{\text{in}} \mathbf{C}_\pi$$

Assume  $\tau_1 \gg \tau_2$

$$\mathbf{b}_1 = \tau_1 + \tau_2 \approx \tau_1$$

$$\mathbf{b}_1 = \mathbf{R}'_{\text{out}} \mathbf{C}_\mu + \mathbf{R}'_{\text{in}} \mathbf{C}_\mu (1 + \mathbf{g}_m \mathbf{R}'_{\text{out}}) + \mathbf{R}'_{\text{in}} \mathbf{C}_\pi$$

$$\omega_{3\text{dB}} \approx \frac{1}{\mathbf{b}_1} = \frac{1}{\mathbf{R}'_{\text{out}} \mathbf{C}_\mu + \mathbf{R}'_{\text{in}} \mathbf{C}_\mu (1 + \mathbf{g}_m \mathbf{R}'_{\text{out}}) + \mathbf{R}'_{\text{in}} \mathbf{C}_\pi}$$

This result is very similar to the Miller Effect calculation  
Additional term  $\mathbf{R}'_{\text{out}} \mathbf{C}_\mu$  taken into account

## Compare the Three Methods of Analyzing the Frequency Response of CE Amplifier

**Full Analysis**—assumes  $\tau_1 + \tau_2 \approx \tau_1$

$$\omega_{3dB} \approx \frac{1}{\tau_1} = \frac{1}{\mathbf{R}'_{out} C_{\mu} + \mathbf{R}'_{in} C_{\mu} (1 + \mathbf{g}_m \mathbf{R}'_{out}) + \mathbf{R}'_{in} C_{\pi}}$$

**Miller Approximation**—does not take into account  $\mathbf{R}'_{out}$

$$\omega_{3dB} = \left[ \frac{1}{\mathbf{R}'_{in}} \right] \left[ \frac{1}{C_{\pi} + (1 + \mathbf{g}_m \mathbf{R}'_{out}) C_{\mu}} \right]$$

**Open Circuit Time Constant**—assumes dominant pole is same as full analysis

$$\omega_{3dB} \approx \frac{1}{b_1} = \frac{1}{\mathbf{R}'_{out} C_{\mu} + \mathbf{R}'_{in} C_{\mu} (1 + \mathbf{g}_m \mathbf{R}'_{out}) + \mathbf{R}'_{in} C_{\pi}}$$

# What did we learn today?

## Summary of Key Concepts

- Full Analysis

- Assumes that  $\tau_1 + \tau_2 \approx \tau_1$

$$\omega_{3dB} \approx \frac{1}{\tau_1} = \frac{1}{\mathbf{R}'_{out} \mathbf{C}_\mu + \mathbf{R}'_{in} \mathbf{C}_\mu (1 + \mathbf{g}_m \mathbf{R}'_{out}) + \mathbf{R}'_{in} \mathbf{C}_\pi}$$

- Miller Approximation

- Does not take into account  $\mathbf{R}'_{out}$

$$\omega_{3dB} = \left[ \frac{1}{\mathbf{R}'_{in}} \right] \left[ \frac{1}{\mathbf{C}_\pi + (1 + \mathbf{g}_m \mathbf{R}'_{out}) \mathbf{C}_\mu} \right]$$

- Open Circuit Time Constant (OCT)

- Assumes a dominant pole as full analysis

$$\omega_{3dB} \approx \frac{1}{b_1} = \frac{1}{\mathbf{R}'_{out} \mathbf{C}_\mu + \mathbf{R}'_{in} \mathbf{C}_\mu (1 + \mathbf{g}_m \mathbf{R}'_{out}) + \mathbf{R}'_{in} \mathbf{C}_\pi}$$