


Problem 1:

$$D, W \gg D.$$

$$(a) R = \frac{W}{\sigma A} = \frac{W L}{\sigma D^2 \pi} \Omega.$$


(b)  $I$  flowing through the device.

$$\vec{H}(r) = ?$$
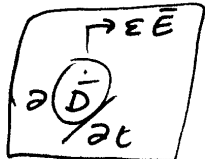
$$\nabla \times \vec{H} = \vec{J} + \frac{\partial \vec{D}}{\partial t} = 0$$


$$\Rightarrow \nabla \times \vec{H} = \vec{J} \rightarrow \oint_{C_1} \vec{H} \cdot d\vec{l} = \int_A \vec{J} \cdot d\vec{a} = I$$

the current flowing in the device

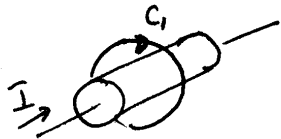

$$d\vec{s} = r d\phi \hat{\phi}$$

$$\Rightarrow \vec{H}(r) = H_{\phi}(r) \hat{\phi}$$

$$\Rightarrow \int_0^{2\pi} H_{\phi}(r) \cdot r d\phi = I$$

$$H_{\phi}(r) \cdot r \cdot (2\pi) = I$$

$$H_{\phi}(r) = \frac{I}{2\pi r}$$

$$\Rightarrow \vec{H}(r) = \hat{\phi} \frac{I}{2\pi r}$$

Problem 2:

$$a) \quad V(t) \Big|_{\omega t < 2 \times 10^{-8}} = \frac{4 \cdot Z_0}{Z_0 + 300} = 1 \quad (\because \text{voltage divider})$$

$$\Rightarrow \quad Z_0 + 300 = 4Z_0$$

$$Z_0 = 300 \Omega$$

$$b) \quad \mu = \mu_0; \quad \epsilon / \epsilon_0 = \epsilon_r \quad v = \frac{1}{\sqrt{\epsilon \mu}} = \frac{c}{\epsilon_{\text{reverse}}} = \frac{1}{1 \times 10^{-8}}$$

$$\Rightarrow v = 1 \times 10^8 \text{ m/s} \rightarrow \frac{1}{\sqrt{\epsilon \mu}} = \frac{c}{\sqrt{\epsilon_r}} = 1 \times 10^8$$

$$\frac{1 \times 10^8}{3 \times 10^8} = \frac{1}{\sqrt{\epsilon_r}} \rightarrow \epsilon_r = 9$$

$$c) \quad L? \quad v = \frac{1}{\sqrt{LC}} \quad Z_0 = \sqrt{\frac{L}{C}}$$

$$(300)^2 = \frac{L}{C} \quad \dots \textcircled{1} \quad (1 \times 10^8)^2 = \frac{1}{LC} \quad \dots \textcircled{2}$$

$$\frac{Z_0}{v} = \sqrt{\frac{L}{C} / \frac{1}{LC}} = L \rightarrow L = \frac{300}{1 \times 10^8} = 3 \times 10^{-6} \text{ H/m}$$

Problem 3:


Sinusoidal Steady State Impedances are sought.

(a) 
$$Z_{th} = \frac{Z_0 (Z_L - j Z_0 \tan k\ell)}{Z_0 - j Z_L \tan k\ell}$$

$$\Rightarrow Z_{th} = \frac{Z_0 (j Z_0 \tan(+\infty))}{j Z_L (+\infty)}$$


$$= \frac{Z_0^2}{Z_L}$$
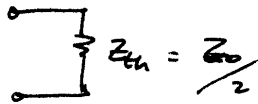
$$\Rightarrow Z_{th} = \frac{Z_0 (-j Z_0 (-\infty))}{-j Z_L (-\infty)} = \frac{Z_0^2}{2 Z_0} = \frac{Z_0}{2}$$



$Z_L = 2 Z_0$

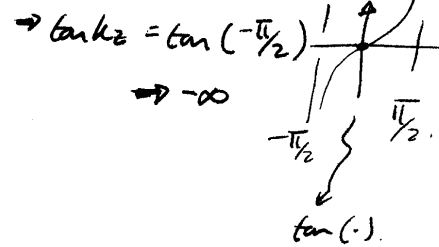$k\ell = \left(\frac{2\pi}{\lambda}\right) \left(\frac{-\lambda}{4}\right) = \frac{-\pi}{2}$



(b)  $Z_L = \frac{1}{j\omega C} = \frac{-j}{\omega C}$

$$\Rightarrow Z_{th} = \frac{Z_0 (-j Z_0 (-\infty))}{-j Z_L (-\infty)} = \frac{Z_0^2 \omega C}{-j} = j Z_0^2 \omega C$$

$\downarrow$  positive  
 $\downarrow$  positive  
 $\downarrow$  positive

