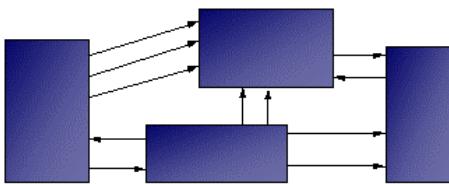


TRANSIENT SIGNALS IN COMPUTERS

Dream World:

Only 1's and 0's
Instantaneous links



Reality:

- Voltages, not 1's and 0's
- Levels and impedances matter
- Delays and transients matter
- Spurious transient waveforms generated at mismatches, can superimpose to flip bits erroneously
- RFI generated and picked up by wires can flip bits
- Ground loops matter


Paradigm:

Use Thevenin equivalent circuits for transmission lines, etc.

L13-1

TEM LINE THEVENIN EQUIVALENT (1)

Basic Equations for Lossless TEM Wires:

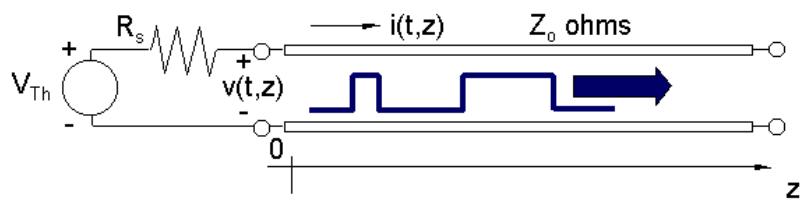

$$v(z,t) = v_+(t - z/c) + v_-(t + z/c)$$

$$i(z,t) = Y_0[v_+(t - z/c) - v_-(t + z/c)]$$

Where:

$$Y_0 = 1/Z_0 = (C/L)^{0.5}$$

This is a "boundary value problem"
The boundary is at $z = 0$

L13-2

TEM LINE THEVENIN EQUIVALENT (2)

Boundary Value Problems, Solution Method:

- 1) Characterize waves in each medium, with unknown coefficients
- 2) Impose boundary condition equations
- 3) Solve equations for unknowns

Example: Given $V_s(t)$:



$$v(z,t) = v_+(t - z/c) + v_-(t + z/c)$$

$$i(z,t) = Y_0[v_+(t - z/c) - v_-(t + z/c)]$$

Assume $v_- = 0$ (no other sources)
Then $v(t, z = 0) = Z_0 i(t, z = 0)$
Yields equivalent circuit; solve it

$$v_+(t, z=0) = (Z_0/[Z_0 + R_s])V_s(t)$$


$$v_+(t, z) = (Z_0/[Z_0 + R_s])V_s(t - z/c)$$

L13-3

TEM LINE THEVENIN EQUIVALENT (3)


Voltages at an Open Circuit:

$$v(z,t) = v_+(t - z/c) + v_-(t + z/c)$$

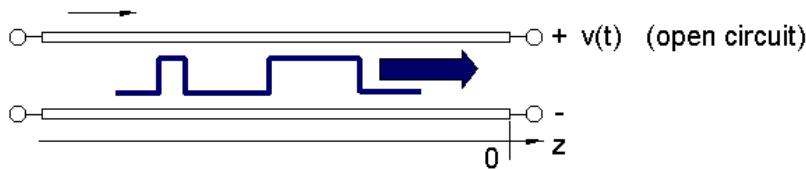

Since: $i(z,t) = Y_0[v_+(t - z/c) - v_-(t + z/c)] = 0$ at $z = 0$
Therefore: $v_+(t) = v_-(t)$ at $z = 0$, and $v(t) = 2v_+(t)$

Thevenin Equivalent for TEM Source:

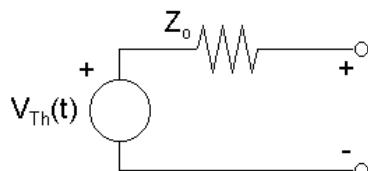

$$v_{\text{open circuit}}(t) = 2v_+(t, z = 0)$$


Therefore:

$$V_{Th}(t) = 2v_+(t, z=0)$$

L13-4

TEM LINE THEVENIN EQUIVALENT (4)

Example—Resistive Load:

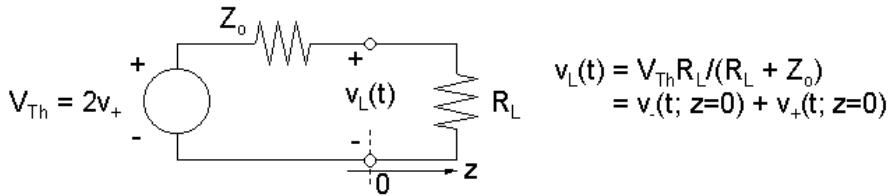



Therefore: $v_-(t; z=0) = v_L(t) - v_+(t; z=0) = 2v_+(t; z=0)[R_L/(R_L + Z_0) - 0.5]$ and
 $\Gamma = v_-/v_+|_{z=0}$ “Reflection Coefficient”
 $\Gamma = 2R_L/(R_L + Z_0) - 1$

$$\Gamma = v_-/v_+|_{z=0} = (R_L - Z_0)/(R_L + Z_0) \quad \begin{cases} = 1 & \text{for } R_L = \infty \\ = 0 & \text{for } R_L = Z_0 \\ = -1 & \text{for } R_L = 0 \end{cases}$$

L13-5

TEM LINE THEVENIN EQUIVALENT (5)

Example, Time-Domain Solution:

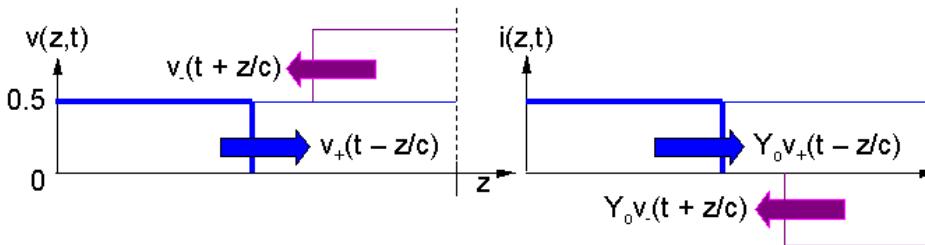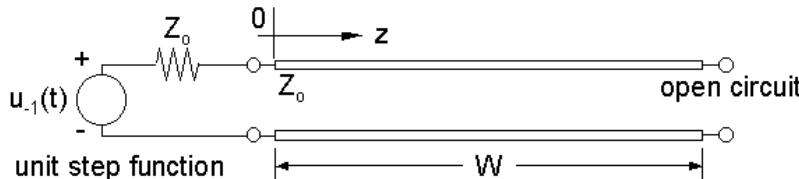



$$v(z,t) = v_+(t - z/c) + v_-(t + z/c) = 0.5[u_-(t - z/c) + u_-(t + z/c - 2W/c)]$$

$$i(z,t) = Y_0[v_+(t - z/c) - v_-(t + z/c)] = 0.5Y_0[u_-(t - z/c) - u_-(t + z/c - 2W/c)]$$

L13-6

CAPACITIVELY TERMINATED TEM LINE

Example—Capacitive Load:

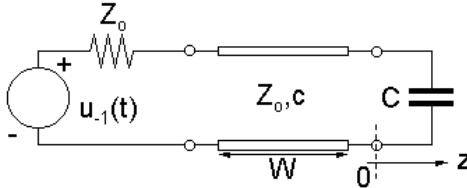
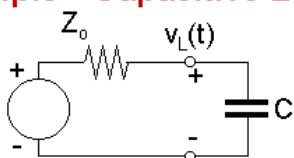


$$V_{Th} = 2v_+(t, z=0)$$

$$= 2[0.5 u_{-1}(t - W/c)]$$

$$v_L(t) = v_-(t; z=0) + v_+(t; z=0)$$
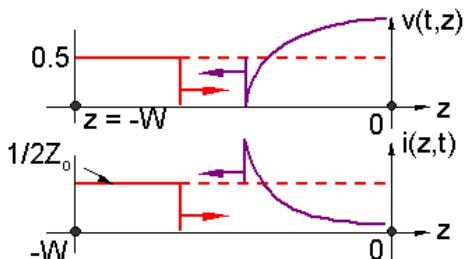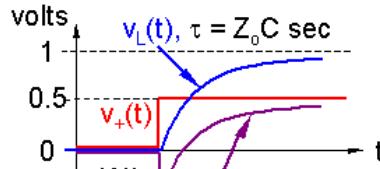
$$\text{Therefore: } v_-(t; z=0) = v_L(t) - v_+(t; z=0)$$





$$i(z, t) = Y_0[v_+(t - z/c) - v_-(t + z/c)]$$

$t = 0+$, short-circuit response
 $t \rightarrow \infty$, open-circuit response


L13-7

DIODE-TERMINATED TEM LINE

Example—Computer Circuit:

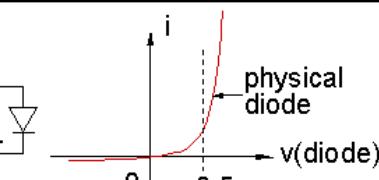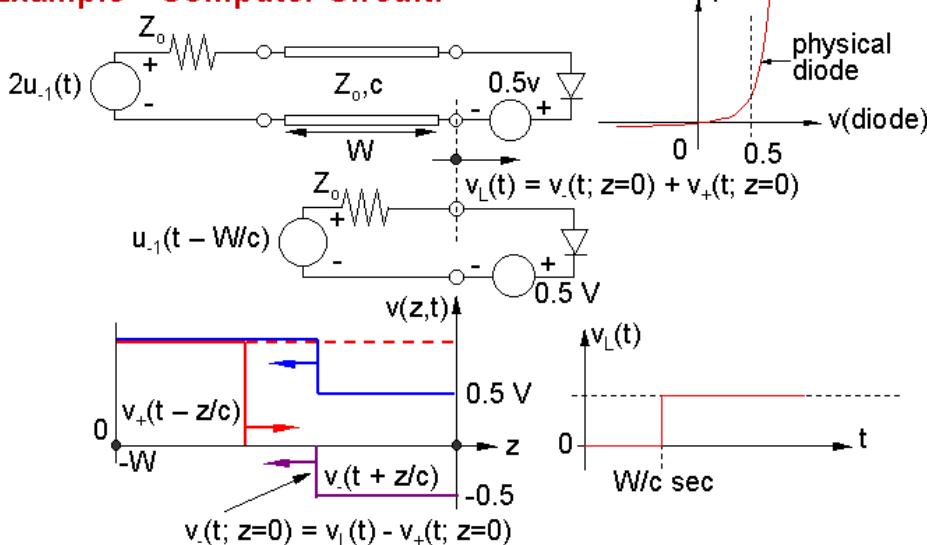

$$v_L(t) = v_-(t; z=0) + v_+(t; z=0)$$

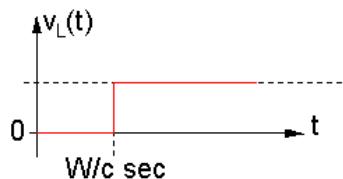

$$v(z, t) = v_+(t - z/c) + v_-(t + z/c)$$


$$i(z, t) = Y_0[v_+(t - z/c) - v_-(t + z/c)]$$

Do we violate KVL, KCL?

L13-8

MISMATCHED SOURCES


Current Source:

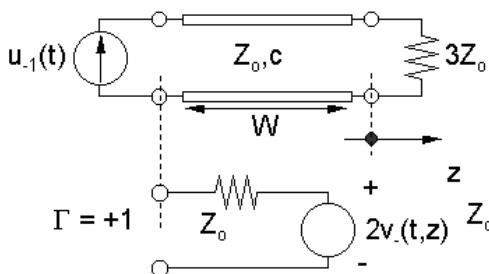

$$\Gamma = (R_L - Z_0)/(R_L + Z_0)$$

$$= (3 - 1)/(3+1) = 1/2$$

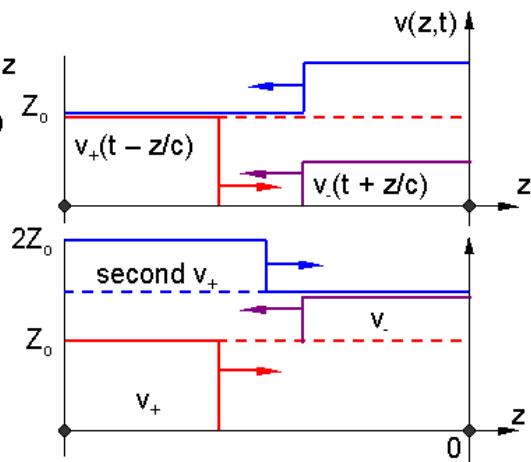Note:
Current source and v_-
superimpose as sources



L13-9