
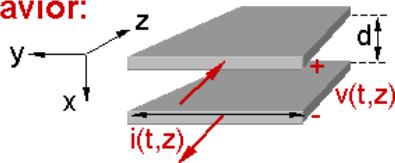


## MICROWAVE CIRCUITS

**Printed Circuits Exhibit R,L,C Behavior:**

Equivalent TEM line circuit:

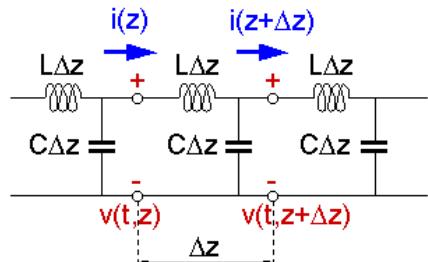

$$\text{"TEM"} \Rightarrow \bar{E} \bullet \hat{z} = \bar{H} \bullet \hat{z} = 0$$

### Difference Equations

$$v(z + \Delta z) - v(z) = -L \Delta z di(z)/dt$$

$$i(z + \Delta z) - i(z) = -C \Delta z dv(z)/dt$$

Limit as  $\Delta z \rightarrow 0$ :

$$dv/dz = -L di/dt$$

$$di/dz = -C dv/dt$$

Let  $v(z,t) = R_e \{ V e^{j\omega t} \}$ :

$$dV(z)/dz = -j\omega L V(z)$$

$$dI(z)/dz = -j\omega C V(z) \Rightarrow$$

### Wave Equation

$$d^2V(z)/dz^2 + \omega^2 LC V(z) = 0$$

L15-1

## TEM SINUSOIDAL STEADY STATE EQUATIONS

**Wave Equation:**  $d^2V(z)/dz^2 + \omega^2 LC V(z) = 0$

**Voltage Solution:**  $V(z) = V_+ e^{-jkz} + V_- e^{jkz}$

$$\begin{aligned} \text{Test solution: } & [(-jk)^2 V_+ e^{-jkz} + (jk)^2 V_- e^{jkz}] + \\ & \omega^2 LC [V_+ e^{-jkz} + V_- e^{jkz}] = 0 \end{aligned}$$

$$\text{Passes test iff: } k^2 = \omega^2 LC$$

**Current I(z):**

$$\text{Since: } \partial V(z)/\partial z = -j\omega L I(z)$$

$$\begin{aligned} \text{Therefore } I(z) &= (1/j\omega L) jk (V_+ e^{-jkz} - V_- e^{jkz}) \\ &= Y_o (V_+ e^{-jkz} - V_- e^{jkz}) \end{aligned}$$

[Characteristic admittance  $Y_o = k/\omega L = \omega(LC)^{0.5}/\omega L = (C/L)^{0.5} = 1/Z_o$ ]

**Transmission Line Equations:**

$$\begin{aligned} V(z) &= V_+ e^{-jkz} + V_- e^{jkz} \\ I(z) &= Y_o (V_+ e^{-jkz} - V_- e^{jkz}) \end{aligned}$$


L15-2

## COMPLEX LINE IMPEDANCE $\underline{Z}(z)$

**Impedance:**

$$\underline{Z}(z) = \underline{V}(z)/\underline{I}(z) = R(z) + jX(z)$$

Resistance      Reactance

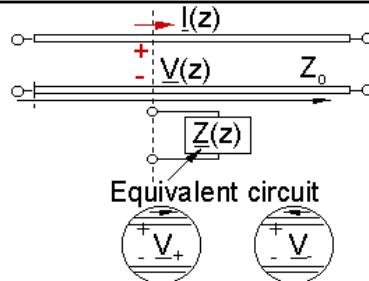

$$\underline{Z}(z) = \underline{V}(z)/\underline{I}(z) = \frac{Z_0 (\underline{V}_+ e^{-jkz} + \underline{V}_- e^{jkz})}{\underline{V}_+ e^{-jkz} - \underline{V}_- e^{jkz}} = Z_0 \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$

**Complex Reflection Coefficient  $\underline{\Gamma}(z)$ :**

$$\underline{\Gamma}(z) = \underline{V}_- e^{jkz} / \underline{V}_+ e^{-jkz} = \underline{\Gamma}_L e^{2jkz} \text{ where } \underline{\Gamma}_L = \underline{\Gamma}(z=0) = \underline{V}_- / \underline{V}_+$$

**Examples:**  $\underline{\Gamma} = 0 \Rightarrow \underline{Z}(z) = Z_0$      $\underline{\Gamma} = +1 \Rightarrow \underline{Z} = \infty$      $\underline{\Gamma} = -1 \Rightarrow \underline{Z} = 0$

L15-3

## GENERAL EXPRESSIONS FOR $Z(z)$

**Complex Reflection Coefficient  $\underline{\Gamma}(z)$ :**

Since  $\underline{Z}(z)/Z_0 = [1 + \underline{\Gamma}(z)]/[1 - \underline{\Gamma}(z)] = \underline{Z}_n(z)$

Therefore:  $\underline{\Gamma}(z) = [\underline{Z}(z) - Z_0]/[\underline{Z}(z) + Z_0]$

**$\underline{Z}(z)$  as a Function of  $Z_L$ ,  $Z_0$ ,  $k$ , and  $z$ :**

Substituting:  $\underline{\Gamma}_L(z) = [\underline{Z}_L - Z_0]/[\underline{Z}_L + Z_0]$

Into: 
$$\begin{aligned} \underline{Z}(z) &= \underline{V}(z)/\underline{I}(z) = Z_0 \frac{\underline{V}_+ e^{-jkz} + \underline{V}_- e^{jkz}}{\underline{V}_+ e^{-jkz} - \underline{V}_- e^{jkz}} \\ &= Z_0 \left[ (e^{-jkz} + \underline{\Gamma}_L e^{jkz}) / (e^{-jkz} - \underline{\Gamma}_L e^{jkz}) \right] \end{aligned}$$

Yields: 
$$\begin{aligned} \underline{Z}(z) &= Z_0 \frac{(\underline{Z}_L + Z_0) e^{-jkz} + (\underline{Z}_L - Z_0) e^{jkz}}{(\underline{Z}_L + Z_0) e^{-jkz} - (\underline{Z}_L - Z_0) e^{jkz}} \\ &= Z_0 \frac{\underline{Z}_L \cos kz - j Z_0 \sin kz}{-j \underline{Z}_L \sin kz + Z_0 \cos kz} \end{aligned}$$

Therefore: 
$$\underline{Z}(z) = Z_0 \frac{\underline{Z}_L - j Z_0 \tan kz}{Z_0 - j \underline{Z}_L \tan kz}$$

L15-4

## EXAMPLES OF $Z(z)$ TRANSFORMATIONS

**Transformation Equation:**  $\underline{Z}(z) = Z_0 \frac{\underline{Z}_L - jZ_0 \tan kz}{Z_0 - j\underline{Z}_L \tan kz}$



**Example—Open Circuit,  $Z_L = \infty$ :**

$$\underline{Z}(-\ell) = -jZ_0 \cot k\ell = -jZ_0/k\ell \text{ for } k\ell \ll 1$$

$$= -j(L/C)^{0.5}/(\omega LC)^{0.5} \ell = 1/j\omega C \ell$$

$$= 0 \text{ when } z = -\lambda/4, -3\lambda/4, \dots$$
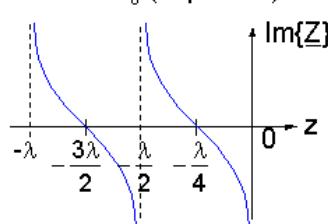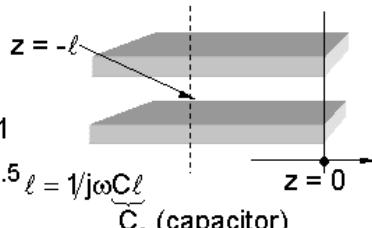
$$= \infty \text{ when } z = 0, -\lambda/2, \dots$$



$$\text{In general: } -j\infty < \underline{Z}(-\ell) < +j\infty$$

(ANY capacitance or inductance at a SINGLE frequency)

L15-5

## MORE EXAMPLES OF $Z(z)$ TRANSFORMATIONS

**Example—Inductive Load,  $Z_L = j\omega L_0$  for  $z = -\lambda/4$ :**

Recall:  $\underline{Z}(z) = Z_0 \frac{\underline{Z}_L - jZ_0 \tan kz}{Z_0 - j\underline{Z}_L \tan kz}$

Since:  $kz = -k\ell = (2\pi/\lambda)/(\lambda/4) = -\pi/2$ , and  $\tan(-k\ell) = -\infty$

Therefore:  $\underline{Z}(z) = Z_0^2/Z_L = (L/C)/(j\omega L_0) = 1/(j\omega CL_0/L) = 1/j\omega C_0$

Note:  $\underline{Z}(z) = 1/j\omega L_0$  if  $\ell = \lambda/2, \lambda, \dots$  ( $\tan(2\pi/\lambda)\lambda = 0$ )

**Example—Transformation of Source Impedances:**


$$\underline{Z}_{Th} = Z_0 \frac{\underline{Z}_s + jZ_0 \tan k\ell}{Z_0 - j\underline{Z}_s \tan k\ell}$$

$$\underline{V}_{Th} = 2\underline{V}_+ = ?$$

$$\underline{V}_A = \underline{V}_s \underline{Z}_A / (\underline{Z}_s + \underline{Z}_A) \text{ where } \underline{Z}_A = jZ_0 \cot k\ell$$


$$= \underline{V}_+ (e^{jk\ell} + e^{-jk\ell}) = 2\underline{V}_+ \cos k\ell$$
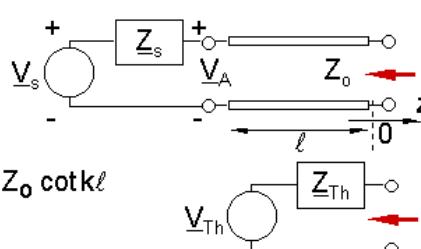
$$\text{Therefore: } \underline{V}_{Th} = \underline{V}_s \underline{Z}_A / [(\underline{Z}_s + \underline{Z}_A) \cos k\ell]$$



L15-6
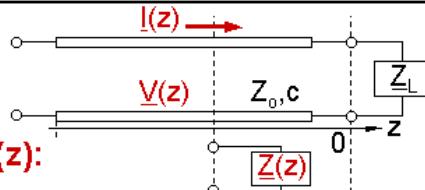
## ALTERNATE APPROACH TO FINDING $\underline{Z}(z)$



**Complex Reflection Coefficient  $\underline{\Gamma}(z)$ :**

$$1) \quad \underline{Z}(z) = \underline{V}(z)/\underline{I}(z) = Z_0 \frac{\underline{V}_+ e^{-jkz} + \underline{V}_- e^{jkz}}{\underline{V}_+ e^{-jkz} - \underline{V}_- e^{jkz}} = \boxed{Z_0 \frac{1 + \underline{\Gamma}(z)}{1 - \underline{\Gamma}(z)} = \underline{Z}(z)}$$

$$2) \quad \underline{\Gamma}(z) = \underline{V}_- e^{+jkz} / \underline{V}_+ e^{-jkz} = \underline{\Gamma}_L e^{2jkz} = \underline{\Gamma}(z) \quad \text{where } \underline{\Gamma}_L = \underline{\Gamma}(z=0) = \underline{V}_- / \underline{V}_+$$

$$3) \quad \underline{\Gamma}_L(z) = [\underline{Z}_L - Z_0] / [\underline{Z}_L + Z_0]$$

$$\underline{\Gamma} = \underline{Z}_n = j \operatorname{Im}\{\underline{\Gamma}\}$$


**$\Gamma$ -Plane Solution Method:**

$$\underline{Z}_L \Leftrightarrow \underline{\Gamma}_L \Leftrightarrow \underline{\Gamma}(z) \Leftrightarrow \underline{Z}(z)$$

(3)

(2)

(1)

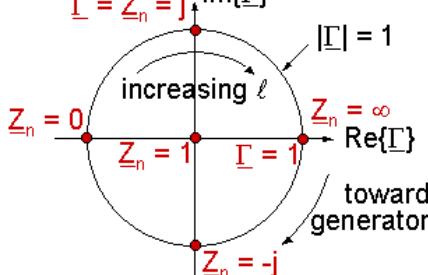


$$\text{Recall: } \underline{Z}_n = \underline{Z}/Z_0$$

L15-7

## GAMMA PLANE $\Rightarrow$ SMITH CHART

**Gamma Plane:**

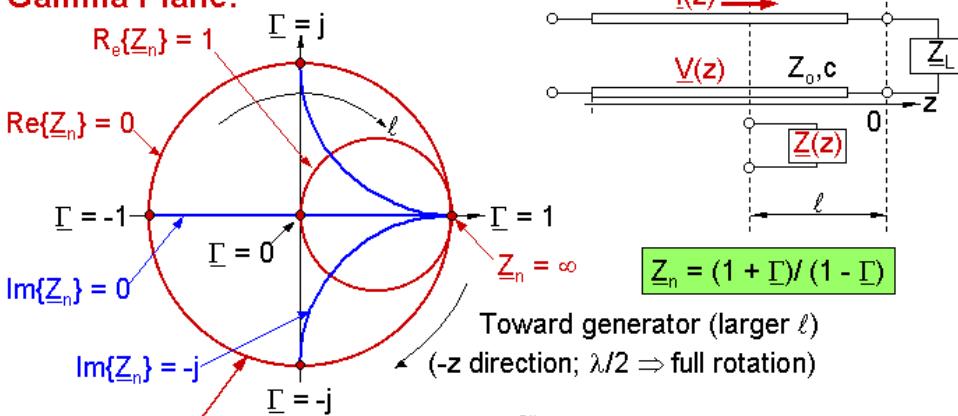


$$\underline{Z}_n = (1 + \underline{\Gamma}) / (1 - \underline{\Gamma})$$

Toward generator (larger  $\ell$ )

(-z direction;  $\lambda/2 \Rightarrow$  full rotation)

**Smith Chart:**

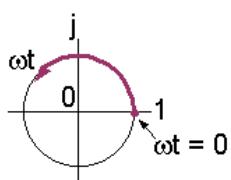

Thus:  $e^{-2jkz}$  goes clockwise as  $\ell \rightarrow \infty$

$$\underline{\Gamma}(z) = \underline{\Gamma}_L e^{2jkz} = \underline{\Gamma}_L e^{-2jk\ell}$$

$$\underline{Z}_L \Leftrightarrow \underline{Z}_{Ln} \Leftrightarrow \underline{\Gamma}_L \Leftrightarrow \underline{\Gamma}(z) \Leftrightarrow \underline{Z}_n(z) \Leftrightarrow \underline{Z}(z)$$

$$\text{Recall: } e^{j\omega t} = \cos \omega t + j \sin \omega t$$

L15-8