

6.014 Electrodynamics

Problem Set 9 Solutions

Available in Tutorials:

April 22, 2002

Problem 9.1

$$\text{Using } V_{Th} = \left(\frac{-jZ_0 \csc kl}{Z_L - jZ_0 \cot kl} \right) V_0 \text{ and } Z_{Th} = Z_0 \left(\frac{Z_L + jZ_0 \tan kl}{Z_L + jZ_0 \tan kl} \right)$$

- a) $Z_{Th} = 100j, V_{Th} = 0$
- b) $Z_{Th} = 80 + 60j, V_{Th} = 0$
- c) $Z_{Th} = 100, V_{Th} = -jV_0$

Problem 9.2

- a) The reflection coefficient at the load is $\Gamma_L = \frac{R_L - Z_0}{R_L + Z_0} = -\frac{1}{3}$. The power absorbed in

the load can be calculated as $P_d = \frac{1}{2Z_0} |V_+|^2 (1 - |\Gamma_L|^2)$ and the incident power at

the load is $\frac{1}{2Z_0} |V_+|^2$, thus the power reflected at the load is

$$\boxed{\frac{1}{2Z_0} |V_+|^2 |\Gamma_L|^2 \Rightarrow \text{ratio power reflected} = |\Gamma_L|^2 = \frac{1}{9}}$$

- b) Now we have $\Gamma_L = \frac{R_L - Z_0}{R_L + Z_0} = -3$. The $\boxed{\text{ratio power reflected} = |\Gamma_L|^2 = 9}$, but this

does not make sense because you are reflecting more than the power incident at the load. Notice that the load is no longer a passive element but rather an active element. Thus the load is adding power to the circuit.

Problem 9.3

- a) $\boxed{D = \frac{I}{4}}$

$$Z_A = \sqrt{Z_0 R} = \sqrt{100 \cdot 200} = \boxed{100\sqrt{2}}$$

- b) In order to match impedences, we start at $Z_{Ln} = (100 + 100j)/100 = 1+j$ on the Smith Chart. We then rotate towards the generator until we reach the R=1 circle in

the lower half of the Smith Chart (we end up at 1-j). The required rotation corresponds to

$$D = \frac{1}{6}$$

Furthermore, $-j\omega L = -jZ_0$

$$\therefore L = \frac{100}{\omega}$$

- c) Since the inductor is connected in parallel, it is easier to look at the admittance (admittances add in parallel). In order to match admittances, we start at $Y_{L1} = 100/(100 + 100j) = (1 - j)/2$. We then rotate towards the generator until we reach the $G=1$ circle on the upper half of the Smith Chart. The required rotation corresponds to

$$D = \frac{1}{4}$$

$$L = \frac{100}{\omega}$$

Problem 9.4

- a) Series RLC resonator: The resonant (natural) frequency of the oscillator is $\omega_0 = \frac{1}{\sqrt{LC}} = 20\pi \times 10^6 \dots (1)$. For the series circuit we know that the decay rate of

the resonator is $\alpha_0 = \frac{R}{2L}$. Furthermore we have $Q = \frac{\omega_0}{2\alpha_0} = \frac{1}{R} \sqrt{\frac{L}{C}} = 100 \dots (2)$.

Thus we have two equations and we solve for L and C. From (1) we find

$L = ((20\pi \times 10^6)^2 C)^{-1}$ and using this relationship in (2) we find

$C = ((100)(20\pi \times 10^6)R)^{-1}$. Substituting $R = 1\Omega$ into the latter we find $C = \frac{1}{2\pi} \text{ nF}$

and $L = \frac{10}{2\pi} \mu\text{H}$.

- b) Parallel R(G)LC resonator: The resonant frequency is unchanged. For the parallel circuit we know that the decay rate of the resonator is $\alpha_0 = \frac{G}{2C}$ (discharging of the capacitor). Furthermore we have $Q = \frac{\omega_0}{2\alpha_0} = \frac{1}{G} \sqrt{\frac{C}{L}} = 100 \dots (2)$. Thus we have two equations and we solve for L and C. From (1) we find $L = ((20\pi \times 10^6)^2 C)^{-1}$ and using this relationship in (2) we find $C = ((100)/(20\pi \times 10^6))G$. Substituting

$G = 1\text{mho}$ into the latter we find $C = \frac{10}{2\pi} \mu\text{F}$ and $L = \frac{1}{2\pi} \text{nH}$. (Note that the conversion from series to parallel resonator is obtained by interchanging the variables as follows $G \leftrightarrow R$ and $L \leftrightarrow C$ (see page 362)).

Problem 9.5

- a) Connect the capacitor in series with the inductor in order to achieve an open-circuit. For $l = I / 4$ and $R=100$, $Z_{Th} = 100$ (the resistance of the lumped circuit, therefore, is 200Ω).

$$\text{Since } Q = \frac{\omega_0 L}{R + R_{Th}},$$

$$L = \frac{Q \cdot R}{\omega_0} = \frac{100 \cdot 200}{2p \cdot 10^7} = \boxed{318\text{mH}}.$$

$$\text{Furthermore, } Q = \frac{1}{R} \sqrt{\frac{L}{C}},$$

$$\therefore C = \frac{L}{(QR)^2} = \boxed{0.79\text{pF}}.$$

b)
$$\boxed{Q_I = \frac{\omega_0 L}{R_I} = 200}$$

$$\boxed{Q_E = \frac{\omega_0 L}{R_E} = 200}$$

c)
$$\mathbf{a} = \mathbf{a}_0 = \frac{\omega_0}{2Q_L} = \frac{2p \cdot 10^7}{200} = \boxed{p \cdot 10^5}$$