




# Pseudo-Doppler Direction Finder

Amanda Ke, Melissa Li, Jimmy Mawdsley
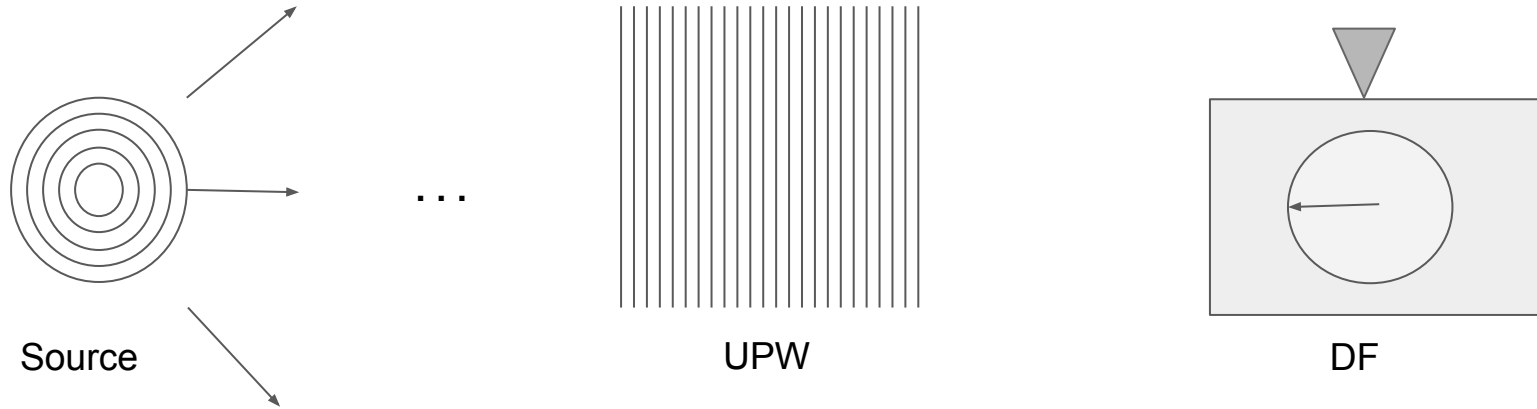
# Background and Project Goals

Determines direction toward signal source (RF, acoustic, etc.)




RDF applications: aerial navigation, tracking, locating pirate radio stations...
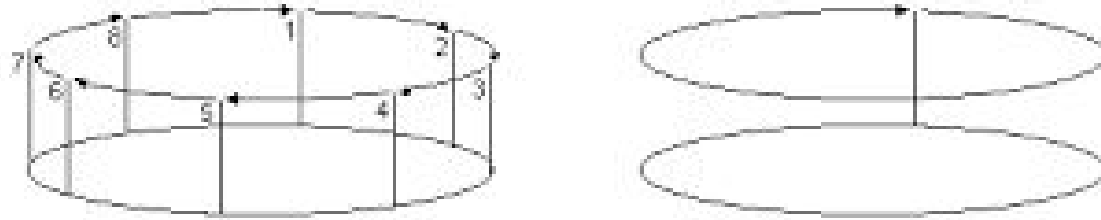
# Pseudo-Doppler Direction Finding

Synthesize a rotating effective antenna by switching between elements in an array

Effective antenna moves toward/away from source  $\rightarrow$  Doppler shift





Typically use a soft-switching profile to reduce phase discontinuities

# Motivation


Originally idea: Radio Direction Finder (RDF) operating in FM band...

Same principle of operation holds for audio frequency

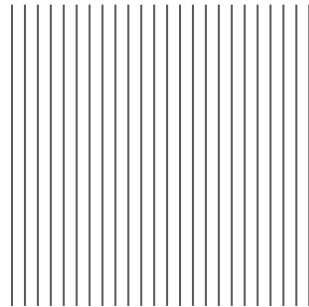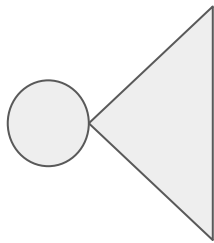Analog solutions for most of the functionality




$c = 340 \text{ m/s}$

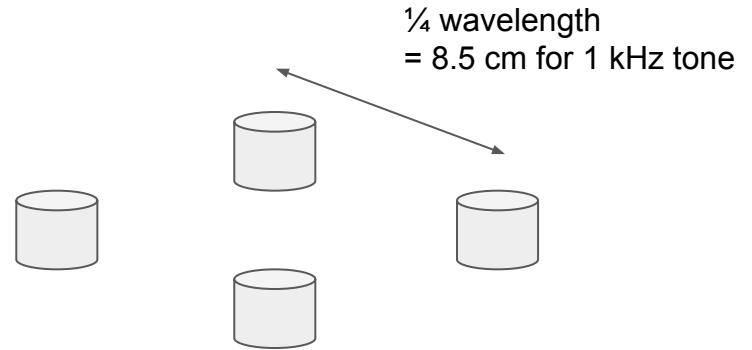


# High-Level Block Diagram

## Pseudo-Doppler DF

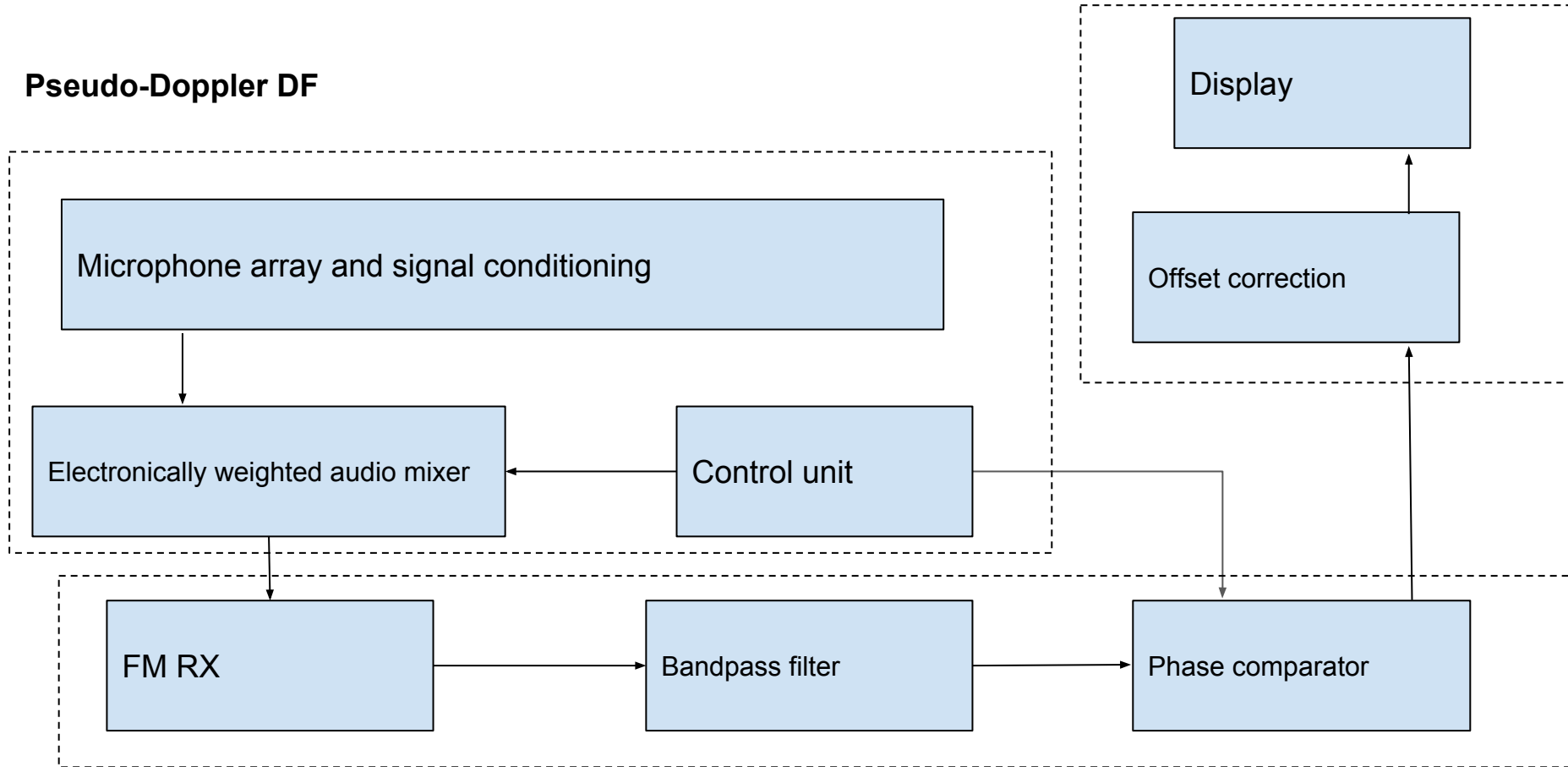


# Overview: Signal Acquisition Module

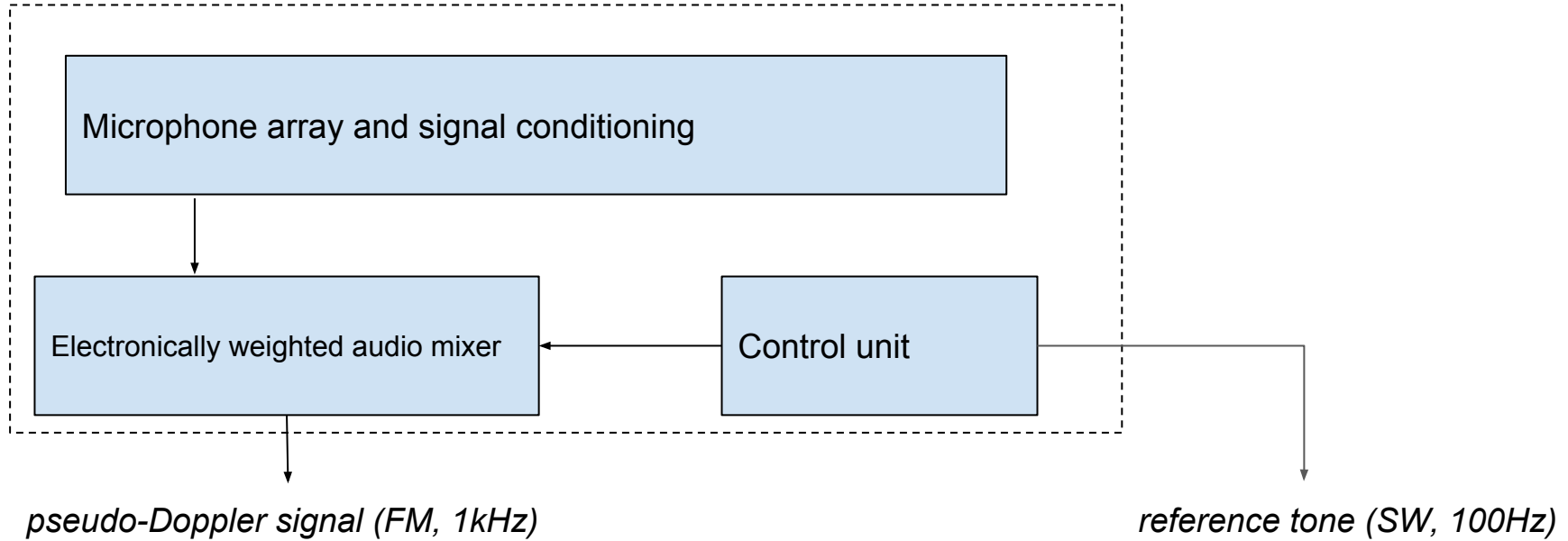

# Close-Up: Signal Acquisition Module

## Signal Conditioning - Block Diagram

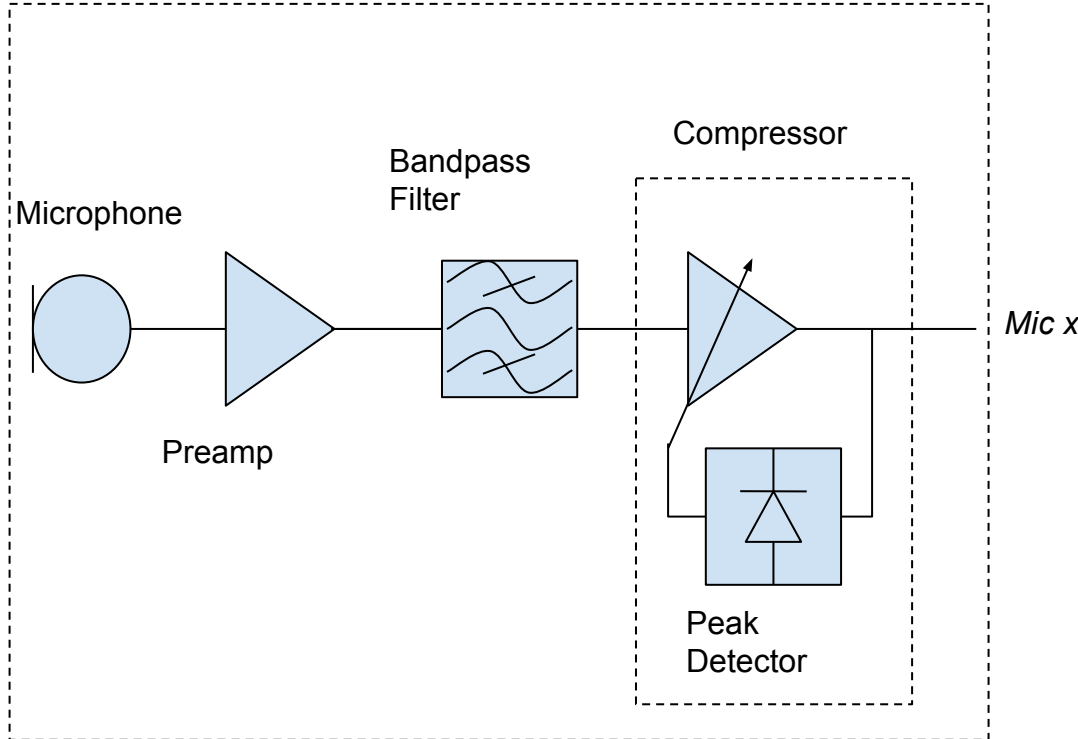


### Considerations:

- Why is AGC needed?
- Why is BPF needed?

# Close-Up: Signal Acquisition Module

## Signal Conditioning - Implementation

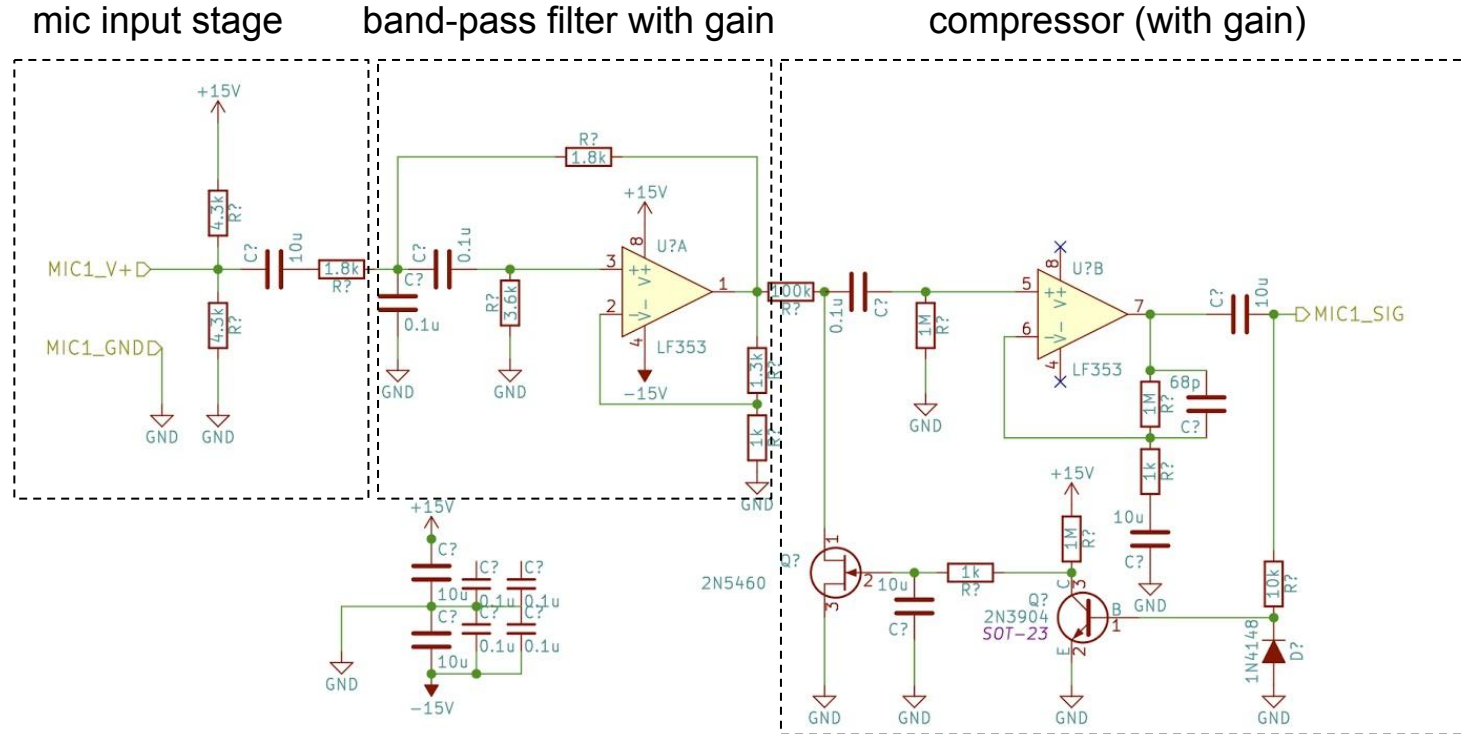


Complications with multipath?



# Close-Up: Signal Acquisition Module

## Control Unit - Block Diagram

*reference  
sinusoid*

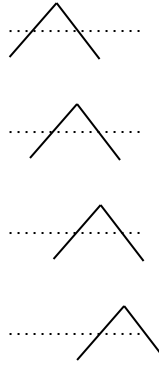

*control bias  
waveforms*


Considerations:

- Shape of bias waveform?
- How to make quadrature?


Implementation: reference sinusoid → square wave → triangle (zero offset) → comparator → quadrature

# Close-Up: Signal Acquisition Module
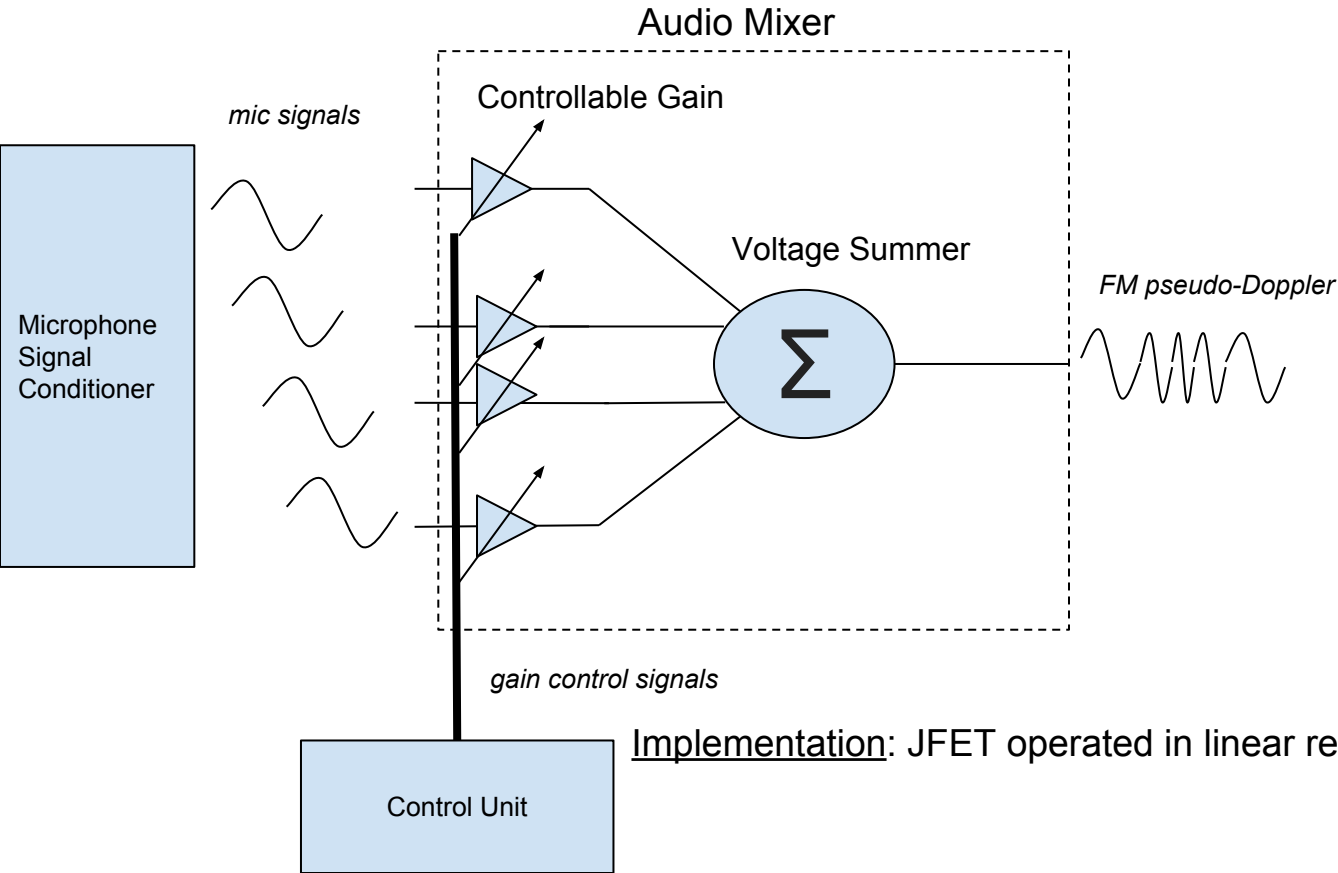
## Voltage Controlled Audio Summer - Block Diagram




# Phase Extraction

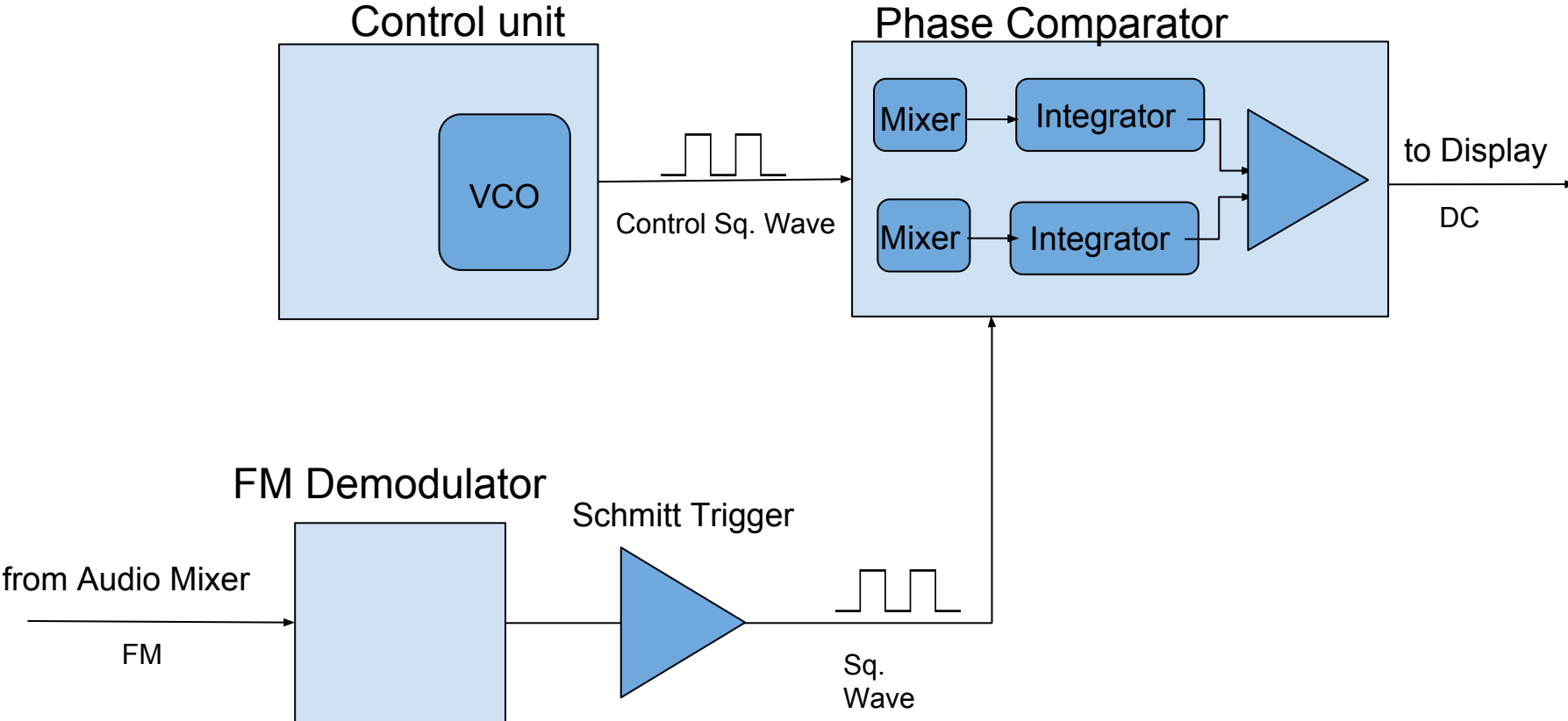


# FM Demodulator

1st-order Phase locked loop

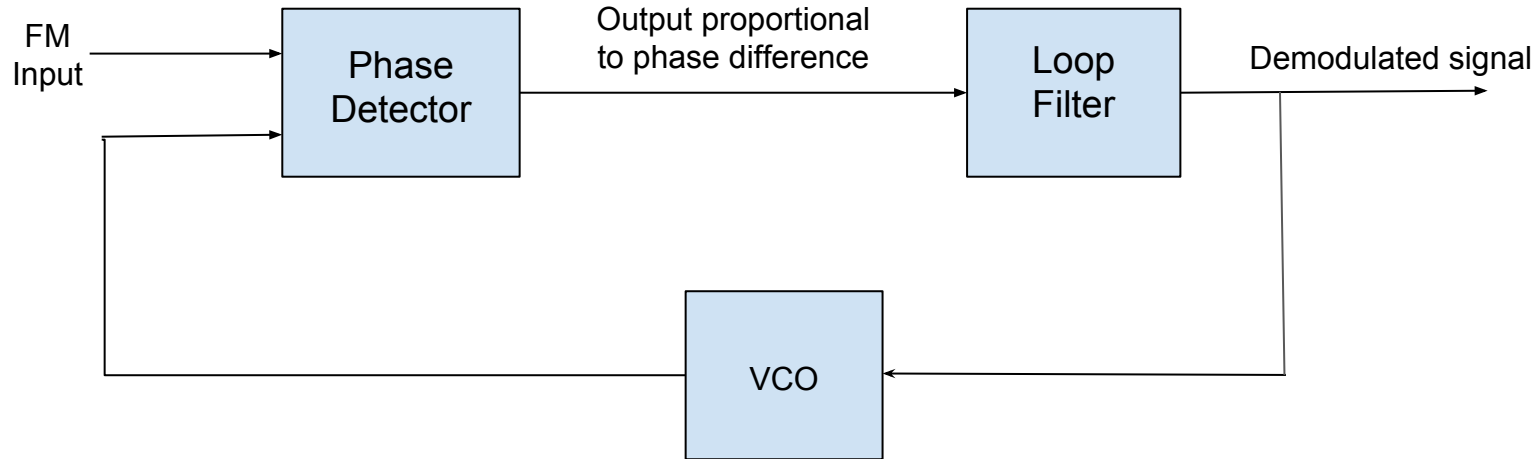

# Close-Up: FM Demodulator



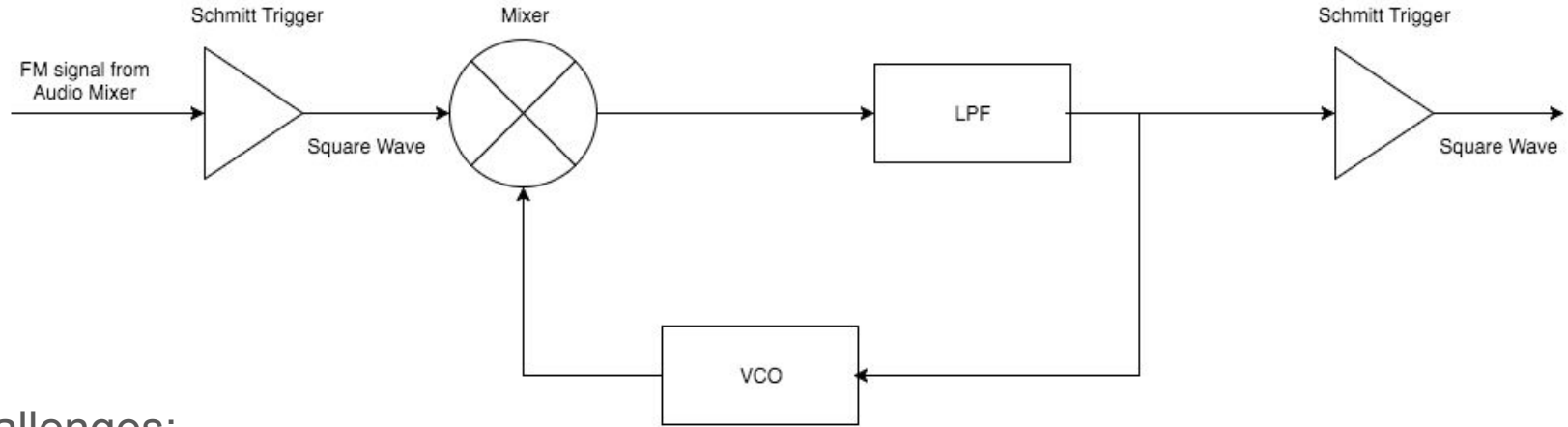


## Challenges:


- Tuning the low pass filter
- Jitter

# Gilbert Cells and Mixing

## Schematic

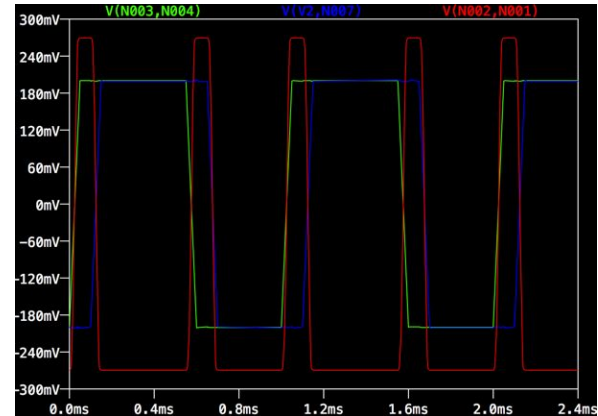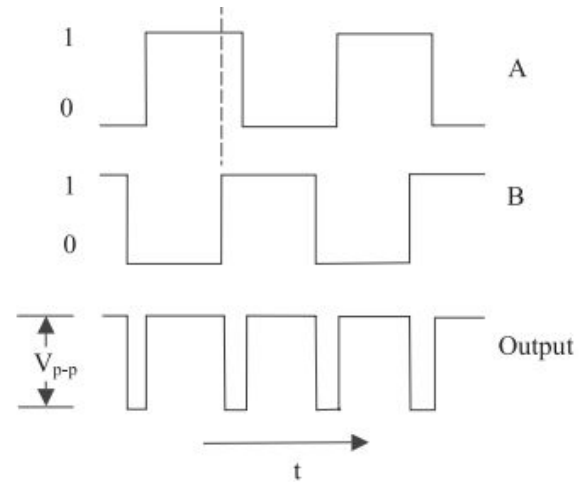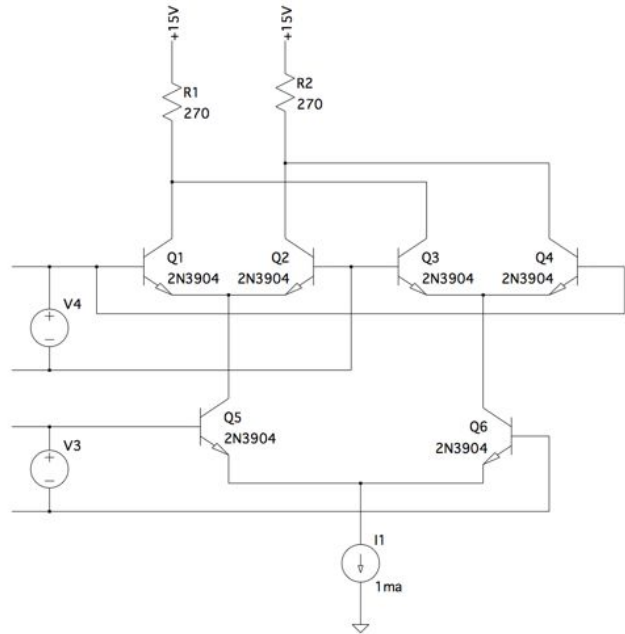


# Phase comparison

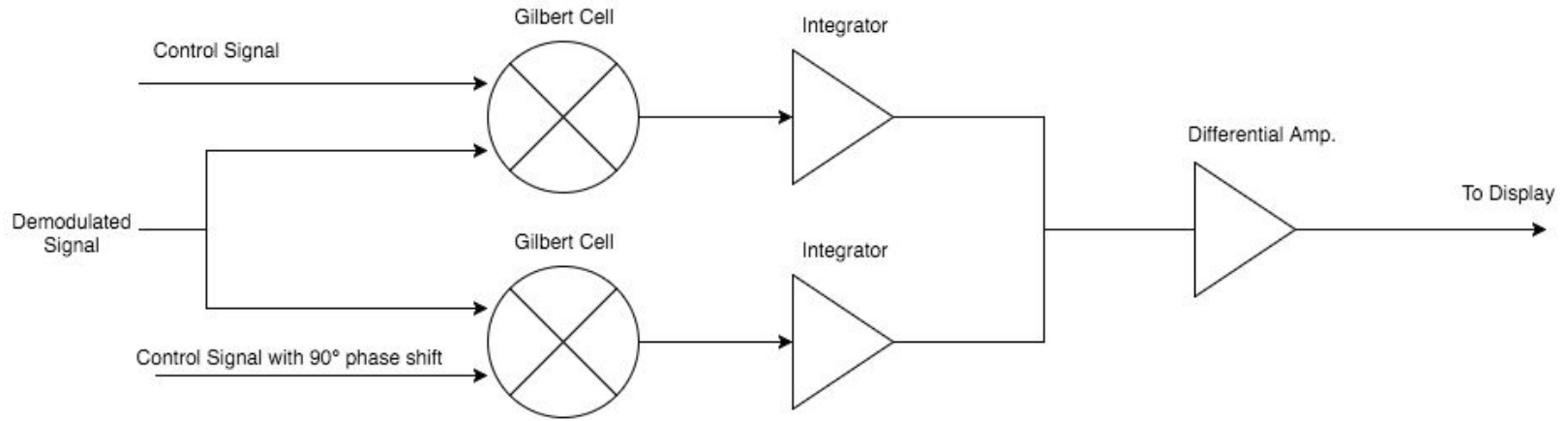

## Challenges:



- Asymmetry of components

# Display

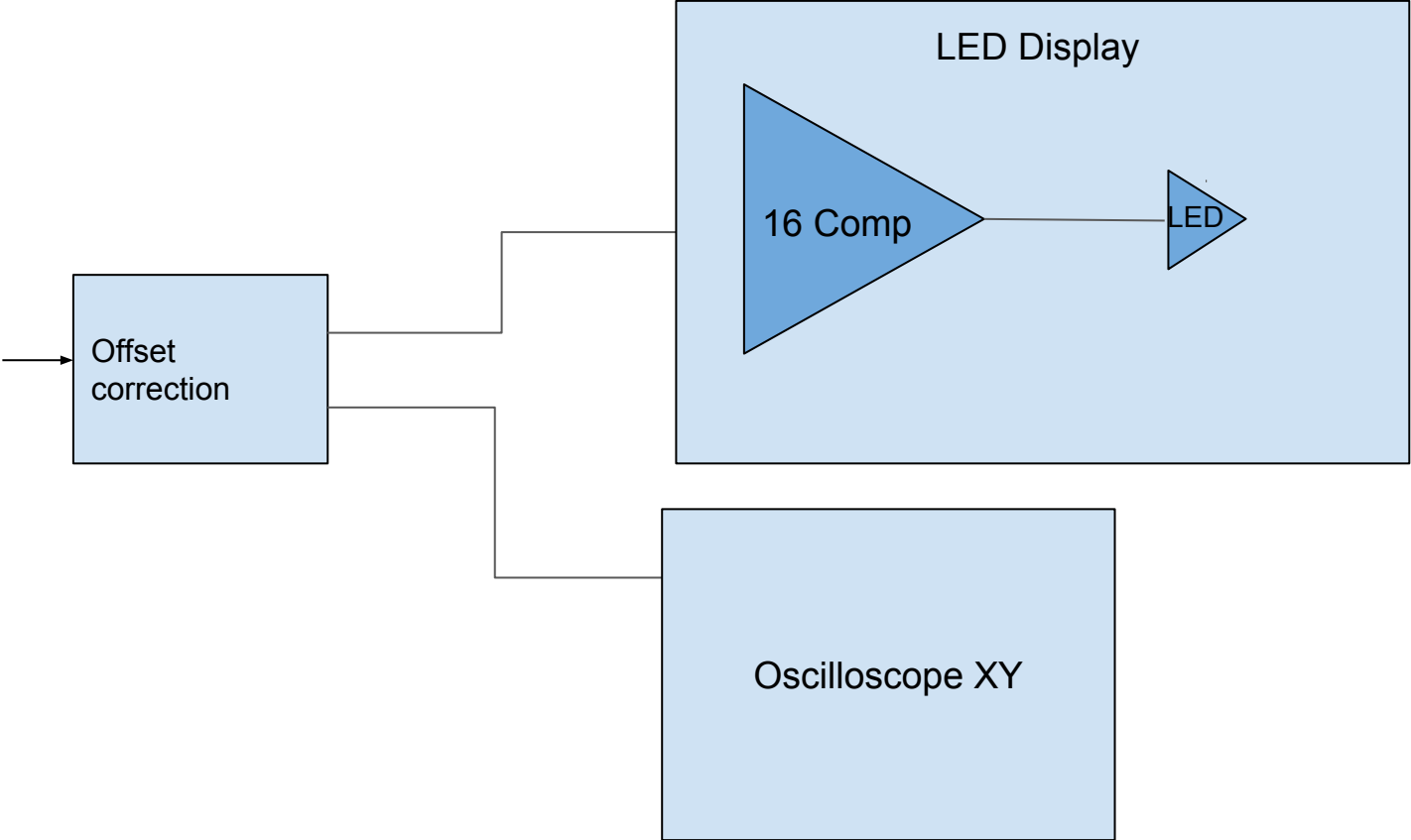



# LED Display

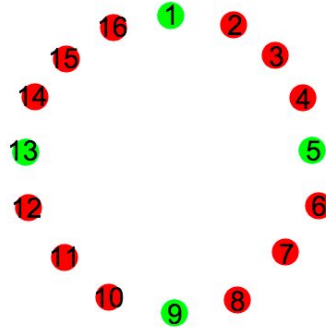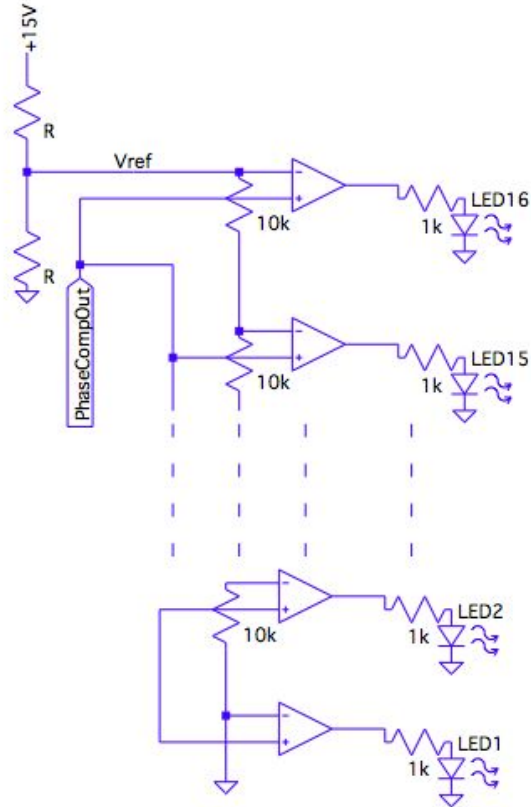


## Negative Terminals

- $0, V_{ref}/15, 2V_{ref}/15, \dots, 14V_{ref}/15, V_{ref}$


## Positive Terminals

- All connected at phase comparator output

# Oscilloscope XY Display

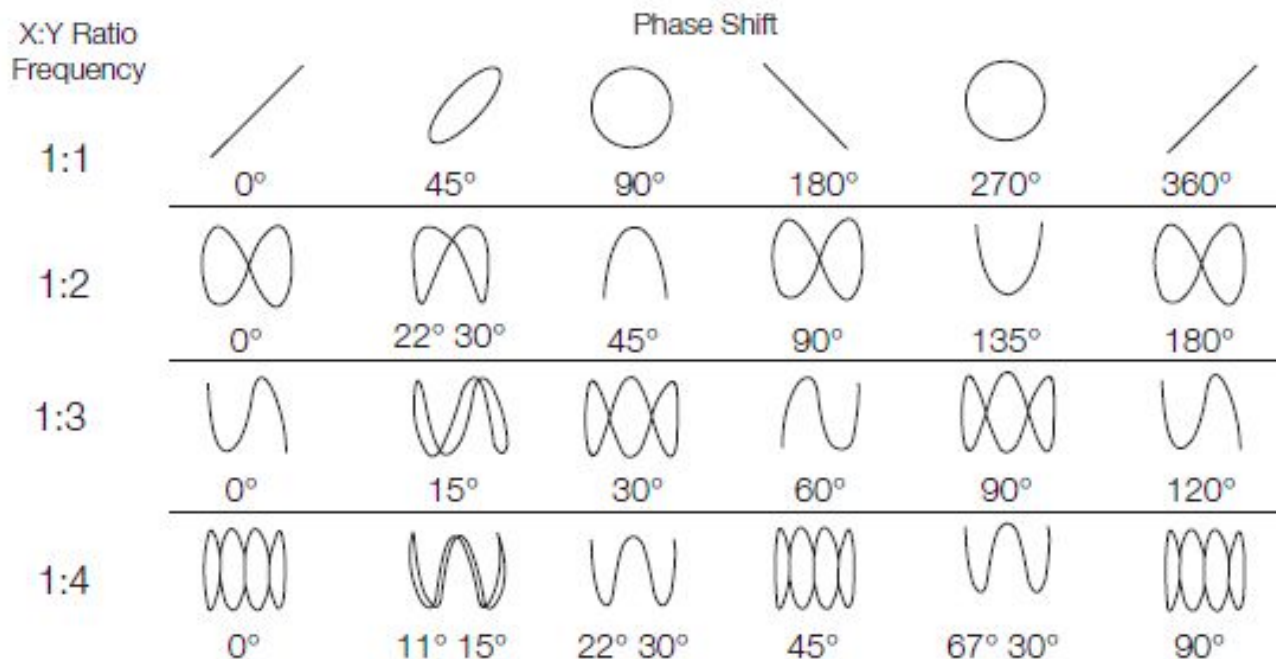

# Oscilloscope XY Display

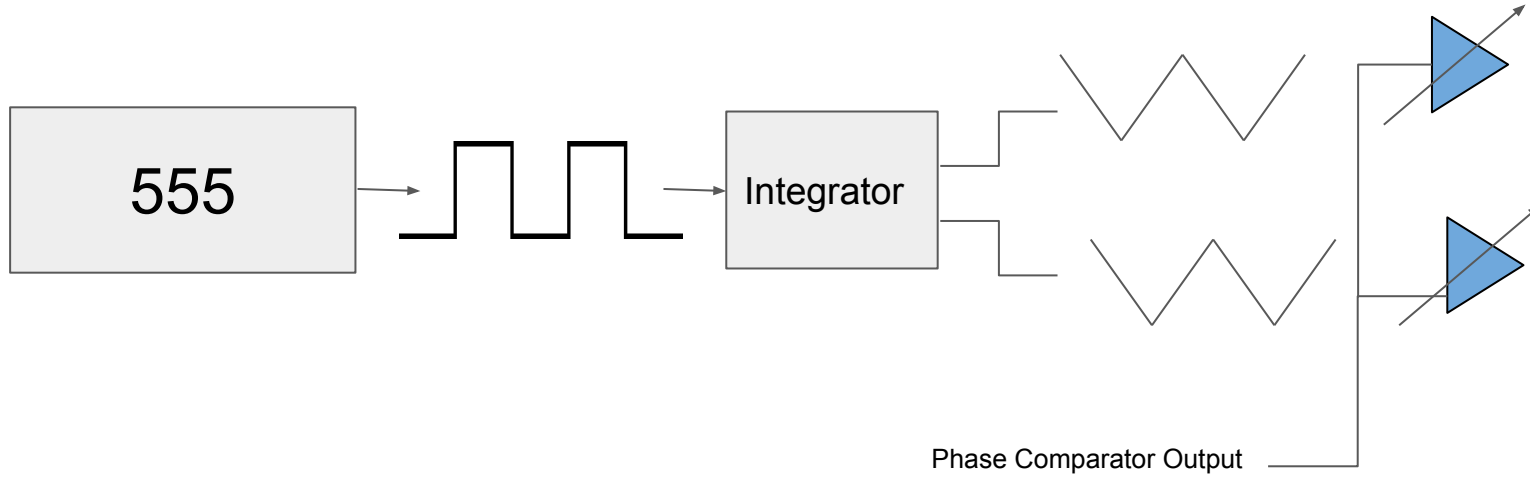

# Schedule

Week of	Tasks
April 11	Begin building individual modules
April 18	Continue building individual modules. Begin integrating/debugging modules
April 25	Continue integrating/debugging modules. Begin working on stretch goals
May 2	Continue working on stretch goals. Demonstration of complete system

# Concluding Remarks

Expected outcome:

- Complete PD-DF system that can point toward speaker with good accuracy
- Extensions: lay out a PCB, redesign for RF, more elaborate interface

Next steps:

- Finish up individual modules (design, construction, test)
- Test interconnected modules



**Questions?**