





- BJT Circuits & Limitations
- LTspice

Tue 2/18: Mon schedule
Lab: Sun closed
Mon 1-11:45pm
Handouts:
lecture notes,
pset 2,
lab 2

Acknowledgements:



Neamen, Donald: Microelectronics Circuit Analysis and Design, 3rd Edition

General Configuration

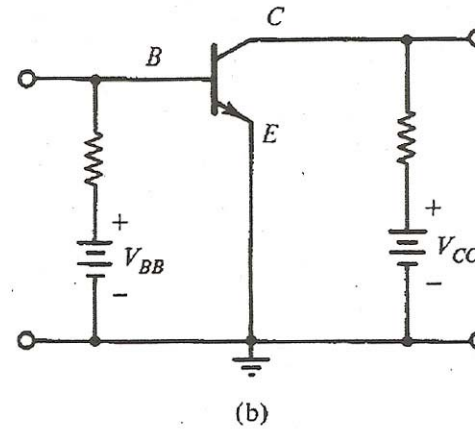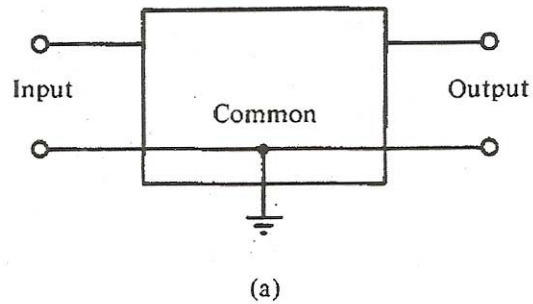


Common
Emitter

Common
Collector

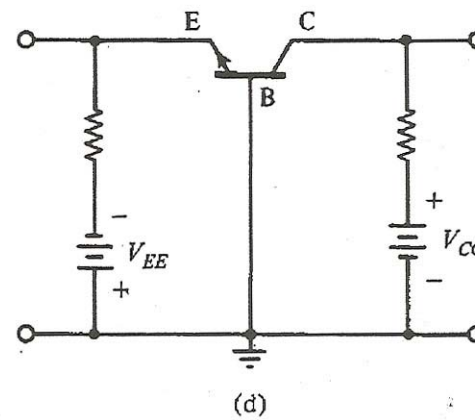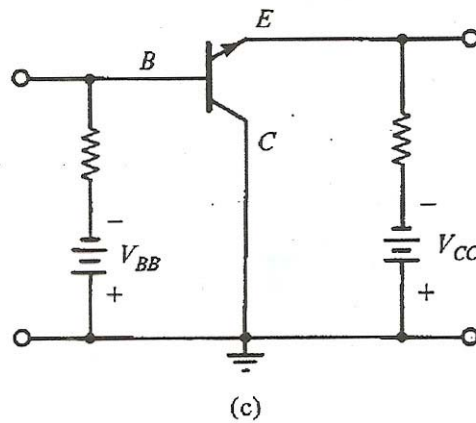


Common
Base


Transistor Configurations

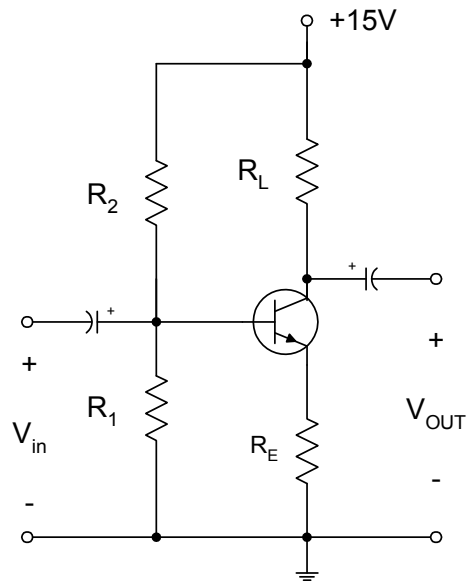

[a] Common Emitter Amplifier

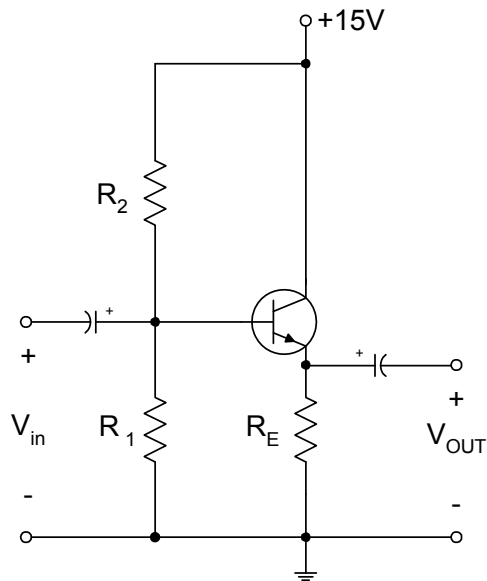


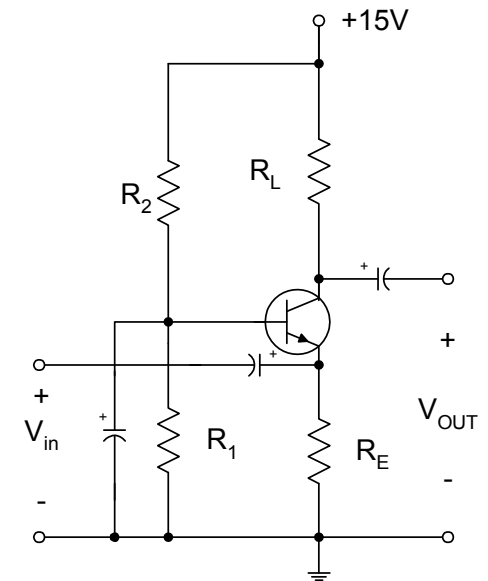[b] Common Collector [Emitter Follower] Amplifier



[c] Common Base Amplifier


Base Current – Resistor Divider

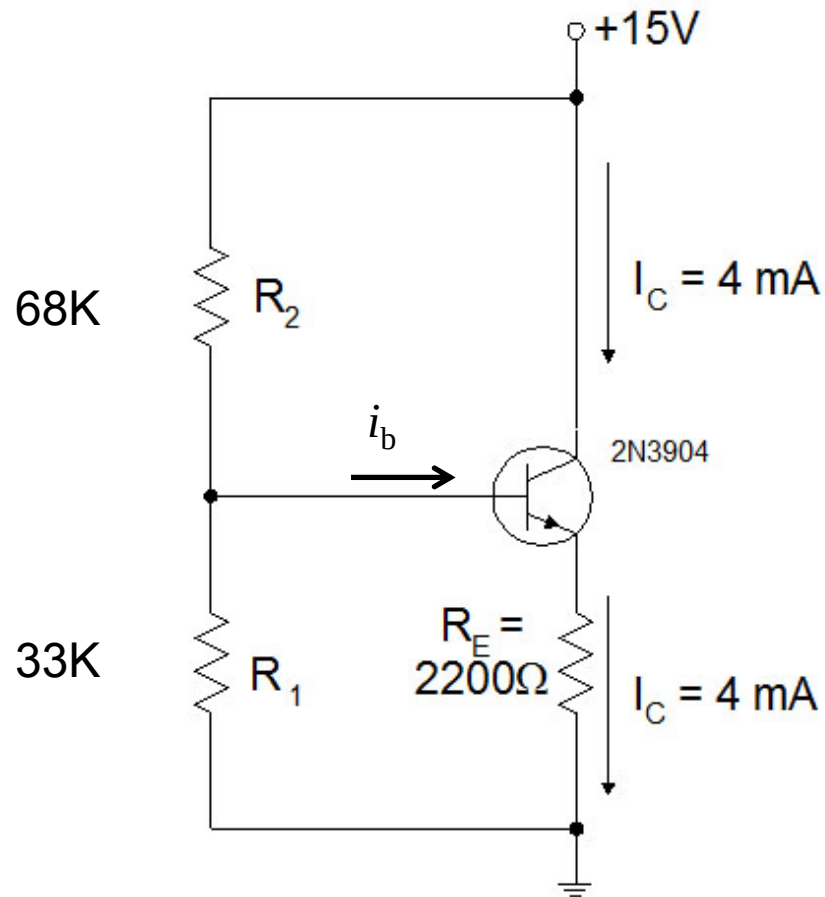

I_C	β_F
3.7 mA	50
4.0 mA	100
4.2 mA	200
4.3 mA	300
$\Delta I_C = 0.6\text{ mA}$	

Make i_b small compared to the current through R_2

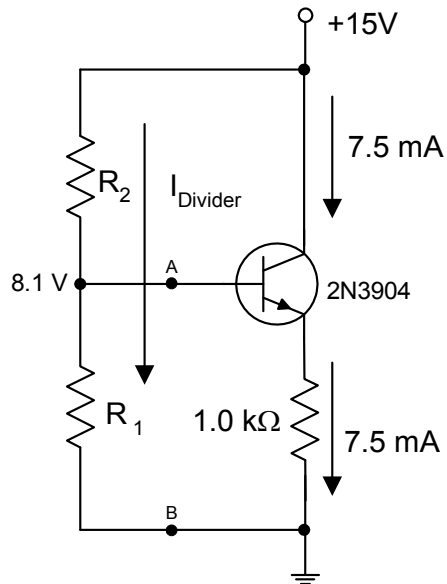Common Collector – Emitter Follower Biasing




- With $R_1 = 24\text{k}\Omega$, $R_2 = 16\text{k}\Omega$, the current through the voltage divider is $15 \div [40\text{k}\Omega] = 375\text{ }\mu\text{A}$.
- The 75 μA base current is 20% of 375 μA .
- With $R_1 = 2\text{k}\Omega$, will need a divider current that is $\sim 4.1\text{ mA}$. (75 μA is only $\sim 2\%$ of 4.1 mA, which is negligible)
- The voltage drop across R_2 will be $[15\text{ V} - 8.1\text{ V}] = 6.9\text{ V}$; $R_2 = 1.7\text{ k}\Omega$
- But input impedance will be low = $\sim 890\Omega$
- Use bootstrapping configuration

= 24.4 k Ω (use 24 k Ω)

Common Emitter – Hybrid π

TRANSISTOR AMPLIFIER CONFIGURATIONS WITH HYBRID- π EQUIVALENT CIRCUITS


COMMON EMITTER AMPLIFIER

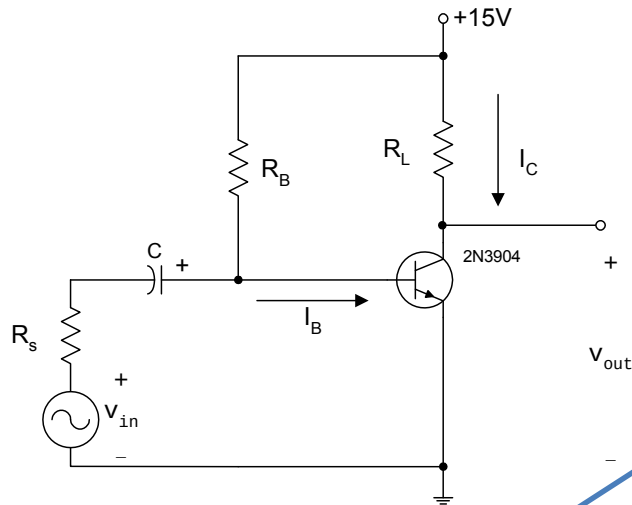

$$\beta_o = g_m r_\pi$$

$$g_m = \frac{I_{CQ}}{V_{TH}}$$


$$V_{TH} = 26\text{mV}$$

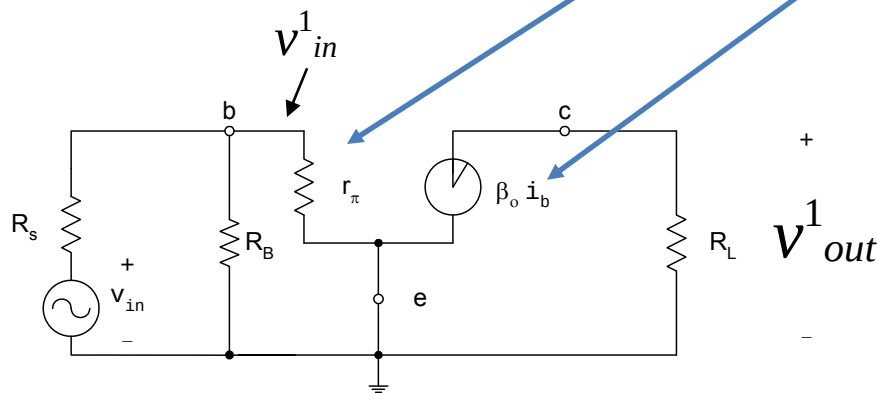

$$A_v = \frac{v_{out}^1}{v_{in}^1} = \frac{-\beta_o i_b R_L}{i_b [r_\pi]} = \frac{-\beta_o R_L}{r_\pi}$$


$$\text{then } A_v = \frac{-\beta_o R_L}{\frac{\beta_o}{g_m}} = -g_m R_L$$

Common Emitter with Emitter Degeneration

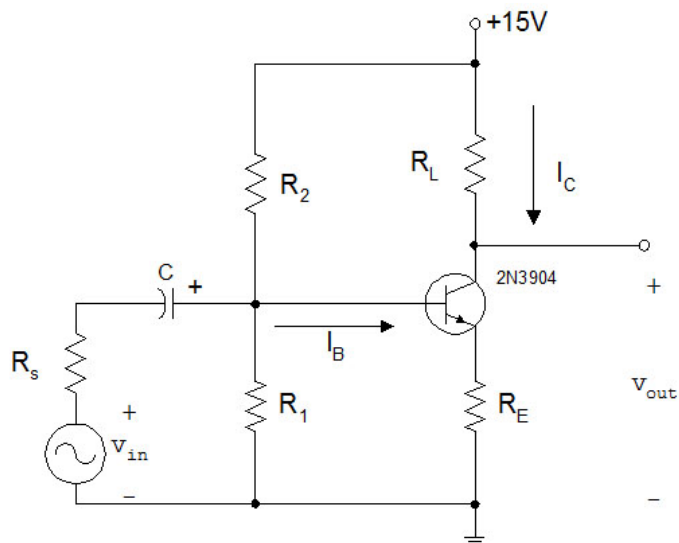

$$A_v = \frac{v_{out}^1}{v_{in}^1} = \frac{-\beta_o i_b R_L}{i_b [r_\pi + (\beta_o + 1)R_E]} = \frac{-\beta_o R_L}{r_\pi + (\beta_o + 1)R_E};$$
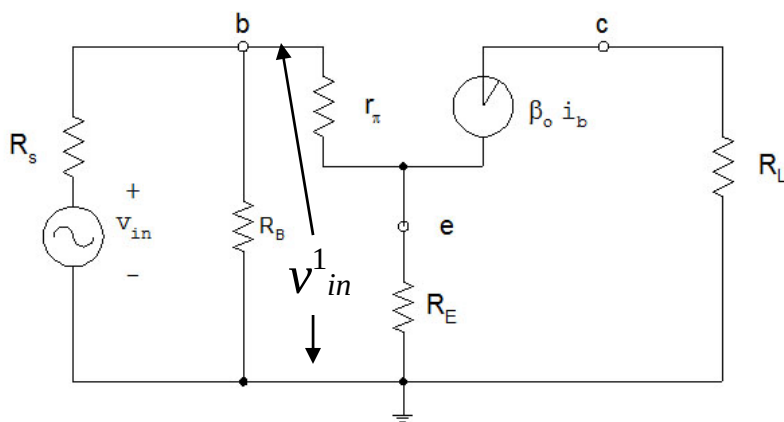
$$\text{if } r_\pi \ll (\beta_o + 1)R_E; \quad \text{then } A_v \approx -R_L / R_E$$




v_{out}^1


- Input resistance $(\beta + 1)R_E$
- Voltage gain reduced by $(g_m R_E)$
- Voltage gain less dependent on β (linearity)

AC Coupled vs DC Coupled Amplifiers

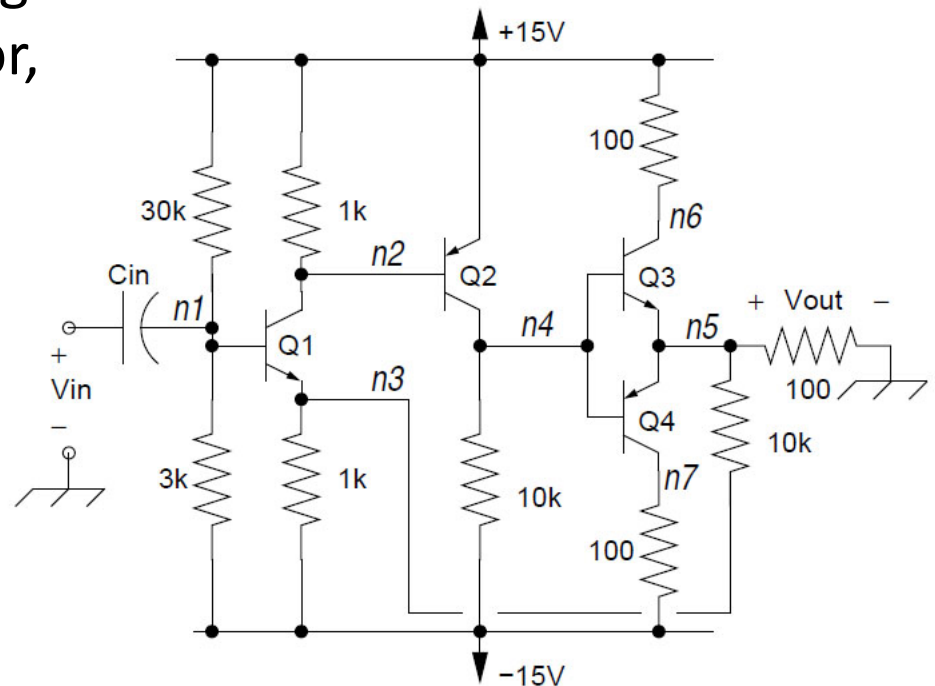- AC Coupling
 - Advantage: easy cascading with DC blocking capacitor, bias stability and stage independent
 - Disadvantage: lot's of R's and C's, no DC gain, need large C for low frequency
- DC coupling
 - Some gain at DC
 - Fewer R's C's




Gain vs Frequency

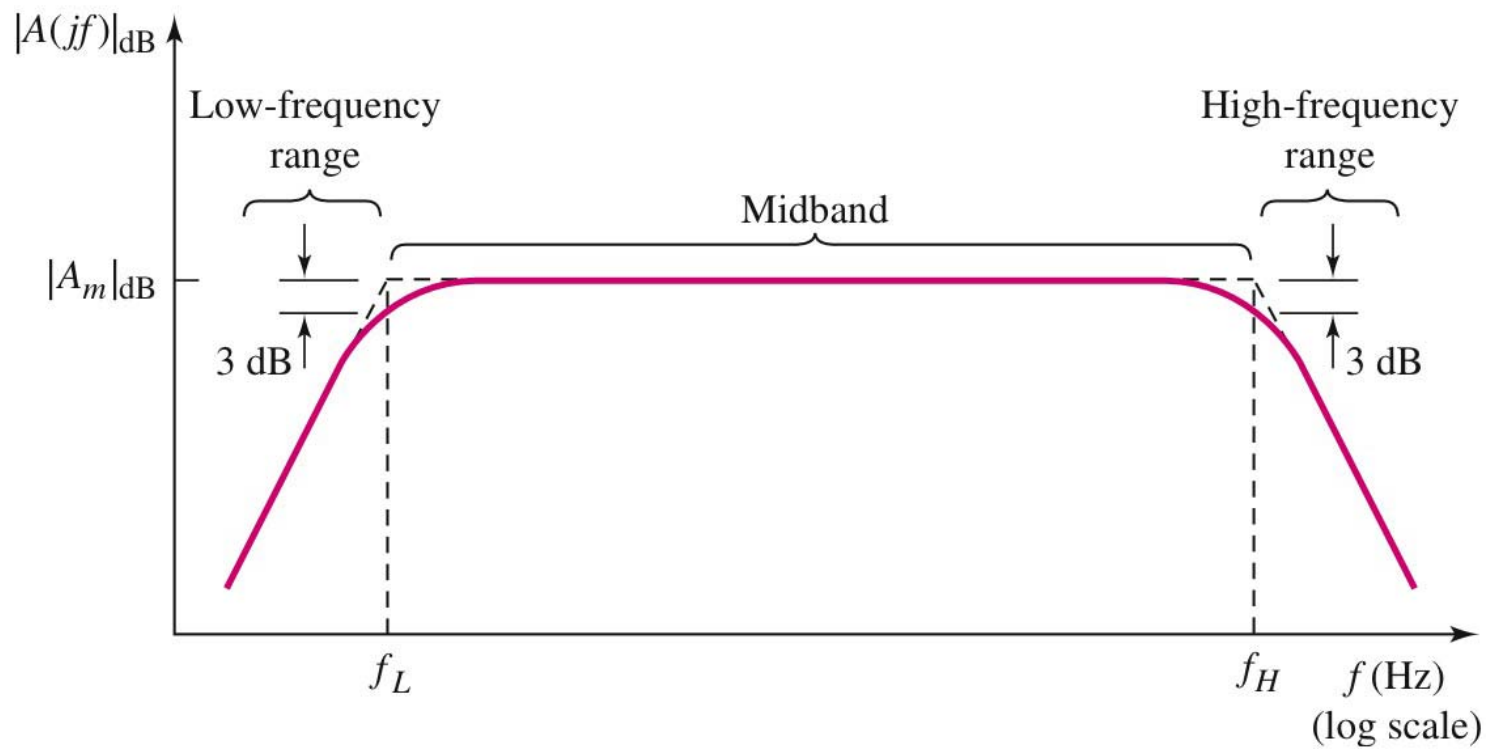


Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Cutoff Frequency Analysis

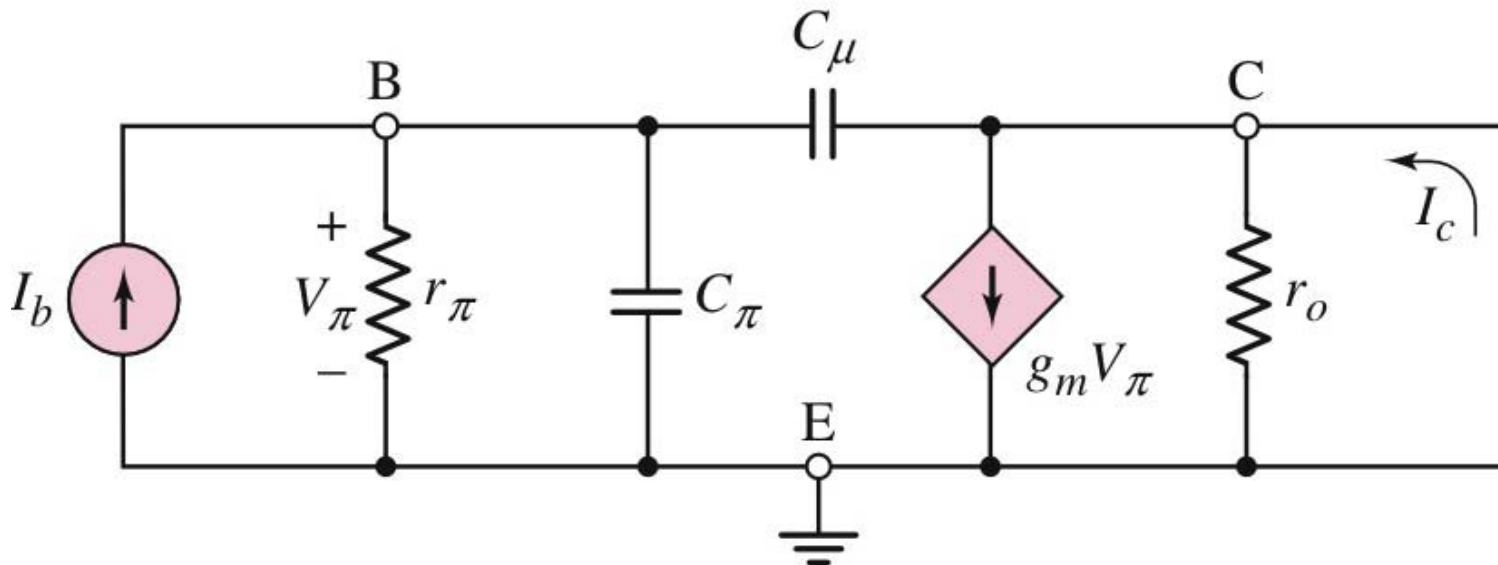

Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Low Pass Filter LPF


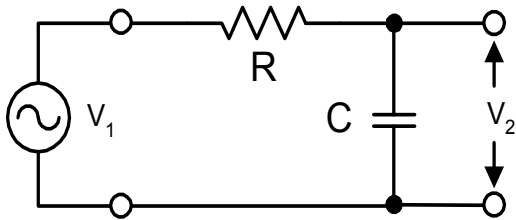


$$A_v = \frac{V_2}{V_1} = \frac{j X_C}{R + j X_C} = \frac{\frac{1}{j \omega C}}{R + \frac{1}{j \omega C}} = \frac{1}{j \omega RC + 1}$$

$$A_v = \frac{1}{sRC + 1}$$


$$\text{High frequency cutoff } f_\beta = \frac{1}{2\pi RC}$$

log scale

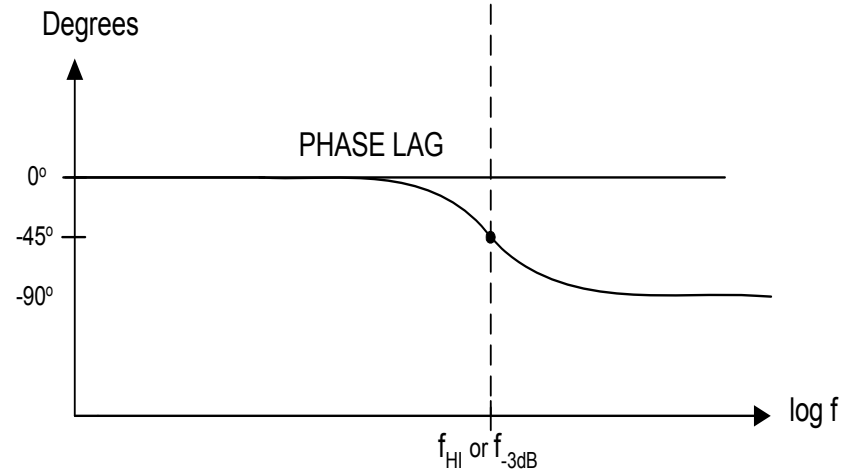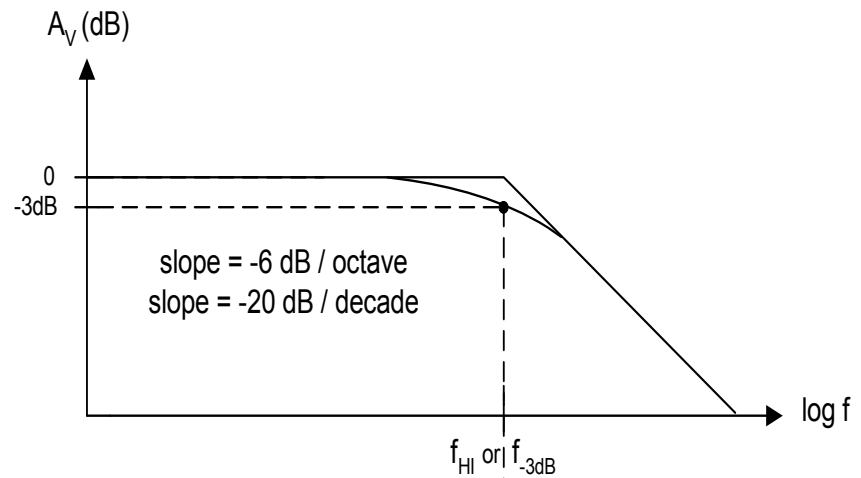

Cutoff Frequency Analysis
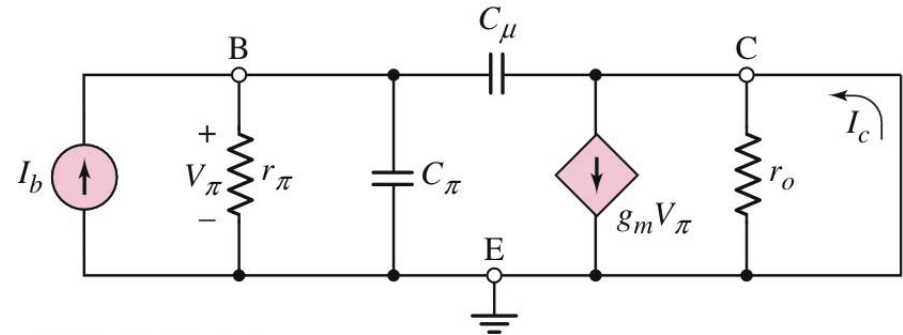
$$3db \quad f_{3db} = f_{\beta} = \frac{1}{2\pi RC} = \frac{1}{2\pi r_{\pi}(C_{\pi} + C_{\mu})}$$



Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

$$i_b = \frac{v_{be}}{r_{\pi}} + v_{be} j\omega (C_{\pi} + C_{\mu})$$

$$v_{\pi} = v_{be}$$

$$h_{fe} = \frac{g_m v_{be}}{i_b} = \frac{g_m r_{\pi}}{1 + j\omega r_{\pi}(C_{\pi} + C_{\mu})} = \frac{\beta}{1 + j\omega r_{\pi}(C_{\pi} + C_{\mu})}$$

This incorrectly
ignores the Miller
effect on C_{μ}

$$h_{fe} = \frac{\beta}{1 + j\left(\frac{f}{f_{\beta}}\right)}$$

$$f_t = h_{fe} = 1 \quad \text{or} \quad f_t = \frac{g_m}{2\pi r_{\pi}(C_{\pi} + C_{\mu})}$$

Cutoff Frequency Parameters

$$g_m = \left(\frac{q}{kT} \right) |I_C|$$

$$\beta_0 = h_{fe} \text{ (datasheet)}$$

$$C_\mu = C_{ob} \text{ (datasheet)}$$

$$\frac{g_m}{2\pi(C_\pi + C_\mu)} = f_T \text{ (transit frequency datasheet)}$$

$$C_\pi = \frac{g_m}{2\pi f_T r_\pi} - C_\mu$$


2N3903 2N3904

ELECTRICAL CHARACTERISTICS ($T_A = 25^\circ\text{C}$ unless otherwise noted) (Continued)


Characteristic	Symbol	Min	Max	Unit
ON CHARACTERISTICS				
DC Current Gain ⁽¹⁾ ($I_C = 0.1 \text{ mAdc}$, $V_{CE} = 1.0 \text{ Vdc}$)	2N3903 2N3904	hFE 20 40	— —	—
($I_C = 1.0 \text{ mAdc}$, $V_{CE} = 1.0 \text{ Vdc}$)	2N3903 2N3904	β 35 70	— —	—
($I_C = 10 \text{ mAdc}$, $V_{CE} = 1.0 \text{ Vdc}$)	2N3903 2N3904	50 100	150 300	—
($I_C = 50 \text{ mAdc}$, $V_{CE} = 1.0 \text{ Vdc}$)	2N3903 2N3904	30 60	— —	—
($I_C = 100 \text{ mAdc}$, $V_{CE} = 1.0 \text{ Vdc}$)	2N3903 2N3904	15 30	— —	—
Collector–Emitter Saturation Voltage ⁽¹⁾ ($I_C = 10 \text{ mAdc}$, $I_B = 1.0 \text{ mAdc}$) ($I_C = 50 \text{ mAdc}$, $I_B = 5.0 \text{ mAdc}$)		$V_{CE(sat)}$ — —	0.2 0.3	Vdc
Base–Emitter Saturation Voltage ⁽¹⁾ ($I_C = 10 \text{ mAdc}$, $I_B = 1.0 \text{ mAdc}$) ($I_C = 50 \text{ mAdc}$, $I_B = 5.0 \text{ mAdc}$)		$V_{BE(sat)}$ 0.65 —	0.85 0.95	Vdc
SMALL–SIGNAL CHARACTERISTICS				
Current–Gain — Bandwidth Product ($I_C = 10 \text{ mAdc}$, $V_{CE} = 20 \text{ Vdc}$, $f = 100 \text{ MHz}$)	2N3903 2N3904	f_T 250 300	— —	MHz
Output Capacitance ($V_{CB} = 5.0 \text{ Vdc}$, $I_E = 0$, $f = 1.0 \text{ MHz}$)		C_{obo} —	4.0	pF
Input Capacitance ($V_{EB} = 0.5 \text{ Vdc}$, $I_C = 0$, $f = 1.0 \text{ MHz}$)		C_{ibo} —	8.0	pF
Input Impedance ($I_C = 1.0 \text{ mAdc}$, $V_{CE} = 10 \text{ Vdc}$, $f = 1.0 \text{ kHz}$)	2N3903 2N3904	h_{ie} 1.0 1.0	8.0 10	k Ω
Voltage Feedback Ratio ($I_C = 1.0 \text{ mAdc}$, $V_{CE} = 10 \text{ Vdc}$, $f = 1.0 \text{ kHz}$)	2N3903 2N3904	h_{re} 0.1 0.5	5.0 8.0	$\times 10^{-4}$
Small–Signal Current Gain ($I_C = 1.0 \text{ mAdc}$, $V_{CE} = 10 \text{ Vdc}$, $f = 1.0 \text{ kHz}$)	2N3903 2N3904	h_{fe} 50 100	200 400	—
Output Admittance ($I_C = 1.0 \text{ mAdc}$, $V_{CE} = 10 \text{ Vdc}$, $f = 1.0 \text{ kHz}$)		h_{oe} 1.0	40	μmhos
Noise Figure ($I_C = 100 \mu\text{Adc}$, $V_{CE} = 5.0 \text{ Vdc}$, $R_S = 1.0 \text{ k } \Omega$, $f = 1.0 \text{ kHz}$)	2N3903 2N3904	NF — —	6.0 5.0	dB

Use max for worst case C_u

Miller Effect* – Common Emitter

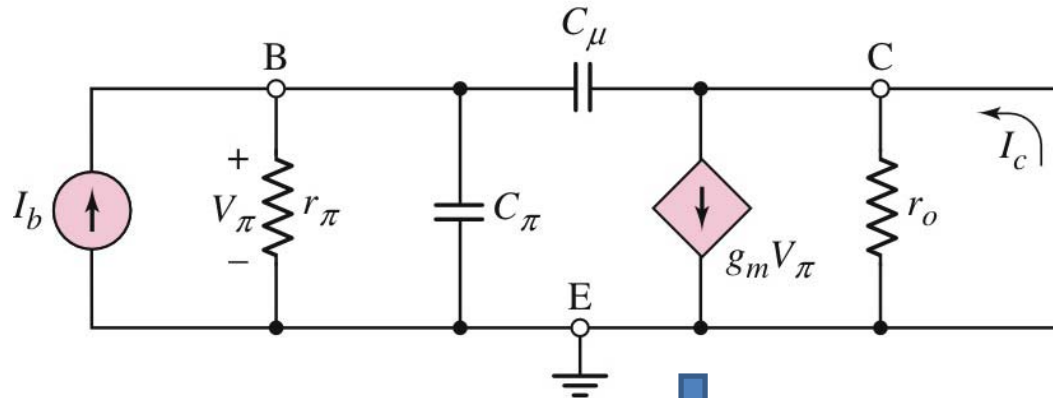

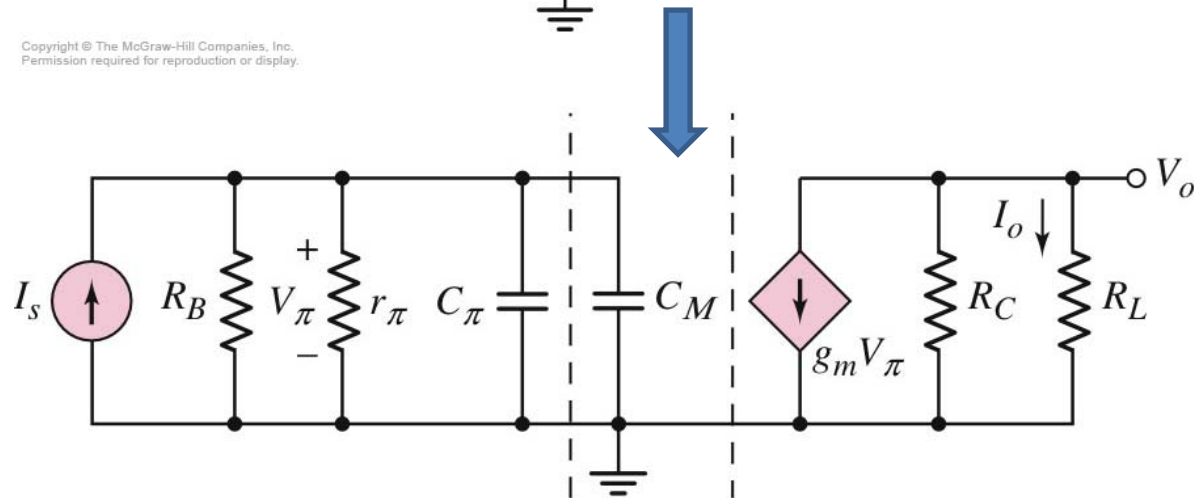Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.



Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

$$C_M = C_\mu [1 + g_m (R_C \parallel R_L)]$$


- Neamen, Microelectronics 3rd Edition p 514

Miller Effect

$$R_C = R_L = 4k \quad r_\pi = 2.6k \quad R_B = 200k$$

$$C_\pi = 4pF \quad C_\mu = 0.2pF \quad g_m = 38.5ma/V$$

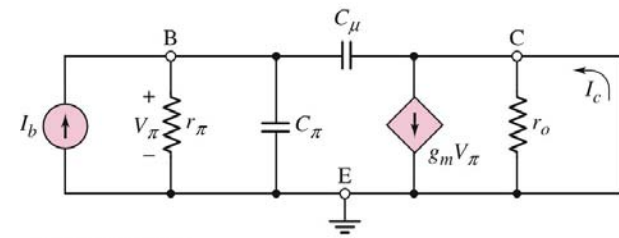
$$f_{3db} = f_\beta = \frac{1}{2\pi(r_\pi \parallel R_B)(C_\pi + C_\mu)} = 15.5MHz$$



with Miller Effect

$$C_M = C_\mu [1 + g_m (R_C \parallel R_L)]$$
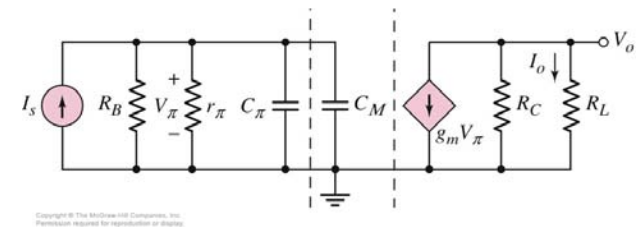
$$f_{3db} = f_\beta = \frac{1}{2\pi(r_\pi \parallel R_B)(C_\pi + C_M)} = 3.16MHz$$




*Neamen, Microelectronics 3rd Edition p 515

2N3904
CE configuration,
 $V_{CC} +15v$

Equation	Example 1 – 1 mA bias	Example 2 – 10 mA bias
$g_m = 40 I_C $	$40 \times 1 \text{ mA} = 40 \text{ mmho}$	$40 \times 10 \text{ mA} = 400 \text{ mmho}$
$\beta_o = h_{fe}$ from spec sheet	Approx. 120 @ 1 mA	Approx. 160 @ 10 mA
$R_{INCE} = r_\pi = \beta_o \div g_m$ $R_{INCB} = r_\pi \div (\beta_o + 1)$	$120/40 \times 10^{-3} = 3000 \Omega$ $3000/121 = 25 \Omega$	$160/0.4 = 400 \Omega$ $400/161 = 2.5 \Omega$
r_x	estimate; $\approx 25 \Omega$	estimate; $\approx 25 \Omega$
CE LF Gain: $A_v = -g_m R_L$	-300 [$R_L = 7.5k$]	-300 [$R_L = 750 \Omega$]
$C_\mu = C_{ob}$ [from spec sheet]	1.8 pF at $V_{cb} = -7.0 \text{ v}$	1.8 pF at $V_{cb} = -7.0 \text{ v}$
f_T from spec sheet	300 MHz	300 MHz
$C_\pi = \frac{g_m}{2\pi f_T} - C_\mu$	$= 21.2 \text{ pF} - 1.8 \text{ pF} \approx 20 \text{ pF}$	212 pF
$C_T = C_\pi + (g_m R_L + 1)C_\mu$ Not good above $\approx 150 / 400 \text{ MHz!}$	$= 20 \text{ pF} + 301 \times 1.8 \text{ pF} = 562 \text{ pF}$	$= 212 \text{ pF} + 301 \times 1.8 \text{ pF} = 754 \text{ pF}$
$f_{hi} = \frac{1}{2\pi R_s \ R_{IN} C_T}$ $R_s' = R_s + r_x = 50 \Omega + 25 \Omega = 75 \Omega$	$= \frac{1}{6.28 \times 73.2 \Omega \times 562 \text{ pF}}$ $f_{hi} = 3.9 \text{ MHz}$	$= \frac{1}{6.28 \times 63 \Omega \times 754 \text{ pF}}$ $f_{hi} = 3.3 \text{ MHz}$
Add shunt the input resistance ($r_x + r_\pi \parallel C_T$) with a 51Ω resistance for maximum power transfer: [note -6dB gain loss]	$= \frac{1}{6.28 \times 49 \Omega \times 562 \text{ pF}}$ $f_{hi} = 5.8 \text{ MHz}$	$= \frac{1}{6.28 \times 44 \Omega \times 754 \text{ pF}}$ $f_{hi} = 4.8 \text{ MHz}$


Common Base Configuration

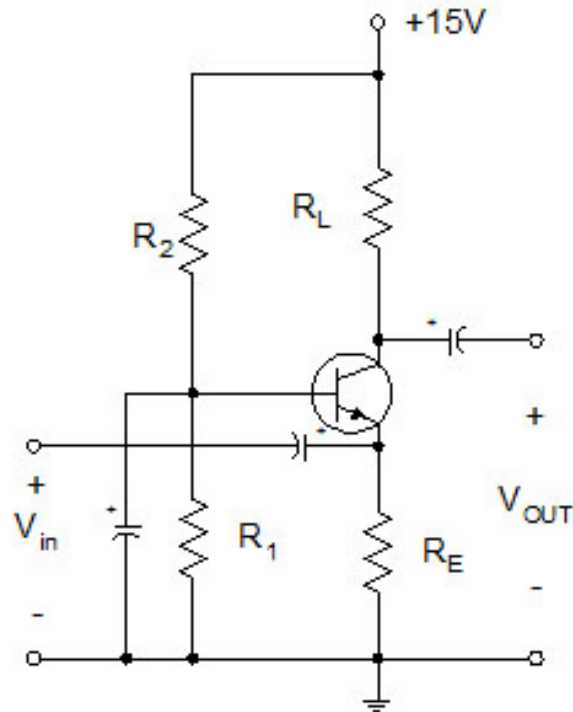

[c] Common Base Amplifier

Equation	Example 1 – 1 mA bias	Example 2 – 10 mA bias
CB input time constant: [no 51Ω] $f_{hi} = \frac{1}{2\pi R_s \parallel R_{IN} C_\pi}$	$= \frac{1}{6.28 \times 12.4\Omega \times 20pF}$ $f_{hi} = 640 \text{ MHz}$	$= \frac{1}{6.28 \times 2.3\Omega \times 212pF}$ $f_{hi} = 332 \text{ MHz}$
CB output time constant: $f_{hi} = \frac{1}{2\pi R_L C_\mu}$	$= \frac{1}{6.28 \times 7500\Omega \times 1.8pF}$ $f_{hi} = 11.8 \text{ MHz}$	$= \frac{1}{6.28 \times 750\Omega \times 1.8pF}$ $f_{hi} = 118 \text{ MHz}$

Common Collector (Emitter Follower)

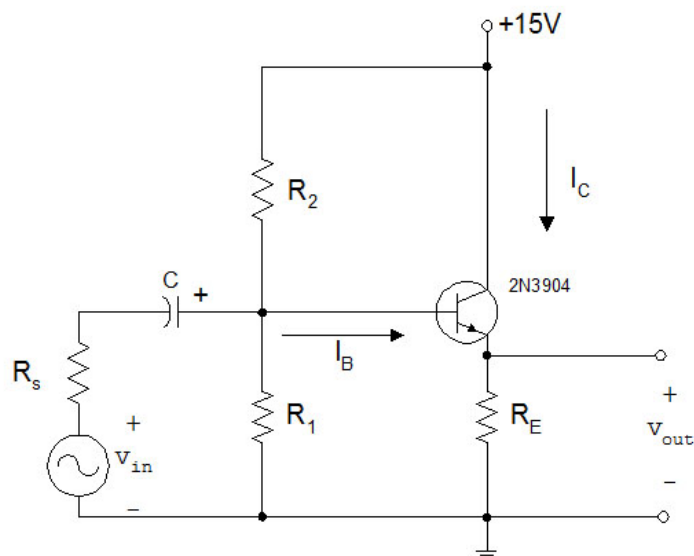


$$\beta_0 = g_m r_\pi$$

$$g_m = \frac{I_{CQ}}{V_{TH}} \quad V_{TH} = 26\text{mV}$$

$$A_v = \frac{v_{out}^1}{v_{in}^1} = \frac{(\beta_o + 1)i_b R_E}{i_b [R'_s + r_\pi + (\beta_o + 1)R_E]} = \frac{(\beta_o + 1) R_E}{R'_s + r_\pi + (\beta_o + 1)R_E};$$
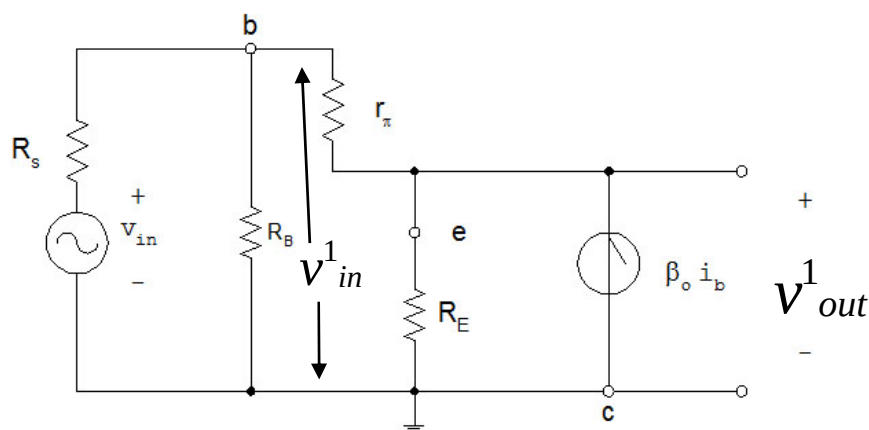
$$\text{if } r_\pi \ll (\beta_o + 1)R_E; \quad \text{then } A_v \approx 1$$



- Buffer with unity gain
- High input resistance driving low output resistance (current gain).

Low Frequency Hybrid- π Equation Chart

Characteristic	Common Emitter	CE with R_E	CC [E. Follower]	Common Base
Voltage Gain [if $r_o \gg R_L$]	$A_v = -g_m R_L$	$A_v \approx -\frac{R_L}{R_E}$	$A_v \approx 1$	$A_v = \frac{\beta_o R_L}{r_\pi // R_E + (\beta_o + 1)R_s}$
Current Gain	β_o	β_o	$\beta_o + 1$	$\frac{\beta_o}{\beta_o + 1}$
Input Impedance	$r_\pi // R_B$	$[r_\pi + (\beta_o + 1)R_E] // R_B$	$[r_\pi + (\beta_o + 1)R_E] // R_B$	$\frac{r_\pi}{\beta_o + 1}$
Output Impedance	R_L [if $r_o \gg R_L$]	R_L [if $r_o \gg R_L$]	$\left[\frac{(r_\pi + R_s // R_B)}{\beta_o + 1} \right] // R_E$	R_L [if $r_o \gg R_L$]
Phase Reversal?	Yes	Yes	No	No
	High gain applications Moderate input resistance High output resistance		Unity gain, low output resistance High input resist.	High gain, better high frequency response Low input resistance