



- MOSFET
- Op Amps
- 741, 356
- Imperfections
- Op-amp applications

Acknowledgements:


Ron Roscoe,

Neamen, Donald: Microelectronics Circuit Analysis and Design, 3rd Edition

March 2020

◀ February

April ▶

Sun	Mon	Tue	Wed	Thu	Fri	Sat
1	2	3	4	5 Lab 4	6 Add date	7
8 Daylight savings	9	10	11 Pizza 6:30	12 Lab 5	13	14
15	16	17 Quiz Review	18	19 Quiz	20	21
22	23 Spring break	24 Spring break	25 Spring break	26 Spring break	27 Spring break 	28



JFET Application Current Source

- Household application: battery charger (car, laptop, mp3 players)
- Differential amplifier current source
- Ramp waveform generator
- High Speed DA converter using capacitors
- Simple circuit: 2N5459 Nchannel JFET


I_{DSS} = current with $V_{GS}=0$

V_P = pinchoff voltage
  
$$i_D = I_{DSS} \left(1 - \frac{v_{GS}}{V_P} \right)^2$$



2017 Quiz Design Question

 

Design a circuit such that when a momentary push button switch is closed, “switched 9v” will be supplied to your design under test for exactly two minutes.

You have available a 2N7000 (n-channel MOSFET) and a ZVP2106A which is a p-channel complement to the 2N7000.

You have a 100uf capacitor that is exactly 100uf with negligible leakage current.

Based on measurements, your 2N7000 has a $V_{GS(th)}$ 3.0 volts and the ZVP2106A has a $V_{GS(th)}$ -3.0.

The 9V battery is a constant 9V during the test.


$$\ln(.3333) = -1.0986$$

$$\ln(.2222) = -1.5041$$

$$\ln(.1111) = -2.1972 \quad [\text{one or more of these constants may be required for your design}]$$



Op-Amps

 - Active device: $V_o = a(V_+ - V_-)$; note that it is the difference of the input voltage!
- a =open loop gain $\sim 10^5 - 10^6$
- Most applications use negative feedback.
- Comparator: no feedback
- Active device requires power. No shown for simplicity.
- Classics op-amps: 741, 357 \sim \$0.20; one, two or four in a package.
- Newer op-amps operate at $<3.3V$ (OPA369 1.8V)




Op-Amp Packaging

LM741 Pinout Diagram

  


LF353

LM324

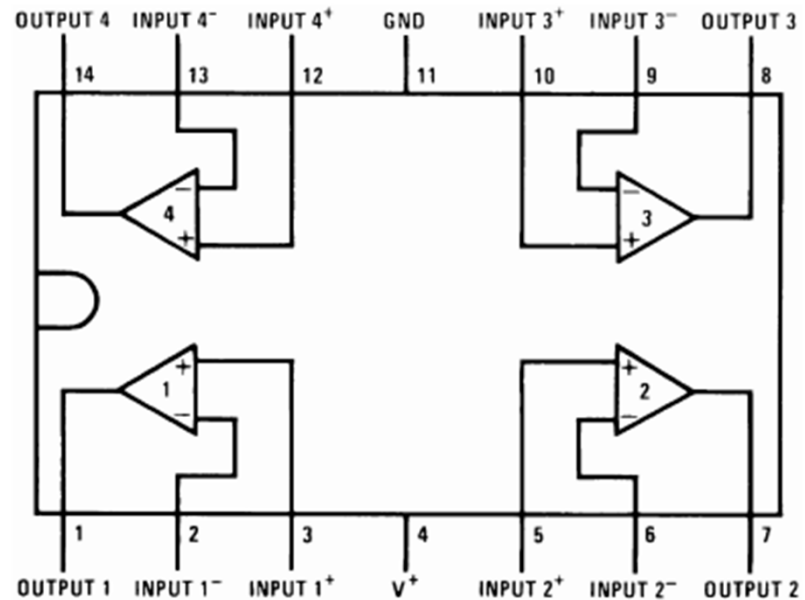

356 JFET Input Op-amp


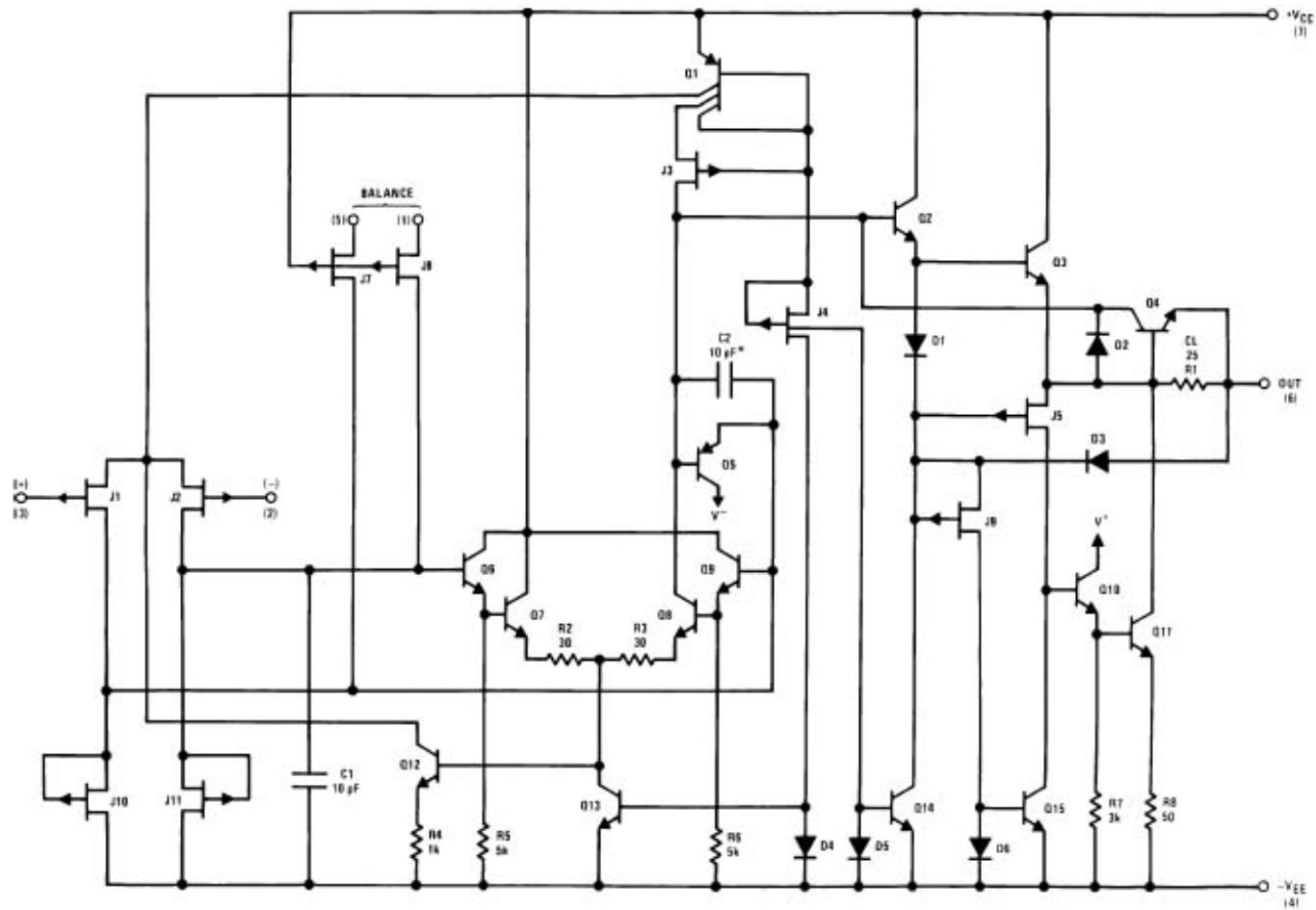


00564613

*C = 3pF in LF357 series.

JFET Differential Pair


Small Signal Model

  


Copyright © The McGraw-Hill Companies, Inc.
 Permission required for reproduction or display.

Copyright © The McGraw-Hill Companies, Inc.
 Permission required for reproduction or display.

741 Circuit

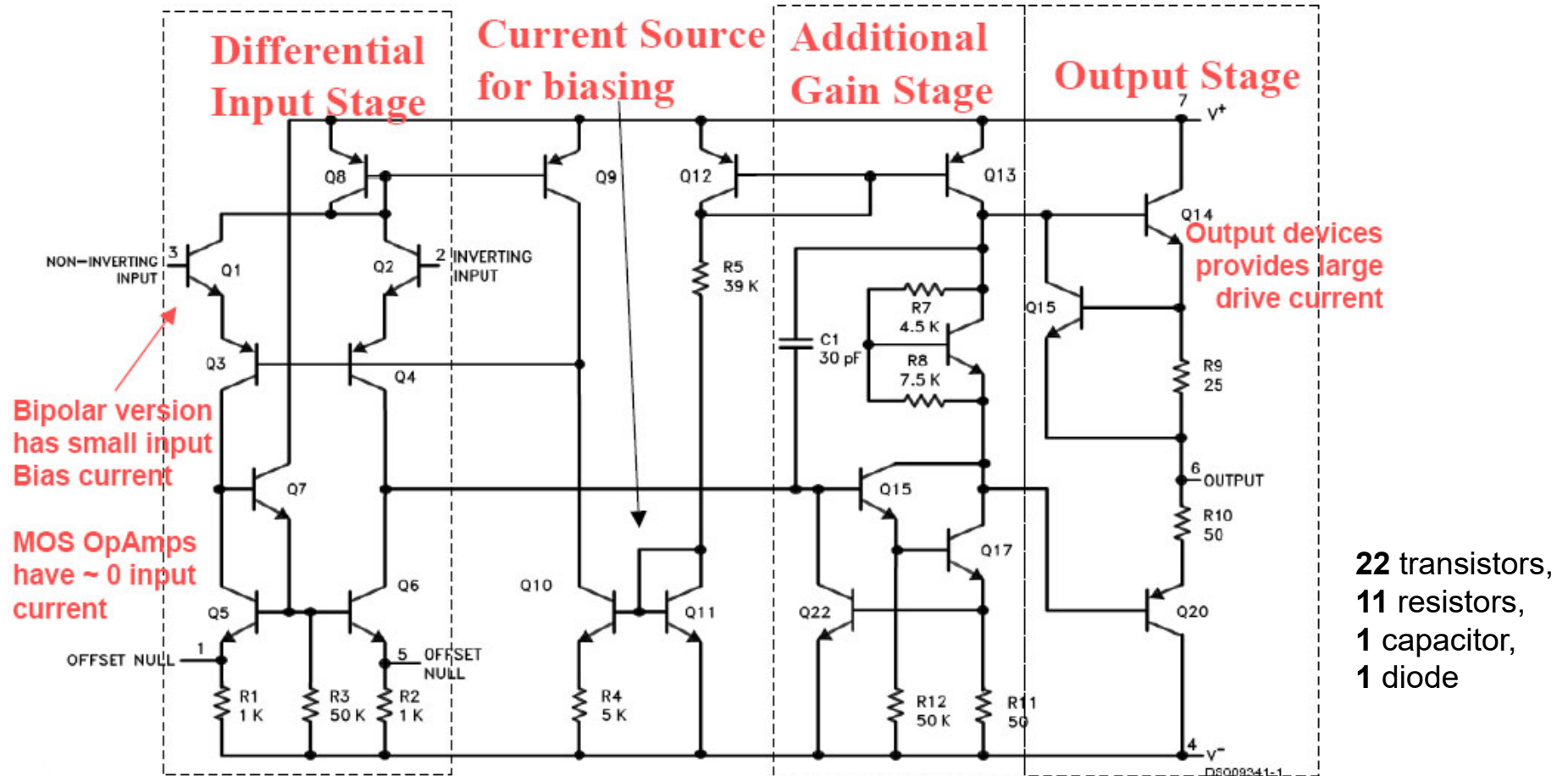


Discrete 741

 


Discrete 741

Schematic Diagram

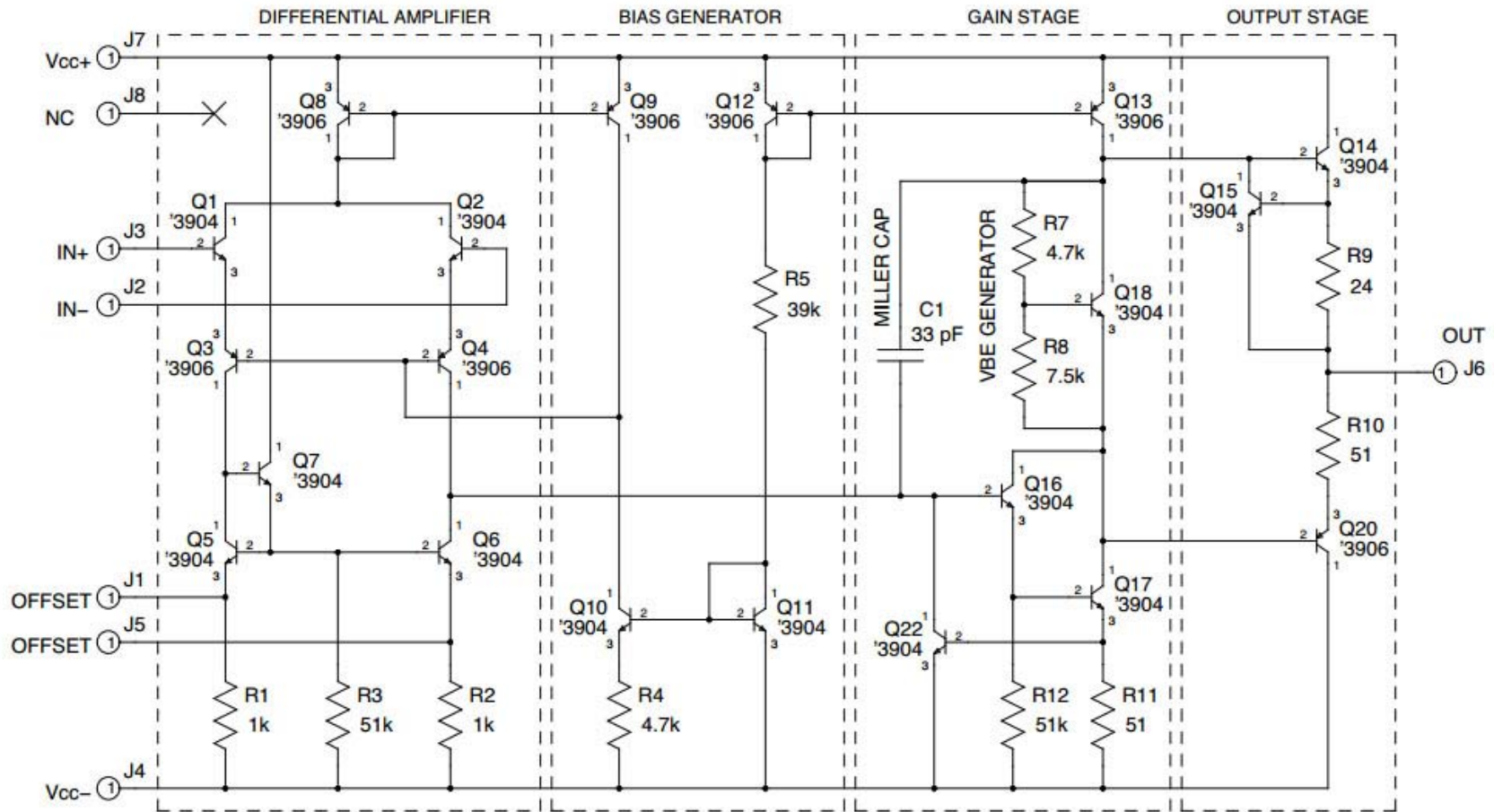


Differential (Emitter Coupled) Pair

BJT Diff Pair

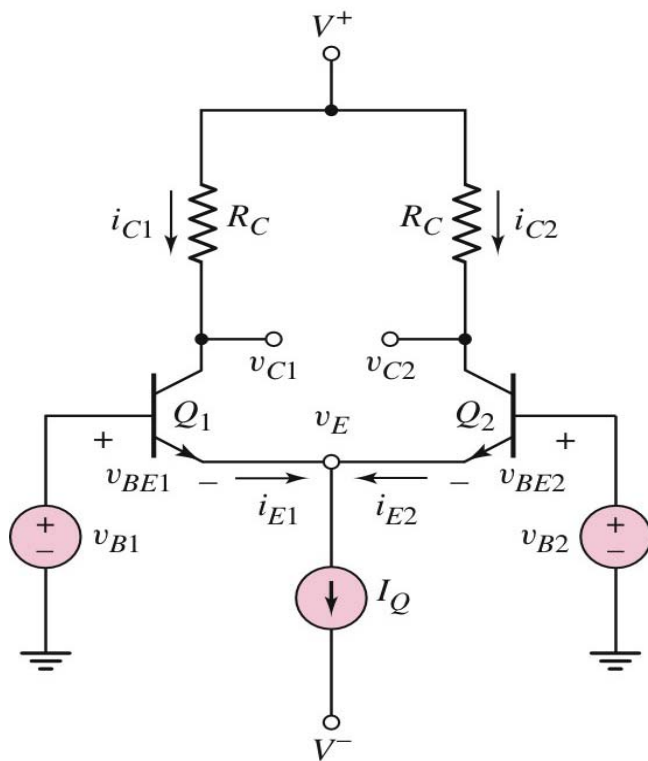

Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.



Small Signal Model

 


Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Differential Pair – Common Mode Voltage

Small Signal Model

 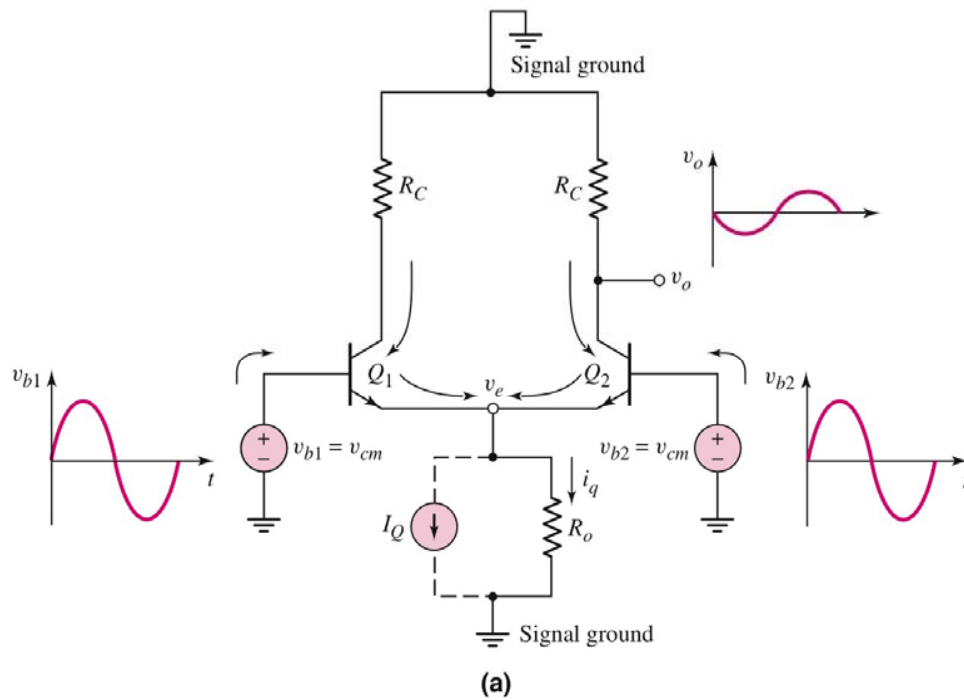


 Differential Pair – Differential Mode Voltage




Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

MOSFET Differential Pair

 


Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Small Signal Model

 

Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Virtual Node Analysis

 

$$V_1 = V_x + \beta V_{out}$$

$$V_1 = V_x + a\beta V_2 - a\beta V_1$$

$$V_1(1 + a\beta) = V_x + a\beta V_2$$

$$V_1 = V_x \left(\frac{1}{1 + a\beta} \right) + \left(\frac{a\beta}{1 + a\beta} \right) V_2 \approx V_2$$

a = gain

β = feedback or loop function

- If $a \gg 1$ and $a\beta \gg 1$ then $v_1 \sim v_2$
- Current into input terminals zero by design
- Typical values:
 $a \sim 100,000$ & $a\beta \gg 1$
- ok for $a = a(s)$ and $\beta = \beta(s)$ as long as $a(s)\beta(s) \gg 1$
- β is the loop transfer function
(not to be confused of β of a BJT)
- $a\beta$ is the loop gain

Op Amps – Virtual Node

- With negative feedback, output will drive the input voltage difference to zero $\Rightarrow V_+ = V_-$
- Input current = 0

Benefits of Feedback

Stabilize gain against device variations, temperature, aging	Reduce distortion by the feedback factor $[(1+a\beta)]$
Input and output impedances adjusted by $(1+a\beta)$	Gain determined by passive components

Disadvantages of Feedback

Loss of gain; need more stages	Greater tendency for instability (oscillations)
--------------------------------	---

$$V_1 = V_x \left(\frac{1}{1+a\beta} \right) + \left(\frac{a}{1+a\beta} \right) V_2 \approx V_2$$

741 Op Amp Max Ratings

common mode voltage
appears at both inputs

Need +Vcc, -Vee for operation

MAXIMUM RATINGS

Rating	Symbol	Value	Unit
Power Supply Voltage	V_{CC}, V_{EE}	± 18	Vdc
Input Differential Voltage	V_{ID}	± 30	V
Input Common Mode Voltage (Note 1.)	V_{ICM}	± 15	V
Output Short Circuit Duration (Note 2.)	t_{SC}	Continuous	–
Operating Ambient Temperature Range	T_A	0 to +70	°C
Storage Temperature Range	T_{stg}	–55 to +125	°C

1. For supply voltages less than +15 V, the absolute maximum input voltage is equal to the supply voltage.
2. Supply voltage equal to or less than 15 V.

Idiot proof

741 Electrical Characteristics

Almost zero

ELECTRICAL CHARACTERISTICS ($V_{CC} = +15\text{ V}$, $V_{EE} = -15\text{ V}$, $T_A = 25^\circ\text{C}$, unless otherwise noted.)

Characteristic	Symbol	Min	Typ	Max	Unit
Input Offset Voltage ($R_S \leq 10\text{ k}$)	V_{IO}	–	2.0	6.0	mV
Input Offset Current	I_{IO}	–	20	200	nA
Input Bias Current	I_{IB}	–	80	500	nA
Input Resistance	r_i	0.3	2.0	–	$M\Omega$
Input Capacitance	C_i	–	1.4	–	pF
Offset Voltage Adjustment Range	$V_{IO\text{R}}$	–	± 15	–	mV
Common Mode Input Voltage Range	$V_{IC\text{R}}$	± 12	± 13	–	V
Large Signal Voltage Gain ($V_O = \pm 10\text{ V}$, $R_L \geq 2.0\text{ k}$)	A_{VOL}	20	200	–	V/mV
Output Resistance	r_o	–	75	–	Ω
Common Mode Rejection ($R_S \leq 10\text{ k}$)	CMR	70	90	–	dB
Supply Voltage Rejection ($R_S \leq 10\text{ k}$)	PSR	75	–	–	dB
Output Voltage Swing ($R_L \geq 10\text{ k}$) ($R_L \geq 2.0\text{ k}$)	V_O	± 12 ± 10	± 14 ± 13	– –	V
Output Short Circuit Current	I_{SC}	–	20	–	mA
Supply Current	I_D	–	1.7	2.8	mA
Power Consumption	P_C	–	50	85	mW
Transient Response (Unity Gain, Noninverting) ($V_i = 20\text{ mV}$, $R_L \geq 2.0\text{ k}$, $C_L \leq 100\text{ pF}$) Rise Time	t_{TLH}	–	0.3	–	μs
($V_i = 20\text{ mV}$, $R_L \geq 2.0\text{ k}$, $C_L \leq 100\text{ pF}$) Overshoot	os	–	15	–	%
($V_i = 10\text{ V}$, $R_L \geq 2.0\text{ k}$, $C_L \leq 100\text{ pF}$) Slew Rate	SR	–	0.5	–	V/ μs

LF356

DC Electrical Characteristics

Symbol	Parameter	Conditions	LF155/6			LF256/7 LF356B			LF355/6/7			Units
			Min	Typ	Max	Min	Typ	Max	Min	Typ	Max	
V_{OS}	Input Offset Voltage	$R_S=50\Omega, T_A=25^\circ\text{C}$		3	5		3	5		3	10	mV
		Over Temperature			7			6.5			13	mV
$\Delta V_{OS}/\Delta T$	Average TC of Input Offset Voltage	$R_S=50\Omega$		5			5			5		$\mu\text{V}/^\circ\text{C}$
$\Delta\text{TC}/\Delta V_{OS}$	Change in Average TC with V_{OS} Adjust	$R_S=50\Omega, ^{(2)}$		0.5			0.5			0.5		$\mu\text{V}/^\circ\text{C}$ per mV
I_{OS}	Input Offset Current	$T_J=25^\circ\text{C}, ^{(1) (3)}$		3	20		3	20		3	50	pA
		$T_J \leq T_{HIGH}$			20			1			2	nA
I_B	Input Bias Current	$T_J=25^\circ\text{C}, ^{(1) (3)}$		30	100		30	100		30	200	pA
		$T_J \leq T_{HIGH}$			50			5			8	nA
R_{IN}	Input Resistance	$T_J=25^\circ\text{C}$		10^{12}			10^{12}			10^{12}		Ω
A_{VOL}	Large Signal Voltage Gain	$V_S=\pm 15\text{V}, T_A=25^\circ\text{C}$	50	200		50	200		25	200		V/mV
		$V_O=\pm 10\text{V}, R_L=2\text{k}$										
		Over Temperature	25			25			15			
V_O	Output Voltage Swing	$V_S=\pm 15\text{V}, R_L=10\text{k}$	± 12	± 13		± 12	± 13		± 12	± 13		V
		$V_S=\pm 15\text{V}, R_L=2\text{k}$	± 10	± 12		± 10	± 12		± 10	± 12		V
V_{CM}	Input Common-Mode Voltage Range	$V_S=\pm 15\text{V}$	± 11	+15.1		± 11	± 15.1		+10	+15.1		V
				-12			-12			-12		V
CMRR	Common-Mode Rejection Ratio		85	100		85	100		80	100		dB
PSRR	Supply Voltage Rejection Ratio	⁽⁴⁾	85	100		85	100		80	100		dB

not rail to rail

LM6132 – Rail to Rail Output

LM6132, LM6134
www.ti.com


SNOS751E – APRIL 2000 – REVISED SEPTEMBER 2014

6.6 5.0V DC Electrical Characteristics

Unless otherwise specified, all limits guaranteed for $V^+ = 5.0V$, $V^- = 0V$, $V_{CM} = V_O = V^+/2$ and $R_L > 1\text{ M}\Omega$ to $V^+/2$. **Boldface** limits apply at the temperature extremes

	PARAMETER	TEST CONDITIONS	TYP ⁽¹⁾	LM6134AI LM6132AI LIMIT ⁽²⁾	LM6134BI LM6132BI LIMIT ⁽²⁾	UNIT
V_{OS}	Input Offset Voltage		0.25	2 4	6 8	mV max
TCV_{OS}	Input Offset Voltage Average Drift		5			$\mu\text{V}/\text{C}$
I_B	Input Bias Current	$0V \leq V_{CM} \leq 5V$	110	140 300	180 350	nA max
I_{OS}	Input Offset Current		3.4	30 50	30 50	nA max
R_{IN}	Input Resistance, CM		104			M Ω
$CMRR$	Common Mode Rejection Ratio	$0V \leq V_{CM} \leq 4V$	100	75 70	75 70	dB min
		$0V \leq V_{CM} \leq 5V$	80	60 55	60 55	
$PSRR$	Power Supply Rejection Ratio	$\pm 2.5V \leq V^+ \leq \pm 12V$	82	78 75	78 75	dB min
V_{CM}	Input Common-Mode Voltage Range		-0.25 5.25	0 5.0	0 5.0	V
A_V	Large Signal Voltage Gain	$R_L = 10k$	100	25 6	15 6	V/mV min
V_O	Output Swing	100k Load	4.992	4.98 4.93	4.98 4.93	V min
			0.007	0.017 0.019	0.017 0.019	V max
		10k Load	4.952	4.94 4.85	4.94 4.85	V min
			0.032	0.07 0.09	0.07 0.09	V max
		5k Load	4.923	4.90 4.85	4.90 4.85	V min
			0.051	0.095 0.12	0.095 0.12	V max

Rail to Rail Input

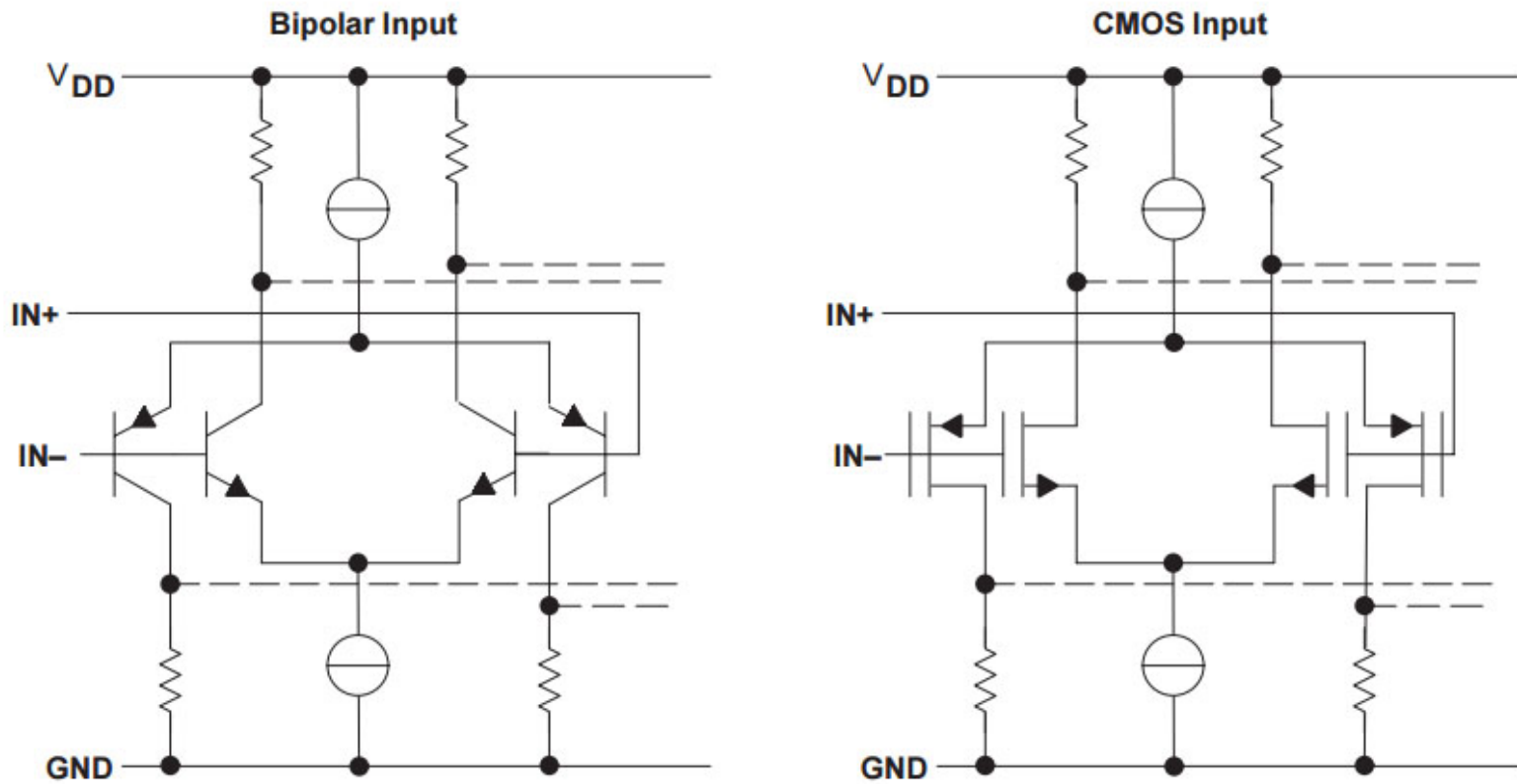

Decibel (dB)

$$dB = 20 \log \left(\frac{V_o}{V_i} \right)$$

$$dB = 10 \log \left(\frac{P_o}{P_i} \right)$$

$$\log_{10}(2) = .301$$

3 dB point = half power point


$$100 \text{ dB} = 100,000 = 10^5$$

$$80 \text{ dB} = 10,000 = 10^4$$


$$60 \text{ dB} = 1,000 = 10^3$$

$$40 \text{ dB} = 100 = 10^2$$

741 Open Loop Frequency Gain

 

Non-Inverting Amplifier

 

Zero input current;

therefore $v_+ = v_{in}$

$$v_- = \frac{R_1}{R_1 + R_2} \times v_{out} \text{ but } v_+ = v_-$$

$$\text{so } v_{in} = \frac{R_1}{R_1 + R_2} \times v_{out};$$

$$\frac{v_{out}}{v_{in}} = \frac{R_1 + R_2}{R_1}$$

$$\text{or } A_v = 1 + \frac{R_2}{R_1}$$


β (not to be confused with β of a BJT)

for finite A

$$\beta = \frac{R_1}{R_1 + R_2}$$

$$\frac{v_{out}}{v_{in}} = A_v = \frac{A}{1 + A\beta}$$

741 Open Loop Frequency Gain

 

Examples at 1 Hz, 1000 Hz, and 10kHz

Voltage gain $A_v = 40\text{dB} = 100$; $R_2 = 100\text{k}\Omega$,
 $R_1 = 1\text{k}\Omega$; $[101 = 40.1\text{dB}]$ $\beta = 0.01$

At 1 Hz, $A_{\text{vol}} = 100 \text{ dB} = 1 \times 10^5 = 100,000$.


$$A_v = \frac{A}{1 + A\beta} = \frac{10^5}{1 + 10^5 \times 0.01} = \frac{10^5}{10^3} = 100 = 40\text{dB}$$

At 1000 Hz, $A_{\text{vol}} = 60 \text{ dB} = 10^3 = 1000$.

$$A_v = \frac{A}{1 + A\beta} = \frac{10^3}{1 + 10^3 \times 0.01} = \frac{10^3}{1 + 10} = \frac{1000}{11} = 90.9 = 39.2 \text{ dB}$$

At 10 kHz, $A_{\text{vol}} = 42 \text{ dB} = 1.26 \times 10^2 = 126$.
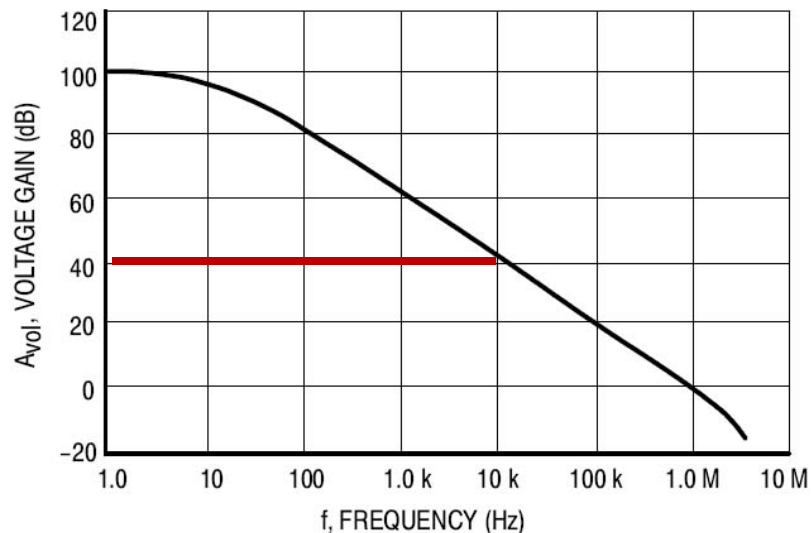
$$A_v = \frac{A}{1 + A\beta} = \frac{126}{1 + 126 \times 0.01} = \frac{126}{1 + 1.26} = \frac{126}{2.26} = 55.8 = 34.9\text{dB}$$



β is the loop transfer function
 $a\beta$ is the loop gain

741 vs 356 Comparison

	741	356
Input device	BJT	JFET
Input bias current	0.5 μ A	0.0001 μ A
Input resistance	0.3 M Ω	10 ⁶ M Ω
Slew rate*	0.5 v/ μ s	7.5 v/ μ s
Gain Bandwidth product	1 Mhz	5 Mhz
Output short circuit duration	continuous	continuous
Identical pin out		


* comparators have >50 v/ μ s slew rate

So Why BJT in Op-amps?

BJTs have higher transconductance (gain), better consistency in spec between pieces, and in some applications, lower noise than FETs.

Like most JFET op amps, the LF356 has a relatively high offset voltage, and relatively high drifts. BJT op-amps tend to have much lower offset voltage and drifts.

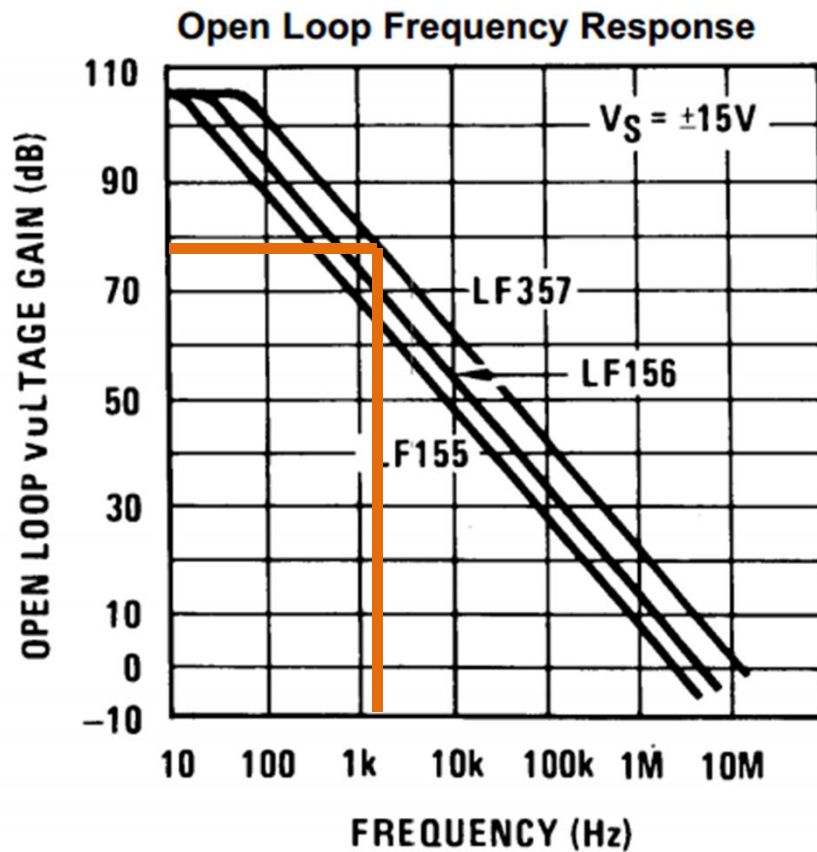Gain Bandwidth Product = Constant (No free lunch)



Gain: 60dB = 10^3
Bandwidth = 5×10^3

Gain Bandwidth product = 5×10^6


Op-Amp Imperfections – Real World

- Input offset voltage
- Input Current Bias
- Input Offset Current
- Finite Output Voltage Swing
- Finite Current
- Finite Gain, gain bandwidth product
- Voltage Noise – Johnson Noise
- Phase Shifts
- Slew Rate

Input Offset Voltage *

DEFINITION OF INPUT OFFSET VOLTAGE

Ideally, if both inputs of an op amp are at exactly the same voltage, then the output should be at zero volts. In practice, a small differential voltage must be applied to the inputs to force the output to zero. This is known as the *input offset voltage*, V_{OS} . Input offset voltage is modeled as a voltage source, V_{OS} , in series with the inverting input terminal of the op amp as shown in Figure 1.

 

◆ **Offset Voltage:** The differential voltage which must be applied to the input of an op amp to produce zero output.

◆ **Ranges:**

- Chopper Stabilized Op Amps: $<1\mu\text{V}$
- General Purpose Precision Op Amps: $50\text{-}500\mu\text{V}$
- Best Bipolar Op Amps: $10\text{-}25\mu\text{V}$
- Best JFET Input Op Amps: $100\text{-}1,000\mu\text{V}$
- High Speed Op Amps: $100\text{-}2,000\mu\text{V}$
- Untrimmed CMOS Op Amps: $5,000\text{-}50,000\mu\text{V}$
- DigiTrim™ CMOS Op Amps: $<100\mu\text{V}\text{-}1,000\mu\text{V}$





741: $6000\mu\text{V}$
357: $10,000\mu\text{V}$

Current technology:
 $10\mu\text{V}$

Figure 1: Typical Op Amp Input Offset Voltage

* Analog Devices MT-037 Tutorial

Offset Adjustments

 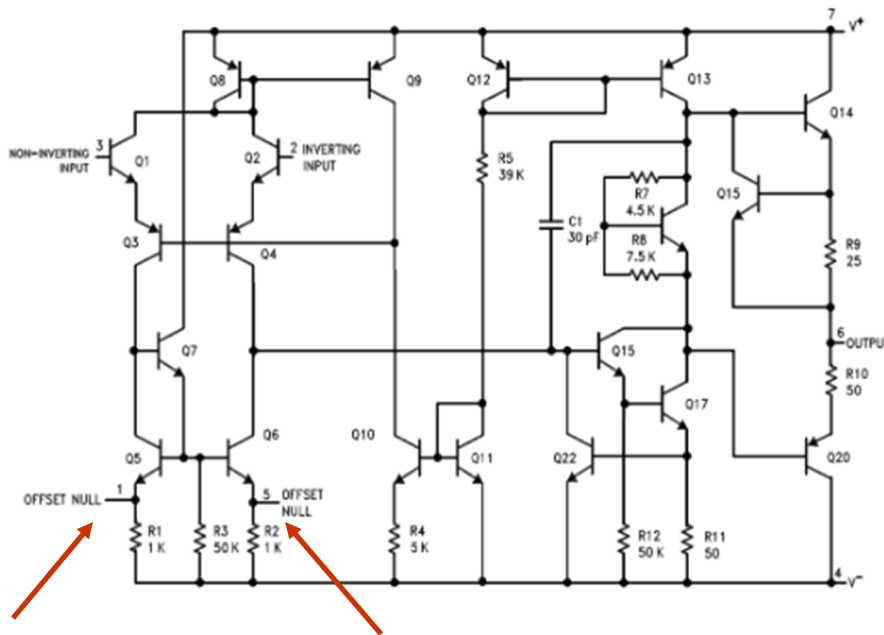  


C = 3pF in LF357 series.

Input Bias Current *

DEFINITION OF INPUT BIAS CURRENT

 Ideally, no current flows into the input terminals of an op amp. In practice, there are always two *input bias currents*, I_{B+} and I_{B-} (see Figure 1).



The *input offset current*, I_{OS} , is the difference between I_{B-} and I_{B+} , or $I_{OS} = I_{B+} - I_{B-}$.

- ◆ A very variable parameter!
- ◆ I_B can vary from 60 fA (1 electron every 3 μ s) to many μ A, depending on the device.
- ◆ Some structures have well-matched I_B , others do not.
- ◆ Some structures' I_B varies little with temperature, but a FET op amp's I_B doubles with every 10°C rise in temperature.
- ◆ Some structures have I_B which may flow in either direction.


Figure 1: Op Amp Input Bias Current

741: 200na
357: 0.05na

Current technology:
3fA LTC6268

* Analog Devices MT-038 Tutorial

 Inverting Amplifier Bias Current Compensation



$$I_{IN} - I_B - I_F = 0$$


$$V_{OFF} = -R_1 I_B$$

$$\frac{V_{IN} - V_{OFF}}{R_{IN}} - I_B - \frac{V_{OFF} - V_{OUT}}{R_F} = 0$$


but with no input signal, V_{IN} and we want $V_{OUT} = 0$, so :

$$-I_B = V_{OFF} \left[\frac{1}{R_{IN}} + \frac{1}{R_F} \right]; \quad -I_B = -R_1 I_B \left[\frac{1}{R_{IN}} + \frac{1}{R_F} \right]$$

 thus : $\left[\frac{1}{R_{IN}} + \frac{1}{R_F} \right] = \left[\frac{1}{R_1} \right]$ as a condition for no offset at V_o .



Common Mode Rejection Ratio CMRR

 

CMRR: ratio of the common-mode gain to differential-mode gain.

Example, if a differential input change of Y volts produces a change of 1 V at the output, and a common-mode change of X volts produces a similar change of 1 V, then the CMRR is X/Y.

CMRR often expressed in dB:

$$CMRR = 20 \log \frac{A_{OL}}{A_{CM}}$$


Inverting Amplifier – Virtual Ground Analysis

Assumptions

Infinite input impedance: $i_+ = 0$; $i_- = 0$

$A = \infty$ $v_- = 0$ because v_+ is grounded.

$$A \gg A_V = \frac{-R_f}{R_{in}}$$

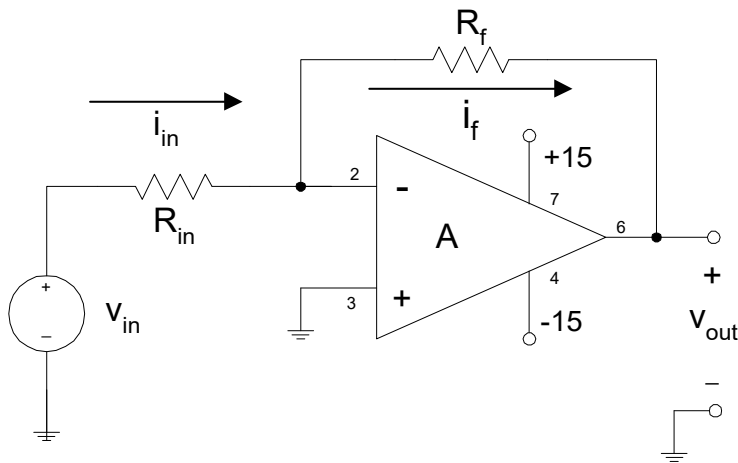


$$i_{in} - i_f = 0$$

$$\frac{v_{in} - 0}{R_{in}} - \frac{0 - v_{out}}{R_f} = 0$$


$$\frac{v_{out}}{v_{in}} = \frac{-R_f}{R_{in}} = A_V$$

Schmitt Trigger

 


- Schmitt trigger have different triggers points for rising edge and falling edge.
- Can be used to reduce false triggering
- This is NOT a negative feedback circuit.

 2015 Quiz Question – Digital Clock Using 60Hz




The 60 Hz waveform crosses the reference voltage multiple times because of the 200mv noise.

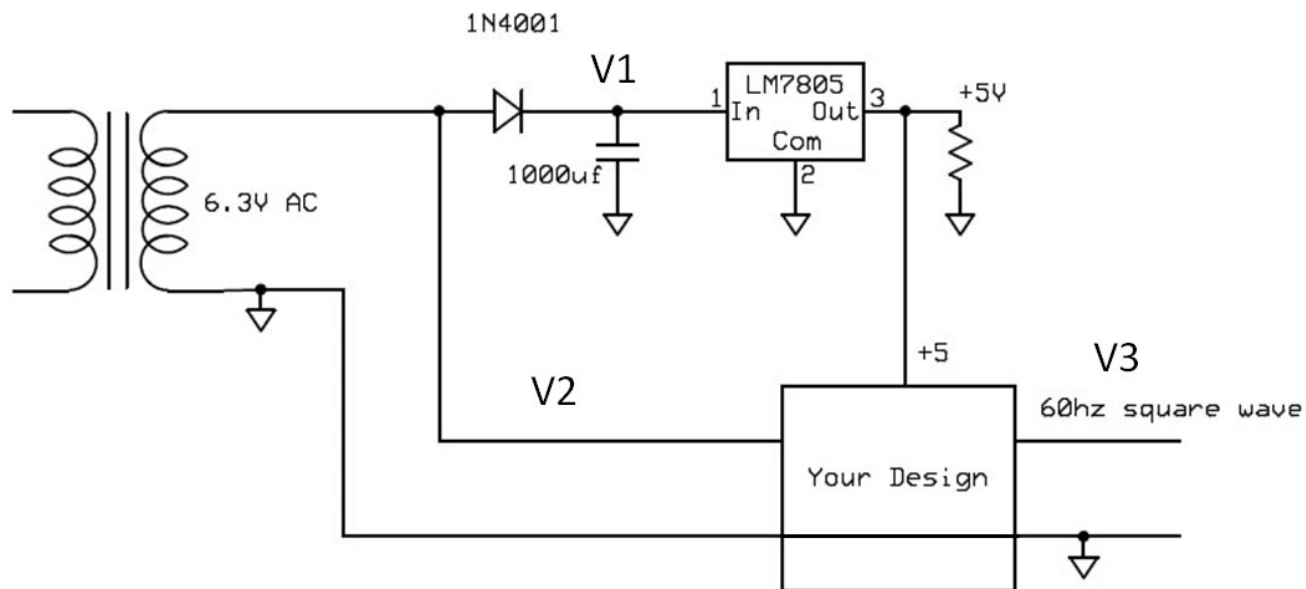Design a circuit with a Schmitt trigger (“Your design”) using a LM6132 with the thresholds greater than 200mv to fix the problem. A LM7805 voltage regulator IC is used to provide a 5V output to power the digital clock circuit (modeled as a resistor) as well as to supply +5V for the LM6132 in “Your design”.




 Schmitt Trigger + RC Feedback = Oscillator





- 741 op-amp.
- R1=10k, R2=4.7k, R3=10K, C=.33uf
- Display V₋ and V_{out} on the scope. Set R3=4.7k. Predict what happens to the frequency.


High Pass Filter HPF

 
  
$$A_v = \frac{V_2}{V_1} = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega CR}{j\omega CR + 1} = \frac{s CR}{s CR + 1}$$



Differentiator Insights


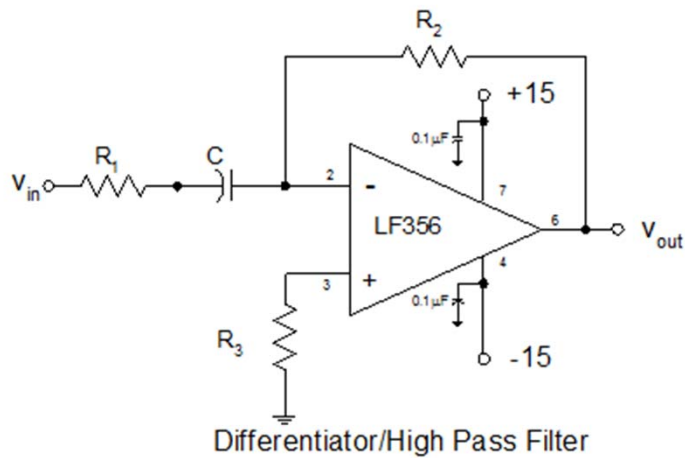


$$A_v = \frac{-R_2}{R_1 + \frac{1}{sC}} = \frac{-sCR_2}{sCR_1 + 1}; \quad s = j\omega;$$

at low frequency $sCR_1 \ll 1$


$$A_v = \frac{-sCR_2}{1}$$

multiplying by s equals differentiation

  



differentiation works only at $f \ll f_{lo}$

Low Pass Filter LPF

 


$$A_v = \frac{V_2}{V_1} = \frac{jX_c}{R + jX_c} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{j\omega RC + 1}$$

$$A_v = \frac{1}{sRC + 1}$$

  

Integrator Insights


 


$$A_v = -\frac{R_2/R_1}{1 + sCR_2}; \quad s = j\omega;$$

at high frequency $sCR_2 \gg 1$


$$A_v = -\frac{R_2/R_1}{sCR_2} = -\frac{1}{sCR_1}$$

dividing by s equals integration

 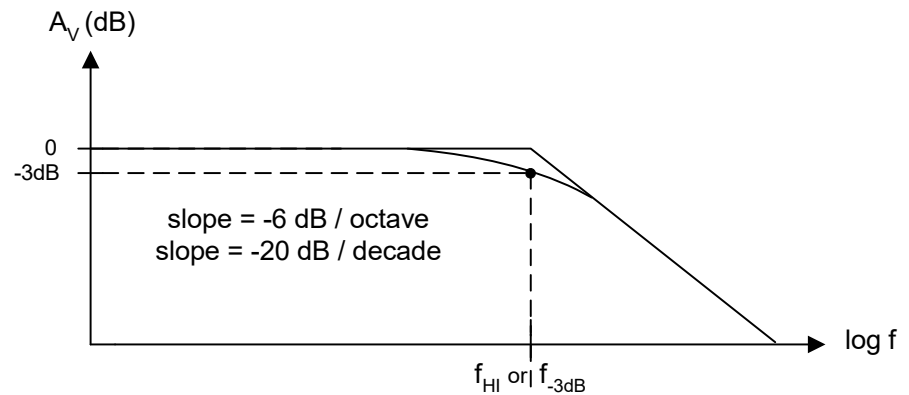

integration works only at $f \gg f_{Hi} \quad sCR_2 \gg 1$




Why R2?

 

Without R2, any DC bias current will saturate V_{out} since the DC gain is the open loop gain


Frequency Domain Insight

   - Integration and differentiation easy to understand in time domain
- In frequency domain, difference between square wave and triangle wave is amplitude and phase – same harmonics.
- Integrator (LPF) rolls off harmonics and phase shift to create a triangle wave
- Differentiator (HPF) amplifies harmonics and phase shift to create a square wave.




Basic OpAmp Circuits

Voltage Follower (buffer)

 


$$v_{out} \approx v_{in}$$

Differential Input

 


$$v_{out} \approx \frac{R_2}{R_1} (v_{in2} - v_{in1})$$

Non-inverting

 


$$v_{out} \approx \frac{R_1 + R_2}{R_1} v_{in}$$

Integrator

 

$$v_{out} \approx -\frac{1}{RC} \int_{-\infty}^t v_{in} dt$$

Crossover Distortion (hole)

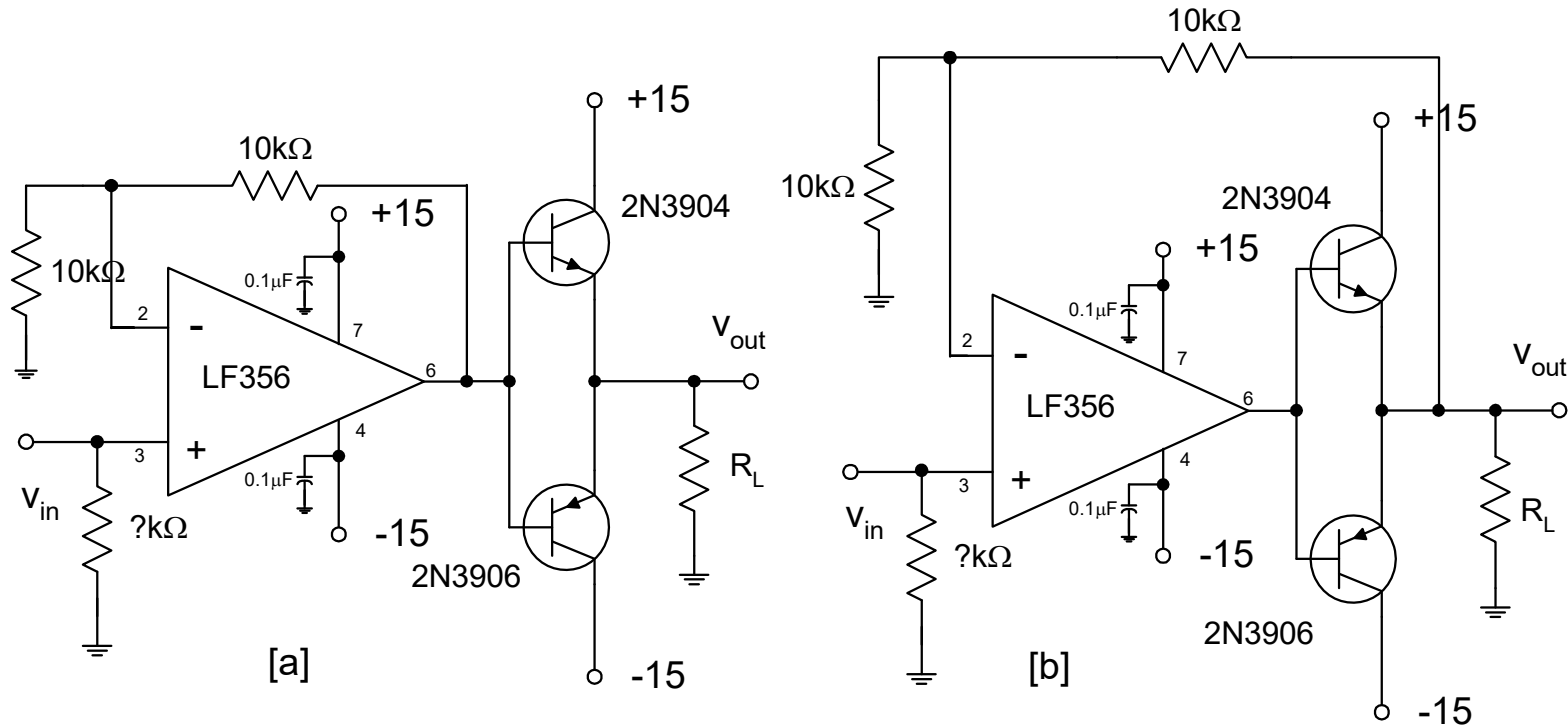

Why is [b] better?

Diode Biasing

