



Introduction to LTspice

Acknowledgment: LTspice material based in part by
Devon Rosner (6.101 TA 2014), Engineer, Linear Technology

SPICE

- Simulation Program with Integrated Circuit Emphasis
- Developed in 1973 by Laurence Nagel at UC Berkeley's Electronics Research Laboratory
- Dependent on user defined device models

Netlists


Components

Commands

```
* C:\Users\Devon\Desktop\6101\6101SallenKey.asc
XU1 N002 Uo U+ U- Uo LT1022
U1 U+ 0 15
U2 0 U- 15
R1 Vi N001 {R}
R2 N001 N002 {R}
C1 N002 0 {1/(2*Pi*R*10k)}
C2 N001 Uo {1/(2*Pi*R*10k)}
U3 Vi 0 SINE(0 1 {f} 0 0 0) AC 1
.step param f list 1k 10k 100k
.param R 1k
.tran 1m
.lib LTC.lib
.backanno
.end
```

LTspice

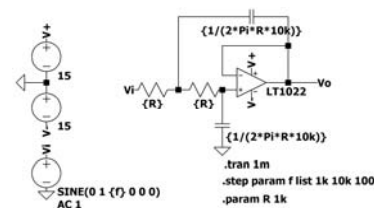- Developed in 1998 by Mike Engelhardt at Linear Technology Corporation
- GUI, simulator, and schematic -> netlist for SPICE
- **FREE** and comes with tons of models




You do this


```
* C:\Users\Devon\Desktop\6101\6101SallenKey.asc
XU1 N002 Uo U+ U- Uo LT1022
U1 U+ 0 15
U2 0 U- 15
R1 U1 N001 {R}
R2 N001 N002 {R}
C1 N002 0 {1/(2*Pi*R*10k)}
C2 N001 Uo {1/(2*Pi*R*10k)}
U3 U1 0 SINE(0 1 {f} 0 0 0) AC 1
.step param f list 1k 10k 100k
.param R 1k
.tran 1m
.lib LTC.lib
.backanno
.end
```

LTspice makes this


Getting Started

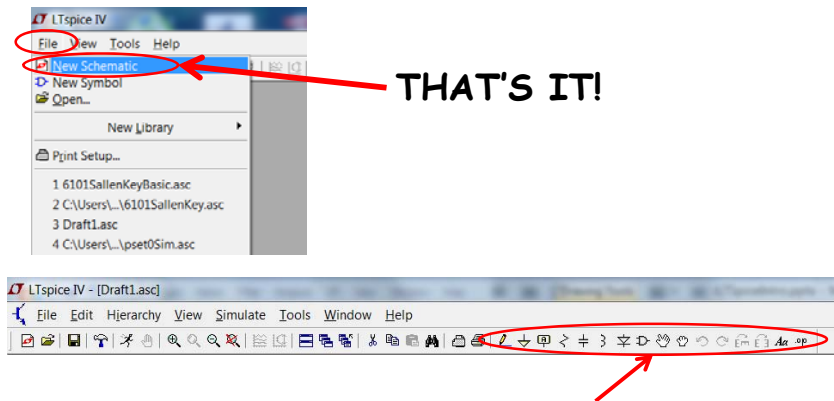

Component to Menu Item Matchup

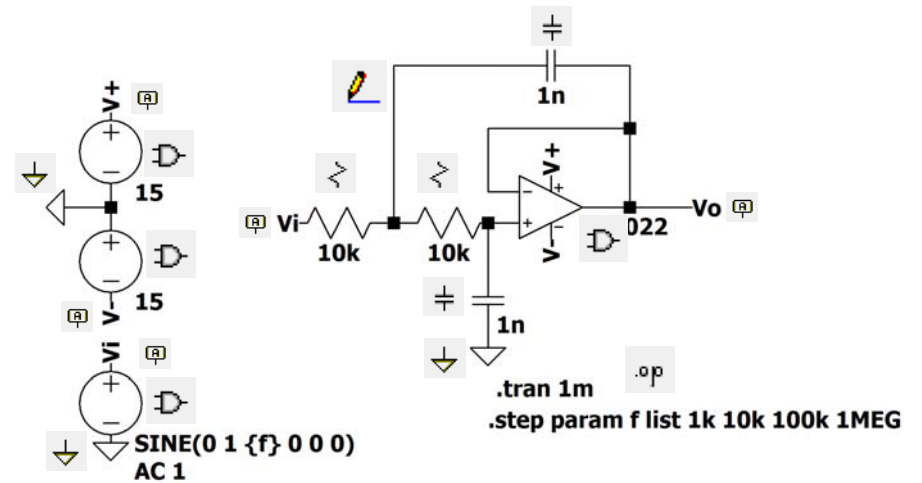


Net Labels

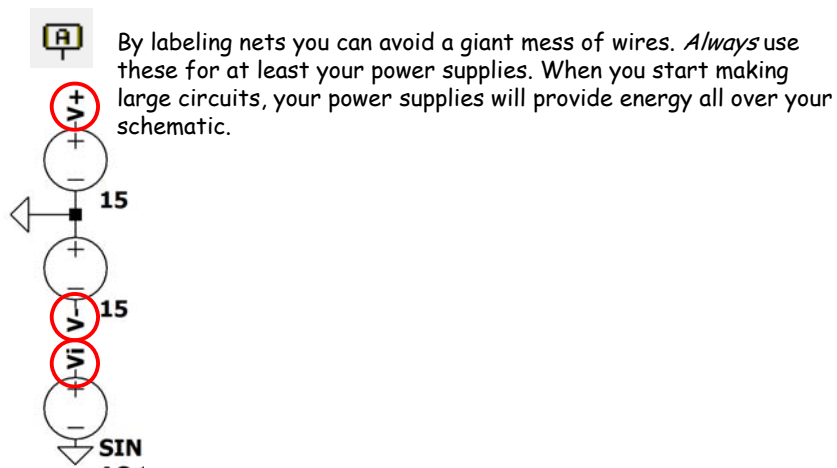


Adding Other Components

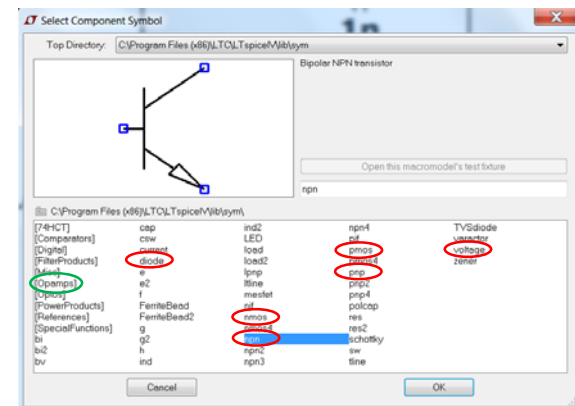Devices besides basic resistors, capacitors, and inductors are found from this button



Op-Amps

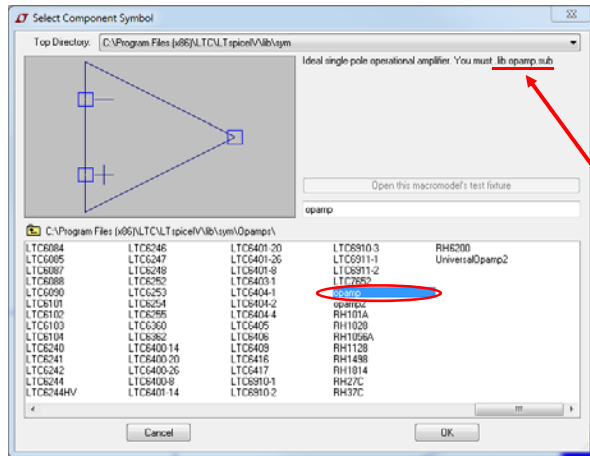There are no "ideal" op-amps in reality. BUT, there are in LTspice.




PAY CLOSE ATTENTION TO THE TEXT

You must literally include `.lib opamp.sub` in your netlist or schematic as a SPICE directive.

Op-Amps

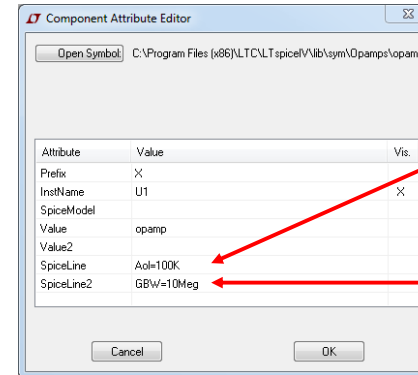Though listed as "ideal" there are still 2 parameters you can tweak.




Open Loop Gain: As this number approaches infinity, the Op Amp becomes more "ideal". Look at some Op Amp data sheets to see some real open loop gains.

Gain Bandwidth: As this number approaches infinity, the Op Amp becomes more "ideal". To check if this is high enough, multiply your desired Closed Loop Gain by your highest desired output frequency.


Op-Amps

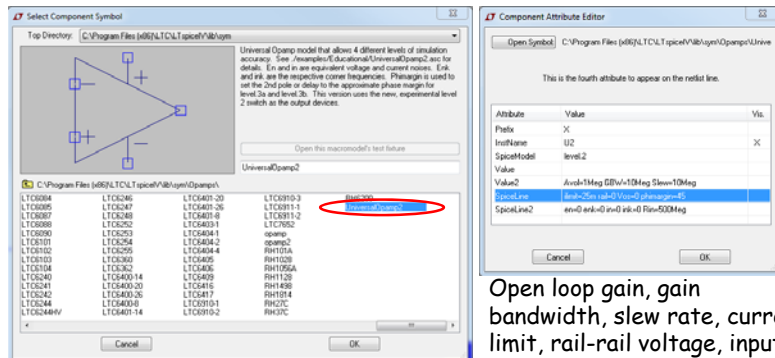To more accurately model a real Op Amp not available in LTspice, UniversalOpamp2 has many tweakable parameters.




Open loop gain, gain bandwidth, slew rate, current limit, rail-rail voltage, input voltage offset, phase margin, Rin, etc.

Editing Components

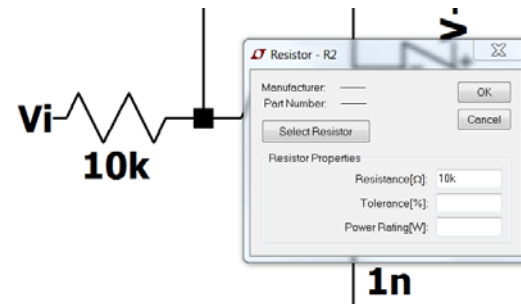

Just right click the component

Editing Components

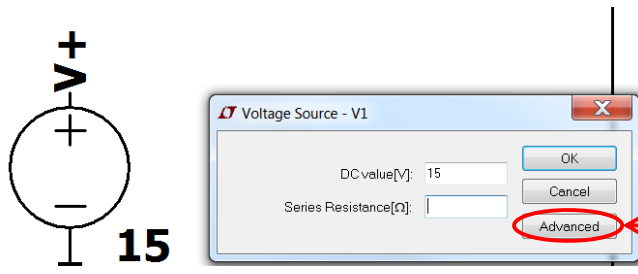

Voltage Source - V1

DC value[V]: 15


Series Resistance[Ω]:

OK Cancel **Advanced**

But what about this?

This is the basic voltage source menu. Use this for DC sources such as power supplies or bias voltages.

Editing Components

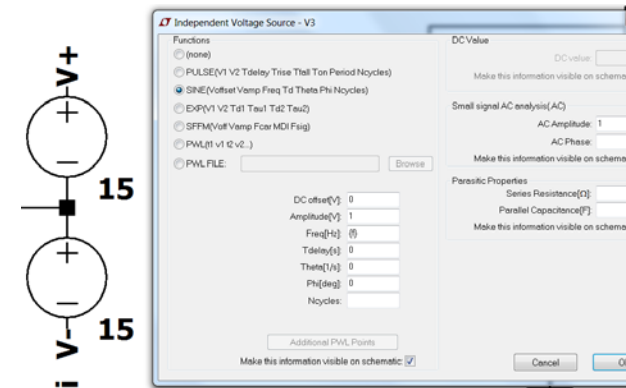

Independent Voltage Source - V3

Functions:

- (none)
- PULSE(V1 V2 Tdelay Trise Tfall Ton Period Ncycles)
- SINE(Voffset Vamp Freq Td Theta Phi Ncycles)**
- EXP(V1 V2 Td1 Tau1 Td2 Tau2)
- SFFM(Volt Vamp Fcar MDI Fsig)
- PWL(t1 v1 t2 v2...)
- PWL FILE: Browse

DC Value:

DC value: DC value

Make this information visible on schematic: ☒

Small signal AC analysis(AC):

AC Amplitude: 1

AC Phase: AC Phase

Make this information visible on schematic: ☒

Parasitic Properties:

Series Resistance[Ω]:

Parallel Capacitance[F]:

Make this information visible on schematic: ☒

Additional PWL Points:


Make this information visible on schematic: ☒

Cancel OK

Voltage sources can produce many test signals. PWL can be used to construct any signal.

Selecting Device Model

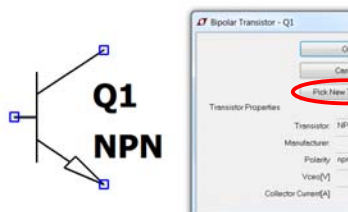There are no "ideal" BJT's, MOSFET's, etc. You can select a model (provided by LTspice), download models, or create your own.



Bipolar Transistor - Q1

Transistor Properties:

Transistor: NPN

Manufacturer:

Polarity: npn

Vbe[V]:

Collector Current[A]:


OK Cancel **Pick New Transistor**

Select Bipolar Transistor

Part No.	Manufacturer	Polarity	Vceo[V]	Ic[mA]	SPICE Model
2N2222	Philips	npn	30.0	800	model 2N2222 NPN(S+1E-14 VAF+100
2N3904	Philips	npn	40.0	200	model 2N3904 NPN(S+1E-14 VAF+100
FZT849	Zetex	npn	30.0	7000	model FZT849 NPN(S+5.8591E-13 NF
ZTX849	Zetex	npn	0.0	7000	model ZTX849 aka FZT849 NPN(Vceo
ZTX1048A	Zetex	npn	17.5	5000	model ZTX1048A NPN(S+13.73E-13 N
2N4124	Fairchild	npn	25.0	200	model 2N4124 NPN(Is+6.73E-13 Egr
2N391A	Fairchild	npn	25.0	500	model 2N391A NPN(Is+12.63E-13 E
7816089	Siemens	npn	75.0	1000	model 7816089 NPN(Is+1E-14 VAF+100

Simulation: Transient

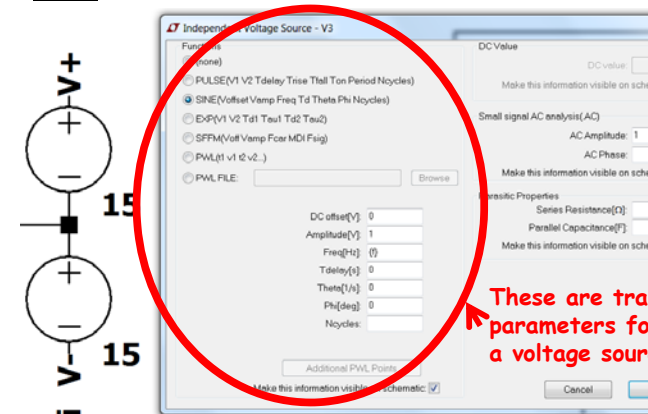Transient simulation gives Voltage and/or Current *vs. time*.



Independent Voltage Source - V3

Functions:

- (none)
- PULSE(V1 V2 Tdelay Trise Tfall Ton Period Ncycles)
- SINE(Voffset Vamp Freq Td Theta Phi Ncycles)**
- EXP(V1 V2 Td1 Tau1 Td2 Tau2)
- SFFM(Volt Vamp Fcar MDI Fsig)
- PWL(t1 v1 t2 v2...)
- PWL FILE: Browse

DC Value:

DC value: DC value

Make this information visible on schematic: ☒

Small signal AC analysis(AC):

AC Amplitude: 1

AC Phase: AC Phase

Make this information visible on schematic: ☒

Parasitic Properties:

Series Resistance[Ω]:

Parallel Capacitance[F]:

Make this information visible on schematic: ☒


Additional PWL Points:

Make this information visible on schematic: ☒

Cancel OK

These are transient parameters for a voltage source

Simulation: Transient

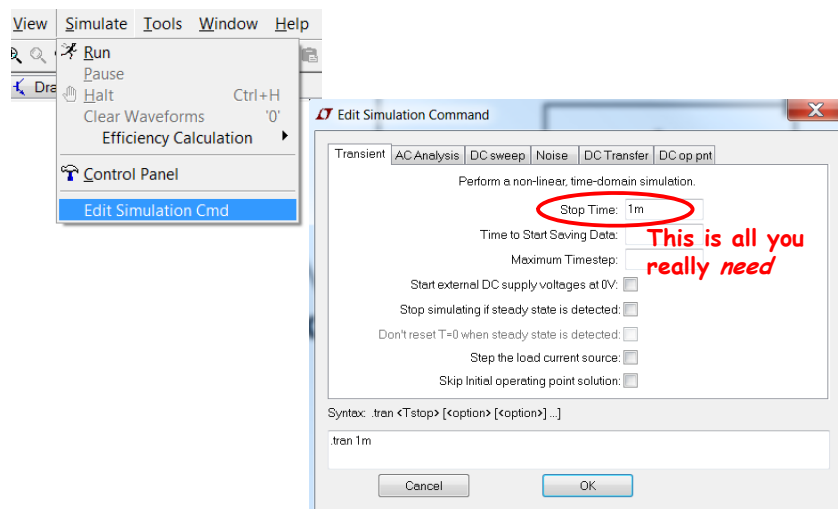


6.101 Spring 2020

Lecture 4

17

Random Tangent: Parameters

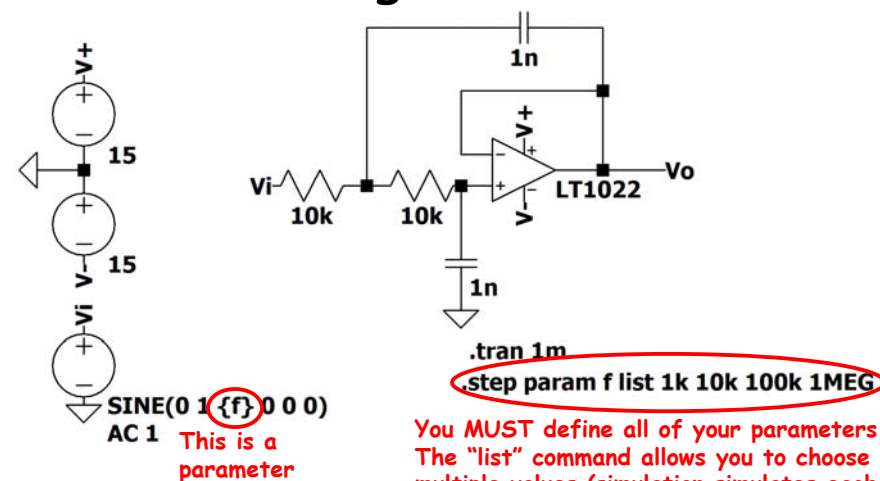


6.101 Spring 2020

Lecture 4

18

What Should My Circuit Do?

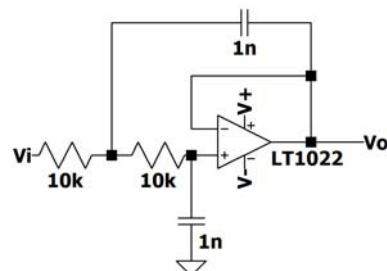- The very first step to any simulation is to know how your circuit *should* behave. Simulation is a verification tool NOT A CIRCUIT SOLVER.
- So how should this circuit behave?




6.101 Spring 2020

Lecture 4

19

Here's Where You Write the Solution

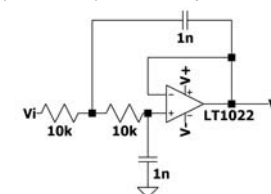


6.101 Spring 2020

Lecture 4

20

Here's Where You Write the Solution

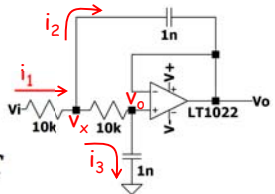

$$i_1 = \frac{v_i - v_x}{R}$$

$$i_2 = (v_x - v_o)sC$$

$$i_3 = \frac{v_x - v_o}{R} = v_o sC$$

$$v_x = v_o(sCR + 1)$$

$$i_1 = i_2 + i_3$$


$$\frac{v_i - v_o(sCR + 1)}{R} = (v_o(sCR + 1) - v_o)sC + v_o sC$$

$$\frac{v_o}{v_i}(s) = \frac{1}{(sCR + 1)^2} \quad \text{A DOUBLE POLE!!}$$


Expected Behavior

- Double pole is at: $f = \frac{1}{2\pi RC} = 16\text{kHz}$
- We expect frequencies up to this point to be large, but frequencies above to quickly drop off due to the -40 dB/decade characteristic of the double pole

Transient Simulation


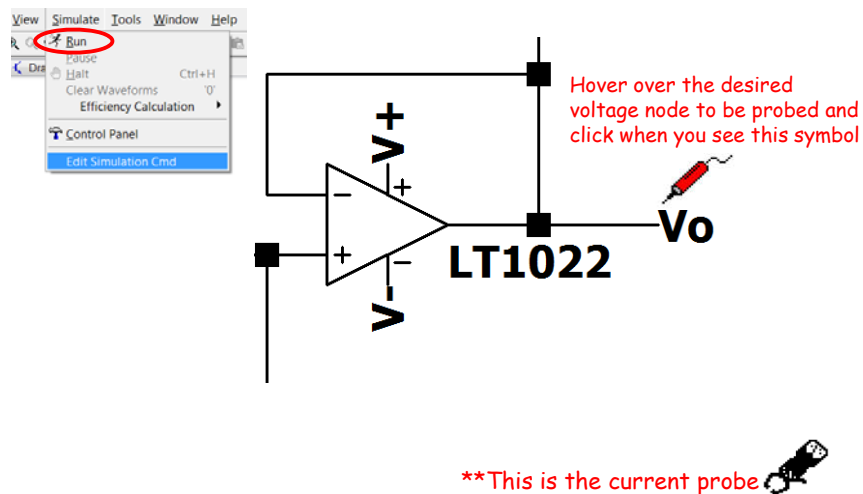


Transient Simulation

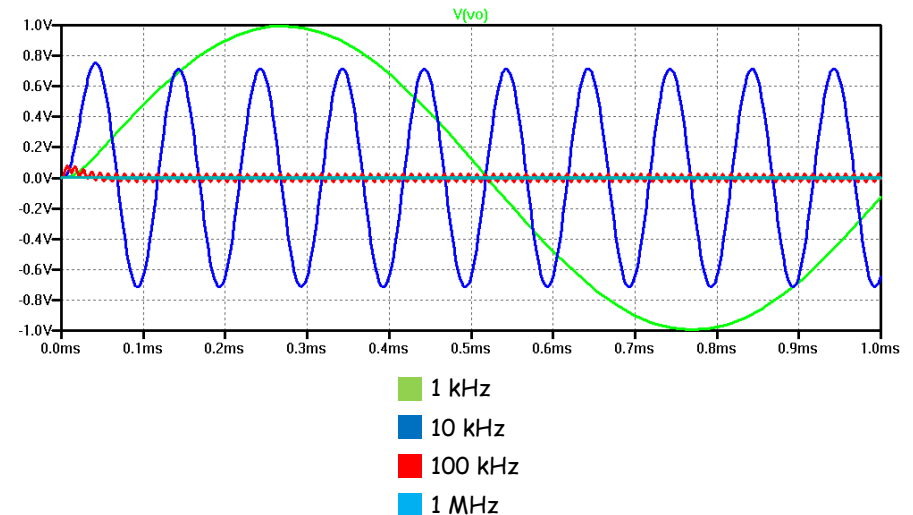


AC Simulation

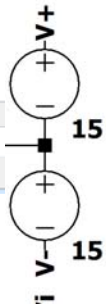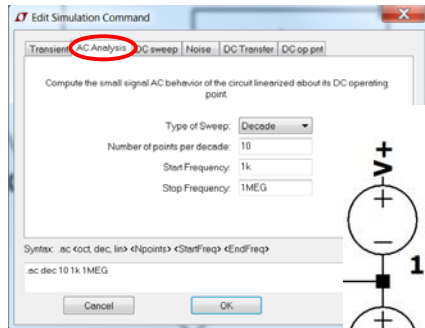AC simulation gives Voltage and/or Current vs. frequency.



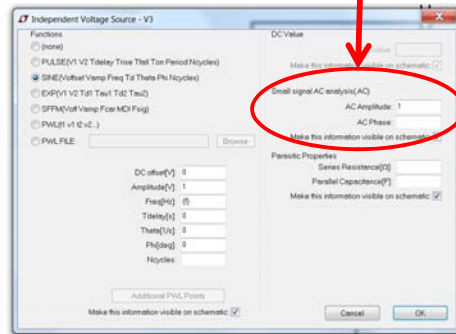This is the AC parameter. Just set the amplitude to 1




6.101 Spring 2020

Lecture 4

25

AC Simulation

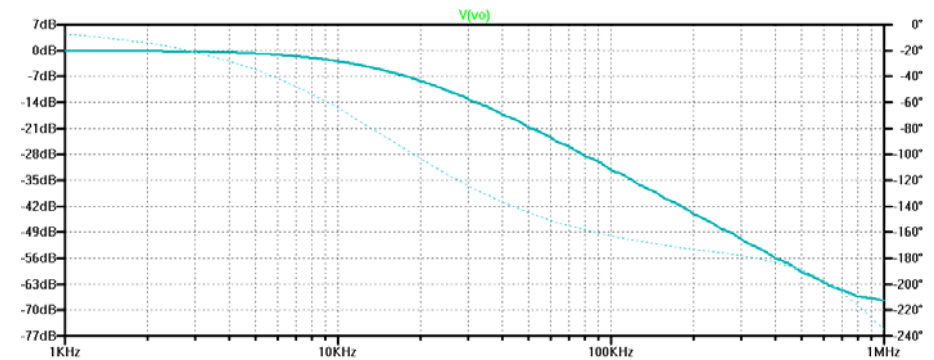


6.101 Spring 2020

Lecture 4

26

Extra Fun: Math in LTspice

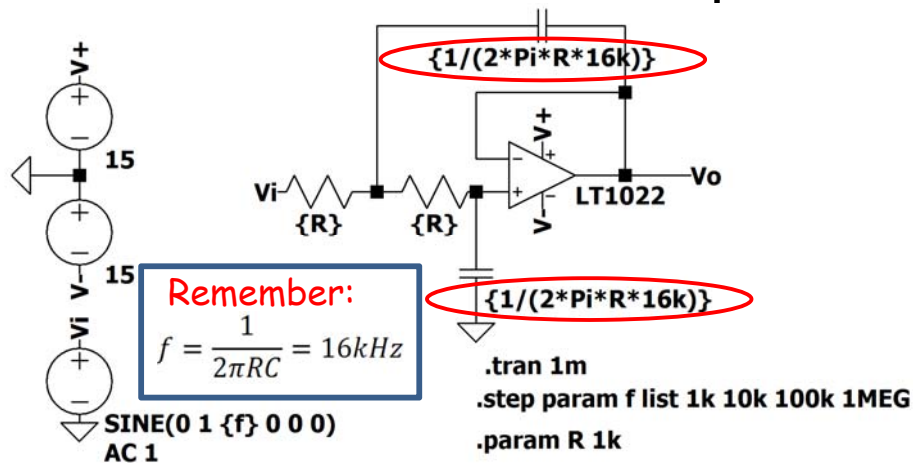


6.101 Spring 2020

Lecture 4

27

Transient Simulation

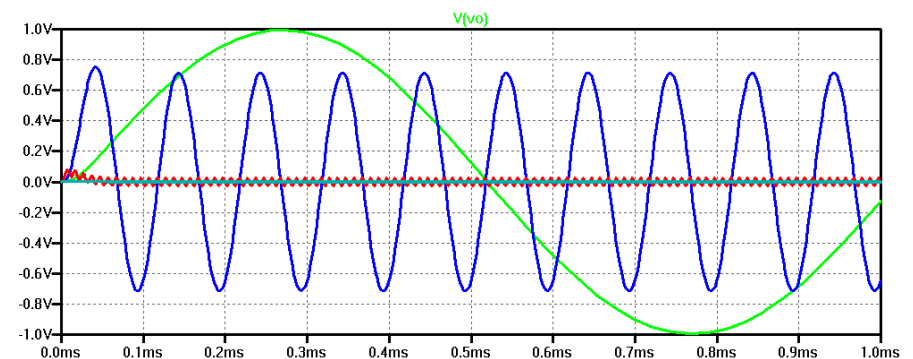


It's the same as before!

6.101 Spring 2020

Lecture 4

28

Even More Fun

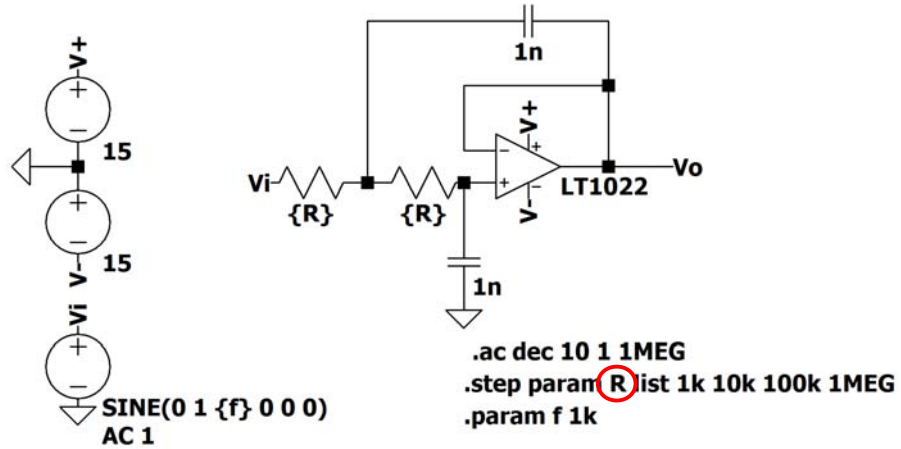


*Note: You can try out some math functions in the simulator window, too! (ex: $V(Vo)/V(Vi)$).

6.101 Spring 2020

Lecture 4

29

AC Simulation

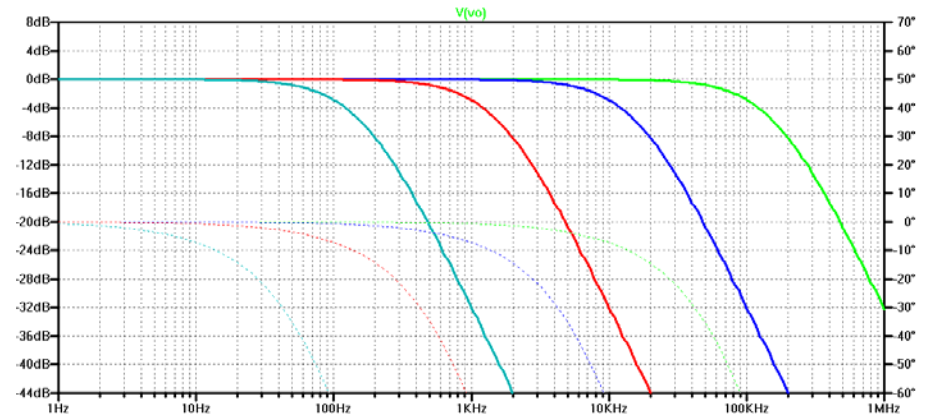


6.101 Spring 2020

Lecture 4

30

Temperature as a Variable

- PTAT current source

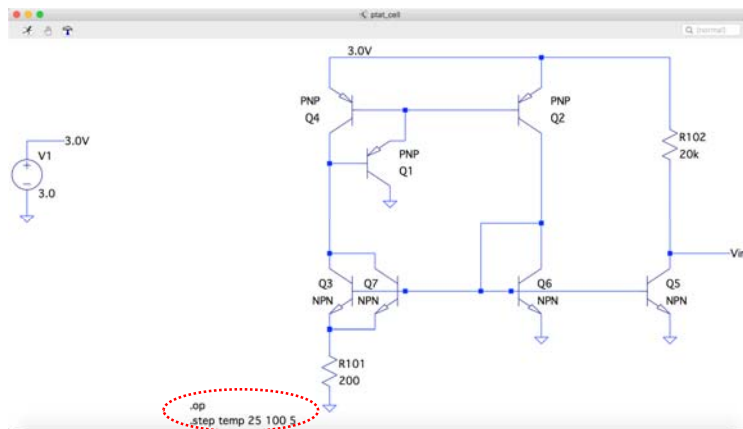


6.101 Spring 2020

Lecture 4

31

Temperature as a Variable

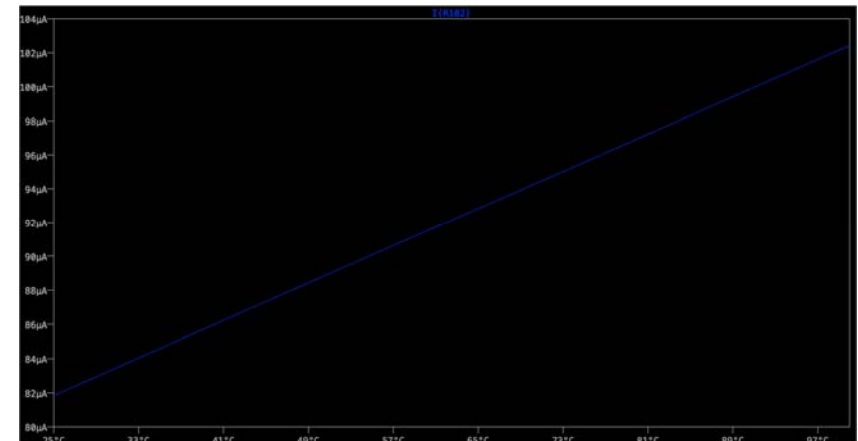


6.101 Spring 2020

Lecture 4

32


Including External Models

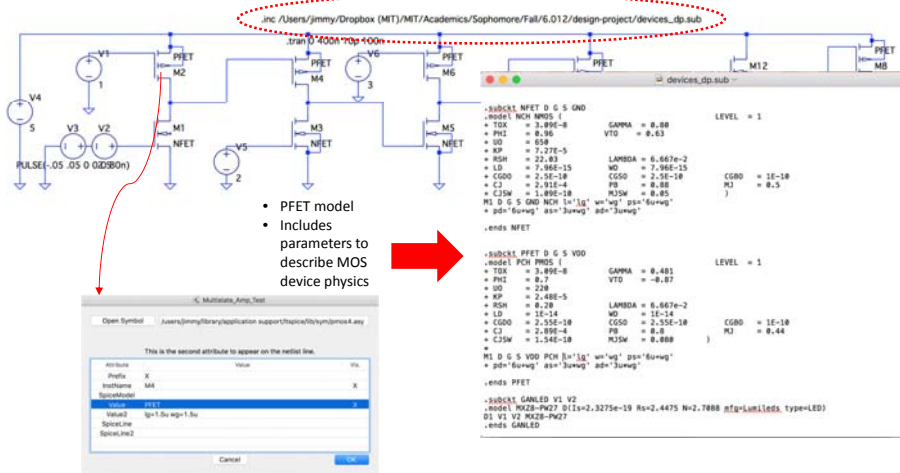

Lecture 4

33


Making Things Pretty

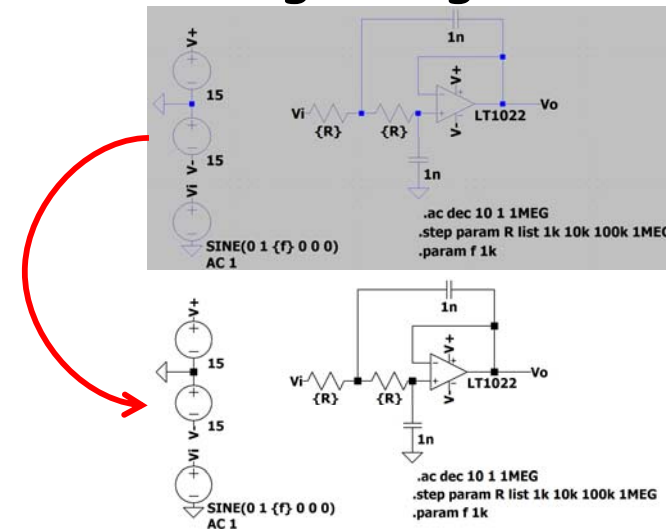

Lecture 4

34

Making Things Pretty

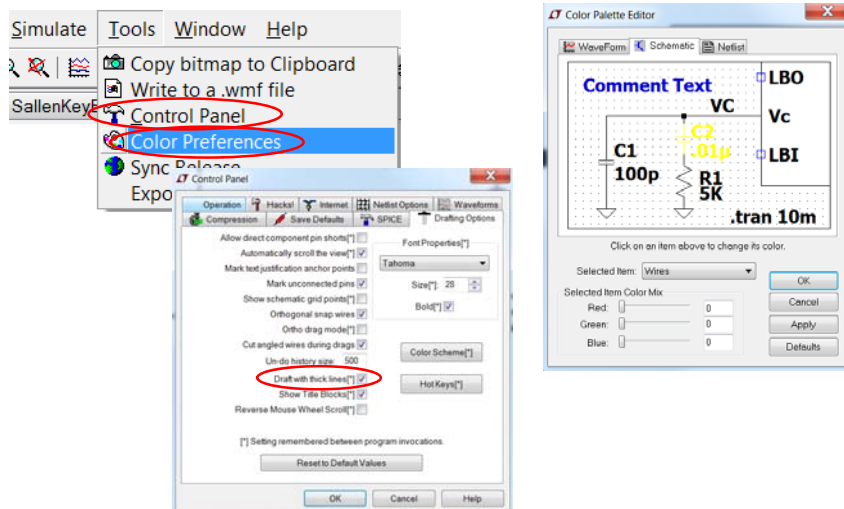

Lecture 4


35

Making Things Pretty

Bob Reay of Linear Technology has provided a nifty tool on his website to give LTspice circuits an even better makeover:

<http://reaylabs.com/tools/SchematicViewer/SchematicViewer.html>

Before:

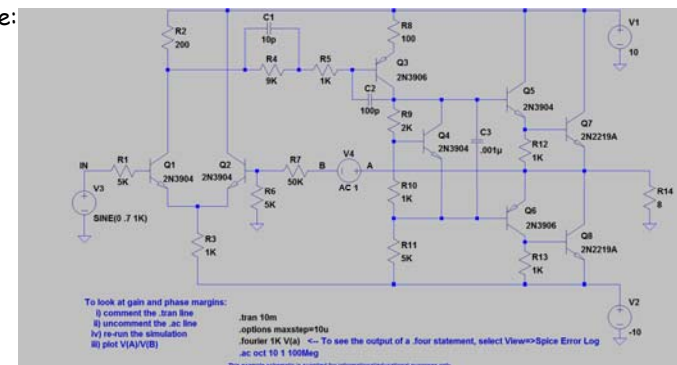

Lecture 4


36

Making Things Pretty

Bob Reay of Linear Technology has provided a nifty tool on his website to give LTspice circuits an even better makeover:

<http://reaylabs.com/tools/SchematicViewer/SchematicViewer.html>

After:

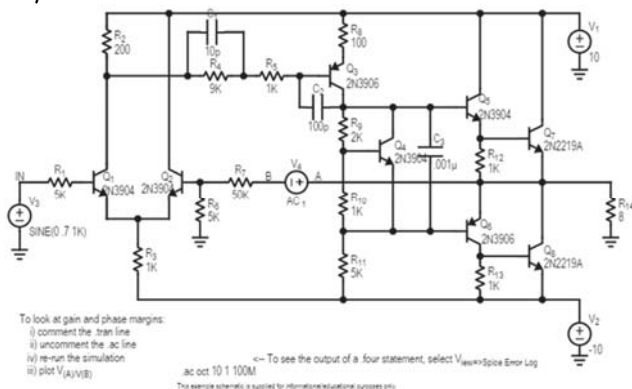

6.101 Spring 2020

Lecture 4

37

LTspice Secrets

Many aspects and functions of LTspice are not documented. You can learn lots of interesting undocumented capabilities of LTspice from:

http://ltwiki.org/?title=Undocumented_LTspice

Of particular interest should be B-sources. These allow you to make devices such as non-linear resistors whose value is determined from a function of voltage, current, if statements, constants, etc. Though you cannot build these, they may be useful to model a part not available in LTspice, or to model a special function in your circuit you have not designed yet.

6.101 Spring 2020

Lecture 4

38

Questions??

6.101 Spring 2020

Lecture 4

39

LTspice HotKeys			
	Schematic	Symbol	Netlist
Modes	ESC – Exit Mode	ESC – Exit Mode	
	F3 – Draw Wire		
	F5 – Delete	F5 – Delete	
	F6 – Duplicate	F6 – Duplicate	
	F7 – Move	F7 – Move	
	F8 – Drag	F8 – Drag	
	F9 – Undo	F9 – Undo	F9 – Undo
	Shift+F9 – Redo	Shift+F9 – Redo	Shift+F9 – Redo
	Ctrl+Z – Zoom Area	Ctrl+Z – Zoom Area	
	Ctrl+B – Zoom Back	Ctrl+B – Zoom Back	
View	Space – Zoom Fit		
	Ctrl+G – Toggle Grid		
	U – Mark Uncon. Pins	Ctrl+W – Attribute Window	
	A – Mark Text Anchors	Ctrl+A – Attribute Editor	
	Alt+Click – Power		
	Ctrl+Click – Attr. Edit		
	Ctrl+H – Halt Simulation		
	R – Resistor	R – Rectangle	
	C – Capacitor	C – Circle	
	L – Inductor	L – Line	
Place	D – Diode	A – Arc	
	G – GND		
	S – Spice Directive		
	T – Text	T – Text	
	F2 – Component		
	F4 – Label Net		
	Ctrl+E – Mirror	Ctrl+E – Mirror	
	Ctrl+R – Rotate	Ctrl+R – Rotate	

Simulator Directives – Dot Commands	
Command	Short Description
.AC	Perform a Small Signal AC Analysis
.BACKANNO	Annotate Subcircuit Pin Names on Port Currents
.DC	Perform a DC Source Sweep Analysis
.END	End of Netlist
.ENDS	End of Subcircuit Definition
.FOUR	Compute a Fourier Component
.FUNC	User Defined Functions
.FERRET	Download a File Given the URL
.GLOBAL	Declare Global Nodes
.IC	Set Initial Conditions
.INCLUDE	Include another File
.LIB	Include a Library
.LOADBIAS	Load a Previously Solved DC Solution
.MEASURE	Evaluate User-Defined Electrical Quantities
.MODEL	Define a SPICE Model
.NET	Compute Network Parameters in a .AC Analysis
.NODESET	Supply Hints for Initial DC Solution
.NOISE	Perform a Noise Analysis
.OP	Find the DC Operating Point
.OPTIONS	Set Simulator Options
.PARAM	User-Defined Parameters
.SAVE	Limit the Quantity of Saved Data
.SAVEBIAS	Save Operating Point to Disk
.STEP	Parameter Sweeps
.SUBCKT	Define a Subcircuit
.TEMP	Temperature Sweeps
.TF	Find the DC Small-Signal Transfer Function
.TRAN	Do a Nonlinear Transient Analysis
.WAVE	Write Selected Nodes to a .WAV file

Suffix	Suffix	Constants
	f	E
T	1e12	Pi
G	1e9	K
Meg	1e6	Q
K	1e3	TRUE
		FALSE

Suffix	Suffix	Constants
	1e-15	E
	1e-12	Pi
	1e-9	K
	1e-6	Q
	1e-3	TRUE
	25.4e-6	FALSE

Command Line Switches	
Flag	Short Description
-ascii	Use ASCII .raw files. (Degrades performance.)
-b	Run in batch mode.
-big or -max	Start as a maximized window
-encrypt	Encrypt a model library
-FastAccess	Convert a binary .raw file to Fast Access Format
-netlist	Convert a schematic to a netlist
-nowine	Prevent use of WINE(Linux) workarounds
-PCBnetlist	Convert a schematic to a PCB netlist
-registry	Store user preferences in the registry
-Run	Start simulating the schematic on open
-SOI	Allow MOSFET's to have up to 7 nodes in subcircuit
-uninstall	Executes one step of the uninstallation process
-wine	Force use of WINE(Linux) workarounds

©2018 Analog Devices, Inc. All rights reserved. Trademarks and registered trademarks are the property of their respective owners. Ahead of What's Possible is a trademark of Analog Devices. LTspice-6/18(E)

analog.com



LTspice

LTSPICE SHORTCUTS ON A MAC

11/5/2013 REV 3

a	DRAW CIRCLE
b	BUS TERMINATION
g	GROUND
l	DRAW LINE
s	ADD SPICE DIRECTIVE (right click for HELP ME EDIT)
t	ADD TEXT COMMENT
w	DRAW BOX

⌘	H	HIDE LTSPICE
⌘	L	SPICE LOG
⌘	N	NEW SCHEMATIC
⌘	O	OPEN
⌘	Q	QUIT LTSPICE
⌘	S	SAVE
⌘	Z	UNDO
⇧⌘	Z	REDO
⌘	M	MINIMIZE
⌘	M	MINIMIZE ALL
⌘	W	CLOSE
⌘	W	CLOSE ALL
⌘	P	PRINT
⇧⌘	P	page seupt

F2	COMPONENT
F3	WIRE
F4	NET NAME
F5	DELETE
F6	DUPLICATE
F7	MOVE (CNTRL-R to rotate, CNTRL-E to mirror)
F8	DRAG (CNTRL-R to rotate, CNTRL-E to mirror)
F9	UNDO
⇧F9	REDO

SPACE BAR	ZOOM TO FIT
2 FINGER PINCH	ZOOM IN
2 FINGER SPREAD	ZOOM OUT

Here are the modifier key symbols you may see in OS X menus:

⌘	COMMAND
⌥	ALT OR OPTION
⇧	SHIFT